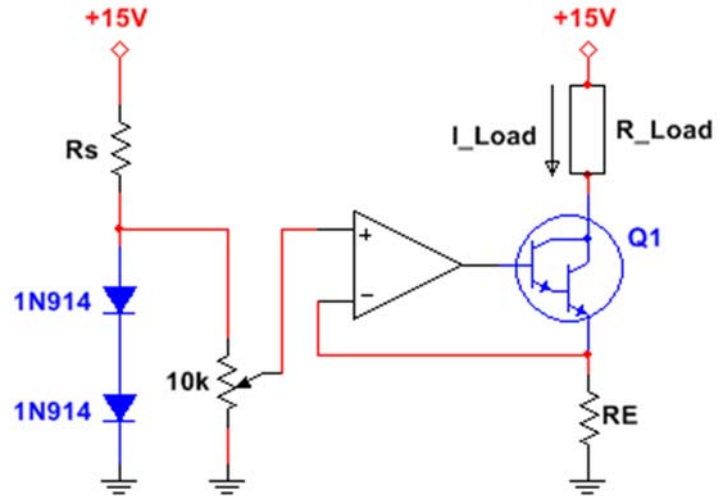


4 problems for 100 pts

Problem #1: Adjustable Current Source (25 pts)

You are asked to design a DC current source that can produce up to 1.2A for a 10 ohm load. Consider the circuit shown to the right, where the load current comes from the Q1 collector. The current is made adjustable by the 10 kohm potentiometer, which samples a portion of the fixed voltage established by the pair of diodes. The design specs are:

- $I_{\text{Load}} = 1.2\text{A}$ (+/- 5% is fine) when the potentiometer is set to 100%.
 - Darlington is either a BC517 or TIP120
 - Available heat sinks are 5, 10, 15, and 20 °C/W.
 - All resistors are standard 5% values with available power ratings of $\frac{1}{4}$, $\frac{1}{2}$, 1, 2, and 5W.
- (a) Perform a “quick” analysis to choose Q1. You must explain why you chose one transistor and not the other one. If Q1 needs a heat sink, you must choose the proper value (assume $T_A = 25^\circ\text{C}$ and $\theta_{\text{CS}} = 0.5^\circ\text{C/W}$).
- (b) **Based on “typical” Q1 and diode parameters**, choose the resistances and power ratings for R_E and R_S .
- (c) Suppose your customer wants a current source to produce 1.2A in a 12 ohm load. Would you recommend using this same circuit you just designed? Explain why or why not.



(extra sheet for work)

Problem #2: Power Amplifier (25 pts)

You are asked to design a single-supply DC power amplifier with a voltage gain of 20 dB. The amplifier must deliver up to 8W into a 9 ohm load. You consider the circuit in the figure to the right:

The design constraints are the following:


- You must choose between the following:
 - TIP31 (power npn)
 - TIP110 (Darlington npn)
- The op amp output current must never exceed 10 mA.

(a) You must choose between $V_{cc} = 9, 12, 15,$ or $18V$. Show all calculations!

(b) Choose the appropriate transistor for Q1, keeping in mind the design constraint on the op amp's output current and **using worst-case transistor parameters**.

(c) Assuming an ambient temperature $T_A = 40^\circ C$ and $\theta_{CS} = 0.5^\circ C/W$, is a heat sink necessary for Q1? If so, you must choose between 6, 12, 18, and $24^\circ C/W$. Show all work!

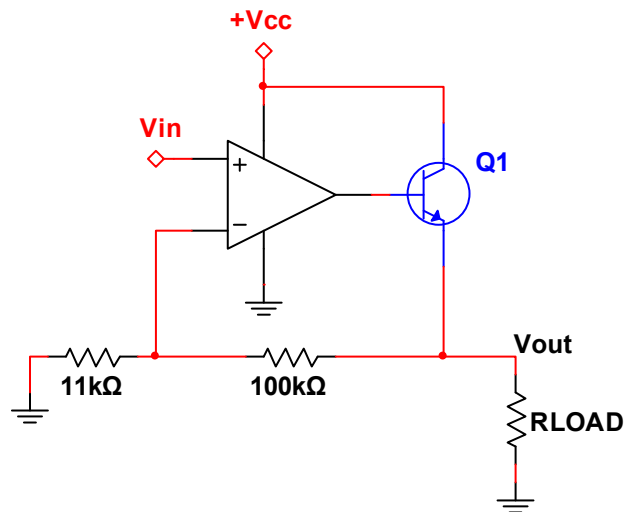
(d) Based on your chosen heat sink, what is the highest ambient temperature T_A that is safe for Q1?



(extra sheet for work)

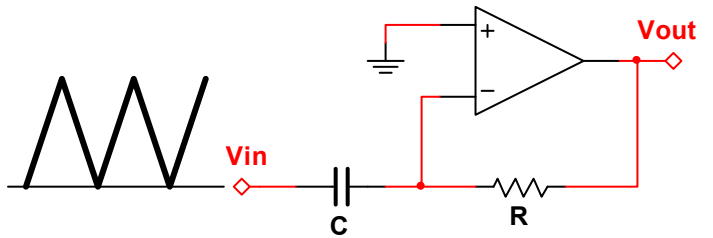Problem #3: Differentiator (25 pts)

A differentiator has many applications, such as being part of a PID control loop. The circuit to the right uses an LM324 op amp. The input signal is a 200 mV_{PP} ramp waveform at 10 kHz.



(a) Use the Golden Rules to show that

$$V_{OUT} = -RC \frac{dV_{IN}}{dt}. \text{ Show all work!}$$

(b) Let $R = 2.2 \text{ Mohm}$ and $C = 470 \text{ pF}$. Assuming $T_A = 25 \text{ }^\circ\text{C}$, what is the worst-case DC output voltage error?

Hint: For DC analysis, what does the capacitor look like (open or short)?

(c) Keeping in mind the op amp's slew rate limitations, sketch the waveforms for V_{IN} and V_{OUT} over a 300 us time interval. Label important features!

(extra sheet for work)


Problem #4: Push-Pull Current Booster (25 pts)

Design an audio power amplifier to drive 125 mW into an 8 ohm load.

The design constraints are the following:

- Use an LF356 op amp.
- Q1 is a 2N4401, Q2 is a 2N4403.
- Assume the diodes have $V_F = 0.62\text{V}$ at 1 mA.
- V_{CC} is either 3, 5, 9, 12, or 15V.
- All resistors are 5% standard values.

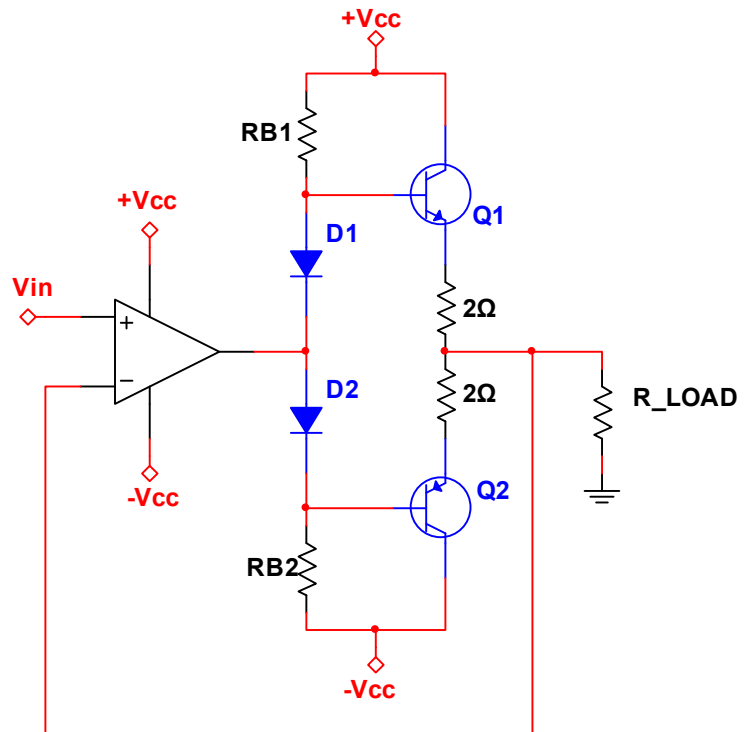- (a) Perform a “quick” analysis to choose V_{CC} . Show all calculations!
- (b) Choose R_{B1} and R_{B2} based on worst-case transistor conditions. You can assume Q1 and Q2 have matching properties.
- (c) Show that the op amp can provide the required output voltage and current, **even under worst-case transistor conditions**.



(extra sheet for work)

(extra sheet for work)