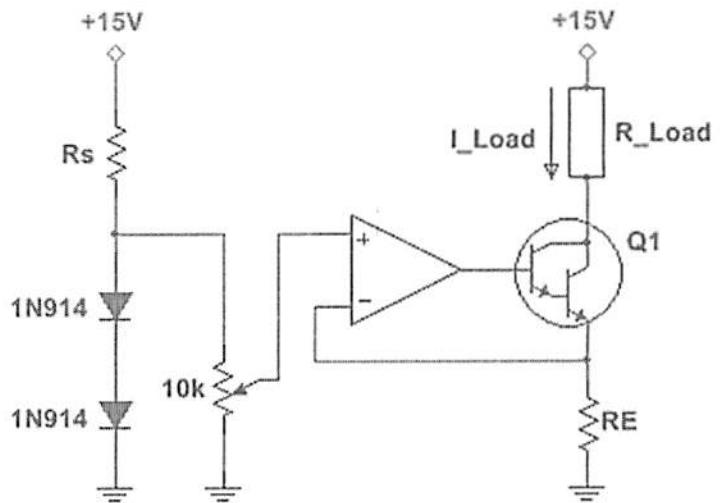


4 problems for 100 pts

Problem #1: Adjustable Current Source (25 pts)

You are asked to design a DC current source that can produce up to 1.2A for a 10 ohm load. Consider the circuit shown to the right, where the load current comes from the Q1 collector. The current is made adjustable by the 10 kohm potentiometer, which samples a portion of the fixed voltage established by the pair of diodes. The design specs are:



- $I_{Load} = 1.2A$ (+/- 5% is fine) when the potentiometer is set to 100%.
- Darlington is either a BC517 or TIP120
- Available heat sinks are 5, 10, 15, and 20 °C/W.
- All resistors are standard 5% values with available power ratings of 1/4, 1/2, 1, 2, and 5W.

- Perform a "quick" analysis to choose Q1. You must explain why you chose one transistor and not the other one. If Q1 needs a heat sink, you must choose the proper value (assume $T_A = 25^\circ C$ and $\theta_{CS} = 0.5^\circ C/W$).
- Based on "typical" Q1 and diode parameters, choose the resistances and power ratings for R_E and R_S .
- Suppose your customer wants a current source to produce 1.2A in a 12 ohm load. Would you recommend using this same circuit you just designed? Explain why or why not.

$\text{Max } I_L = 1.2A \xrightarrow{\times 2} 2.4A \text{ rating}$
 $P = \frac{1.2A}{2501} (1.4) + \frac{2500}{2501} (1.2A)(V_C - V_E) = 1.92W \xrightarrow{\times 2 \text{ Rating}} 3.84W$
 $15 - 1.2A \times 10\Omega = 3V$

	Max I_c	Max P (no Hs)	Max P (w/ Hs)
BC517	1.2A X		
TIP120	5A ✓	2W X	65W ✓

Choose TIP120 + Heat Sink

$$T_J = 25^\circ C + (1.92W)(1.92^\circ C/W + 0.5^\circ C/W + \theta_{SA}) < 85^\circ C$$



$$\Rightarrow \theta_{SA} < 28.8^\circ C/W$$

↳ Choose 20°C/W

(extra sheet for work)

(b) want ~1mA in diodes

+10

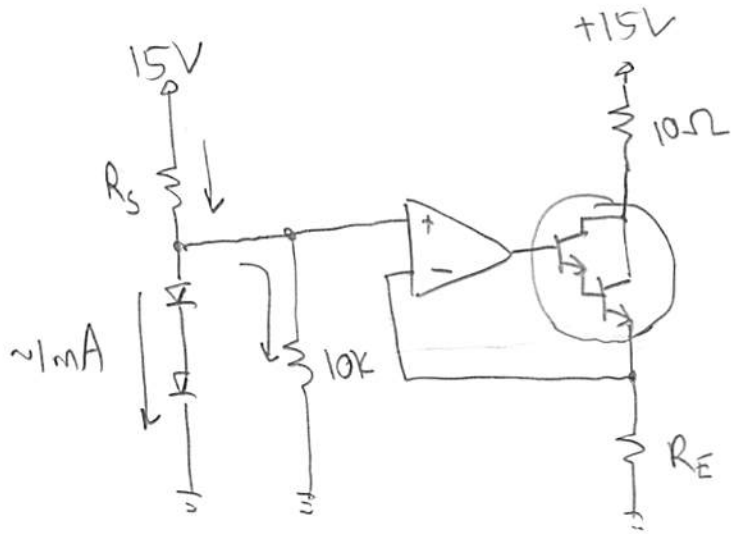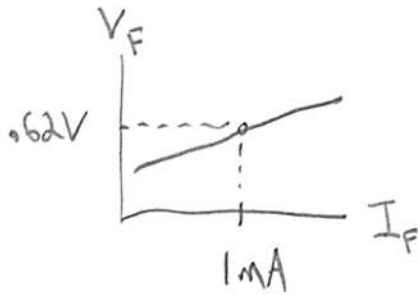


$$\frac{15 - \overbrace{2 \times 0.62}^{1.24V}}{R_S} \sim 1mA + \frac{2 \times 0.62V}{10K} \Rightarrow R_S \approx 12.24K \quad \text{Choose } R_S = 12K$$

$$\frac{(15 - 1.24)^2}{12K} = 15.8mW \xrightarrow{\times 2} 31.6mW$$

$\frac{1}{4}W$ rating

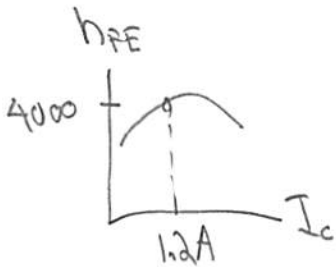want $I_c = \alpha I_E = \frac{4000}{4001} \times \frac{1.24V}{R_E} \sim 1.2A$



$$R_E = 1.03\Omega \Rightarrow \text{Choose } R_E = 1.0\Omega$$

$$\frac{(1.24V)^2}{1\Omega} = 1.54W \xrightarrow{\times 2} 3.08W$$

5W rating

(c) $V_{Load} = 1.2A \times 12\Omega = 14.4V$


+5

Q_1 's $V_{CE} = \underbrace{(15 - 14.4)}_{0.6V} - (1.24) < 0 \nabla$, Q_1 not in active mode ;)

NO, do not recommend same circuit.

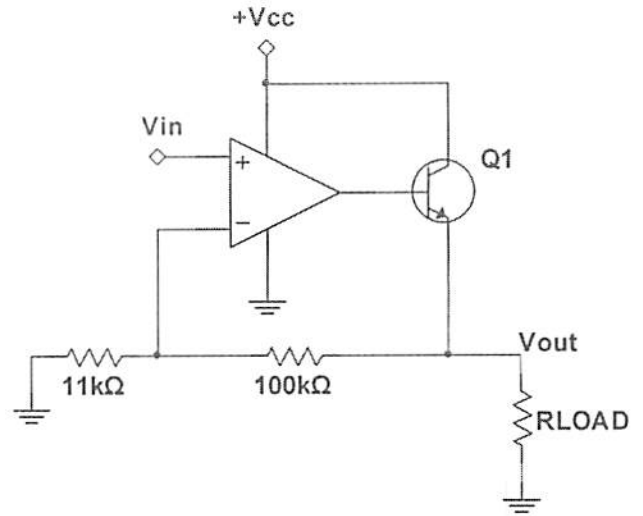Problem #2: Power Amplifier (25 pts)

You are asked to design a single-supply DC power amplifier with a voltage gain of 20 dB. The amplifier must deliver up to 8W into a 9 ohm load. You consider the circuit in the figure to the right:



The design constraints are the following:

- You must choose between the following:
 - TIP31 (power npn)
 - TIP110 (Darlington npn)
 - The op amp output current must never exceed 10 mA.
- (a) You must choose between $V_{cc} = 9, 12, 15,$ or $18V$. Show all calculations!
- (b) Choose the appropriate transistor for Q1, keeping in mind the design constraint on the op amp's output current and **using worst-case transistor parameters**.
- (c) Assuming an ambient temperature $T_A = 40^\circ C$ and $\theta_{CS} = 0.5^\circ C/W$, is a heat sink necessary for Q1? If so, you must choose between 6, 12, 18, and $24^\circ C/W$. Show all work!
- (d) Based on your chosen heat sink, what is the highest ambient temperature T_A that is safe for Q1?

$$\textcircled{a} \text{ want } V_{cc} > V_{Load} + V_{CE,sat} + 2 \quad \text{Head room} \Rightarrow V_{cc} > 8.49 + 2 = 10.49V$$

$$8W = \frac{V_L^2}{9\Omega} \quad \text{OV} \quad \text{Choose } \boxed{V_{cc} = 12V}$$

$$\text{Max } V_L = 8.49V$$

$$\textcircled{b} \text{ Max } I_L = \frac{8.49V}{9\Omega} = 0.94A \xrightarrow{\times 2} \underline{1.89A \text{ rating}}$$

	<u>Max I_c</u>	<u>Max P</u>	\leftarrow w/HS		
TIP31	3A ✓	40W ✓		TIP31:	$P \sim \frac{0.94A}{101} (0.7) + 0.99(0.94)(12 - 8.49)$
TIP110	2A ✓	50W ✓			$= 3.27W \xrightarrow{\times 2} 6.55W \text{ rating}$
				TIP110:	$P \sim \frac{0.94A}{2501} (1.4) + \frac{2500}{2501} (0.94)(12 - 8.49)$
					$= 3.3W \xrightarrow{\times 2} 6.6W \text{ rating}$

Both OK, but what about BASE current?

(extra sheet for work)

$$\min \beta @ I_c = 1A$$

TIP31

25

→

$$I_b = \frac{.94A}{26} = 36mA \quad X$$

TIP110

1000

→

$$I_b = \frac{.94A}{1001} = \underline{\underline{.94mA}} \quad \checkmark$$

+7

choose TIP110

© We already know Q_1 needs a HS for $T_A = 25^\circ C$
(6.6W rating > 2W without HS rating)

$$P = \frac{.94A}{1001} (2.8V) + \frac{1000}{1001} (.94A) (12 - 8.49) = 3.3W$$

$$T_J = 40^\circ C + 3.3W \times (2.5^\circ C/W + 0.5^\circ C/W + \theta_{SA}) < 85^\circ C$$

+7

$$\theta_{SA} < 10.6^\circ C/W$$

choose 6^\circ C/W


© $T_{A,max} + 3.3 (2.5 + .5 + 6) < 85$

+4

$$T_A < 55.3^\circ C$$

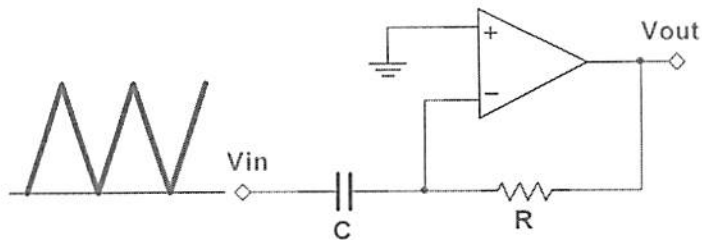Problem #3: Differentiator (25 pts)

A differentiator has many applications, such as being part of a PID control loop. The circuit to the right uses an LM324 op amp. The input signal is a 200 mV_{PP} ramp waveform at 10 kHz.



(a) Use the Golden Rules to show that

$$V_{OUT} = -RC \frac{dV_{IN}}{dt}. \text{ Show all work!}$$

(b) Let $R = 2.2 \text{ Mohm}$ and $C = 470 \text{ pF}$. Assuming $T_A = 25^\circ\text{C}$, what is the worst-case DC output voltage error?


Hint: For DC analysis, what does the capacitor look like (open or short)?

(c) Keeping in mind the op amp's slew rate limitations, sketch the waveforms for V_{IN} and V_{OUT} over a 300 μs time interval. Label important features!

(a)

$$i = C \frac{d}{dt}(V_{IN} - 0) = \frac{0 - V_{OUT}}{R}$$

$$V_{OUT} = -RC \frac{dV_{IN}}{dt}$$

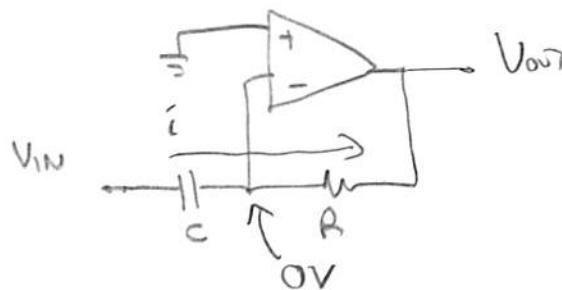

(b)

$$T_A = 25^\circ\text{C}: I_{IN(BIAS)} = 150 \text{ nA (max)}$$

$$R_{TH(+)} = 0$$

(+9)

$$I_{IN(OS)} = 30 \text{ nA (max)}$$


$$R_{TH(-)} = 2.2 \text{ M}$$

$$V_{IN(OS)} = 7 \text{ mV (max)}$$

$$\text{Gain} = 1$$

$$\begin{aligned} \Delta V_{OUT} &= (150 \times 10^{-9}) (2.2 \times 10^6) \times 1 \\ &+ (30 \times 10^{-9}) \left(\frac{2.2 \times 10^6 + 0}{2} \right) \times 1 \\ &+ 0.007 \times 1 = 0.33 + 0.33 + 0.007 = \boxed{0.37 \text{ V}} \end{aligned}$$


Buffer
(G=1)

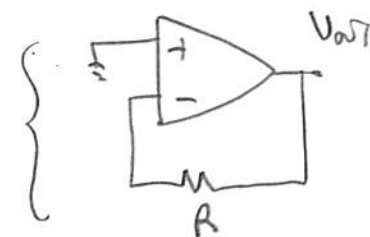

(extra sheet for work)

Ⓒ
+9


10kHz \rightarrow 100 μ s period

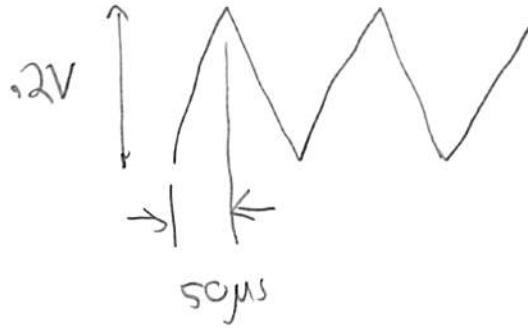

$$\left| \frac{dV_{in}}{dt} \right| = 4 \times 10^3 \frac{V}{s}$$


$$RC = (2.2 \times 10^6) (470 \times 10^{-12}) = 1.03 \times 10^{-3} s$$

$$V_{out} = \pm 4.14V \text{ (ideal)}$$

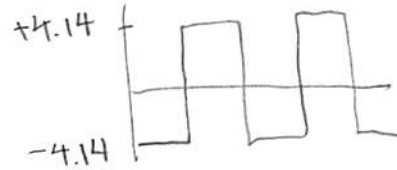


BUT, $SR = 0.4 V/\mu s$
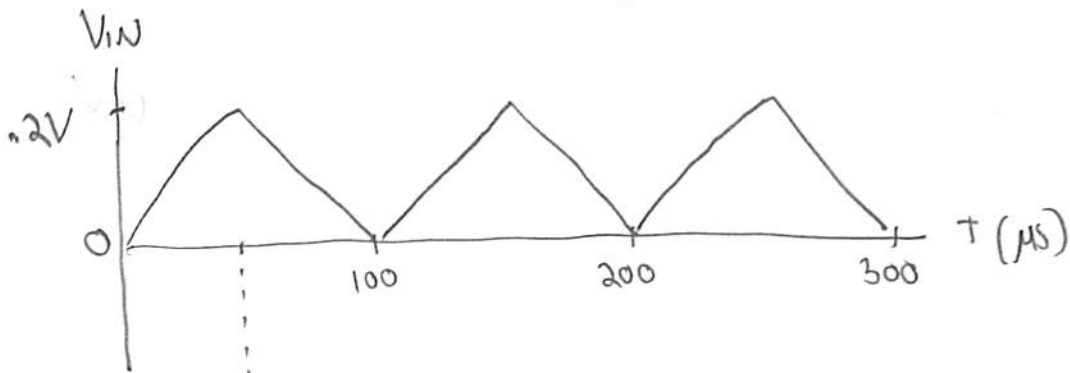
$$T_{SR} = \frac{0.8 \times 2 \times 4.14V}{0.4 V/\mu s} = \underline{\underline{16.6 \mu s}}$$



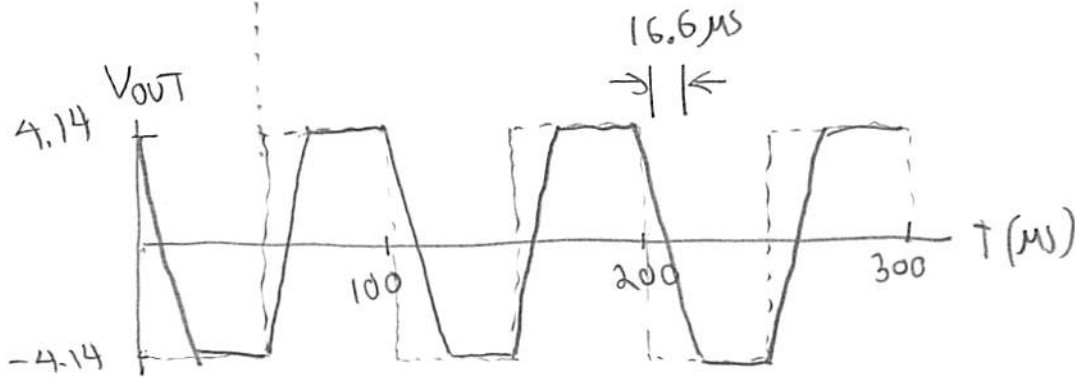Problem did not ask for this.

Does not include worst case ΔV_{out} error




Problem #4: Push-Pull Current Booster (25 pts)

Design an audio power amplifier to drive 125 mW into an 8 ohm load.

The design constraints are the following:

- Use an LF356 op amp.
- Q1 is a 2N4401, Q2 is a 2N4403.
- Assume the diodes have $V_F = 0.62V$ at 1 mA.
- V_{CC} is either 3, 5, 9, 12, or 15V.
- All resistors are 5% standard values.

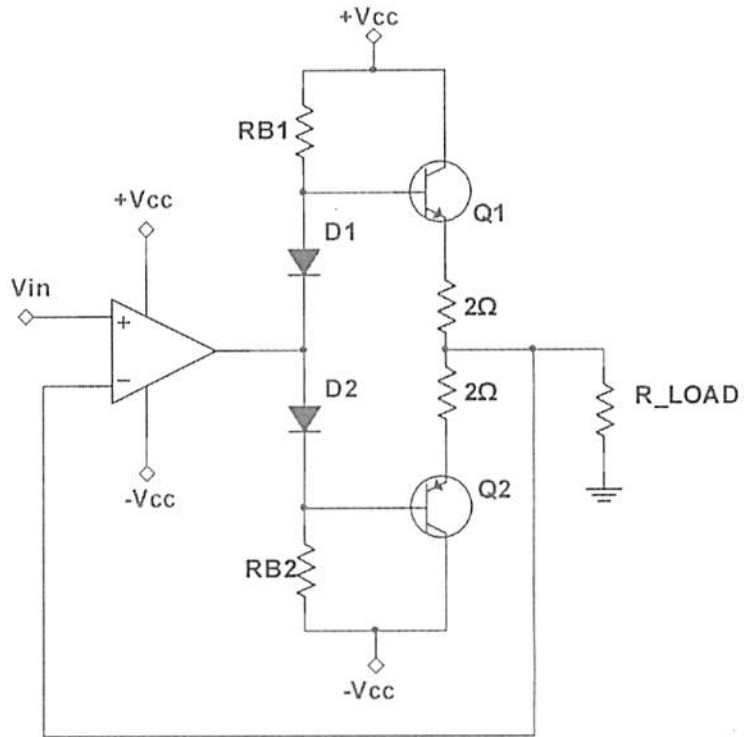- Perform a "quick" analysis to choose V_{CC} . Show all calculations!
- Choose R_{B1} and R_{B2} based on worst-case transistor conditions. You can assume Q1 and Q2 have matching properties.
- Show that the op amp can provide the required output voltage and current, **even under worst-case transistor conditions.**



$$\frac{V_{max}^2}{2 \times 8\Omega} = 0.125W \rightarrow V_{max} = \sqrt{0.125 \times 16} = 1.41V$$

$$I_{max} = 0.177A$$

want $V_{CC} > 1.41 + (0.177A)(2\Omega) + 0 + 2 = 3.76V$

Choose $V_{CC} = 5V$


Head room

$$\text{Max } V_B = 1.764 + \text{max } V_{BE}$$

$$= 2.714V$$

$$0.95V @ 150mA$$

 (close enough)

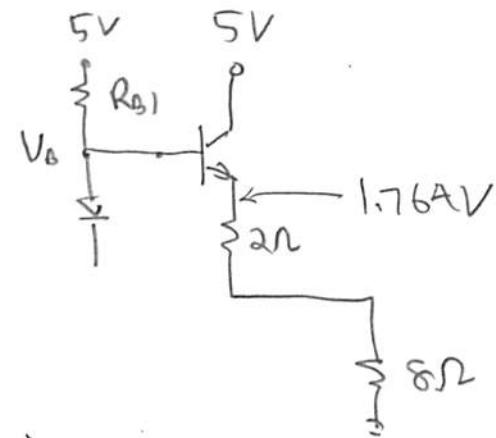

want $\frac{5 - 2.714}{R_{B1}} - \frac{0.177A}{100} \approx 1mA$


(extra sheet for work)

Choose $R_{31} = 820\Omega = R_{32}$

(c)

$$R_{in} = 820 // 820 // (10071)(r_o' + 278)$$

$$\frac{.026V}{.177A} = .15\Omega$$

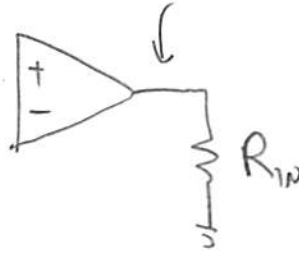

$$\begin{aligned} \text{Max } V_o &= 2.714 - .62 \\ &= \underline{\underline{2.094V}} \end{aligned}$$


$$= 292.9\Omega$$

$$\rightarrow \text{max } i_o = \frac{2.094V}{292.9\Omega} = \underline{\underline{7.15mA}}$$

$$\text{op amp head room: } 5 - 2.094 = \underline{\underline{2.91V}}$$

$$V_{cc} = 15V : \text{max } V_o = 15 - 2.91 = \underline{\underline{12.1V_p}} \leftarrow \begin{matrix} 24V_{pp} \end{matrix}$$

Data sheet:

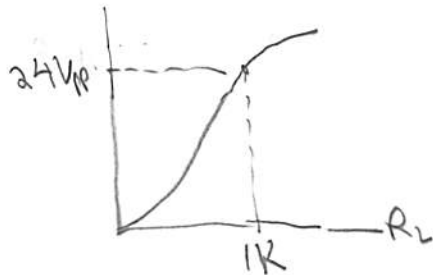

$$\text{max } i_o = \frac{12V_p}{1k} = \underline{\underline{12mA}} > 7.15mA \checkmark$$

(+8)

YES, op amp is good! 😊