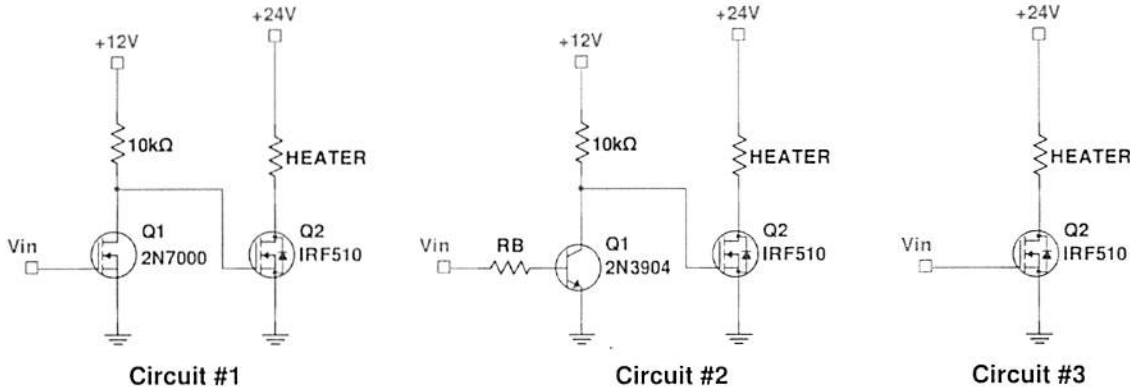


4 problems for 100 pts

Problem #1: Transistor Switch (25 pts)

You are asked to design a circuit to control a heater with a microcontroller unit (MCU). The heater is rated at 24V @ 60W while the MCU outputs 3.3V logic. You decide to drive the heater with an IRF510 power MOSFET, but you are wondering how exactly to hook up the MCU.



- (a) Explain why Circuit #2 is the best choice and why Circuits #1 and #3 are not good choices. Use the appropriate data sheet parameters, particularly worst-case transistor parameters.
- (b) For Circuit #2, compute the appropriate 5% standard resistor for RB assuming typical Q1 parameters.
- (c) Suppose $T_A = 40\text{ }^\circ\text{C}$ and the available heat sinks are $\theta_{SA} = 4, 8, 12, 16, 18, \text{ and } 24\text{ }^\circ\text{C/W}$. You want your circuit to be capable of driving the heater with any duty cycle (e.g. 0 to 100%). Select the appropriate heat sink assuming worst-case Q2 parameters. Show all work!

Q1
 (a) Circuit #1: 2N7000 has max $V_{GS,TH} = 3V$ ← Too close to 3.3V logic } May not fully turn on ☹️

Circuit #2: • $V_{in} = 3.3V$ is plenty to drive the Q1 base ✓
 • When $V_{in} = 0$, Q1 collector = 12V = Q2 gate
 ↑
 way above max $V_{GS,TH} = 4V$ } Fully turns on ☺️
 • When $V_{in} = 3.3V$, Q1 collector < 0.1V = Q2 gate
 } Q2 fully turns OFF ☺️

(+3) Circuit #3: $V_{in} = 3.3V$ is below Q2's max $V_{GS,TH} = 4V$ ← Q2 cannot fully turn ON ☹️

(extra sheet for work)

Q1: $I_c \sim \frac{12-0V}{10K} = 1.2mA$ $V_{CE,sat} \sim .05V @ 1.2mA$
 $I_c \sim \frac{12-.05}{10K} = \underline{\underline{1.2mA}}$

2N3904: $V_{BE(sat)} \sim 0.7V @ I_c = 1.2mA$

$$I_B = \frac{3.3 - 0.7}{R_B} \approx \frac{1.2mA}{10} \rightarrow R_B = 21.67K$$

+7

choose $R_B = 22K$

Load: $R_L = \frac{(24V)^2}{60W} = 9.6\Omega$ IAF510: Max $R_{\theta_{jw}} = .54\Omega$

$$I_L = \frac{60W}{24V} = 2.5A$$
$$I_D \sim \frac{24-0}{9.6+.54} = 2.37A$$

+4

$$P = (2.37)^2 (.54\Omega) = \underline{\underline{3.03W}}$$

$$T_J = 40 + (3.03W)(3.5^\circ C/W + .5^\circ C/W + \theta_{SA}) < 85^\circ C$$

$$\theta_{SA} < 10.85^\circ C/W$$

choose $\theta_{SA} = 8^\circ C/W$


+4

Problem #2: Sawtooth Oscillator (25 pts)

You are asked to design a sawtooth oscillator for an LED PWM driver. You decide to use a 555 timer to operate at 20 kHz (+/- 2%). Let $V_{CC} = 6V$. Some comments:

- $f = 3 \cdot I_0 / (C \cdot V_{CC})$
- The available capacitors are 1 nF, 10nF, and 100 nF.
- I_0 is typically between 0.1 to 1 mA.
- **Assume typical parameters for Q1 and both diodes.**

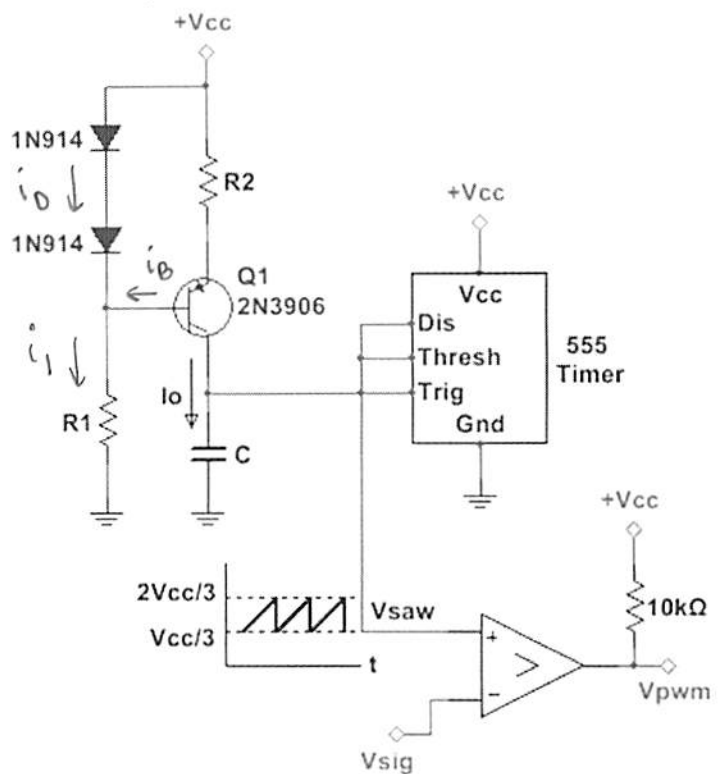- Choose values for your capacitor C and current source value I_0 .
- Choose a standard 5% resistor for R2.
- Choose a standard 5% resistor for R1.
- Confirm your frequency satisfies the design requirement.
- Suppose $V_{sig} = 2.5V$. Compute the duty cycle and sketch V_{pwm} over a 200 μs time interval. Label important features!



$$\textcircled{a} \quad f = 20 \times 10^3 = \frac{3 I_0}{C \cdot 6V} \rightarrow \frac{I_0}{C} = 4 \times 10^4 \frac{V}{s}$$

C	I_0
1 nF	40 μA X
10 nF	4 mA \checkmark
100 nF	4 mA X

+6

Choose $C = 10 \text{ nF}$ and $I_0 = 0.4 \text{ mA}$

$$\textcircled{b} \quad \begin{array}{l} 1N914: V_f \sim 0.62V @ 1mA \\ 2N3906: V_{BE} \sim 0.63V @ 0.4mA \end{array} \quad \left. \begin{array}{l} I_0 = 0.4 \text{ mA} = \alpha \frac{2 \times 0.62 - 0.63}{R_2} \\ \alpha = \frac{\beta}{\beta + 1} = \frac{120}{121} = 0.992 \end{array} \right\} R_2 = 1.51 \text{ k}$$

+5

Choose $R_2 = 1.5 \text{ k}$

$$\textcircled{c} \quad i_D + i_B = i_1$$

$$1 \text{ mA} + \frac{1}{121} (0.4 \text{ mA}) = \frac{6 - 2 \times 0.62}{R_1}$$

$R_1 = 4.74 \text{ k} \rightarrow$ Choose $R_1 = 4.7 \text{ k}$

+5


(extra sheet for work)

$$\textcircled{d} \text{ Actual } I_0 = .992 \frac{2 \times 1.62 - .63}{1.5K} = .403 \text{ mA}$$

$$\textcircled{+3} \quad f = \frac{3 \times (.403 \times 10^{-3})}{(10 \times 10^{-9})(6V)} = 2.02 \times 10^4 \text{ Hz} \leftarrow$$

.75% error ✓

e

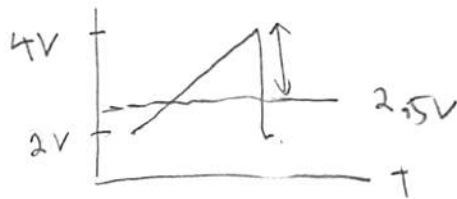


$$\text{Duty Cycle} = \frac{4 - 2.5}{4 - 2} = \boxed{75\%}$$

$\textcircled{+2}$

$$20 \text{ kHz} \rightarrow 1 \text{ cycle} = 50 \mu\text{s}$$

$$4 \text{ cycles} = 200 \mu\text{s}$$

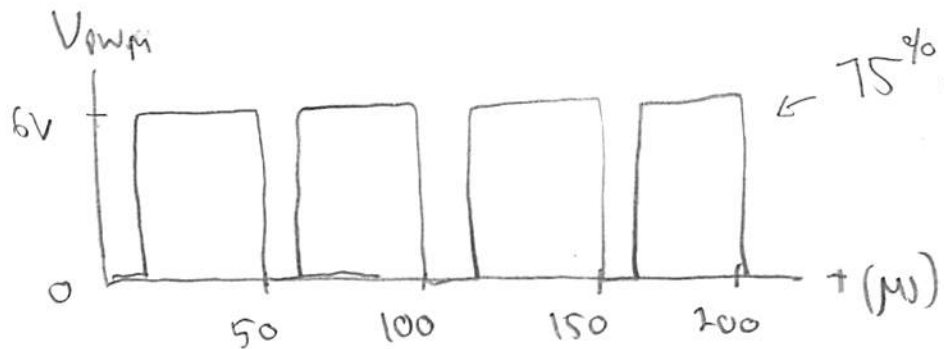


$\textcircled{+4}$

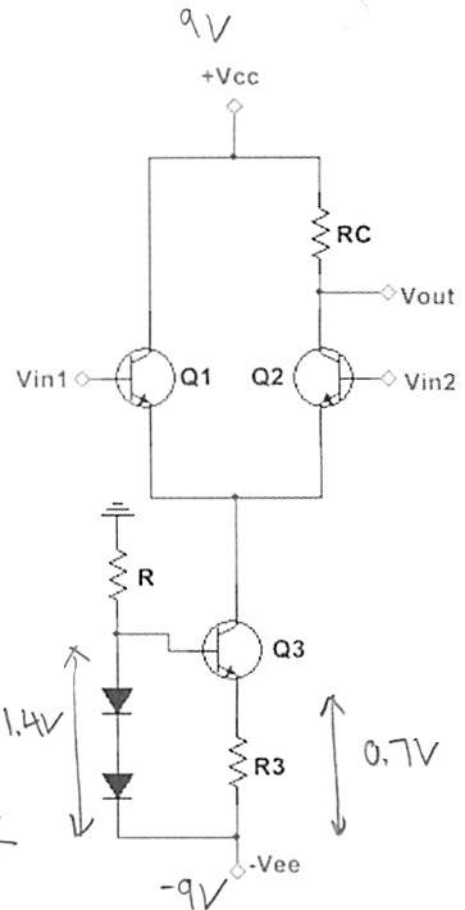Problem #3: Differential Amplifier (25 pts)

Your application requires a differential amplifier with the following specs:

- $A_d = +37.5$ dB (+/- 0.4 dB is OK)
 - $Z_{IN} \geq 75$ kohm
 - Assume quick analysis parameters for all transistors and diodes.
 - $V_{in1} = 3 + V_{sig}/2$ and $V_{in2} = 3 - V_{sig}/2$.
- a) You must choose between $R_3 = 4.3$ kohm or 5.6 kohm. Which is the best choice? **You must also show why the other value is a bad choice.** Show all work!
- b) Choose an appropriate 5% standard value for R . Show all work!
- c) Choose the appropriate 5% standard value for R_C and show that you have satisfied the design requirement. Show all work!
- d) Assuming $A_{CM} \approx 0$, compute the maximum amplitude of V_{sig} that does not result in a clipped V_{out} .



$$\textcircled{a} \quad Z_{IN} = 2(\beta+1)r_e' = 2(\beta+1) \frac{.026}{\frac{1}{2} I_T} \geq 75K$$

$$I_T \leq \underline{0.14 \text{ mA}}$$

current source: $I_T = .99 \frac{.7V}{R_3}$

+6

$R_3 = 4.3K \rightarrow I_T = .16 \text{ mA} \times \text{TOO HIGH}$
 $5.6K \rightarrow I_T = .124 \text{ mA} \checkmark$

$$\textcircled{b} \quad \hat{i}_R = \hat{i}_D + \hat{i}_B$$

$$\frac{0 - (-9 + 1.4)}{R} = 1 \text{ mA} + \frac{.124 \text{ mA}}{100}$$

+5

$R = 7.59K$ choose $R = 7.5K$

$$\textcircled{c} \quad 37.5 \text{ dB} = 20 \log_{10} A_d \rightarrow A_d = 10 \quad = 74.99 = \alpha \frac{R_C}{2r_e'}$$

$$r_e' = \frac{.026}{15 (.124 \text{ mA})} = 1419K \rightarrow R_C = \frac{74.99}{.99} 2(1419K) = 63.5K$$

(extra sheet for work)

Choose $R_C = 62K$

+6

check: $A_d = .99 \frac{62K}{2(.419K)} = 73.25$

$20 \log_{10}(73.25) = 37.3 \text{ dB}$

+2

-0.2 dB error ✓

d) $V_{out} = V_{CQ} + \Delta V_{out}$
 $A_d \Delta V + A_{cm} V_{cm} \approx 0$

$V_{CQ} = 9 - .99 \frac{.124 \text{ mA}}{2} (62K) = \underline{5.19V}$


$V_E \sim 3 - 0.7 = \underline{2.3V}$

★ Don't want to saturate Q_2 !

$5.19 - |\Delta V_{out}| > 2.3V$

$|\Delta V_{out}| < 2.89V$

$\Delta V_{in} = (3 + \frac{V_{sig}}{2}) - (3 - \frac{V_{sig}}{2}) = V_{sig} \rightarrow |V_{sig}| < \frac{2.89}{73.25} = .0395V$

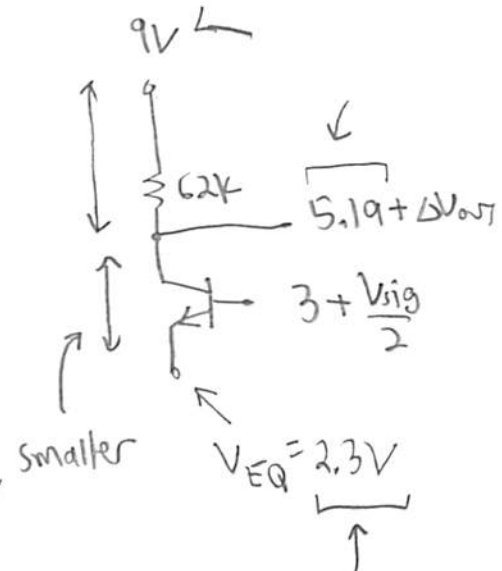



+6

$|V_{sig}| < 39.5 \text{ mV}$

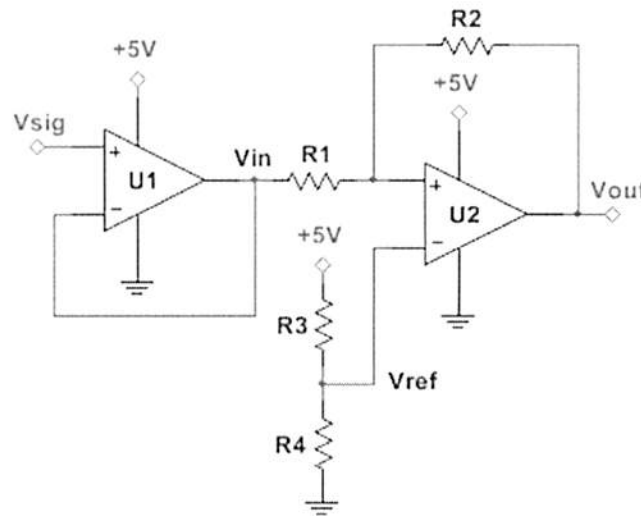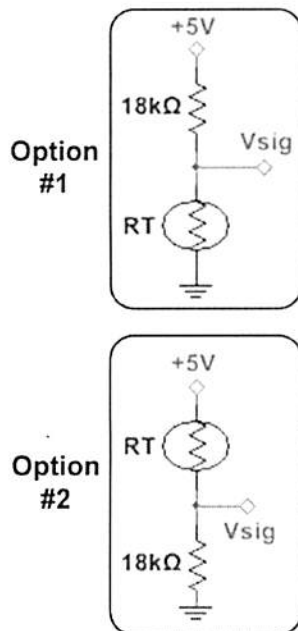Problem #4: Thermostat (25 pts)

A chemical processing machine requires cooling a sample and maintaining the temperature within a certain range. Temperature is measured with a thermistor (thermally sensitive resistor). The specs are the following:

- Temperature sensor:
 - The thermistor resistance is $R_T = 12.49 \text{ kohm}$ @ 20°C and $R_T = 25.34 \text{ kohm}$ @ 5°C .
 - The thermistor R_T is either in the bottom (Option #1) or top (Option #2) of a voltage divider.
- Both op amps are operated from a single-supply. Assume $V_{SAT(+)} = V_{CC} - 1\text{V}$ and $V_{SAT(-)} = 0\text{V}$.
 - Op amp U1 is just a buffer. Op amp U2 is a Schmitt trigger with V_{OUT} being:
 - HIGH when the temperature rises above 20°C
 - LOW when the temperature dips below 5°C
- Some useful formulas for the Schmitt trigger are:
 - Upper Trip Point: $UTP = (1 + R_1/R_2) \cdot V_{REF} - (R_1/R_2) \cdot V_{SAT(-)}$
 - Lower Trip Point: $LTP = (1 + R_1/R_2) \cdot V_{REF} - (R_1/R_2) \cdot V_{SAT(+)}$



- Would you use Option #1 or Option #2 to produce V_{sig} ? **Explain your reasoning (e.g. a table helps).**
- Compute the UTP and LTP values for V_{sig} to **3 decimal places** (e.g. 1.234V) based on your answer to (a).
- Based on the UTP and LTP formulas, choose appropriate 5% values for R_1 and R_2 . NOTE: R_2 should be in the 100 kohm range.
- Determine V_{REF} , and choose 5% values for R_3 and R_4 . NOTE: R_4 should be in the 100 kohm range.

+5

(a) Higher

Want V_{sig} for $T=20^\circ\text{C}$

T	R_T	V_{sig} (option #1)	(option #2)
20°C	12.49K	$5 \times \frac{12.49}{12.49+18} = 2.048$	$5 \times \frac{18}{18+12.49} = 2.952$
5°C	25.34K	$5 \times \frac{25.34}{25.34+18} = 2.923$	$5 \times \frac{18}{18+25.34} = 2.071$

choose option #2

ECE 363: Design of Electronic Circuits Exam 2 Nov 12, 2019

(extra sheet for work)

(b) From Table:

$UTP = 2.952V$ $LTP = 2.077V$

+5

$$2.952 = \left(1 + \frac{R_1}{R_2}\right) V_{REF} - 0$$

$$- \quad 2.077 = \left(1 + \frac{R_1}{R_2}\right) V_{REF} - \frac{R_1}{R_2} 4$$

$$0.875 = 4 \frac{R_1}{R_2} \rightarrow \frac{R_1}{R_2} = 0.219$$

+8

let

$R_2 = 100K$
$R_1 = 22K$

 $\Rightarrow \frac{R_1}{R_2} = 0.22 \checkmark$

(d) $2.952 = (1 + 0.22) V_{REF} \Rightarrow V_{REF} = 2.420V = 5 \frac{R_4}{R_3 + R_4}$

+7

$$\frac{R_3 + R_4}{R_4} = 1 + \frac{R_3}{R_4} = 2.066$$

$$\frac{R_3}{R_4} = 1.066$$

R_4	R_3	R_4/R_3
100K	110K	1.1
110K	120K	1.09
120K	130K	1.083
130K	150K	1.154
150K	160K	1.067 \checkmark