
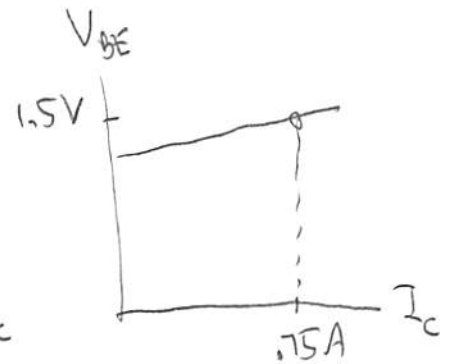


(extra sheet for work)

© MJE800 plots.

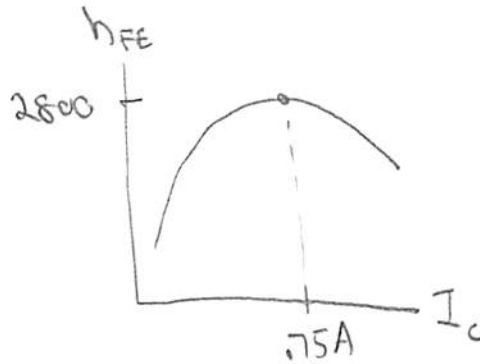


$$\text{WANT } I_c = 0.75A = \alpha I_E$$

$$= \frac{2800}{2801} \frac{3.3 - 1.5V}{R_E} = 0.75A \rightarrow R_E = 2.4\Omega$$

$$i_2 = i_s - i_B \geq 10mA$$

$$\frac{15 - 3.3}{R_s} - \frac{0.75A}{2801} > 0.010A$$

$$R_s < 1139.5\Omega$$

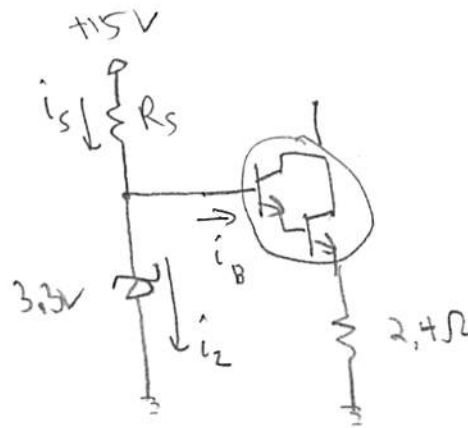


min $i_2 = 10mA$ is not super strict, so ok to choose $R_s = 1.1K$

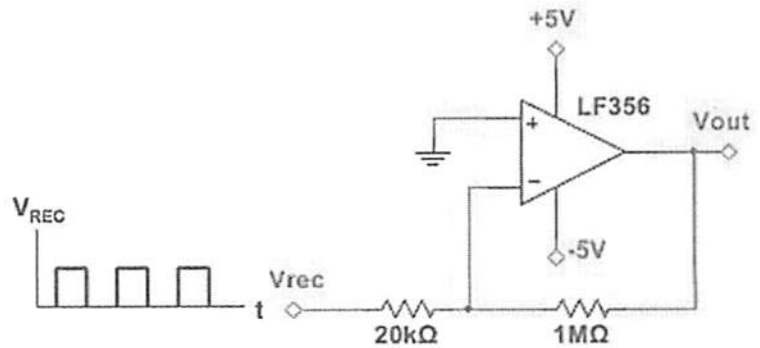Problem #2: Amplifier Output Error (25 pts)

Consider an optical communication link for an infrared remote control. A transmitter sends a train of infrared pulses. The receiver converts the optical pulses into voltage pulses.

Suppose the receiver output V_{REC} consists of 50% duty cycle pulses with a 20 mV amplitude and 40 kHz frequency. These tiny pulses are sent to an inverting amplifier built with an LF356 op amp.



- Is the amplifier output limited by small-signal bandwidth or slew rate? Show all work!
- Compute the worst-case output error voltage (assume $T_A = 25^\circ\text{C}$). Show all work!
- Assuming worst-case output error voltage, sketch both V_{REC} and V_{OUT} over a 50 μs interval. Label important features!

a) Inverting amplifier: $G = -\frac{10^6 \Omega}{20 \times 10^3 \Omega} = -\frac{1000}{20} = \underline{\underline{-50}}$

LF356: $GBW = 5\text{MHz}$, $SR = 12\text{V}/\mu\text{s}$

$$BW = \frac{5\text{MHz}}{50} = \underline{\underline{0.1\text{MHz}}}, \quad T_R = \frac{0.35}{0.1\text{MHz}} = \underline{\underline{3.5\mu\text{s}}}$$

$$T_{SR} = \frac{0.8 V_{OUT,PP}}{SR} = \frac{0.8 (50 \times 0.020\text{V})}{12\text{V}/\mu\text{s}} = \underline{\underline{0.067\mu\text{s}}}$$

Limited by small signal BW

b) $R_{TH(+)} = 0$

$$R_{TH(-)} = 20\text{k} \parallel 1000\text{k} = \underline{\underline{19.61\text{k}}}$$

$$I_{IN, BIAS} = 200\text{pA}$$

$$I_{IN, OS} = 50\text{pA}$$

$$V_{IN(OS)} = 10\text{mV}$$

$$\Delta V_{OUT} = (200 \times 10^{-12}\text{A})(19.61 \times 10^3 - 0) \times |50| = \underline{\underline{0.196\text{mV}}} \leftarrow I_{IN, BIAS}$$

$$(50 \times 10^{-12}) \left(\frac{19.61 \times 10^3 + 0}{2} \right) \times |50| = \underline{\underline{0.0245\text{mV}}}$$




$$10\text{mV} \times |50| = 500\text{mV}$$

$$\text{Worst-case } V_{OUT} = 0.196\text{mV} + 0.0245\text{mV} + 500\text{mV} = \boxed{500.2\text{mV}}$$

(extra sheet for work)

© $V_{out} = (0.020V)(-50) = -1V$

40 kHz: $1 \text{ cycle} = 25 \mu s$

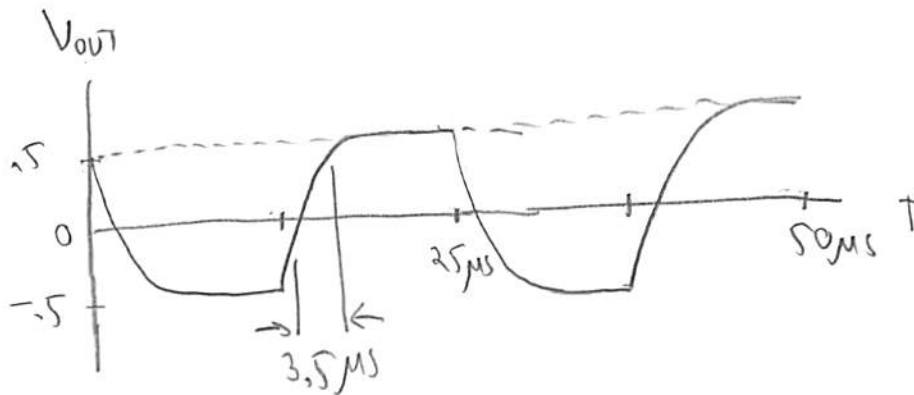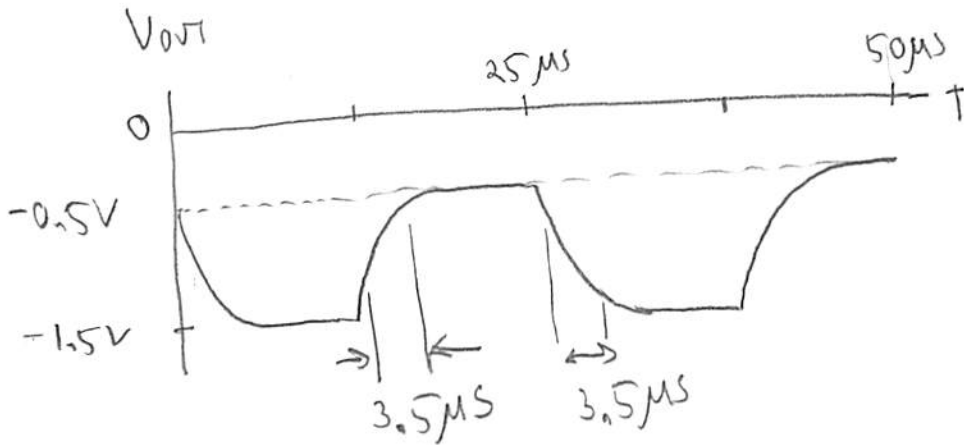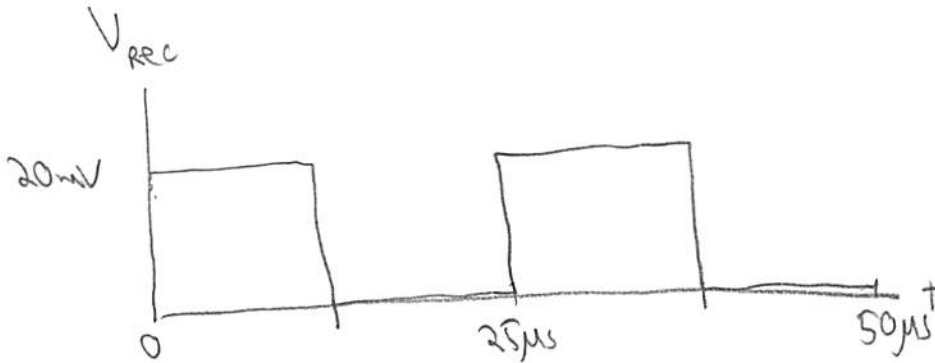


Either plot is fine

Problem #3: Digital-to-Analog Converter (25 pts)

Recall binary numbers from ECE 118. A 3-bit binary number ($B_2 B_1 B_0$) is equal to $B_2 \cdot 2^2 + B_1 \cdot 2^1 + B_0 \cdot 2^0$. For example, (110) is equal to $1 \cdot 4 + 1 \cdot 2 + 0 \cdot 1 = 6$. As another example, (011) is equal to $0 \cdot 4 + 1 \cdot 2 + 1 \cdot 1 = 3$.

How do we use hardware to convert a binary number into decimal? The digital outputs from a microcontroller are typically 5V logic. Therefore, a binary "1" is really +5V, while a binary "0" is really 0V.

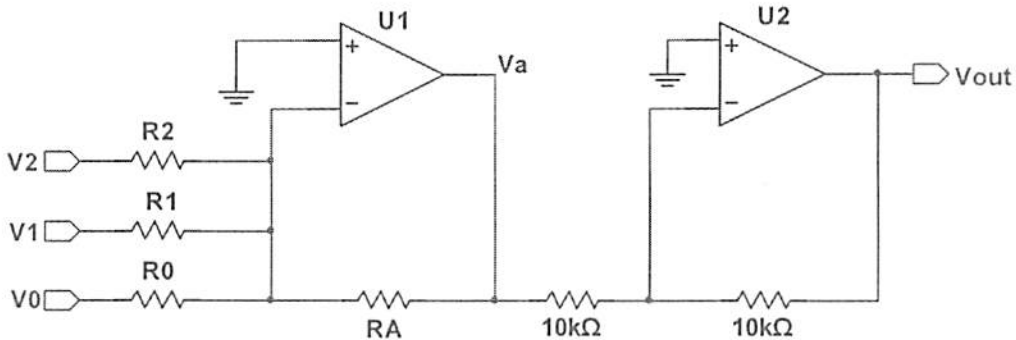A simple 3-bit digital-to-analog converter (DAC) is shown below. The input voltages V_2, V_1, V_0 come from a microcontroller. The output V_{OUT} is an "integer" from 0 to 7V. For example, the binary number (110) should produce $V_{out} = 6V$, while the binary number (011) should produce $V_{out} = 3V$.



(a) Use the Golden Rules to derive an expression for V_{OUT} in terms of $V_2, V_1,$ and V_0 . Show all work!

Hint: Think about V_{OUT} in terms of V_a , and then V_a in terms of the inputs.


(b) Suppose $R_A = 40 \text{ kohm}$. Determine the ideal values for $R_2, R_1,$ and R_0 . Show all work!

(c) Suppose you are using LF356 op amps, and assume the final output is connected to a load $R_L \geq 10 \text{ kohm}$. Would you use $V_{cc} = 8V$ for this circuit? How about $V_{cc} = 9V$? Show all work!

① $V_- = V_+ = 0$

$$i = \frac{V_a - 0}{10k} = \frac{0 - V_{out}}{10k}$$


$$\rightarrow V_{out} = -V_a \quad (1)$$

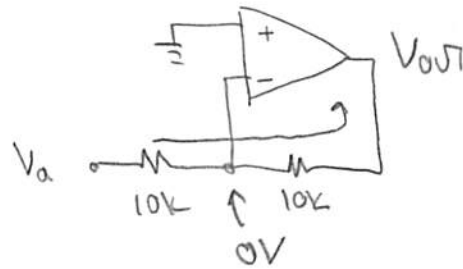

$$V_- = V_+ = 0$$

$$i_2 + i_1 + i_0 = i_A$$
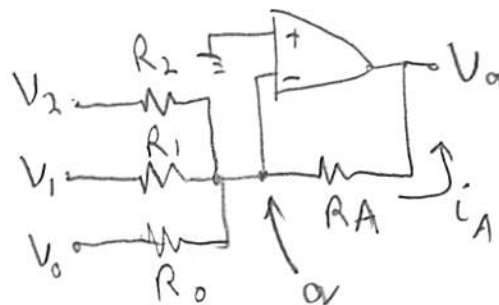
$$\frac{V_2 - 0}{R_2} + \frac{V_1 - 0}{R_1} + \frac{V_0 - 0}{R_0} = \frac{0 - V_a}{R_A} \quad (2)$$



$$(1) \text{ into } (2) = \frac{V_2}{R_2} + \frac{V_1}{R_1} + \frac{V_0}{R_0} = \frac{V_{out}}{R_A} \Rightarrow V_{out} = \frac{R_A}{R_2} V_2 + \frac{R_A}{R_1} V_1 + \frac{R_A}{R_0} V_0$$

(extra sheet for work)

Binary (001) \Rightarrow $(0, 0, 5V)$ $\rightarrow V_{out} = \frac{40k}{R_o} \times 5V = 1V$

$R_o = 200k$

Binary (010) \Rightarrow $(0, 5V, 0)$ $\rightarrow V_{out} = \frac{40k}{R_1} \times 5V = 2V$

$R_1 = 100k$

Binary (100) \Rightarrow $(5V, 0, 0)$ $\rightarrow V_{out} = \frac{40k}{R_2} \times 5V = 4V$

$R_2 = 50k$


Max $V_o = 7V \leftarrow$ Binary (111)

If $V_{cc} = 8V \rightarrow$ op amp headroom $= 8 - 7 = 1V$, $i_o = \frac{7V}{10k} = \underline{0.7mA}$ max

Cannot use $V_{cc} = 8V$

For $V_{cc} = 15V$

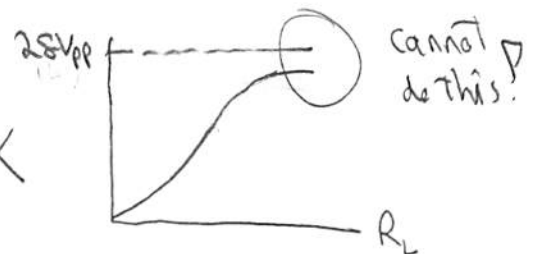
$\hookrightarrow V_o = 15 - 1 = \underline{14V}$



If $V_{cc} = 9V \rightarrow$ op amp headroom $= 9 - 7 = 2V$

For $V_{cc} = 15V$

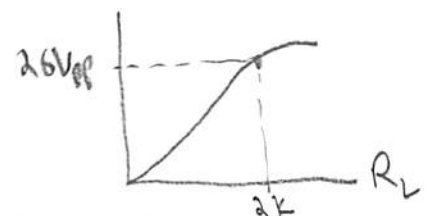$\hookrightarrow V_o = 15 - 2 = \underline{13V}$



OK to use $V_{cc} = 9V$


$i_o = \frac{13V}{2k} = \underline{6.5mA} \gg \underline{0.7mA}$ ✓

Oct 15, 2019

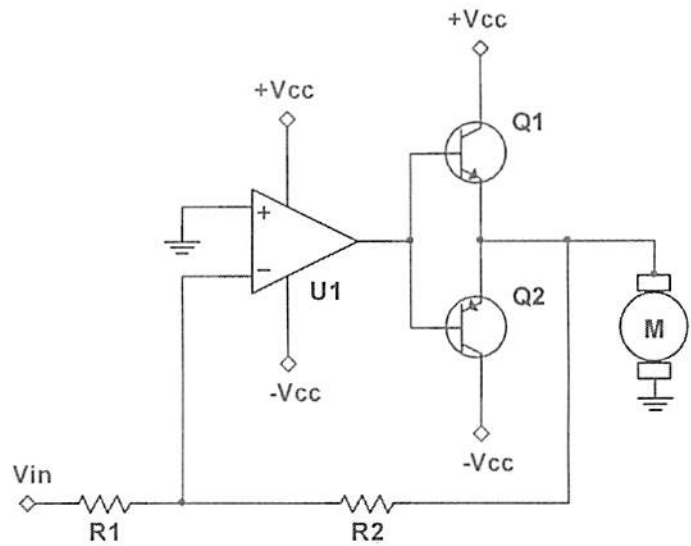Problem #4: Push-Pull Current Booster (25 pts)

Design a voltage amplifier to drive a 6V DC motor with a max power consumption of 1.2W. The motor voltage must not exceed 6V by more than 5%. The input signal can swing between -0.2V and 0.2V. The design constraints are the following:

- Use an LF356 op amp.
- Q1 is either a 2N4401 or TIP31.
NOTE: The pnp versions are the 2N4403 and TIP32.
- V_{CC} is either 4.5, 6, 9, or 12V
- Input impedance $Z_{IN} \geq 10 \text{ kohm}$
- All resistors are 5% standard values.



- Perform a "quick" analysis to choose V_{CC} . Show all calculations!
- Perform a "quick" analysis to choose Q1. You must explain why you chose one transistor and not the other one. If Q1 needs a heat sink, you must compute the max θ_{SA} (assume $\theta_{CS} = 0.5^\circ\text{C/W}$).
- Show that the op amp can provide the required output voltage and current, even under worst-case transistor conditions.
- Choose R1 and R2. Show all work!

a) Load: $V_{max} = 6V$, $I_{max} = \frac{1.2W}{6V} = 0.2A$

$V_{cc} > 6 + 0 + 2 = 8V \rightarrow$ Choose $V_{cc} = 9V$

b) Max $I_c \approx 0.2A$, Max $V_{CE} = 9 - (-6) = 15V$

\downarrow
 $> 0.4A$ rating $\xrightarrow{x2}$ $> 30V$ rating

$P = \frac{0.2A}{101} (0.7) + 0.99 (0.2A)(9-6) = 0.595W \xrightarrow{x2} 1.19W$ rating

	Max I_c	Max V_{CE}	P (no HS)	P (w/HS)
--	-----------	--------------	-----------	----------

2N4401

0.6A ✓

40V ✓

0.625W ✗

1.5W ✓

TIP31A

3A ✓

40V ✓

2W ✓

40W

2N4401
Needs HS.

TIP31 does not need HS

(extra sheet for work)

Appendix

If you chose TIP31 without HS:

$$\frac{\text{Max } V_{BE}}{\text{Typ } V_{BE}} = \frac{1.8V}{1.2V} = \frac{2}{0.7V} \rightarrow \text{min } V_{BE} = \underline{\underline{1.05V}} \quad \left. \begin{array}{l} \\ \\ \end{array} \right\} \text{Max } V_o = 6 + 1.05 = \underline{\underline{7.05V}}$$

$$\frac{\text{Min } h_{FE}}{\text{Type } h_{FE}} = \frac{25}{65} = \frac{2}{130} \rightarrow \text{min } h_{FE} = \underline{\underline{50}} \quad \left. \begin{array}{l} \\ \\ \end{array} \right\} \text{Max } i_o = \frac{0.2A}{51} = \underline{\underline{3.9mA}}$$

op amp headroom = $9 - 7.05 = 1.95V$

If $V_{cc} = 15V$, then $\text{max } V_o = 15 - 1.95 = \underline{\underline{13.05V}}$

$$\text{max } i_o = \frac{13.05V}{2k} = \underline{\underline{6.5mA}}$$

op amp is ok with TIP31!

