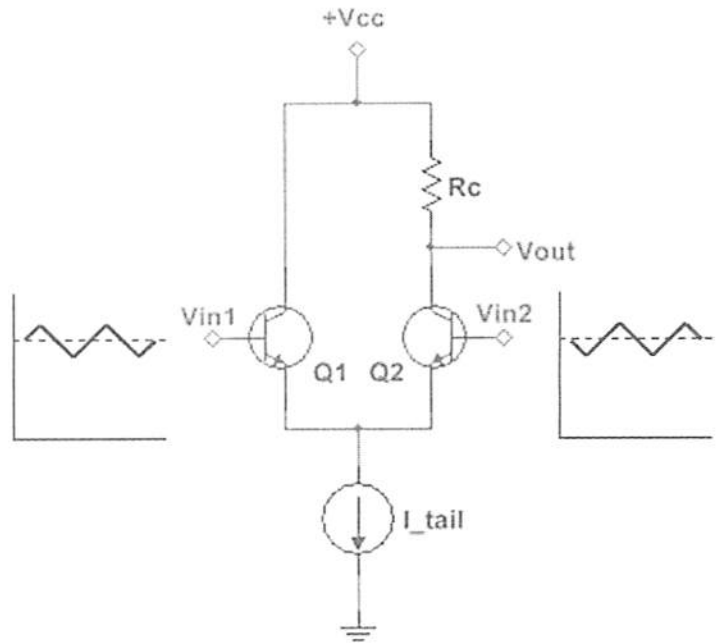


## Problem #2: Differential Amplifier (25 pts)

Your application requires a differential amplifier with  $A_d = +34$  dB ( $\pm 0.5$  dB is OK). Suppose  $V_{CC} = +15$  V and a 0.2 mA current sink produces the tail current. Assume Q1 and Q2 have the same properties as the 2N3904. The voltage inputs are given by:

- Compute the minimum and typical values for the amplifier input impedance  $Z_{IN}$ .
- Choose a standard 5% value for  $R_C$  and compute the resulting differential gain. Assume typical transistor parameters. Show all work!
- What is the minimum CMRR needed to ensure that  $\Delta V_{OUT} < 10$  mV for a 5V common-mode input? Express your answer in dB.
- Suppose  $V_{in1} = 5 + \Delta V(t)$  and  $V_{in2} = 5 - \Delta V(t)$ , where  $\Delta V(t)$  is an 100 mV peak-to-peak triangle wave at 20 kHz. Compute and sketch  $V_{OUT}$  over a 150  $\mu$ s time interval. You can assume  $A_{CM} \approx 0$ . Label important features!



a)  $Z_{IN} = 2(\beta+1)r_e' = 2(\beta+1) \frac{0.026V}{\frac{1}{2} I_T \leftarrow 0.2mA}$

Min  $Z_{IN} = 2(41) \frac{0.026}{\frac{1}{2}(0.2mA)} = 21.3K$

Typ  $Z_{IN} = 2(231)(0.26K) = 120.1K$

At  $I_c \sim \frac{1}{2}(0.2mA) = 0.1mA$

$\beta_{min} = 40$

$\beta_{typ} = 230$

$\alpha = \frac{230}{231} = 0.996$

b)  $20 \log_{10} A_d = 34 dB \rightarrow A_d = 10^{34/20} = 50.1 = 0.996 \frac{R_C}{2(0.26K)}$

$A_d = 0.996 \frac{27K}{2(0.26K)} = 51.7$   
 $= 34.27 dB$  ✓  
 within 0.5 dB  
 $R_C = 26.2K$   
 Choose  $R_C = 27K$

c) Want  $A_{CM} V_{CM} < 0.010V$

$A_{CM} < \frac{0.010}{5} = 0.002 \rightarrow CMRR \geq 20 \log_{10} \left( \frac{51.7}{0.002} \right)$   
 $= 88.3 dB$

(extra sheet for work)

$$\textcircled{d} \quad \Delta V_{in} = 2\Delta V(t) = 200 \text{ mV}_{pp} [\text{triangle wave}] = 100 \text{ mV}_p [\text{triangle wave}]$$

$$\text{So, } V_{out} = V_{ceq} + A_d \Delta V_{in} + \underbrace{A_{cm} V_{cm}}_{\approx 0} = 12.31 + 51.7 \times 0.1 \text{ V} [\text{triangle wave}]$$


$$\underbrace{15 - \frac{0.996 \text{ mA}}{2} (27\text{k})}_{12.31 \text{ V}}$$

$$= 12.31 + 5.17 \times [\text{triangle wave}]$$

$$\text{Max } V_{out} = 12.31 + 5.17 = 17.48 \text{ V} \times \leftarrow \text{cannot exceed 15V due to } Q_2 \text{ cut-off}$$

$$\text{Min } V_{out} = 12.31 - 5.17 = 7.14 \text{ V} \checkmark \leftarrow \text{Does not saturate } Q_1$$

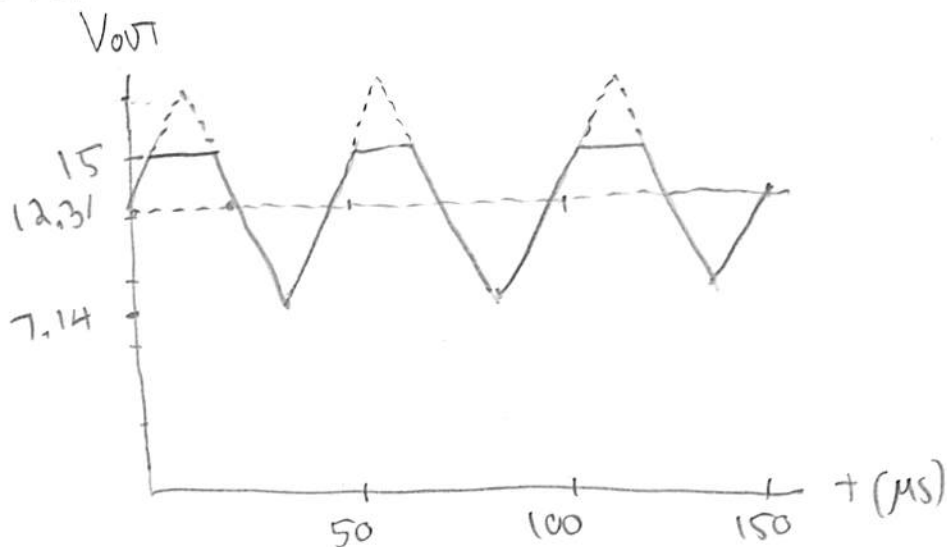20 kHz  $\rightarrow$  1 cycle = 50  $\mu$ s





8
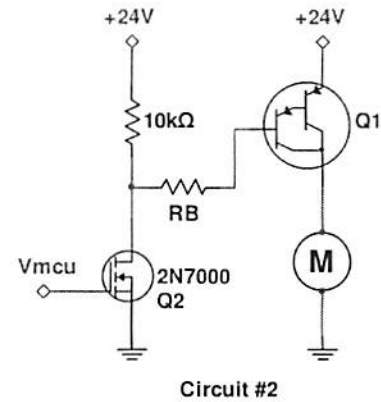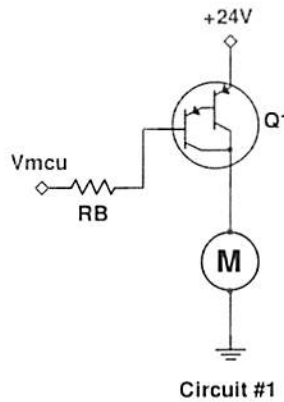
## Problem #2: Transistor Switches (25 pts)

You are asked to design a circuit to allow a microprocessor unit (MCU) to operate a DC motor.

- The MCU output  $V_{mcu}$  is 5V logic with a 20 mA current limit.
- The motor is rated at 4A for voltages between 22 and 24V.
- The motor must be operated with a high-side transistor switch.



- Explain why Circuit #1 would not work while Circuit #2 would work OK.
- Q1 must either be a TIP115 or TIP105 transistor. Choose the appropriate transistor by only considering  $\max I_C$  and  $V_{CE}$ .
- Given your choice of Q1, would a 10, 15, or 20 °C/W heat sink be adequate? Assume typical Q1 properties.
- Compute the appropriate 5% standard resistor for  $R_B$ . Assume typical Q1 and Q2 conditions.

**(a)**

Circuit #1:

$Q_1 = \text{ON}$

$V_{BE} \approx 22.6V$

$V_{CE} \approx 22.6V$

$I_C = 4A$

Circuit #2:

$Q_1 = \text{OFF}$

$V_{BE} = 24 - 24 = 0V$

$V_{GS} = 0 < 2.4V$

$Q_1 = \text{ON}$

$V_{BE} \approx 1.4V$

$V_{GS} = 5 > 2.1V$

$I_C = 4A$

$\star Q_1$  is always ON, so circuit #1 will not work! ☹️

$\star Q_1$  is OFF or ON, so circuit #2 will work! 😊

(extra sheet for work)

		<u>Max <math>I_c</math></u>	<u>Max <math>V_{ce}</math></u>	<u>+4</u>
ⓑ	TIP115:	2A X	60V ✓	
	TIP105:	8A ✓	60V ✓	Choose <b>TIP105</b>

ⓒ  $|V_{ce}| \sim 1.55V$ ,  $|V_{be}| \sim 2.1V @ I_c = 4A$

$P = \left(\frac{4A}{250}\right)(2.1V) + (4A)(1.55V) = \underline{6.23W}$  +5

$25^\circ C + 6.23W (1.56^\circ C/W + 0.5^\circ C/W + \Theta_{SA}) < 100^\circ C$

$\Theta_{SA} < \frac{100 - 25^\circ C}{6.23W} - (1.56 + 0.5^\circ C/W)$

Choose  $10^\circ C/W$   
heat sink



$< \underline{9.98^\circ C/W}$  +5

Close enough  
to  $10^\circ C/W$

ⓓ Estimate  $Q_2$  drain current:

$I_D \sim 18.4mA$

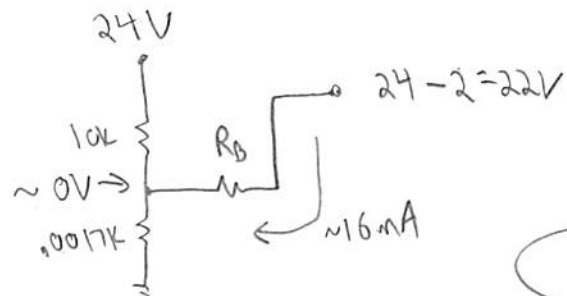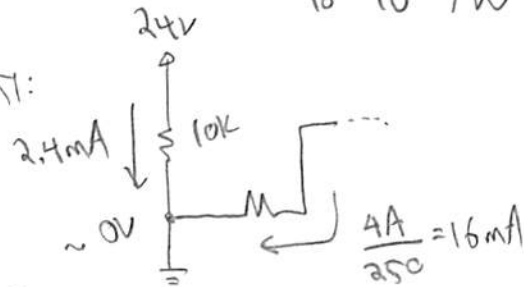$R_{os,on} \sim \frac{0.5V}{0.3A} = 1.67\Omega$



Assuming  $R_{os,on} \ll R_B$ ,

$\frac{22 - 0}{R_B} = 16mA$

$R_B = 1.375K$

check later  
✓

$1.67\Omega \ll 1.3K \checkmark$

Choose  **$R_B = 1.3K$**

+5


### Problem #3: Servo Motor Controller (25 pts)

You are asked to design the PWM circuit for a digital servo motor controller. The triangle wave oscillator must have a frequency  $f = 50$  Hz and peak-to-peak amplitude of  $3V_{pp}$ . Use TLV2371 op amps powered by +5V and GND. These rail-to-rail op amps have  $V_{SAT(+)} = V_{CC}$  and  $V_{SAT(-)} = 0$ . Some useful formulas are shown below:


$$V_{TH} = 0.5(V_{SAT(+)} - V_{SAT(-)})R_1/R_2$$

$$V_{REF} = 0.5(V_{SAT(+)} - V_{SAT(-)})$$

$$f = R_2/(4R_1R_3C)$$

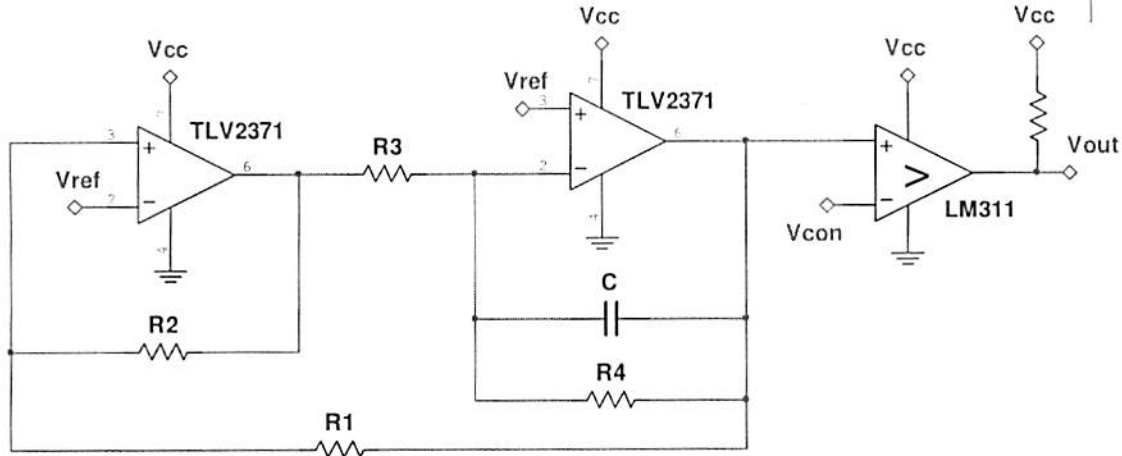

- Choose 5% values for  $R_1$  and  $R_2$  such that the resulting triangle wave peak amplitude is **within 5% of the desired value**. Show all work!
- Choose 5% values for  $R_3$ ,  $R_4$ , and  $C$  and confirm the resulting triangle wave frequency is **within 5% of the desired value**. Show all work!
- In many servos, a PWM pulse width (e.g. duration of the HIGH portion) of 1.5 ms puts the motor in the "home" position. What control voltage  $V_{CON}$  is needed to make this possible? Show all work!

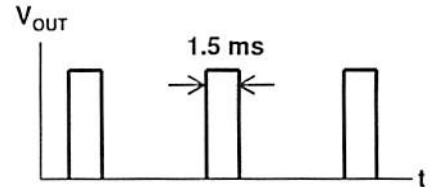

$$\textcircled{a} \quad V_{TH} = 1.5V = 0.5(5-0) \frac{R_1}{R_2} \Rightarrow \frac{R_1}{R_2} = 0.6 \text{ or } \frac{R_2}{R_1} = 1.667$$

$$2V_{TH} = 2 \times \frac{5-0}{2} \frac{12k}{20k}$$

$$= \underline{3V} \leftarrow 0\% \text{ error!}$$

Choose

$$\boxed{R_1 = 12k}$$

$$\boxed{R_2 = 20k}$$

$R_1$	$R_2$
10k	16.67k
11k	18.34k
12k	20.0k

→

+9

(extra sheet for work)

b)  $f = \frac{20k}{4(12k)R_3C} = 50\text{Hz} \rightarrow R_3C = 8.333 \times 10^{-3}\text{s}$


	C	R <sub>3</sub>	5% R <sub>3</sub>	
	100 nF	83.33K	82K	-1.6%
Choose	C = 150 nF	69.44K	68K	-2.1%
	R <sub>3</sub> = 56K	55.55K	56K	-0.8%

+9

$f = \frac{20k}{4(12k)(56 \times 10^3)(150 \times 10^{-9})} = 49.6\text{Hz}$

$100 \times \frac{49.6 - 50}{50} = -0.8\%$

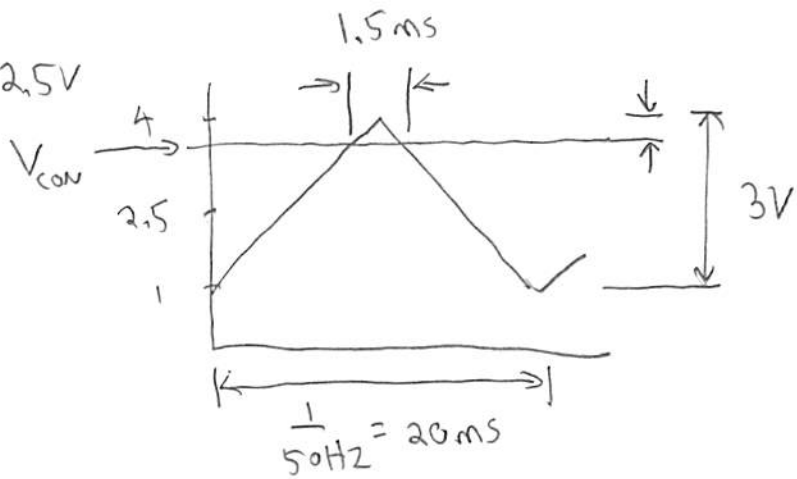c)  $V_{REF} = \frac{5-0}{2} = 2.5\text{V}$



want  $\frac{1.5\text{ms}}{20\text{ms}} = \frac{4 - V_{CON}}{4 - 1\text{V}}$

$4 - V_{CON} = 3 \frac{1.5}{20}$


$V_{CON} = 4 - 3 \times \frac{1.5}{20} = 3.775\text{V}$

+7

### Problem #4: Water Valve Controller (25 pts)

A greenhouse needs an automatic sprinkler system. Here's how it works: when the plants are too dry, a solenoid valve turns on and water flows through the sprinkler system. The system has four parts:

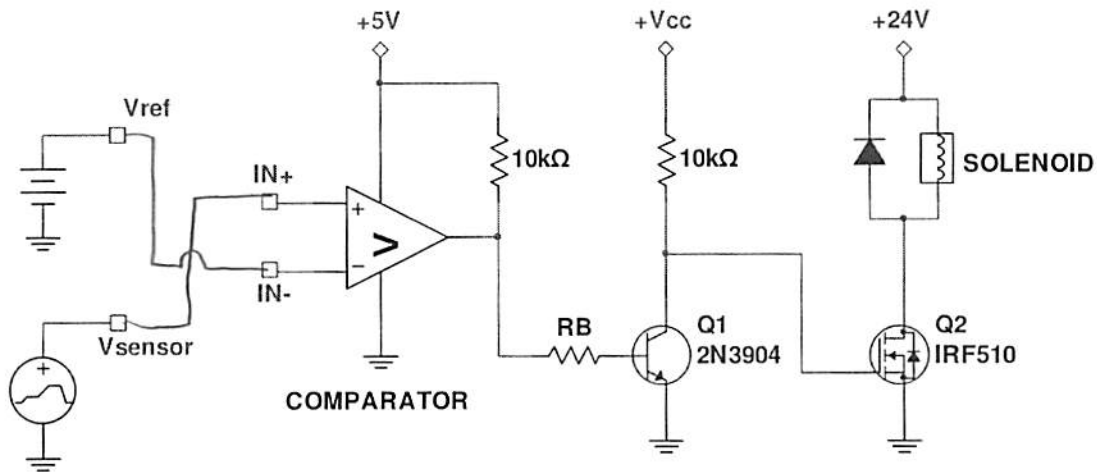- (1) Water-level sensor produces  $V_{\text{SENSOR}}$  between 1V (water = empty) and 2V (water = full).
- (2)  $V_{\text{SENSOR}}$  and  $V_{\text{REF}}$  are inputs to a voltage comparator with open collector output.
- (3) 2N3904 transistor switch drives an IRF510 power MOSFET.
- (4) 24V, 1A solenoid turns on to allow water flow.



- (a) How would you connect  $V_{\text{SENSOR}}$  and  $V_{\text{REF}}$  to the comparator?
- (b) You must choose between  $V_{\text{CC}} = 5, 12, \text{ and } 24\text{V}$ . Use the appropriate 2N3904 and IRF510 data sheet parameters to explain why your chosen  $V_{\text{CC}}$  works and why the other two values do not.
- (c) Compute the appropriate 5% standard resistor for  $R_B$ . Assume typical Q1 conditions and keep in mind that the comparator has an open collector output.

(a) When dry:  $V_{\text{sensor}} < V_{\text{ref}} \rightarrow$  Comparator is LOW  $\rightarrow$  Q1 OFF  $\rightarrow$  Q2 ON  
 WET:  $V_{\text{sensor}} > V_{\text{ref}} \rightarrow$  Comparator is HIGH  $\rightarrow$  Q1 ON  $\rightarrow$  Q2 OFF

(b) Q2 gate is the key!

$V_{\text{CC}}$	$V_{\text{GS}}$	Notes
5V	5V	Not much higher than 4V. May not fully turn ON Q2
12V	12V	Good! Fully turn on Q2 without damage.
24V	24V	Exceeds max allowable $V_{\text{GS}}$


Max  $V_{\text{GS,TH}} = 4\text{V}$   
 Max  $V_{\text{GS}} = 20\text{V}$

WINNER! (with trophy icon)

+10

(extra sheet for work)

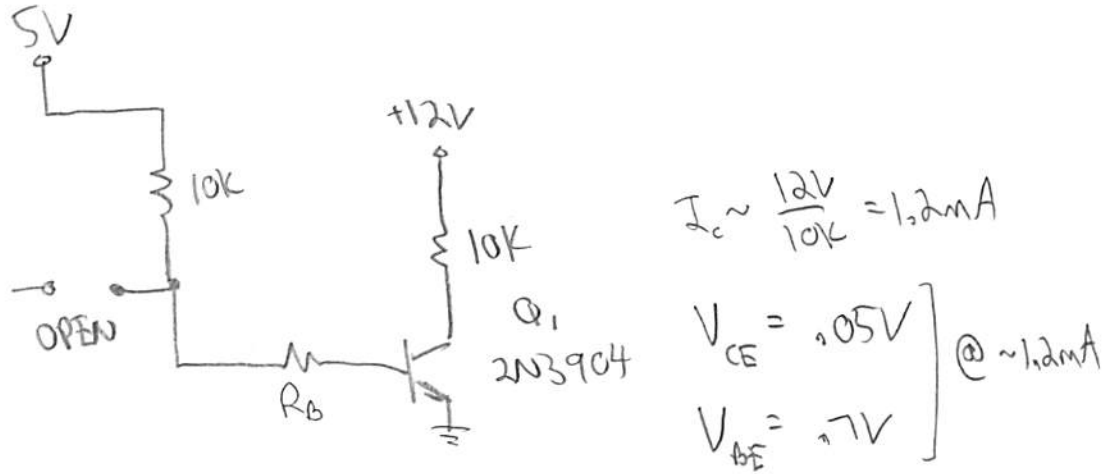Ⓒ Comparator HIGH output means open collector.



So, want  $I_B = \frac{I_c}{10}$

$$\frac{5 - 0.7}{10k + R_B} = \frac{1}{10} \frac{12 - 0.05V}{10k} = 0.12mA$$

+9

$\rightarrow R_B = 25.98k$

choose  $R_B = 27k$