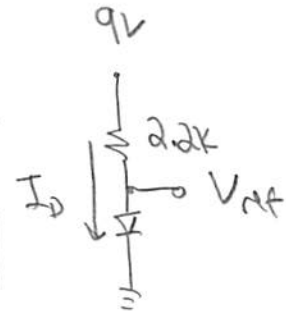


① a)

$$9 - I_D \times 2.2k - 0.7 = 0$$

$$I_D = \frac{9 - 0.7}{2.2k} = \boxed{3.77 \text{ mA}}$$


$$V_{REF} = \boxed{0.7 \text{ V}}$$



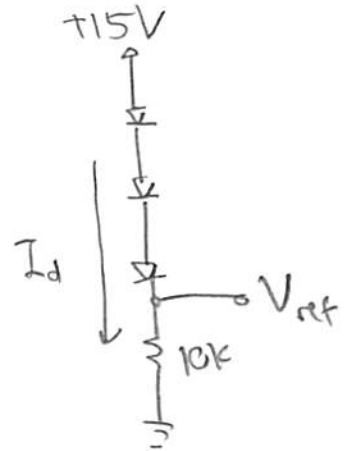b) Assume diodes ON;

$$V_{REF} = 15 - 3 \times 0.7 = \boxed{12.9 \text{ V}}$$


$$I_D = \frac{12.9 - 0}{10k} = \boxed{1.29 \text{ mA}}$$



$$c) V_{REF} = V_Z = \boxed{6.2 \text{ V}}$$

(Assume zener ON).

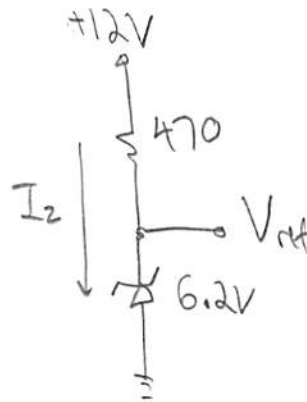
$$I_Z = \frac{12 - 6.2}{470} = 0.0123 \text{ A} = \boxed{12.3 \text{ mA}}$$



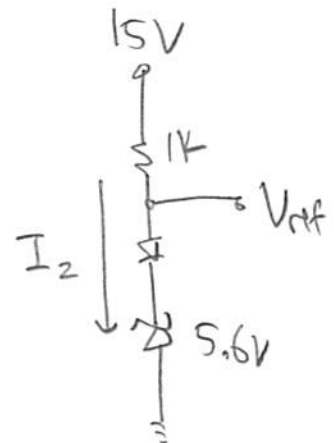d) Assuming zener + diode ON:

$$V_{REF} = 5.6 + 0.7 = \boxed{6.3 \text{ V}}$$


$$I_Z = \frac{15 - 6.3}{1k} = \boxed{8.7 \text{ mA}}$$



2

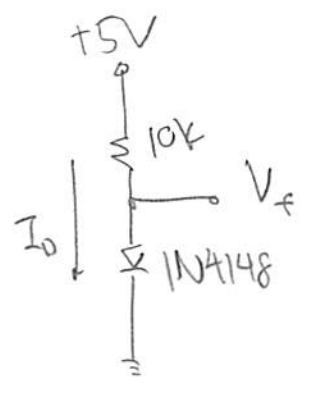(a) "Quick" analysis means  
assume diode has 0.7V:


$$I_d = \frac{5 - 0.7}{10k} = \boxed{0.43mA}$$



(b)

For  $I_d = 0.43mA$

$$\rightarrow \boxed{V_F \sim 0.6V}$$

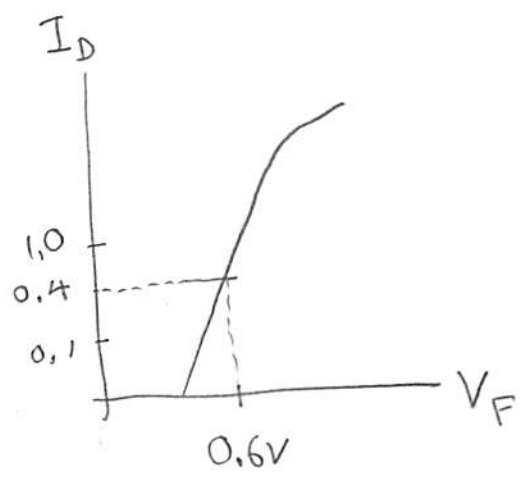


(c) using  $V_F = 0.6V \rightarrow I_d = \frac{5 - 0.6}{10k} = \boxed{0.44mA}$

← slight change from (a).

★ NOTE: You can repeat this process, if necessary, to get more accurate result. What's really going on is we are numerically finding the intersection of 2 curves.

①  $I_D - V_F$  plot

②  $I_D = \frac{5 - V_F}{10k}$

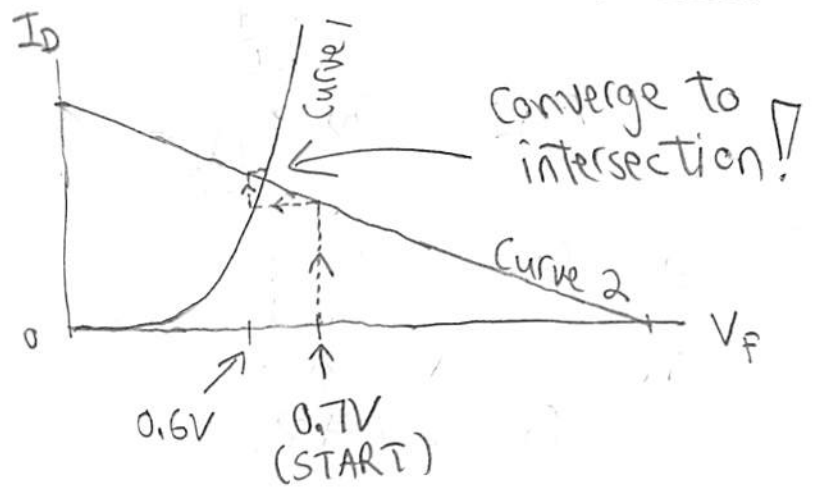

③


- want  $I_z > 10\text{mA}$

$$\text{Min } I_z = \frac{10 - (5.6 + 0.7)}{R} > .010\text{A}$$

$$R < 370\Omega \xrightarrow{\times .95} 351.5$$

Choose  $R = 330\Omega$

(360 $\Omega$  would be OK)

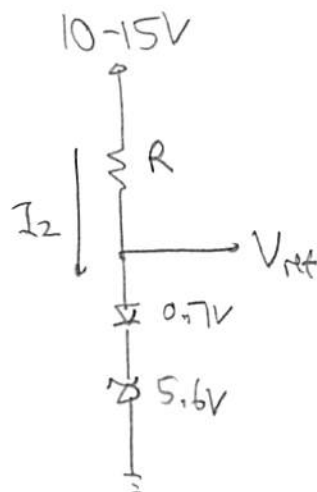

- want  $P_{\text{rating}} > 2 \times (\text{max power dissipation})$


$$\text{Max } P = \frac{(15 - 6.3)^2}{330} = 0.23\text{W}$$

$$P_{\text{rating}} > 2 \times .23 = .46\text{W} \rightarrow \text{choose } \boxed{\frac{1}{2}\text{W rating}}$$

4

(a) 
$$I_{PIN} = \frac{5 - 0V}{80\Omega}$$


$$= \boxed{62.5\text{ mA}}$$

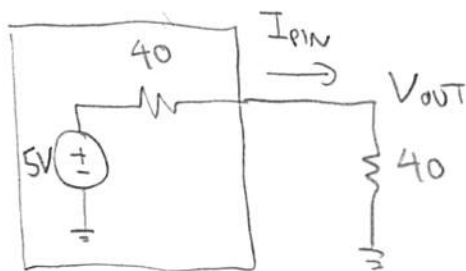

$$V_{OUT} = (0.0625A)(40\Omega) = \boxed{2.5V}$$

(b)  $V_{OUT} \ll 4V \leftarrow$  NOT ACCEPTABLE! ☹️

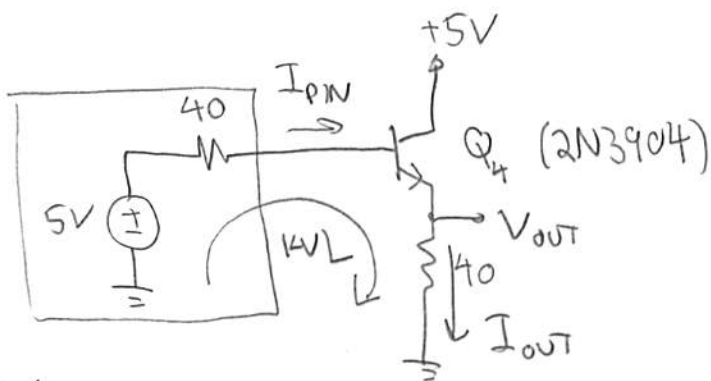(c) KVL: 
$$5 - I_{PIN} \cdot 40 - 0.7 - I_{OUT} \cdot 40 = 0$$



$$I_{OUT} = \frac{5 - 0.7V}{\frac{40}{101} + 40} = \underline{\underline{106.4\text{ mA}}}$$



$$\rightarrow V_{OUT} = (0.1064)(40) = \boxed{4.26V} \leftarrow \text{OK!}$$

(d) Since  $I_c \sim 0.99(106.4\text{ mA}) = 105.3\text{ mA}$

$V_{BE} = 0.8V$

$\beta = 150$

From plots on page 3 of data sheet

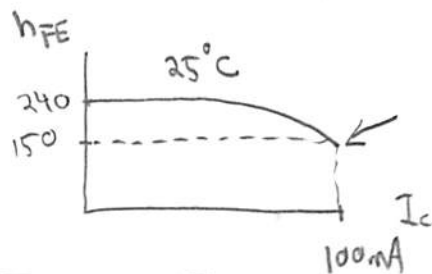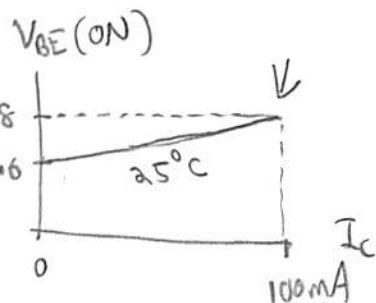

$$\rightarrow I_{OUT} = \frac{5 - 0.8V}{\frac{40}{150+1} + 40} = 104.3\text{ mA}$$

$$\rightarrow V_{OUT} = (0.1043)(40) = \boxed{4.17V} \leftarrow \text{OK!}$$

$$I_{PIN} = \frac{I_{OUT}}{\beta + 1} = \frac{104.3 \text{ mA}}{150 + 1} = \boxed{0.69 \text{ mA}}$$

Nice and small! 😊


© Worst-Case:

• Table says min  $h_{FE} = 30$  @  $I_C = 100 \text{ mA}$  ← use this!

max  $V_{BE} = .95 \text{ V}$  @  $I_C = 50 \text{ mA}$  ← kind of far away from 100 mA

$$\frac{V_{BE(max)}}{V_{BE(min)}} = \frac{.95 \text{ V}}{.85 \text{ V}} = \frac{?}{.9 \text{ V}}$$

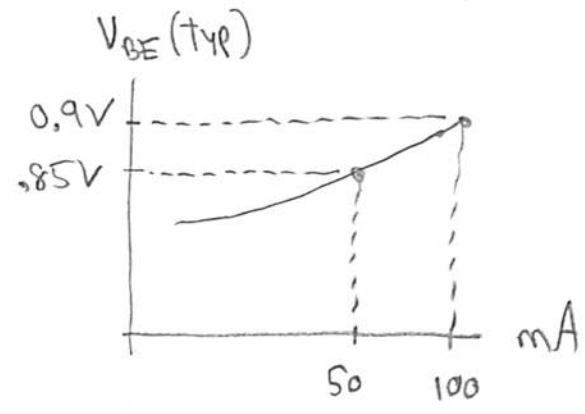$\underbrace{\hspace{2cm}}_{50 \text{ mA}} \qquad \underbrace{\hspace{2cm}}_{100 \text{ mA}}$



$$\Rightarrow ? = 1.006 \approx \underline{\underline{1.01 \text{ V}}}$$

SO,  $I_{OUT} = \frac{5 - 1.01}{\frac{40}{30 + 1} + 40} = .0966 \text{ A} = \underline{\underline{96.6 \text{ mA}}}$

$$V_{OUT} = (.0966)(40) = \boxed{3.865 \text{ V}}$$

Just below minimum acceptable value!

$$I_{PIN} = \frac{96.6 \text{ mA}}{30 + 1} = \boxed{3.12 \text{ mA}} \leftarrow \text{OK}$$


Need a slightly "tougher" transistor.   
 2N4401 has  $\beta_{min} = 100$  }  $I_C = \underline{\underline{150 \text{ mA}}}$    
 max  $V_{BE} = .95 \text{ V}$

5) a) want  $I_2 > 10\text{mA}$

$$I_2 = I_s - I_L > 10\text{mA}$$

$$I_2 = \frac{10 - 8.2}{100} - \frac{8.2 - 0}{100}$$

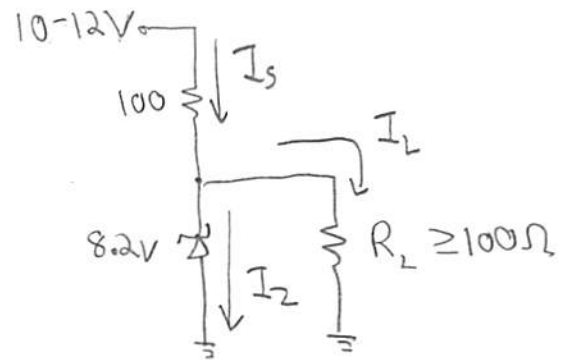
$$= 18\text{mA} - 82\text{mA} = \underline{\underline{-64\text{mA}}} \quad \boxed{\text{NO!}}$$



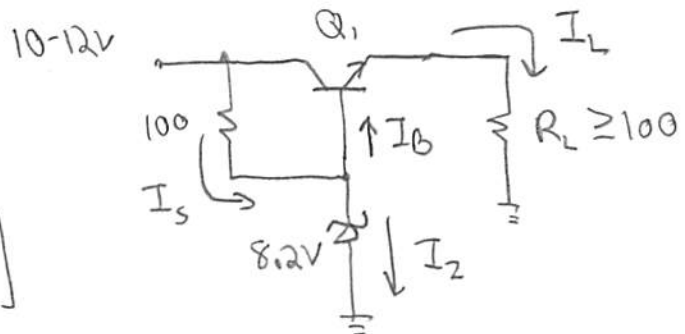b)  $I_2 = I_s - I_B > 10\text{mA}?$

$$= \frac{10 - 8.2\text{V}}{100\Omega} - \frac{1}{\beta + 1} \left[ \frac{8.2 - 0.7\text{V}}{100\Omega} \right]$$

$$= 18\text{mA} - 0.74\text{mA} = \underline{\underline{17.3\text{mA}}} \quad \boxed{\text{YES}}$$



c) Max  $I_L = \frac{8.2 - 0.7\text{V}}{100\Omega} = 75\text{mA}$  ← worst case load  $V_{BE} \approx 0.8\text{V}$  from 2N3904 data sheet  $\beta \approx 200$

$$P = i_B V_{BE} + i_C V_{CE}$$

$$= \frac{i_E}{\beta + 1} V_{BE} + \alpha i_E V_{CE}$$

$$i_E = \frac{8.2 - 0.8\text{V}}{100\Omega} = 74\text{mA}$$

$$= \frac{74\text{mA}}{201} \cdot 0.8\text{V} + 0.995 (74\text{mA}) \left[ 12 - (8.2 - 0.8) \right] \alpha = \frac{200}{201} = 0.995$$

$$= 0.3\text{mW} + 338.7\text{mW} \quad \text{← worst case supply}$$

$$= \underline{\underline{339\text{mW}}}$$

$$T_J = 25^\circ\text{C} + 339\text{mW} \times 200^\circ\text{C}/\text{W} = \underline{\underline{92.8^\circ\text{C}}} > 85^\circ\text{C} \quad \nabla$$

**YES, need a heat sink**

d)


Max Zener power dissipation  
is max  $I_z$

$$I_z = I_s - \underbrace{I_B}_0$$


$$= \frac{12 - 8.2V}{100\Omega} = .038A$$

$$P = (.038A)(8.2V) = \underline{0.312W} < \frac{1}{2} (1W) \checkmark$$

**YES, zener is OK!**

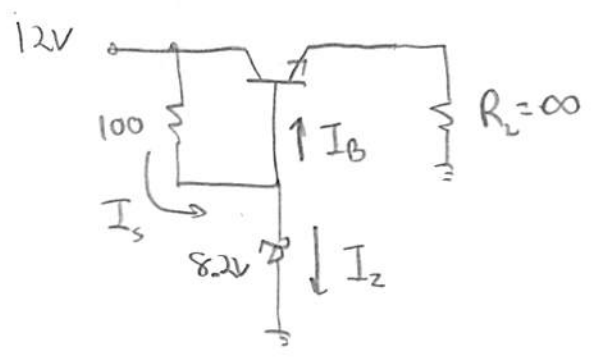

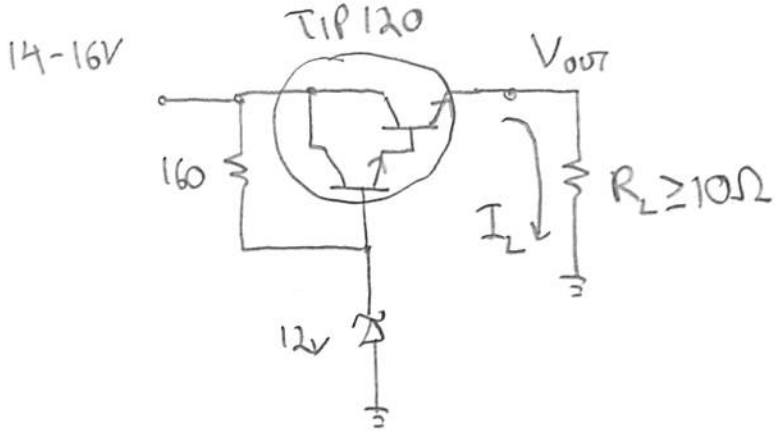6) a)  $I_z = I_s - I_B$   
 $= I_s - \frac{I_L}{\beta + 1}$



Darlington "quick" analysis:

$V_{BE} = 1.4V, \beta = 2500$

$\min I_s = \frac{14 - 12V}{160\Omega} = 12.5 \text{ mA}$

$\max I_B = \frac{1}{2501} \times \frac{(12 - 1.4)}{10\Omega} = \frac{1.06A}{2501} = \underline{0.42 \text{ mA}}$

$\Rightarrow \min I_z = 12.5 \text{ mA} - 0.42 \text{ mA} = \underline{12.08 \text{ mA}} > 10 \text{ mA} \checkmark$

**YES, zener is happy!**

b)  $P = I_B V_{BE} + I_C V_{CE}$

$= (0.42 \times 10^{-3}) (1.4) + \frac{2500}{2501} (1.06A) (16 - \overbrace{(12 - 1.4)}^{10.6V})$

$= 0.0006 + 5.7217 = \underline{5.72 \text{ W}}$

$T_J = 25^\circ\text{C} + 5.72 \text{ W} \times \underbrace{62.5^\circ\text{C/W}}_{\theta_{JA}} = \underline{382.5^\circ\text{C}}$

Yikes! Need a heat sink!

c)  $T_J = 25^\circ\text{C} + 5.72 \text{ W} \times (\theta_{JC} + \theta_{CS} + \theta_{SA}) < 85^\circ\text{C}$

$\Rightarrow \theta_{SA} < \frac{85 - 25^\circ\text{C}}{5.72 \text{ W}} - 1.92^\circ\text{C/W} - 0.5^\circ\text{C/W}$

$< \underline{8.07^\circ\text{C/W}}$  use  **$5^\circ\text{C/W}$  heat sink**



7)

(a) 2N3904:  $\Theta_{JA} = 200^\circ\text{C/W}$

$$\text{Max } P = \frac{150 - 25^\circ\text{C}}{200^\circ\text{C/W}} = \boxed{.625\text{W}}$$

$$\frac{150 - 50}{200} = \boxed{0.5\text{W}}$$

$$\frac{150 - 75}{200} = \boxed{.375\text{W}}$$

(b) TIP31:  $\Theta_{JA} = 62.5^\circ\text{C/W}$

$$\text{Max } P = \frac{150 - 75^\circ\text{C}}{62.5^\circ\text{C/W}} = 1.2\text{W}$$

$$\text{Actual } P = .75\text{W} \xrightarrow{\times 2} 1.5\text{W}$$

NO! TIP31 cannot handle .75W @  $T_A = 75^\circ\text{C}$

(c)  $T_J = 40^\circ\text{C} + 15\text{W} \times \left( \underbrace{3.125^\circ\text{C/W}}_{\Theta_{JC}} + \underbrace{.5^\circ\text{C/W}}_{\Theta_{CS}} + \Theta_{SA} \right) < 85^\circ\text{C}$

$$\Rightarrow \Theta_{SA} < \boxed{-.625^\circ\text{C/W}}$$

NOT possible!

(d) MJE3055:  $\Theta_{JC} = 1.67^\circ\text{C/W}$

$$40 + 15(1.67 + .5 + \Theta_{SA}) < 85^\circ\text{C}$$

$$\Rightarrow \Theta_{SA} < \boxed{0.83^\circ\text{C/W}}$$

YES!  
Need a really big heat sink  
(Fan might be necessary)


8)

a)

$$V_z - 0.7 \sim 6V$$

$$V_z \sim 6.7V$$

Choose  $V_z = 6.8V$

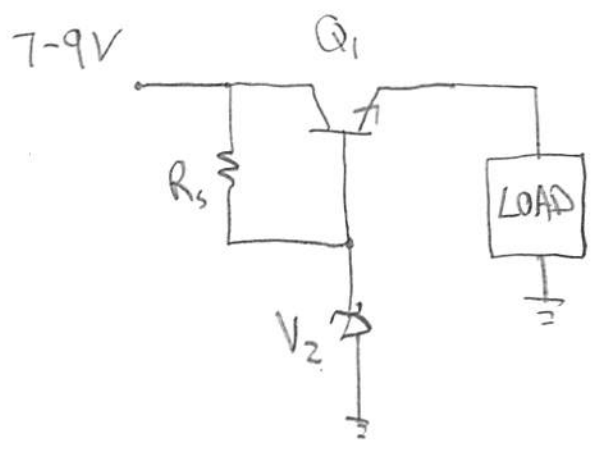

b)

	Max $I_c$	Power Rating No HS	Power Rating w/HS
--	-----------	-----------------------	----------------------

2N3904    200mA ✓

625mW ✓

TIP31    3A ✓

2W

MJE3055    10A ✓

75W

• Max  $I_L \sim 50mA$

• Max  $P \sim \frac{50mA}{101} (1.7) +$

$$\frac{100}{101} (50mA)(9-6.1)$$

$$= 143.9mW$$

Need > 287.8mW rating  $\times 2$

⇒ use  $2N3904$

other 2 transistors would work,  
but they are much larger than necessary!

c) want min  $I_z > 10mA$

$$I_z = \frac{7-6.8}{R_s} - \frac{50mA}{101} > 10mA \Rightarrow R_s < 0.01911k \overset{\times 0.95}{\sim} 18.1\Omega$$

Choose  $R_s = 18\Omega$

Max Power dissipation:  $\frac{(9-6.8)^2}{18} = 0.269W \overset{\times 2}{\sim} 0.538W$

Choose 1W (although 1/2W probably OK)


9)

(a) Choose Zener :

$$V_z - 1.4 \sim 6V$$

$$V_z \sim 7.4V$$

Choose  $V_z = 7.5V$

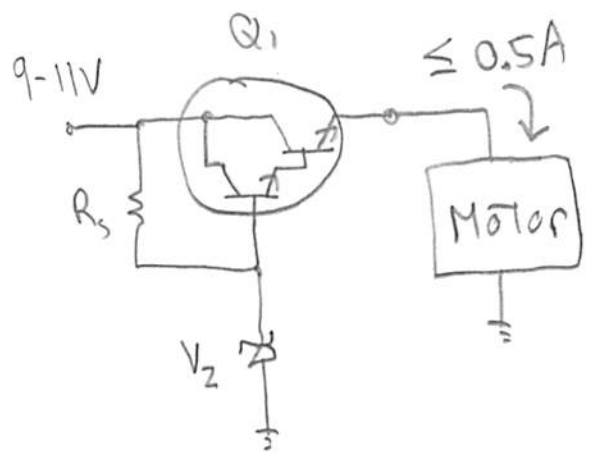

(b)

	Max $I_c$	$P_{rating}$ (No HS)	$P_{rating}$ (with HS)
KSP13	500mA ✓	625mW x	
TIP120	5A ✓	2W x	65W ✓
TIP140	10A ✓		125W ✓

Since max  $I_L = 0.5A$ ,

$$\text{max } P \sim \left( \frac{0.5A}{2501} \right) (1.4) + \frac{2500}{2501} (0.5A) \left( 11 - \overbrace{(7.5 - 1.4)}^{6.1V} \right)$$

$$= 0.0003W + 2.4490W \approx \underline{\underline{2.45W}} \xrightarrow{\times 2} \underline{\underline{4.9W}} \text{ Need rating}$$

Choose  $TIP120 + \text{heat sink}$

KSP13  $\rightarrow$  can't handle power



TIP140  $\rightarrow$  would work, but larger than necessary.

$$\textcircled{c} \quad T_J = 40^\circ\text{C} + 2.45\text{W} \times \left( \underbrace{1.92^\circ\text{C/W}}_{\Theta_{JC}} + \underbrace{.5^\circ\text{C/W}}_{\Theta_{CS}} + \Theta_{SA} \right) < 85^\circ\text{C}$$

$$\Theta_{SA} < \frac{85 - 40^\circ\text{C}}{2.45\text{W}} - 1.92^\circ\text{C/W} - .5^\circ\text{C/W}$$

$$< 15.95^\circ\text{C/W} \quad \boxed{\text{Choose } 12^\circ\text{C/W}}$$

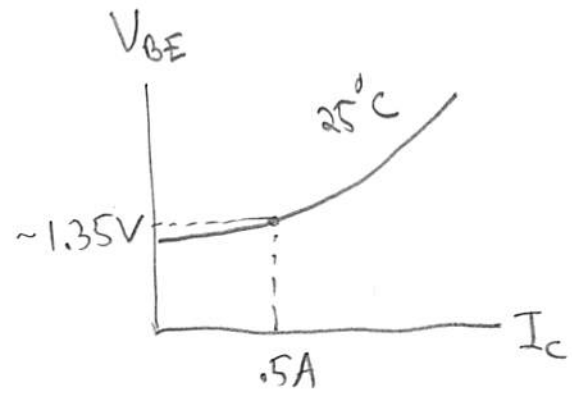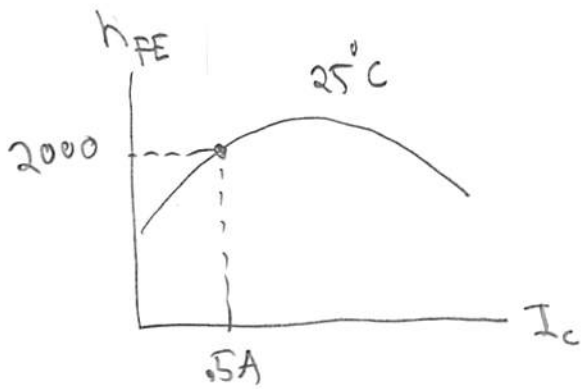$\textcircled{d}$  TIP120 data sheet (OK to use  $25^\circ\text{C}$  curves, since hand calculations are estimates)



$$I_2 = I_s - I_B > .01\text{A}$$

$$\frac{9 - 7.5}{R_s} - \frac{.5\text{A}}{2001} > .01\text{A} \Rightarrow R_s < 146.3\Omega \xrightarrow{\times .95} 139\Omega$$

$$\text{Choose } \boxed{R_s = 130\Omega}$$

$$\text{Max } P: \frac{(11 - 7.5)^2}{130} = .094\text{W} \xrightarrow{\times 2} .19\text{W rating or higher}$$

$$\boxed{1/4\text{W rating is fine}}$$

10)

• Want  $6.2 \times \frac{R_2}{R_1 + R_2} \sim 5V$

$$\frac{6.2}{5} = \frac{R_1 + R_2}{R_2} = \frac{R_1}{R_2} + 1$$

$$\Rightarrow \frac{R_1}{R_2} = 0.24 \quad (1)$$

• Also want  $\frac{6.2V}{R_1 + R_2} < 1mA \Rightarrow R_1 + R_2 > \underline{6.2K} \quad (2)$

Put (1) into (2):  $0.24R_2 + R_2 > 6.2K$

$$R_2 > 5K$$

Power ratings:

$$i = \frac{6.2V}{1.2K + 5.1K} = 0.98mA$$

$$P_1 = (0.98mA)^2 (1.2K) = 1.15mW$$

$$P_2 = (0.98mA)^2 (5.1K) = 4.9mW$$

$\frac{1}{4}W$  is fine

Try  $R_2 = \underline{5.1K} \rightarrow R_1 = 0.24 \times 5.1 = 1.22K$

$$\Rightarrow \underline{R_1 = 1.2K}$$

• Check  $V_{out}$ :  $V_{out} = 6.2 \times \frac{5.1K}{1.2K + 5.1K} = \underline{5.02V}$  ← within 0.4% of 5V! 😊

•  $R_s$ : Assuming amplifier inputs draw negligible current:


$$\frac{8 - 6.2}{R_s} - \frac{6.2}{1.2K + 5.1K} > 10mA$$

$$R_s < 1639K \xrightarrow{\times 0.95} 156\Omega$$

Choose  $R_s = \underline{150\Omega}$

Power:  $\frac{(12 - 6.2)^2}{150} = 224mW \xrightarrow{\times 2} 448mW$

$\frac{1}{2}W$  rating

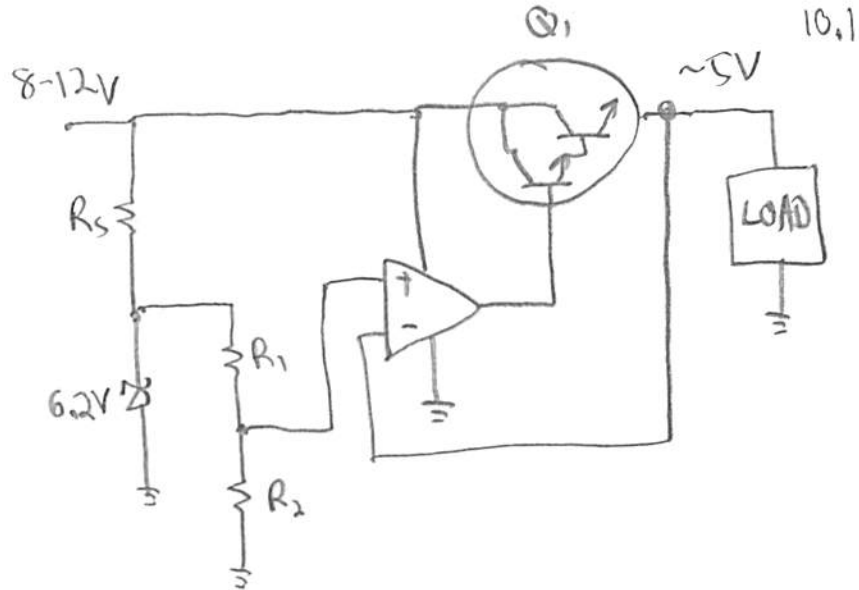

(b)

• For  $R_1$  and  $R_2$ :

Want  $1.235V = 9 \times \frac{R_2}{R_1 + R_2}$

$$\frac{R_1 + R_2}{R_2} = \frac{9}{1.235}$$

$$1 + \frac{R_1}{R_2} = \frac{9}{1.235} \rightarrow \frac{R_1}{R_2} = 6.2875 \quad (1)$$

• Also,  $\frac{9V}{R_1 + R_2} \leq 1mA \rightarrow R_1 + R_2 \geq 9K \quad (2)$

Put (1) into (2):  $6.2875 R_2 + R_2 \geq 9K$

$$R_2 \geq 1.235K$$

Some combinations:

Power ratings:

$$i = \frac{9.025V}{1.3K + 8.2K} = .95mA$$

All OK, but  $R_2 = 1.3K$  is closest.

$$P_1 = (.95mA)^2 (8.2K) = 7.4mW$$

$$P_2 = (.95mA)^2 (1.3K) = 1.2mW$$


$\frac{1}{4}W$  is fine

•  $R_s$ :  $\frac{12 - 1.235}{R_s} \sim 1mA$

$$\rightarrow R_s \sim 10.77K \Rightarrow R_s = 10K$$

Power<sup>2</sup>:  $Max P = \frac{(15 - 1.235)^2}{10K} = 18.95mW$

$\frac{1}{4}W$  is fine

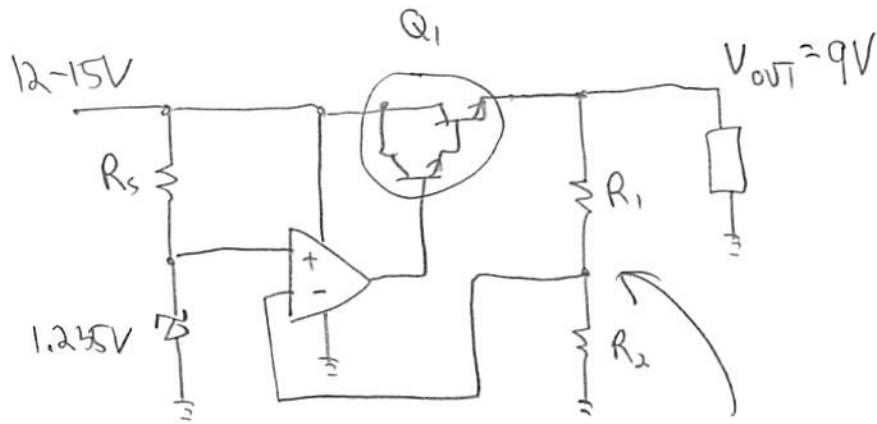

$$1.235 = V_{OUT} \frac{R_2}{R_1 + R_2}$$

$$\rightarrow V_{OUT} = 1.235 \left(1 + \frac{R_1}{R_2}\right)$$