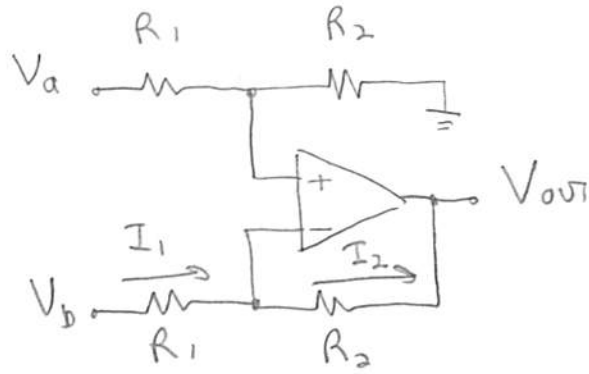


ECE 363
HW2 Solns

Total = 100 pts



(1) (a) $V_- = V_+ = V_a \frac{R_2}{R_1 + R_2}$ (1)

KCL at node (-):

$$I_1 = I_2 + 0$$

$$\frac{V_b - V_-}{R_1} = \frac{V_- - V_{out}}{R_2} \rightarrow \frac{V_b}{R_1} - \left(\frac{1}{R_1} + \frac{1}{R_2}\right)V_- = -\frac{V_{out}}{R_2}$$

$$V_{out} = -\frac{R_2}{R_1}V_b + R_2 \left(\frac{R_1 + R_2}{R_1 R_2}\right)V_- = -\frac{R_2}{R_1}V_b + \frac{R_1 + R_2}{R_1} V_a \frac{R_2}{R_1 + R_2}$$

$$\Rightarrow \boxed{V_{out} = \frac{R_2}{R_1}(V_a - V_b)}$$


(b) $\left. \begin{matrix} R_1 = 10K \\ R_2 = 100K \end{matrix} \right\} V_{out} = 10(V_a - V_b)$

$$V_a = 3 + 0.1 \text{rect}(t/T)$$

$$V_b = 3 - 0.1 \text{rect}(t/T)$$


$$V_a - V_b = 0.2 \text{rect}(t/T)$$

SO, $V_{out} = 2 \text{rect}(t/T)$

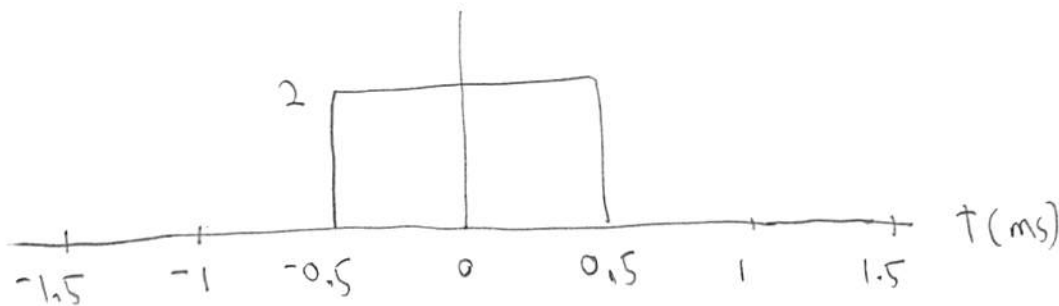


2

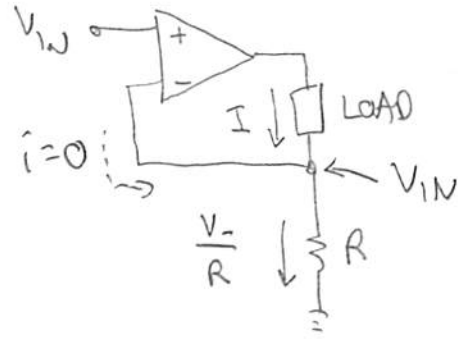
(a) $V_- = V_+ = V_{IN}$
 $I_{LOAD} = \frac{V_-}{R} = \boxed{\frac{V_{IN}}{R}}$



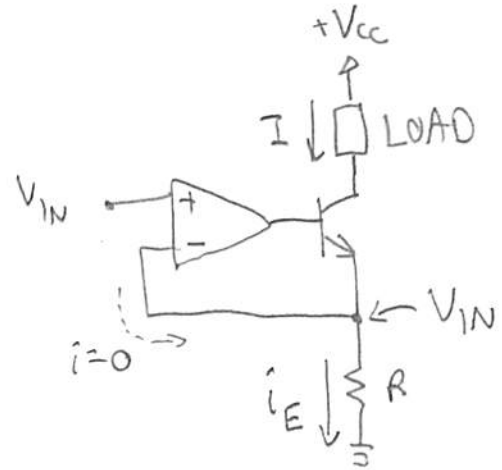(b) $V_- = V_+ = V_{IN}$
 $\hat{i}_E = \frac{V_{IN}}{R}$
 $\hat{i}_{LOAD} = \hat{i}_C = \alpha \hat{i}_E = \boxed{\alpha \frac{V_{IN}}{R}}$



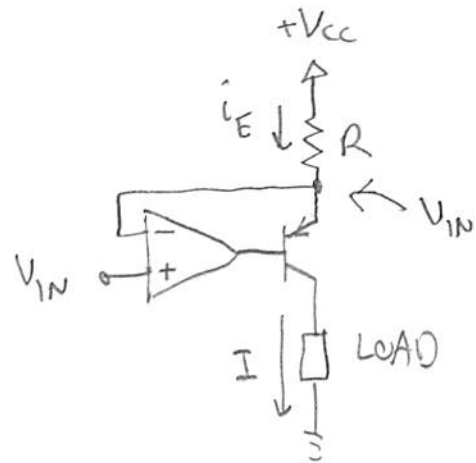(c) $V_- = V_+ = V_{IN}$
 $\hat{i}_E = \frac{V_{CC} - V_{IN}}{R}$
 $\hat{i}_{LOAD} = \hat{i}_C = \alpha \hat{i}_E = \boxed{\alpha \frac{V_{CC} - V_{IN}}{R}}$



This is a little tricky to use, since $V_{IN} = 0$ (no signal) produces large current!

3


(a) $V_- = V_+ = 0$

KCL at node (-):

$$\frac{V_{IN} - 0}{R} = C \frac{d}{dt} (0 - V_{OUT})$$

$$\Rightarrow \frac{dV_{OUT}}{dt} = -\frac{1}{RC} V_{IN} \Rightarrow$$




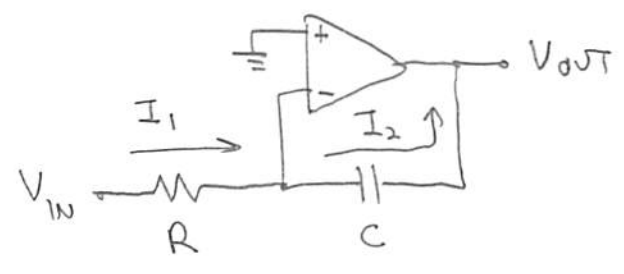
$$V_{OUT} = -\frac{1}{RC} \int V_{IN} dt$$



(b) $R = 100k$
 $C = 100nf$ $\left\{ \frac{1}{RC} = \frac{1}{10^5 \times 10^{-7}} = 100 s^{-1} \right.$

$$\Rightarrow V_{OUT} = -100 \int V_{IN} dt$$

$\int V_{IN} dt =$ Area under curve

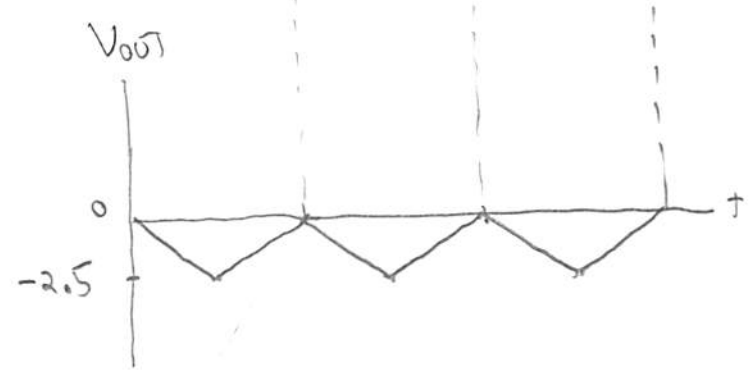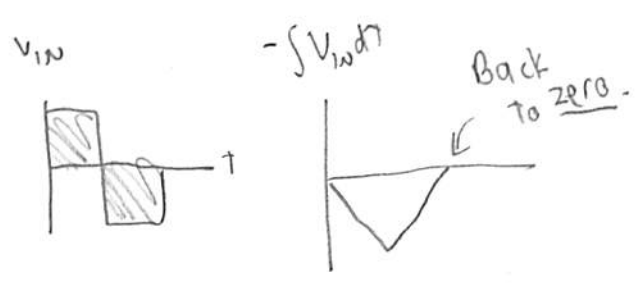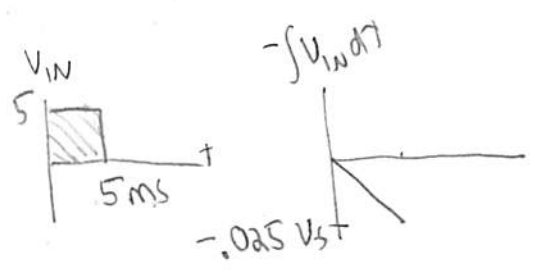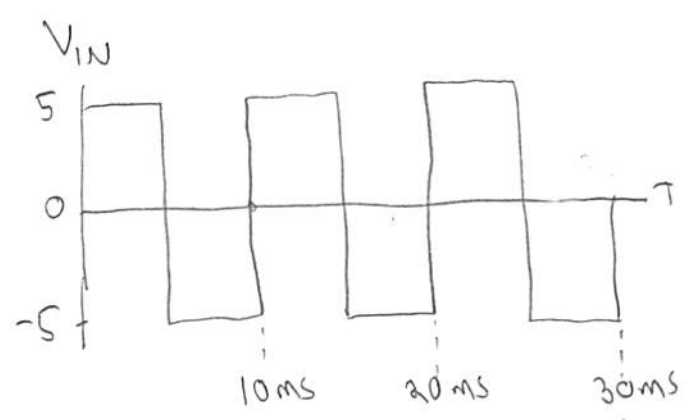


$$Peak = -100 \int V_{IN} dt = -100 (0.25) = \underline{\underline{-2.5V}}$$



④ a) $V_+ = 0 = V_-$

$V_{out} = 0 - IR$
 \uparrow
 $C \frac{d}{dt}(V_{in} - 0)$

$V_{out} = -RC \frac{dV_{in}}{dt}$

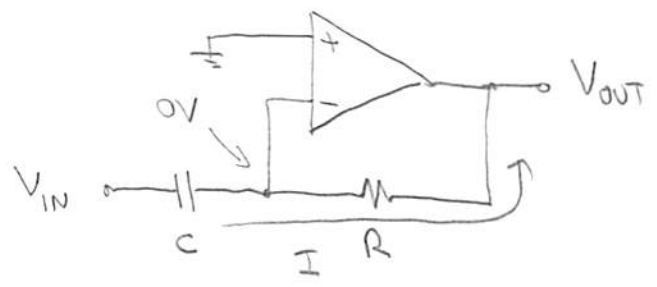

b) Derivative is the slope of curve

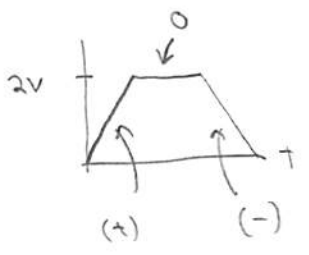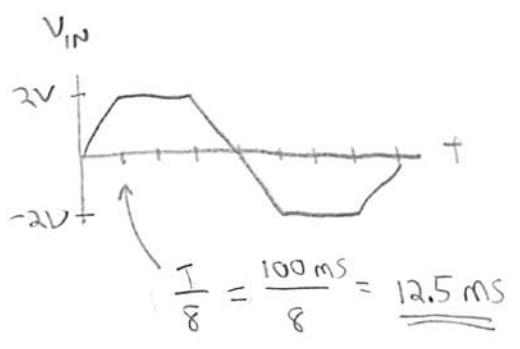



$Slope = \frac{2V}{0.0125s} = 160 V/s$

$Slope = -\frac{2V}{0.0125s} = -160 V/s$



$RC = 10^5 \times 10^{-7} = 0.01s$

$-RC \frac{dV}{dt} = -1.6V$

$-RC \frac{dV}{dt} = 1.6V$

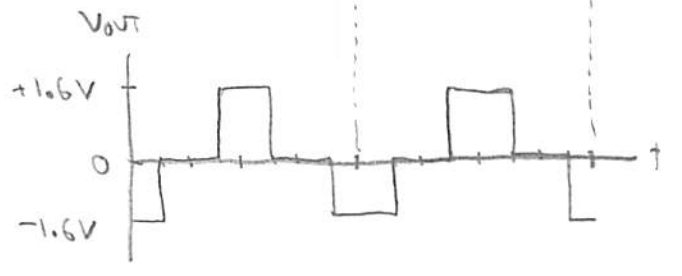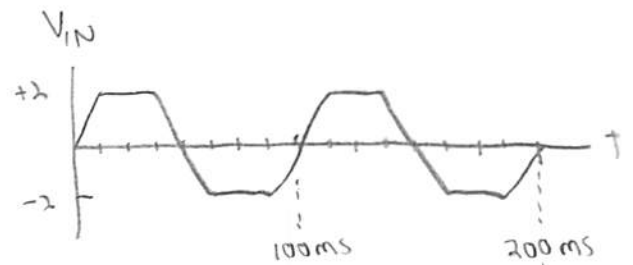

5 a

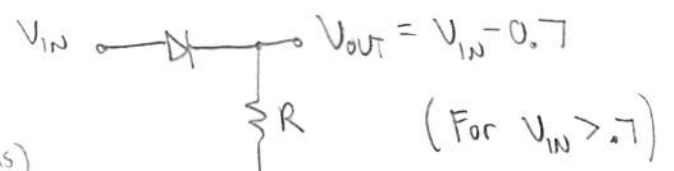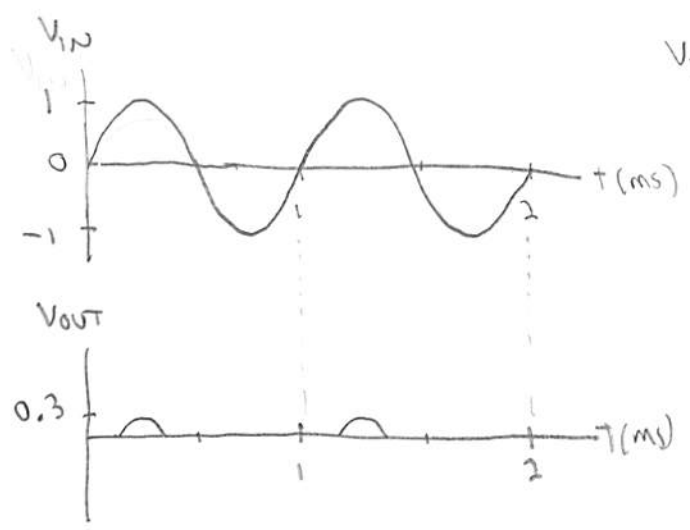

b


$V_{IN} \geq 0$:

$V_+ = V_{IN} = V_-$

Current through R

is $I = \frac{V_{IN}}{R}$

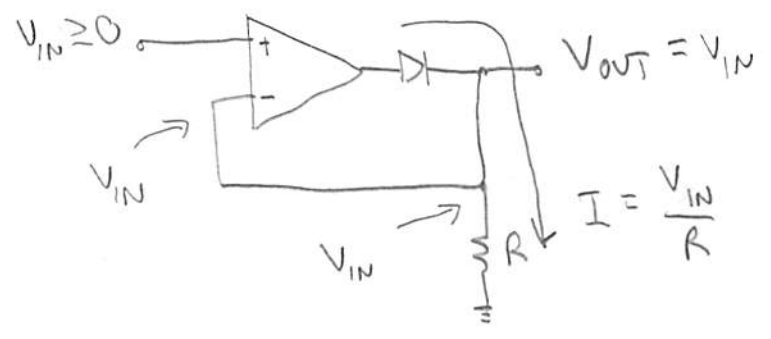$\rightarrow V_{OUT} = IR = V_{IN}$ when $V_{IN} \geq 0$




$V_{IN} < 0$:

$V_+ = V_{IN} = V_- ?$



If this were true, then current must flow against the diode!

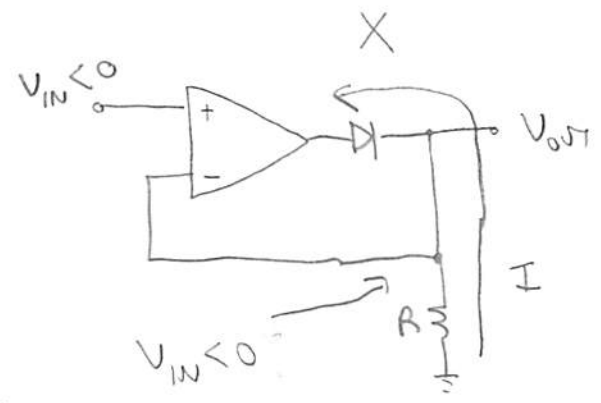\rightarrow Since $I = 0$, $V_{OUT} = 0$ when $V_{IN} < 0$



NOTE: Golden Rules are violated when $V_{IN} < 0$ because diode blocks (-) feedback loop.

c

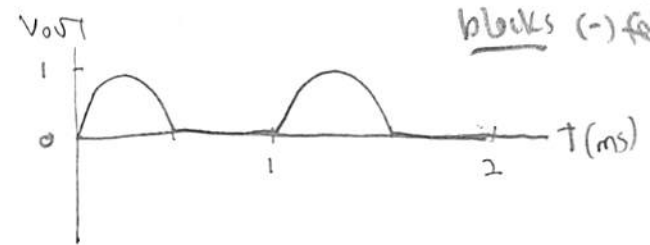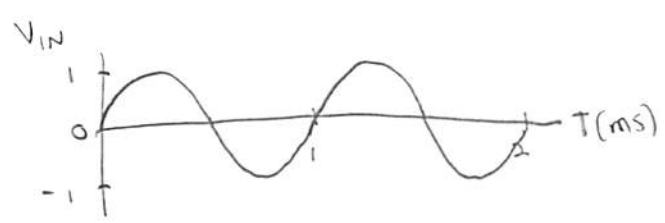


6

a) $V_- = V_+ = V_{IN}$

$$I = \frac{V_{IN} - 0}{10K} = \frac{V_{OUT} - V_{IN}}{91K}$$

$$\frac{91K}{101K} V_{IN} = V_{OUT} - V_{IN}$$
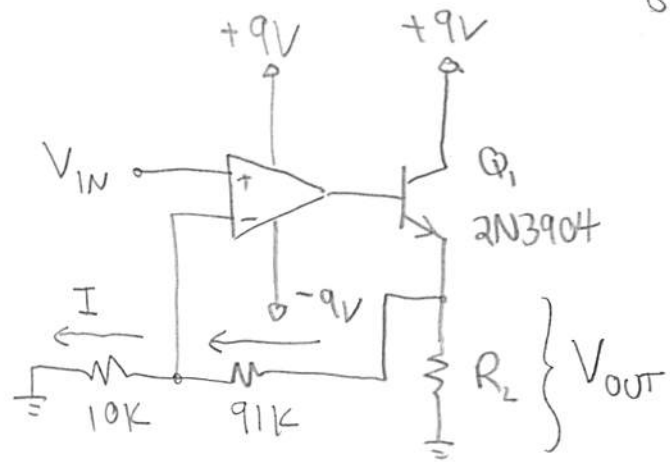
$$\frac{V_{OUT}}{V_{IN}} = (1 + 9.1) = \boxed{10.1}$$



b)

$$V_{OUT} = 10.1 \times 0.5 = \boxed{5.05V}$$


$$I_{Load} = \frac{5.05V}{100\Omega} = \boxed{50.5mA}$$

c)

2N3904 data sheet: $h_{FE} = 200$ (typ)

$= 60$ (min) @ 50mA

From table

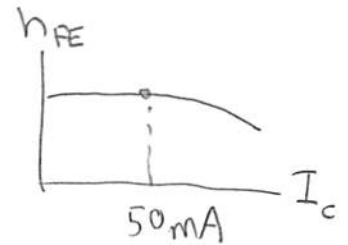

$$\text{Typical op amp current} = \frac{50.5mA}{200+1} = \boxed{0.25mA}$$

$$\text{NOTE: Worst case op amp current} = \frac{50.5mA}{60+1} = 0.83mA$$

OK to ignore current in 91K resistor (negligible)

d) For Q_1 , $P = I_B V_{BE} + I_C V_{CE}$

$$= (0.83mA)(0.78V) + \frac{200}{201} (50.5mA)(9 - 5.05)$$

$$= \boxed{199.1mW}$$

Data sheet

Typical $V_{BE} = 0.78V$ at $\beta = 200$ $I_C = 50mA$

e) Need $> 199.1mW \times 2 = \underline{398.2mW}$ rating.

2N3904 has 625mW rating \rightarrow NO heat sink needed!

7


(a) Require

$$V_{cc} > V_{out} + V_{CE,sat} + 2$$

$$> 12.3 + 0 + 2$$

$$> \underline{\underline{14.3V}}$$


Head room

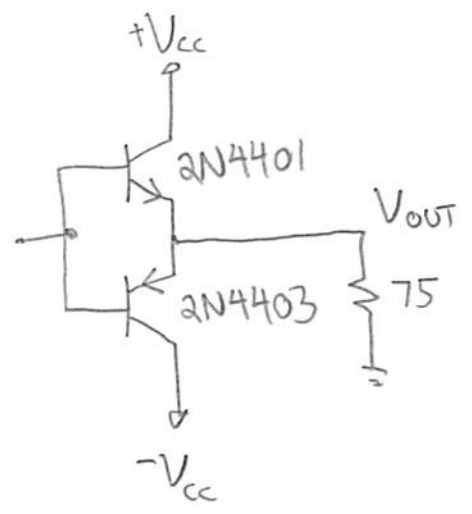

Choose $V_{cc} = 15V$





(b)
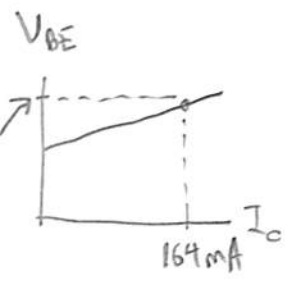
$$\text{Max } I_L \sim \frac{12.3V}{75\Omega} = \underline{\underline{164mA}} \rightarrow V_{BE} \cong 0.78V$$



$$\Rightarrow V_{out} = 13 - 0.78 = \underline{\underline{12.22V}}$$
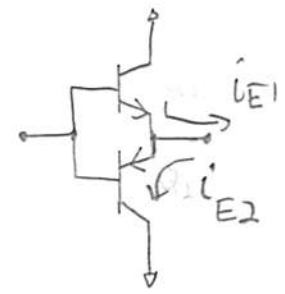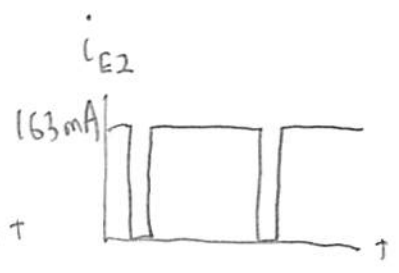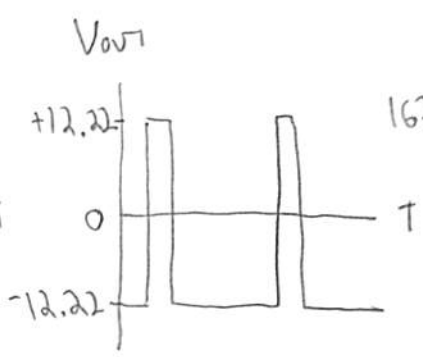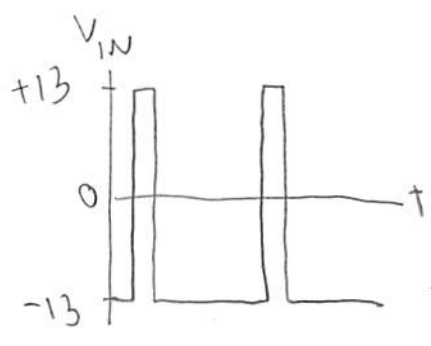
$$I_{Load} = \frac{12.22V}{75\Omega} = 0.163 = \underline{\underline{163mA}}$$



© 2N4401 data sheet: $\left. \begin{matrix} \max V_{BE} = 0.95V \\ \min h_{FE} = 100 \end{matrix} \right\} I_c = 150mA$

2N4401; worst case $V_{Load} = 13 - .95 = \underline{12.05V}$

$I_{Load} = 160.7mA$

$I_B = \frac{160.7}{100+1} = \underline{1.59mA}$

• Q_1 is on 25% of time:

$\langle P \rangle = 0.25 [i_B V_{BE} + i_c V_{CE}] = 0.25 [(1.59mA)(0.95V) + \frac{100}{101} (160.7mA)(15-12.05V)]$
 $= \boxed{117.7mW}$

• Q_2 is on 75% of time:

$\langle P \rangle = 0.75 [|i_B V_{BE}| + |i_c V_{CE}|] = 0.75 [(1.59mA)(.95V) + \left| \frac{100}{101} (160.7mA)(-15+12.05) \right|]$
 $= \boxed{353.1mW}$


$\langle P \rangle_{avg} = 117.7mW + 353.1mW = 470.8mW$

$\langle P \rangle_{avg} = 470.8mW$


The average power is high but because the high V

8

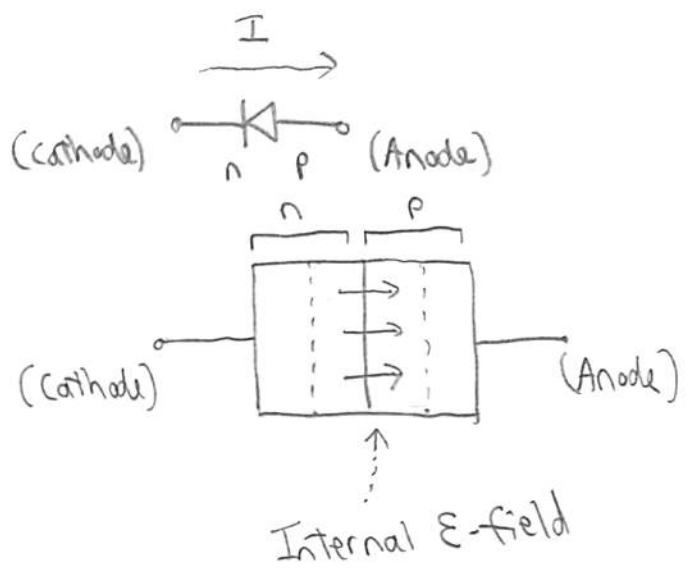(a) Photodiode current flows from cathode to anode.



For positive V_{out} :

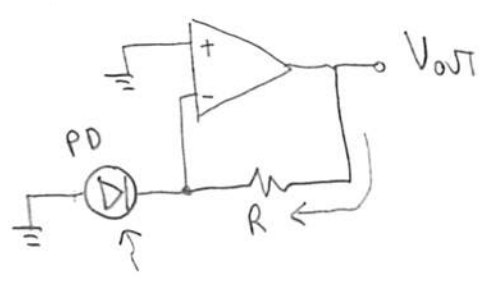

(b) BPV22F data sheet: $\lambda = 950\text{nm} \rightarrow I = 9\mu\text{A} @ E = 0.1\text{mW/cm}^2$

want $V_{out} = (9\mu\text{A}) \times R \geq 5\text{V}$

$R \geq 555.6\text{K}$

choose $R = 560\text{K}$

(c) $\lambda = 850\text{nm} \rightarrow S \sim 0.35$

$\Rightarrow V_{out} = 0.35 \times 9\mu\text{A} \times 560\text{K} = 1.76\text{V}$

NOTE: 620K is safer choice due to $\pm 5\%$ tolerance

15.13 mV


→ 2N4401 and TIP31 are "bigger" transistors (higher I_c).

⇒ Since 2N3904 works, and is the "smallest"

transistor, choose the 2N3904 and 2N3906
npr ppp

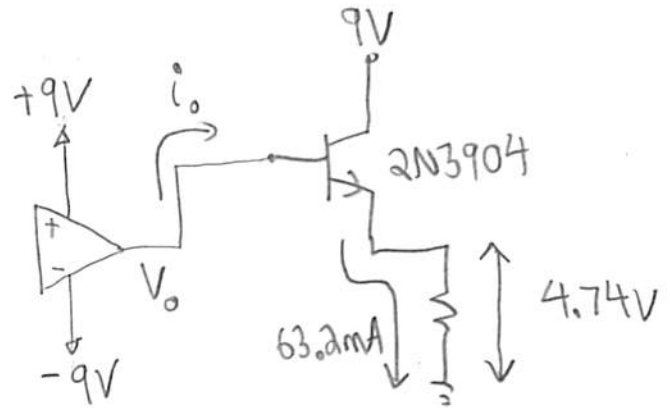d)
$$\text{Max } V_o = 4.74 + V_{BE}$$

$$\text{Max} = 0.95V \text{ for } I_c = 50mA$$



→
$$\text{Max } V_o = \underline{\underline{5.69V}}$$

$$\text{Max } i_o = \frac{63.2mA}{\beta_{min} + 1} = \frac{63.2mA}{60 + 1} = \underline{\underline{1.04mA}}$$


 at $I_c = 50mA$

Op amp head room = $9 - 5.69 = \underline{\underline{3.31V}}$

LF411:
$$\text{Max } V_o = 15 - 3.31 = 11.69V$$

$$\times 2 \rightarrow 23.4V_{pp}$$
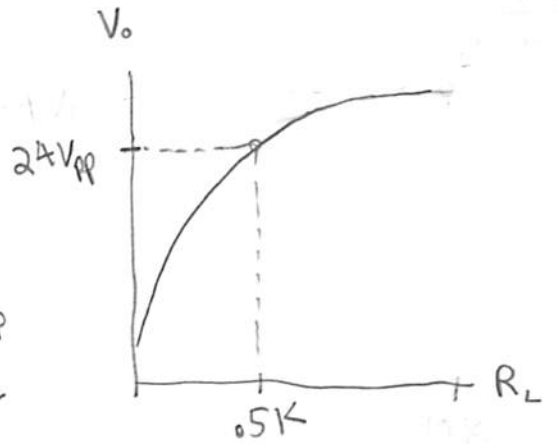
$$\text{Max } i_o = \frac{11.69V}{.5K} = 23.4mA > 1.04mA \checkmark$$



Op amp is OK! 😊

e) For non-inverting op amp,

$$G = 1 + \frac{R_2}{R_1}$$

$$G_{dB} = 20 \log_{10}(G) \Rightarrow G = 10^{\frac{12dB}{20}} = 4$$

$$1 + \frac{R_2}{R_1} = 4$$

choose $R_1 = 1K$
 $R_2 = 3K$ ← 3.3K is fine