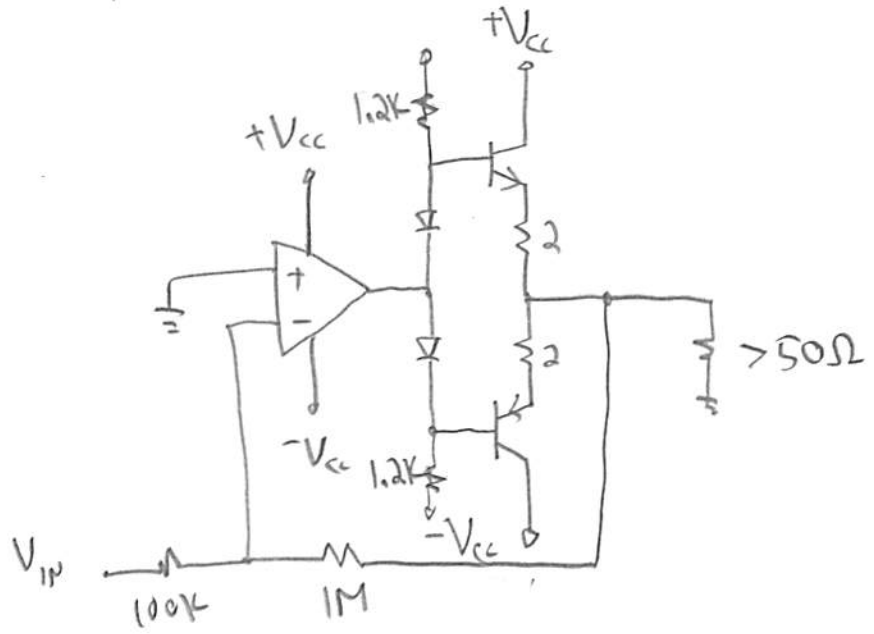


① a) $G = -\frac{1M}{100K} = \underline{\underline{-10}}$

Max $V_{out} = -10 \cdot (\pm 0.5V_p)$
 $= \underline{\underline{\pm 5V}}$

$I_{out} = \frac{5V}{50\Omega} = \underline{\underline{0.1A}}$



b) want $i_{diode} = \frac{V_{cc} - V_{BI,max}}{1.2K} - i_{BI,max} > 1mA$

$V_{BI,max} = 5V + (0.1A)(2\Omega) + 0.7 = \underline{\underline{5.9V}}$

$i_{BI,max} = \frac{0.1A}{100\mu} = \underline{\underline{99mA}}$



$\Rightarrow \frac{V_{cc} - 5.9}{1.2K} - 99mA > 1mA$

$V_{cc} > 8.29V \Rightarrow$ choose $\underline{\underline{V_{cc} = 9V}}$

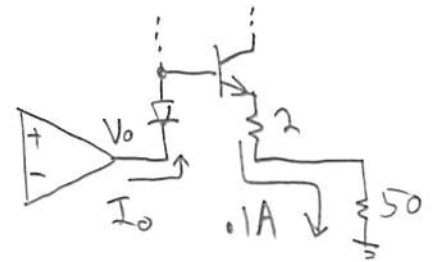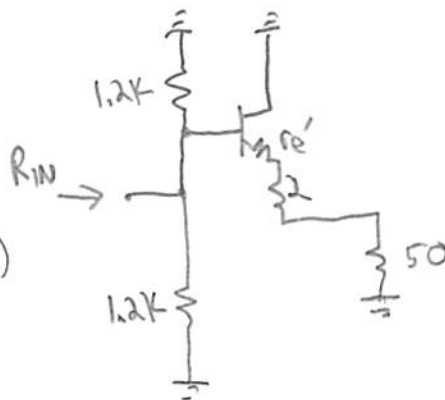c) $V_o = 0.1A \cdot (50 + 2) + 0.7 - 0.7 = \underline{\underline{5.2V}}$

$I_o = \frac{V_o}{R_{in}}$

$R_{in} \approx 1.2K // 1.2K // (\beta + 1)(5\Omega)$
 $= 1200 // 1200 // 5252$
 $= \underline{\underline{538.5\Omega}}$




$\Rightarrow I_o = \frac{5.2V}{538.5\Omega} = \underline{\underline{9.7mA}}$

Op amp head room: $9 - 5.2 = \underline{\underline{3.8V}}$

For $V_{cc} = 15V \rightarrow V_o = 15 - 3.8 = 11.2V$
($22.4V_{pp}$)
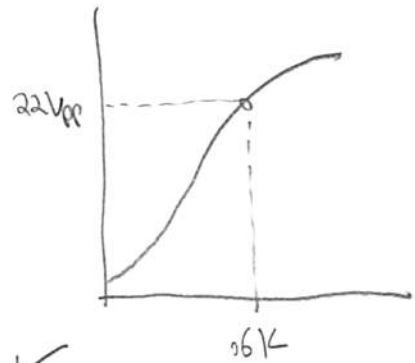
$$i_o = \frac{11.2V}{.6K} = 18.7mA > 9.7mA \checkmark$$



YES, op amp is OK! 😊


2

(a) For sine wave,

$$P = \frac{1}{2} \frac{V_{max}^2}{R} \quad .4W$$

$$\rightarrow V_{max} = \sqrt{0.4W \times 2 \times 32\Omega} = \boxed{5.06V}$$
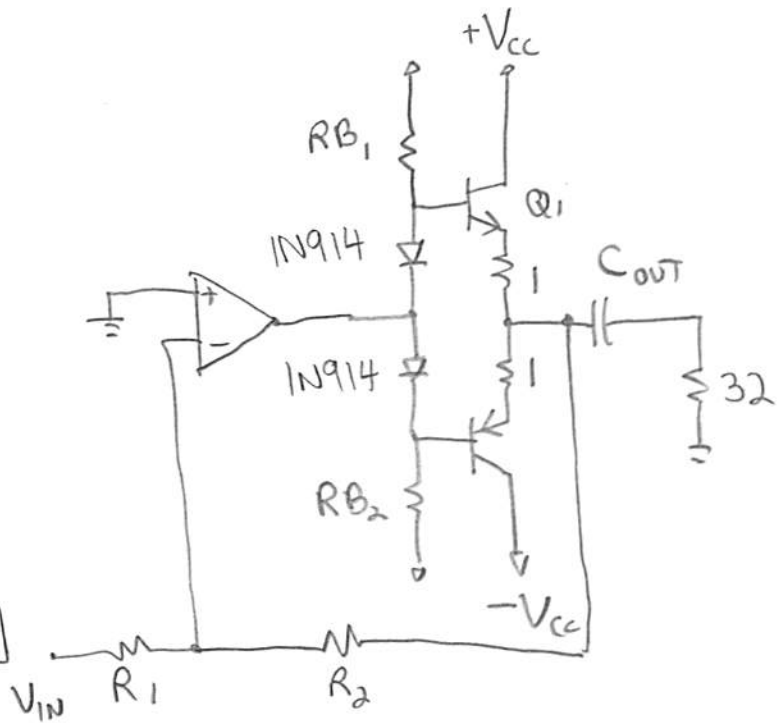
$$i_{max} = \frac{5.06V}{32\Omega} = \boxed{158mA}$$




(b)

$$V_{cc} > V_{L,max} + (i_{max} \times 1\Omega) + V_{CE,sat} + 2$$

\uparrow \uparrow \uparrow \uparrow
 5.06V \uparrow 0V for now \uparrow Head room
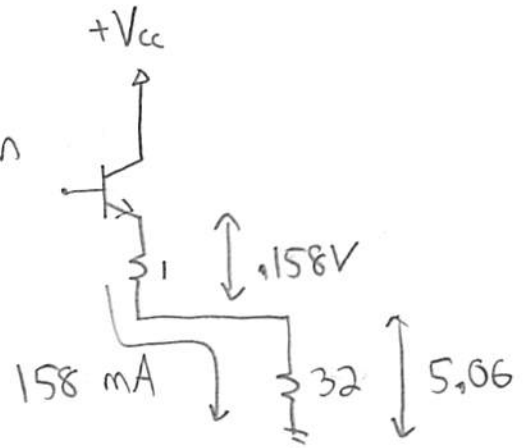
$$V_{cc} > 5.06 + .158 + 2 = \boxed{7.22V}$$



Choose $V_{cc} = 9V$ ← May need to change this later.

$$\textcircled{c} \text{ Max } I_c \cong 160mA \xrightarrow{\times 2} 320mA \text{ rating} \quad P \sim \frac{.158A}{101} (0.7V) + .99 (.158A)(3.78V)$$

$$\text{Max } V_{CE} = 9 - (-5.22) = 14.22 \xrightarrow{\times 2} 28V \text{ rating} = \underline{0.592W}$$

	Max I_c	Max V_{CE}	P_{rating} (no Hs)	P_{rating} (w/Hs)	
2N3904	200mA X	40V ✓	.625W X	1.5W ✓	$\downarrow \times 2$ <u>> 1.18W rating</u>

2N4401 600mA ✓ 40V ✓ .625W X 1.5W ✓

Need to find Θ_{SA} : $T_J = 25^\circ C + .592W \times (83.3 \frac{^\circ C}{W} + 0.5 \frac{^\circ C}{W} + \Theta_{SA}) < 85^\circ C$


$\rightarrow \Theta_{SA} < \boxed{17.6^\circ C/W}$ ✓

Choose $\boxed{2N4401 + 2N4403}$

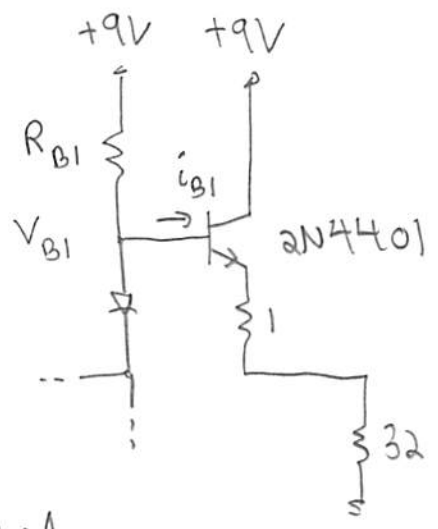d) Choose R_{B1} :

$i_{Diode} = \frac{9 - V_{BE,max}}{R_{B1}} - i_{BE,max} > 1mA$

$V_{BE,max} = (1.158A)(33\Omega) + \underbrace{0.95V}_{\text{Max } V_{BE} @ I_C = 150mA}$
 $= \underline{6.16V}$



$i_{BE,max} = \frac{158mA}{100 + 1} = 1.56mA$
 \uparrow
 $\beta_{min} @ 150mA$

$\frac{9 - 6.16V}{R_{B1}} - 1.56mA > 1mA$



$\rightarrow R_{B1} < 1.11K$ Choose $\boxed{R_{B1} = 1.1K} = R_{B2}$

e) $V_o = 5.21 + V_{BE,max} - V_F$
 \uparrow max = 0.95 \uparrow min = 0.62V

$= \underline{5.54V}$ min β

$R_{in} = 1.1K // 1.1K // (100+1)(33\Omega)$
 $= \underline{472\Omega}$

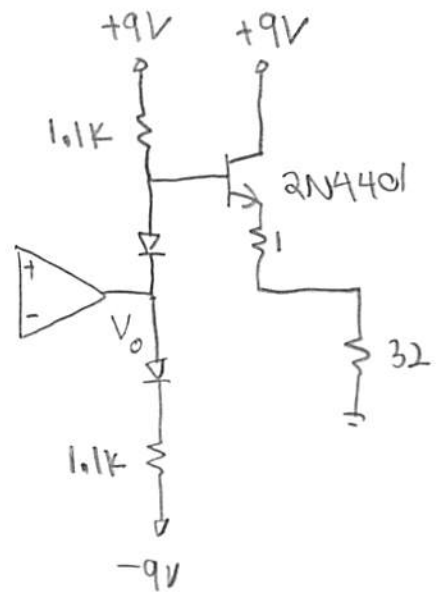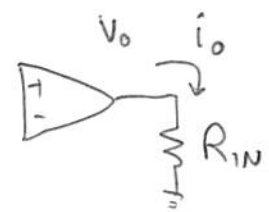$i_o = \frac{5.54V}{472\Omega} = \underline{11.7mA}$




$$\text{op amp head room} = 9 - 5.54 = 3.46\text{V}$$

$$V_{cc} = 15\text{V} \rightarrow V_o = 15 - 3.46 = 11.54\text{V}$$

$$i_o = \frac{11.5\text{V}}{.7\text{K}} = \underline{\underline{16.5\text{mA}}} > 11.7\text{mA}$$
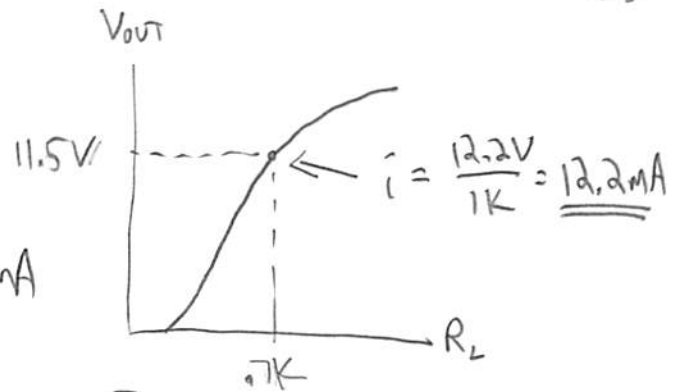
$$\Rightarrow V_{cc} = 15 - 0.7 \times 16.5 = 8.775\text{V}$$



YES, op amp is OK! 😊

Ⓕ Since $P_{\text{Load}} \leq 400\text{mW}$

$V_{\text{Load}} \leq 5.06\text{V}$

$$|V_{\text{Load}}| = |G V_{iN, \text{max}}| \leq 5.06\text{V}$$

$$|G| \leq \frac{5.06\text{V}}{0.5\text{V}} = \underline{\underline{10.12}}$$

using $|G| = \frac{R_2}{R_1}$ and $Z_{iN} = R_1 \geq 10\text{K}$

Choose $\boxed{R_1 = 11\text{K}}$
 $\boxed{R_2 = 110\text{K}} \leftarrow G = \frac{110\text{K}}{11\text{K}} = 10 \checkmark$

Ⓖ Lowest freq of interest = 200Hz


$$\left| \frac{1}{j\omega C_{\text{out}}} \right| = \frac{1}{2\pi(200\text{Hz})C_{\text{out}}} < \frac{1}{10^4 32\Omega} \Rightarrow C_{\text{out}} > 2.49 \times 10^{-4}\text{F}$$

$$> 249 \times 10^{-6}\text{F}$$

Choose $\boxed{C_{\text{out}} = 470\mu\text{F}}$

3

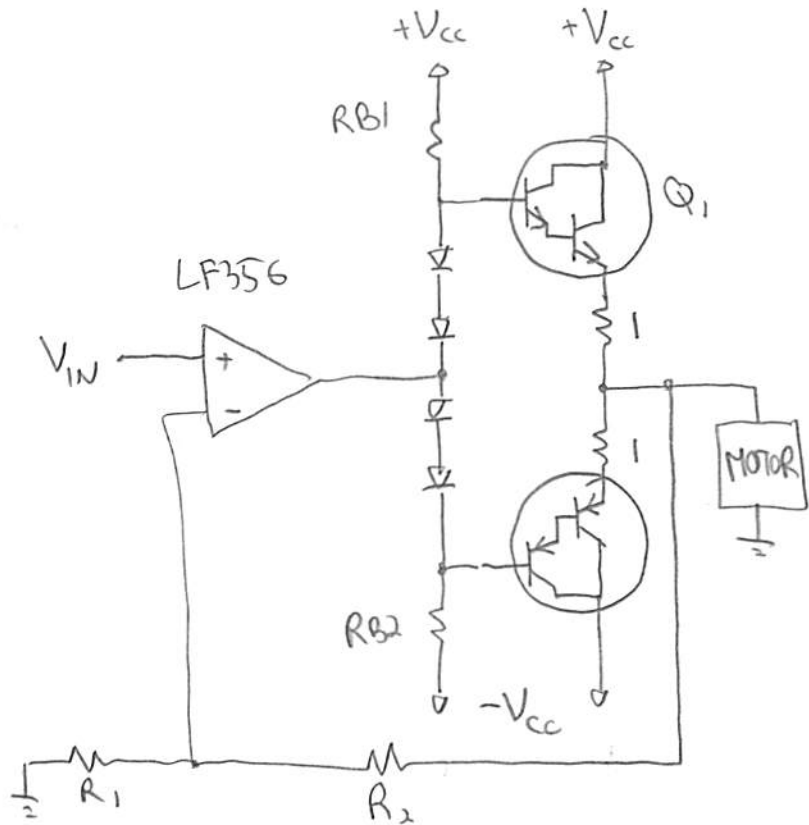
- a) Max $V_{Load} = 6V$
 $I_{Load} = 900mA$



b)
$$V_{cc} > \underbrace{V_{Load}}_{6V} + \underbrace{I_{Load} \times 1\Omega}_{0.9V} + \underbrace{V_{CE,sat}}_{0.7V \text{ for Darlington}} + 2V = 9.6V$$

Choose $V_{cc} = 12V$

Need $> 1.8A$ rating

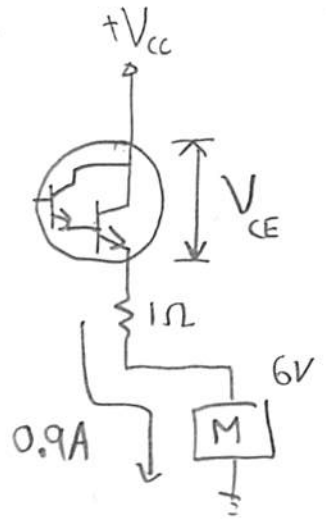

c)
$$\text{Max } V_{CE} = 12 - (-6.9) = 18.9V$$

$$P = \frac{0.9A}{2501} (1.4V) + \frac{2500}{2501} (0.9A)(5.1V) = 4.64W!$$

$\frac{\text{Max } I_c}{800mA \times}$	$\frac{\text{Max } V_{CE}}{60V \checkmark}$	$\frac{P_{Rating} \text{ (no HS)}}{2W \times}$	$\frac{P_{Rating} \text{ (w/HS)}}{50W \checkmark}$	$\times 2 \rightarrow 9.28W \text{ rating or higher}$
--	---	--	--	---

MPSA29

TIP110

2A

60V ✓

2W X

50W ✓

This works!

Typical $h_{FE} = 2800 \checkmark$

13.37

Heat sink: $\theta_{SA} T_J = 25^\circ\text{C} + (4.64\text{W})(2.5^\circ\text{C/W} + .5^\circ\text{C/W} + \theta_{SA}) < 85^\circ\text{C}$

$$\theta_{SA} < \frac{85 - 25^\circ\text{C}}{4.64\text{W}} - 3^\circ\text{C/W}$$

$$< 9.93^\circ\text{C/W} \checkmark$$

Choose TIP110

Complement is $Q_2 = \text{TIP115}$

d)

Want $i_{\text{diode}} = \frac{12 - V_{B1, \text{max}}}{R_{B1}} - i_{B1, \text{max}} > 1\text{mA}$

$$V_{B1, \text{max}} = 6.9 + \underbrace{2.8\text{V}}_{\text{Max } V_{BE}} = \underline{9.7\text{V}}$$

$$i_{B1, \text{max}} = \frac{.9\text{A}}{1000+1} = 0.9\text{mA}$$

min β
@ 1A

So, $\frac{12 - 9.7}{R_{B1}} - 0.9\text{mA} > 1\text{mA}$

$$R_{B1} < 1.2\text{k}\Omega \quad \text{Choose } \boxed{R_{B1} = 1.2\text{k}}$$

(1.1k is fine)

e)

(worst case)

$$\text{Max } V_o = \text{Max } V_{B1} - 2 \times \text{min } V_F$$


$$= 9.7 - 2 \times .62 = \underline{8.46\text{V}}$$

$$R_{in} = 1200 // 1200 // (1000+1) \left(1 + \frac{6\text{V}}{.9\text{A}}\right)$$

min β

$$\Rightarrow R_{in} = \underline{556.5\Omega}$$

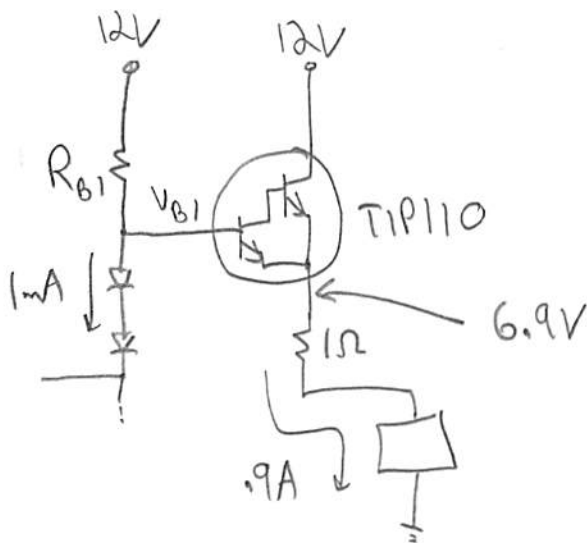For this problem, OK to treat motor as simple resistor.




$$\text{So, } i_o = \frac{8,46\text{V}}{556,5\Omega} = \underline{\underline{15,2\text{mA}}}$$

$$\text{Op amp headroom} = 12 - 8,46 = 3,54\text{V}$$

$$V_{cc} = 15\text{V} \therefore V_o = 15 - 3,54 = 11,46\text{V}$$

(22,9V_{pp})

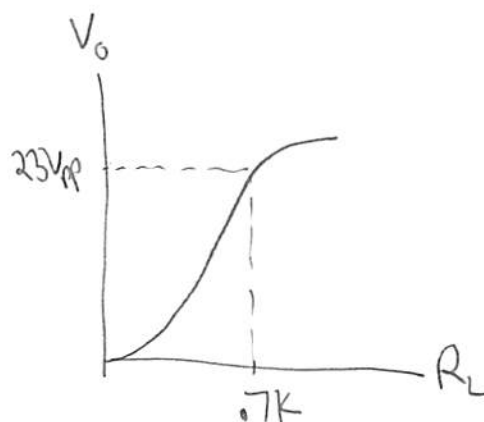

$$\rightarrow \text{max } i_o = \frac{11,46\text{V}}{,7\text{K}} = \underline{\underline{16,4\text{mA}}} > 15,2\text{mA} \text{ (barely!)} \quad \text{max}$$

YES, op amp can produce desired ^{max} output!

$$\textcircled{F} \text{ Set } G = 1 + \frac{R_2}{R_1} = \frac{6}{,5} = 12 \Rightarrow \frac{R_2}{R_1} = 11$$

Let

$R_1 = 10\text{K}$
$R_2 = 110\text{K}$


4

a) LF356: (Max)

$$I_{IN(BIAS)} = 200 \text{ pA}$$

$$I_{IN(OS)} = 50 \text{ pA}$$

$$V_{IN(OS)} = 10 \text{ mV}$$

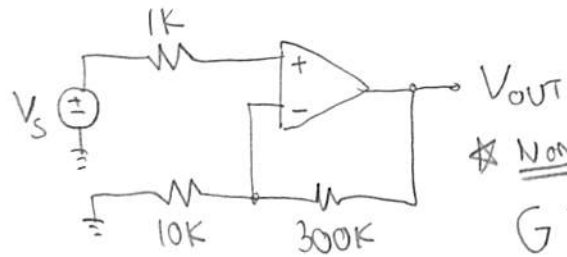

* Non-inv op amp
 $G = 1 + \frac{300K}{10K}$
 $= \underline{\underline{31}}$

$$R_{TH(+)} = 1K$$

$$R_{TH(-)} = 10K // 300K = 9.68K$$

$$I_{IN(BIAS)} : \Delta V_{OUT} = 31 \times (200 \times 10^{-12}) (9.68 \times 10^3 - 10^3) = \boxed{53.8 \mu V}$$

$$I_{IN(OS)} : \Delta V_{OUT} = 31 \times (50 \times 10^{-12}) \frac{9.68 \times 10^3 + 10^3}{2} = \boxed{8.28 \mu V}$$

$$V_{IN(OS)} : \Delta V_{OUT} = 31 \times 10 \text{ mV} = \boxed{310 \text{ mV}} \leftarrow$$

b) Main source of error is $V_{IN(OS)}$



c) worst case is to add all three together.

$$\text{Max } \Delta V_{OUT} = 0.0538 \text{ mV} + 0.00828 \text{ mV} + 310 \text{ mV}$$

$$= \boxed{310.062 \text{ mV}}$$

5

a

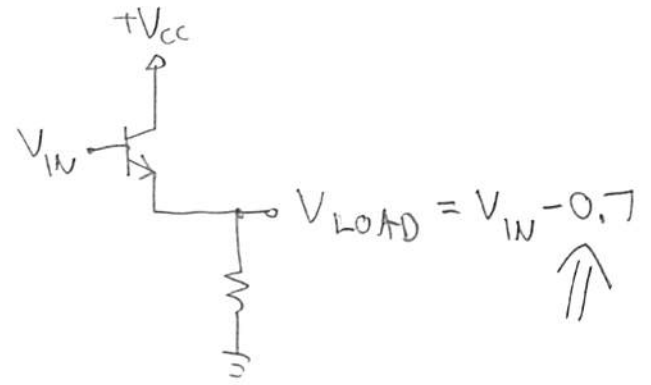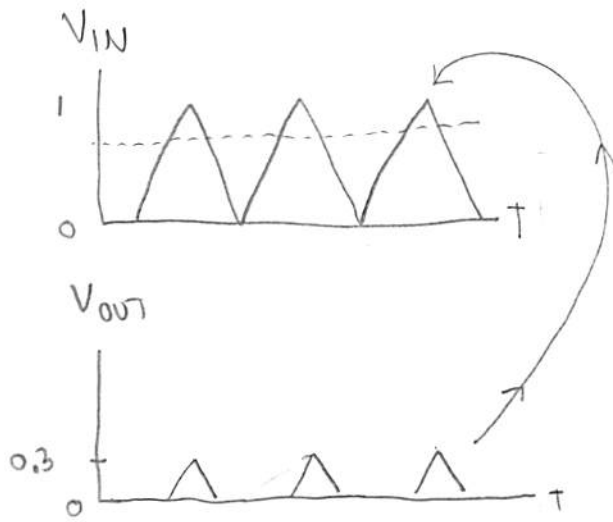


b

$$V_- = V_+ = V_s$$

Since $I = 0$

$$\Rightarrow V_{OUT} = V_- = V_s$$
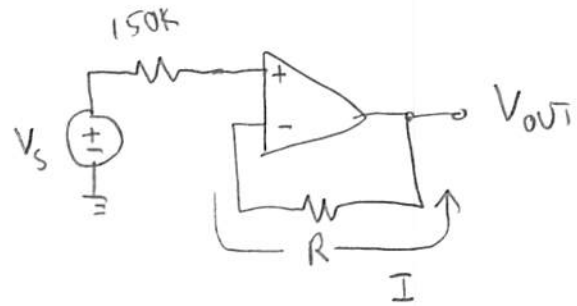
$$\Rightarrow \boxed{V_{OUT} = V_{sensor}}$$



c To minimize error due to $I_{IN(BIAS)}$, make $R_{TH(+)} = R_{TH(-)}$

$$\Rightarrow \boxed{R = 150k}$$

d Worst-case: use max value (unless stated otherwise) in problem

$$I_{IN(BIAS)}: 1 \times (500 \text{ nA}) \times (150k - 150k) = 0V$$

$$I_{IN(OS)}: 1 \times (200 \times 10^{-9}) \times \frac{150k + 150k}{2} = 30 \text{ mV}$$

$$V_{IN(OS)}: 1 \times 6 \text{ mV} = 6 \text{ mV}$$

$$\text{Worst-case } \Delta V_{OUT} = 0 + 30 + 6 \text{ mV} = \boxed{36 \text{ mV}}$$


⑥

① For inverting amplifier,

$$Z_{in} = R_1 \geq 10K$$


Choose $R_1 = 11K$
 $R_2 = 560K$
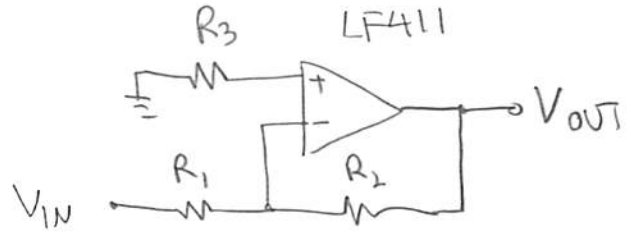
$$\rightarrow G = -\frac{560K}{11K} = -50.9 \checkmark$$



② $R_{TH(s)} = (1K + 11K) // 560K$
 $= 11.75K$

Choose $R_3 = 12K$

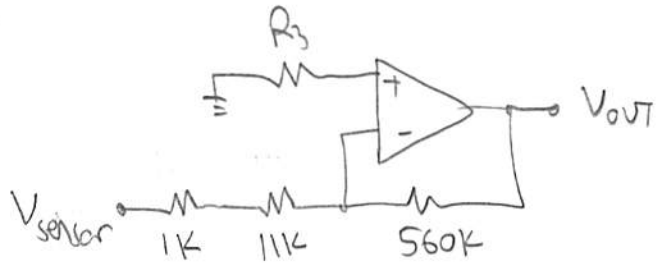

③ For LF411, $GBW = 4MHz$

$$\rightarrow BW = \frac{4MHz}{50.9} = 78.6KHz$$


7

$$V(t) = V_0 (1 - e^{-t/RC})$$

$$\textcircled{a} \quad 0.1V_0 = V_0 (1 - e^{-t_{10}/RC})$$

$$e^{-t_{10}/RC} = 0.9$$
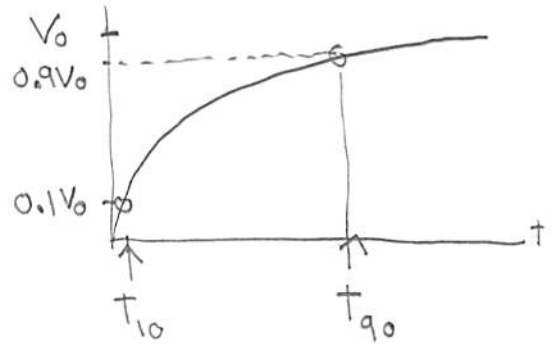
$$-\frac{t_{10}}{RC} = \ln(0.9) \rightarrow \boxed{t_{10} = -RC \ln 0.9}$$



$$\textcircled{b} \quad 0.9V_0 = V_0 (1 - e^{-t_{90}/RC})$$

$$e^{-t_{90}/RC} = 0.1 \rightarrow -\frac{t_{90}}{RC} = \ln 0.1 \rightarrow \boxed{t_{90} = -RC \ln 0.1}$$

$$\textcircled{c} \quad T_R = t_{90} - t_{10} = -RC \ln 0.1 - (-RC \ln 0.9)$$

$$= RC [\ln 0.9 - \ln 0.1] = RC \ln \frac{0.9}{0.1}$$

$$\boxed{T_R = RC \times \ln 9 = 2.2RC}$$

$$\textcircled{d} \quad f_c = \frac{1}{2\pi RC} \rightarrow RC = \frac{1}{2\pi f_c}$$

$$\text{So, } T_R = 2.2 \frac{1}{2\pi f_c} = \boxed{\frac{0.35}{f_c}}$$

8

8

(a) 741 data sheet does not give f_{unity}
 but does give $\underbrace{\text{rise time} = 0.3 \mu\text{s}}_{\text{for } G=1}$

$$T_R = \frac{0.35}{f_c} \rightarrow f_c = \frac{0.35}{T_R}$$

$$f_{unity} = \frac{0.35}{0.3 \mu\text{s}} = \underline{\underline{1.2 \text{ MHz}}}$$

$$BW = \frac{f_{unity}}{G} \leftarrow 10^{26 \text{ dB}/20} = 19.95$$


$$= \frac{1.2 \text{ MHz}}{19.95} = \boxed{60 \text{ KHz}}$$

$$T_R = \frac{0.35}{1060 \text{ MHz}} = \boxed{5.83 \mu\text{s}}$$

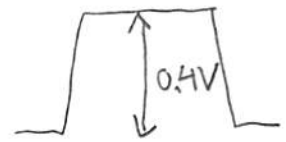(b) Slew rate affects op amp output


$$V_{out} = G V_{in} = 19.95 \times 0.020 \text{ V}_{pp} = 0.399 \text{ V}_{pp} \sim 0.4 \text{ V}_{pp}$$

$$T_{SR} = \frac{0.8 \times 0.4 \text{ V}}{0.5 \text{ V}/\mu\text{s}} = \boxed{0.64 \mu\text{s}}$$



(c) Since $T_R \gg T_{SR}$, amplifier is limited by small-signal BW

(d) 20 KHz
 1 cycle = 50 μs

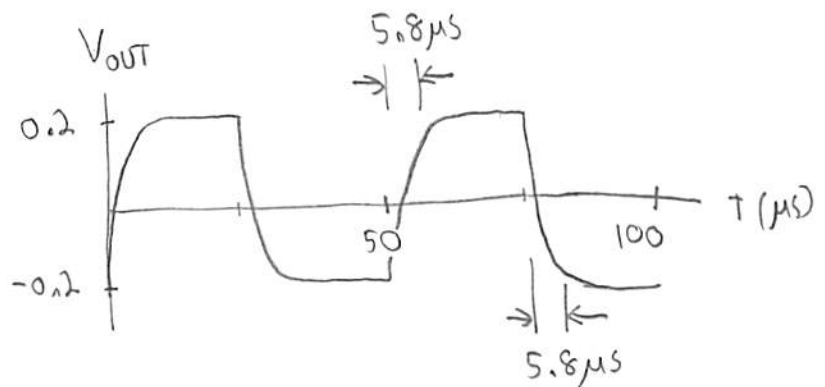

9

a) Slew rate affects op amp output

$$|G| = 30 \text{ dB} \rightarrow G = 10^{30/20} = \underline{\underline{31.6}}$$

$$V_{\text{OUT}} = -31.6 \cdot 0.1 V_p = -3.16 V_p$$

Only for
sine
waves!

$$\Rightarrow \underbrace{\text{Large-signal BW}}_{\text{same as "power"}} = \frac{\text{SR}}{2\pi V_p} = \frac{15 \text{ V}/\mu\text{s}}{2\pi (3.16 \text{ V})} = 0.755 \text{ MHz} = \boxed{755 \text{ KHz}}$$

$$\text{b) Small-signal BW} = \frac{f_{\text{unity}}}{G} = \frac{4 \text{ MHz}}{31.6} = 0.127 \text{ MHz} = \boxed{127 \text{ KHz}}$$

c) Since $127 \text{ KHz} < 755 \text{ KHz}$

→ Limited by small-signal BW