


①

a) Switch connected to ground:

$$\rightarrow I_B = 0$$

 $\rightarrow Q_1 \text{ is OFF}$


$$I_{LED} = I_c = 0$$

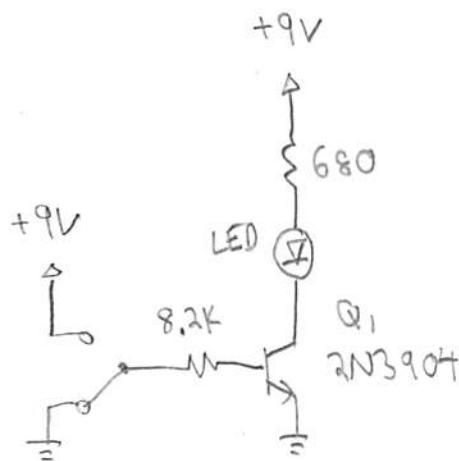

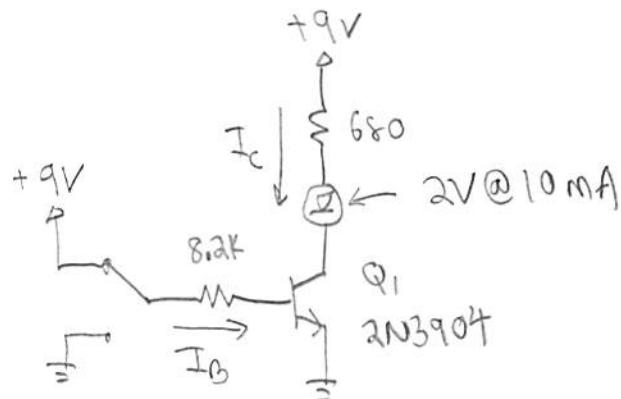b) Switch connected to +9V:

From data sheet plots: $V_{CE(sat)} = 0.05V$ For typical values
 $V_{BE(sat)} = 0.75V$

$$\left. \begin{array}{l} V_{CE(sat)} = 0.05V \\ V_{BE(sat)} = 0.75V \end{array} \right\} \text{At } I_c = 10 \text{ mA}$$



$$9 - I_B (8.2k) - V_{BE(sat)} = 0 \rightarrow I_B = \frac{9 - 0.75V}{8.2k} = 1.01 \text{ mA} \sim 1.0 \text{ mA}$$

$$9 - I_c (680) - V_F - V_{CE(sat)} = 0 \rightarrow I_c = \frac{9 - 2 - 0.05V}{680\Omega} = 10.2 \text{ mA}$$

$$\textcircled{c) } \quad \frac{I_c}{I_B} = \frac{10.2 \text{ mA}}{1.0 \text{ mA}} = 10.2 \quad \text{YES}$$

NOTE:

$$\frac{I_c}{I_B} > 10 \text{ is OK}$$


 $\frac{I_c}{I_B} \sim 20$ is usually fine for small-signal transistors.

②

ⓐ Heater rating: 12V @ 20W

$$\text{Rated current} = \frac{20\text{W}}{12\text{V}} = \underline{\underline{1.67\text{A}}}$$
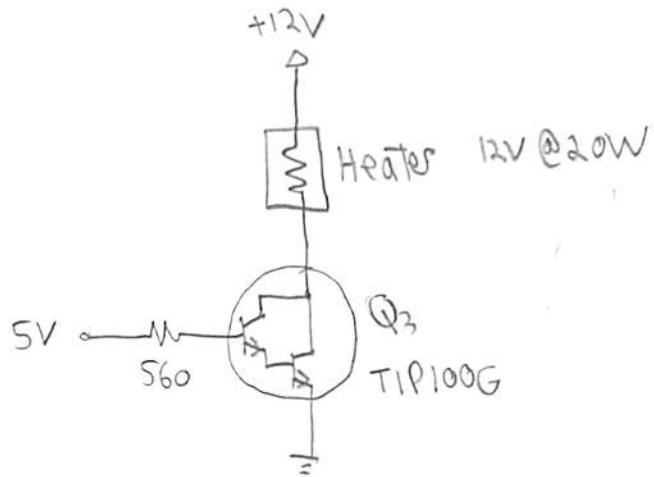
$$\text{Resistance} = \frac{(12\text{V})^2}{20\text{W}} = \underline{\underline{7.2\Omega}}$$



From TIP100 data sheet plots: For typical values

$$\left. \begin{array}{l} V_{BE(\text{sat})} = 1.6\text{V} \\ V_{CE(\text{sat})} = 0.9\text{V} \end{array} \right] \text{At } I_c \sim 1.67\text{A}$$

$$I_B = \frac{5 - 1.6\text{V}}{560\Omega} = .0061\text{A} = \boxed{6.1\text{mA}} \quad \checkmark \quad \text{YES, OK with micro controller.}$$

ⓑ Estimate P:

$$P = I_B V_{BE} + I_c V_{CE} = \left(\frac{1.67\text{A}}{250} \right) (1.6\text{V}) + (1.67\text{A})(0.9\text{V})$$

↑
OK to use rated load current since actual current will be less due to $V_{CE(\text{sat})}$

$$\text{Darlington, } = \frac{1}{2} \times 1.51\text{W} \xrightarrow{x2} 3.03\text{W}$$

TIP100: Max P = 2W (no HS) X,
80W (w/HS) ✓

⇒ Need heat sink

$$\textcircled{c} \quad T_J = 25^\circ\text{C} + (1.51\text{W}) (\Theta_{JC} + \Theta_{CS} + \Theta_{SA}) = \boxed{70.4^\circ\text{C}} < 85^\circ\text{C}$$

↑ ↑ ↑
1.56°C/W 0.5°C/W 28°C/W

YES, this heat sink is fine.


(3)

① In steady state, solenoid is

$$\text{a resistor: } 6W = \frac{(24V)^2}{R_L}$$

$$\rightarrow R_L = \underline{\underline{96\Omega}}$$
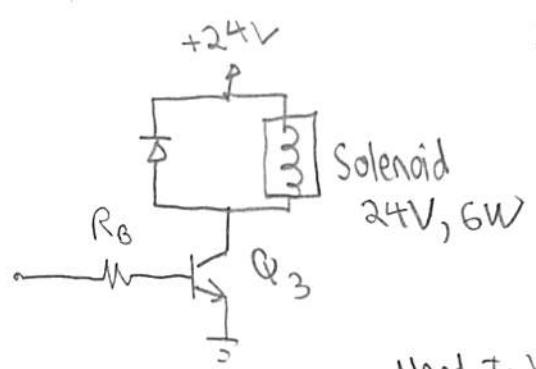
$$I_L = \frac{6W}{24V} = 0.25A \xrightarrow{\times 2} \underline{\underline{0.5A \text{ rating}}}$$



Need to be
 $> 2 \times 24 =$
 $\underline{\underline{48V}}$

BC546 Max I_c
100mA X

2N2222A 800mA ✓



V_{CE}

50V ✓

$$> 24 \times 2 = 48V$$

P (no HS)

500mW

This works!

Diode

IN4148:

I_{FSM}

1A (1s) ✓
2A (1μs)

V_{RRM}

75V ✓

IN4001: 30A (8.3ms) 50V

$$\text{Typ } V_{BE(\text{sat})} = 0.88V$$

$$P \approx \frac{0.25A}{10} (.88V) + .25A (.17V) = .0645W$$

$$\downarrow 129mW \quad \xrightarrow{\times 2}$$

$< 500mW$ rating

Choose 2N2222A w/o heat sink

(b)

$$V_{CE(\text{sat})}: \text{Typ} = 0.13V$$

$$0.17V$$

$$\text{Max} = 0.3V$$

$$?$$

$$\xrightarrow{@ 150mA}$$

$$\xrightarrow{@ 250mA}$$

$$\left. \begin{array}{l} \text{Max } V_{CE(\text{sat})} = \frac{0.3}{0.13} \times 0.17 = \underline{\underline{0.4V}} \end{array} \right\}$$

$$V_{BE(\text{sat})}: \text{Typ} = 0.85$$

$$0.9V$$

$$\text{Max} = 1.2V$$

$$?$$

$$\xrightarrow{@ 150mA}$$

$$\xrightarrow{@ 250mA}$$

$$\left. \begin{array}{l} \text{Max } V_{BE(\text{sat})} = \frac{1.2}{0.85} \times 0.9 \\ = \underline{\underline{1.27V}} \end{array} \right\}$$

$$\circ \text{Min } V_L = 24 - 0.4 = \boxed{23.6V}$$

$$\text{Min } I_L = \frac{23.6V}{96\Omega} = \boxed{0.246A}$$

③ Typical $V_{BE(\text{sat})} = 0.9V$

$$\left. \begin{array}{l} V_{CE(\text{sat})} = 0.17V \end{array} \right\} @ 250\text{nA}$$

$$I_c = \frac{24 - 0.17V}{96\Omega} = 248\text{A}$$

$$I_b = \frac{5 - 0.9V}{R_b} \sim \frac{248\text{A}}{10} \Rightarrow R_b \sim 165.3\Omega \quad \checkmark$$

Choose $R_b = 160\Omega$

④ Actual $I_b = \frac{5 - 0.9}{160\Omega} = 25.6\text{mA} \Rightarrow \frac{I_c}{I_b} = \frac{248\text{mA}}{25.6\text{mA}} = 9.69$

Worst case Q₃: $I_b = \frac{5 - 1.27}{160} = 23.3\text{mA} \Rightarrow \frac{I_c}{I_b} = \frac{246\text{mA}}{23.3\text{mA}} = 10.6$

↑
still plenty saturated?

⑤ Typical $I_b = 25.6\text{mA} < 40\text{mA}$ OK?

Worst case I_b is max value $\rightarrow \min V_{BE} = 0.6 @ 150\text{mA}$

$$\min V_{BE} = \frac{0.6}{0.85} \times 0.9 = 0.635V$$

$$I_b = \frac{5 - 0.635}{160\Omega} = 27.3\text{mA} < 40\text{mA}$$

NOTE: Better to be below 50% of current limit.


(Darlington would be better Q₃).

(4)

⑤ Stall current = 1.7A

$$\hookrightarrow \text{max } I_L = \underline{0.85A} \quad \xrightarrow{x2}$$

Need 1.7A rating

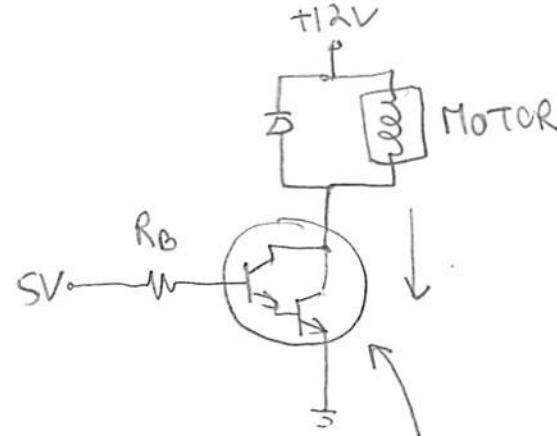

<u>Max I_C</u>	<u>V_{CE}</u>	<u>$P(\text{no Hs})$</u>	<u>$P(\text{w/Hs})$</u>	<u>0.85A</u>
-----------------------------	----------------------------	-------------------------------------	------------------------------------	--------------

MPSA29 800mA X

TIP110 2A ✓ 60V 2W 50W

$$\text{Typ} \left\{ \begin{array}{l} V_{BE(\text{sat})} = 1.5V \\ V_{CE(\text{sat})} = .83V \end{array} \right.$$

$$\text{Need} > 2 \times 12 = \underline{\underline{24V}} \quad \checkmark$$

$$\text{Estimate } P = \frac{.85A}{250} (1.5V) + (.85A)(.83V) = 0.71W \xrightarrow{x2} \underline{\underline{1.42W}} < 2W$$

Need > 1.7A rating

Choose TIP110

(typical conditions)

↓
Diode:

<u>I_{FSD}</u>	<u>V_{RRM}</u>
-----------------------------	-----------------------------

IN4148 1A (1s) X

IN4002 30A (8.3ms) 100V ✓

Choose IN4002

(6)

$$\text{Max } V_{CE(\text{sat})} = 2.5V$$

?

$$\text{Typ } V_{CE(\text{sat})} = \underbrace{1V}_{2A}, \underbrace{0.83V}_{0.85A}$$

$$\text{Max } V_{CE(\text{sat})} = \frac{2.5}{1} \times 0.83 = \underline{\underline{2.08V}}$$

$$V_{\text{Motor}} = 12 - 2.08 = \boxed{9.92V}$$

(c)

$$I_B = \frac{5 - 1.5V}{R_B} \sim \frac{.85A}{250} \rightarrow R_B = 1029\Omega$$

Choose $R_B = 1k\Omega$ ← 1.1k would also work.

(d)

Max P is when V_{CE} is max.

$$\text{Max } V_{CE(\text{sat})} = 2.08V \text{ (from (b))}$$

$$\begin{aligned} \text{Max } V_{BE(\text{sat})} &= 2.8V, \quad ? \\ \text{Typ } V_{BE(\text{sat})} &= 1.7V, \quad 1.5V \\ &\quad \underbrace{\qquad}_{2A} \quad \underbrace{\qquad}_{.85A} \end{aligned}$$

$$\left. \begin{aligned} \text{Max } V_{BE(\text{sat})} &= \frac{2.8}{1.7} \times 1.5 \\ &= \underline{\underline{2.47V}} \end{aligned} \right\}$$

$$P \approx \frac{.85A}{250} (2.47) + .85A (2.08V) = \underline{\underline{1.78W}}$$

$$\begin{aligned} T_J &= 25^\circ C + (1.78W) (2.5^\circ C/W + .5^\circ C/W + 25^\circ C/W) \\ &= \boxed{74.8^\circ C} < 85^\circ C \end{aligned}$$

$\boxed{\text{YES}}$ ∵

(5)

④ ZVN3306A data sheet:

$$\text{Max } V_{GS,TH} = \boxed{2.4V}$$

⑤ When $V_{GS} = 5V$,


$$R_{DS,ON} = \frac{1}{\text{slope}} \sim \frac{1}{0.17A} = \boxed{5.9\Omega}$$

Clearly, $I_{LED} = 20mA \ll 0.3A$

\rightarrow Ohmic region ✓

$$5 - I_D \times 150 - V_F - I_D R_{DS,ON} = 0$$
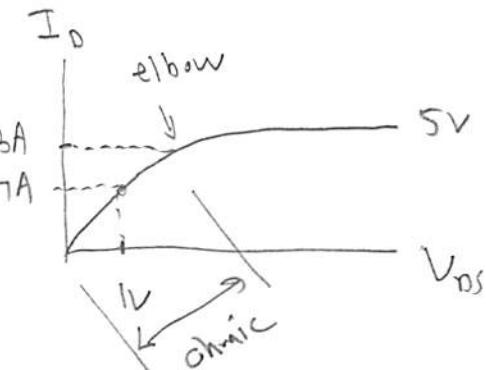
$$I_D = \frac{5 - 2.2V}{150 + 5.9\Omega} = \boxed{0.018A}$$





(6)

200Hz

$$\Rightarrow 1 \text{ cycle} = 5ms$$

40% duty cycle


$$\Rightarrow ON = 2ms$$

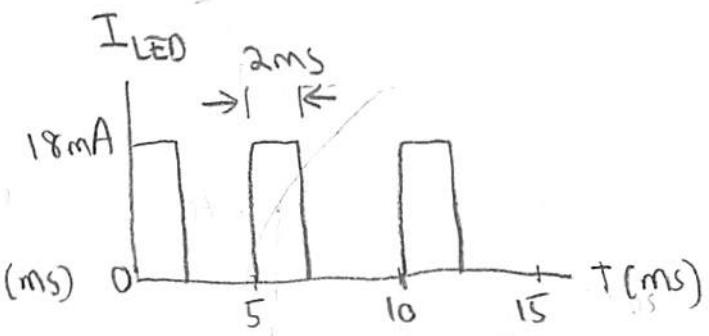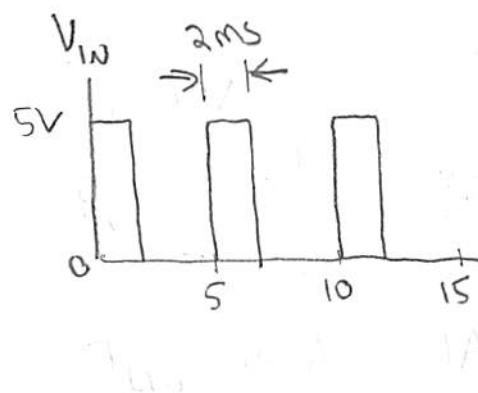⑥ Q_S: Instantaneous $P = (0.018A)^2 (5.9\Omega) = 1.9mW$

$$\text{Avg } P = 0.4 \times 1.9mW = \boxed{0.76mW}$$

LED: Instantaneous $P = (0.018A)(2.2V) = 39.6mW$

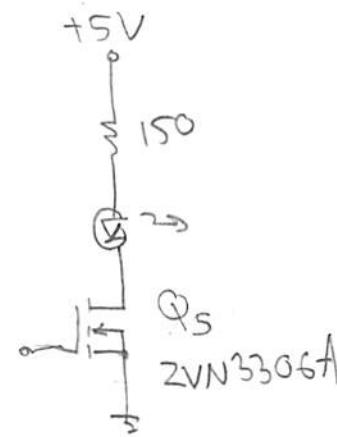
$$\langle P \rangle = 0.4 \times 39.6mW = \boxed{15.8mW}$$



⑥

(a) 2N7000 data sheet


$$\boxed{\text{Max } V_{GS,TH} = 3V}$$

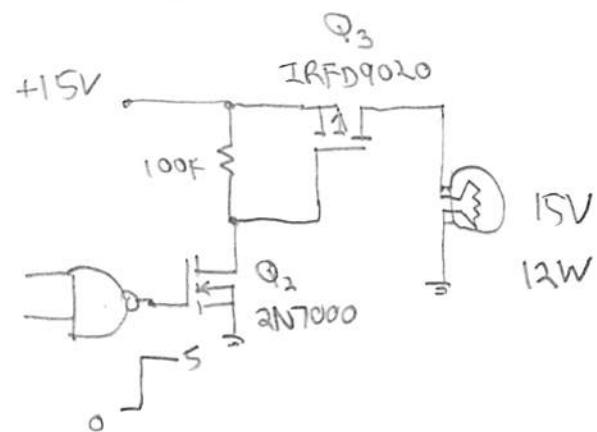(b) NAND output = 0V << 3V \leftarrow Q₂ OFF ✓= 5V >> 3V \leftarrow Q₂ ON ✓

(c)


$$I_D = \frac{15 - 0V}{100k + R_{DS(on)}} \approx \frac{15V}{100k} = 0.15mA \leftarrow \text{tiny!}$$

Definitely in ohmic region! ✓ \Rightarrow Q₂ is operating near the origin $\Rightarrow .15mA$

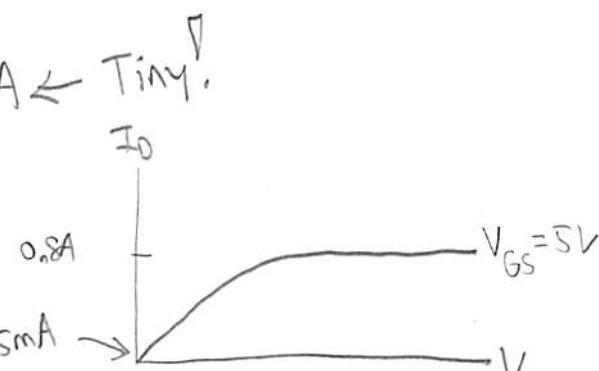(d) IRFD9020: $\boxed{\text{Max } V_{GS,TH} = -4V}$ (e) Q₂ is OFF \rightarrow Q₃ has $V_{GS} \approx 15 - 15 = 0V$ \leftarrow Much more positive than -4V, so Q₃ is OFFQ₂ is ON \rightarrow Q₃ has $V_{GS} \approx 0 - 15 = -15V$ \leftarrow Much more negative than -4V, so Q₃ is ON

(f) Light bulb current rating = $\frac{12W}{15V} = 0.8A$

Ohmic ✓ [Clearly in linear region]

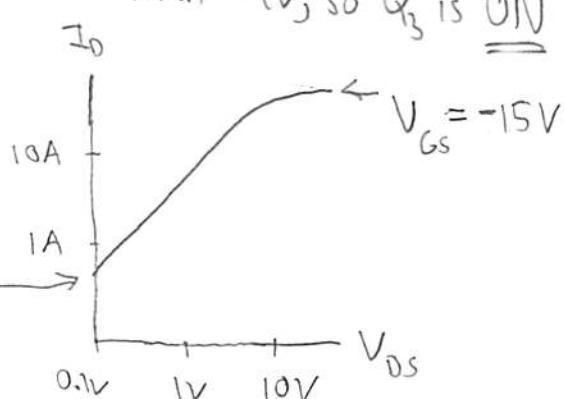

⑨ When Q_3 is ON: $R_{DS,ON} \approx \frac{1}{0.8A/0.1V} = \frac{1}{8} = \boxed{125\Omega}$

$$R_{Bulb} = \frac{(15V)^2}{12W} = \underline{\underline{18.75\Omega}}$$

$$I_D = \frac{15 - 0V}{125 + 18.75\Omega} = \boxed{0.795A}$$

$$\text{Light bulb power} = I_D^2 R_{Bulb}$$

$$= (0.795A)^2 (18.75\Omega) = \boxed{11.85W}$$

(7)

② Compare MOSFETs:

	<u>ZVN3306A</u>	<u>ZVN3106A</u>	<u>IRFD9020</u>
Max cont I_c	270mA ✓	450mA ✓	-1.6A
Max V_{DS}	60V ✓	60V ✓	-60V
Max V_{GS}	$\pm 20V$ ✓	$\pm 20V$ ✓	$\pm 20V$ ✓
Max $V_{GS,TH}$	2.4V ✓	2.4V ✓	$-4V$
Typical $R_{DS(on)}$	$\frac{1V}{0.18A} = 5.6\Omega$		0.28Ω

$$P = (0.010A)^2 (5.6\Omega) = .00056W \xrightarrow{\times 2} \underline{\underline{1.1mW}}$$


MUCH less than
625 mW rating for ZVN3306

⇒ ZVN3306A works!

Ohmic region?
Check $I_o - V_{DS}$ curve

Definitely
in
linear
region!

10mA is
way
down here

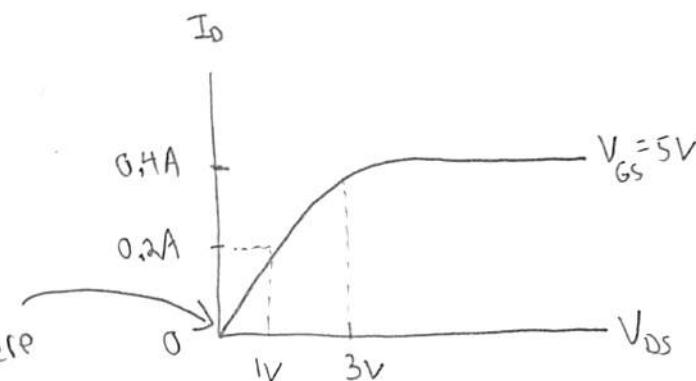


③ Typical conditions: $Q_1 \Rightarrow R_{DS(on)} \approx \frac{1}{0.18A} = 5.6\Omega$

$$\text{LED} \rightarrow V_F = 1.9V$$

$$\text{So, } 5 - V_F - I_D R - I_D R_{DS(on)} = 0$$

$$= \frac{5 - 1.9V - 0.010 \times 5.6\Omega}{0.010A} = 304.4\Omega$$

Choose $R = 300\Omega$

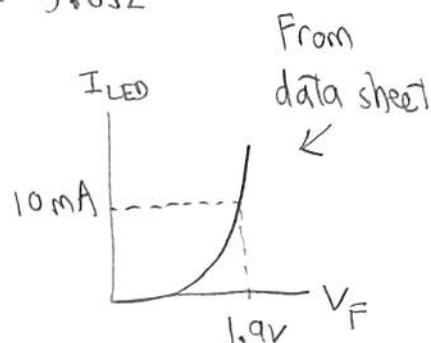

② From data sheets : LED $\rightarrow V_F = 2.5V$ (max)


$$Q_1 \rightarrow R_{DS,ON} = 5\Omega \text{ (max at } V_{GS} = 10V\text{)}$$

$$\begin{aligned} \text{Min } I_{LED} &= \frac{5 - 2.5V}{300 + 5} \\ &= \boxed{8.2 \text{ mA}} \end{aligned}$$

Not the most appropriate value to use, especially since typical value is $\underline{\underline{5.6\Omega}}$ @ $V_{GS} = 5V$.
But we'll use it anyway.


⑧ a) Sketch of circuit:

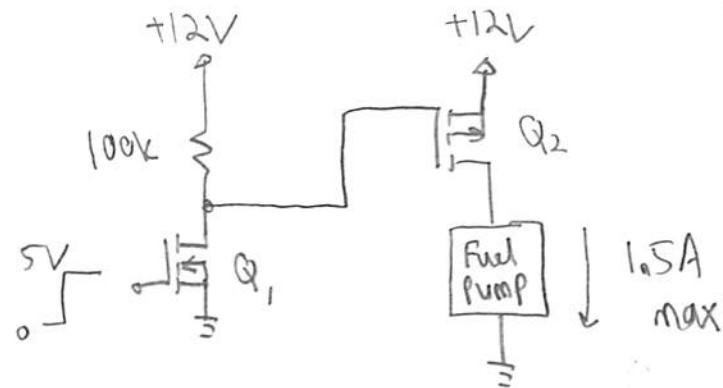Q_2 needs $> 3A$ rating
 ~
 Power MOSFET?



→ Need logic level shifter

b) Q_2 : Max I_{DS} Max V_{GS} Max V_{DS}

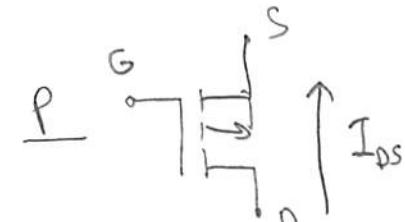

ZVTP3310 -14A X

For $T_c = 25^\circ C$

ZVTP2106 -28A X

IRF9520 -6.8A ✓ 120V -100V ✓ 60W ← (w/HTS)

$$> 2 \times 5 = \underline{\underline{10V}}$$

$$> 2 \times 12 = \underline{\underline{24V}}$$

Worst Case P: $P = (1.5A)^2 \times \underbrace{0.6\Omega}_{\text{max } R_{DS(on)}} = \underline{\underline{1.35W}} \xrightarrow{x2} \underline{\underline{2.7W}}$

max $R_{DS(on)}$

< 60W

Choose IRF9520 w/HTS ← Choose later

c) Q_1 : $I_D \sim \frac{12V}{100k} = \underline{\underline{0.12mA}}$ (tiny)

2N7003:

	Max I_C	V_{GS}	V_{DS}
	200mA	±120V	60V
↑	↑	↑	↑
> 0.24mA	> 2 × 5 = 10V	$2 \times 12 = 24V$	
✓	✓	✓	✓

Start with smallest MOSFET


This works!

d) without HTS:

$$T_J = 25 + 1.35 \times 62.$$

$$= \boxed{108.7^\circ C} > 85^\circ C \square$$

Need HTS

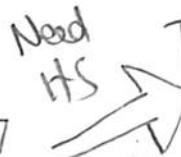

$$T_J = 25 + 1.35 (2 \times 5 + 5 + \Theta_{SA}) K 85^\circ C$$

$$\rightarrow \Theta_{SA} < 41.4^\circ C/W$$