

A. RELAXATION OSCILLATOR

1) Show that the relaxation oscillator frequency is given by:
$$f = \frac{1}{2RC \ln\left(\frac{1+B}{1-B}\right)}$$

An easy way to do this is to consider a capacitor with an initial voltage $V_C = -V_{TH}$. As shown in Fig. 1, it is charged by a resistor R connected to $+V_{SAT}$. We can figure out how long it takes the capacitor to go from $-V_{TH}$ to $+V_{TH}$ (assuming $V_{TH} < V_{SAT}$, which is indeed true).

a) Derive the first-order differential equation for V_C .

Hint #1: The current through R is the same as the current through C . Write the expression for each current and set them equal to each other.

Hint #2: You should get: $\frac{dV_C}{dt} + \frac{1}{RC}V_C = \frac{1}{RC}V_{SAT}$

b) Let the initial condition be $V_C(0) = -V_{TH}$ and the steady state solution be $V_C(\infty) = +V_{SAT}$. Solve the differential equation for $V_C(t)$. Hint: You should get $V_C(t) = V_{SAT} - (V_{TH} + V_{SAT})e^{-t/RC}$.

c) Derive the time value when V_C reaches $+V_{TH} = V_{SAT} R1/(R1 + R2)$. Hint: You should get $t = RC \ln\left(\frac{1+B}{1-B}\right)$, where $B = R1/(R1+R2)$.

d) Derive the frequency of the square wave output from the relaxation oscillator.

2) Design a relaxation oscillator with a frequency of 1 kHz. Use standard 5% resistor values and 10% capacitor values.

a) A reasonable choice of the feedback ratio is $B = 0.5$. $R1$ and $R2$ are typically in the 100 kohm range.

b) Choose R and C . Note: R is typically around 100 kohm, and C is typically 0.1 uF or less.

NOTE: Using resistors in the 100 kohm range ensures the max op amp output current is well below 1 mA.

c) Based on your choice of components, show that your frequency is within 5% of the desired value.

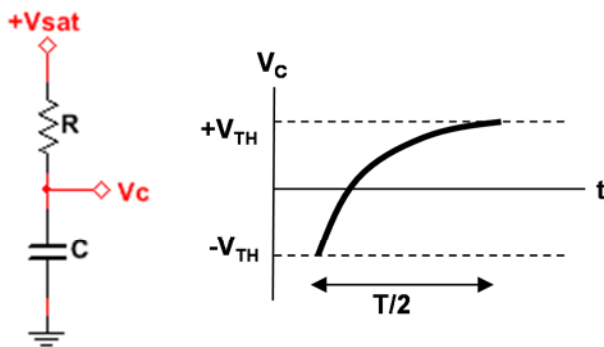


Fig. 1

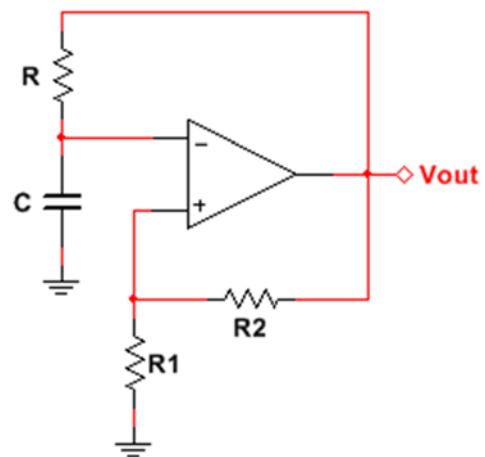


Fig. 2

B. SCHMITT TRIGGER

3) A non-inverting Schmitt trigger is basically a voltage comparator with hysteresis.

- The output goes HIGH ($V_{OUT} = +V_{SAT}$) when the input rises above the UTP.
- The output goes LOW ($V_{OUT} = -V_{SAT}$) when the input dips below the LTP.

Including some hysteresis (meaning $UTP \neq LTP$) produces a much less jittery output V_{OUT} when the input contains noise fluctuations.

Consider the non-inverting Schmitt trigger shown in Fig. 3. Assume $V_{CC} = 15V$, $+V_{SAT} = V_{CC}-1$ and $-V_{SAT} = -V_{CC}+1$.

- Compute the UTP and LTP levels.
- The input voltage V_{IN} has some fluctuations, as shown in Fig. 3. Sketch both V_{IN} and V_{OUT} . Label important features, such as the UTP and LTP on the V_{IN} plot and $\pm V_{SAT}$ on the V_{OUT} plot.

4) Consider the non-inverting Schmitt trigger shown in Fig. 4. The reference voltage $V_{REF} = 5V$ is connected to the (-) input of the op amp. Assume $V_{CC} = 15V$, $+V_{SAT} = V_{CC}-1$ and $-V_{SAT} = -V_{EE}+1$.

- Derive general expressions for the UTP and LTP levels (e.g. in terms of V_{REF} , R_1 , and R_2).

Hint #1: Use a similar procedure as the derivations in the Lecture 11 notes.

Hint #2: You should get $UTP = (1 + R_1/R_2) V_{REF} + V_{SAT}R_1/R_2$ and $LTP = (1 + R_1/R_2) V_{REF} - V_{SAT}R_1/R_2$.

- The input voltage V_{IN} has some fluctuations, as shown in Fig. 4. Sketch both V_{IN} and V_{OUT} . Label important values, such as the UTP and LTP on the V_{IN} plot and $\pm V_{SAT}$ on the V_{OUT} plot.

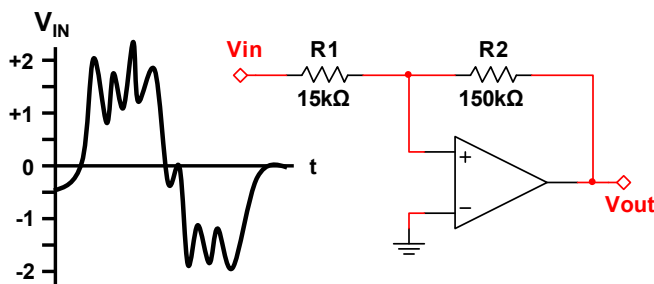


Fig. 3

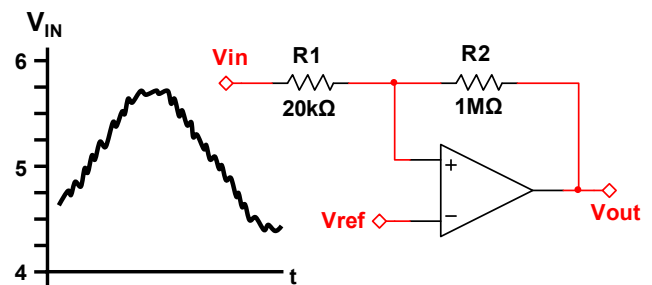


Fig. 4

C. TRIANGLE WAVE GENERATOR

5) As we've seen in Lecture 11, a good way to generate a triangle wave is to use a closed loop circuit formed with a non-inverting Schmitt trigger and an op-amp integrator (see Fig. 5). The square wave (Schmitt trigger output) goes from $+V_{SAT}$ to $-V_{SAT}$ while the triangle wave goes between $-V_{TH}$ to $+V_{TH}$. However, we did not discuss the frequency of the triangle wave. Show that the triangle wave frequency is given by $f = \frac{R_2}{4R_1R_3C}$

Hint #1: The integrator output is $V_{OUT} = -\left(\frac{1}{R_3C}\right) \int V_{IN} dt$, where V_{IN} is the square wave from the Schmitt trigger.

Hint #2: It helps to sketch one cycle of the square wave and integrator output, as shown in Fig. 5. During a duration $T/2$, the integrator output changes from $+V_{TH}$ to $-V_{TH}$ while the square wave is held at $+V_{SAT}$. You know that $V_{TH} = V_{SAT}R_1/R_2$, so you can therefore solve for T .

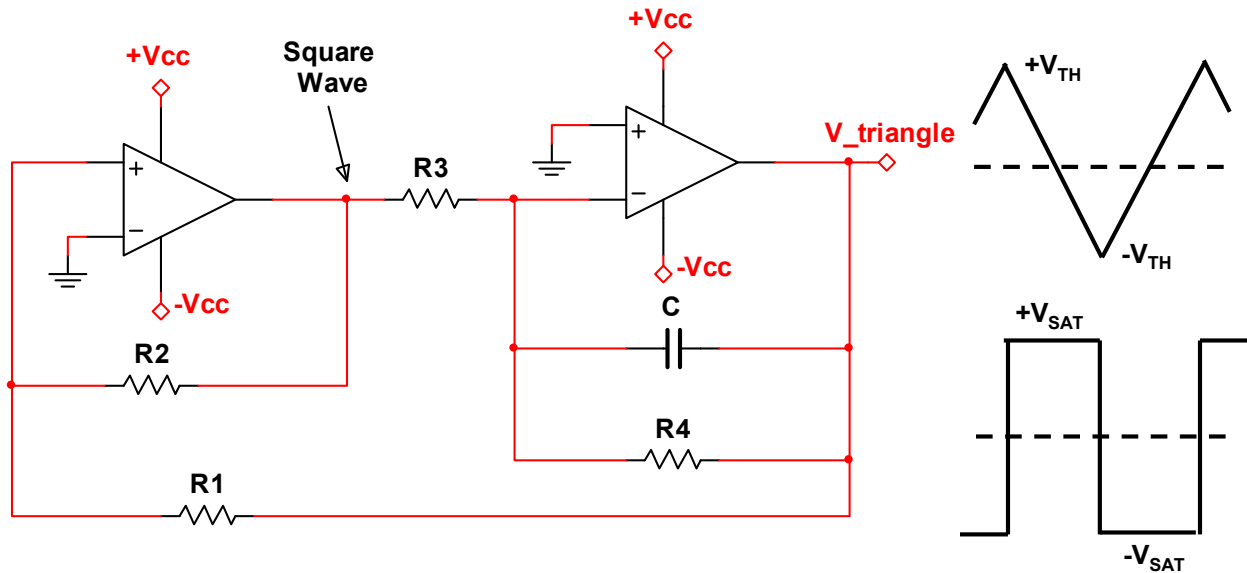


Fig. 5

6) Design a triangle wave generator to output a 20V peak-to-peak waveform with a 500 Hz frequency. Your op-amps are powered by +/- 15 V. Use standard 5% resistors and 10% capacitors.

a) Choose R_1 and R_2 . Hint: R_2 is typically 100 kohm or higher. This ensures the max op amp current is pretty low.

b) Choose R_3 , C , and R_4 . C is typically between 1 nF and 100 nF while R_3 is typically between 1 kohm and 100 kohm.

c) Most integrators have a large resistor in parallel with the capacitor (see Fig. 6). The purpose is to suppress output drift over long periods of time. This resistor R_4 is typically chosen to be at least 10 times higher than R_3 . What value should you use for your 500 Hz triangle wave generator?

d) Show that your resulting frequency is within 5% of the desired value.


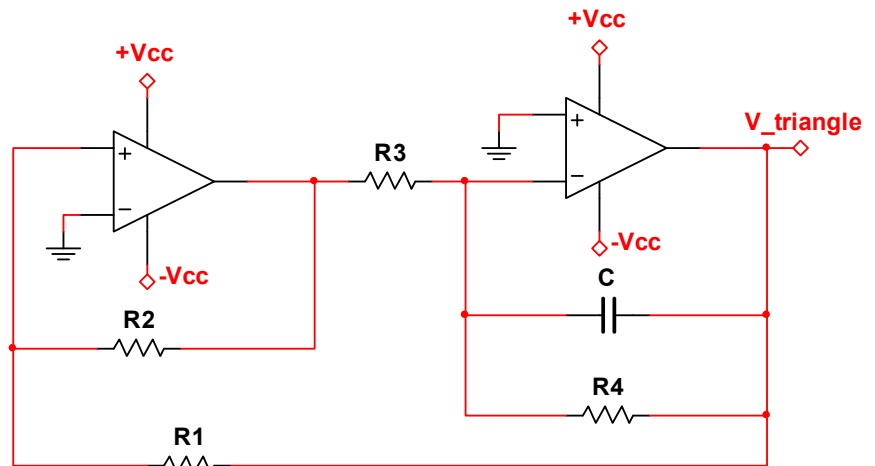


Fig. 6

7) A PWM signal can also be made with a “sawtooth” waveform, which is similar to a triangle wave but has steep falling edges. A common method to generate a sawtooth waveform is to charge a capacitor with a constant current source. The capacitor is discharged once the voltage has reached a threshold value. As shown in the figure below, we can use a 555

timer chip to do this! The discharge transistor turns on when the capacitor voltage reaches $2V_{CC}/3$ and turns off once the capacitor voltage drops to $V_{CC}/3$ (NOTE: Buma corrected the lecture notes to show this). Show that the sawtooth frequency is given by $f = 3 I_O / (V_{CC} C)$

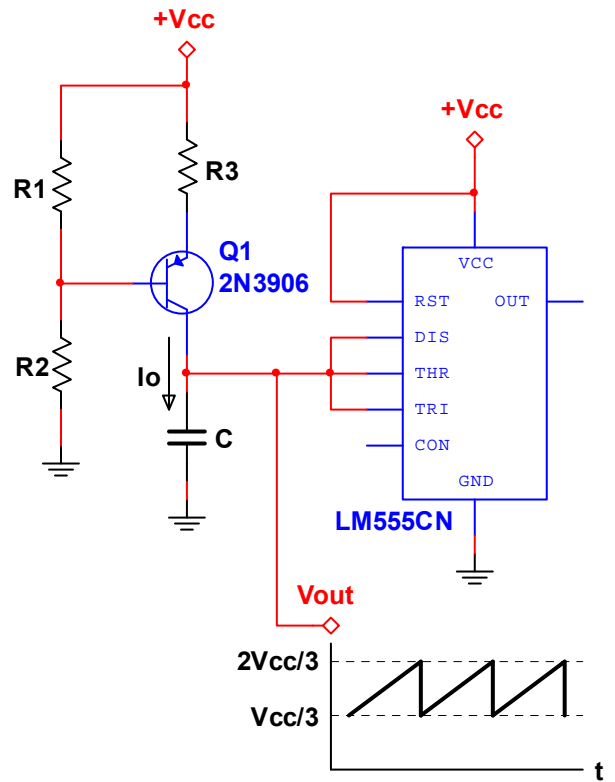- 8) Design a sawtooth oscillator using a 555 timer to operate at 10 kHz ($\pm 5\%$ is fine). Let $V_{CC} = 9V$. Some comments:
- The available capacitor values are 100 pF, 1 nF, 10nF, and 100 nF.
 - I_O is typically between 0.1 to 1 mA.
 - Assume “quick” analysis parameters for Q1.
 - Typically, the voltage across R3 is about 1V.
 - Make R1 and R2 a “firm” divider. This means that $R_1/R_2 \approx (\beta+1)R_3/10$.
- a) Choose values for your capacitor C and current source value I_O . Keep in mind the comments above!
- b) Choose your resistor R3.
- c) Choose your divider resistors R1 and R2.



D. Pulse Width Modulation

- 9) Analyze the pulse width modulator shown in Fig. 7. The comparator is just an op amp (no hysteresis). Assume $\pm V_{SAT} = \pm (V_{CC} - 1)$.
- a) Compute the amplitude of the triangle wave.
- b) Compute the frequency of the triangle wave.
- c) Compute the duty cycle of the PWM output.
- d) Sketch the triangle wave, V_{REF} , and output V_{PWM} over a 2 ms interval. Label important features!

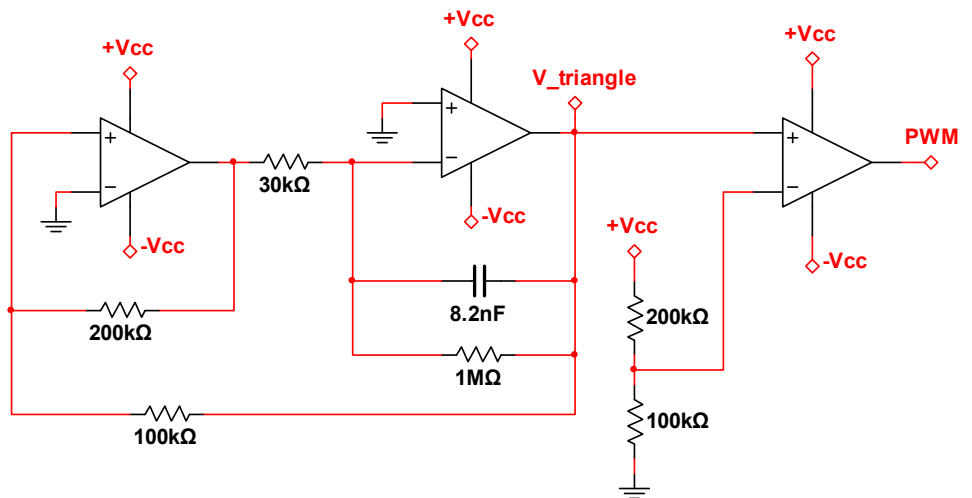


Fig. 7

(continued on next page)

10) Suppose we want to make a night light that turns on when ambient light is low. Ambient light is detected with a photocell, which is basically a light-sensitive resistor. A photocell has high resistance in darkness, and low resistance in bright light. Photocells are notorious for having a wide resistance tolerance (see data sheet).

Consider the voltage comparator circuit shown in Fig. 10. The photocell and resistor R1 form a voltage divider. A reference voltage is produced with a voltage divider made from R2 and a 100 kohm resistor. All voltage dividers and the comparator are powered by $V_{CC} = +5V$. The design constraints are below:

- R1 and R2 must be chosen from: 1 kohm, 10 kohm, 100 kohm, or 1 Mohm
 - High speed operation is NOT necessary from the comparator (this affects your choice of R).
- (a) Based on the photocell's data sheet, what is the appropriate value of R1 to ensure V_{sig} has widely different values between bright (> 10 lux) and dark conditions?
 - (b) Compute the appropriate value for R2.
 - (c) Would you use $R = 220$ ohm or 10 kohm for the comparator output? Explain.
 - (d) Sketch your circuit, and **explain your reasoning** for how the comparator's (+) and (-) inputs are connected to the V_{sig} and V_{ref} voltage dividers.

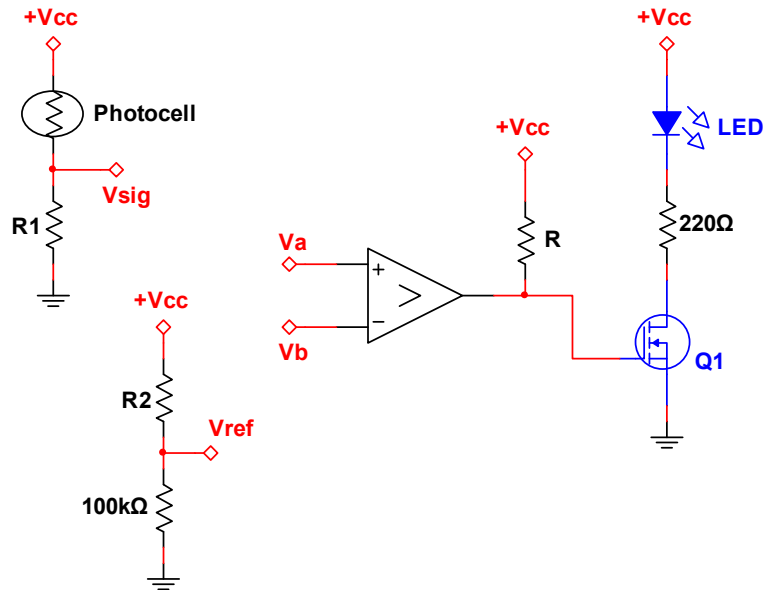


Fig. 10: Night light circuit for Problem 8. The photocell is a light sensitive resistor, where more light causes LOWER resistance.