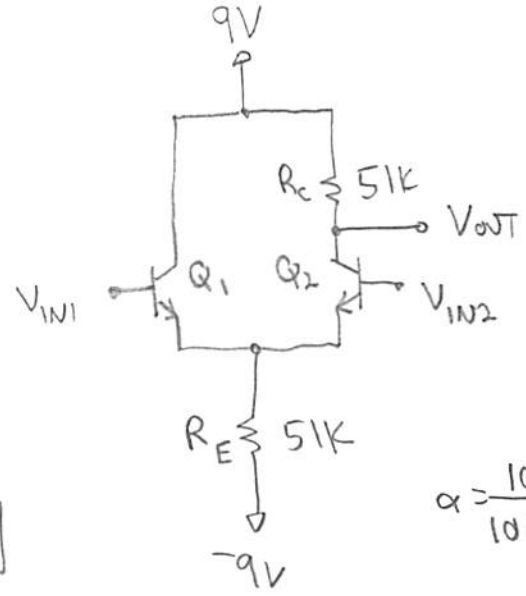


(1)

(a) For quiescent,
assume $V_{IN1} = V_{IN2} = 0$

$$I_T = \frac{-0.7 - (-9)}{51K} = \boxed{0.163 \text{ mA}}$$

$$V_{CQ} = 9 - .99 \frac{.163 \text{ mA}}{2} (51K) = \boxed{4.885 \text{ V}}$$



$$\alpha = \frac{100}{101} = 0.99$$

(b) $r_e' = \frac{.026}{.5 (.163 \text{ mA})} = \underline{\underline{.319 \text{ K}}}$ $A_d = \frac{.99 \times 51K}{2 (.319 \text{ K})} = \boxed{79.1}$

$$A_{cm} = \frac{-.99 \times 51K}{2 (51K)} = \boxed{-0.495}$$

$$CMRR = 20 \log_{10} \left| \frac{79.1}{-0.495} \right| = \boxed{44.1 \text{ dB}}$$

(c) $V_{OUT} = V_{CQ} + \overbrace{\Delta V_{OUT}}^{A_d \Delta V_{IN} + A_{cm} V_{cm}}$

$$= 4.885 + (79.1) \times (4 - 3.98) + (-0.495) \left(\frac{4 + 3.98}{2} \right)$$

$$= 4.885 + 1.582 - 1.975 = \boxed{4.492 \text{ V}}$$

(d) $Z_w = 2(\beta + 1) r_e' = 2(101)(.319 \text{ K}) = \boxed{64.44 \text{ K}}$


2)

$$a) V_{ceq} = V_{cc} - \alpha \frac{I_T}{2} R_c$$

Need I_T !

$$I_T = \frac{-0.7 - (-15)}{100k} = \underline{\underline{.143mA}}$$
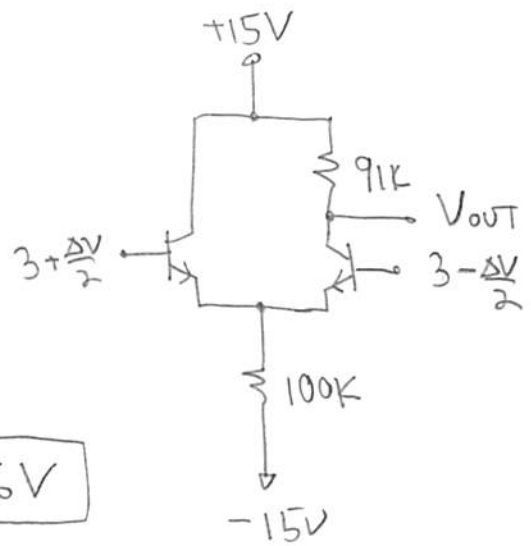
$$V_{ceq} = 15 - .99 \frac{.143mA}{2} (91k) = \boxed{8.56V}$$



$$b) r_e' = \frac{.026}{.5 (.143mA)} = \underline{\underline{0.364k}} \quad A_d = \frac{.99 \times 91k}{2 (.364k)} = \boxed{123.8}$$

$$A_{cm} = - \frac{.99 \times 91k}{2 (100k)} = \boxed{-0.45}$$


$$c) \Delta V_{IN} = \left(3 + \frac{\Delta V}{2}\right) - \left(3 - \frac{\Delta V}{2}\right) = \Delta V = \underline{\underline{.02 \sin 2\pi f_0 t}}$$

$$V_{cm} = \frac{\left(3 + \frac{\Delta V}{2}\right) + \left(3 - \frac{\Delta V}{2}\right)}{2} = \underline{\underline{3V}}$$

$$V_{OUT} = V_{ceq} + A_d \Delta V_{IN} + A_{cm} V_{cm}$$

$$= 8.56 + 123.8 (.02 \sin 2\pi f_0 t) + (-.45) \times 3$$
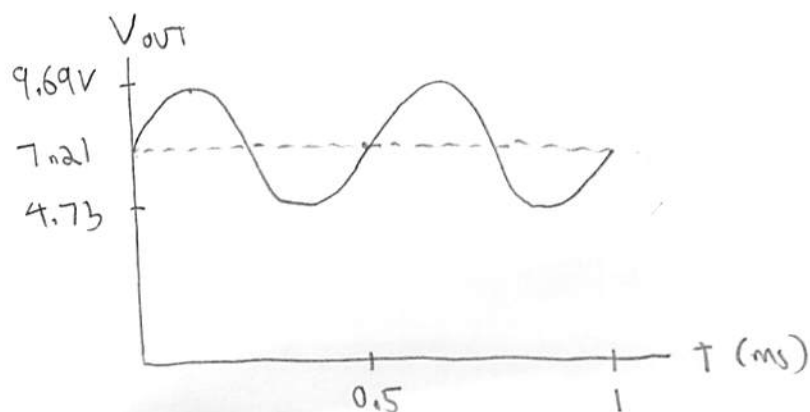
$$= 7.21 + 2.48 \sin 2\pi f_0 t \quad f_0 = 2kHz \rightarrow 1 \text{ period} = .5 \text{ ms}$$



④ $\Delta V = 0.05 \sin 2\pi f_0 t \rightarrow A_d \Delta V = 6.19 \sin 2\pi f_0 t$



Sorry, typo in handout!

Max $V_{out} = 7.21 + 6.19 = 13.4V \leftarrow$ Less than +15V ✓

Min $V_{out} = 7.21 - 6.19 = 1.02V \leftarrow$ clipping?

For Q_2 , V_C cannot go too low (limited by saturation)!

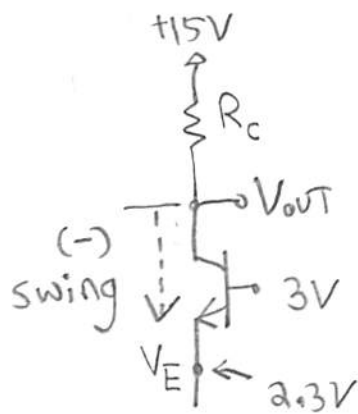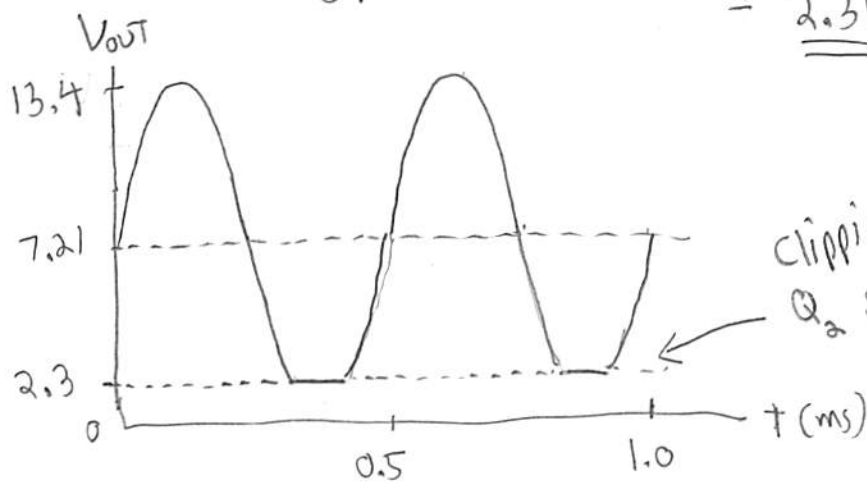$V_{CE} > \underbrace{V_{CE(sat)}}_{0V} \rightarrow V_C > V_E \cong V_{CM} - 0.7$ (assuming $\Delta V \ll V_{CM}$)
 $= \underline{2.3V} \leftarrow$ Min V_{out} is clipped!




⑤ $\Delta V = 0.08 \sin 2\pi f_0 t \rightarrow A_d \Delta V = 9.9 \sin 2\pi f_0 t$

Sorry, typo in handout!

Max $V_{out} = 7.21 + 9.9 = \underline{17.1} \leftarrow$ clipped at 15V! \leftarrow Due to Q_2 cut-off
 cannot exceed V_{CC}

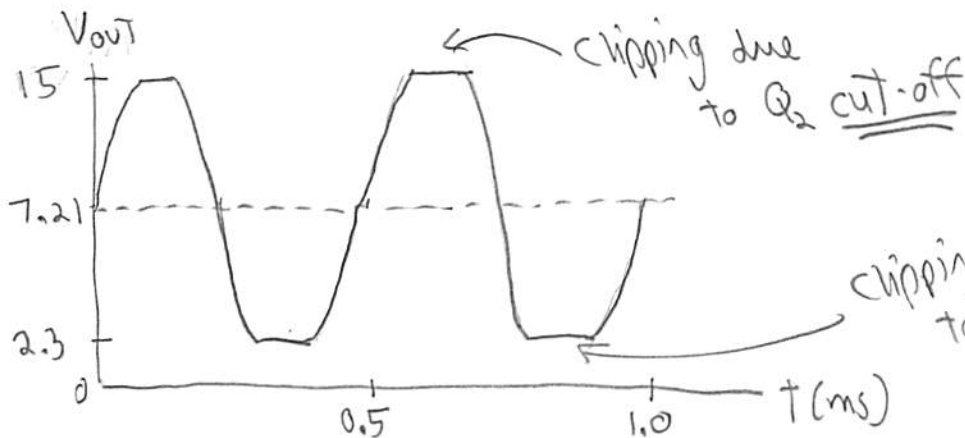Min $V_{out} = 7.21 - 9.9 = -2.7V \leftarrow$ clipped at 2.3V! \leftarrow Due to Q_2 saturation



$$\textcircled{3} \quad \textcircled{a} \quad Z_{in} = 2(\beta+1)r_e' = 2(\beta+1) \frac{.026}{.5 I_T} \geq 50K$$

$$I_T \leq 2(\beta+1) \frac{.026}{.5(50K)}$$

• Start with "Quick" analysis: $\beta=100 \rightarrow I_T \leq 2(101) \frac{.026}{.5(50K)} = \underline{.21mA}$

• 2N3904 Data sheet: $\beta \sim 225 @ .2mA$

$$\Rightarrow I_T \leq 2(226) \frac{.026}{.5(50K)} = \boxed{0.47mA}$$

\textcircled{b} Data sheet: $V_{BE} \approx \underline{0.63V} @ I_C = \frac{I_T}{2} = .235mA$

$$SO, I_T = \frac{12 - .63}{R_E} \leq .47mA \rightarrow R_E \geq 24.2K$$

use $\boxed{R_E = 27K}$

\textcircled{c} Actual $I_T = \frac{12 - .63}{27K} = \boxed{0.42mA}$ $Z_{in} = 2(225+1) \frac{.026}{\frac{1}{2}(.42mA)}$
 $= \boxed{56K} > 50K \checkmark$

\textcircled{d} $r_e' = \frac{.026}{\frac{1}{2}(.42mA)} = 0.124K$ $A_d = .996 \frac{R_c}{2(.124K)} \geq 100 \rightarrow R_c \geq 24.9K$

$$\alpha = \frac{225}{226} = .996$$

choose $\boxed{R_c = 27K}$

\textcircled{e} Actual $A_d = .996 \frac{27K}{2(.124K)} = \boxed{108.4}$

$$V_{CQ} = 12 - .996 \frac{.42mA}{2} (27K) = \boxed{6.35V}$$

$$A_{cm} = -.996 \frac{27K}{2(27K)} = \boxed{-0.498}$$


$$CMRR = 20 \log_{10} \left(\left| \frac{108.4}{-0.498} \right| \right) = \boxed{46.8 \text{ dB}}$$

4)

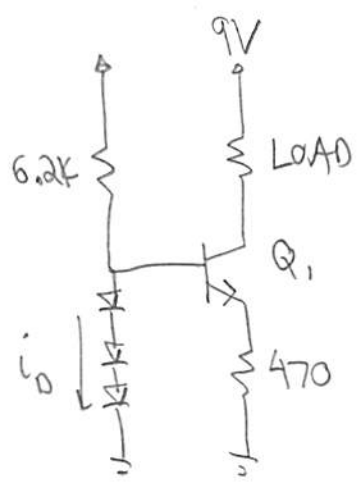(a) Assuming diodes are ON:

$$i_E = \frac{2.1 - 0.7V}{470\Omega} = 2.98mA$$

$$i_L = (0.99)(2.98mA) = \boxed{2.95mA}$$



$$\beta = 100$$

$$\alpha = \frac{100}{101} = 0.99$$


$$i_D = \frac{9 - 2.1V}{6.2k} - \frac{2.98mA}{101} = \boxed{1.08mA} \leftarrow \text{Diodes are happy :)}$$

(b) Voltage Compliance = Max load voltage

$$= 9 - V_{c,min}$$

$$= 9 - (1.4 + V_{(CE,sat)})$$

$$= \boxed{7.6V}$$

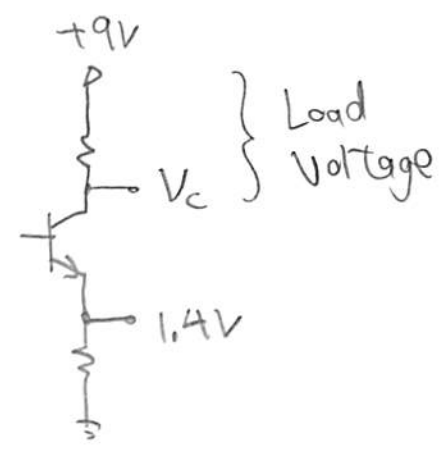

(c) $V_{cc} = 7.5V$.

$$\rightarrow i_E = \frac{2.1 - 0.7}{470} = 2.98mA$$

$$i_L = (0.99)(2.98) = \boxed{2.95mA} \leftarrow \text{SAME as } V_{cc} = 9V! \text{ :)}$$

$$i_D = \frac{7.5 - 2.1}{6.2k} - \frac{2.98mA}{101} = \boxed{0.84mA} \leftarrow \text{Fairly close to } 1mA, \text{ so diodes are still OK.}$$


$$\text{Voltage Compliance} = 7.5 - 1.4 = \boxed{6.1V} \leftarrow \text{Less than } V_{cc} = 9V.$$

5)

(a) Stiff divider?

$$\underbrace{2000 // 620}_{473.3} \stackrel{?}{<} \underbrace{\frac{1}{100} (101) 470}_{474.7 \Omega}$$

YES

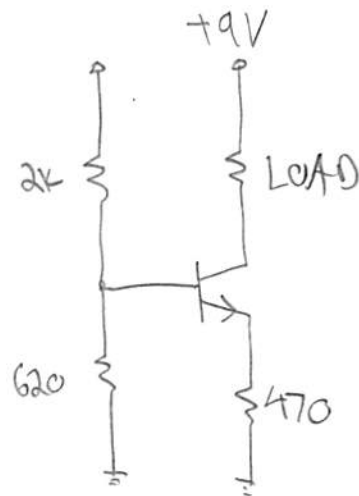

$$\beta = 100$$

$$\alpha = \frac{100}{101} = 0.99$$

$$\begin{aligned} \text{(b)} \quad I_L &= \alpha I_E = 0.99 \frac{V_{BB} - 0.7}{470} & V_{BB} &= 9 \cdot \frac{620}{620 + 2000} = 2.13V \\ &= \boxed{3.01 \text{ mA}} \end{aligned}$$

(c) V_{cc} drops to 7.5V.

$$\Rightarrow V_{BB} = 7.5 \cdot \frac{620}{620 + 2000} = \underline{\underline{1.775V}}$$

$$\Rightarrow I_L = 0.99 \frac{1.775 - 0.7}{470 \text{ K}} = \boxed{2.26 \text{ mA}}$$

↑
Much Lower than $V_{cc} = 9V!$

99


)

6)

ⓐ Assuming Zener is ON:

$$I_E = \frac{5.6 - 0.7}{100} = 0.049 \text{ A}$$
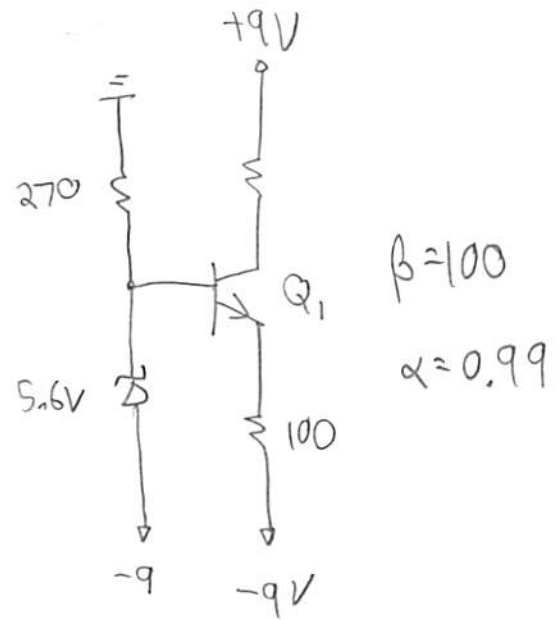
$$I_L = 0.99 (0.049 \text{ A}) = \boxed{48.5 \text{ mA}}$$



ⓑ $I_2 = I_s - I_B$

$$= \frac{0 - (-9 + 5.6)}{0.27 \text{ K}} - \frac{49 \text{ mA}}{101} = \boxed{12.1 \text{ mA}} > 10 \text{ mA} \checkmark$$

YES!

ⓒ Voltage

$$\begin{aligned} \text{Compliance} &= 9 - \underbrace{V_{C, \min}} \\ &= V_E + V_{CE, \text{sat}} \\ &= (-9 + 5.6 - 0.7) + 0 \text{ V} \\ &= -4.1 \text{ V} \end{aligned}$$

$$= 9 - (-4.1) = \boxed{13.1 \text{ V}}$$

7

a) $Z_{in} = 2(\beta+1)r_e' = 2(\beta+1) \frac{.026}{.5 I_T} \geq 50K \rightarrow I_T \leq 2(\beta+1) \frac{.026}{.5(50K)}$

• "Quick" analysis to start:

$\beta = 100 \rightarrow I_T \leq 2(101) \frac{.026}{.5(50K)} = .21mA \leftarrow$


For 2N3904, $I_c =$
 typical $\beta \sim \underline{225}$ @ $\frac{.1mA}{\frac{1}{2} I_T}$

• $I_T \leq 2(226) \frac{.026}{.5(50K)} = \boxed{0.47mA}$

b) want $I_D \sim 1mA$

1N4148: Typical $V_F = .62V @ 1mA$

2N3904: Typical $V_{BE} = .65V @ .47mA$

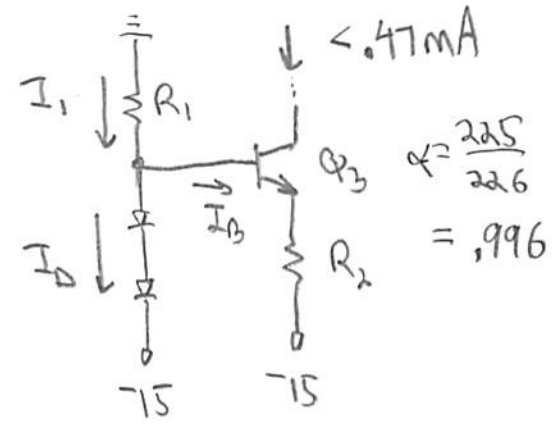

• $I_T = .996 \frac{2 \times .62 - .65}{R_2} \leq .47mA$

$R_2 \geq 1.25K \xrightarrow{\times 1.05} 1.31K$ Choose $\boxed{R_2 = 1.5K}$

• Actual $I_T = .996 \frac{2 \times .62 - .65}{1.5K} = \underline{0.39mA}$

(1.3K would probably be OK)

• $I_D = I_1 - I_B = \frac{0 - (-15 + 2 \times .62)}{R_1} - \frac{.39mA}{225} \sim 1mA$

$R_1 \sim 13.7K \rightarrow$ Choose $\boxed{R_1 = 13K}$

c) Actual $I_T = .996 \frac{2 \times .62 - .65}{1.5K} = \boxed{0.39mA}$

$\times 1.05$

d) $A_v = \frac{\alpha R_c}{2r_e'} \geq 120, r_e' = \frac{.026V}{.5(.39mA)} = .133K \rightarrow R_c \geq 32.0K \rightarrow 33.7K$

Choose $\boxed{R_c = 35K}$
(33K probably OK)

$$\textcircled{c} \text{ Actual } A_d = .996 \frac{35\text{K}}{2(.133\text{K})} = \boxed{131.1}$$

$$V_{ce} = 15 - .996 \left(\frac{39\text{mA}}{2} \right) (35\text{K}) = \boxed{8.2\text{V}}$$

$$\text{CMRR} = 20 \log_{10} \left(\frac{5 \times 10^3 \text{K}}{.133\text{K}} \right) = \boxed{91.5 \text{dB}}$$

8) Start with "Quick":

(a) $2(101)I_T = 2(101) \frac{0.026V}{.5 I_T} \geq 10K$


$I_T \leq \underline{1.05mA}$

For $I_c \sim \frac{I_T}{2} = .5mA$

\hookrightarrow Typ $h_{FE} \approx 93$

So, $2(94) \frac{0.026}{.5 I_T} \geq 10K$

$I_T \leq \boxed{.98mA}$

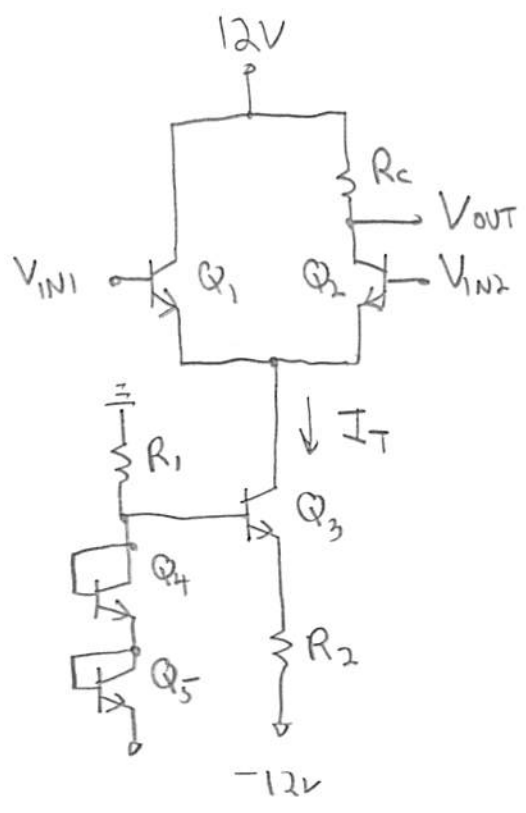

(b) From LM3046 plots:

$Q_3: h_{FE} \sim \underline{100} @ .98mA$ ($\alpha = \frac{100}{101} = .99$) and $V_{BE} \sim \underline{.72V}$

$Q_4, Q_5: V_{BE} \sim .72V @ 1mA$

$\rightarrow \frac{12 - 2(.72)}{R_1} - \frac{.98mA}{.99(101)} \sim 1mA$

$\Rightarrow R_1 \sim 10.5K \Rightarrow$ choose $\boxed{R_1 = 10K}$

(c) $I_T = .99 I_E = .99 \left[\frac{2 \times .72 - .72}{R_2} \right] \leq .98mA$

$R_2 \geq .727K >$ choose $\boxed{R_2 = 820\Omega}$

\hookrightarrow $.76K$ (750Ω probably OK)

$$(d) A_d = \frac{\alpha R_c}{2r_e'}$$

$$r_e' = \frac{.026}{\frac{1}{2} I_T} \leftarrow \text{Actual } I_T = .99 \left[\frac{2 \cdot .72 - .72}{.82K} \right] = 0.87 \text{ mA}$$

$$= \frac{.026}{\frac{1}{2} (.87 \text{ mA})} = .06K$$

$$\text{For } Q_2: \text{ Typical } h_{FE} \approx 90 @ \frac{1}{2} I_T = .435 \text{ mA} \rightarrow \alpha = \frac{90}{91} = 0.989$$

$$A_d = .989 \frac{R_c}{2(.06K)} \geq 100 \rightarrow R_c \geq 12.1K$$

Choose $R_c = 13K$

$$(e) \text{ Actual } A_d = .989 \frac{13K}{2(.06K)} = \boxed{107.1} > 100 \checkmark$$


$$Z_{in} = 2(90+1)(.06K) = \boxed{10.92K} > 10K \checkmark$$

9

$$a) V_{out} = A_d \Delta V + A_{cm} V_{cm}$$

$$= A_d V_s \cdot RO \cdot \frac{L}{L_{Rated}}$$
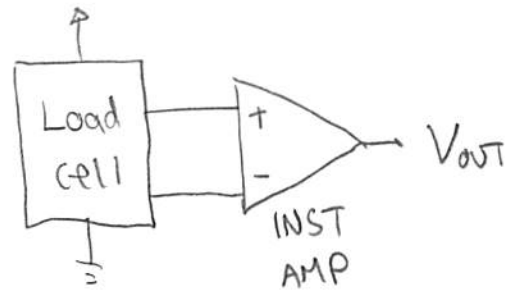
$$= 500 \times 10V \times \frac{3mV}{V} \times \frac{0.020kg}{20kg} = \boxed{15mV}$$



$$b) V_{out} = \underbrace{A_d \Delta V}_{15mV} + \boxed{A_{cm} V_{cm}}$$

↑ want this < 15mV

$$A_{cm} \times 5V < 15mV$$

$$A_{cm} < \frac{15mV}{5V} = .003$$

$$CMRR = 20 \log_{10} \left(\frac{500}{.003} \right) = \boxed{104.4 dB}$$


10

a) When $V_{IN1} = V_{IN2} = V_{CM}$

$$\rightarrow I = \frac{V_{CM} - V_{CM}}{R_G} = 0$$

Therefore,

$$V_{OUT1} = V_{CM} = V_{OUT2}$$

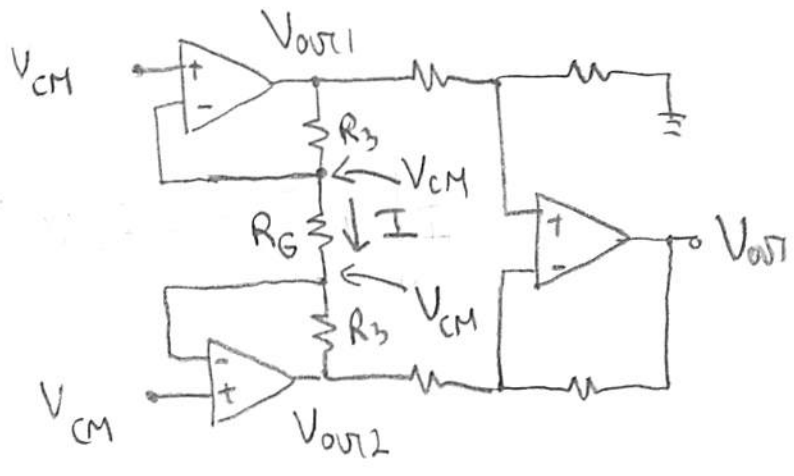


b)

$$I = \frac{V_{IN1} - V_{IN2}}{R_G}$$

$$= \frac{V_{OUT1} - V_{OUT2}}{R_3 + R_G + R_3}$$
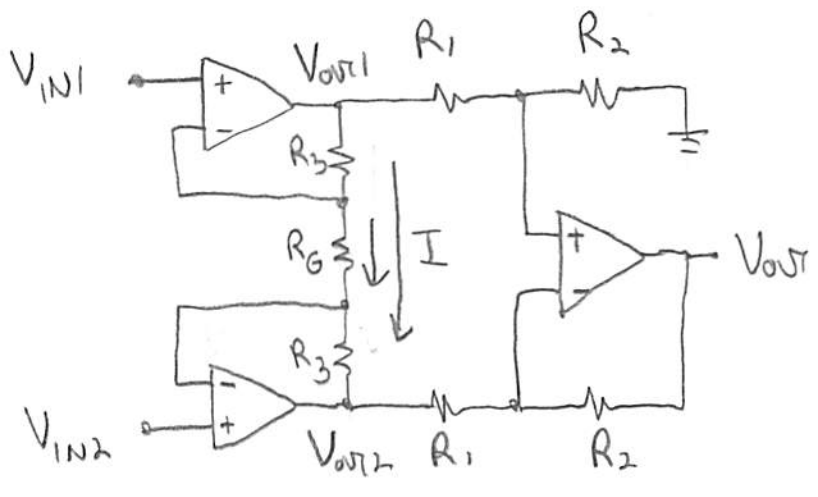
$$= \frac{V_{OUT1} - V_{OUT2}}{R_G + 2R_3}$$



SO, $V_{OUT1} - V_{OUT2} = \frac{R_G + 2R_3}{R_G} (V_{IN1} - V_{IN2}) = \left(1 + \frac{2R_3}{R_G}\right) (V_{IN1} - V_{IN2})$

c) Since $V_{OUT} = \frac{R_2}{R_1} (V_{OUT1} - V_{OUT2})$

$$= \frac{R_2}{R_1} \left(1 + \frac{2R_3}{R_G}\right) (V_{IN1} - V_{IN2})$$

A_d

$$\Rightarrow A_d = \left(1 + \frac{2R_3}{R_G}\right) \times \frac{R_2}{R_1}$$