

Lab 1a: Zener Follower

● GOAL

The overall goal of Lab 1 is to demonstrate a linear voltage regulator to drive a 5V DC brushless fan (e.g. a computer fan). This is a two-week lab.

- Lab 1a is a simple power supply based on a Zener follower.
- Lab 1b explores improved power supply circuits using negative feedback to produce a stable output voltage.



Fig. 0: 5V DC brushless fan.

● OBJECTIVES

The objectives of Lab1a are the following:

- 1) Heat sink:
 - a. Compute the smallest heat sink (largest θ_{SA}) needed for the pass transistor.
 - b. Attach a heat sink to the power transistor.
- 2) Zener Diode:
 - a. Measure the zener voltage and current versus input voltage (V_{IN} is between 12 to 15V).
 - b. Compute the zener resistance and line regulation.
- 3) Zener Follower:
 - a. Measure the power supply efficiency when driving a 5V fan.
 - b. Make appropriate measurements to compute the line and load regulation.
 - c. Better understand the pass transistor's properties.

● GENERAL GUIDELINES

- 1) Each student must design, build, and test his/her own circuits.
- 2) Students are allowed (even encouraged) to work together (e.g. share a test station). **However, you must make measurements and demo your own circuit!**
- 3) Do NOT use "Autoscale" on the scope! Buma will deduct 300 pts if he catches you doing this.
- 4) **Use neat wiring for your circuits! Starting in Lab 2, a messy circuit will cost you 10 pts.**
- 5) This lab (includes Lab1a and Lab1b) has a report. Each student must turn in his/her own lab report. See the course website for the template.

Honor Code Compliance: You must turn in your own work! Blatant duplication of circuit analysis, design, simulations, and/or lab reports will result in ZERO points and possible reporting to the Honor Council.

● PARTS AND MATERIALS

- Lab kit
- Benchtop power supply, multimeter, and probe box (contains banana cables, multimeter probes, etc.)
- Heat sink + mounting kit
- Zener diode: 1N4734A (5.6V)
- Transistor (TIP31A)
- Resistors:

22 ohm (red/red/black)	2 W (really thick resistor!)
220 ohm (red/red/brown)	¼ W
510 ohm (green/brown/brown)	½ W (sort of thick resistor)
2.2 kohm (red/red/red)	¼ W
- 5V DC brushless fan

● PART 1: HEAT SINK FOR PASS TRANSISTOR

Fig. 1 shows the circuit we had designed in class. A heat sink is required to keep the pass transistor Q1 reasonably cool. Remember that device lifetime is reduced by roughly 50% for every 10 °C increase in junction temperature!

How do we choose a heat sink? Our goal is to compute the maximum θ_{SA} that will keep the junction temperature T_J below a desired value. As explained in the Lab 1a tutorial, the main equation is:

$$T_J = T_A + P \cdot (\theta_{JC} + \theta_{CS} + \theta_{SA}) \quad \text{Eqn. (1)}$$

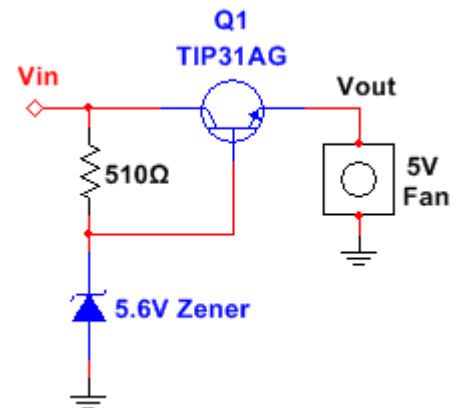


Fig. 1: Zener follower circuit.

- **Task 1a:** Compute the maximum allowable heat sink thermal resistance θ_{SA} . Use the following assumptions:
 - $T_J < 85\text{ °C}$ NOTE: This is a very conservative value (i.e. a very safe operating temperature)
 - $T_A = 25\text{ °C}$ NOTE: This is fine for an open air circuit (i.e. not in a small enclosure)
 - You can use the same power dissipation value from Lecture 01 (see notes)
 - Use the TIP31 data sheet to find θ_{JC}
 - Assume $\theta_{CS} = 0.5\text{ °C/W}$
 - Hint: You should get a value between 22 and 26 °C/W.

- **Task 1b:** Attach the heat sink using the “heat sink mounting kit”
 - We are using a 20 °C/W heat sink, which is slightly larger (physically) than necessary.
 - Fig. 2 shows how the heat sink should be mounted to the “TO-220” package of the transistor.
 - Remember to apply a THIN layer of thermal paste to both the heat sink AND the transistor!
 - There is only one tube of thermal paste, so remember to share!
 - NOTE: The thermal paste fills in tiny air gaps to ensure good thermal conduction.
 - You can consult Buma’s breadboard for guidance.

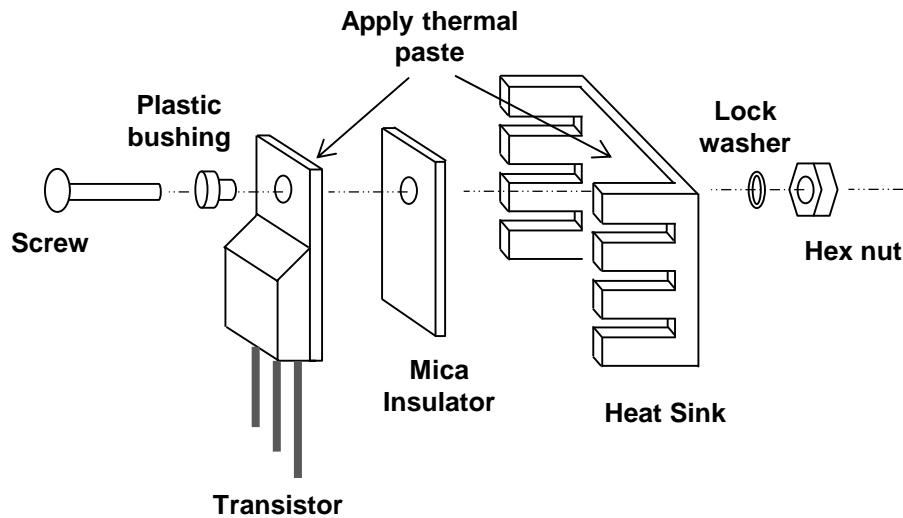


Fig. 2: Remember to apply a thin layer of thermal paste to the "back" of the transistor and "front" of the heat sink!

● PART 2: ZENER DIODE

A zener diode is a decent voltage reference, but it **MUST** be operated along the steep part of the I-V curve (see Lecture 01 notes). For this class, we’ll use 10 mA as a minimum acceptable I_Z . This is not a universally accepted value, but it’s a reasonable rule of thumb for many zeners.

- **Task 2a:** Build the zener voltage reference (Fig. 3). Some comments:
 - You must use NEAT and COLOR-CODED wiring on your breadboard:
 - RED = $+V_{IN}$ (from benchtop power supply)
 - BLACK = GND
 - YELLOW = everything else
 - On the zener, the black band is the cathode (the “crooked” line of the zener symbol).

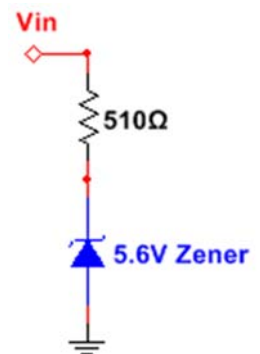


Fig. 3: Zener voltage reference

- Do NOT cram your circuit into a tiny space on the breadboard!
 - It is difficult to measure current in a crowded circuit.
 - You can consult Buma's breadboard for an example.
- **Task 2b:** Measure V_Z and I_Z for $V_{IN} = 12V$ and $15V$ to complete Table 1.
 - Use the multimeter to do this.
 - Set the benchtop supply current limit to 0.75A.
 - Make sure you use the correct settings (e.g. voltage range) to give the most accurate measurements!
 - To measure current, remember that you must "break" the circuit and place the multimeter probes between the break points!

Table I: Zener Measurements

V_{IN}	V_Z	I_Z
12V		
15V		

- **Task 2c:** Data analysis
 - Compute the Zener resistance: $R_Z = \Delta V_Z / \Delta I_Z$
 - It should be less than 10 ohms.
 - How does your experimental value compare with the " Z_{ZT} " value in the 1N4734A data sheet?
 - ❖ The " Z_{ZT} " is the zener impedance at the test current I_{ZT} .
 - Remember that the slope of the I-V curve is $1/R_Z$. A steep slope (small R_Z) is good for a zener!
 - Compute the following: Line Regulation = $(V_{Z,HIGH} - V_{Z,LOW}) / (V_{Z,LOW}) \times 100\%$
 - It should be less than 1%, which is pretty good.
 - NOTE: It turns out zeners in the 5.6V range are better than other values (e.g. 20V) in terms of zener resistance and line regulation.

● PART 3: ZENER REGULATOR

A transistor is needed to buffer the zener from a power-hungry load. The zener only sees the small I_B , while the load is driven by the large I_E . However, transistor power dissipation impacts efficiency and device lifetime. Furthermore, transistor properties (e.g. current gain) are not perfectly constant but instead vary with I_C as well as temperature.

- **Task 3a:** Build the rest of the zener regulator (Fig. 4). Some comments:

- You must still use neat and color-coded wiring.
- Do NOT cram your circuit into a tiny space on the breadboard!
- The TIP 31 pin diagram is on its datasheet (see course website).
- The fan wiring is RED = V_{OUT} and BLACK = GND.
 - The fan wires a little flimsy, so be careful when you insert them into the breadboard.
- Your circuit works when the fan turns on AND the benchtop power supply shows a current draw of roughly 0.25A.
 - The heat sink will get pretty warm after about 30 seconds of operation.

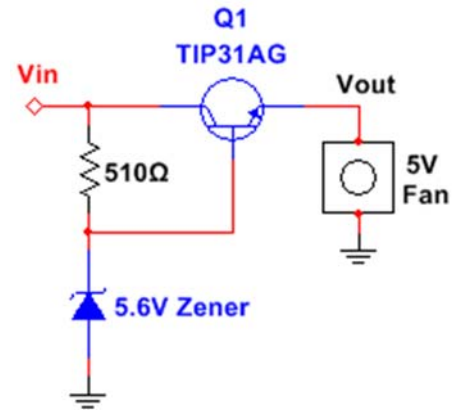


Fig. 4: The mighty Zener follower!

- **Task 3b:** Measure the efficiency of your zener regulator for $V_{IN} = 12V$ and $15V$.
 - To do this, make the necessary multimeter measurements and calculations to complete Table 2.
 - You should get an efficiency of roughly 40% for $V_{IN} = 12V$ and 30% for $V_{IN} = 15V$.
 - Compute the following: Line Regulation = $(V_{OUT,HIGH} - V_{OUT,LOW}) / (V_{OUT,LOW}) \times 100\%$
 - NOTE: Line regulation describes V_{OUT} stability for different V_{IN} but the SAME load.

Table II: Zener Follower Measurements

V_{IN}	I_{IN}	V_{OUT}	I_{OUT}	Computed Efficiency
12V				
15V				

- **Task 3c:** The transistor's V_{BE} decreases with temperature by approximately $-2 \text{ mV}/^\circ\text{C}$. The temperature dependence of V_{BE} is a real issue and must not be ignored in practical applications!
 - Set $V_{IN} = 15V$ and turn off power to the breadboard.
 - Let the TIP31 transistor cool off for about 5 minutes.
 - Configure the multimeter to measure DC voltage (use the 2V range).
 - Measure the transistor's V_{BE} IMMEDIATELY after turning on power to the board! Enter this “cool” V_{BE} value into Table 3.
 - Keeping the multimeter probes on V_{BE} , you should see V_{BE} decrease as the transistor warms up.
 - After about 5 minutes, enter the “hot” V_{BE} value into Table 3.

Table III: “Cool” and “Hot” V_{BE} Measurements ($V_{in} = 15V$)

Cool V_{BE}	Hot V_{BE}

- **Task 3d:** The transistor’s V_{BE} as well as its current gain depend on both temperature AND current. So annoying! We’ll vary the load current by replacing the fan with different resistors.
 - Make the necessary multimeter measurements to complete Table 4.
 - Remember to use the proper multimeter settings to get the most accurate measurements!
 - Compute Load Regulation = $(V_{OUT,MAX} - V_{OUT,MIN}) / (V_{OUT,MIN}) \times 100\%$
 - Load regulation measures V_{OUT} stability for the same V_{IN} but DIFFERENT load currents.

Table IV: Measurements for different load currents ($V_{in} = 15V$)

R_{LOAD}	V_{OUT}	I_{OUT}	I_B	Computed current gain
2.2 kohm				
220 ohm				
22 ohm				

● PART 4: CIRCUIT DEMO

- **Show Buma your working circuit in all its glory!**
 - The load should be the 5V fan.
 - Demonstrate that V_{OUT} is near 5V as V_{IN} is varied from 12 to 15V.
- **Show Buma the following data:**
 - Heat sink calculation
 - Computed zener resistance and line regulation (based on Table 1)
 - Computed efficiencies (based on Table 2)
 - “Cool” and “Hot” V_{BE} (Table 3)
 - Load regulation and Table 4

(End of Lab 1a)