

PreLab 1: Linear Regulator

• GOAL

The overall goal of Lab 1 is to demonstrate a linear voltage regulator to drive a 5V DC brushless fan (e.g. a computer fan). This is a two-week lab.

- Lab 1a is a simple power supply based on a Zener follower.
- Lab 1b explores improved power supply circuits using negative feedback to produce a stable output voltage.

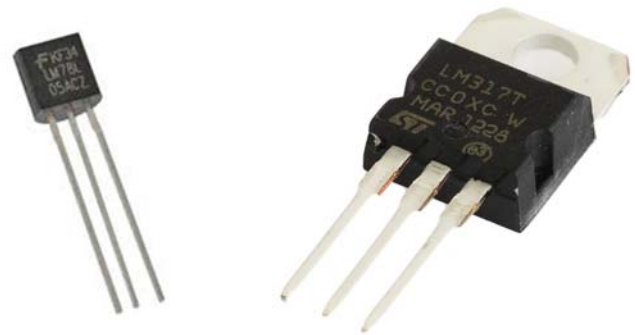


Fig. 0: (Left) 78L05 linear regulator (+5V @ 100 mA) (Right) LM317 adjustable linear regulator (1.5A).

• GENERAL GUIDELINES

- 1) Each student must turn in his/her own PreLab assignment (include calculations, schematics, and waveforms).
- 2) Students are allowed (even encouraged) to work together. However, you must turn in your own work!
- 3) **SAVE ALL SCHEMATIC AND WAVEFORM FILES** – you will need them later.

• INTRODUCTION

The Zener follower from Lab 1a works pretty well, but its output V_{OUT} does change slightly with load current. In other words, the Zener follower has pretty good “*load regulation*”, but it could be better. Improved performance is possible by including *negative feedback* (see Lecture 02 notes), which is a major topic of Lab 1b!

In most practical situations involving a voltage regulator, the most cost-effective and best performing option is to use a convenient integrated circuit (IC) chip. During Lab 1b, we will explore three regulators: (1) a modified circuit based on the Lab 1a Zener follower (2) a fixed +5V regulator (78L05 chip) (3) an adjustable regulator (LM317 chip).

• ZENER FOLLOWER WITH FEEDBACK

In class, we discussed how to add an op amp and a voltage divider to produce a more stable voltage regulator. However, we only discussed the case when $V_{OUT} > V_Z$.

- **TASK 1:** Sketch (by hand) a modification of the Lab 1a circuit (see Fig. 1), where you add an op amp and 10 kohm potentiometer to produce a +5V output. Some comments:
 - Use HW 1 (Problem 10) to decide where to put the voltage divider.

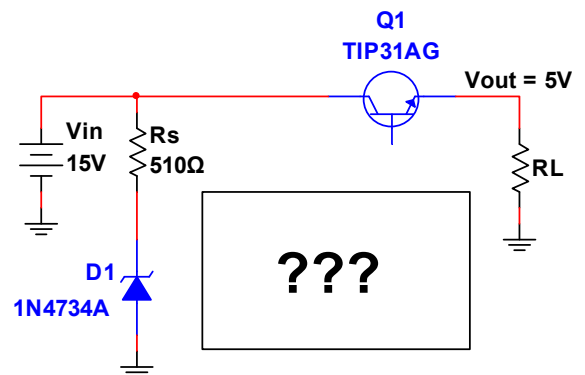


Fig. 1: Figure out how to add an op amp and 10 kohm potentiometer to make a 5V voltage regulator.

- Use the Lecture 02 notes (page 2.2) to figure out how to use a potentiometer.
- **TASK 2: Simulate your circuit in Multisim.** Some comments:

- Use $V_{IN} = 15V$.
- The 1N4734A is the 5.6V zener.
- Use the TIP31AG transistor.
- Use the LF356N op amp. You only need to connect the following pins:
 - ❖ Pin 2 = (-) input, Pin 3 = (+) input,
 - ❖ Pin 4 = GND, Pin 6 = output, Pin 7 = V_{IN}
- Use a 10 kohm potentiometer.
 - ❖ Double-click on the potentiometer, go to the “Value” property and make sure “Resistance = 10 kohm” and “Increment = 1%”.
 - ❖ If you want the potentiometer wiper to be on the right side, use “flip horizontal” rather than “rotate”!
 - ❖ Fig. 2(top) shows the correct orientation using “flip horizontal”. ☺
 - ❖ Fig. 2 (bottom) shows the incorrect orientation using “rotate”. ☹

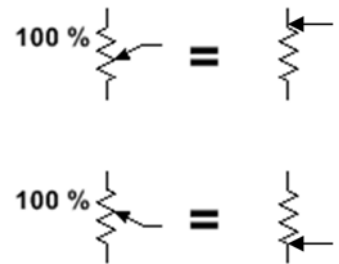


Fig. 2: The correct (top) and incorrect (bottom) orientation of the potentiometer in Multisim.

- Initially use a load resistor $R_L = 2.2 \text{ kohm}$.
- Place voltage and current probes on V_{OUT} .
- Perform either an “Interactive Simulation” or “DC Operating Point Analysis” to find the correct potentiometer setting to achieve $V_{OUT} = 5V$ (within 0.02V). What setting (e.g. 64%) works for you?
- Next, make the measurements to complete Table 1.

Table 1: V_{OUT} vs R_L

R_L	2.2 kohm	220 ohm	22 ohm
V_{OUT}			
I_{OUT}			

- **TASK 3: Data Analysis**
 - Compute the load regulation (see Lab 1a handout) for your AWESOME voltage regulator.
 - How does it compare to your measurement from Lab 1a (Task 3d)? It should be better.

❖ **Submit answers to all TASKS (show all work!) and your Multisim circuit schematic.**

(End of PreLab 1)