

Lecture 1 : Emitter Follower

1. BJT Review
2. Emitter Follower Analysis
3. Emitter Follower Design

★ minerva.union.edu/bumat

- PreLab 1 due next Thu (Sep 19)
- HW1 due next Fri (Sep 20)

Textbook

Reading :

- 6-3 Transistor currents
- 6-8 Reading data sheets
- 6-10 Variations in current gain
- 7-11 pnp transistors
- 9-6 Darlington
- 9-7 Zener Follower

Analysis vs. Design

- ECE 248: Analyze circuits with diodes and transistors.

★ ECE 363: Design circuits with op amps and transistors!

↳ "Accuracy"

[e.g. Stable voltage gain]


op amps typically output $< 25 \text{ mA}$

↳ "Heavy Lifting"


[e.g. Delivers load current]

Small transistor (100 mA)
Power transistor ($\sim 5 \text{ A}$)

Example Emitter Follower

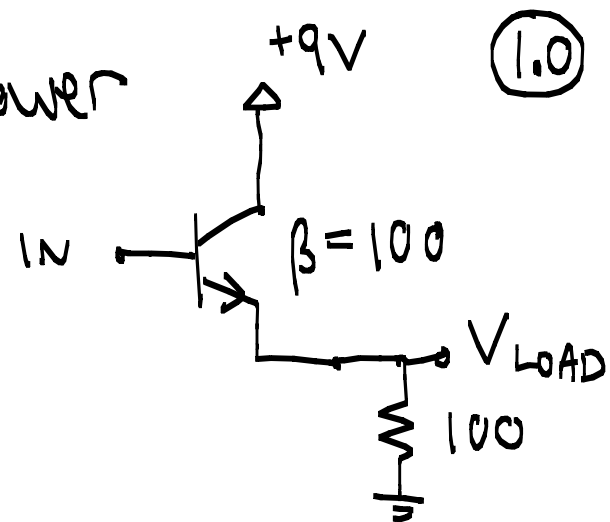

Example Audio Amplifier

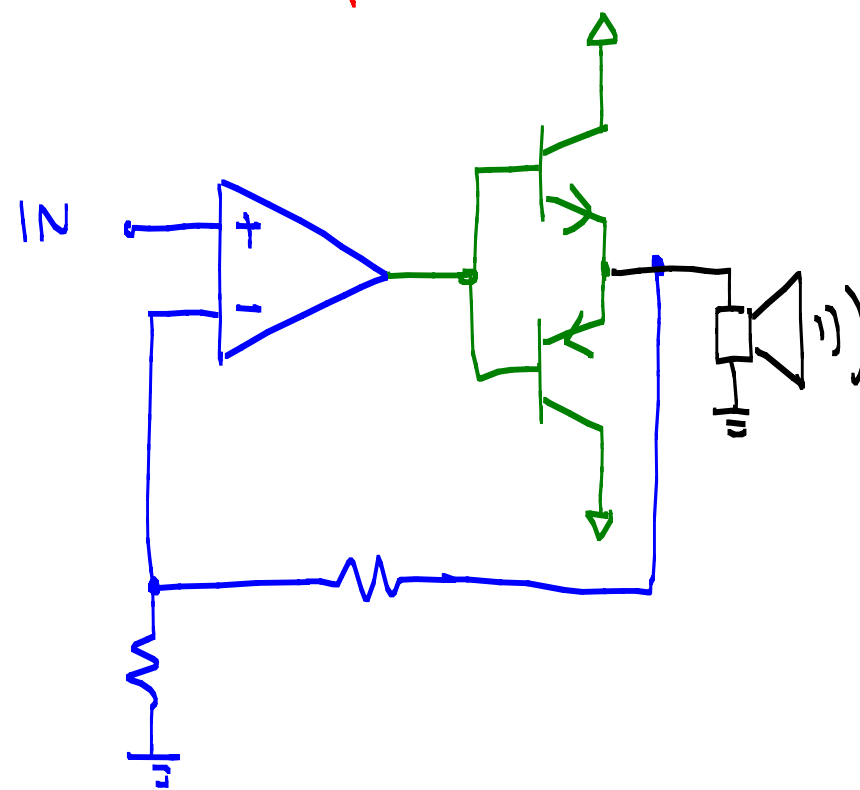


1. Linear DC Supply

e.g. 12V

- Many electronic devices require a DC voltage.
- Wall outlet provides AC voltage ($120V_{rms}$, 60Hz)
- Linear DC power supplies have the following:



Benchtop Supply

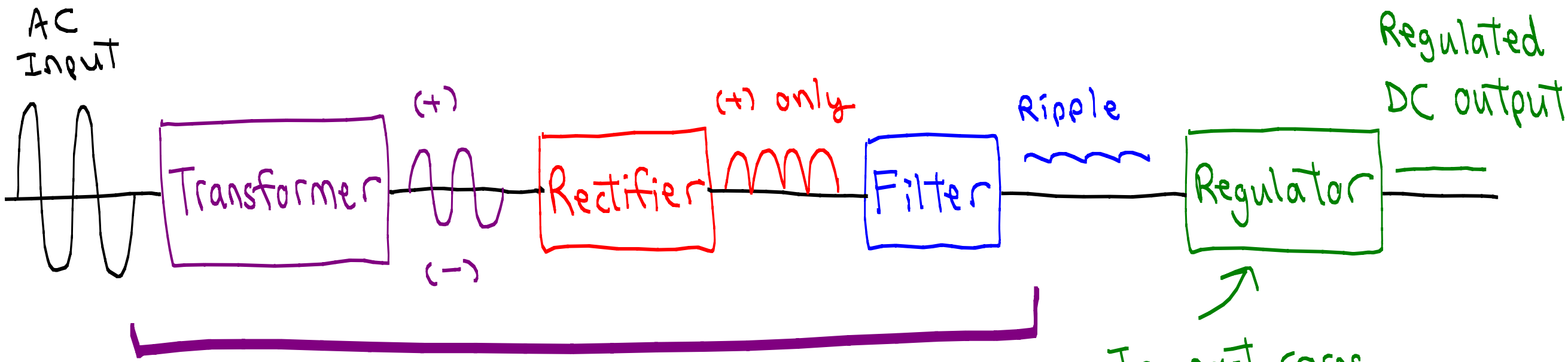

Unregulated DC supply

In most cases, you would use an IC chip (e.g. LM7812)

Q: How to make a voltage regulator? → 3 key ingredients!

- ① Voltage reference
 - Powered by V_{IN}
 - Produces stable V_{REF}

- ② Pass Transistor
 - Acts like a pressure valve

Control knob is V'

Input is V_{IN}


Output $V_{OUT} < V_{IN}$

- ③ Negative Feedback

• Monitor V_{OUT} to adjust pass transistor



If V_{OUT} too high $\rightsquigarrow V_F > V_{REF} \rightsquigarrow V' \downarrow \rightsquigarrow V_{OUT} \downarrow \text{☺}$

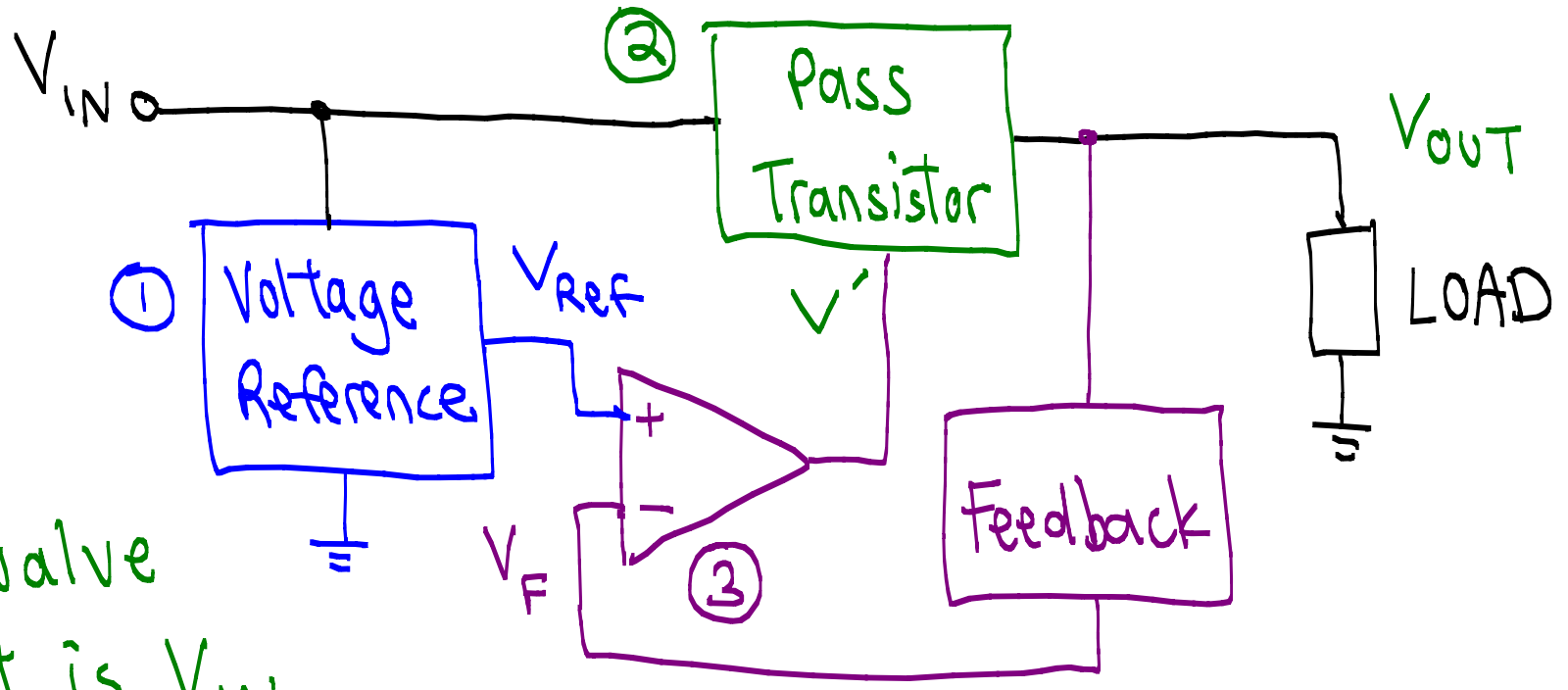If V_{OUT} too low $\rightsquigarrow V_F < V_{REF} \rightsquigarrow V' \uparrow \rightsquigarrow V_{OUT} \uparrow \text{☺}$




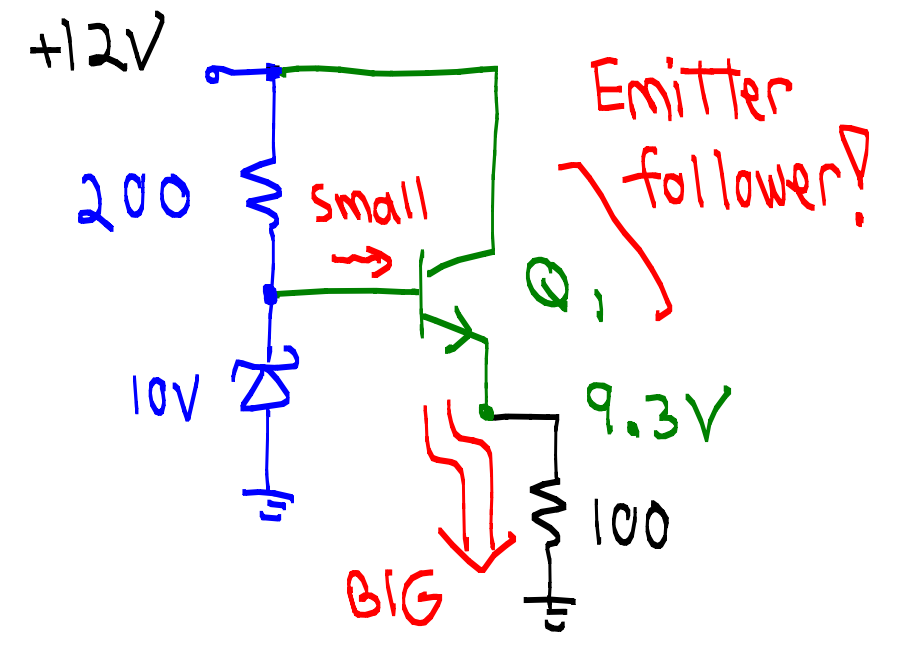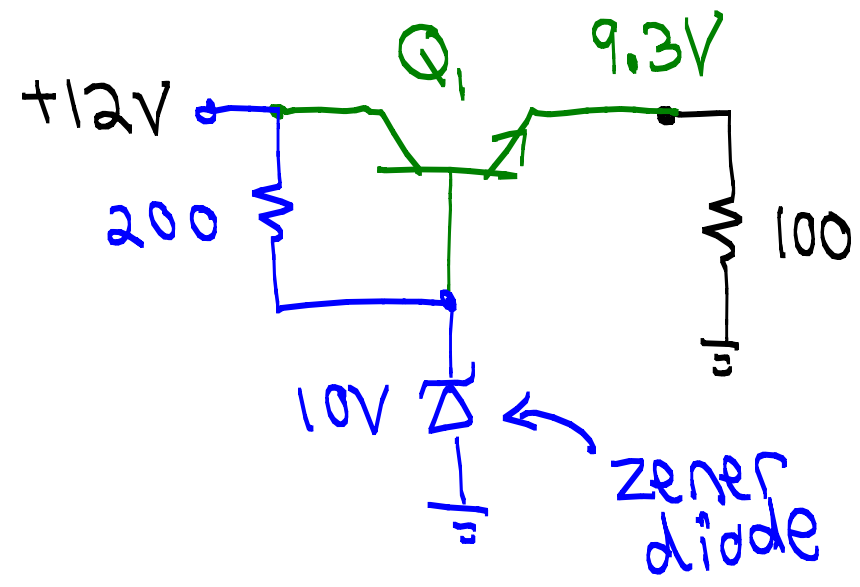2. Emitter Follower Analysis

• Recall the zener follower from ECE 248:



• "Quick" analysis (ECE 248 style):


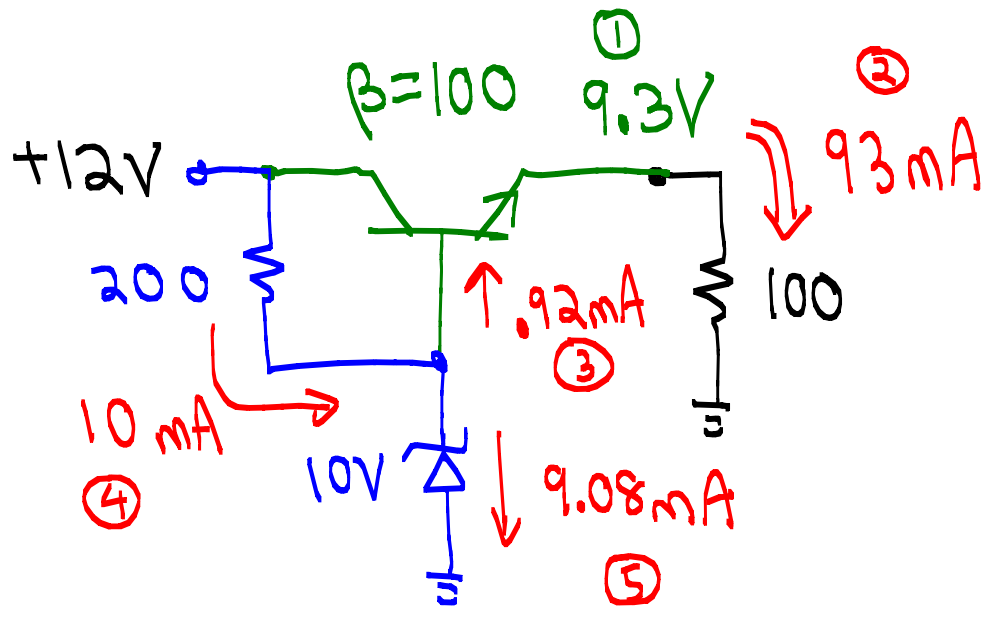


* Problems with this circuit?


- ∴ ① Value of V_{out} ← limited by available V_Z
- ∴ ② No feedback! ← V_{out} is not actively stabilized

Diode Review

"Typical" Diode

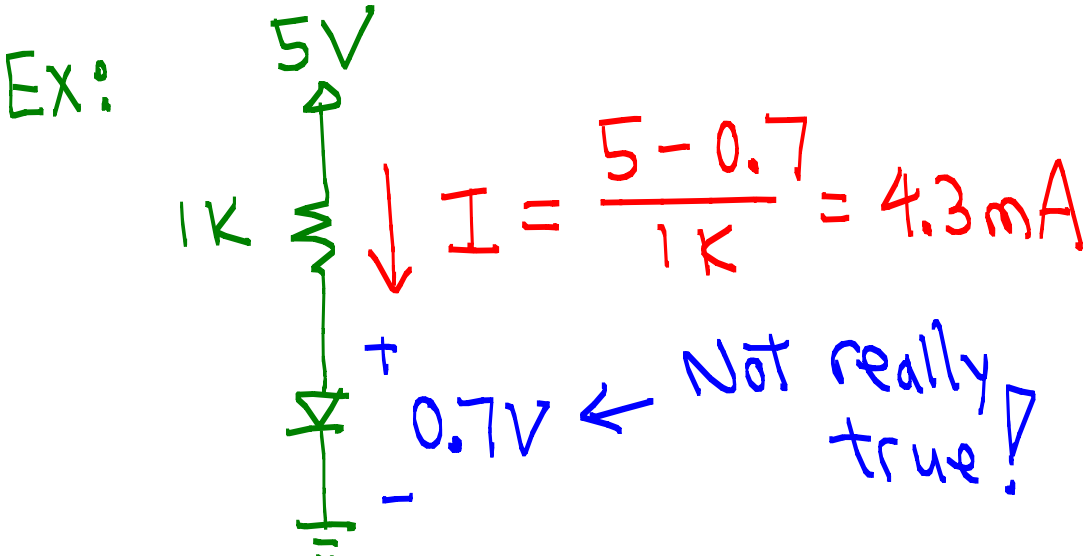
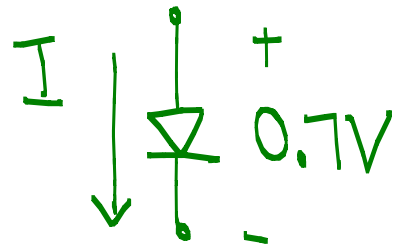


Ex: 1N4148

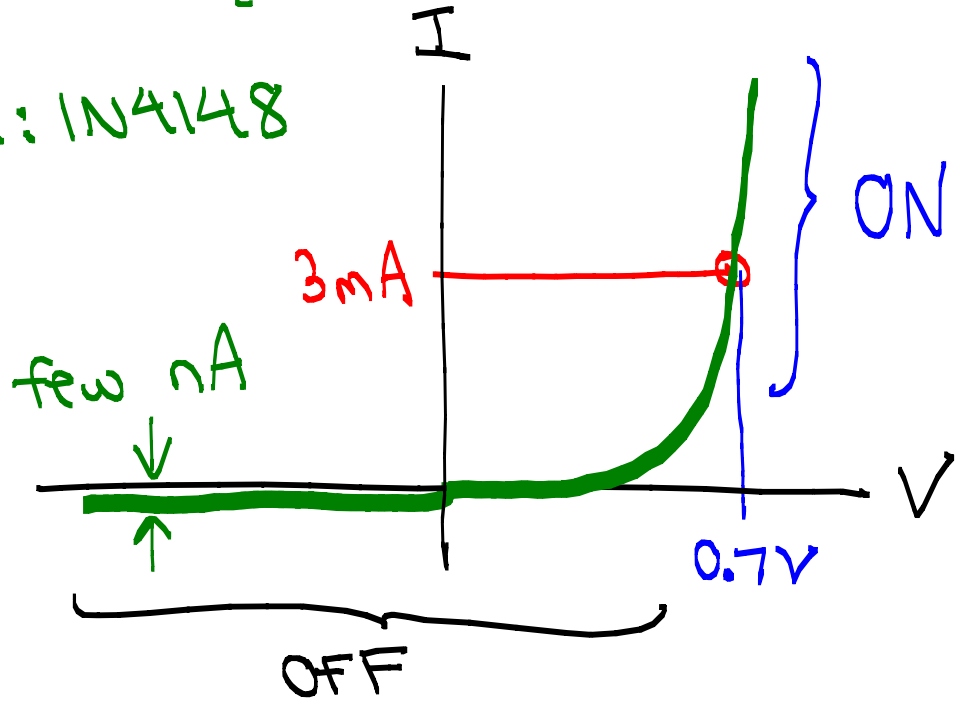

Zener Diode


used "backwards"

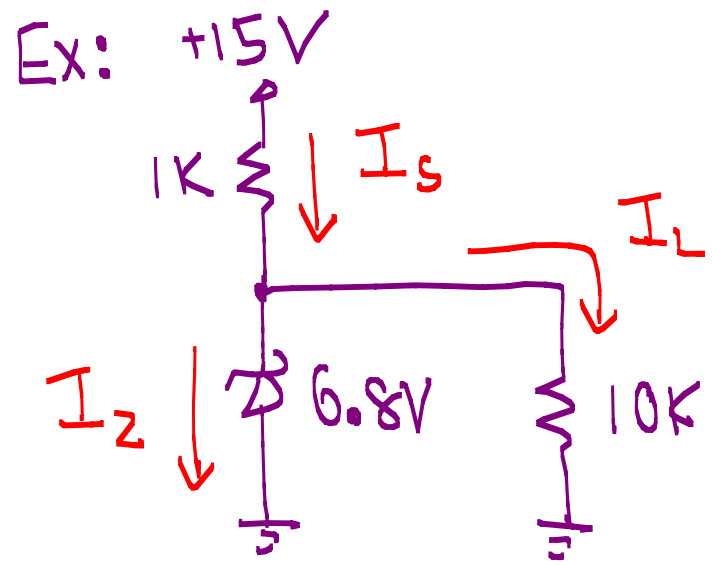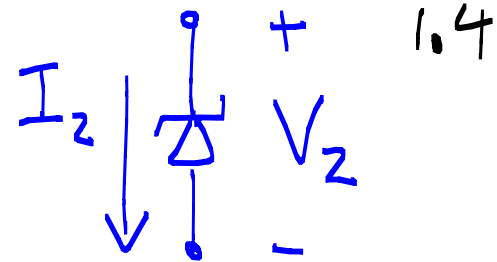

$$I_2 = I_s - I_L$$

$$= \frac{15 - 6.8}{1K} - \frac{6.8 - 0}{10K}$$
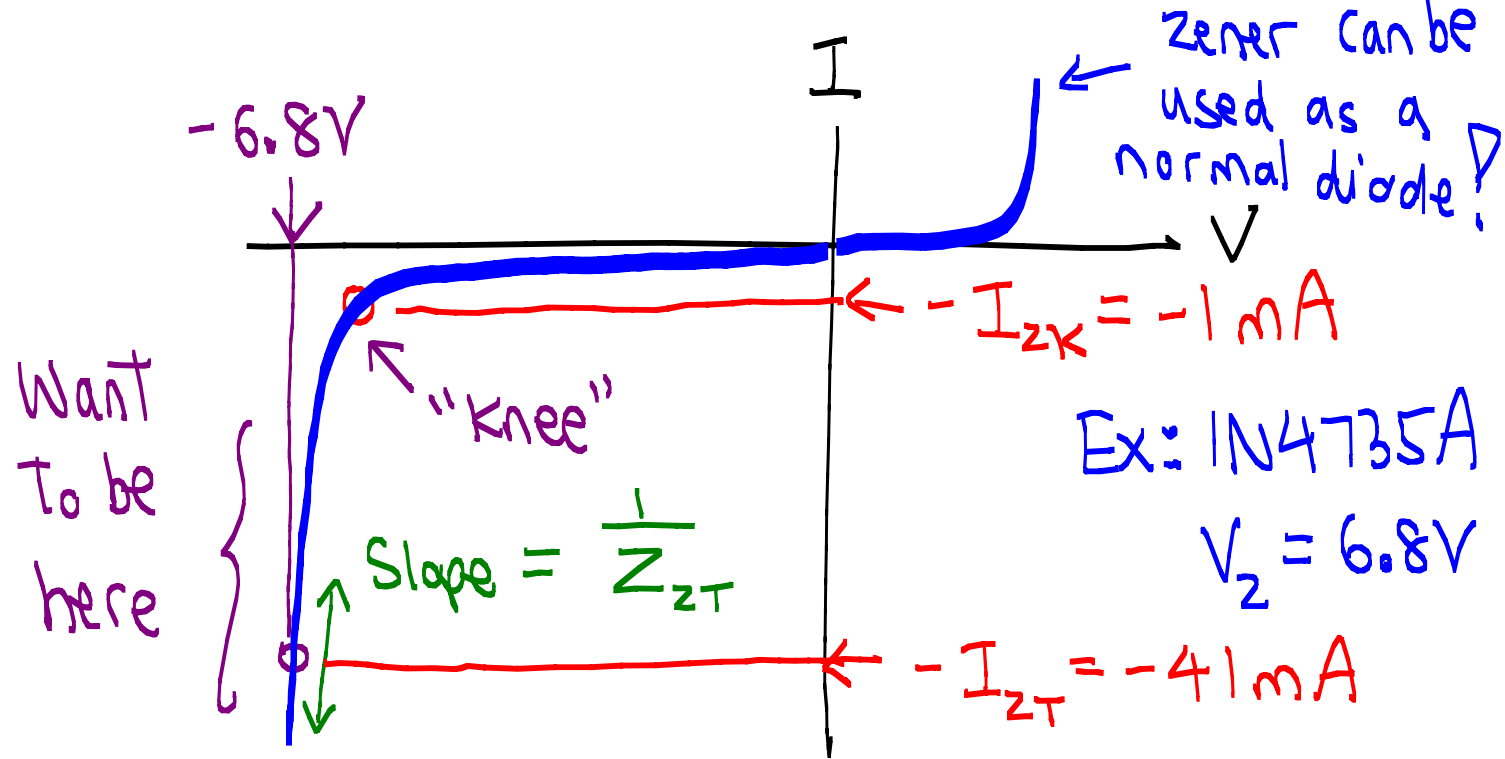
$$= \underline{\underline{7.52 \text{ mA}}}$$




Ex: 1N4735A
 $V_z = 6.8 \text{ V}$

Transistor Review (Active Mode)

C = Collector
 B = Base
 E = Emitter

$$i_c = \beta i_B = \alpha i_E$$

$\frac{\beta}{\beta+1}$

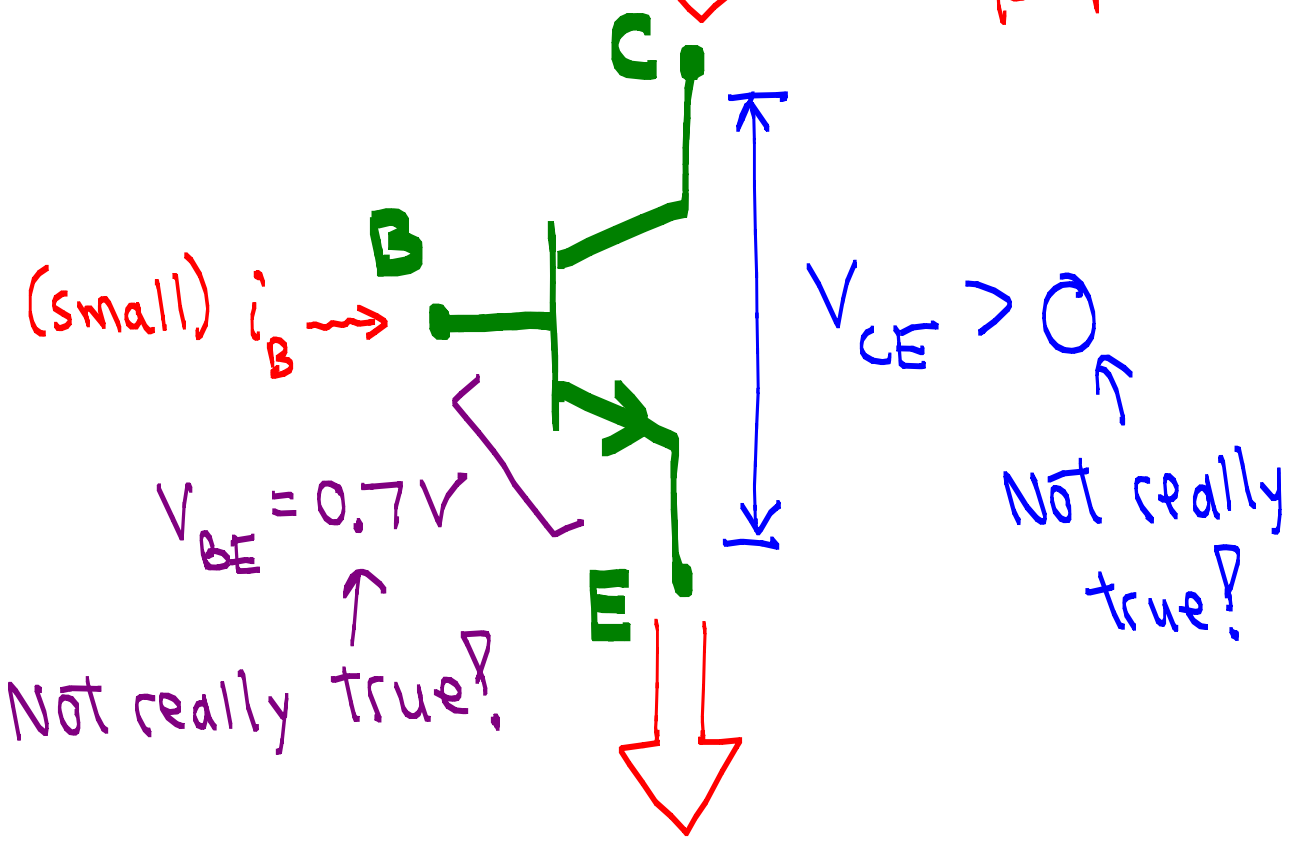


$$i_E = (\beta + 1) i_B = i_c + i_B$$

2N3904



TIP31

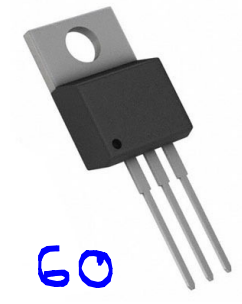

2N3055




1.5

Typical

$\beta = 200$	60	30
$I_c = .010A$	1A	5A

Ex:

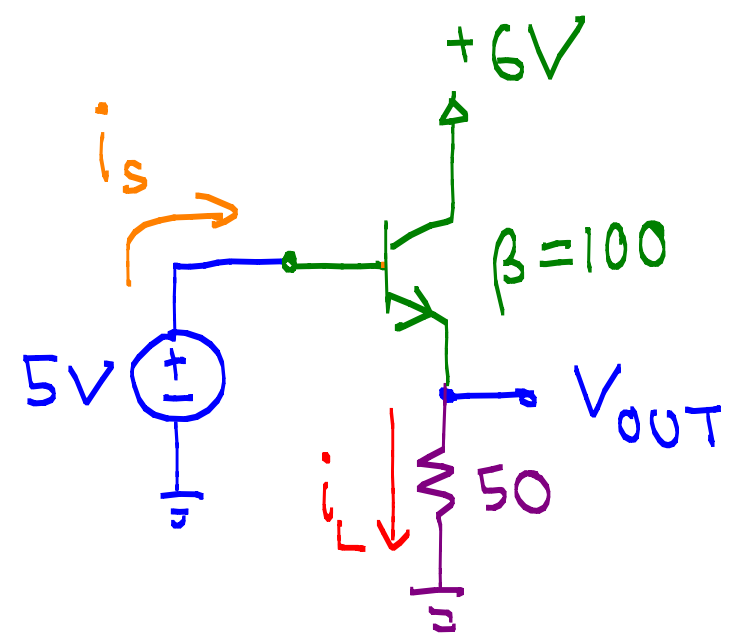


- ① $V_{OUT} = 5 - 0.7 = 4.3V$
- ② $i_L = 4.3 / 50\Omega = 0.086A = 86mA$
- ③ $i_s = \frac{86mA}{101} = 0.85mA$

• Power Dissipation

Device failure is usually due to thermal breakdown!

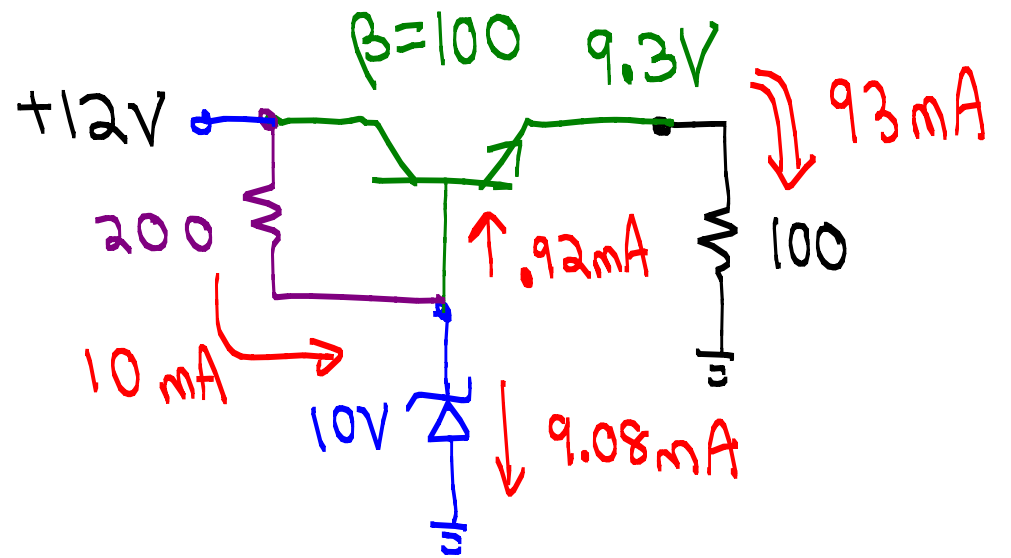★ Rule of thumb: Stay below 50% of device's max power limit!



Ex: 1/4 W resistor

$$\begin{aligned}
 P &= I^2 R = \frac{V^2}{R} \\
 &= (.01)^2 200 = \frac{(12-10)^2}{200} \\
 &= .02 W = \underline{\underline{20 \text{ mW}}} \checkmark
 \end{aligned}$$

1/2 W zener

$$\begin{aligned}
 P &= I_z V_z \\
 &= (9.08 \text{ mA})(10 \text{ V}) \\
 &= \underline{\underline{90.8 \text{ mW}}} \checkmark
 \end{aligned}$$


0.6 W Transistor

$$\begin{aligned}
 P &= I_B V_{BE} + I_C V_{CE} \\
 &= (.92 \text{ mA})(0.7) \\
 &\quad + .99 (93 \text{ mA})(12-9.3) \\
 &= \underline{\underline{249.2 \text{ mW}}} \checkmark
 \end{aligned}$$

Q: What determines max power limit?


A: The temperature of the "junction" must not exceed a max value!
(BJT: 150°C, MOSFET: 175°C)

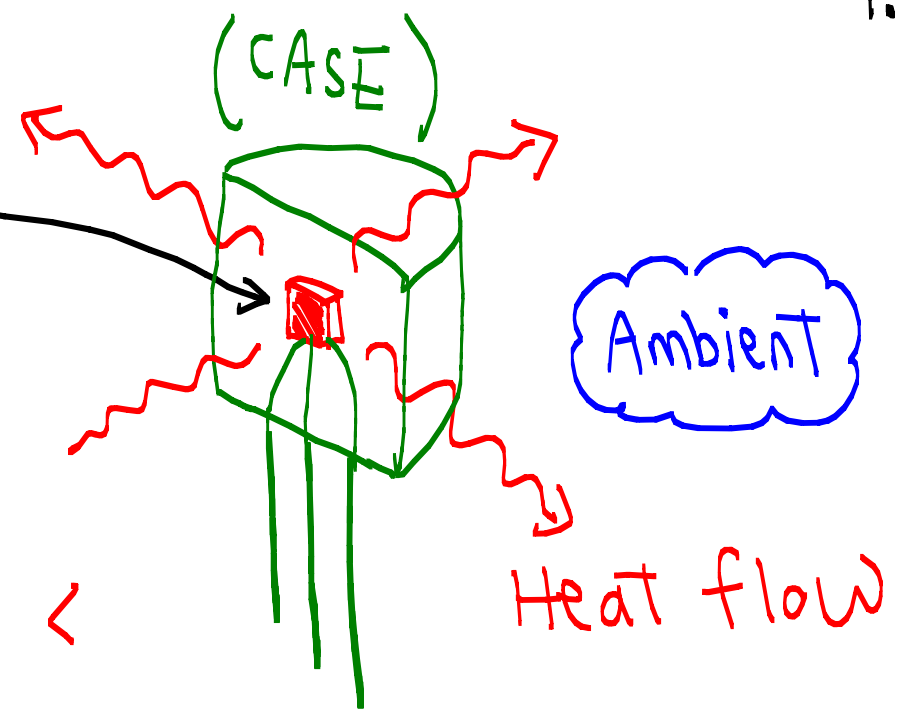⇒ Can compute T_J with "Thermal Ohm's Law"



$$T_J - T_A = P \times \Theta_{JA}$$

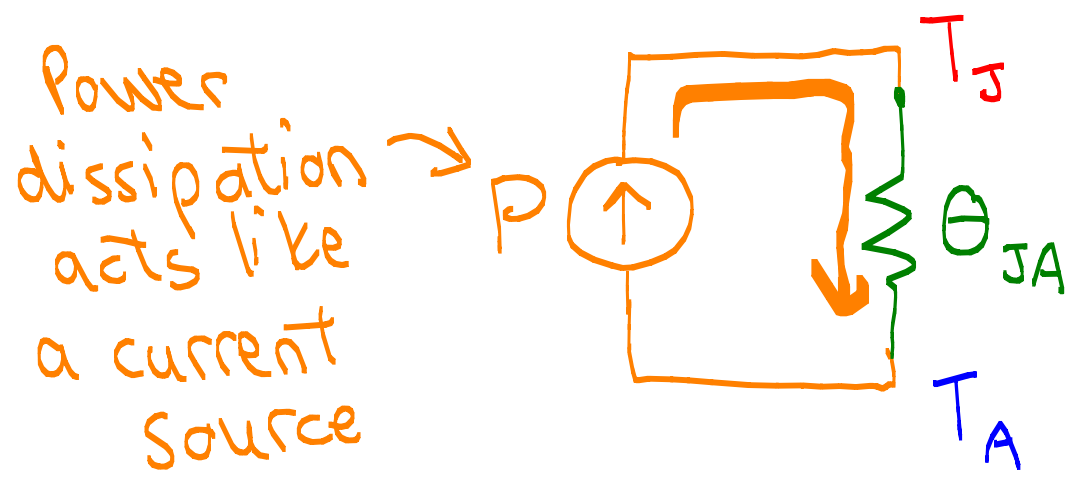Thermal resistance from junction to ambient



① Power dissipation in junction creates heat

② Heat travels from junction to case

③ Heat escapes from case to ambient

Θ_{JA}

Thermal Characteristics $T_a = 25^\circ\text{C}$ unless otherwise noted For 2N3904 transistor

Symbol	Parameter	Max.			Units
		2N3904	*MMBT3904	**PZT3904	
P_D	Total Device Dissipation Derate above 25°C	625 5.0	350 2.8	1,000 8.0	mW mW/ $^\circ\text{C}$
$R_{\theta JC}$	Thermal Resistance, Junction to Case	83.3			$^\circ\text{C/W}$
$R_{\theta JA}$	Thermal Resistance, Junction to Ambient	200	357	125	$^\circ\text{C/W}$

For BJT, max $T_J = 150^\circ\text{C}$!

$(T_A = 25^\circ\text{C})$


$$P_{\text{Rating}} = \frac{T_J - T_A}{\theta_{JA}}$$

$$= \frac{150 - 25^\circ\text{C}}{200^\circ\text{C/W}} = \underline{\underline{.625\text{ W}}}$$

$(T_A = 75^\circ\text{C})$


$$P_{\text{Rating}} = \frac{150 - 75^\circ\text{C}}{200^\circ\text{C/W}} = \underline{\underline{.375\text{ W}}}$$

Derating Curve

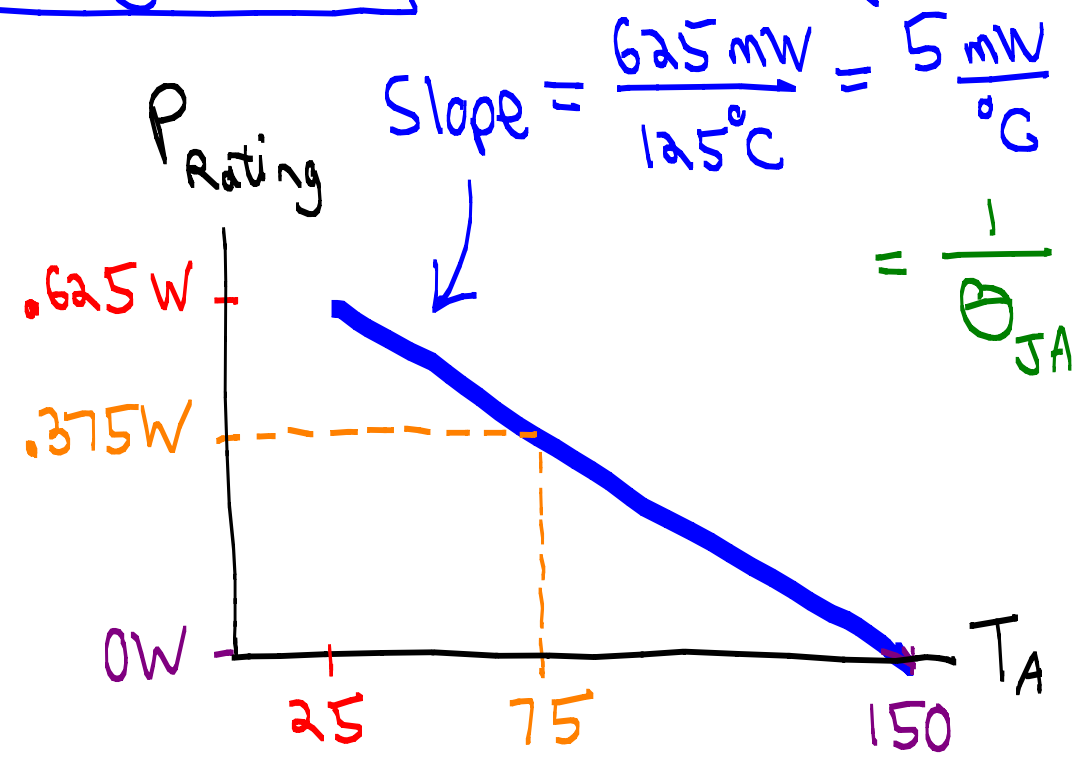

3. Emitter Follower Design

Q: How to choose components?

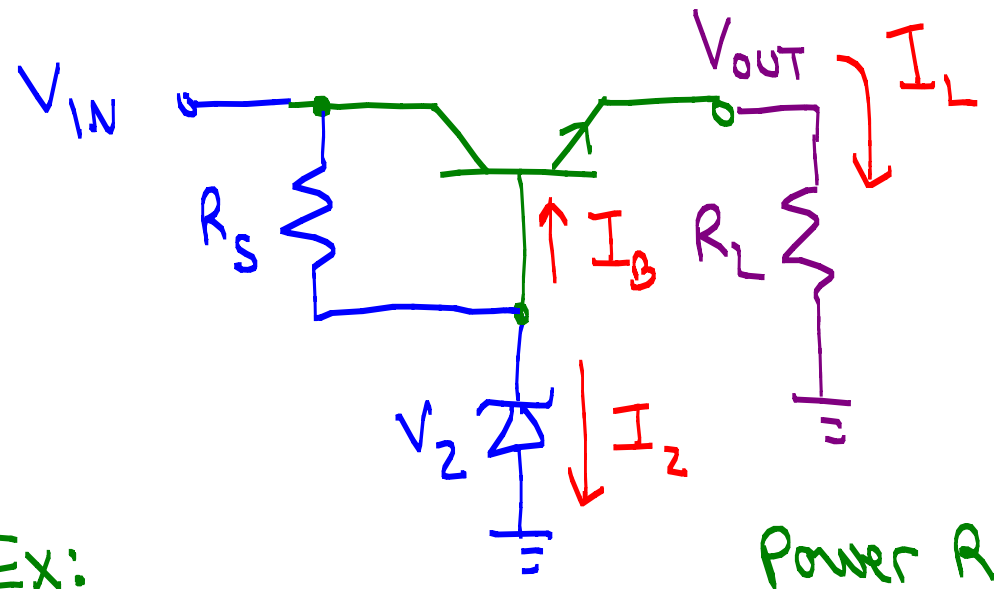

★ Know your load: Greatest demand (e.g. max current)

★ Proper Transistor:

- Max I_c and V_{CE}

★ Zener: $I_z \geq 10\text{mA}$

★ Power rating for all components!

Ex:


Transistor	Max I_c	Power Rating	
		No heat sink $T_A = 25^\circ\text{C}$	With Heat sink $T_c = 25^\circ\text{C}$

2N3904	200 mA X	625 mW	
2N4401	600 mA ✓	625 mW X	1.5W X
TIP31	3 A ✓	2 W X	40W ✓


2N3904



2N4401

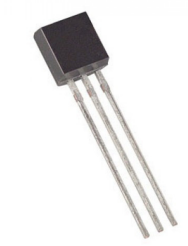

TIP31

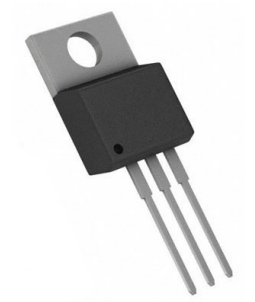


Design example

12-15V

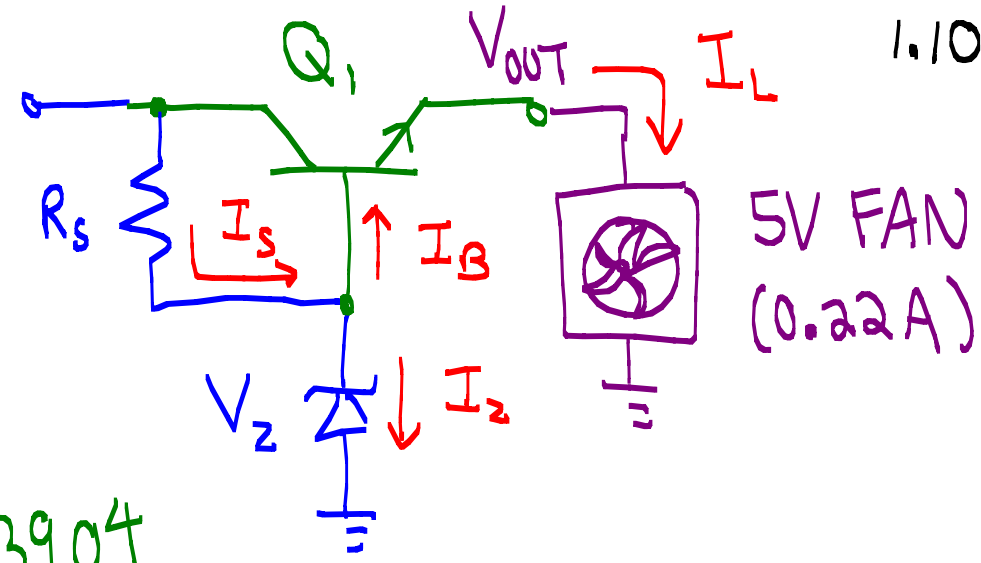1.10

$V_{out} = 5V = V_z - V_{BE} \sim V_z - 0.7$

$\Rightarrow V_z = 5.7V \Rightarrow$ Try 5.6V ZENER IN4734A



Q_1 ? We know $I_E = 0.22A \leftarrow$ Rules out 2N3904

Estimate max P $= I_B V_{BE} + I_C V_{CE} = \frac{.22A}{101} (0.7V) + \frac{100}{101} (.22A)(15-5) = \underline{\underline{2.18W}}$

R_s ? Zener needs $\min I_z > 10mA$

$\min I_s - \max I_B > 10mA$

$\frac{12-5.6}{R_s} - \frac{.22A}{\beta+1} > .010A$

\nwarrow From TIP31 data sheet

$\times 2$
safety factor

Need $> 4.36W$ rating

Choose
TIP31 +
Heat sink

• If designing for "typical" Q, properties:

$\beta \approx \underline{120}$ (see Appendix #1) $\rightarrow R_s < 541.5 \Omega$ $\xrightarrow{5\% \text{ tolerance } \downarrow \times 0.95}$ $514.5 \Omega \Rightarrow$ Choose 510Ω

Power rating? $\text{Max } P = \frac{(15 - 5.6)^2}{510 \Omega} = .173 \text{ W} \xrightarrow{\times 2}$ $.347 \text{ W}$ ($\frac{1}{2} \text{ W}$ rating ✓)

Zener? $\text{Max power} \approx \left(\frac{15 - 5.6}{510 \Omega} \right) (5.6 \text{ V}) = .103 \text{ W} \xrightarrow{\times 2}$ $\underline{.206 \text{ W}}$ ($\frac{1}{4} \text{ W}$ rating or higher)

• If designing for "worst case" Q, properties:

$\beta = \underline{46}$ (Appendix #1) $\rightarrow R_s < 436 \Omega \xrightarrow{\times 0.95}$ 414Ω } Choose 390Ω (430Ω probably OK)

$P = \frac{(15 - 5.6)^2}{390} = .23 \text{ W} \xrightarrow{\times 2}$ $.46 \text{ W}$ ($\frac{1}{2} \text{ W}$ rating)

Zener? $\text{Max power} \approx \left(\frac{15 - 5.6}{390} \right) (5.6 \text{ V}) = .135 \text{ W} \xrightarrow{\times 2}$ $.27 \text{ W}$ ($\frac{1}{4} \text{ W}$ rating or higher)

Appendix #1

In reality, β depends on I_c !

To obtain "typical" value, use graph of β vs I_c in datasheet (A1.1)

TIP 31

$\sim 220 \text{ mA}$
↓

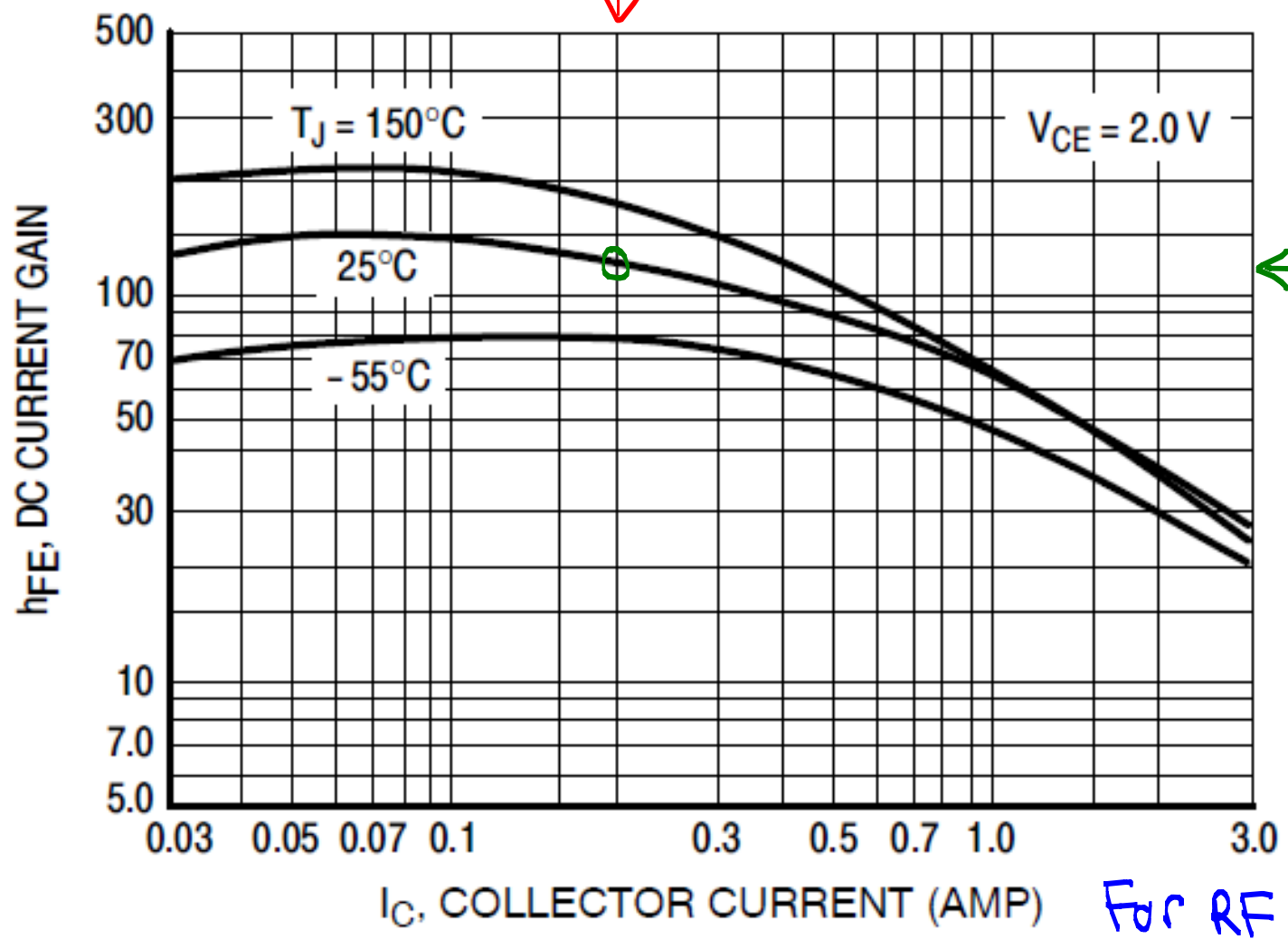


Figure 9. DC Current Gain

STEP 1 Estimate I_c using "quick" analysis or known load parameters
→ $I_c \sim 0.22 \text{ A}$

STEP 2 use plot to find β (same as h_{FE})
 $h_{FE} \sim \underline{\underline{120}}$

Not the same as h_{fe}

called "DC" or "pulsed" current gain.

For RF applications

- Any device parameter has "typical" and "worst case" values!
 use the table of "On Characteristics" ←

TIP 31

only for $I_c = 1A!$

ON CHARACTERISTICS (Note 2)

		min	max
DC Current Gain ($I_C = 1.0 \text{ Adc}, V_{CE} = 4.0 \text{ Vdc}$) ($I_C = 3.0 \text{ Adc}, V_{CE} = 4.0 \text{ Vdc}$)	h_{FE}	25 10	- 50
Collector-Emitter Saturation Voltage ($I_C = 3.0 \text{ Adc}, I_B = 375 \text{ mAdc}$)	$V_{CE(sat)}$	-	1.2 Vdc
Base-Emitter On Voltage ($I_C = 3.0 \text{ Adc}, V_{CE} = 4.0 \text{ Vdc}$)	$V_{BE(on)}$	-	1.8 Vdc

- Table only has β_{min} for $I_c = 1A$.
 → but we need $I_c \sim 220 \text{ mA}$.

@ $1A, 25^\circ C$ @ $.22A$

★ OK to assume $\frac{\beta_{min}}{\beta_{typ}} \approx \text{constant}$:


$$\frac{25}{65} \approx \frac{\beta_{min}}{120}$$

From graph

$$\Rightarrow \beta_{min} = \underline{\underline{46}} @ .22A$$

Appendix #2


npn

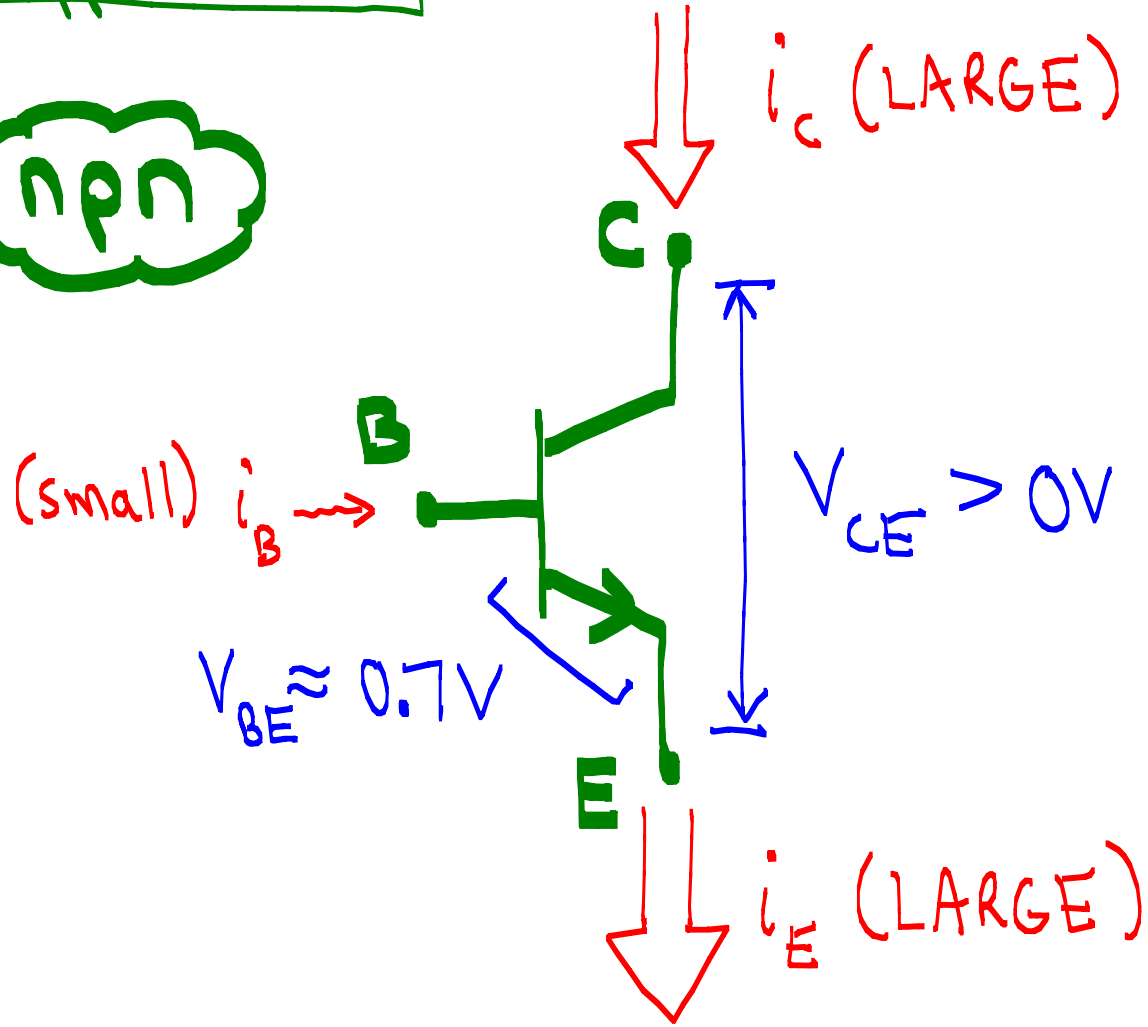


Always true!

$$i_B + i_C = i_E$$

★ For both npn + pnp

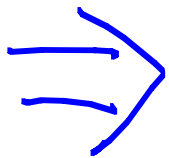

pnp

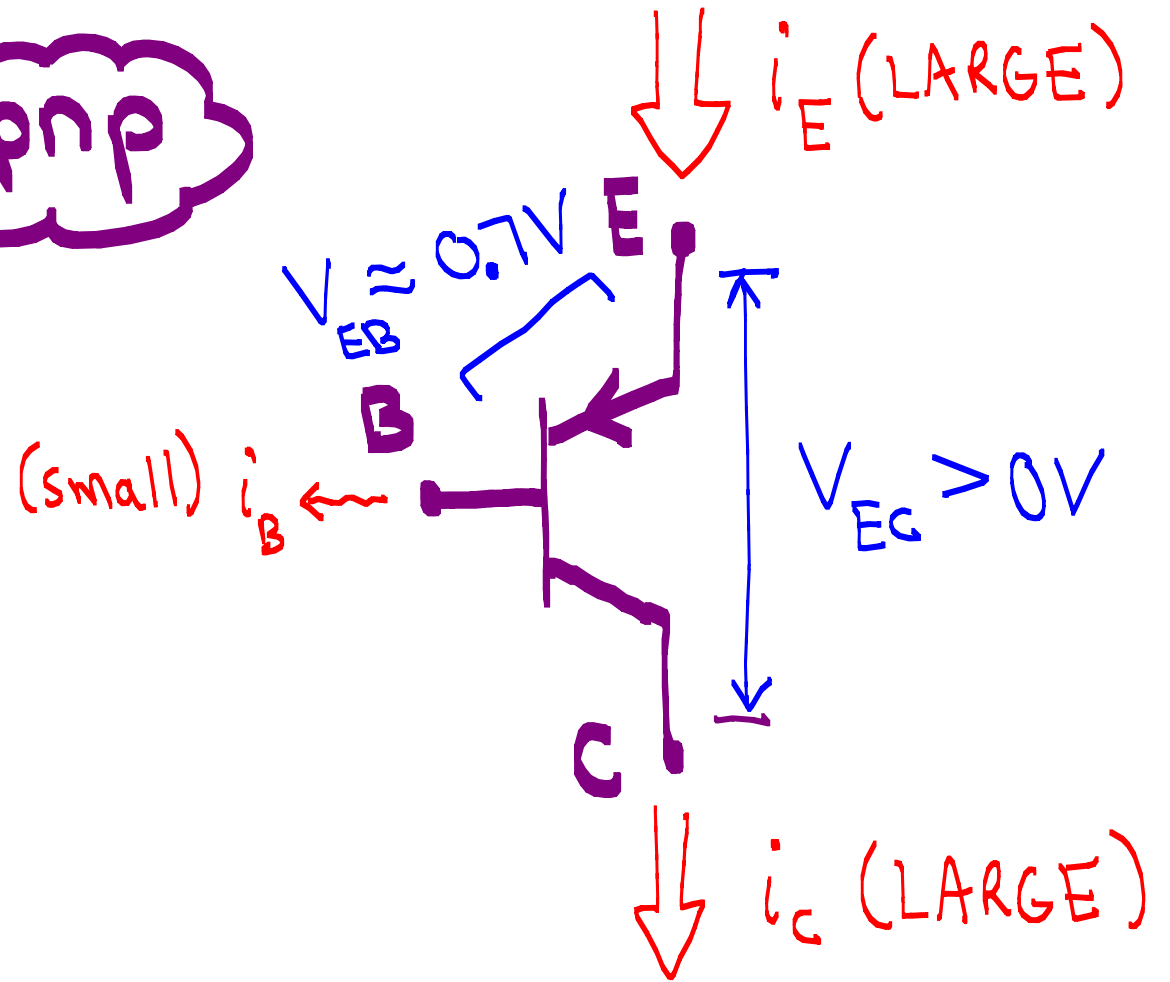


Only true for Active Mode




$$i_C = \beta i_B = \alpha i_E \text{ AND } i_E = (\beta + 1) i_B$$

• T-model ← useful for understanding amplifier gain and input/output impedance

npn

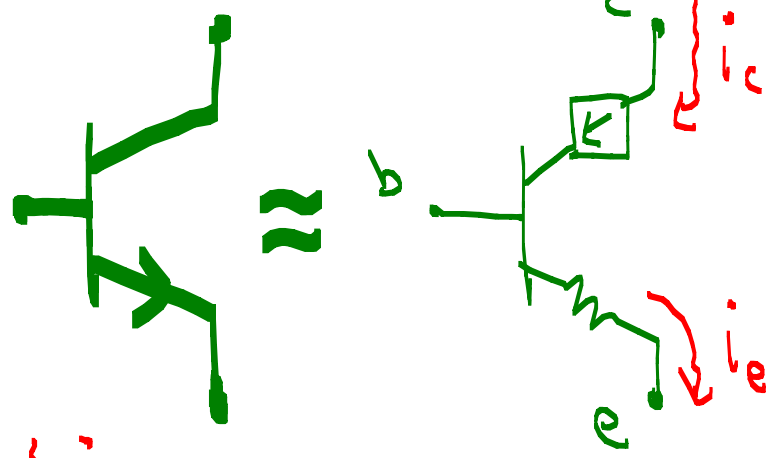

pnp

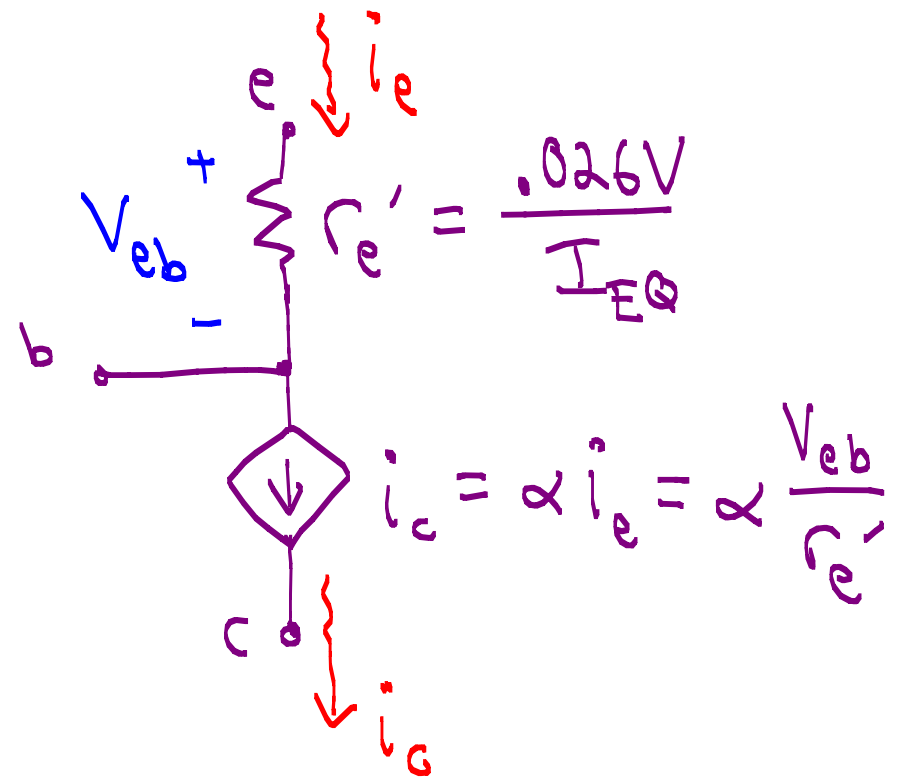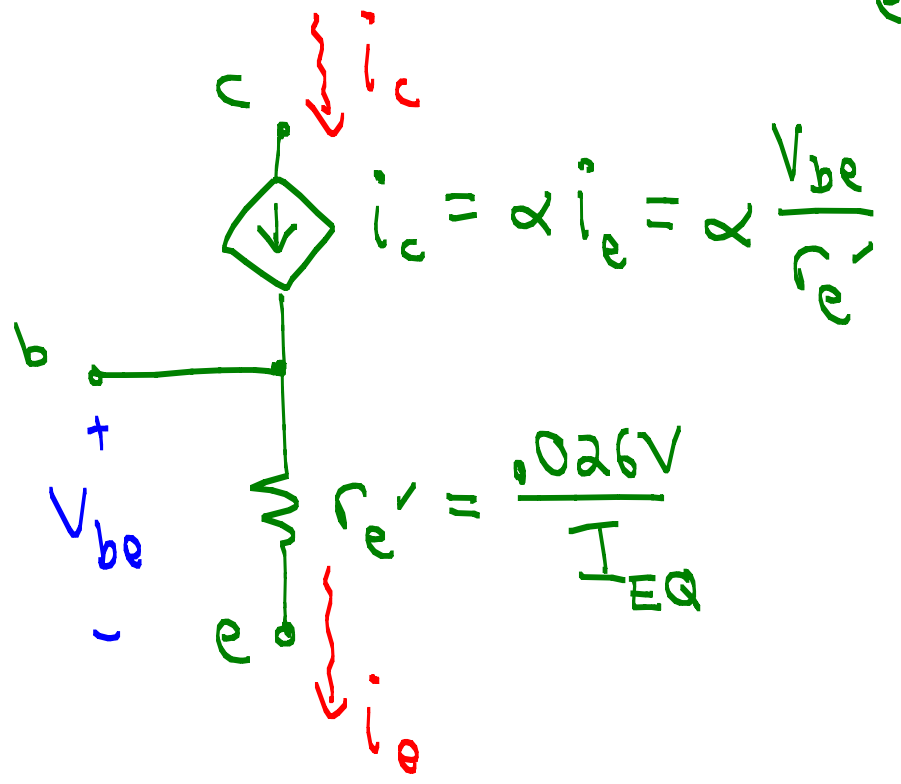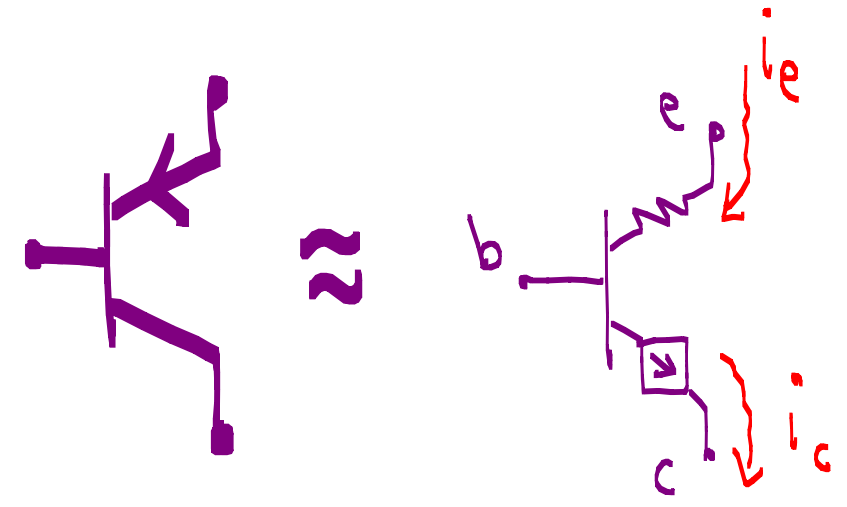

Appendix #3


A3.1

$\beta \approx 2500$

- Extra high current gain is possible with a Darlington!

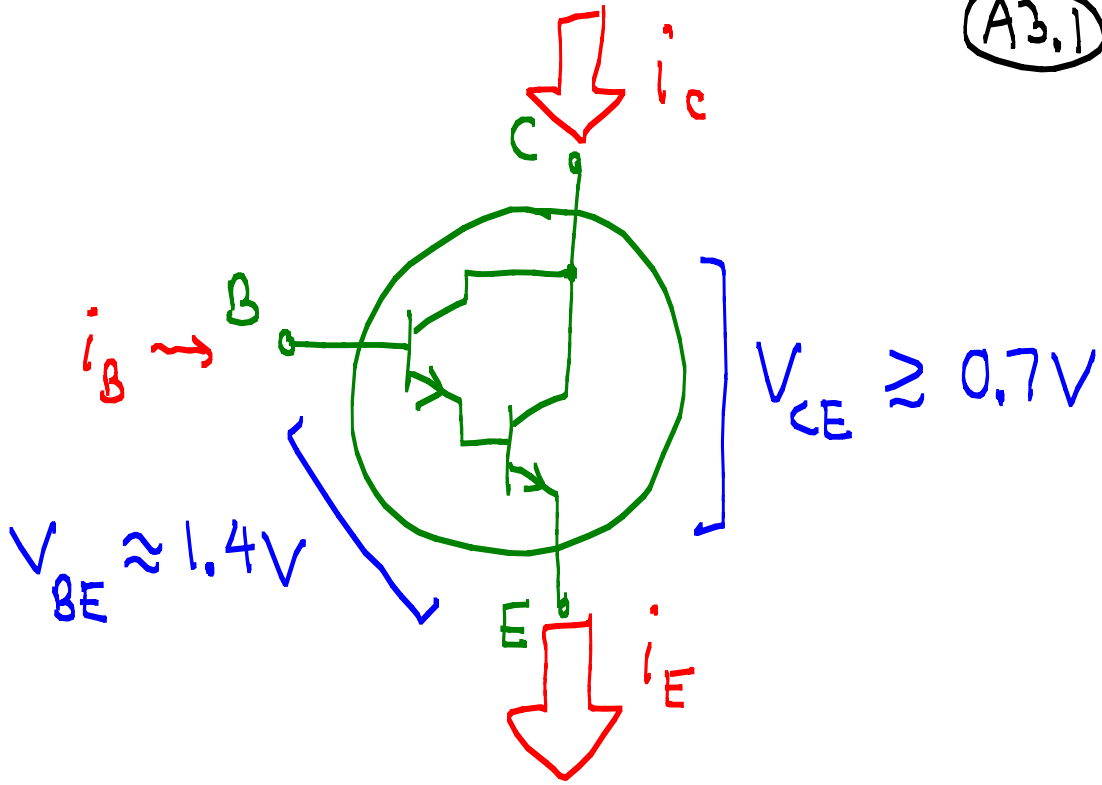
(a) Darlington Transistor

→ single device containing both transistors (e.g. KSP14, TIP120)



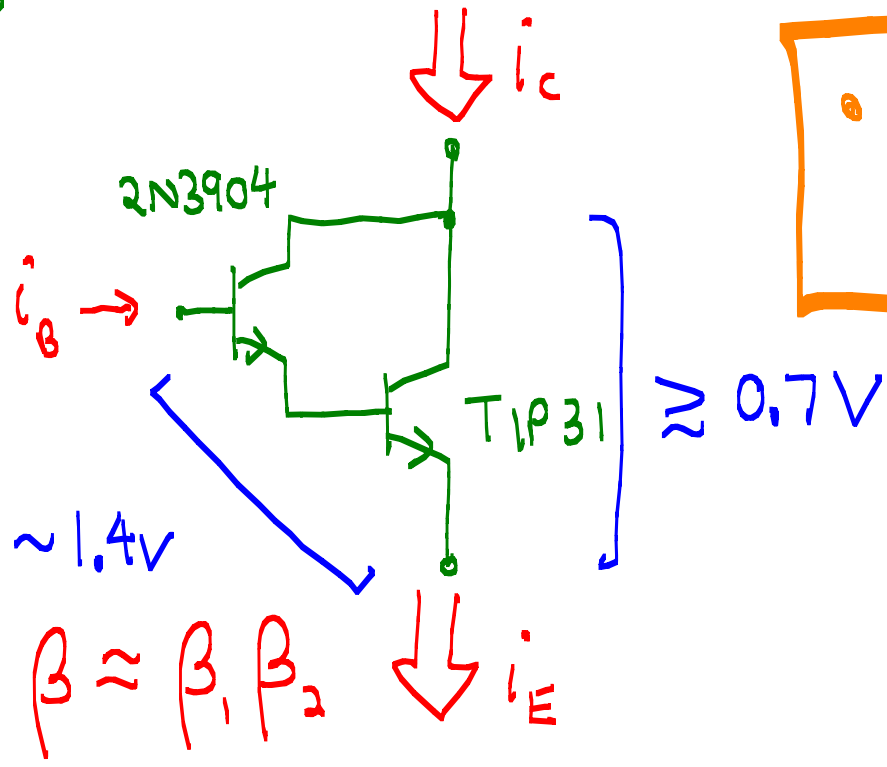(b) Darlington Pair

→ two separate transistors connected to each other (e.g. 2N3904 + TIP31)




• For Darlington "quick" analysis,
 $V_{BE} = 1.4V$
 $\beta = 2500$
 $V_{CE(sat)} = 0.7V$

pnP Darlington

Method 1

Two pnp's

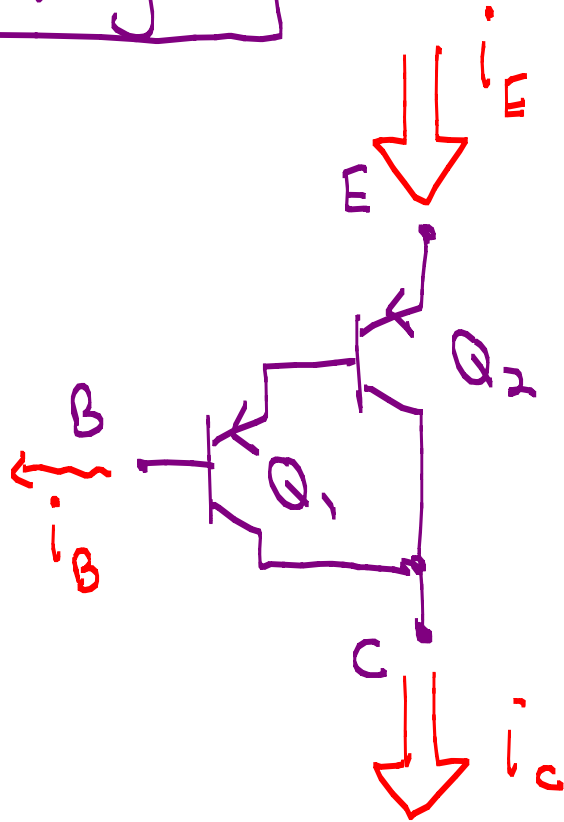


Method 2

$Q_1 = \text{pnp}$

$Q_2 = \text{nnp}$


nnp can handle
higher currents
than pnp

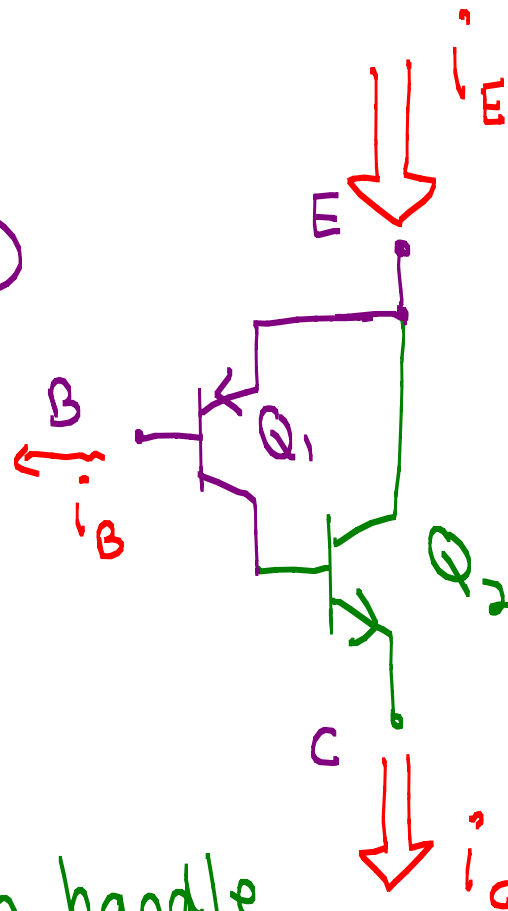

Called
"Complementary"
or
"Sziklai"
Pair

Appendix #4 Heat sink formulas

• NO heat sink

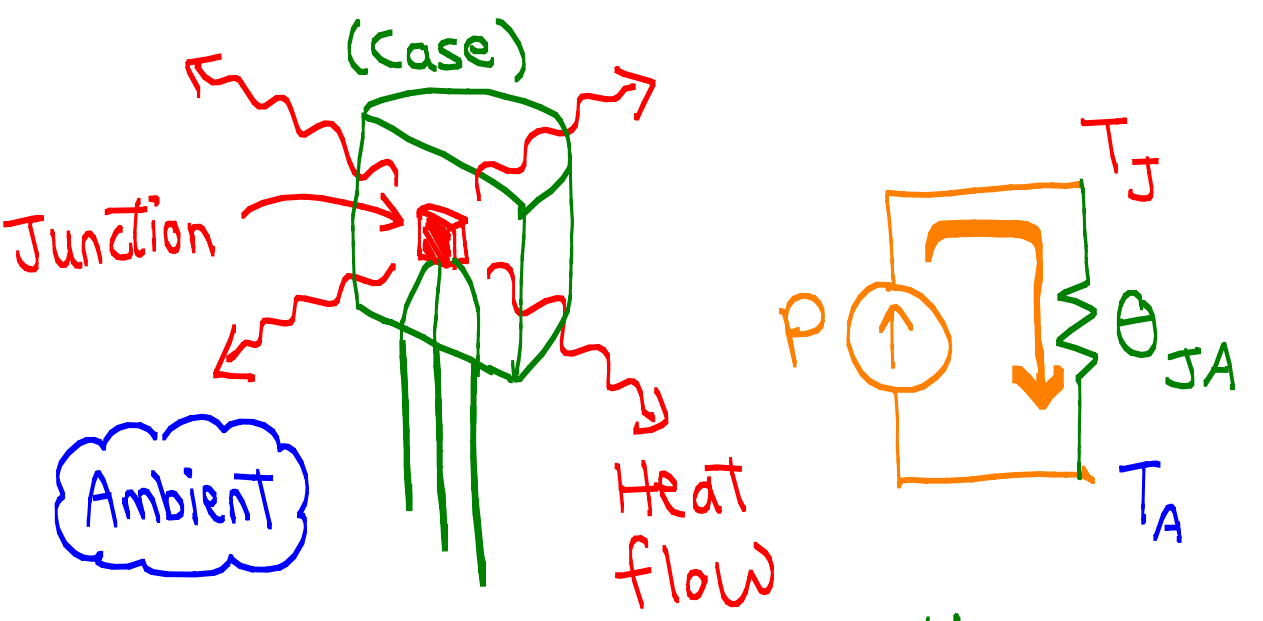


$$T_J = T_A + P \times \Theta_{JA}$$

← Junction to Ambient

$$= T_A + P \times [\Theta_{JC} + \Theta_{CA}]$$

↑ Junction to case ↑ Case to Ambient

• WITH heat sink

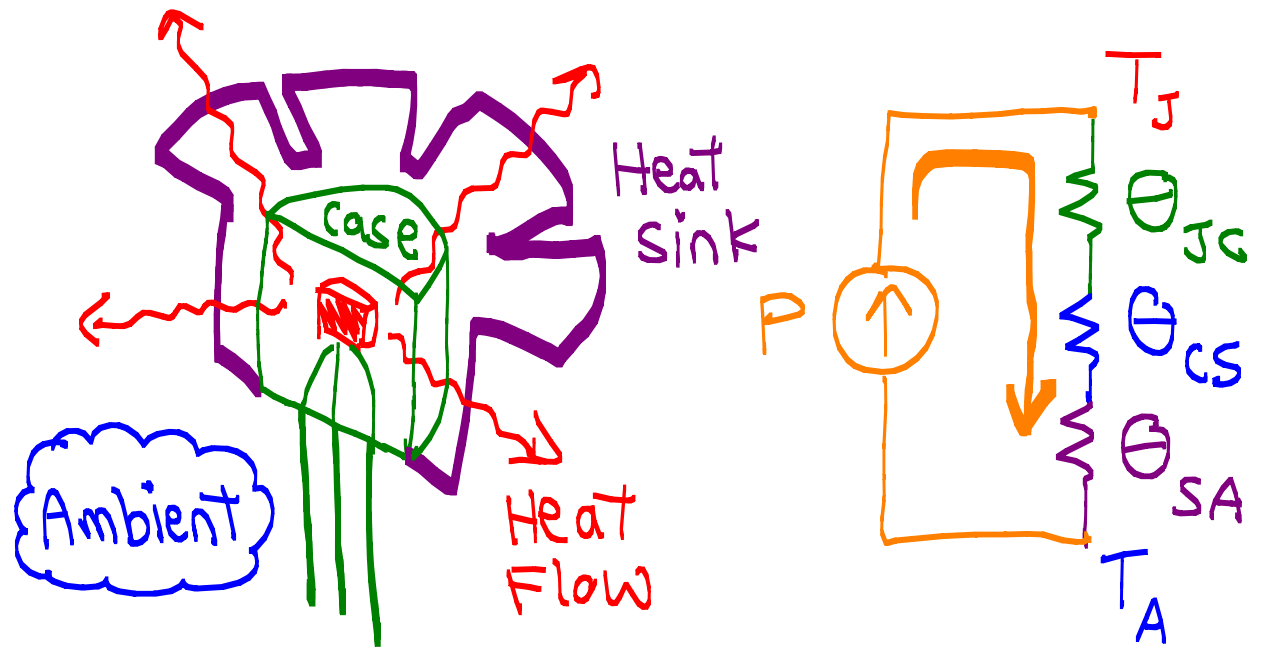

$$T_J = T_A + P \times [\Theta_{JC} + \Theta_{CS} + \Theta_{SA}]$$

↑ Junction to case ↑ Case to sink ↑ sink to Ambient

"new" Θ_{JA}