

Lecture 2: Linear Regulator

0. Review

1. Op amp feedback

2. Design example

3. Current limiting

• PreLab1 due Thu (Sep 19)
at lab session

• HW1 due Fri (Sep 20)
→ leave in box outside
my office

• Quiz1 next Tue (Sep 24)

Helpful textbook reading:



Ch 22-1 Power Supply Characteristics

22-3 Series regulators



22-4 Monolithic Linear regulators

0. Review



Diode

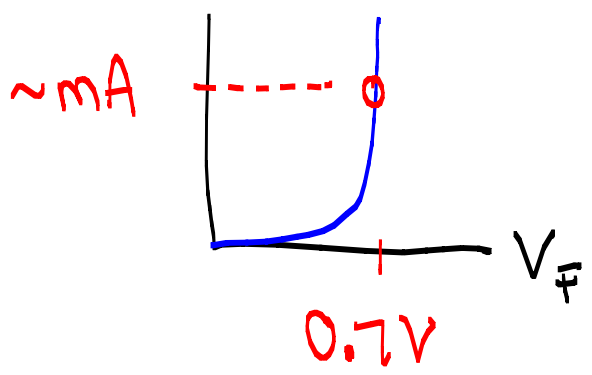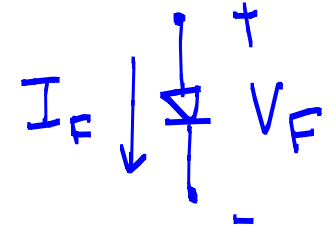

Zener

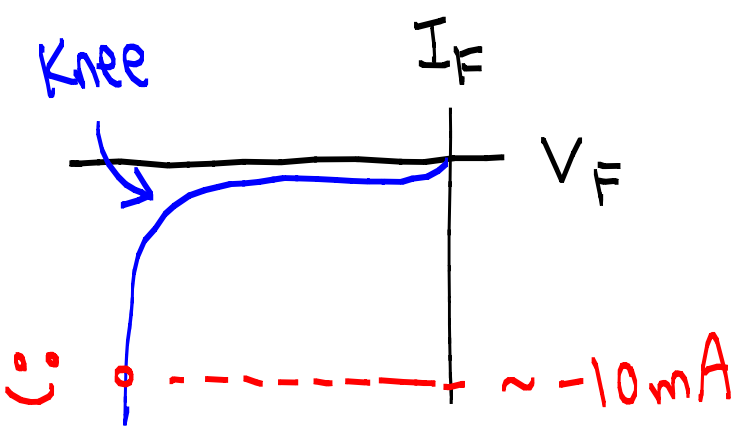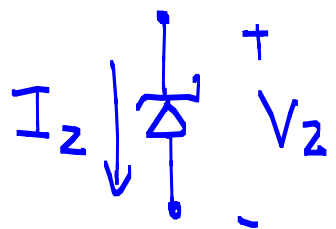


Zener Follower

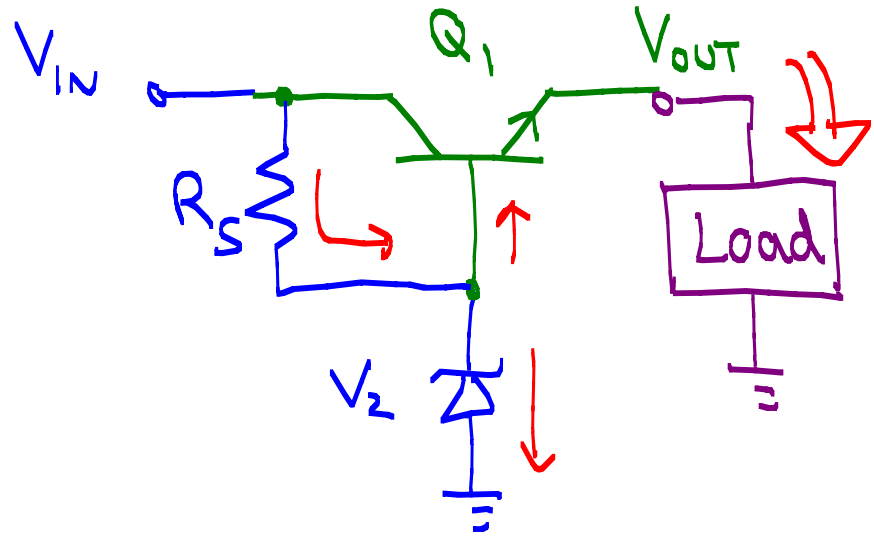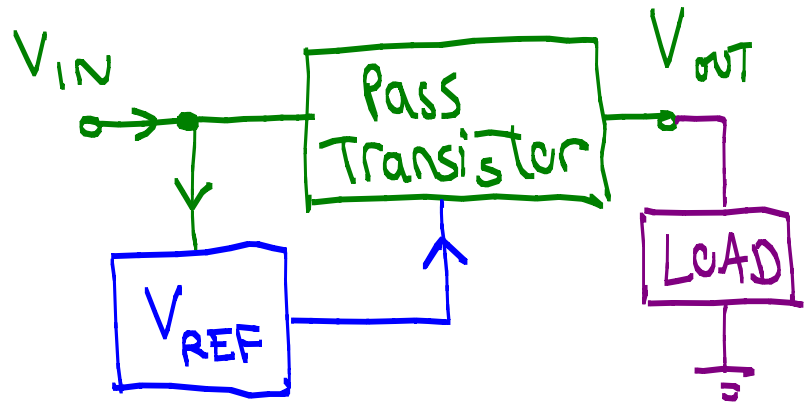

$$V_{OUT} = V_Z - V_{BE}$$

Heat sinks

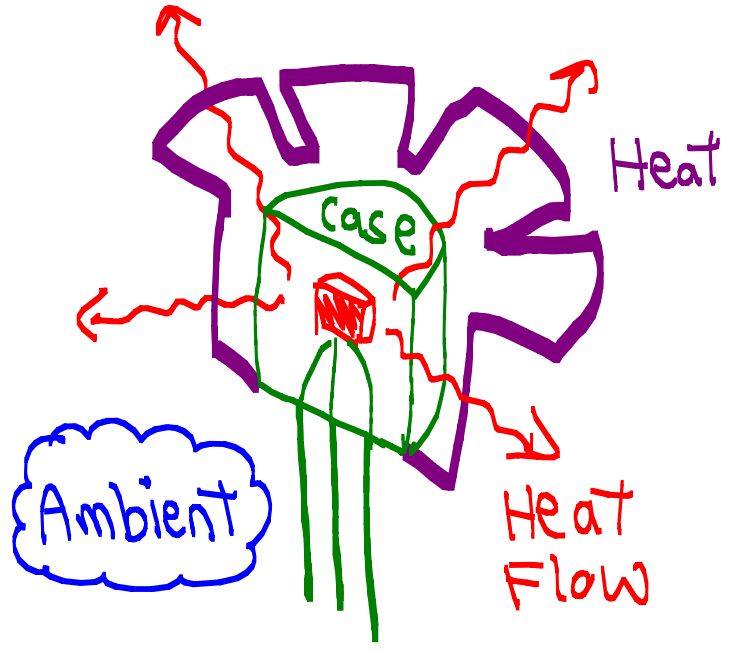

Θ_{JA} w/ heat sink

$$T_J = T_A + P \times [\Theta_{JC} + \Theta_{CS} + \Theta_{SA}]$$


↑ Junction to case
↑ Case to sink
↑ sink to Ambient

1. Negative Feedback


• Zener follower problems:

① Limited selection of zener values (eg. 5.6V, 8.2V)

② V_{BE} varies with current

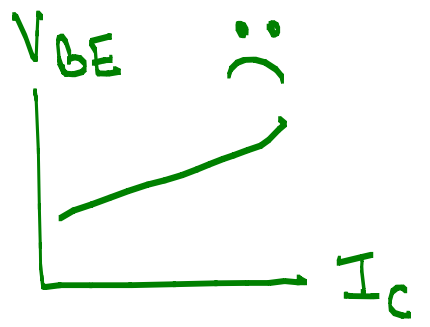


③ V_{BE} varies with temp! ☹️

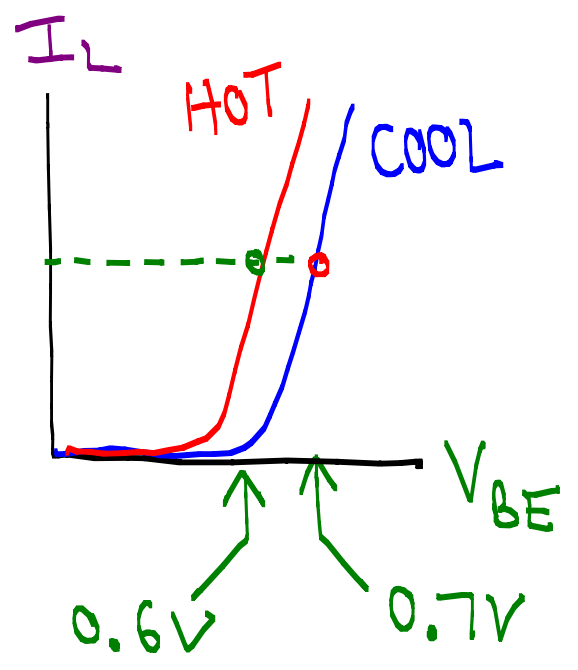

$$\frac{\Delta V_{BE}}{\Delta T} = -2 \frac{mV}{^{\circ}C}$$

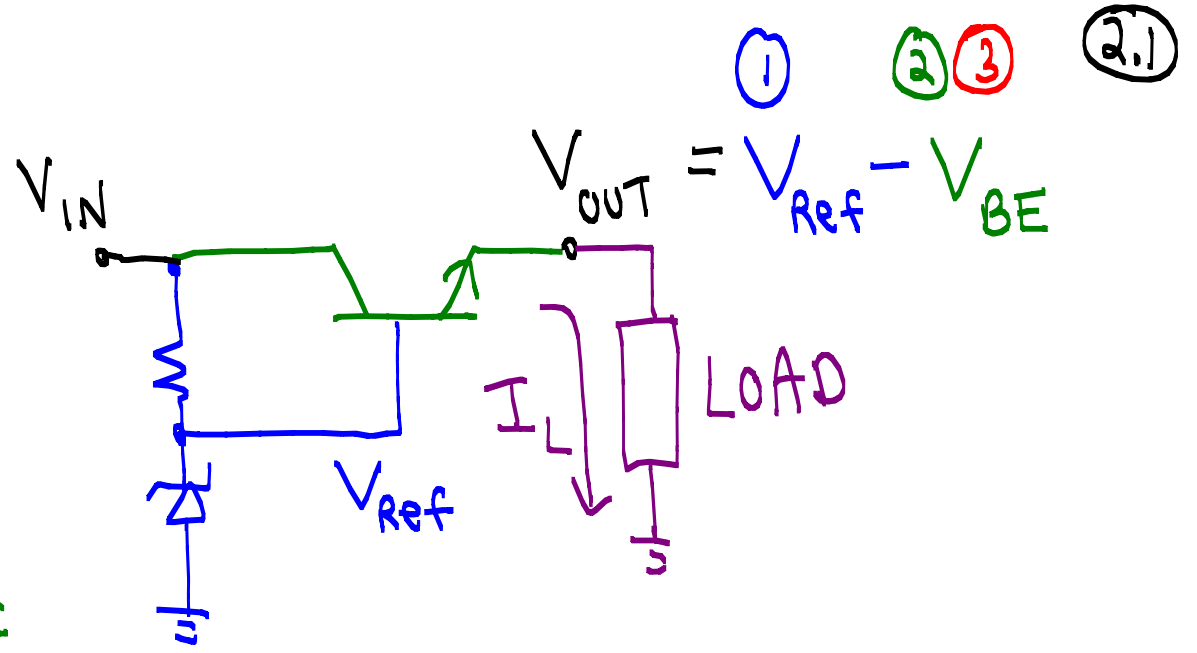EX: $V_{BE} = \begin{cases} 0.7V @ 25^{\circ}C \\ 0.6V @ 75^{\circ}C \end{cases}$



• A voltage regulator actively stabilizes V_{out} using negative feedback!

- (a) Sample a portion of V_{out}
- (b) Create error signal
- (c) Adjust V_{out}

Q: How to do this?

★ Use an op amp with negative feedback!


→ An op amp makes $V_- = V_+$

$$V_{OUT} = \frac{R_1}{R_1 + R_2} V_2$$


SO, $V_{OUT} = V_2 * (1 + \frac{R_2}{R_1})$

→ Can achieve any V_{OUT} by choosing R_2/R_1

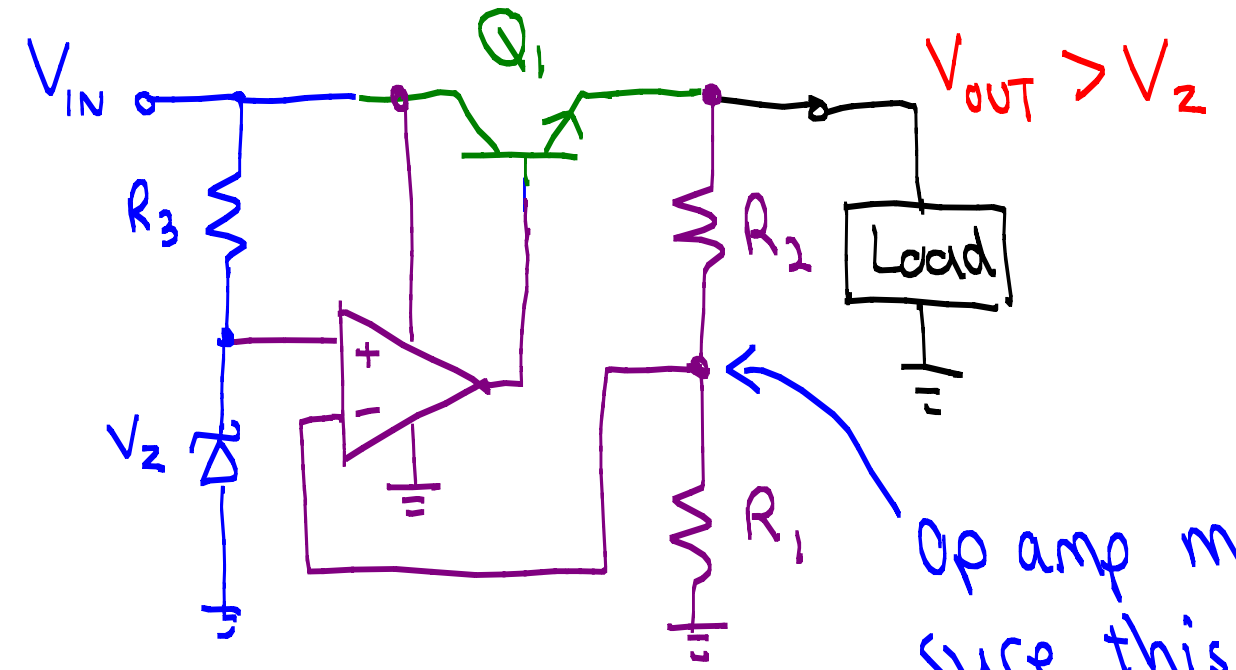→ V_{OUT} does NOT depend on V_{BE} , so Q_1 variation don't matter! 😊



Op amp makes sure this is equal to V_2 !

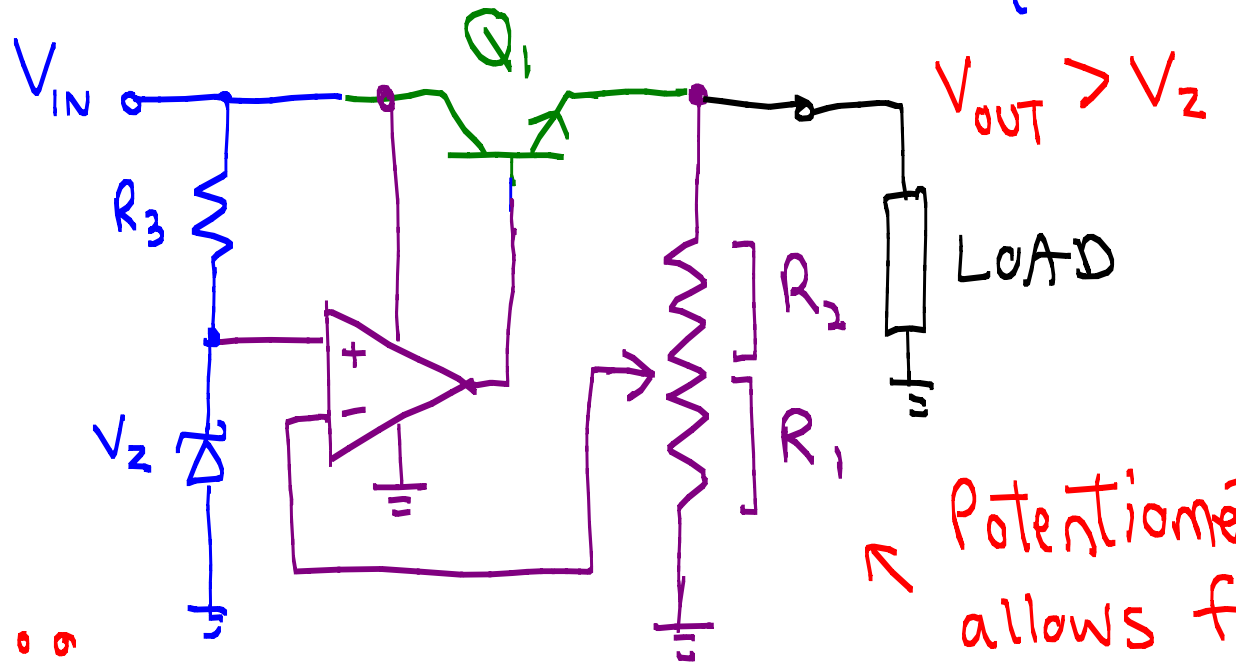

Potentiometer allows fine adjustment

Op Amp Review

Ideal op amp with (-) feedback obeys two Golden Rules:

① The two input terminals are at the same voltage.

$$V_- = V_+$$

② The two input terminals draw no current.

"Virtual Short"

Golden Rule #2

KCL at node V_- : $i_2 = i_1$


$$\frac{V_{out} - V_-}{R_2} = \frac{V_- - 0}{R_1} \Rightarrow V_{out} = \left(1 + \frac{R_2}{R_1}\right) V_-$$

$$\Rightarrow \boxed{\frac{V_{out}}{V_{in}} = 1 + \frac{R_2}{R_1}}$$

NOTE: $R_2 = 0$
 $R_1 = \infty$ } $V_{out} = V_{in}$!
 (buffer)

Ex. 2


Non-inverting Amplifier

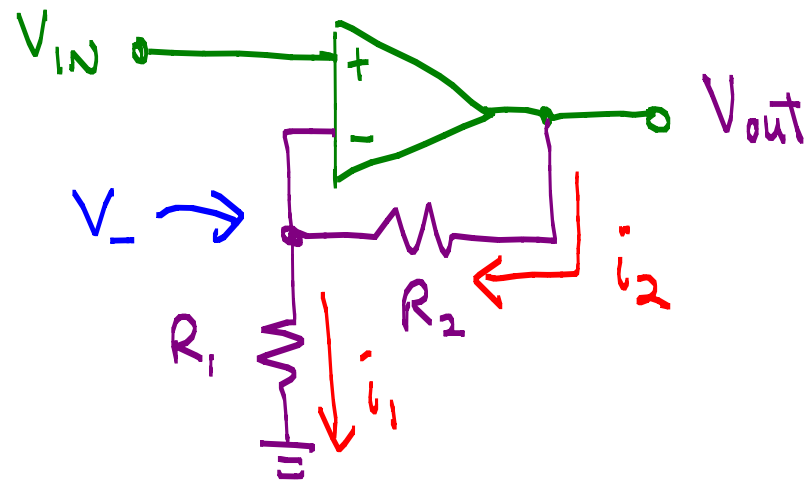

Golden Rule #1

V_{in}

Ex. 1 Voltage Buffer

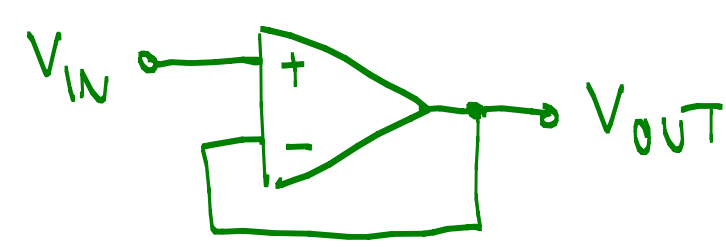


$$V_- = V_+$$

$$\boxed{V_{out} = V_{in}}$$

Q: How does the op amp do this?

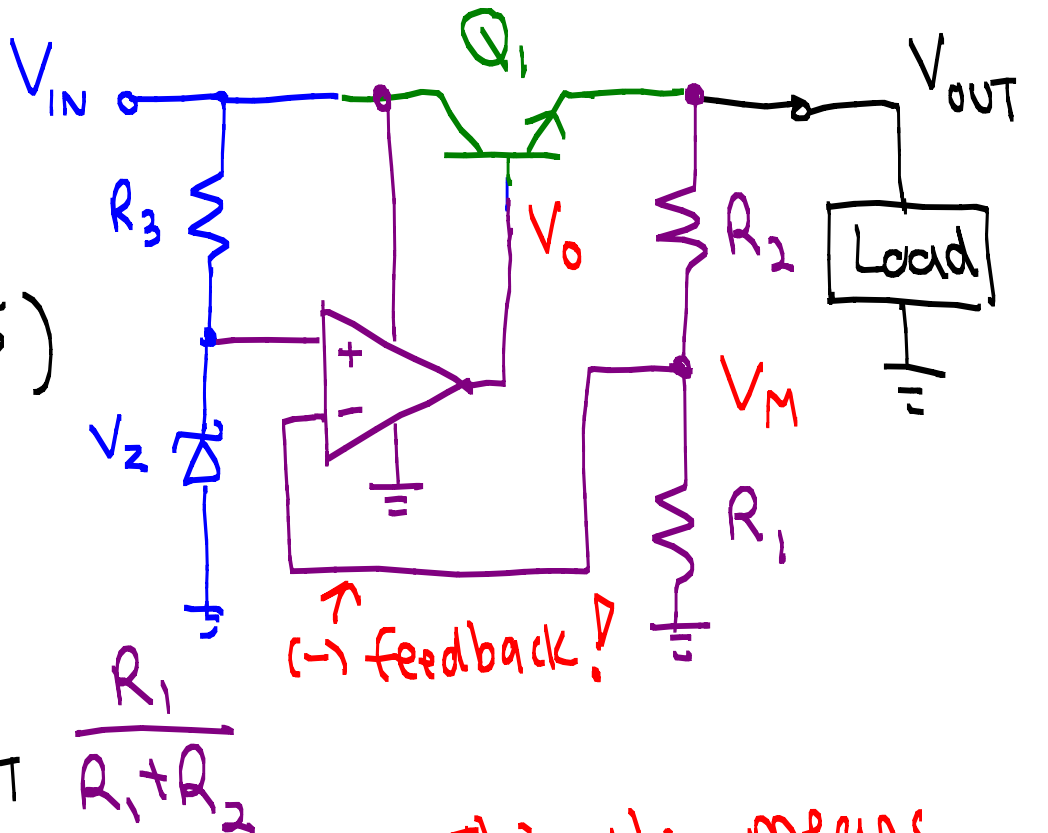An op amp is basically a differential amplifier with super high gain ($\sim 10^5$)



$$V_O = A \times (V_+ - V_-) = A \times (V_2 - V_M)$$

$\underbrace{\hspace{10em}}_{V_{OUT} + V_{BE}}$

SO, $V_{OUT} + V_{BE} = A V_2 - A \frac{R_1}{R_1 + R_2} V_{OUT}$

$$\Rightarrow V_{OUT} = \frac{A V_2 - V_{BE}}{1 + A \frac{R_1}{R_1 + R_2}} \approx \frac{A V_2}{A \frac{R_1}{R_1 + R_2}} = V_2 \left(1 + \frac{R_2}{R_1} \right)$$


When A is HUGE

This also means $V_M = V_{OUT} \frac{R_1}{R_1 + R_2} = V_2$ ✓





- Negative feedback greatly improves V_{out} regulation. ☺
- Need to be careful with large I_{out}
 - ↳ Pass transistor has large I_B
 - ⇒ Most op amps are limited to $\sim 25\text{mA}$ output current! ☹

EX:

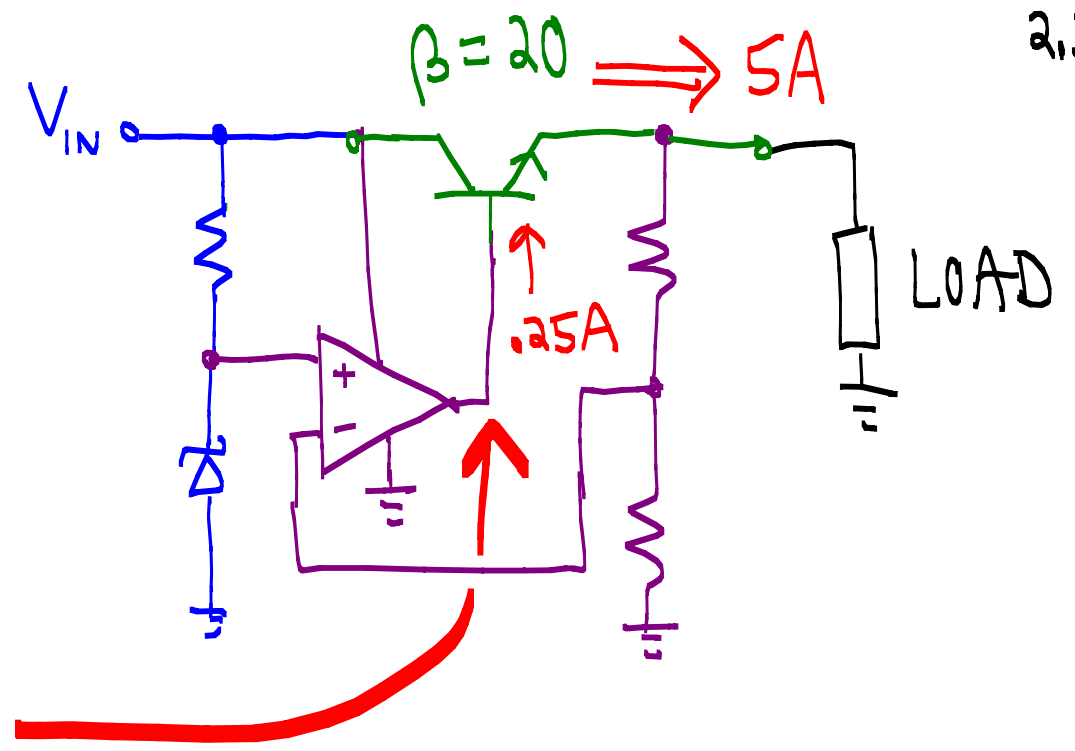

A: use a Darlington connection!

EX:

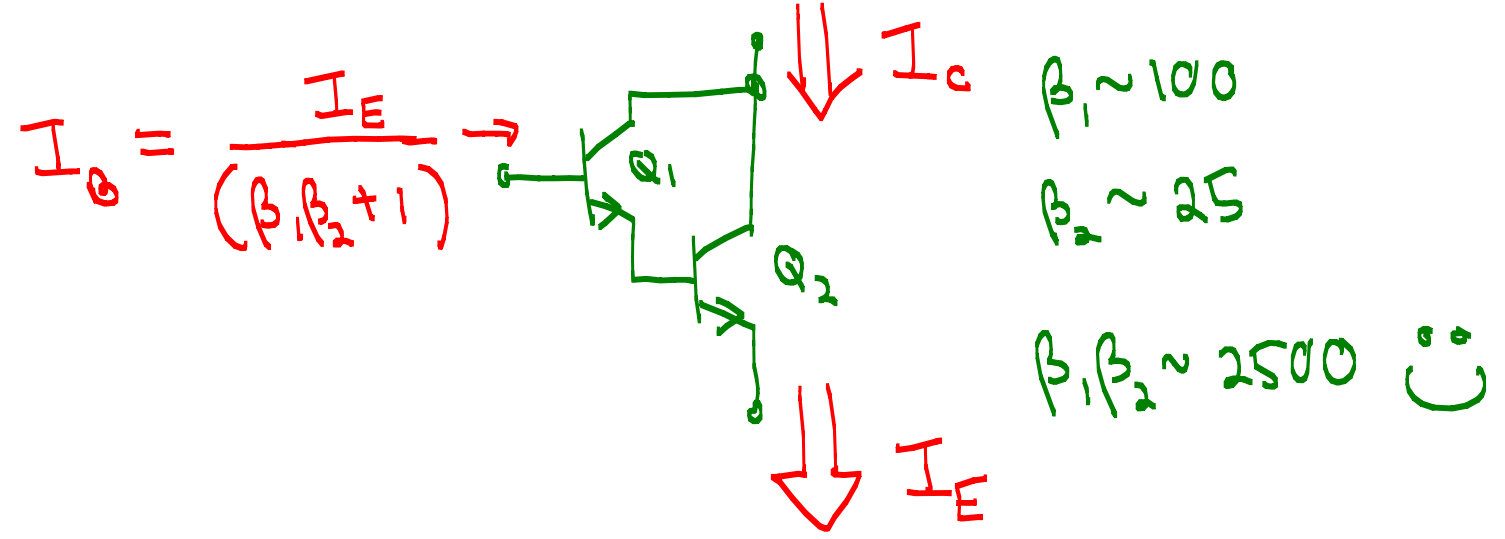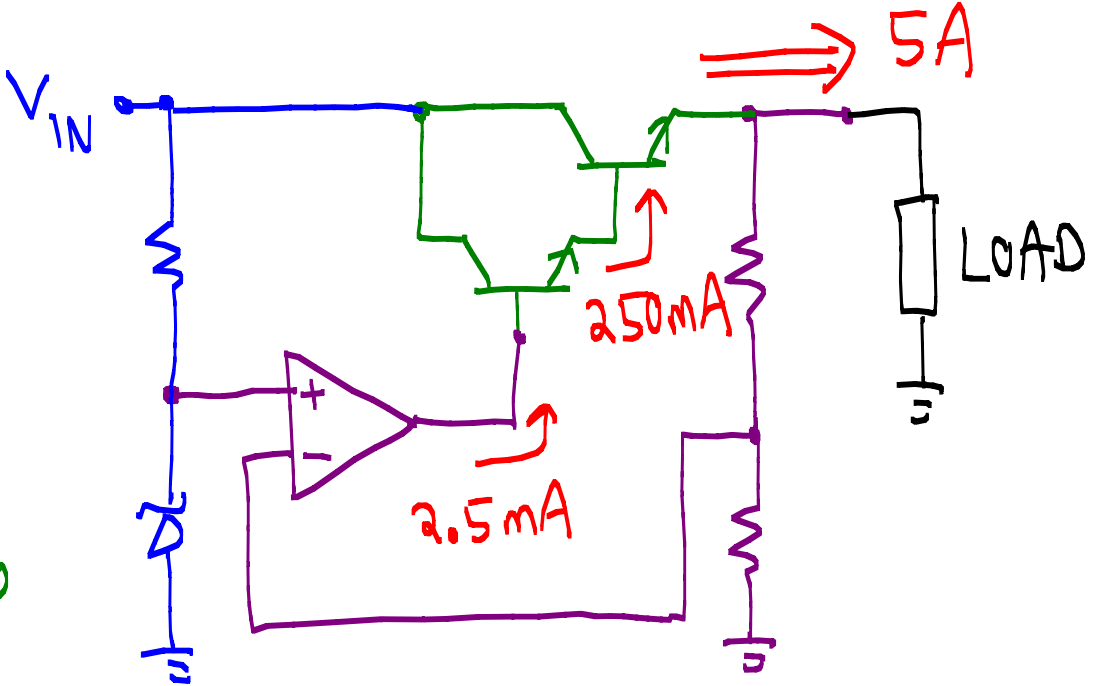


$$I_B = \frac{I_E}{(\beta_1 \beta_2 + 1)}$$

$\beta_1 \sim 100$
 $\beta_2 \sim 25$
 $\beta_1 \beta_2 \sim 2500$ ☺

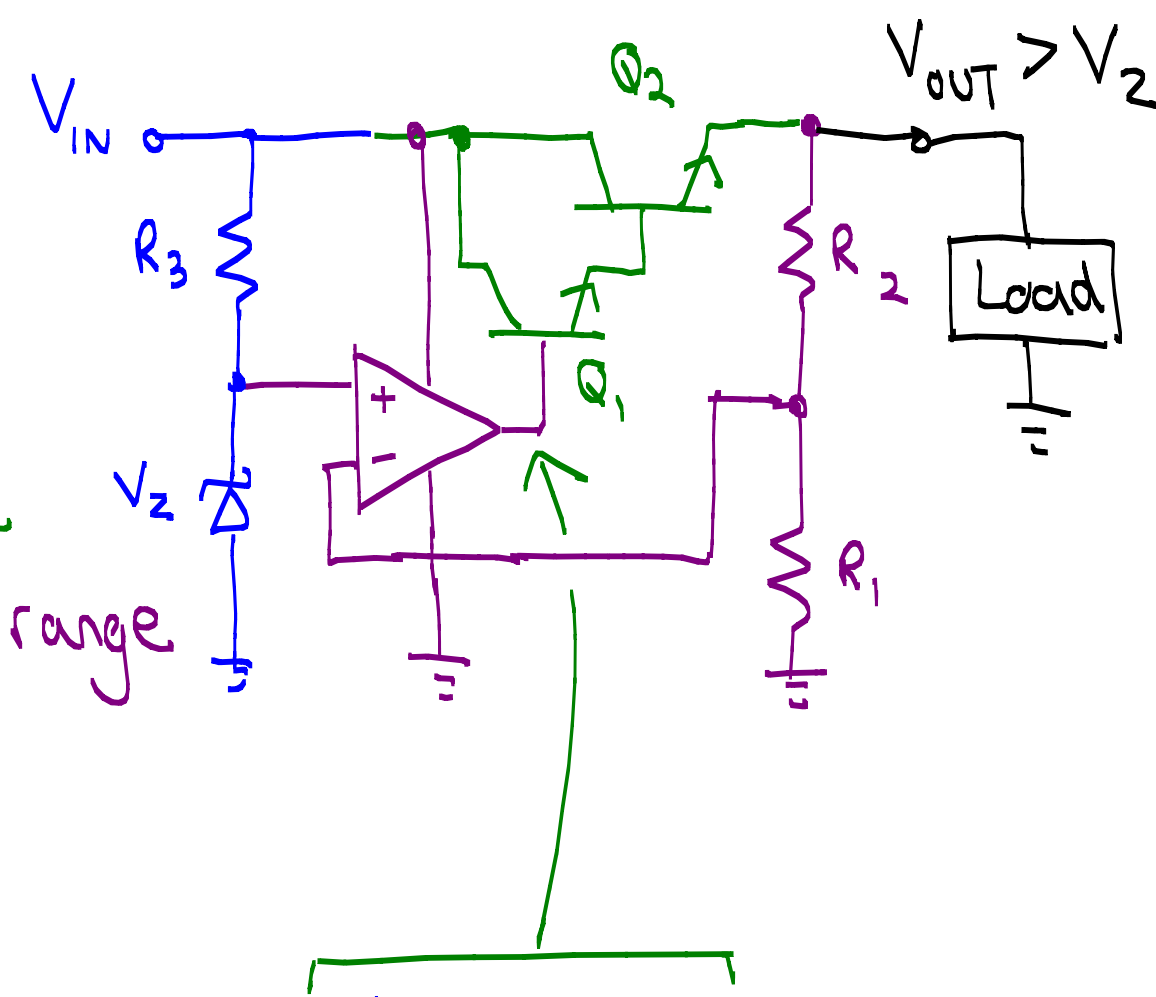3. Design Guidelines for Linear Regulator

- Minimum I_Z is 10 mA
→ Ensure zener is happy
- Max Q_1 base current < 5 mA
→ Does not significantly reduce max op amp output voltage
- R_1 and R_2 are typically $k\Omega$ or $10k\Omega$ range
★ Draw ≤ 1 mA from V_{OUT}
- Make sure minimum $V_{IN} > V_{OUT} + 3V$
→ Ensures op amp output can reach $\approx V_{OUT} + 1.4V$
- Don't fry your components.
→ Choose power ratings $> 2x$ actual power dissipation



Example: $V_{in} = 19-22V$, $V_{out} = 15V$, $R_L > 20\Omega$

① choose $V_z = 6.2V$ ← Zeners in ~6V range have small temp drift

$10\text{ mA} < \frac{19-6.2}{R_3} \Rightarrow R_3 < 1.28\text{ k} \xrightarrow{\times 0.95} 1.22\text{ k} \Rightarrow \text{choose } R_3 = 1.2\text{ k}$

② $I_{L,max} = \frac{15V}{20\Omega} = 0.75A$

Need to choose Q_2 and Q_1 ! Q_2 :

		Max P	
		Max I_c ($T_A=25^\circ C$)	($T_c=25^\circ C$)

2N3904	200 mA	x	.625W	
2N4401	600 mA	x	.625W	1.5W
TIP31	3 A	✓	2W	x
2N3055	15 A			40W ✓
				115W

"Quick" analysis: $\beta = 100$

"Typical" : $\beta \sim 70 @ .75A$

$\rightarrow \text{Max } P = I_B V_{BE} + I_C V_{CE}$

$= \left(\frac{.75A}{71}\right)(.8V) + \frac{70}{71} (.75A)(22-15) = 5.18W \xrightarrow{\times 2} 10.4W$

Typ V_{BE}

Determine heat sink later \rightarrow TIP31 ✓

Q1: $I_{E1} = \frac{I_{E2}}{\beta + 1} = \frac{.75A}{71} = 10.6 \text{ mA} \leftarrow \underline{\underline{2N3904}}$ seems OK

$\beta_{Typ} \sim 225 \rightarrow P = \frac{10.6 \text{ mA}}{226} (0.72) + \frac{225}{226} (10.6 \text{ mA})(22 - 15.7 \text{ V})$
 $= 66.5 \text{ mW} \checkmark$
 (don't need heat sink)

$I_{B1} = \frac{10.6 \text{ mA}}{226} = .047 \text{ mA} \checkmark$

③ $V_{out} = 15 = 6.2 \left(1 + \frac{R_2}{R_1}\right) \rightarrow \frac{R_2}{R_1} = 1.42$

$I_{divider} = \frac{15}{R_1 + R_2} < 1 \text{ mA} \rightarrow R_1 + R_2 > \underline{\underline{15 \text{ K}}}$

④ Minimum $V_{in} = 19 \text{ V} > (15 + 3) \checkmark$

⑤ Power ratings

R_1	$1.42 R_1$	Closest R_2	Actual R_2/R_1
9.1K	12.9K	13K	1.43
10K	14.2K	15K	1.5
11K	15.6K	16K	1.45
12K	17.0K	18K	1.5

$\frac{1}{4} \text{ W}$ is fine


$V_2: \text{Max } I_2 = \frac{22 - 6.8}{1.2 \text{ K}} = 12.7 \text{ mA} \rightarrow P = (12.7 \text{ mA})(6.2 \text{ V}) = 78.7 \text{ mW} \leftarrow$

R3: Max P = (22-6.8)^2 / 1.2K = 192.5mW -> Use 1/2W rating!

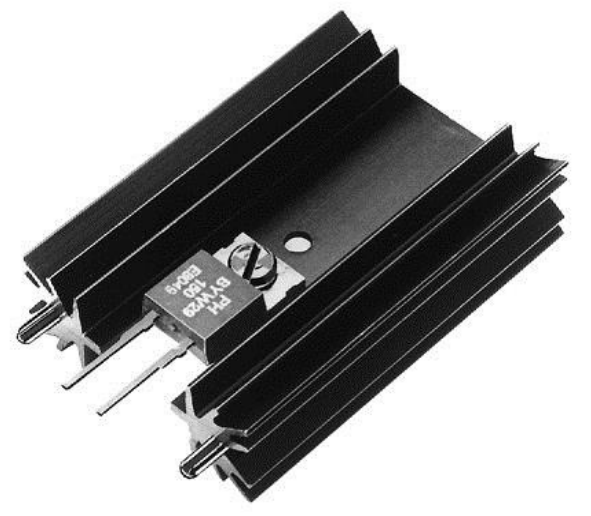Q2: TIP31 needs a heat sink! Let's assume: TA = 25C, Max TJ = 85C

TJ = TA + P * (theta_JC + theta_CS + theta_SA) < 85C

25C + 5.18W * (3.125C/W + .5C/W + theta_SA) < 85C



Actual power

Data sheet



Assume this

theta_SA < 7.96 C/W

R1 and R2: I = 15V / (9.1K + 13K) = .68mA -> (.68mA)^2 * (9.1K) = 4.2mW, (.68mA)^2 * (13K) = 6.0mW. 1/4w resistors are fine

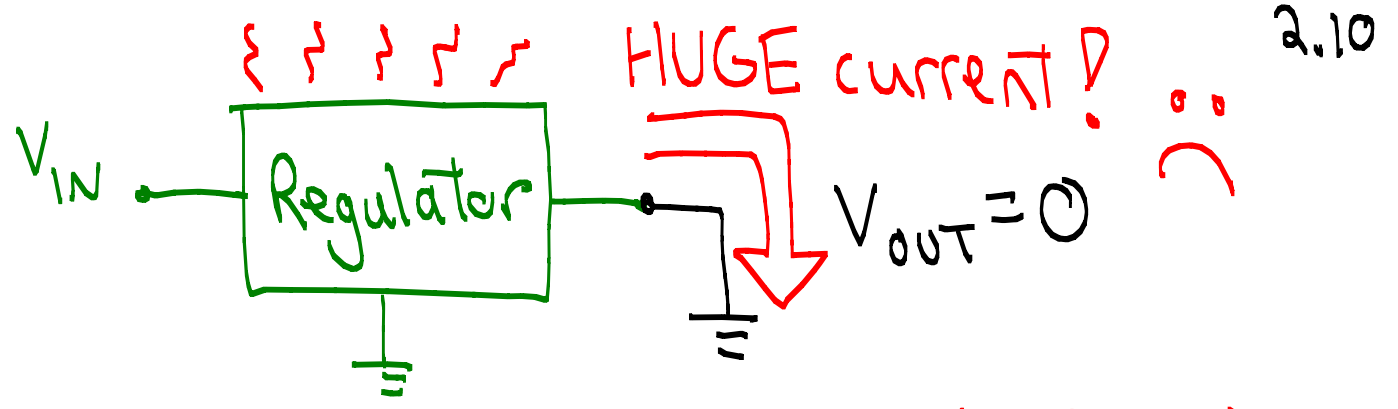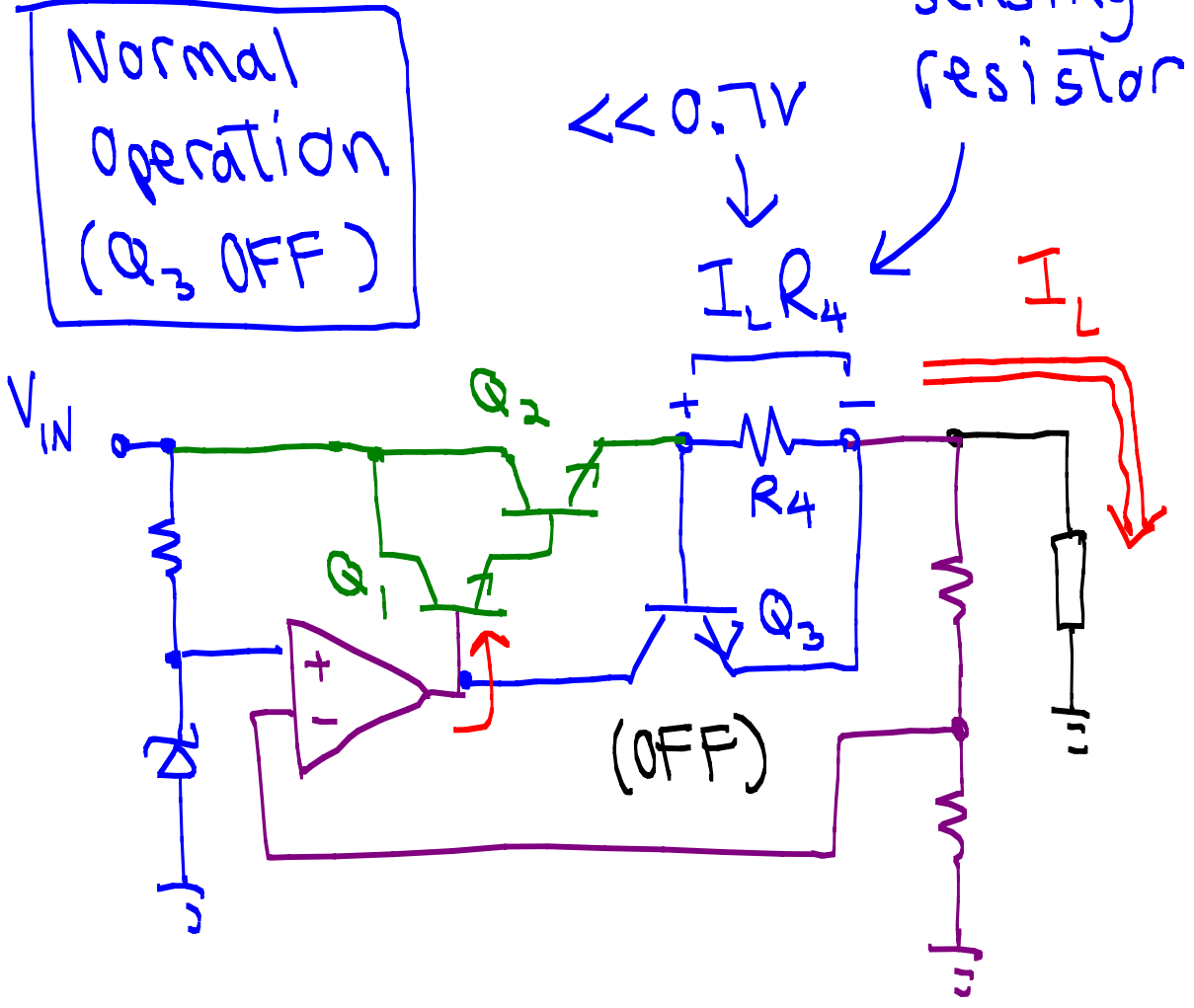3. Current Limiting

- Any regulator needs protection from short circuited output
- Simple method:




Short Circuit (Q_3 ON)

I_{sc} has limited value because Q_3 steals Q_1 base current


$\sim 0.7V$

$I_{sc} R_4$



I_{sc}

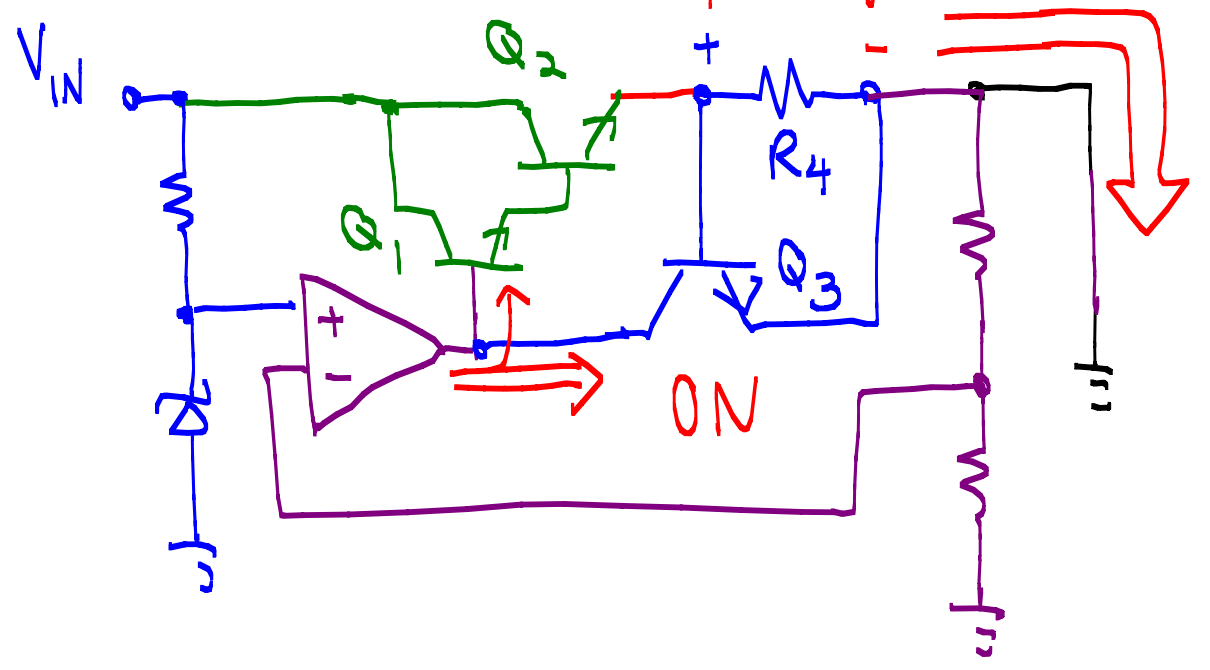

NOTE #1: Q_3 does not abruptly turn ON.

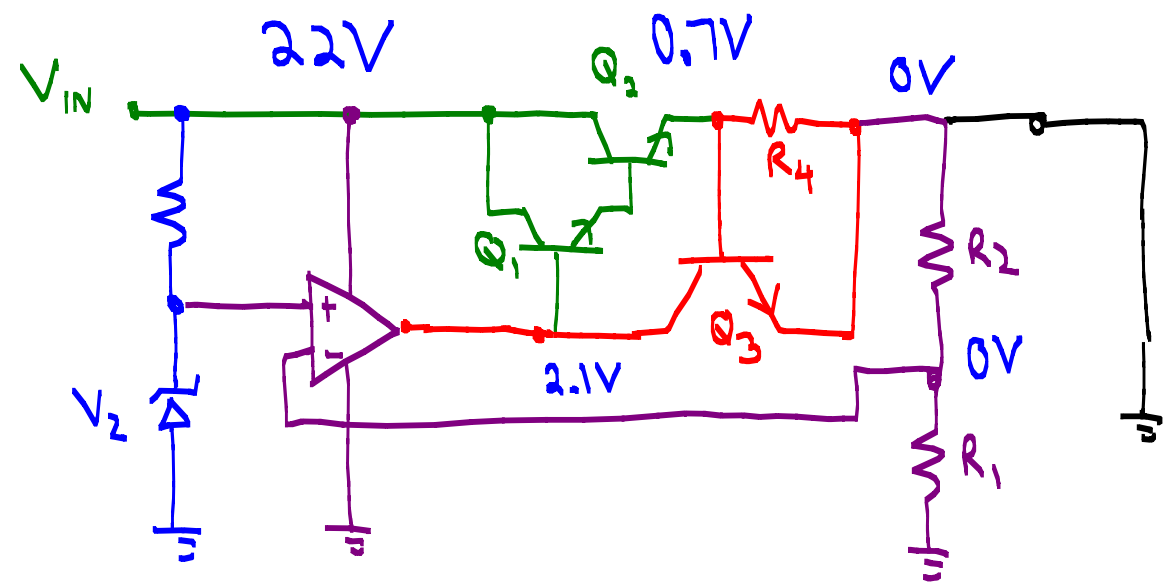

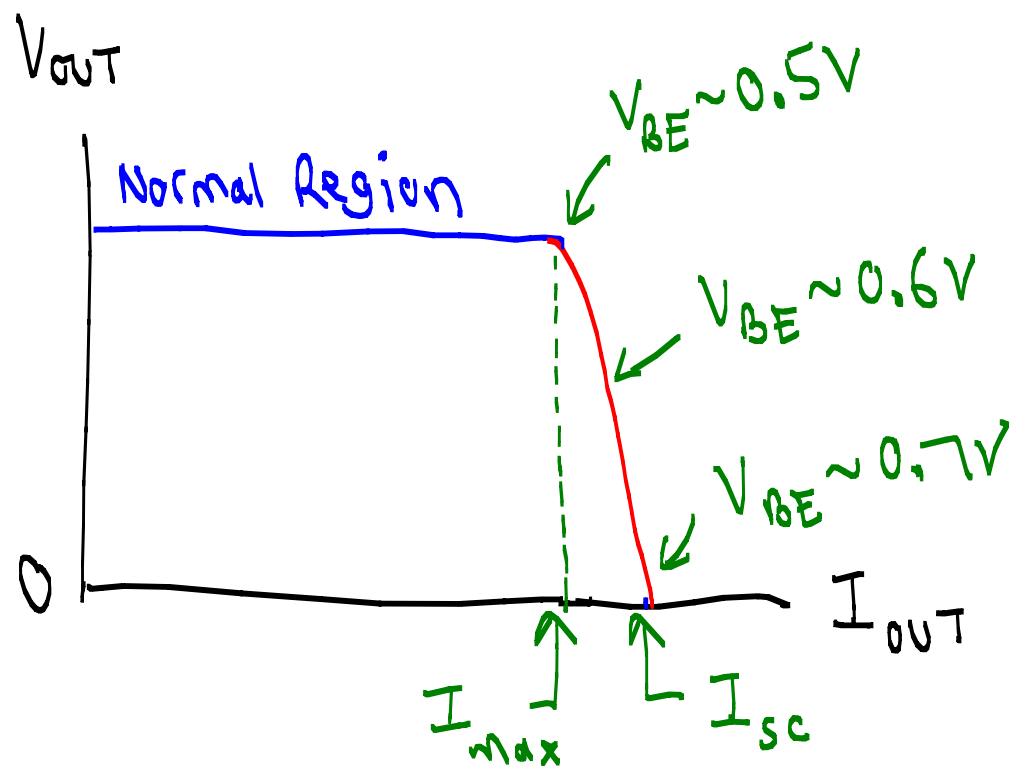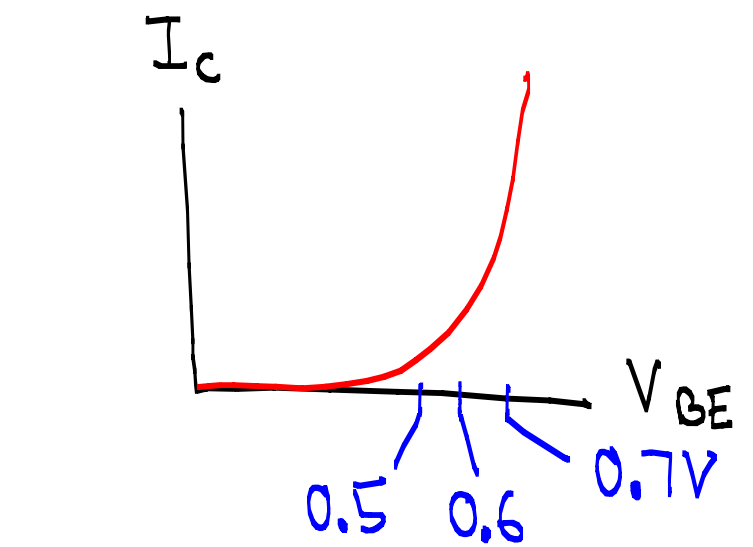NOTE #2: When $I_{out} = I_{sc}$, power dissipation in Q_2 can still be pretty large.



Ex: $R_4 = 0.8\Omega, V_{IN} = 22V$

$\Rightarrow I_{sc} \sim \frac{0.7V}{0.8\Omega} = 0.83A$

$P_a = \frac{0.83A}{71} (0.8V) + \frac{70}{71} (0.83A)(22 - 0.7) = \underline{\underline{17.4W!}}$

Appendix #1

TIP31

Typical $\beta \sim 70$

0.75A

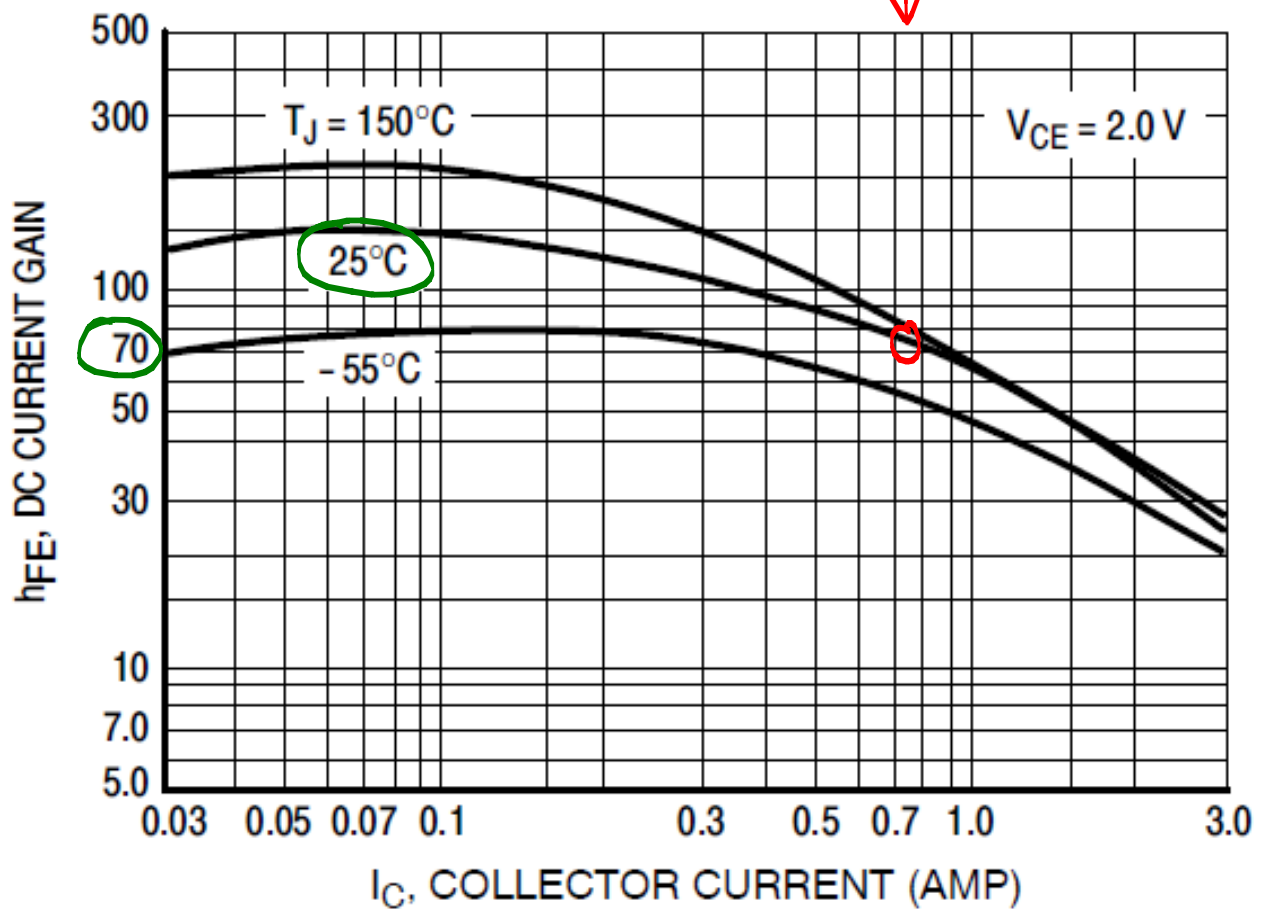


Figure 9. DC Current Gain

For BJT Switch

BJT active mode

$V_{BE} \sim 0.8V$

0.75A

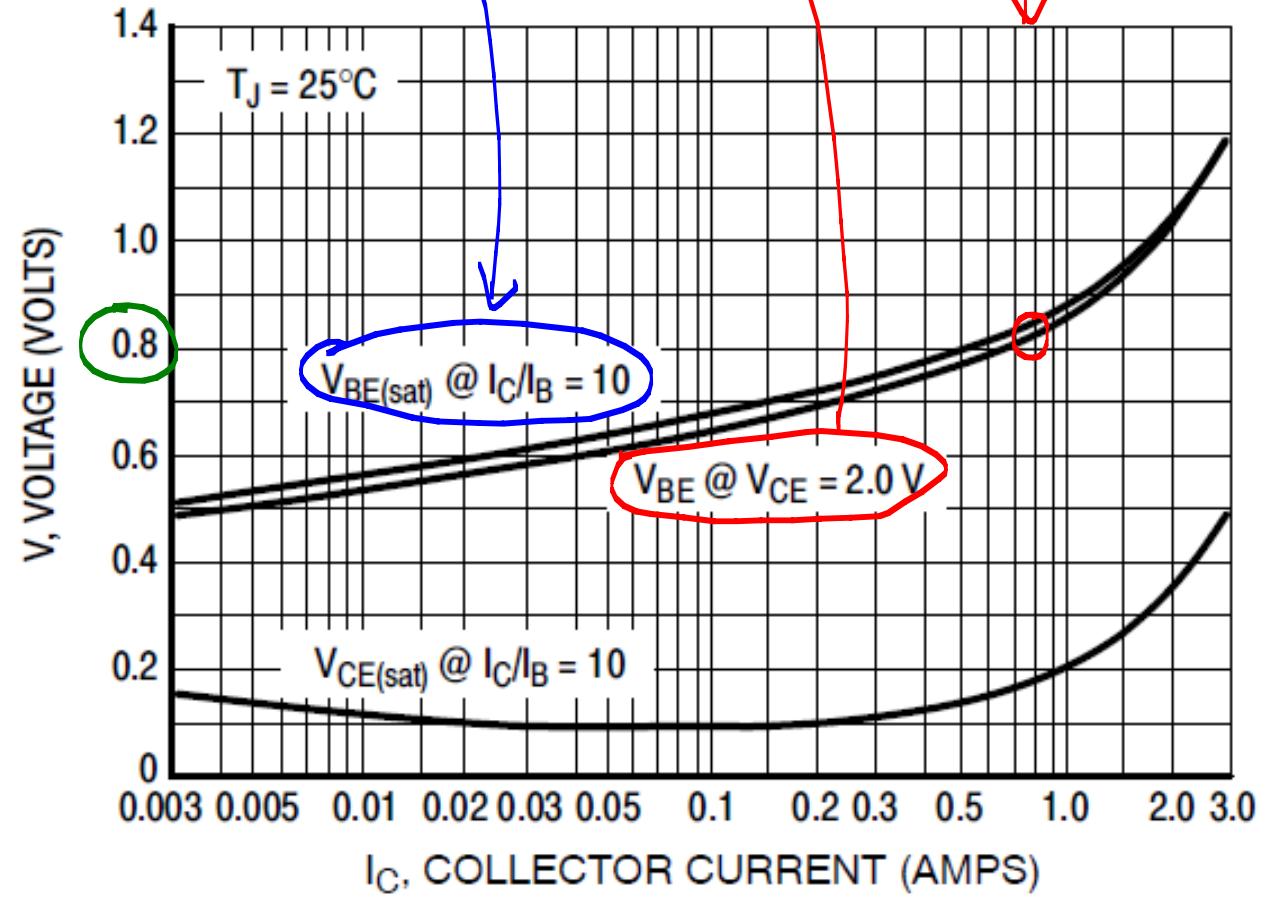


Figure 11. "On" Voltages

2N3904


$\beta \sim 225$



10 mA

$\sim 0.72V$

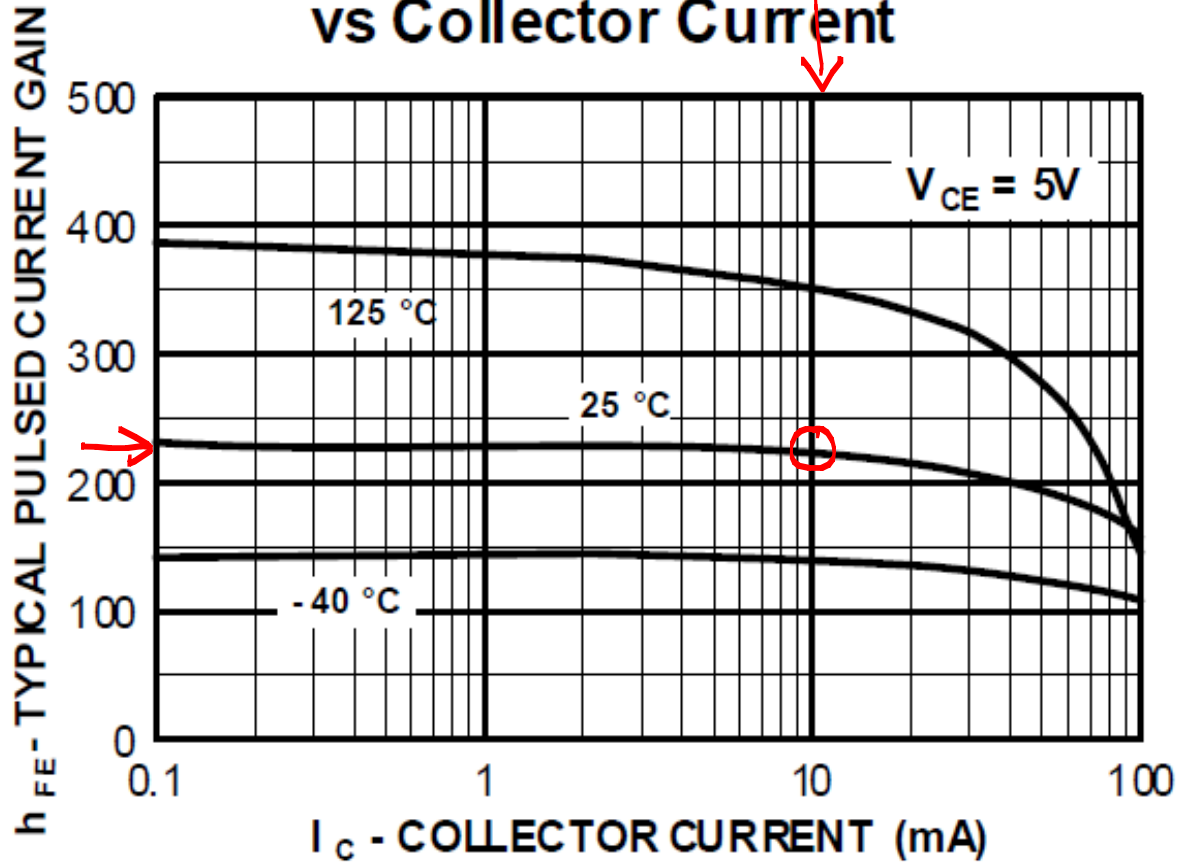Typical Pulsed Current Gain vs Collector Current



Base-Emitter ON Voltage vs Collector Current

