

Lecture 2: Linear Regulator

0. Review

1. Op amp feedback

2. Design example

3. Current limiting

• PreLab1 due Thu (Sep 19)
at lab session

• HW1 due Fri (Sep 20)
→ leave in box outside
my office

• Quiz1 next Tue (Sep 24)

Helpful textbook reading:



Ch 22-1 Power Supply Characteristics

22-3 Series regulators



22-4 Monolithic Linear regulators

0. Review



Diode

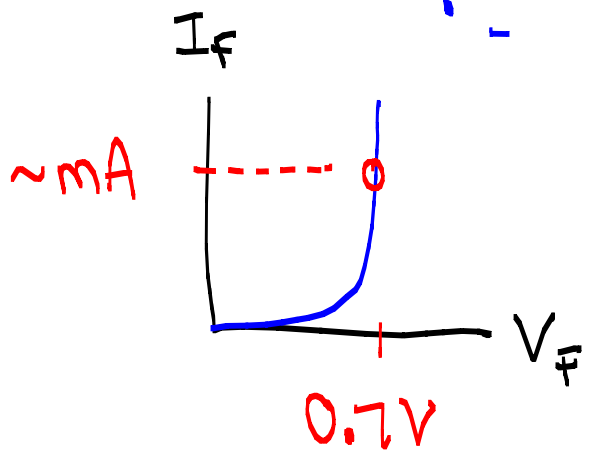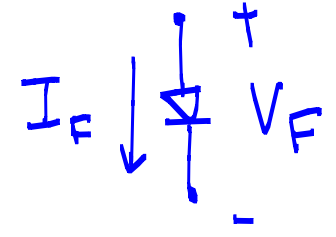

Zener

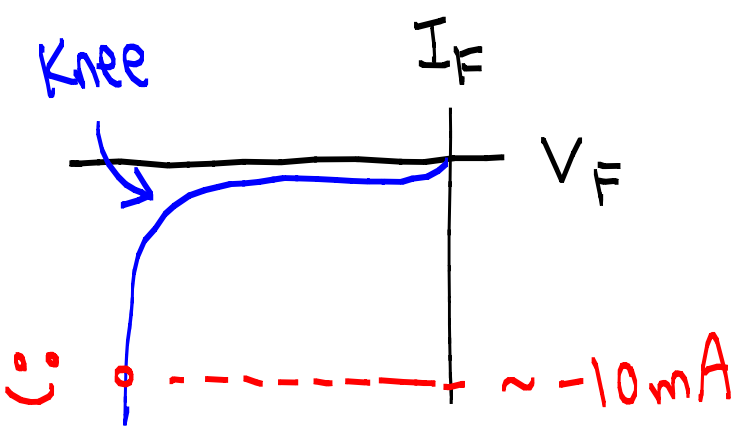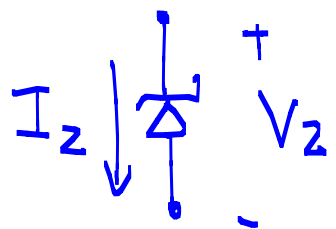


Zener Follower

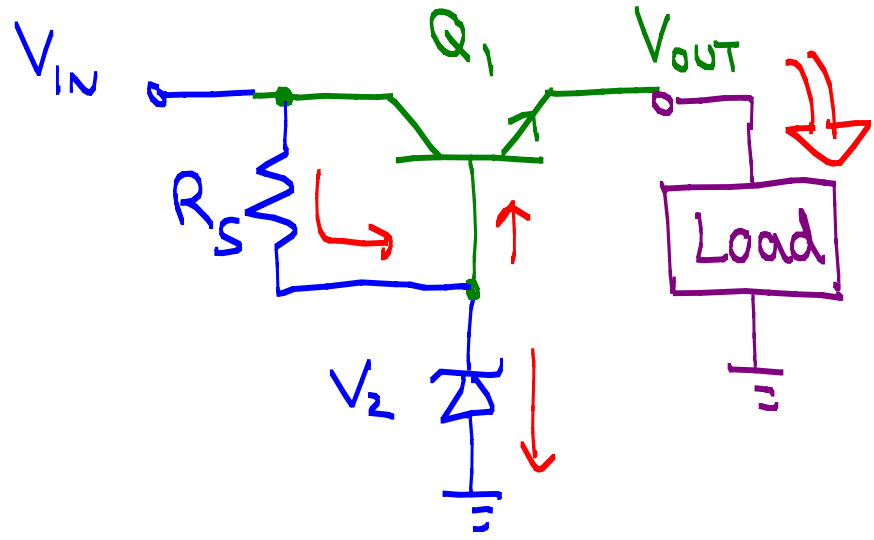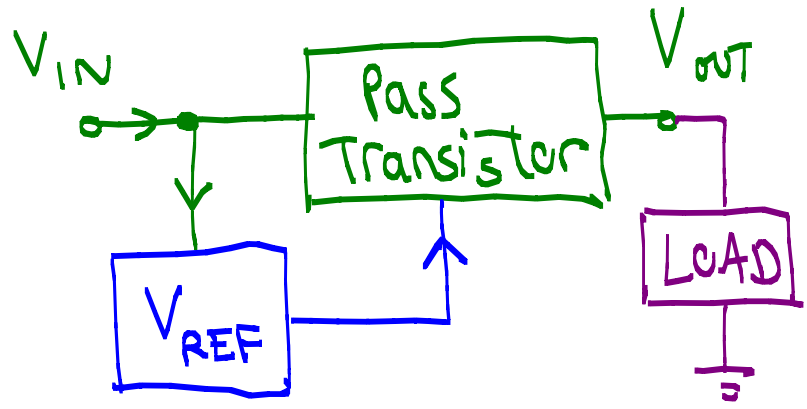

$$V_{OUT} = V_Z - V_{BE}$$

Heat sinks

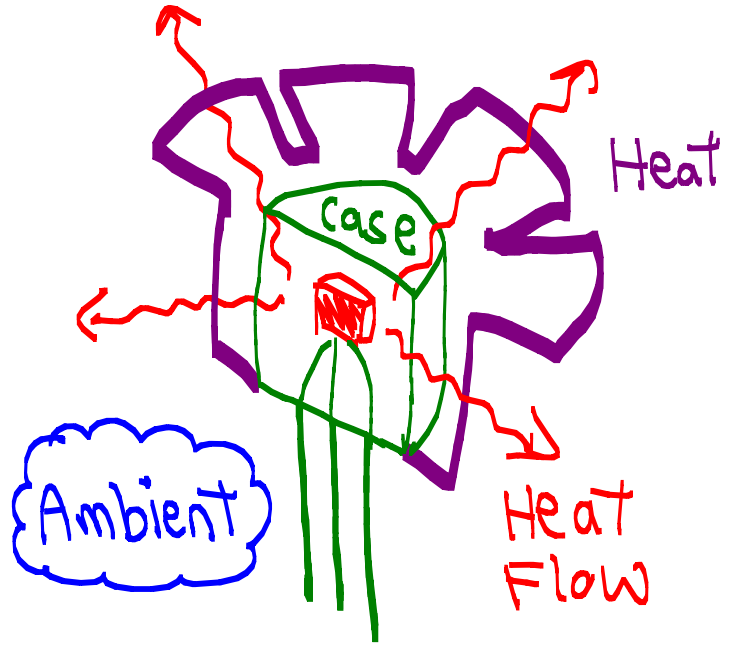

Θ_{JA} w/ heat sink

$$T_J = T_A + P \times [\Theta_{JC} + \Theta_{CS} + \Theta_{SA}]$$

↑ Junction to case
↑ Case to sink
↑ sink to Ambient


1. Negative Feedback

• Zener follower problems:

①


②

③

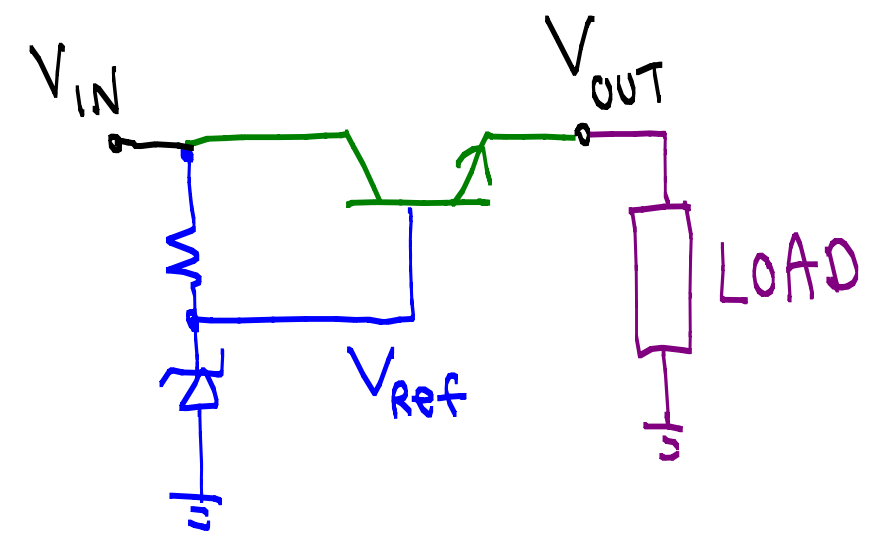


• A voltage regulator actively stabilizes V_{out} using _____ !

★ Use an op amp with negative feedback!

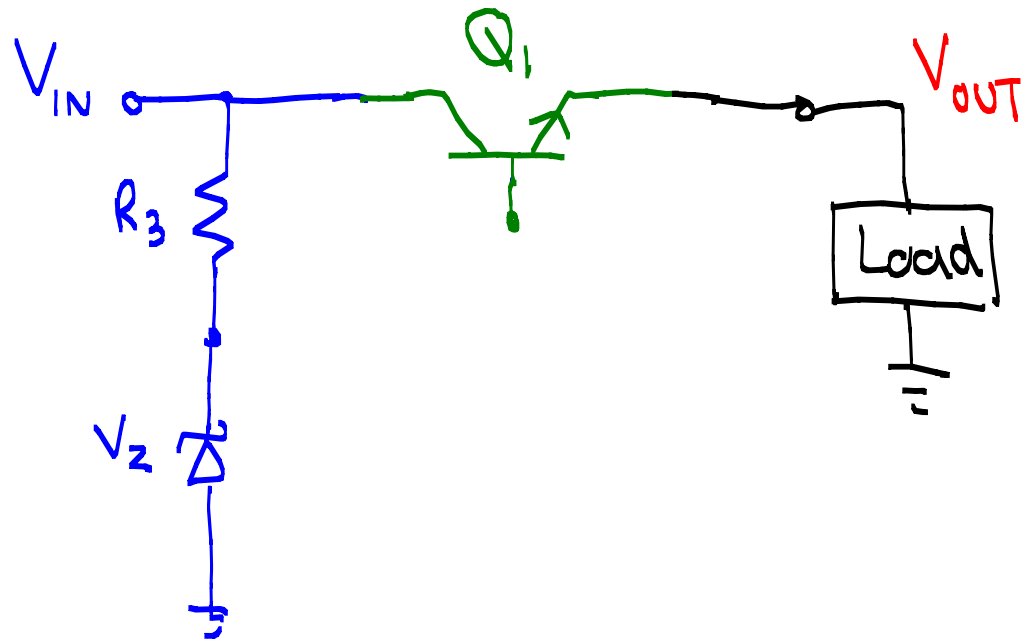

2.2

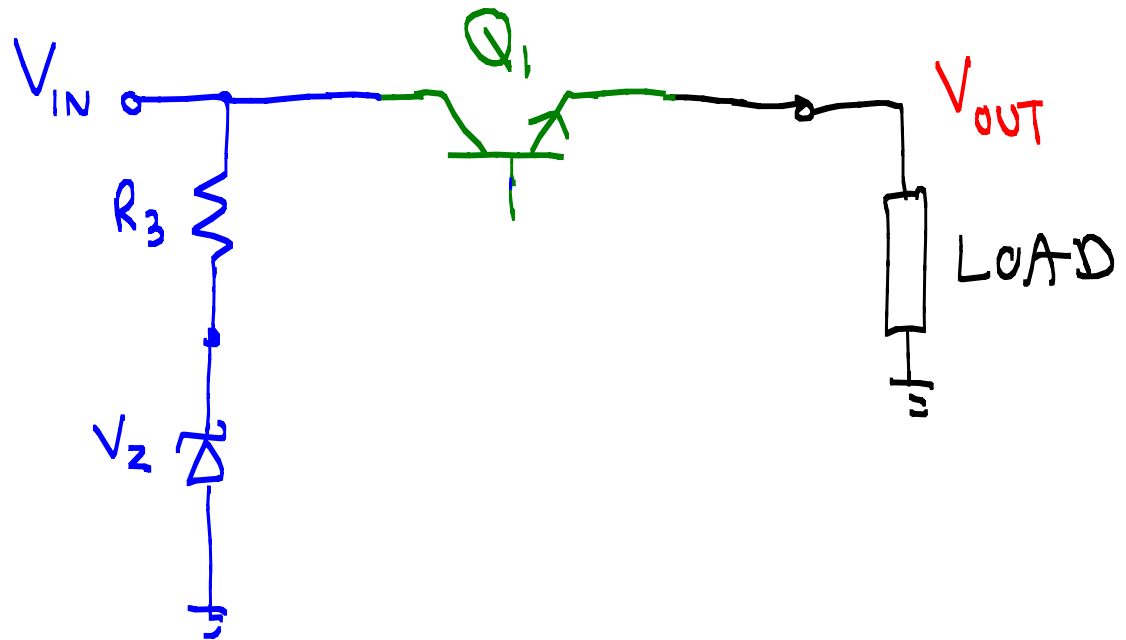


Op Amp Review

Ideal op amp with (-) feedback obeys two Golden Rules:

①

②


Ex. 1 Voltage Buffer

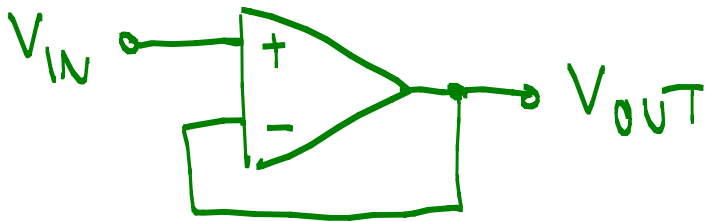

Ex. 2

Non-inverting Amplifier


2.3

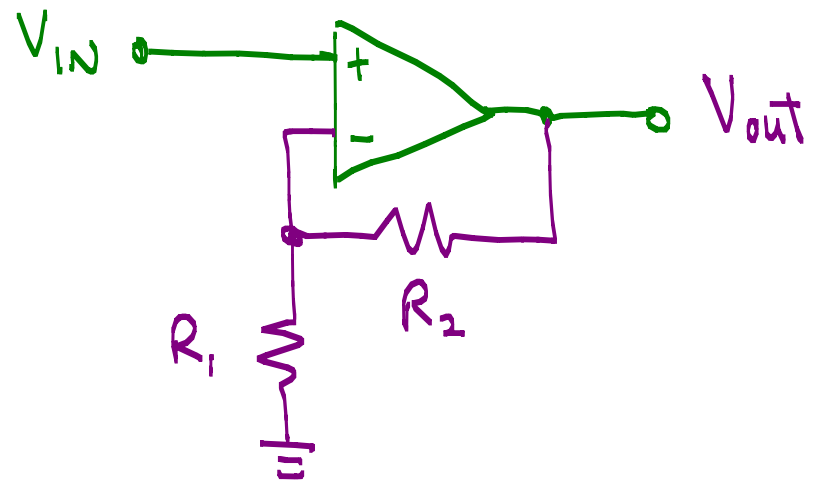

Q: How does the op amp do this?

An op amp is basically a _____
amplifier with _____

$$\Rightarrow V_{out} =$$


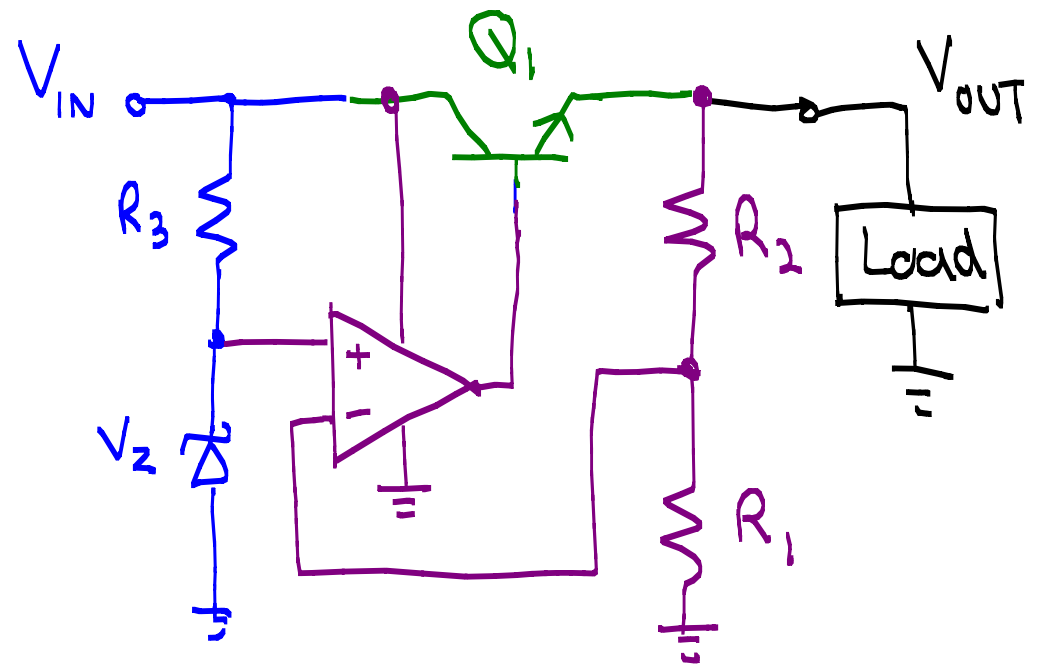


2.4

- Negative feedback greatly improves V_{OUT} regulation.


- Need to be careful with large I_{OUT}

EX:

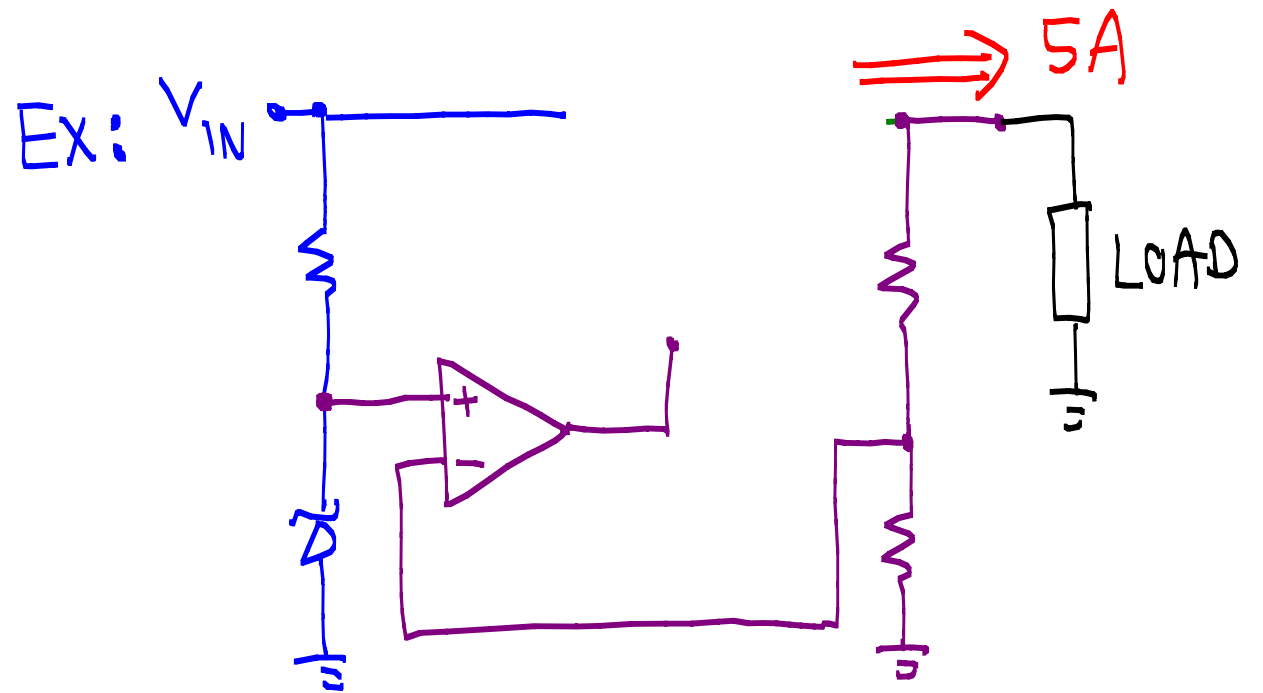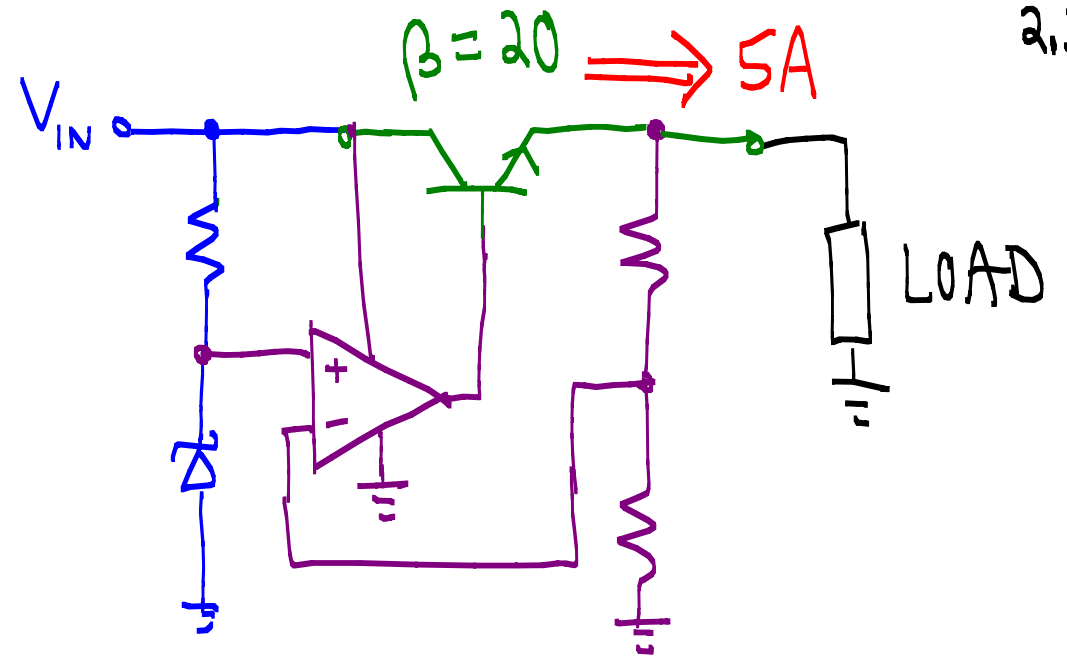

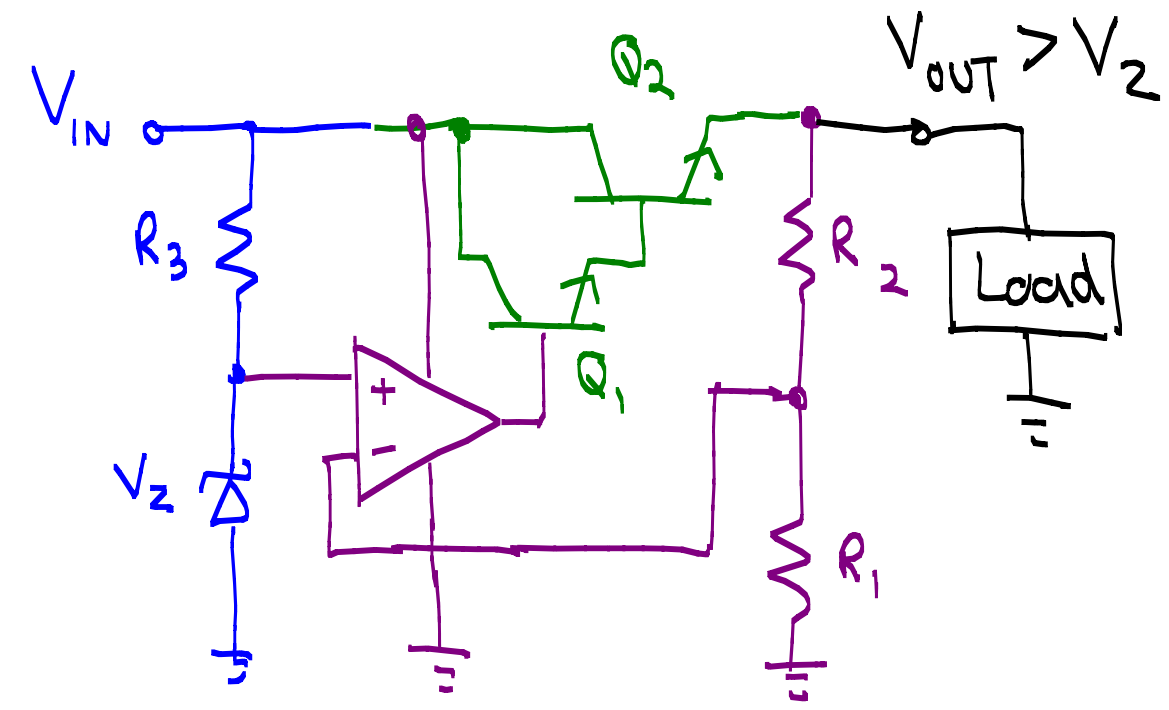3. Design Guidelines for Linear Regulator

- Minimum I_2
- Max Q_1 base current
- R_1 and R_2
- Make sure
- Don't fry



Example: $V_{in} = 19-22V$, $V_{out} = 15V$, $R_L > 20\Omega$

① Choose $V_z =$

② $I_{L,max} =$

Need to choose Q_2 and Q_1 ! Q_2 :

		Max P	
	Max I_c	($T_A=25^\circ C$)	($T_c=25^\circ C$)
2N3904	200 mA	.625W	
2N4401	600 mA	.625W	1.5W
TIP31	3 A	2W	40W
2N3055	15 A		115W

$$Q_1: I_{E1} =$$


$$\textcircled{3} V_{out} =$$

④ Minimum V_{in}

⑤ Power ratings

$R_3: \text{Max } P =$

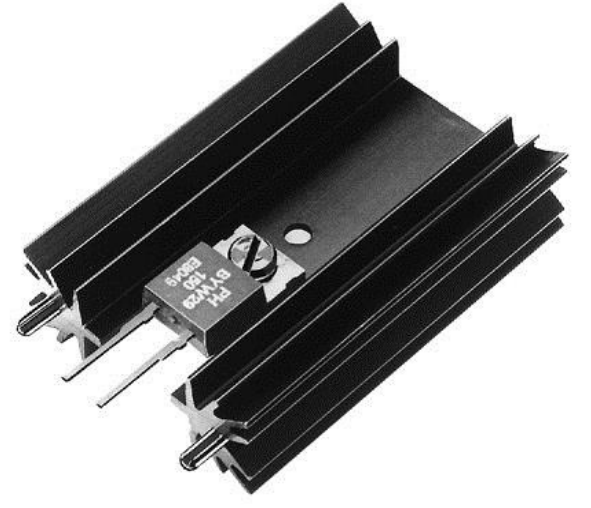$Q_2: \text{ TIP31 needs a heat sink! Let's assume: } \begin{cases} T_A = \\ \text{Max } T_J = \end{cases}$




R_1 and $R_2:$



3. Current Limiting

- Any regulator needs protection from short circuited output
- Simple method:



Normal Operation

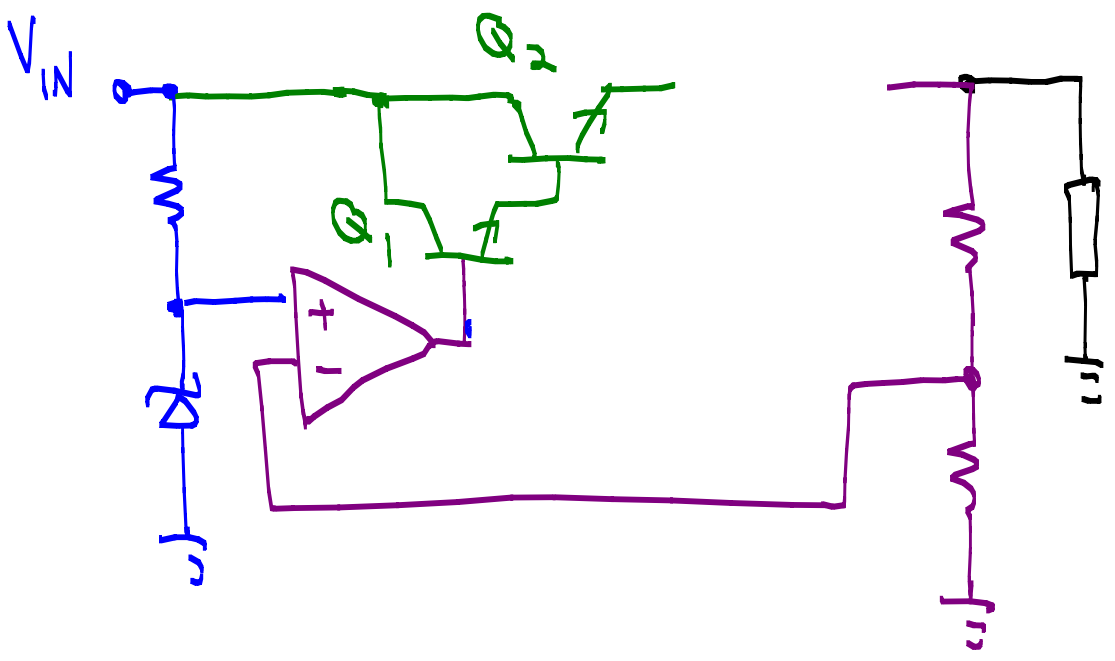


Short Circuit

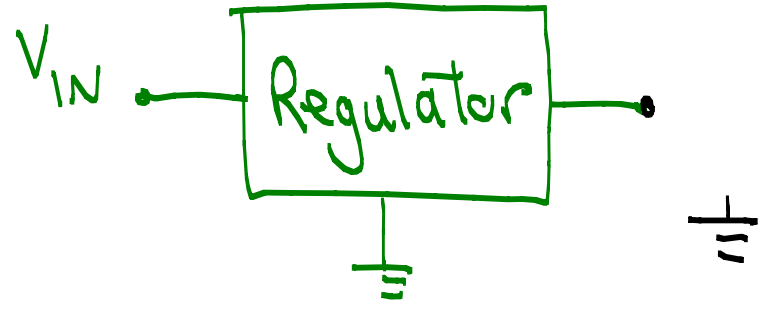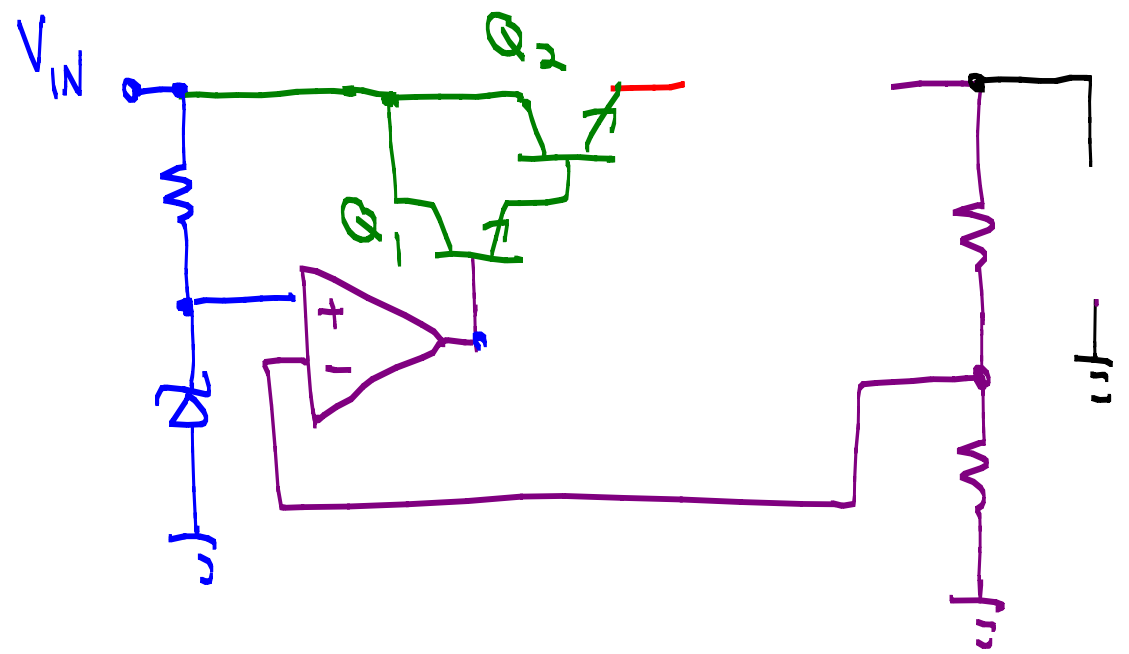

NOTE #1: Q_3 does not abruptly turn ON.

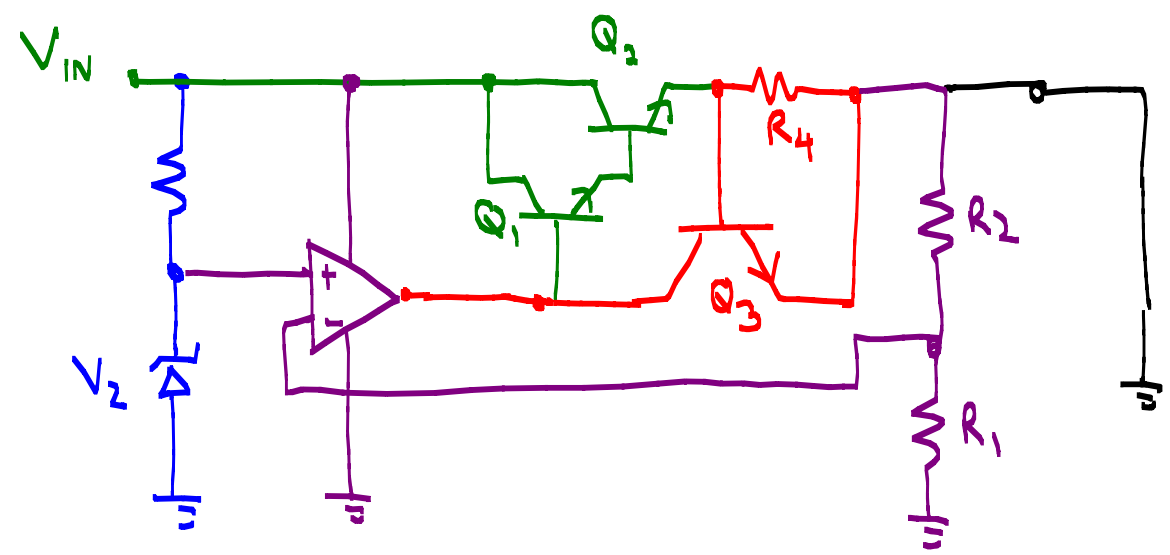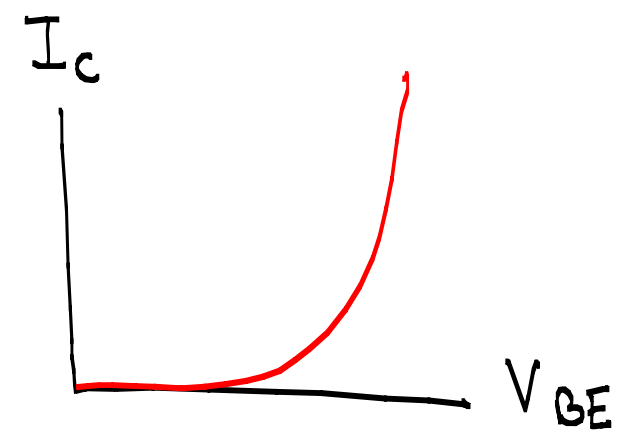

NOTE #2: When $I_{out} = I_{sc}$,

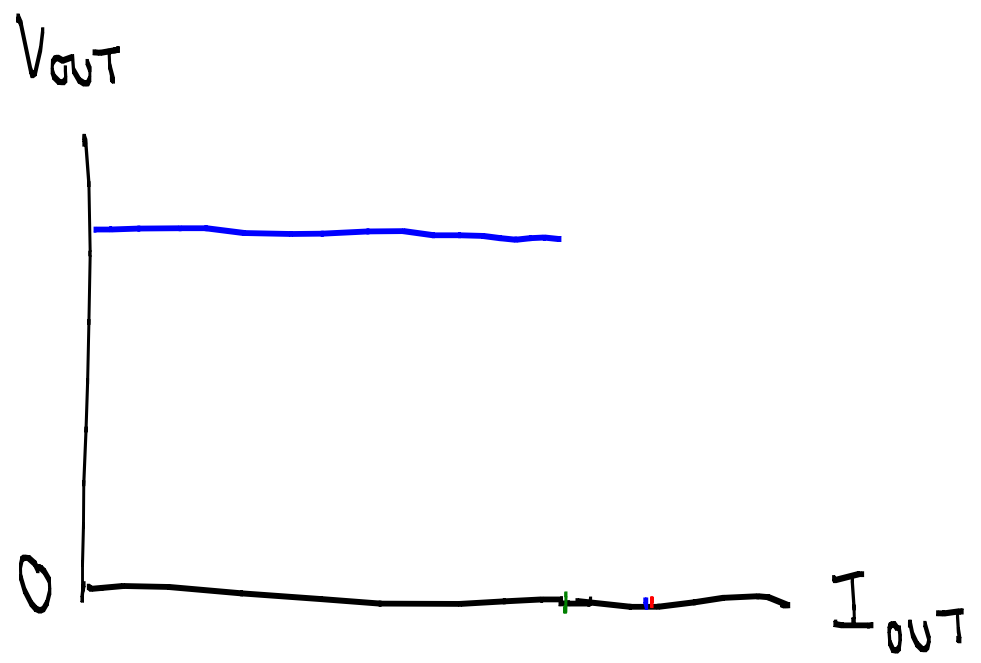

EX: $R_4 = 0.8 \Omega$, $V_{IN} = 22V$

Appendix #1

TIP31

Typical $\beta \sim 70$

0.75A

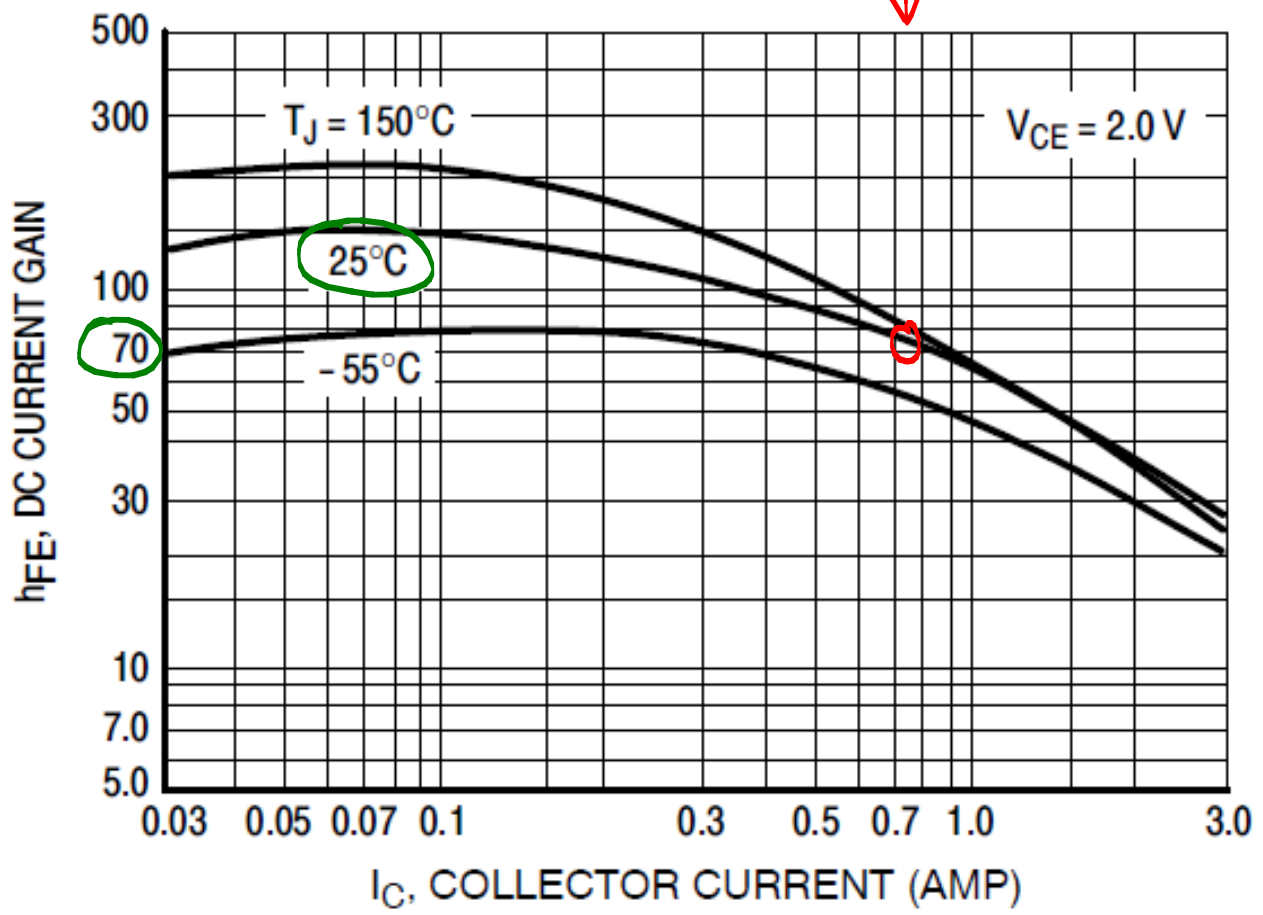


Figure 9. DC Current Gain

For BJT Switch

BJT active mode

$V_{BE} \sim 0.8V$

0.75A

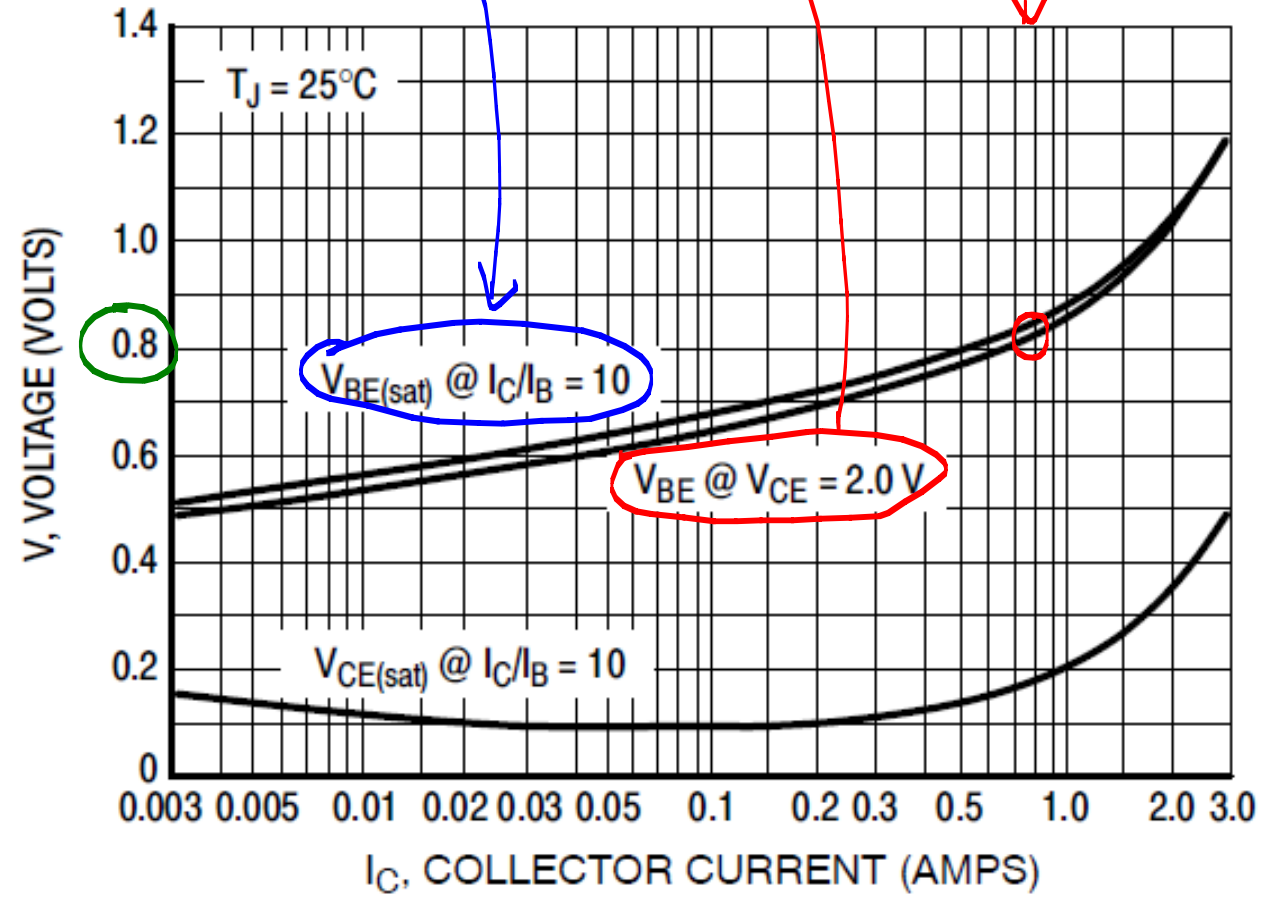


Figure 11. "On" Voltages


2N3904

$\beta \sim 225$

10 mA

$\sim 0.72V$

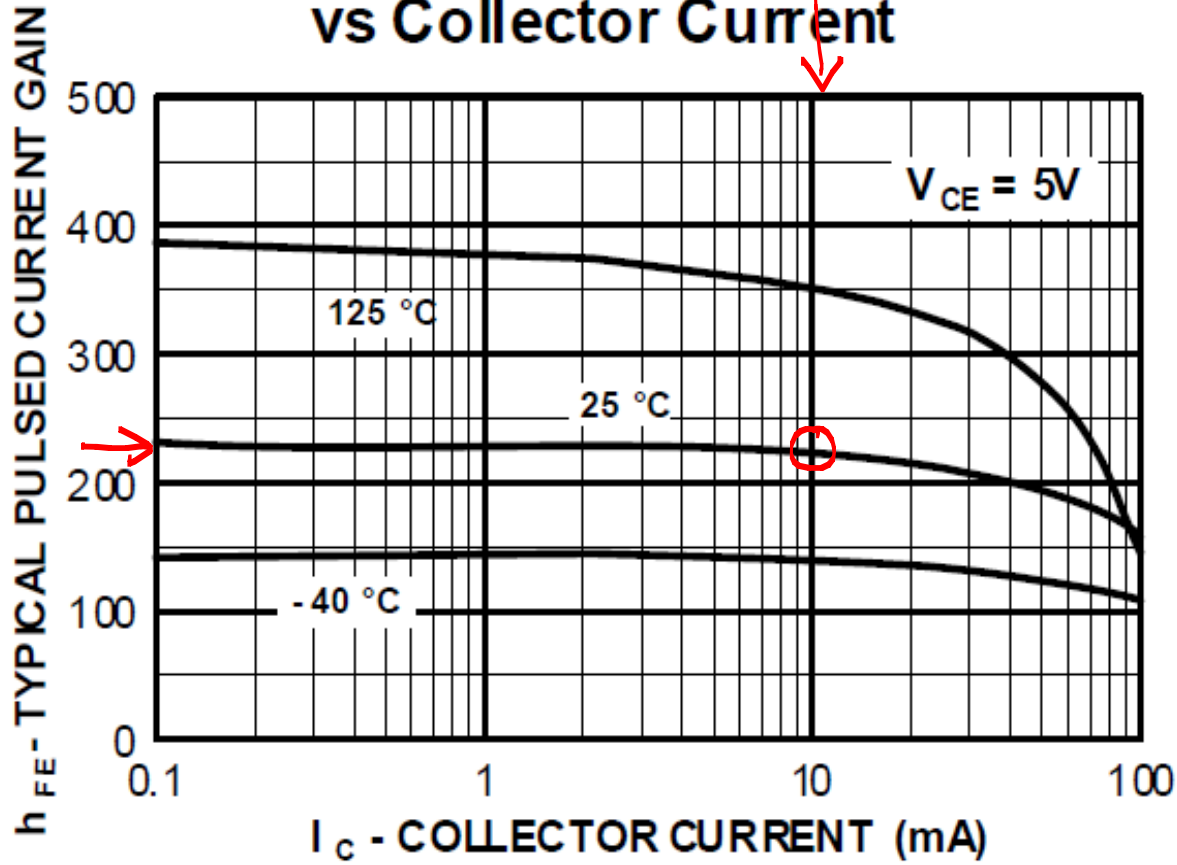Typical Pulsed Current Gain vs Collector Current



Base-Emitter ON Voltage vs Collector Current

