

Lecture 3 : Op Amp Basics

0. Quiz

1. Review

2. Op Amp Intro

3. Some useful op amp circuits

- Quiz next Tue (sep 24)

- PreLab 2 ← due at lab session

- Lab 1 report

↑ see course website for template

- HW2 due next Fri (sep 27)

Textbook reading: 16-1 Intro to Op Amps

16-4 Non-inverting amplifier


0. Review

- Zener follower + neg feedback


→ V_{out} no longer depends on V_{BE} !

→ Use Darlington for larger I_{out}
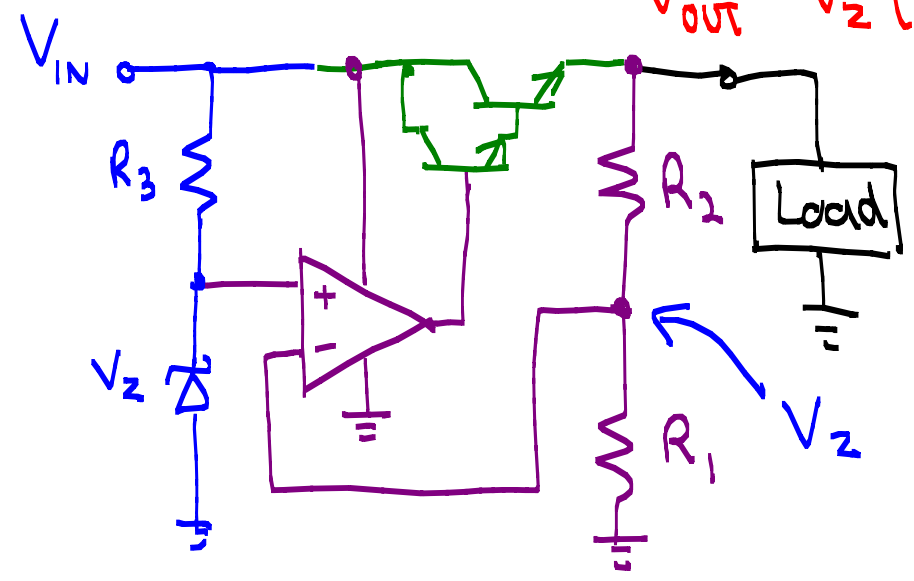
$$V_{out} = V_z \left(1 + \frac{R_2}{R_1} \right)$$




Short Circuit (Q_3 ON)

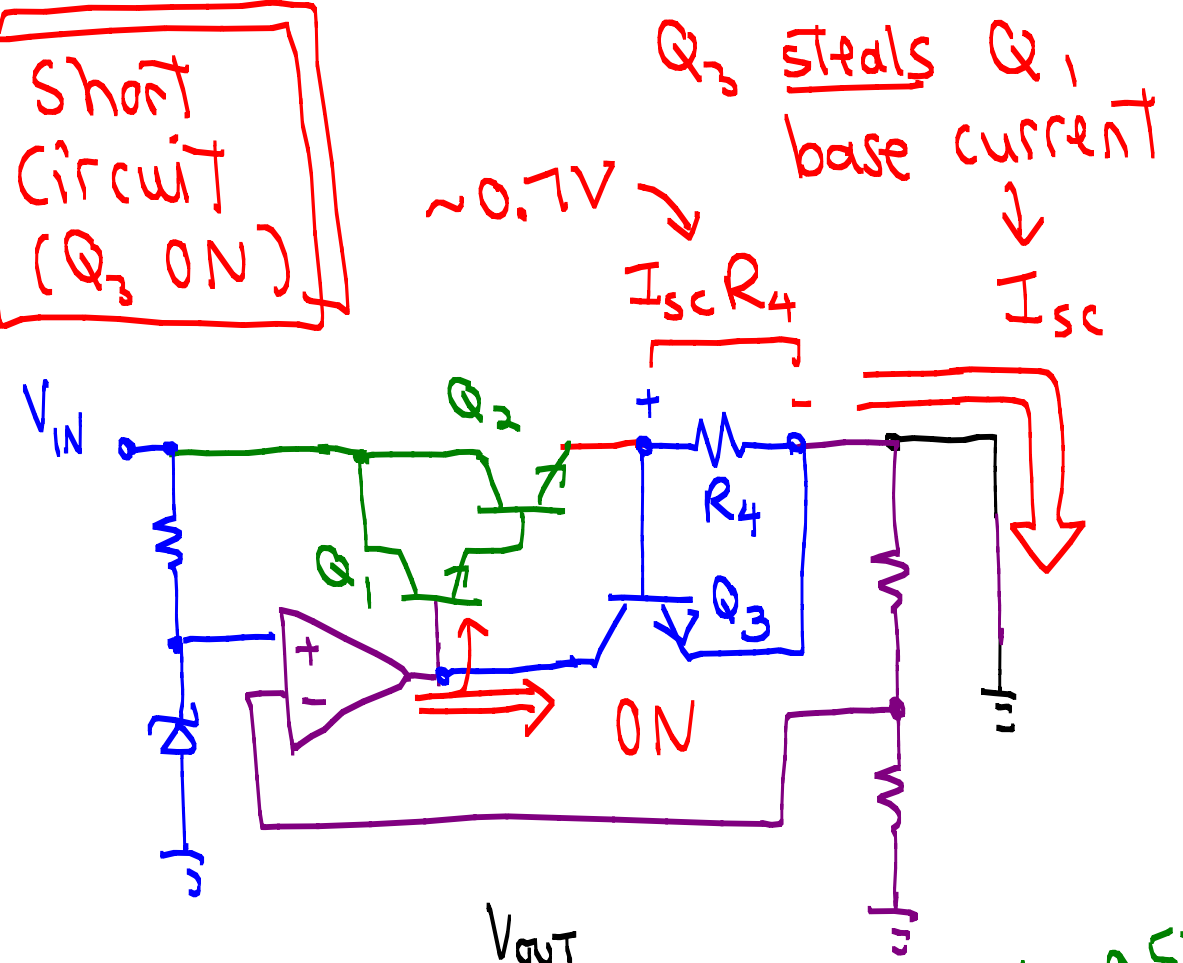


NOTE:

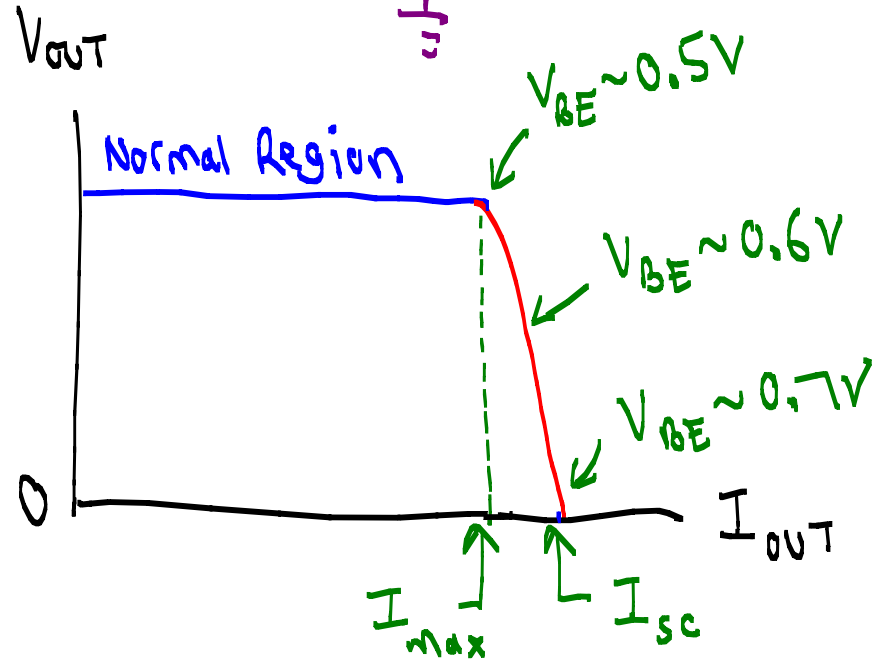- Q_3 does not abruptly turn ON
- Q_3 can dissipate lots of power!



1. Op Amp Intro


• Consider the following application ...

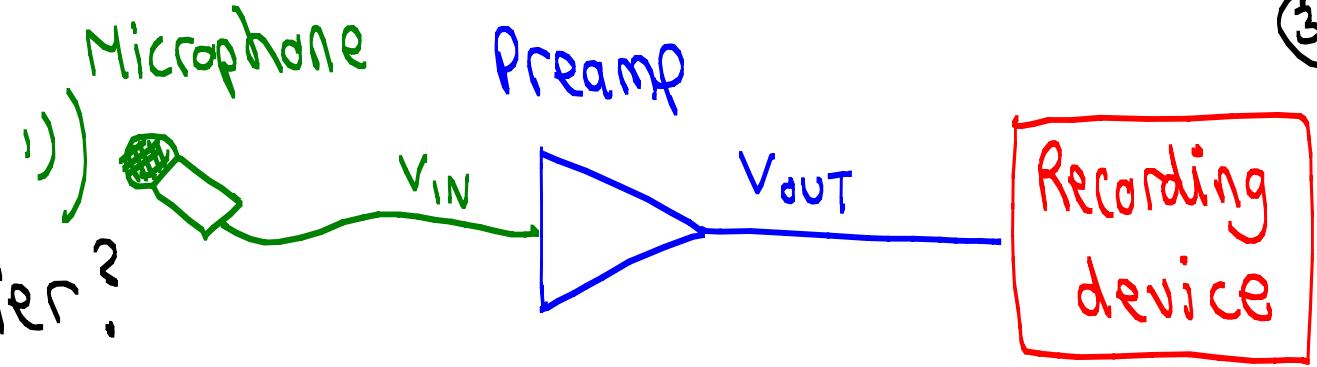

Q: How to make an audio preamplifier?

• How about a common emitter amplifier?

EX:

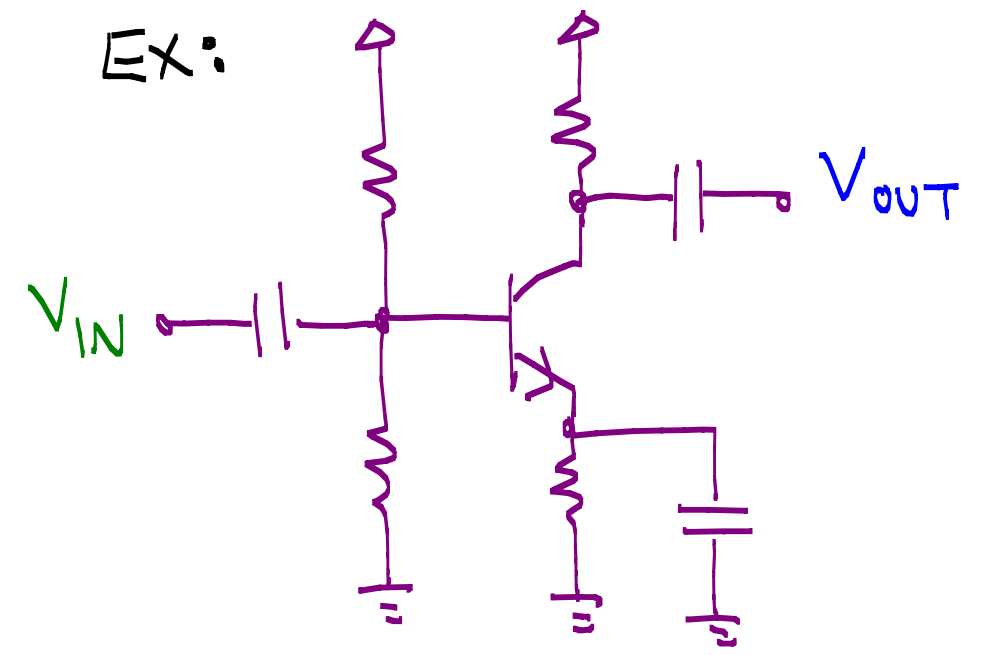


Only for AC signals
 Medium Z_{IN} ($k\Omega$), Large Z_{OUT} ($k\Omega$)

Variations in β affect performance

★ An op amp is usually the best choice for designing an amplifier!

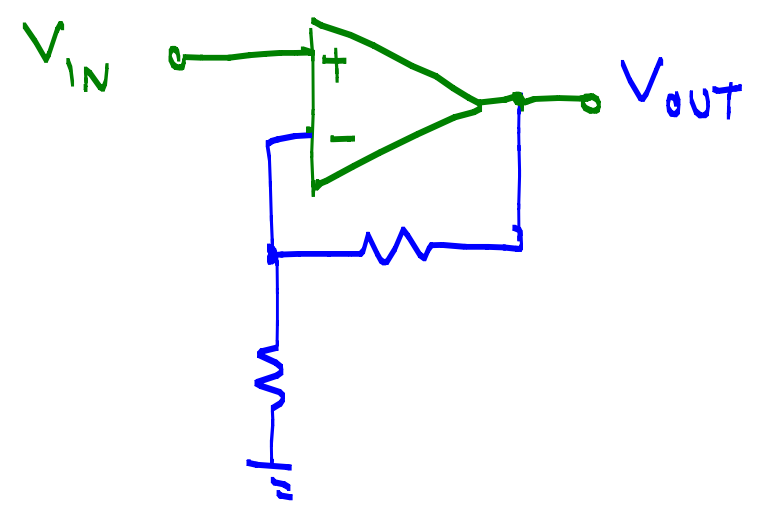- DC or AC amplifiers possible
- Large Z_{IN} ($M\Omega$), tiny Z_{OUT} ($< 1\Omega$)
- Accurate + stable performance




• Most op amp circuits can be understood by using two Golden Rules:

Ex: Inverting Amplifier

- ① The two input terminals are at the same voltage.
- ② the two input terminals draw no current.

"Virtual Short"

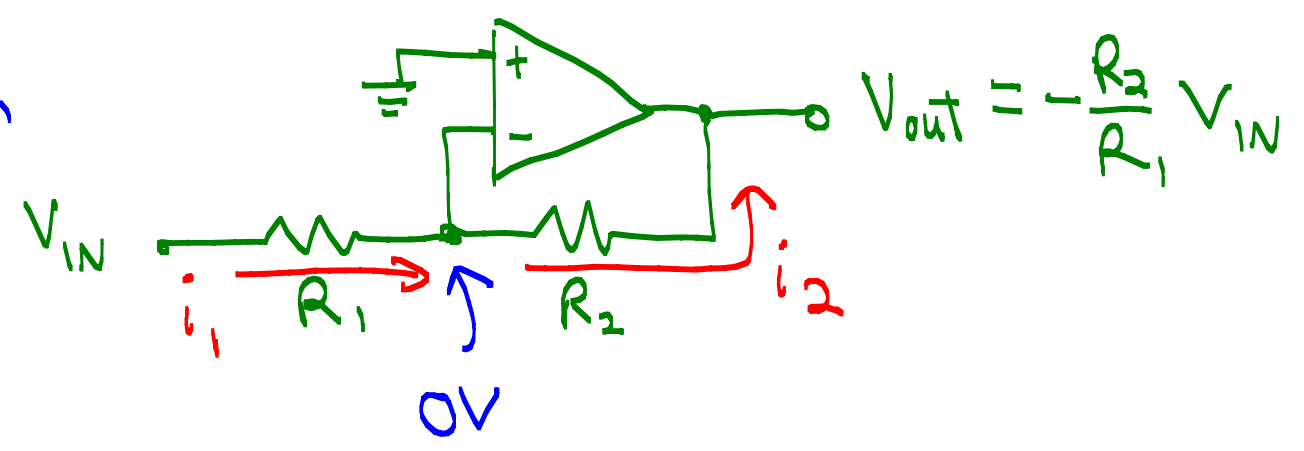

(1) Golden Rule #1: $V_- = V_+ = 0$

(2) KCL at node V_- : $i_1 = i_2$


$$\frac{V_{IN} - 0}{R_1} = \frac{0 - V_{OUT}}{R_2}$$

$\Rightarrow V_{OUT} = -\frac{R_2}{R_1} V_{IN}$ ✓ inverting!

Gain = $\frac{V_{OUT}}{V_{IN}} = -\frac{R_2}{R_1}$

NOTE: These golden rules assume an ideal op amp used with negative feedback! We'll soon discuss real properties...

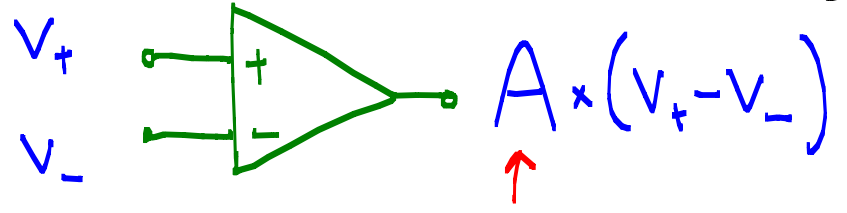An op amp is really a differential amplifier with HUGE GAIN.



→ Negative feedback means a portion of the output is fed back to (-) input.

(NOTE: This simplified derivation still assumes op amp draws zero current.)


Open Loop Gain $\sim 10^6!$

$$V_{OUT} = A * (V_+ - V_-) = A * (0 - V_-) = -A V_-$$

$$= -A V_{IN} \frac{R_2}{R_1 + R_2} - A V_{OUT} \frac{R_1}{R_1 + R_2}$$

$$V_{OUT} \approx \frac{-A \frac{R_2}{R_1 + R_2} V_{IN}}{1 + A \frac{R_1}{R_1 + R_2}} \approx -\frac{R_2}{R_1} V_{IN}$$

(A is HUGE)

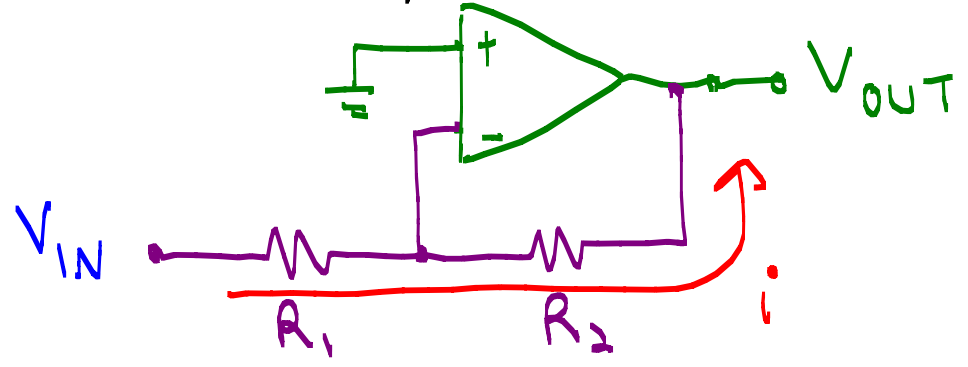



$$V_- = V_{IN} - i R_1 = V_{IN} - \frac{V_{IN} - V_{OUT}}{R_1 + R_2} R_1$$

$$= V_{IN} \left(1 - \frac{R_1}{R_1 + R_2} \right) + V_{OUT} \frac{R_1}{R_1 + R_2}$$

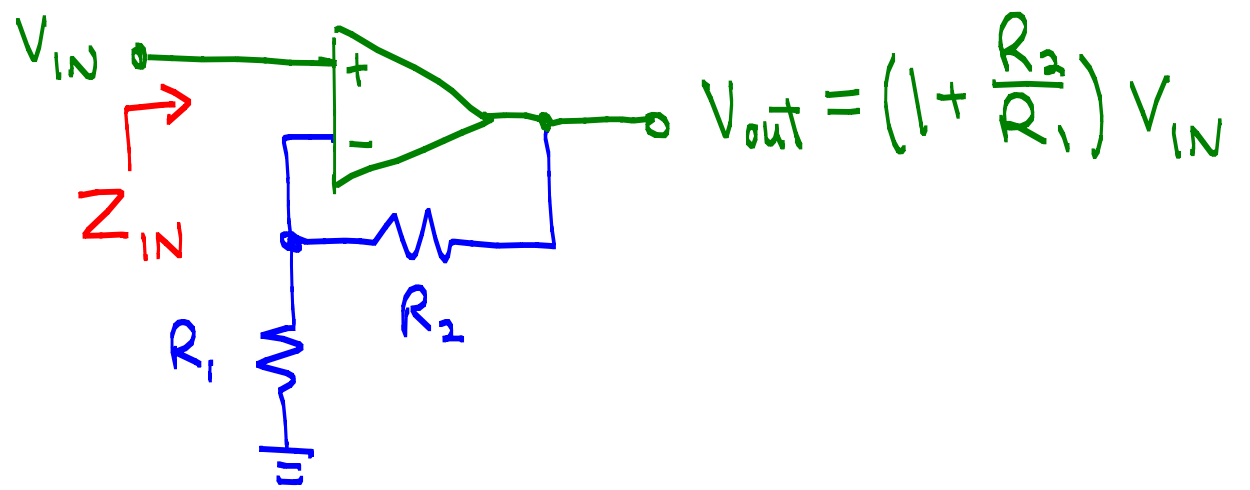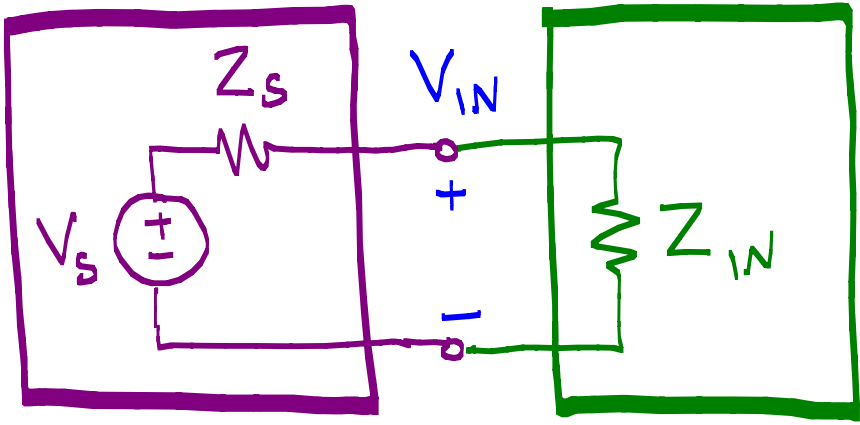2. Some useful op amp circuits

- Non-inverting amplifier


* Very high Z_{in} ($> 100 M\Omega$)
 is good for signal sources
 with large Z_s !



$$V_{out} = \left(1 + \frac{R_2}{R_1}\right) V_{in}$$

NOTE: Typically, $R_1 > 1 K\Omega$

$R_2 < 10 M\Omega$

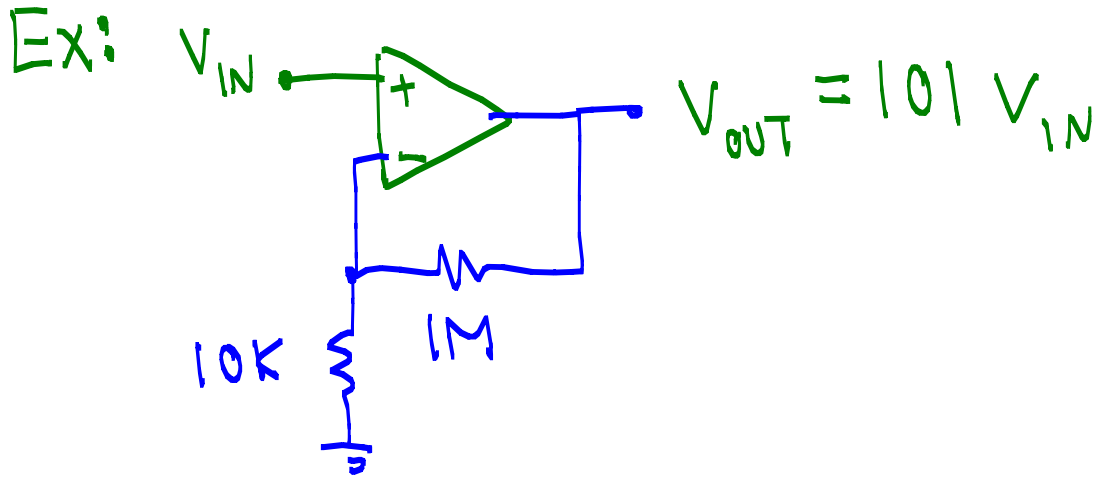


• Photodetector Amplifier

Many photodetectors produce a current output. Why?

→ Usually based on semiconductors

- ① Light generates electron-hole pairs
- ② Internal field separates the pairs
- ③ output is a "photocurrent"

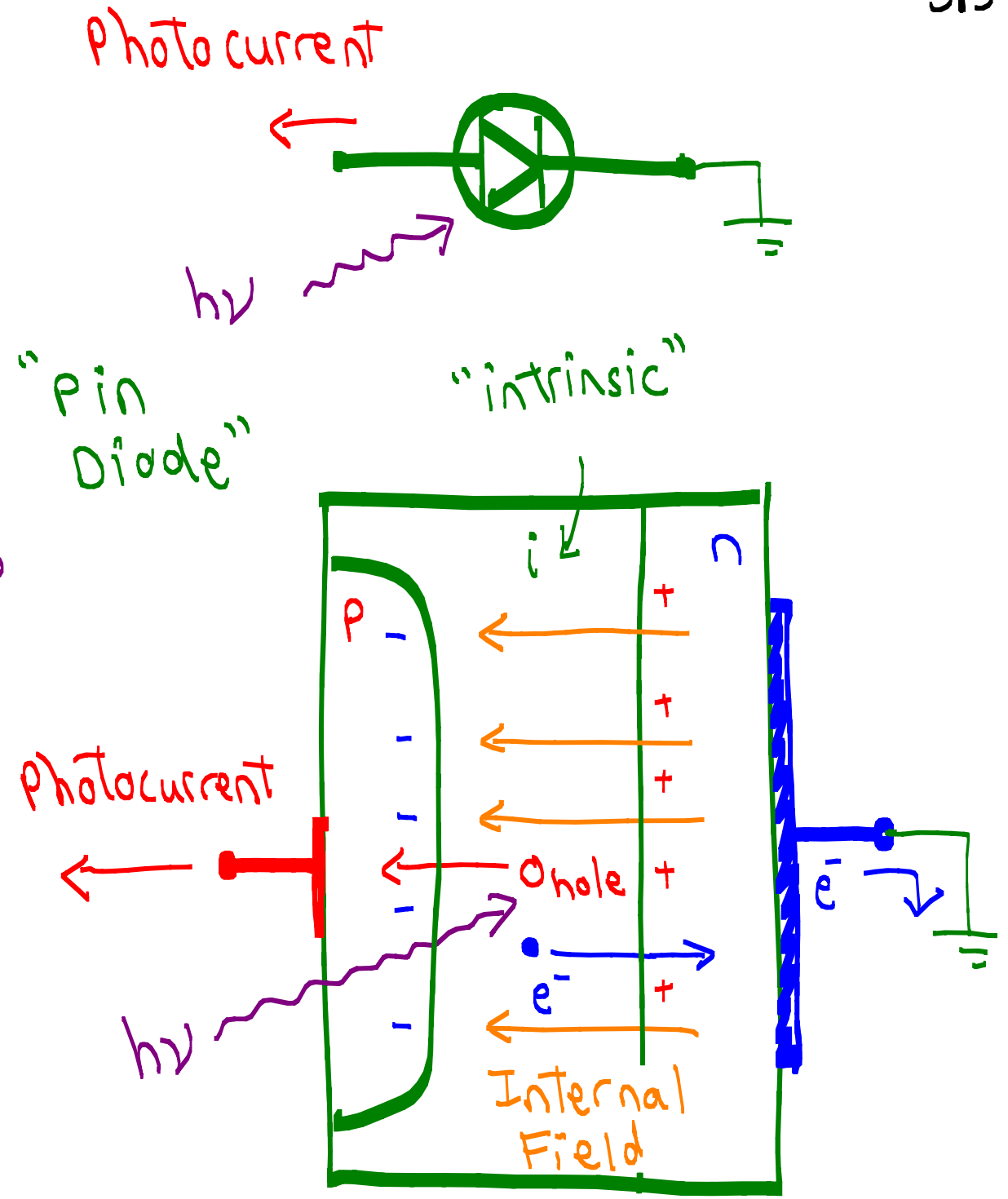Q: How to convert this into a voltage signal?





- Transimpedance Amplifier ← Also called "current-to-voltage converter"

KCL at node v_- :

$$I_{IN} = I = \frac{V_{OUT} - 0}{R_F}$$

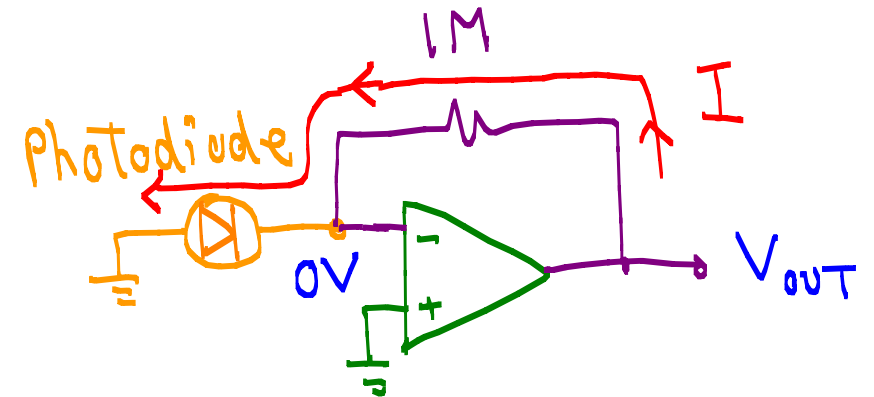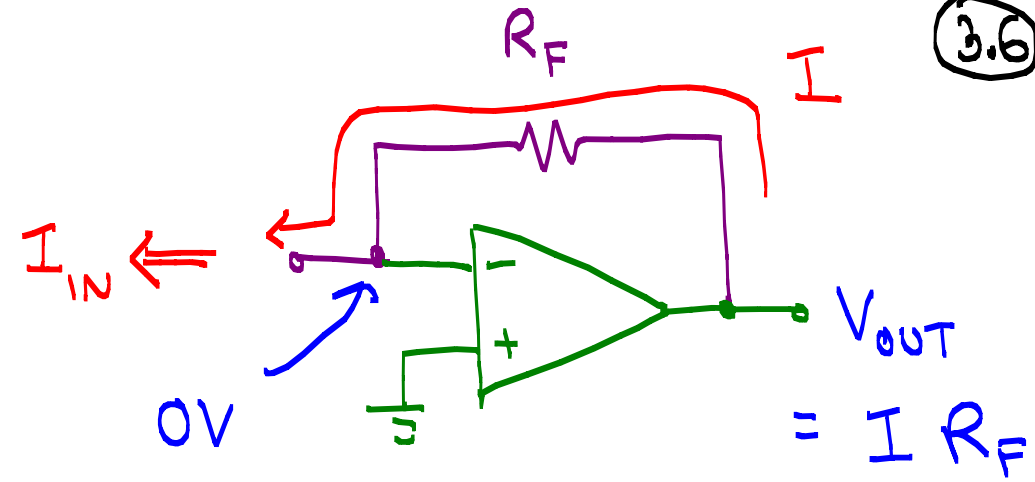
$$\Rightarrow \boxed{V_{OUT} = I_{IN} R_F}$$



★ Very useful for photodetectors!

- Light produces current
- Virtual ground makes $Z_{in} \sim 0$
- Fixed sensor voltage leads to more linear response

Good for sensor producing a current

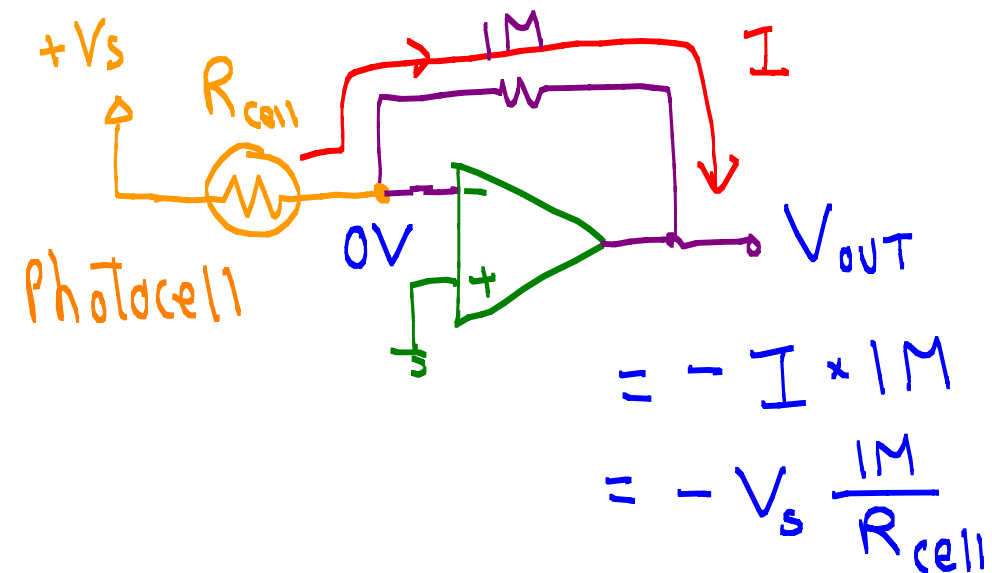

• Summing amplifier ←
e.g. audio mixer

$$V_- = V_+ = 0 \text{ (Rule \#1)}$$


$$i_1 + i_2 = i$$

$$\frac{V_{IN1} - 0}{R_1} + \frac{V_{IN2} - 0}{R_2} = \frac{0 - V_{OUT}}{R}$$


$$\Rightarrow V_{OUT} = - \left(\frac{R}{R_1} V_{IN1} + \frac{R}{R_2} V_{IN2} \right)$$

$$V_{OUT} = - \left(\frac{R}{R_1} V_1 + \frac{R}{R_2} V_2 + \dots + \frac{R}{R_n} V_n \right)$$

Sometimes (+) input
is top

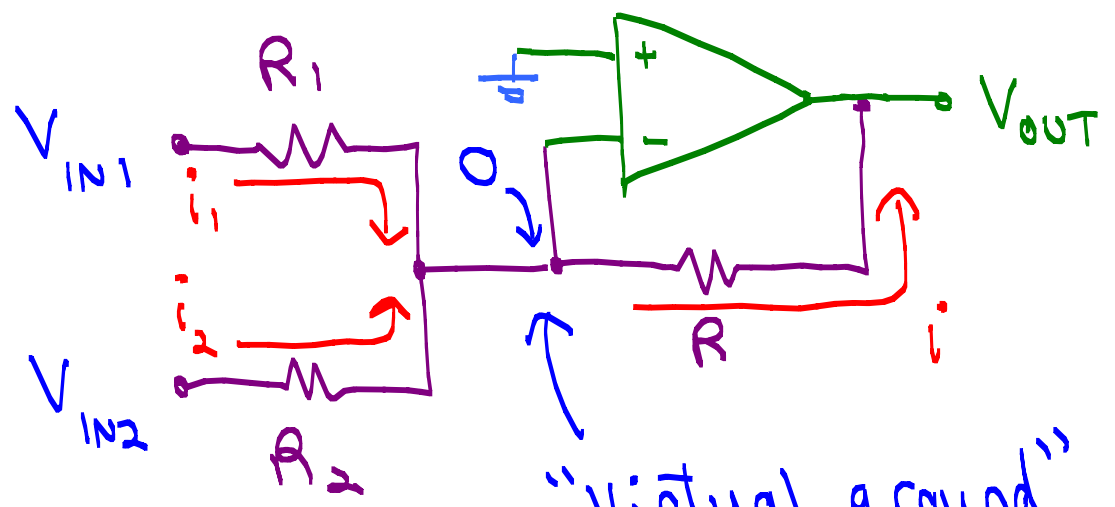

"Virtual ground"
is very useful!

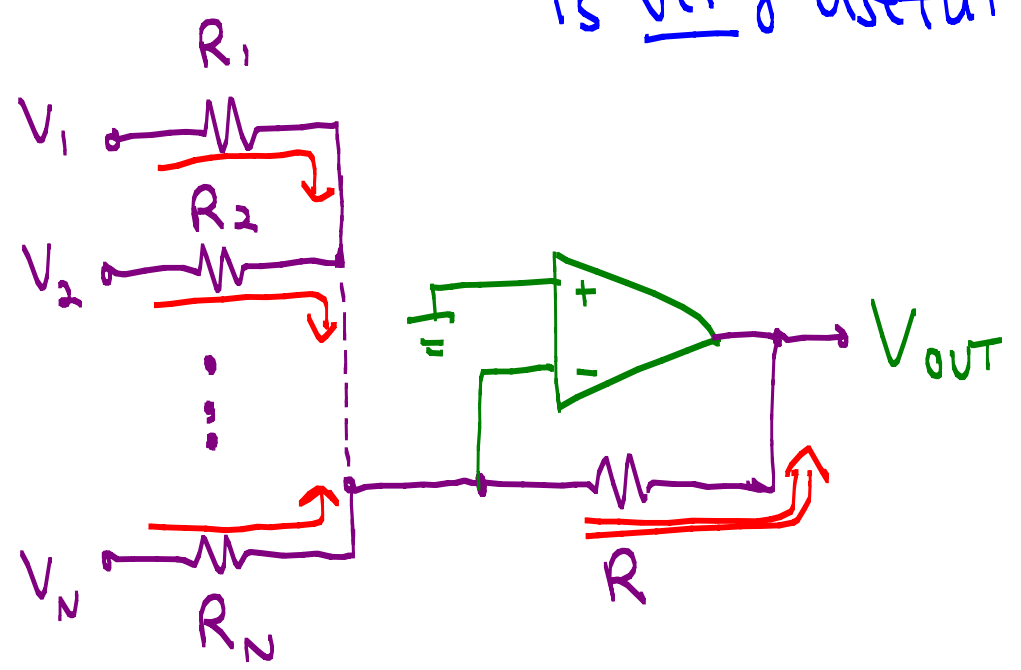


- For other useful circuits, consult application notes from manufacturers! (3.8)

Ex:



Application Report
SNOA621C-February 1969-Revised May 2013


AN-20 An Applications Guide for Op Amps

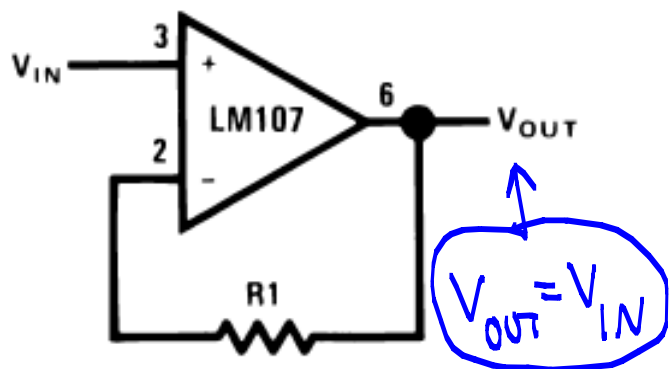


Voltage Buffer



Discuss this later...

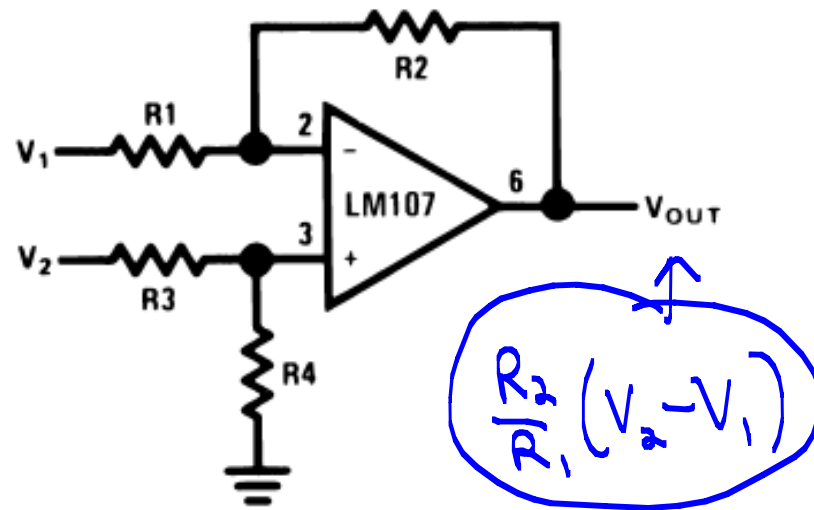

Difference Amplifier

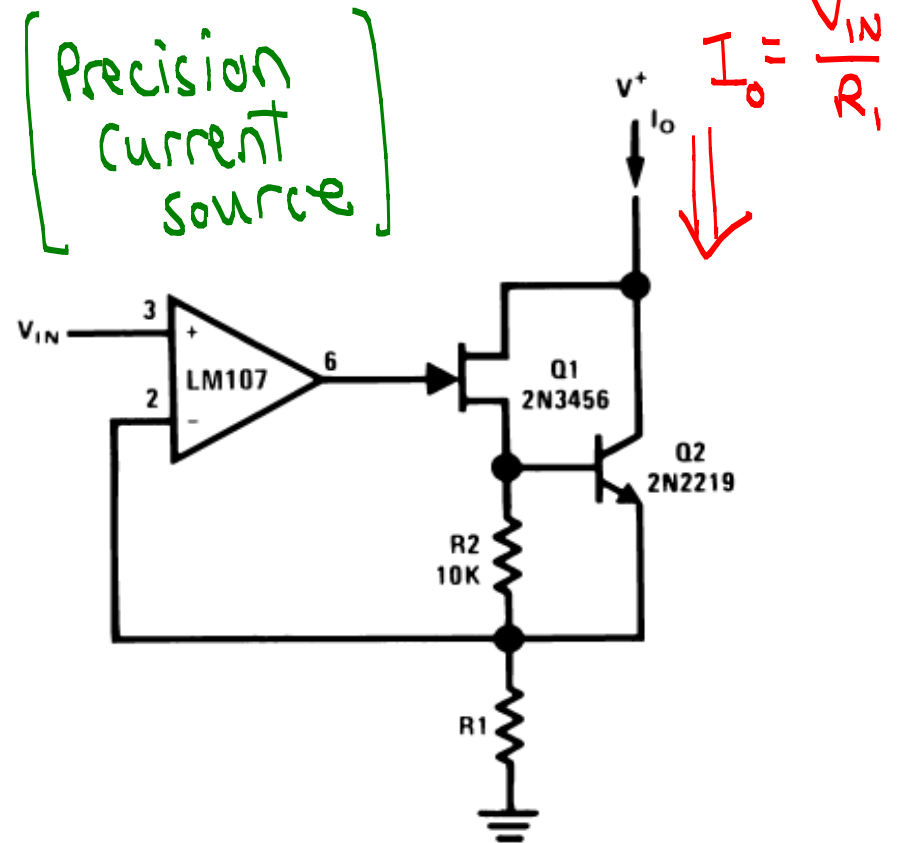

Precision Current Source


$I_{OUT} = \frac{V_{OUT}}{R_1}$

3. Unidirectional Current Boosters

- Op amps can be used to make a huge variety of circuits. (see App notes)
- HOWEVER, most op amps are limited to ~25 mA output current.


Example: Voltage Buffer

(3.9)

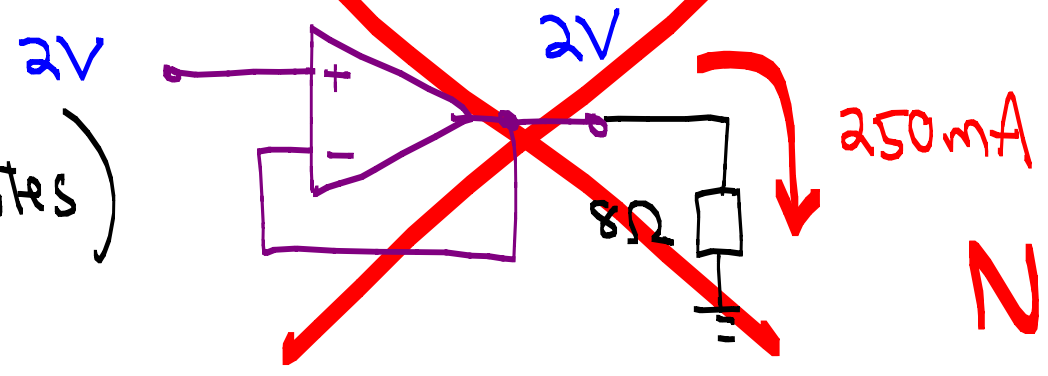

NO!
:(

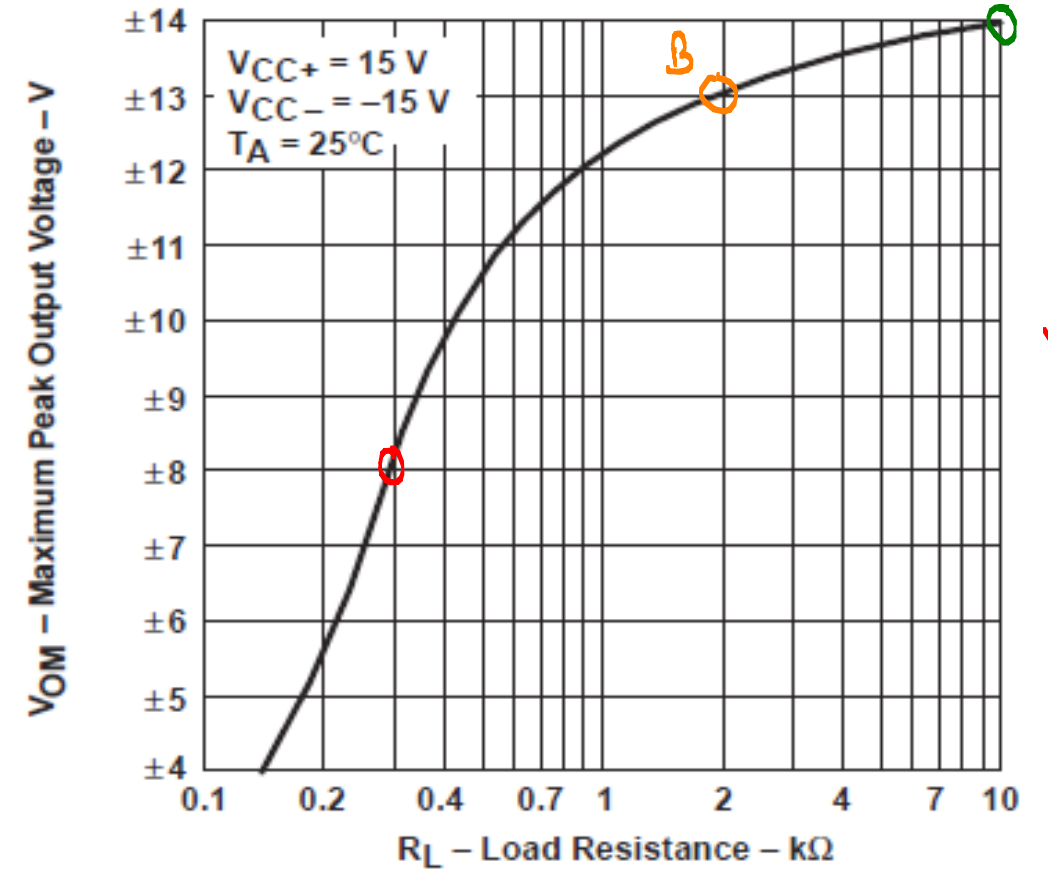MAXIMUM PEAK OUTPUT VOLTAGE VS LOAD RESISTANCE



Max V_{OUT}

I_{OUT}

A: ±14V

$$\pm \frac{14V}{10K} = \pm \underline{\underline{1.4mA}}$$

B: ±13V

$$\pm \frac{13V}{2K} = \pm \underline{\underline{6.5mA}}$$

C: ±8V


$$\pm \frac{8V}{.3K} = \pm \underline{\underline{26.7mA}}$$

LF356

V_S = ±15V

- Adding an external transistor (e.g. emitter follower) can significantly boost the load current.

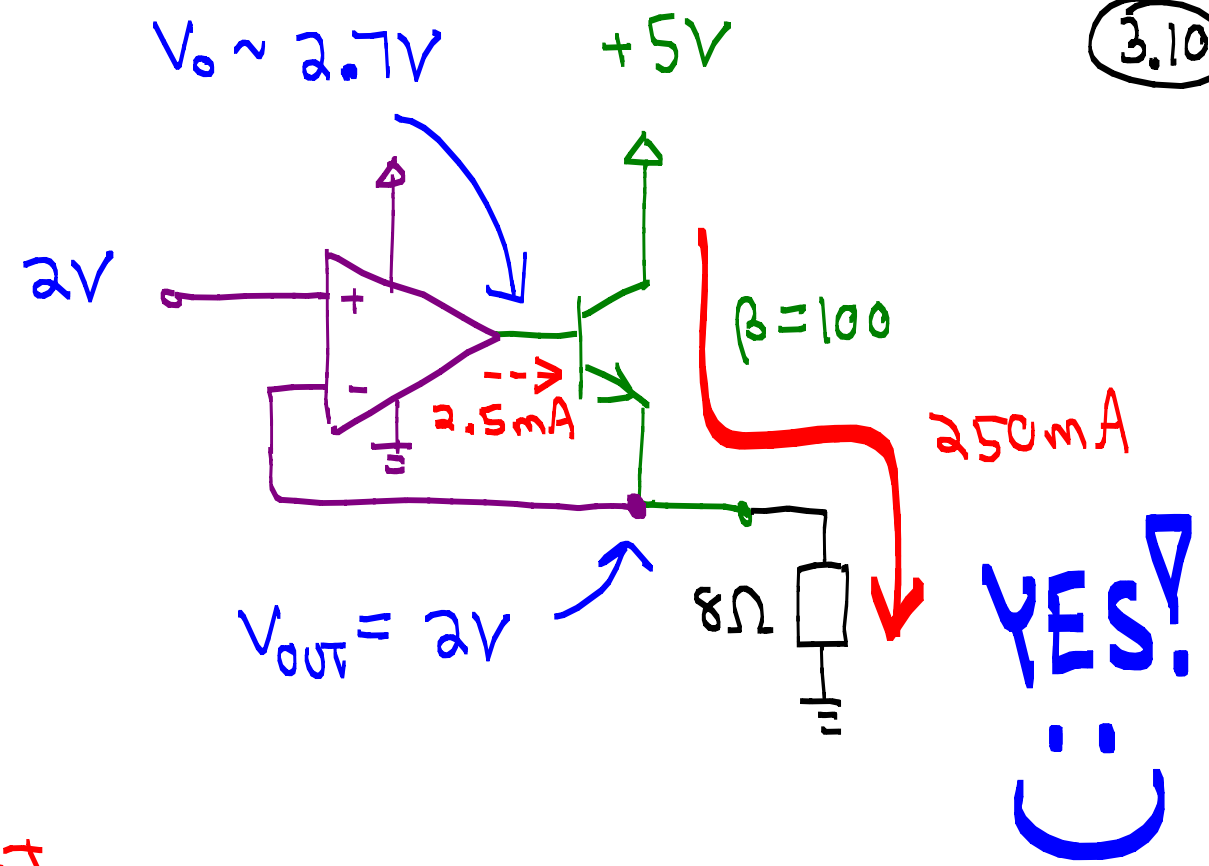NOTE: Most op amp outputs are limited to $\sim V_{supply} - 1V$ for tiny current



YES!
😊

★ Usually a good idea to include $\sim 2V$ "head room"

⇒ Max expected $V_o < V_{supply} - 2V$