

Lecture 4 : Push-Pull Output Stage

(Quiz)

0. Review

1. Push-Pull Stage

2. Push-Pull Design

• Quiz today

• PreLab 2 due at lab session

• HW2 due Fri (Sep 27)

• Lab1 report due next Wed (Oct 01)

→ see course website for template

Textbook reading: 16-2 The 741 Op Amp

16-3 The Inverting Amplifier

16-5 Two Op Amp applications

18-7 Current Boosters

0. Review


Op Amp

Golden Rules:


"virtual short"

- ① $V_{IN+} = V_{IN-}$
- ② Zero input current


Summing Amplifier

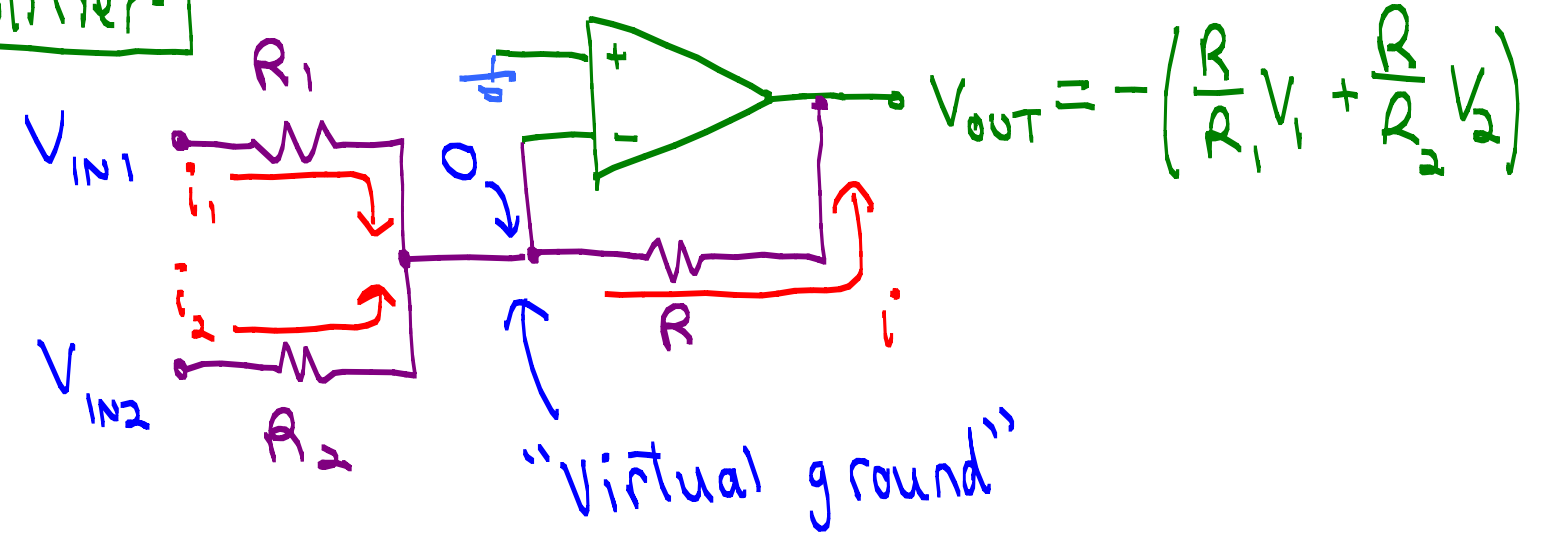

Transimpedance Amplifier


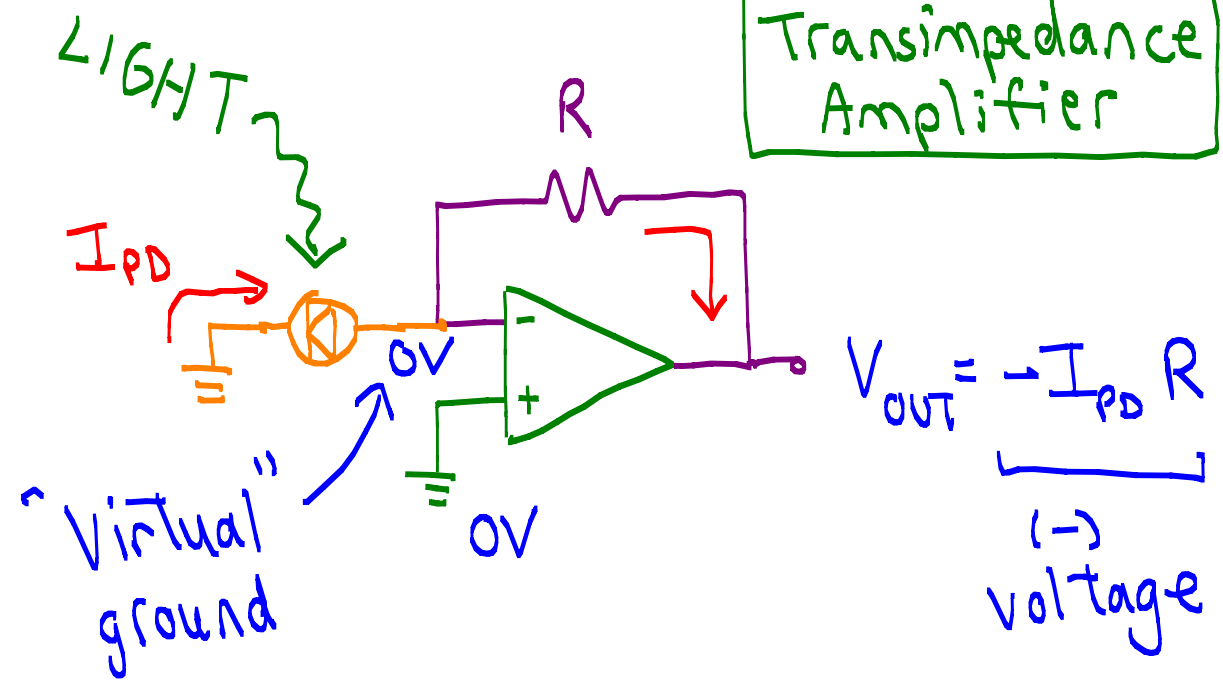


Op Amp Current Booster


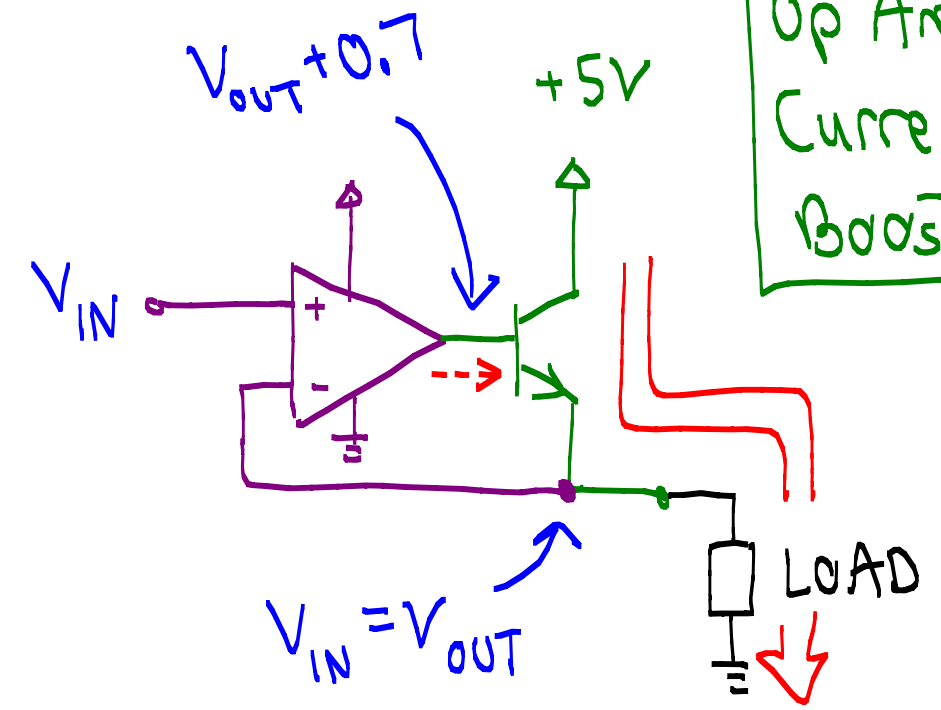


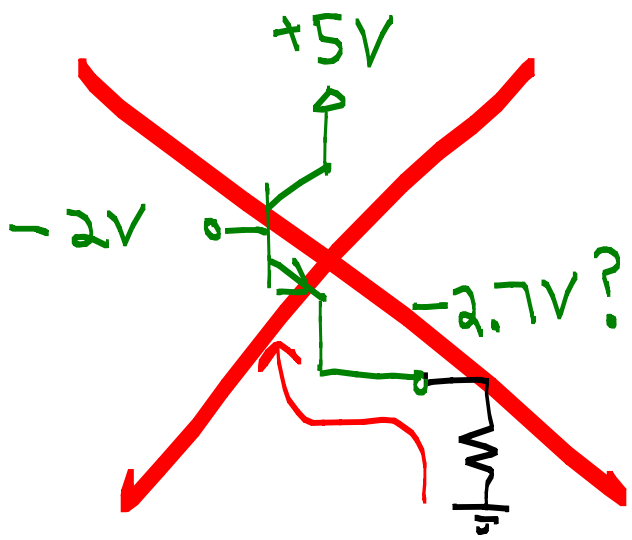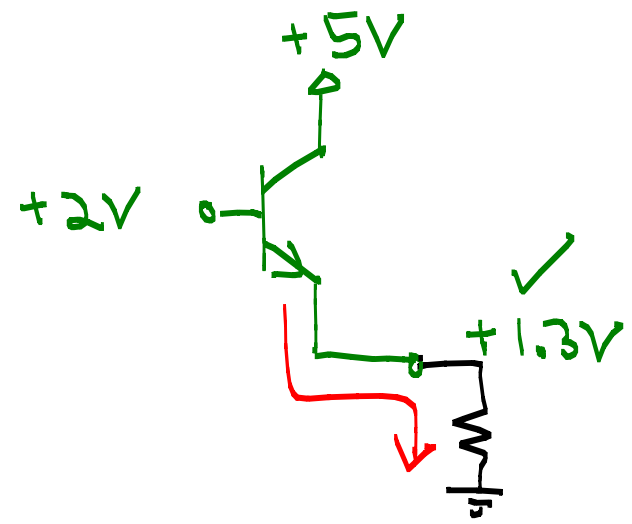1. Push-Pull Stages



• An npn follower can only "push" current



• A pnp follower can only "pull" current

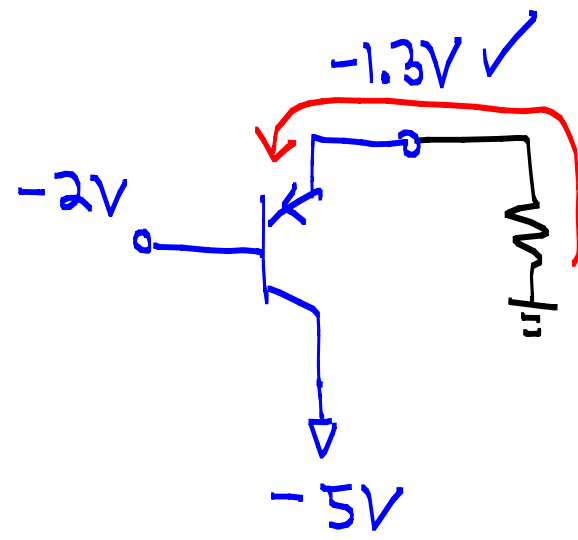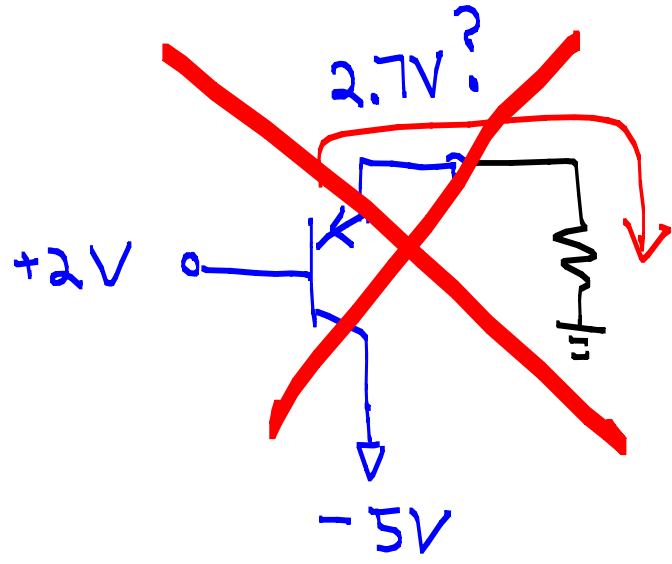

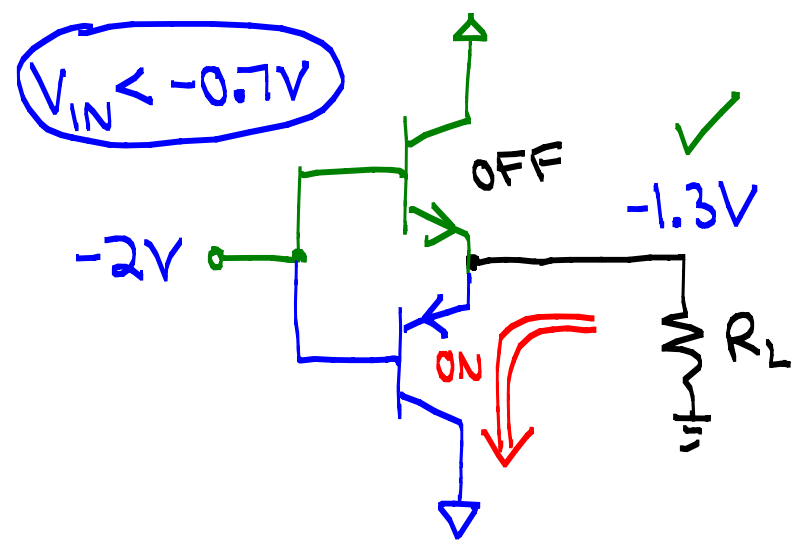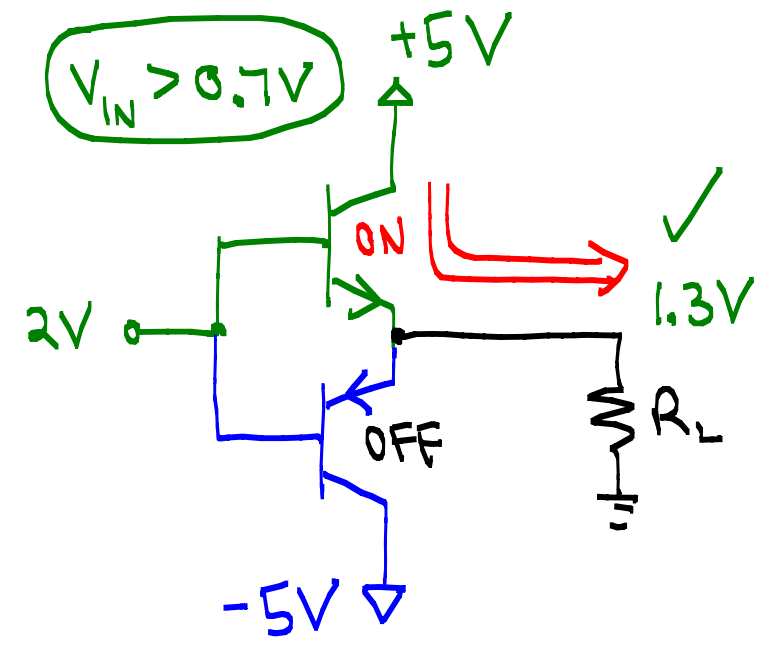• Combine npn + pnp to "push-pull" current! (4.1)





★ Called a Class B "push-pull" or "totem-pole" stage


Is there a catch? Unfortunately, YES. ☹️

⇒ Crossover Distortion!

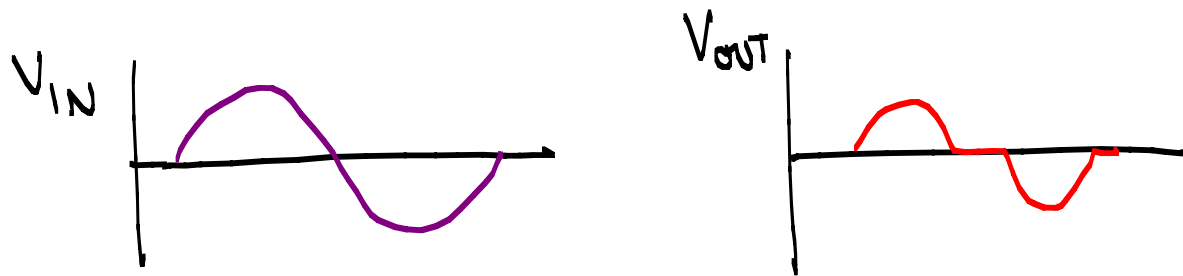• $V_{out} = 0$ when $-0.7V < V_{in} < +0.7V$ } output has "Dead zone"
(Both Q_1 and Q_2 are OFF)



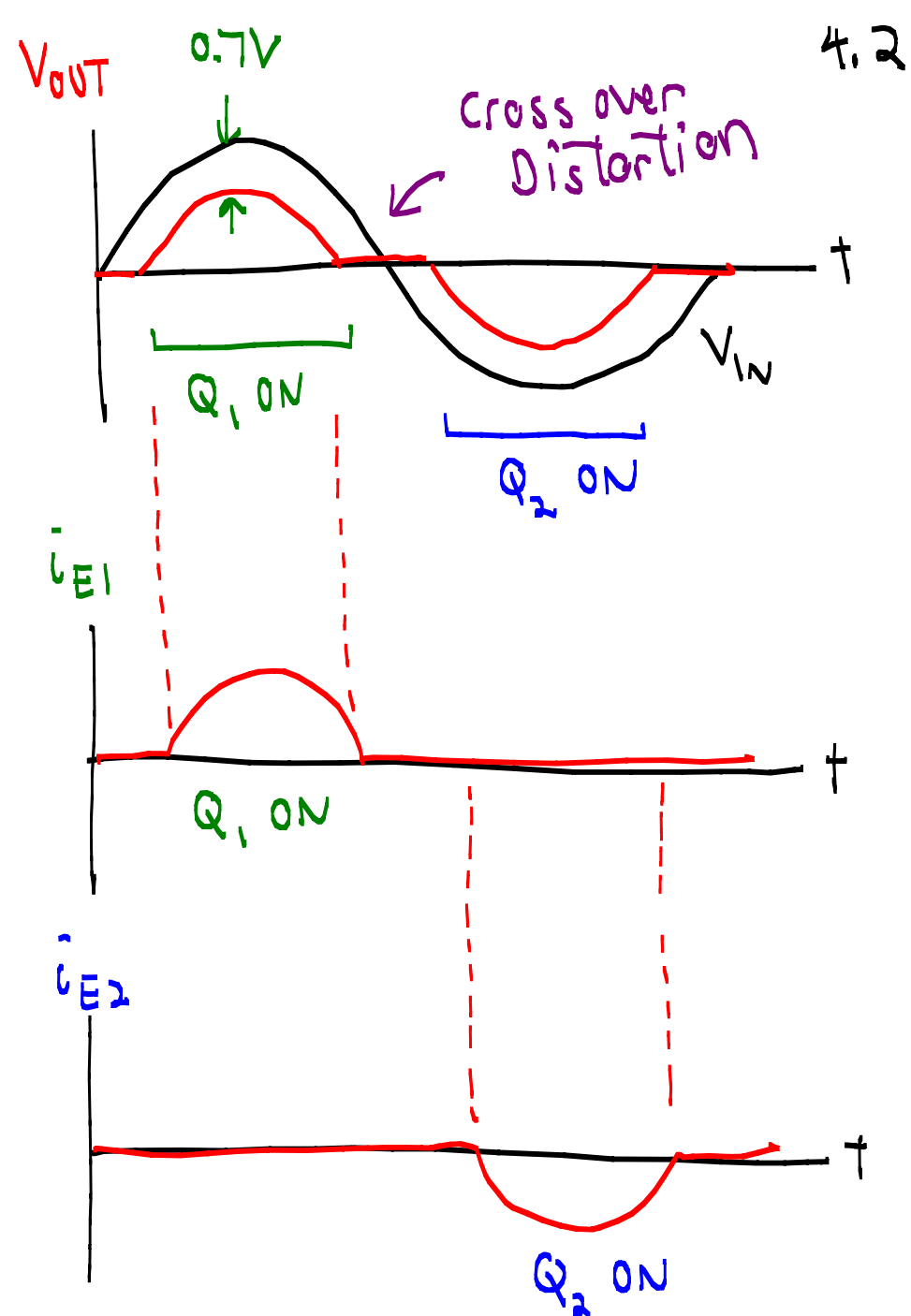⇒ Obviously,  is not a desirable output waveform.



One way to reduce crossover distortion is to use the push-pull with an op amp.


Example

$\beta = 100$ (4.3)

→ op amp makes sure that $V_{LOAD} = V_{IN}$

when $V_{IN} > 0$: $V_o = V_{LOAD} + 0.7$

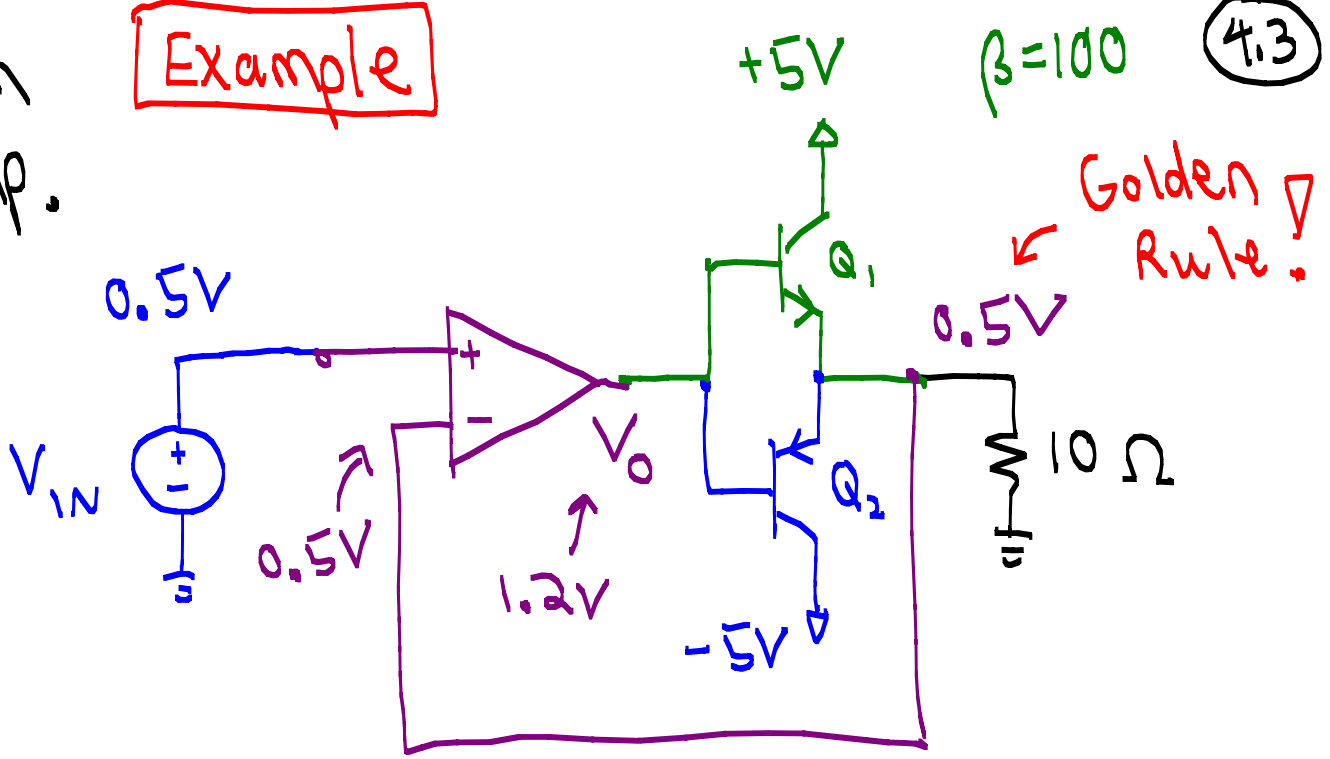
when $V_{IN} < 0$: $V_o = V_{LOAD} - 0.7$



★ NOTE: Even with an op amp, crossover distortion gets worse at high freq

why? op amp output has large $\frac{dV}{dt}$ in crossover region

↳ limited by op amp's slew rate (V/us)

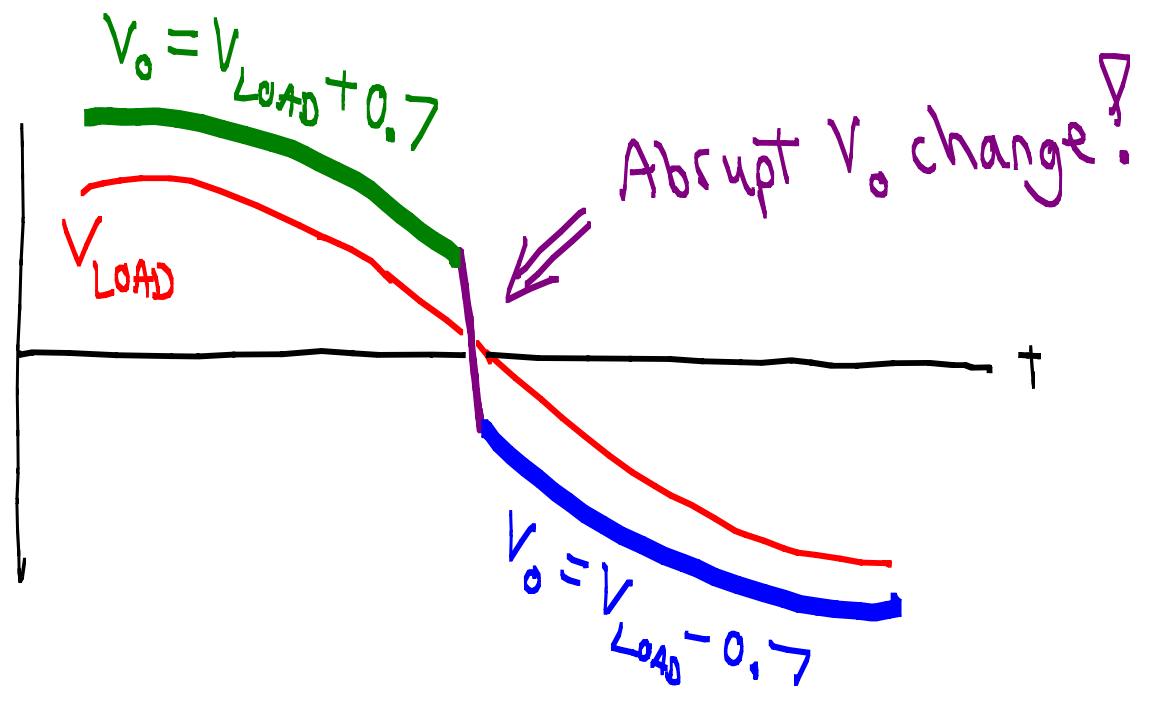

2. Push-Pull Design

$V_{cc} = 9, 12, 15, \text{ or } 18V$

Example: Motor driver

- $\pm 9V$ max
- $2W$ max
- Gain = $20 \pm 5\%$


We'll use "worst case" parameters for this example.

① Start with max desired output

Max $V_{out} = \pm 9V$

Max $I_{out} = ?$ $P = IV$

$I = \frac{2W}{\pm 9V} = \pm 0.222A$

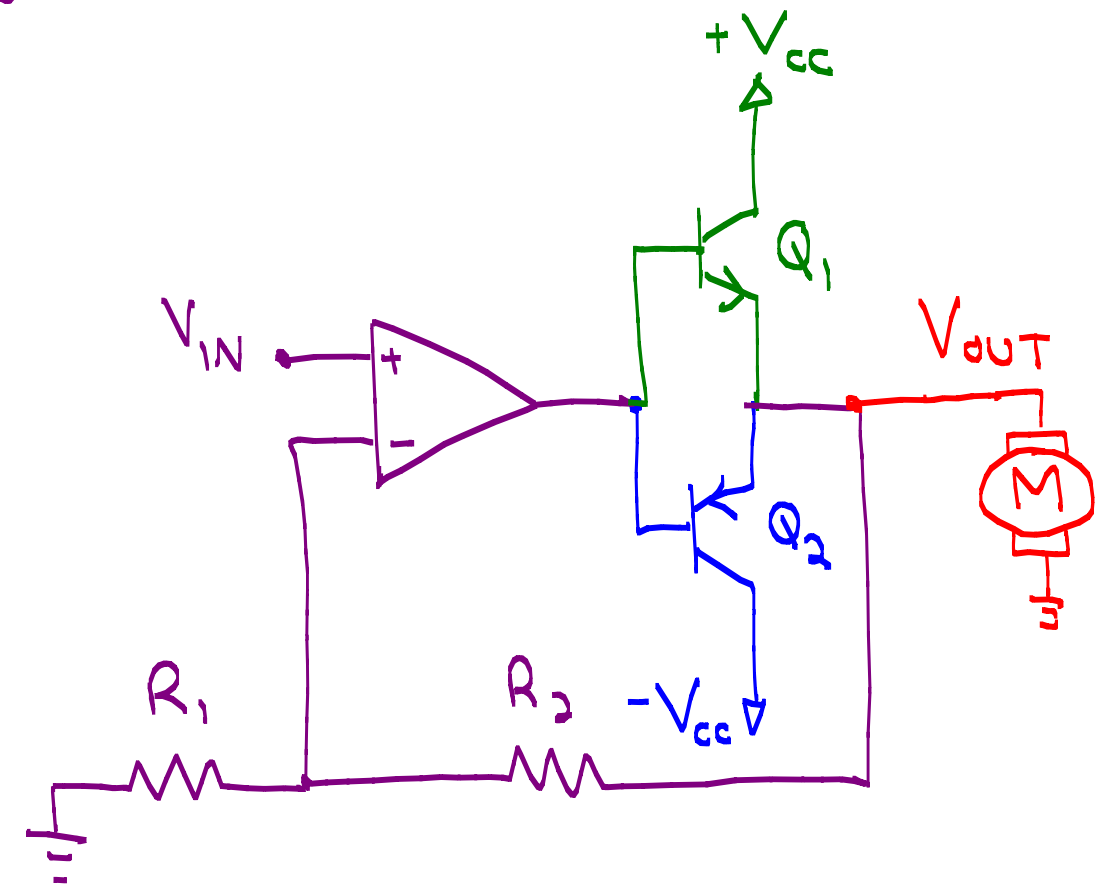


② Choose V_{CC}

Make sure Q_1 never saturates!

"Head room" is a good idea

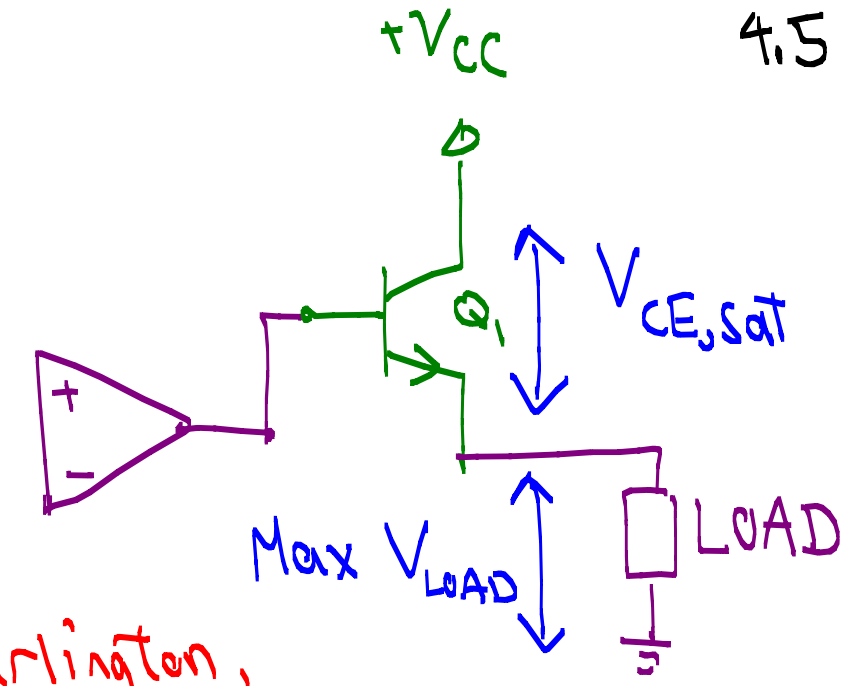★ We want $\underbrace{\min V_{CE}}_{V_{CC} - \max V_L} > V_{CE,sat} + \underbrace{2V}$



If Q_1 Darlington, this would be 0.7V

$$\Rightarrow V_{CC} > \max V_L + V_{CE,sat} + 2V$$

• First do "quick" analysis to estimate V_{CC} :

$$V_{CC} > 9 + 0 + 2$$

$$\underline{V_{CC} > 11V} \Rightarrow \text{Try } \boxed{V_{CC} = 12V}$$

May need to revise later.

③ Choose Transistor

Demanded by circuit:


Max $I_c \approx 222 \text{ mA}$

$\times 2$

Ideally have $> 340 \text{ mA}$ rating

Max $V_{CE} = 12 - (-9) = 21 \text{ V}$

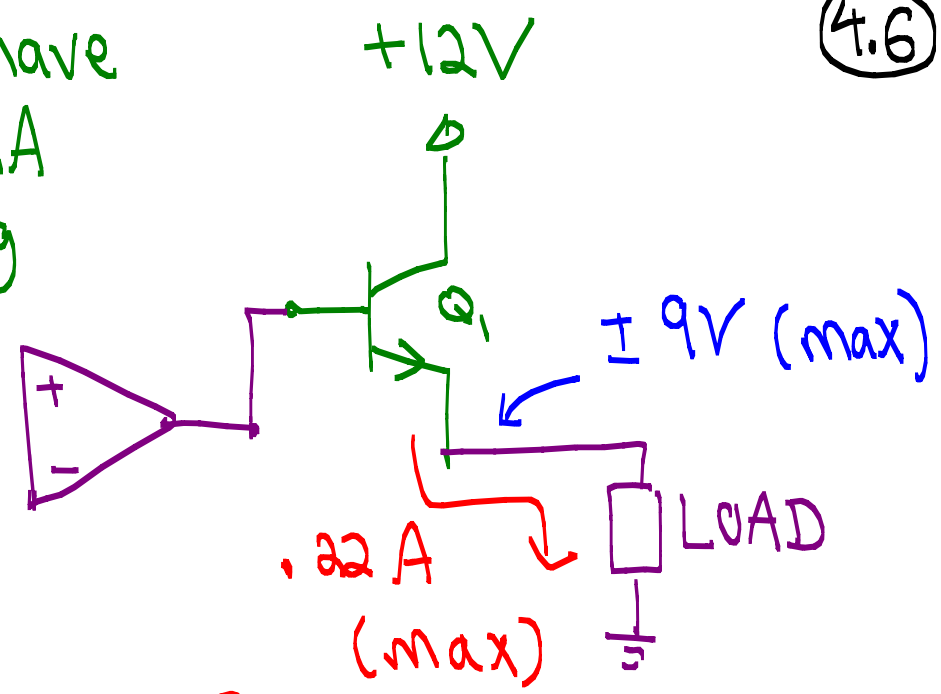When Q_1 off \uparrow $> 42 \text{ V}$ rating
 Q_2 on



Estimate

max $P = \frac{0.22}{101} (0.7) + 0.99 (0.22) (12 - 9) = 0.655 \text{ W} \xrightarrow{\times 2} 1.31 \text{ W}$ rating or higher

(no HS)

(w/HS)



<u>Q_1</u>	<u>Max I_c</u>	<u>Max V_{CE}</u>	<u>P_{Rating}</u>	<u>P_{Rating}</u>
2N3904	200 mA X		0.625 W	
2N4401	600 mA ✓	40 V ✓ (close enough)	0.625 W X	1.5 W ✓

Choose heat sink later

④ Max op amp output OK?

Data sheet uses $V_{CC} = 15V$

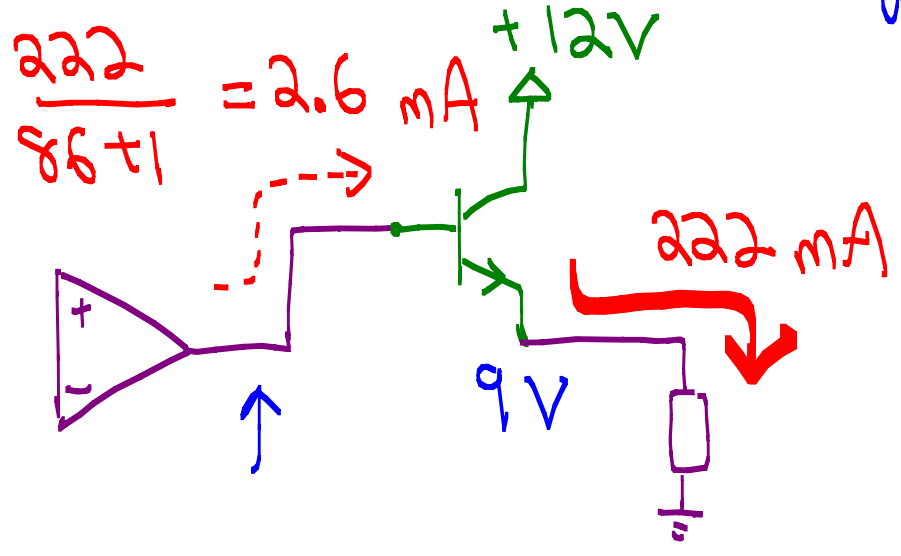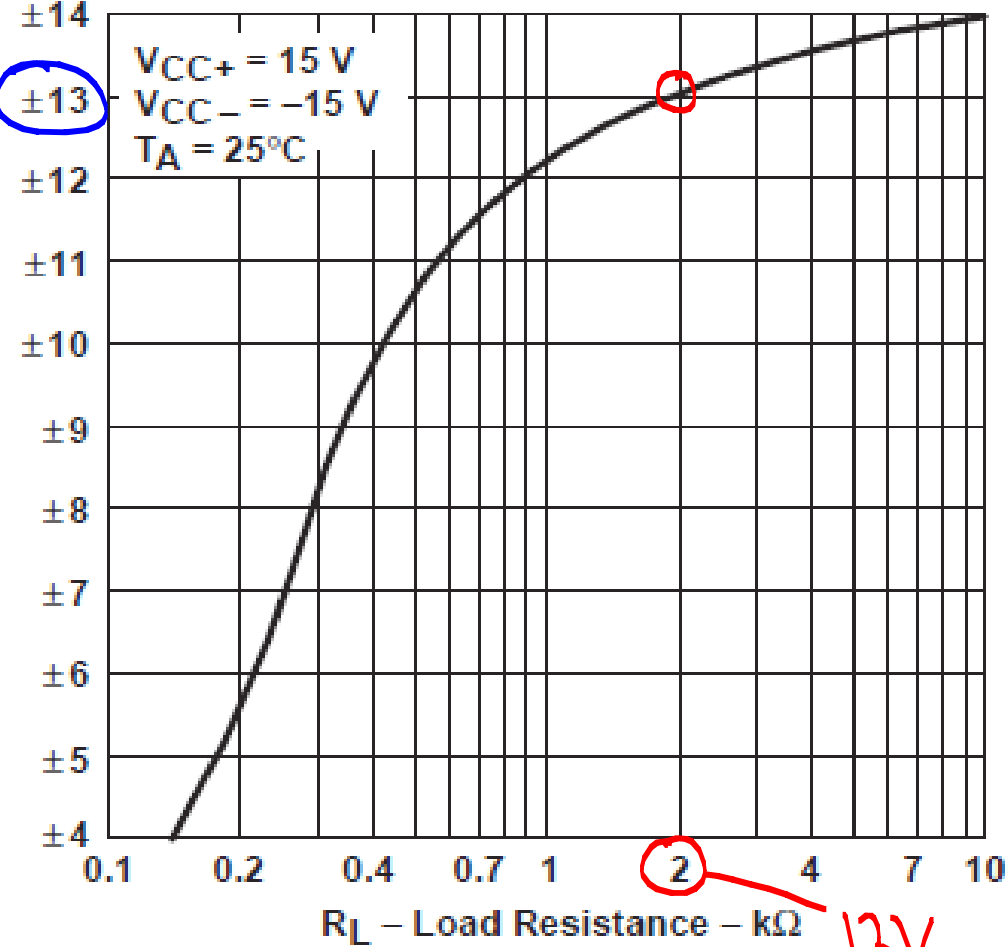MAXIMUM PEAK OUTPUT VOLTAGE VS LOAD RESISTANCE



$$\frac{222}{86+1} = 2.6 \text{ mA}$$

See appendix:
 Min $\beta \sim 86$
 ($I_c = 222 \text{ mA}$)

$$V_{BE} \approx 1V$$

$$(I_c = 222 \text{ mA})$$

$$\text{Max } V_o = 9 + V_{BE} = \underline{\underline{10V}}$$

$$\text{Op amp headroom} = V_{CC} - \text{max } V_o = 12 - 10 = \boxed{2V}$$

Q: Can op amp output 2.6 mA with 2V headroom?

Same headroom with $V_{CC} = 15V$

$$\text{is } \text{max } V_o = 15 - 2 = \underline{\underline{13V}} \text{ @ } 6.5 \text{ mA} > 2.6 \text{ mA}$$

YES!

$$\frac{13V}{2K} = \underline{\underline{6.5mA}}$$

⑤ Compute heat sink:

★ Find Θ_{SA} needed for $T_J < 85^\circ C$:

$$25^\circ C + (0.66 W)(83.3^\circ C/W + 0.5^\circ C/W + \Theta_{SA}) < 85^\circ C$$

$\Rightarrow \Theta_{SA} < \underline{\underline{7.1^\circ C/W}}$ ← Pretty low value
(Probably need forced air)

• Op amp feedback resistors?


$$G = 1 + \frac{R_2}{R_1} = 1 + \frac{R_2}{10K} = 20$$

Typically, $1K < R_1 < 10K$



$R_2 = 190K$ Choose $R_2 = 200K$
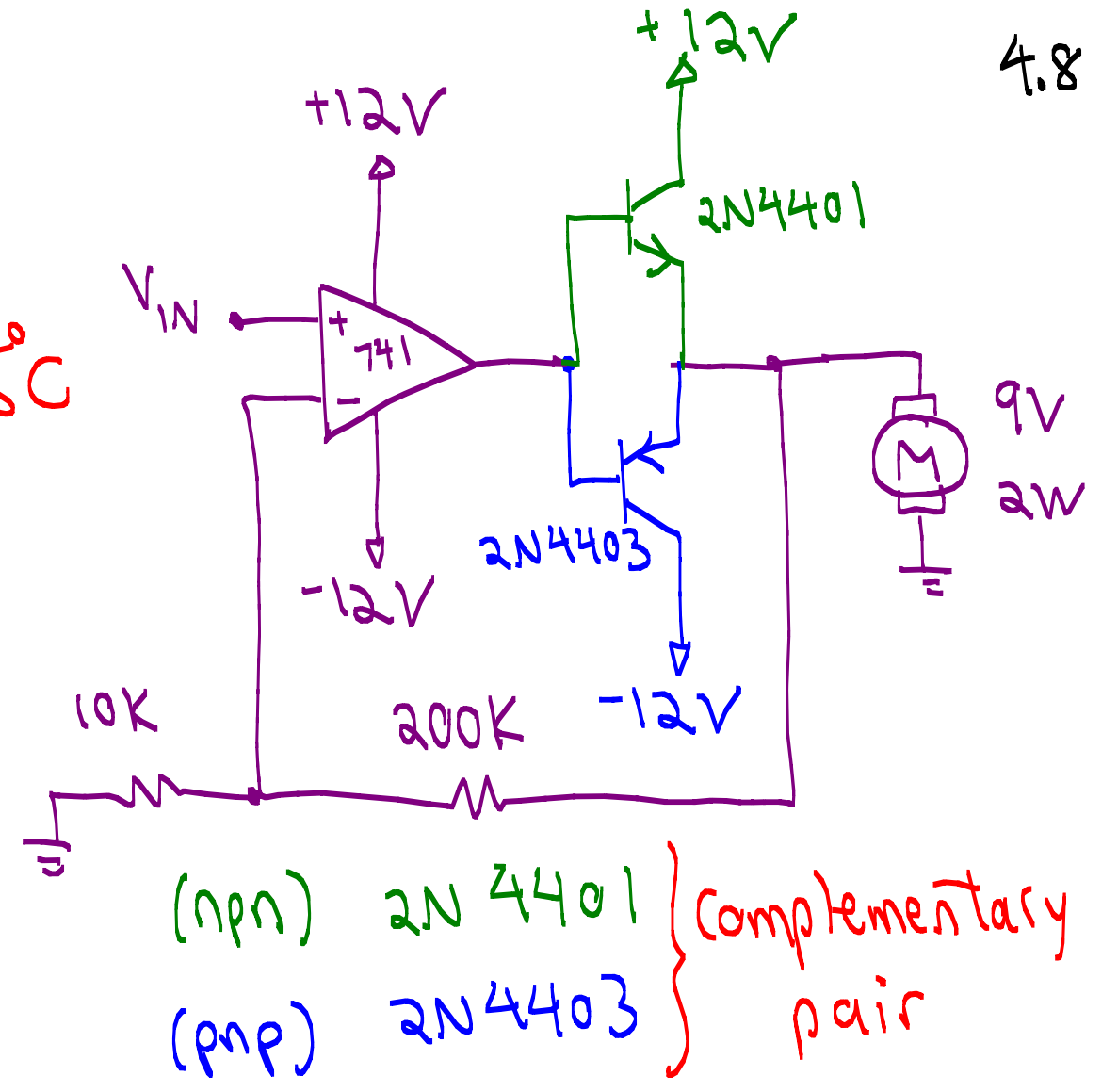
$$\text{Actual } G = 1 + \frac{200K}{10K} = 21 \leftarrow (+5\%) \checkmark$$




Appendix

2N4401 data sheet (Fairchild)

A.1

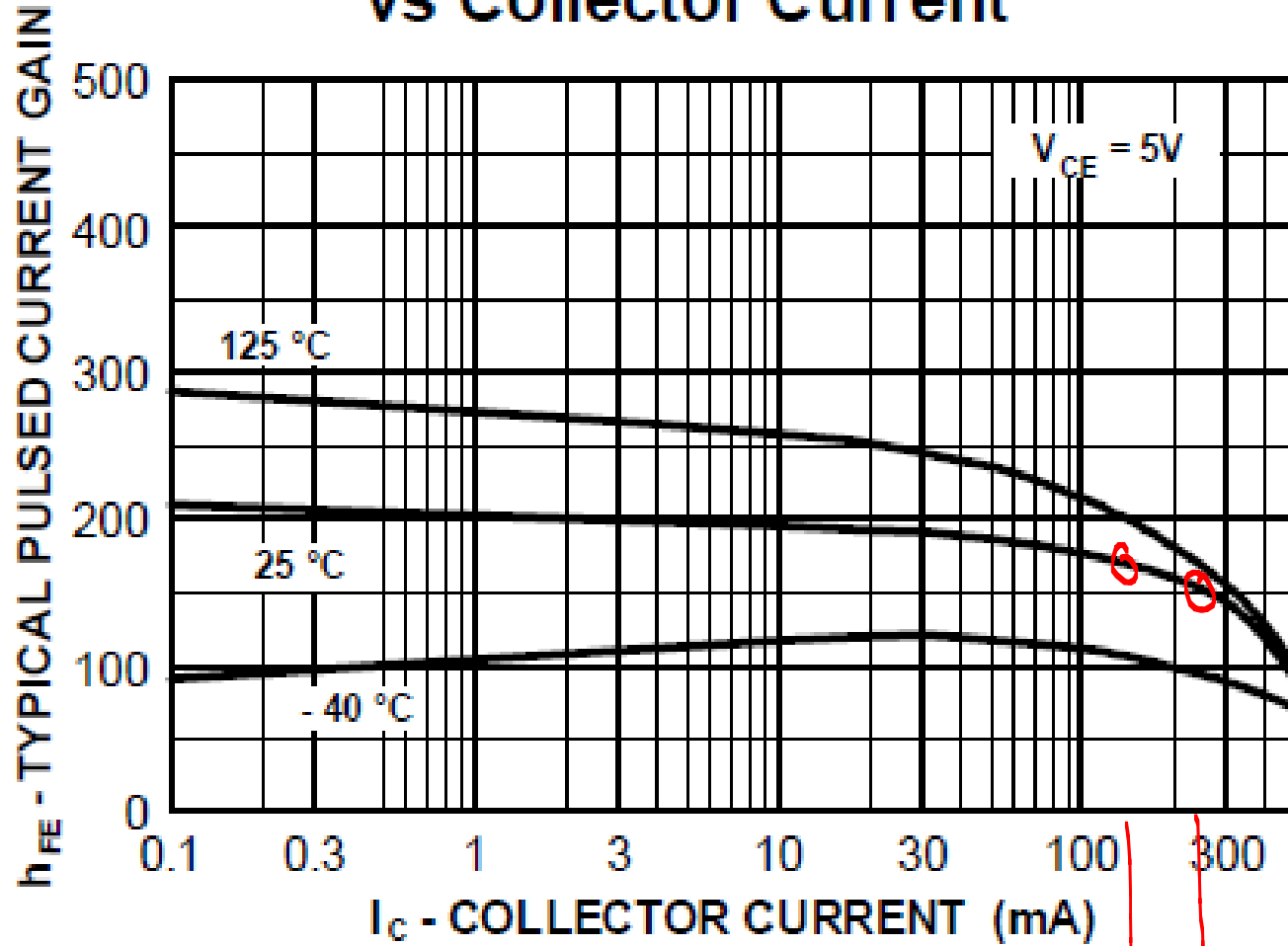Typical Pulsed Current Gain vs Collector Current



150mA

~222mA

150mA


222mA

$$\frac{\beta_{typ}}{\beta_{min}} \approx \frac{175}{100} \approx \frac{150}{?}$$

$$\Rightarrow \beta_{min} \approx 150 \times \frac{100}{175} = 86 @ 222mA$$

★ V_{BE} increases with I_c

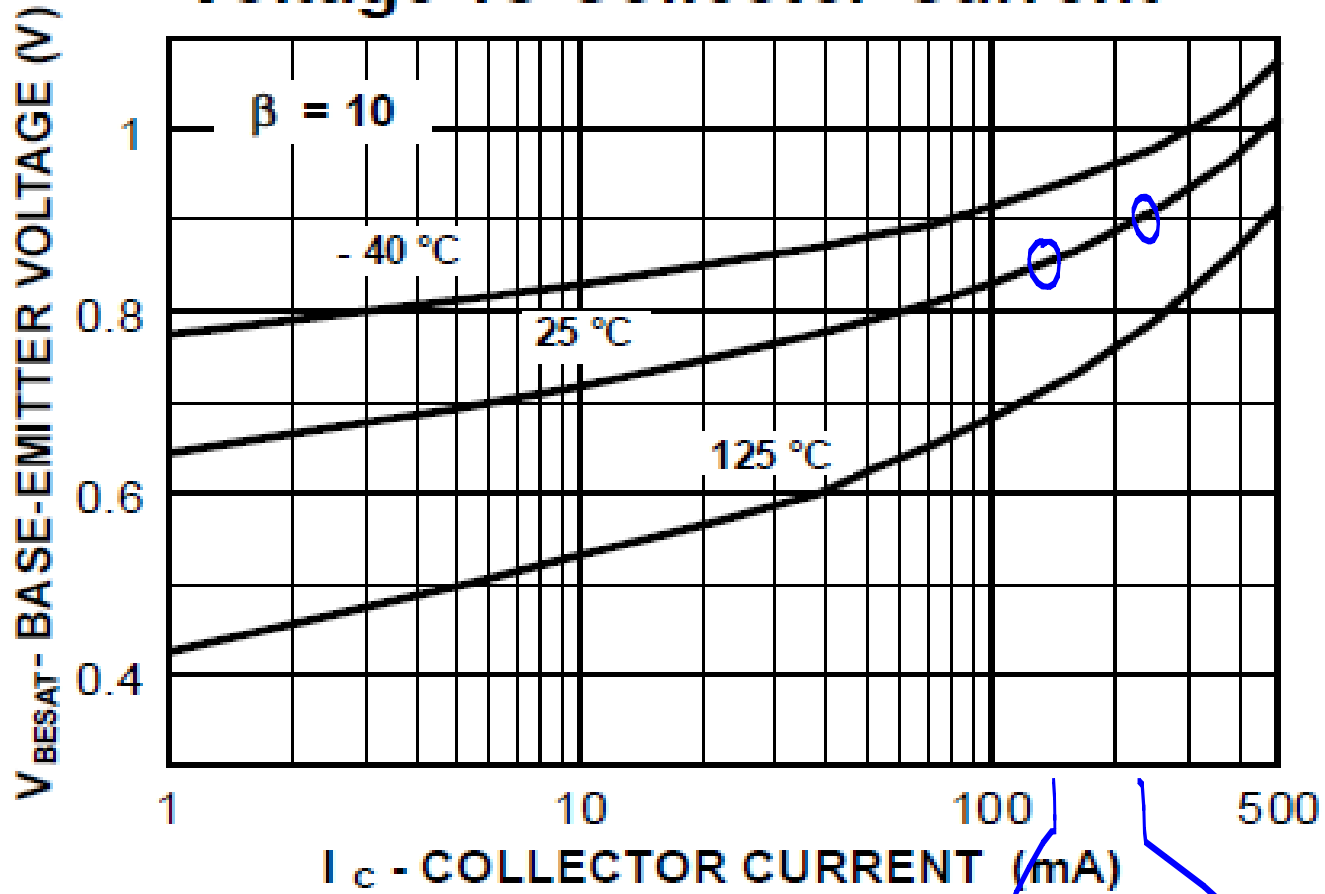Base-Emitter Saturation Voltage vs Collector Current



150mA 222mA

$$\frac{\text{Typical } V_{BE}}{\text{Max } V_{BE}} \approx \frac{0.85V}{0.95V} \approx \frac{0.9V}{?}$$

$$\Rightarrow \text{max } V_{BE} \approx 0.9 \times \frac{0.95}{0.85}$$

$$\approx 1V @ 222mA$$