

Lecture 6 : Op Amp Output Error

(Quiz)

0. Review
1. Input Bias Current
2. Input Offset Current
3. Input Offset Voltage

Textbook reading:

15-4 : Input characteristics of an op amp

- Today { Quiz
Lab 1 report due
- PreLab 3 due at lab session
↳ Choose Design Project topic, teammates, preliminary design
- HW3 due next Fri (Oct 11) in box outside my office.
→ No class Oct 8 + 10


0. Review

• Class AB Output Stage

→ Push-pull current booster

* Biasing diodes make Q_1 and Q_2 slightly on
⇒ Greatly reduces crossover distortion!
😊

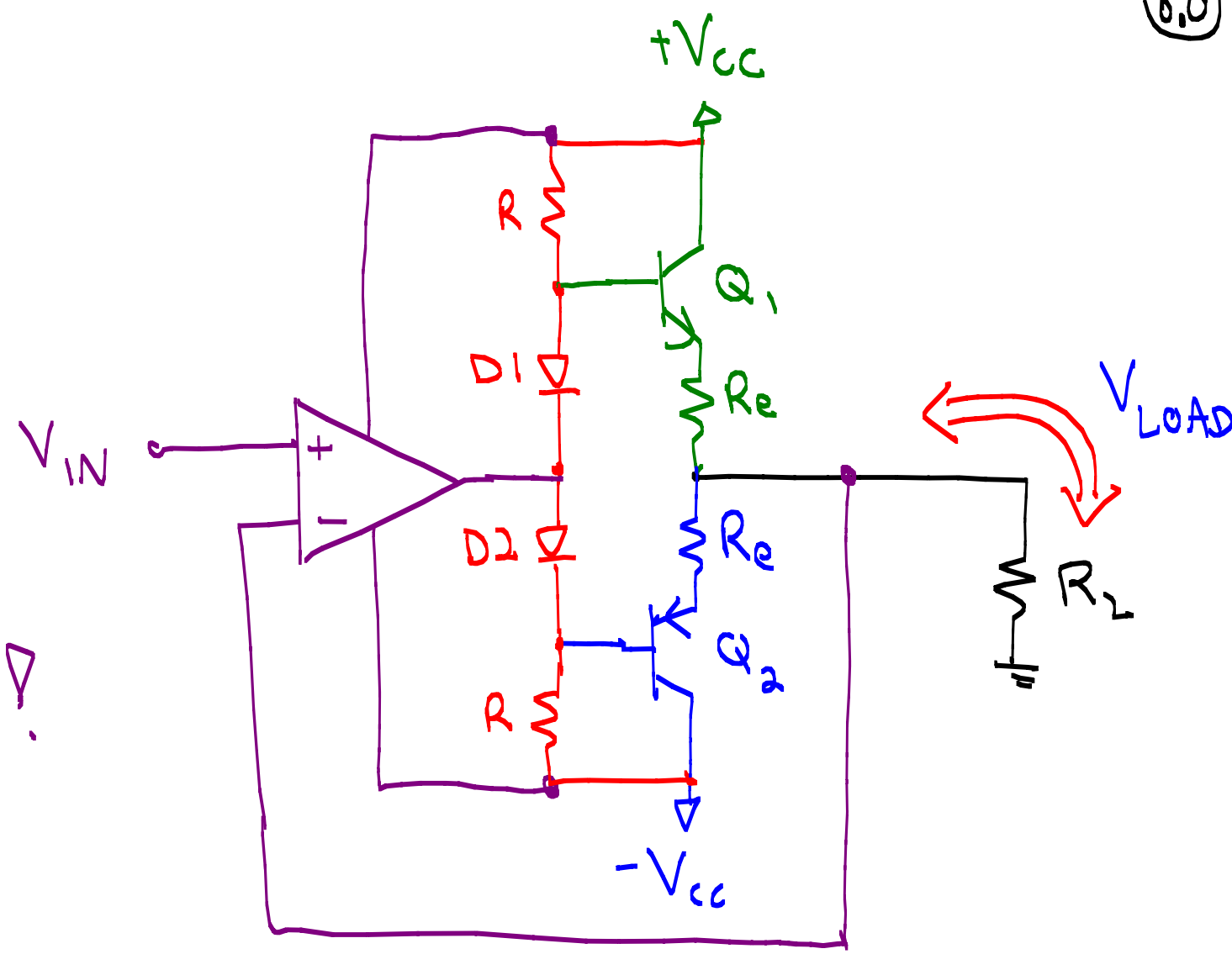* R must be low enough to provide sufficient current to diodes AND transistor bases




1. Input Bias Current


• Real op amps do NOT produce zero output when the input is zero.

Q: What causes ΔV_{IN} ?


① Input bias current $I_{IN(BIAS)}$

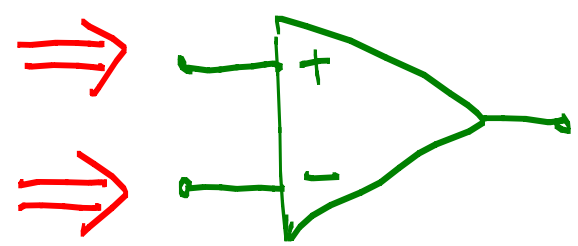


Example

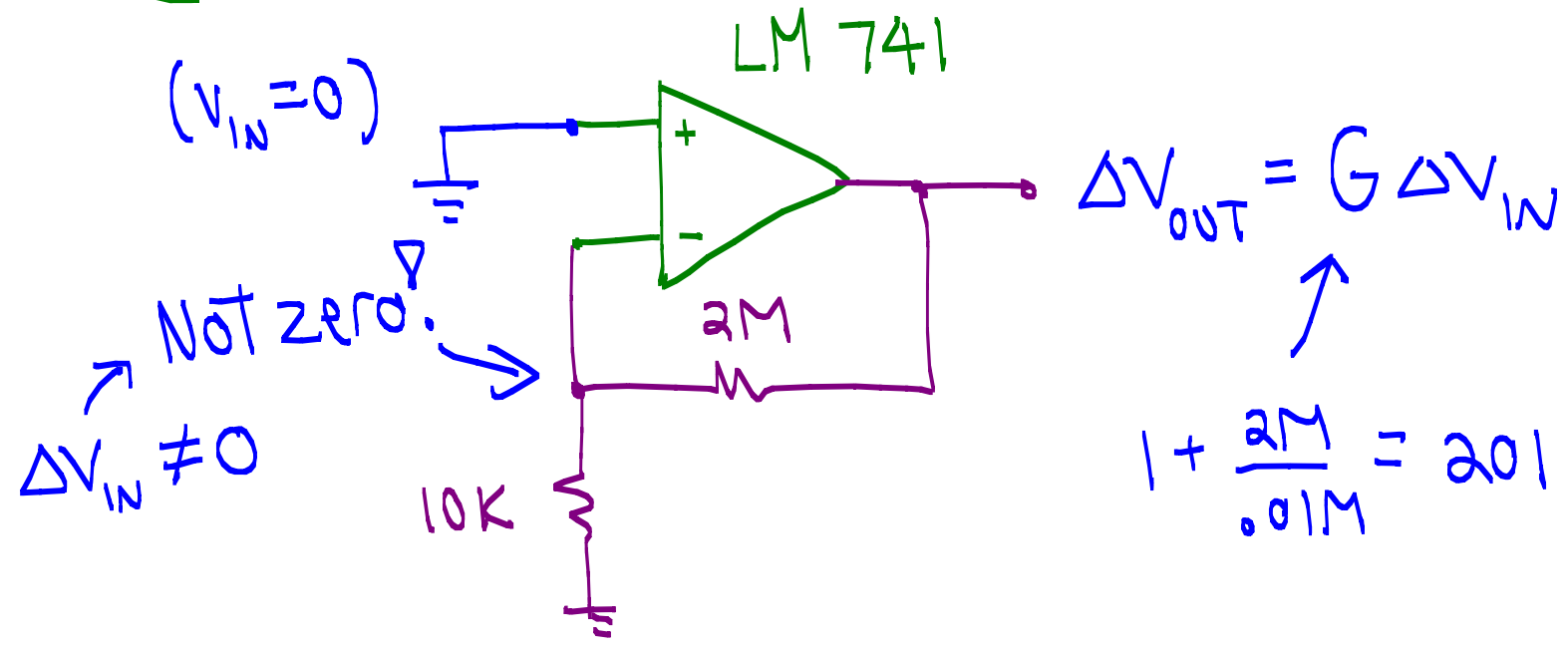

② Input offset current $I_{IN(OS)}$

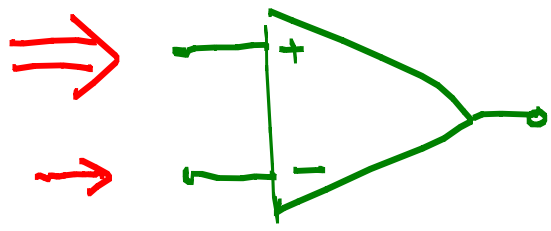




③ Input offset voltage $V_{IN(OS)}$

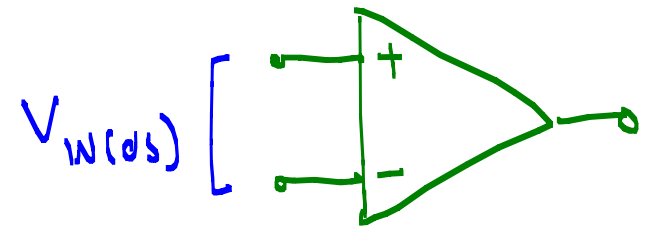

● 741
Op Amp

Schematic Diagram

(over 20 transistors!)

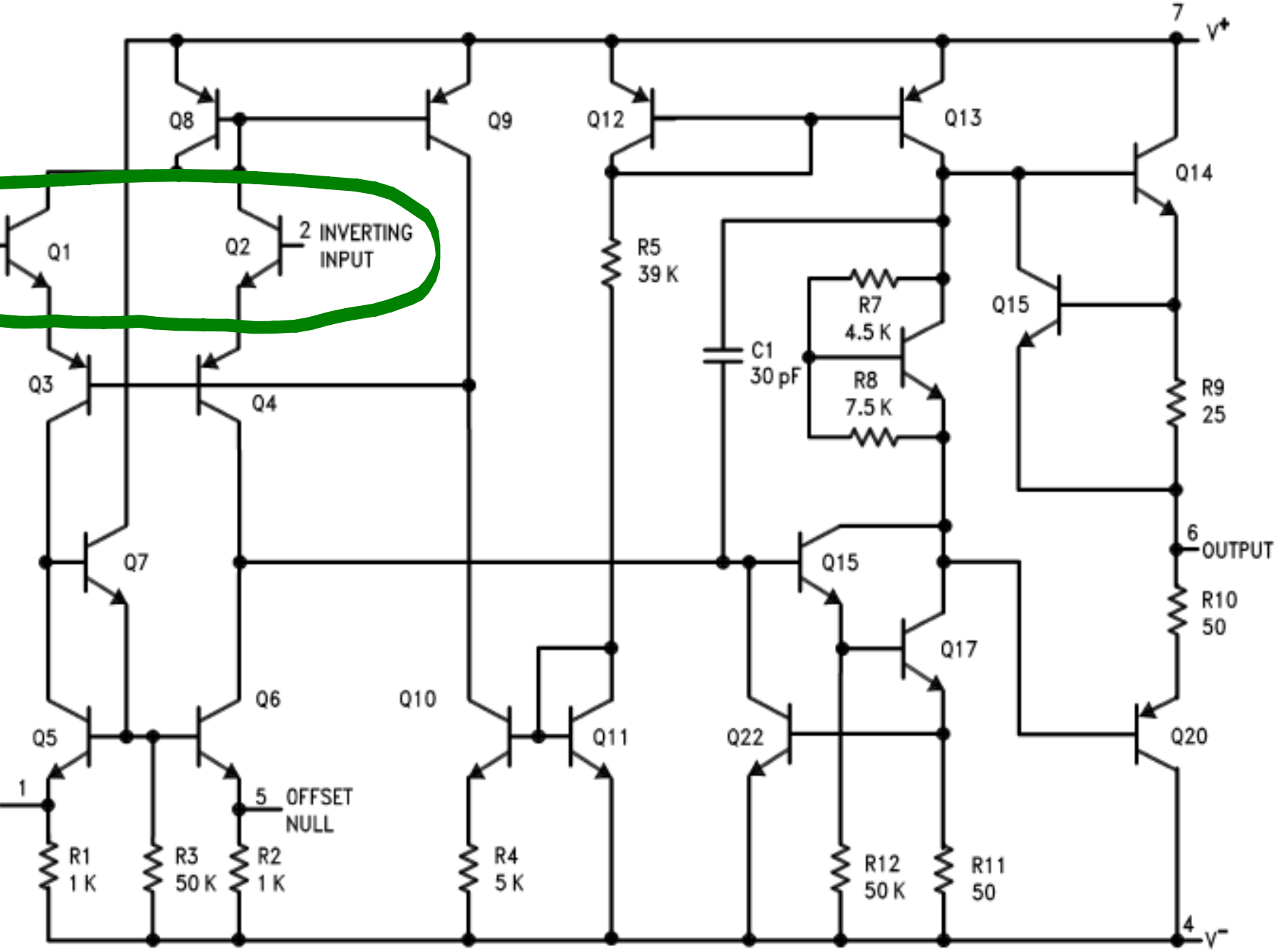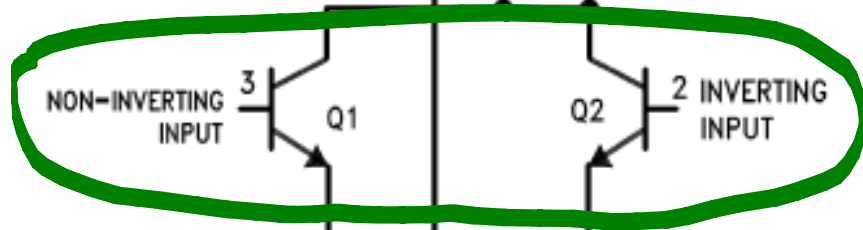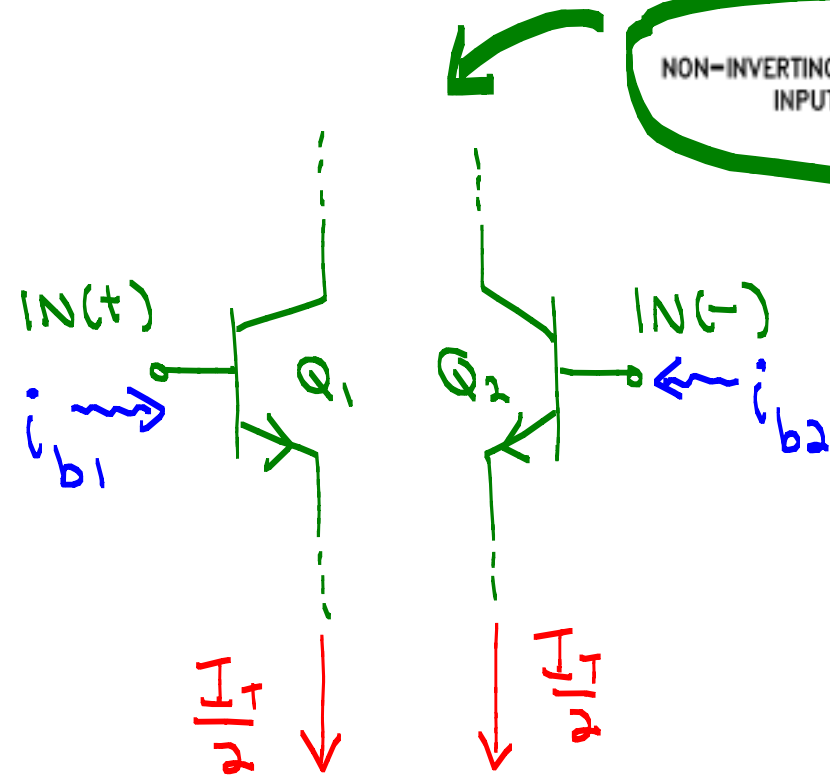


★ Bias current is the quiescent base current of Q_1 and Q_2 !

• Effect of input bias current $I_{IN(BIAS)}$

$$\Delta V_{IN} = I_{IN(BIAS)} \times [R_{TH(-)} - R_{TH(+)}]$$

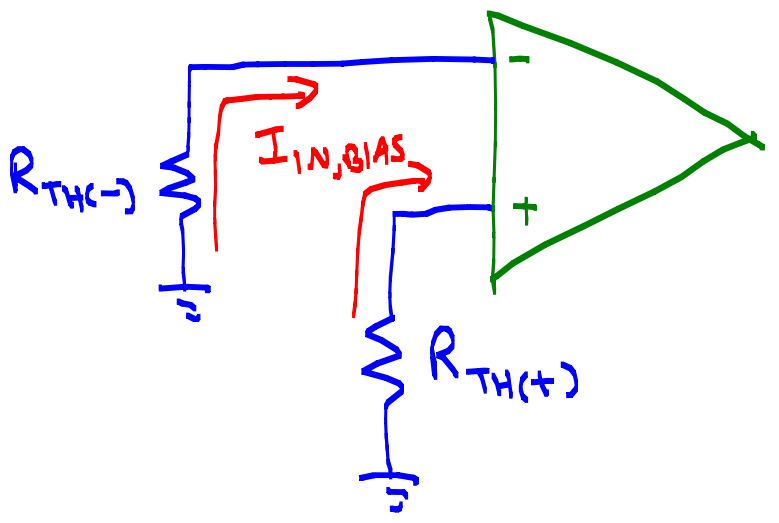Difference in
Thevenin resistance
seen by (-) and (+) inputs




Example LM741: $I_{IN(BIAS)} = 80 \text{ nA (TYP)}$ ($V_{IN} = 0$)

$$R_{TH(-)} = 10 \text{ K} \parallel 2 \text{ M} = 9.95 \text{ K}$$


$$R_{TH(+)} = 0$$
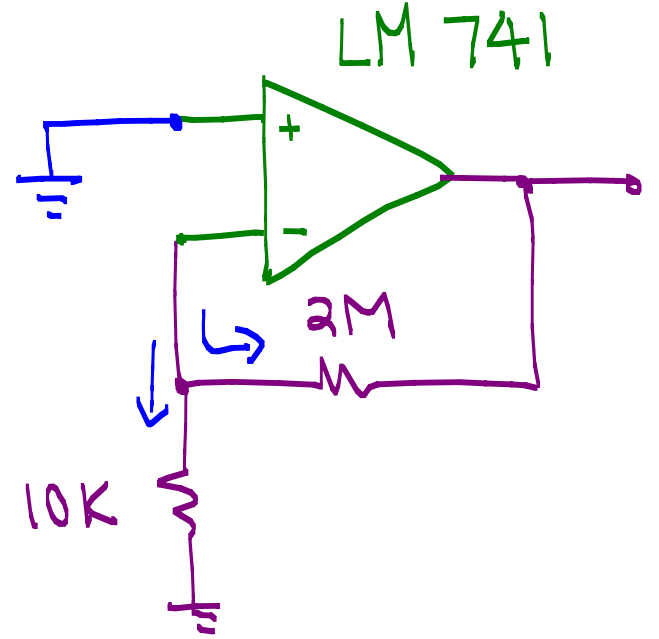
$$\Rightarrow \Delta V_{IN} = (80 \times 10^{-9}) (9.95 \times 10^3 - 0) = \underline{\underline{0.8 \text{ mV}}}$$




Q: How to minimize error due to $I_{IN(BIAS)}$?

① Try to make $R_{TH(+)} = R_{TH(-)}$!

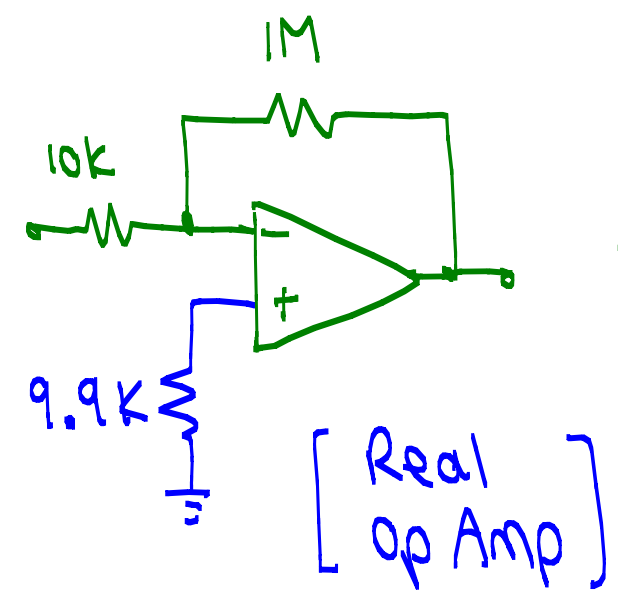


VS.

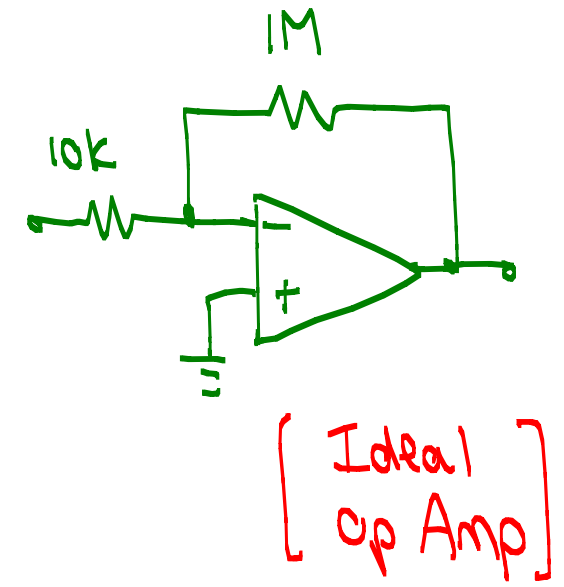

② use a JFET-input op amp

Recall that Field Effect Transistors (FETs) have negligible gate current...


Ex: LF356, LF411, TL081

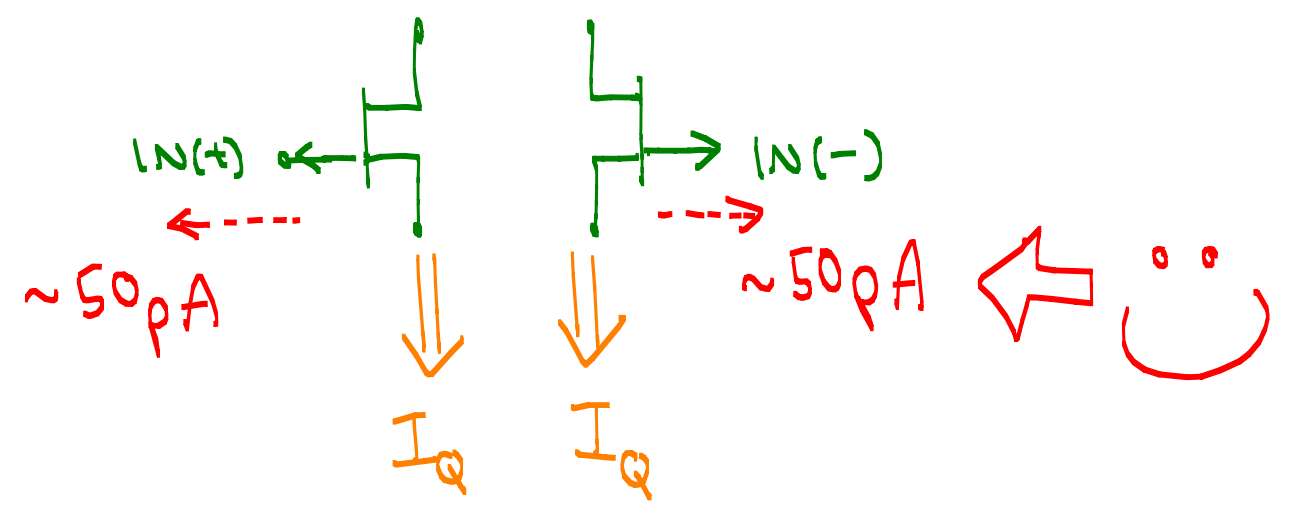

Example Transimpedance Amplifier

Ideal

$(i_{IN} = 0)$

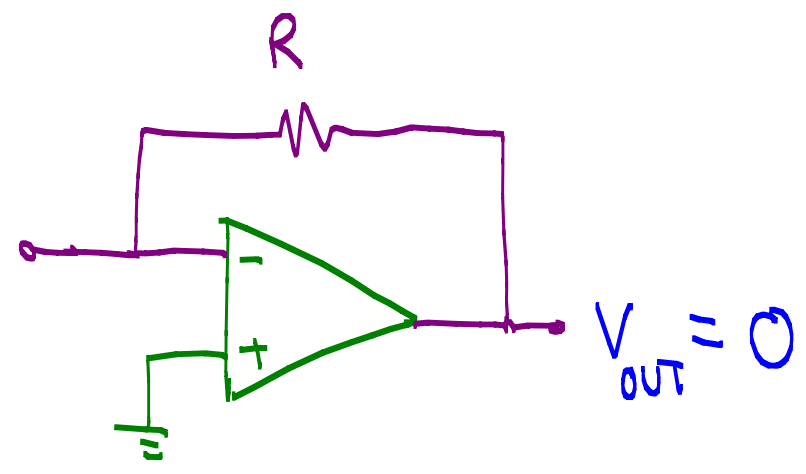


741C: $I_{BIAS} = 80 \text{ nA (typ)}$

LF356: $I_{BIAS} = 30 \text{ pA (typ)}$

Actual

$(i_{IN} = 0)$

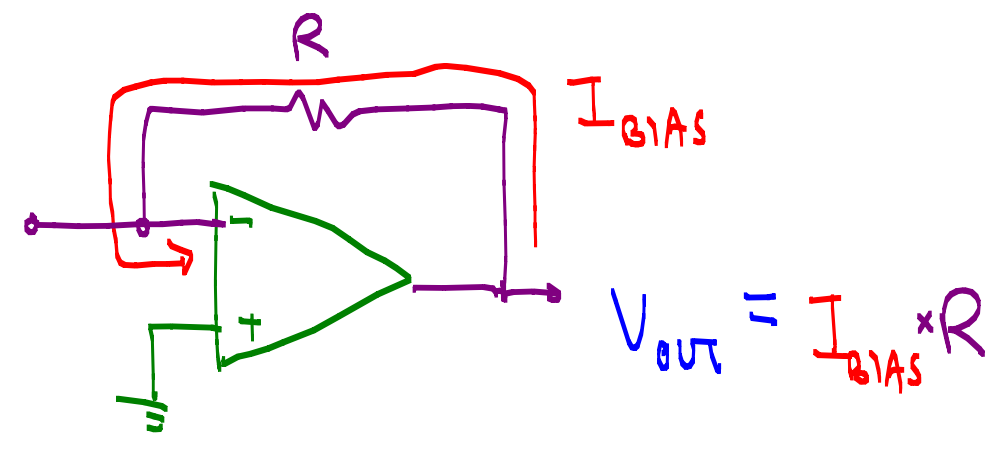

If $R = 1M$,

$V_{OUT} = 80 \text{ mV (741C)}$ ☹️


$= 30 \text{ } \mu\text{V (LF356)}$ ✓

NOTE: The LF356 is a really good general purpose op amp (MUCH better than 741...)

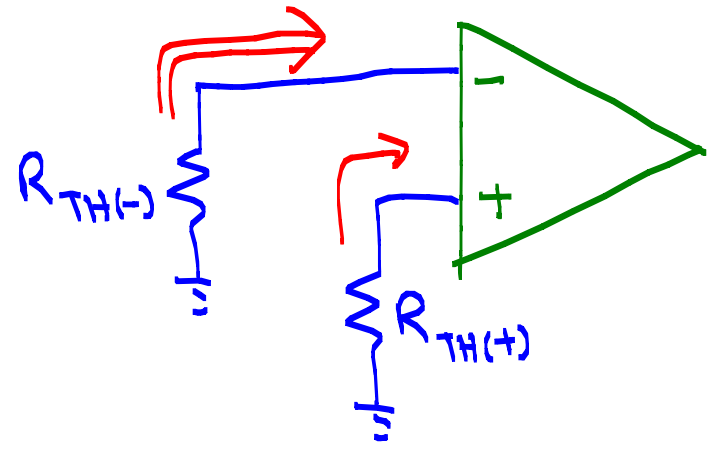2. Input offset current

$$\Delta V_{IN} = I_{IN(OS)} \times \left[\frac{R_{IN(-)} + R_{IN(+)}}{2} \right]$$


Average Thevenin resistance
seen by op amp inputs



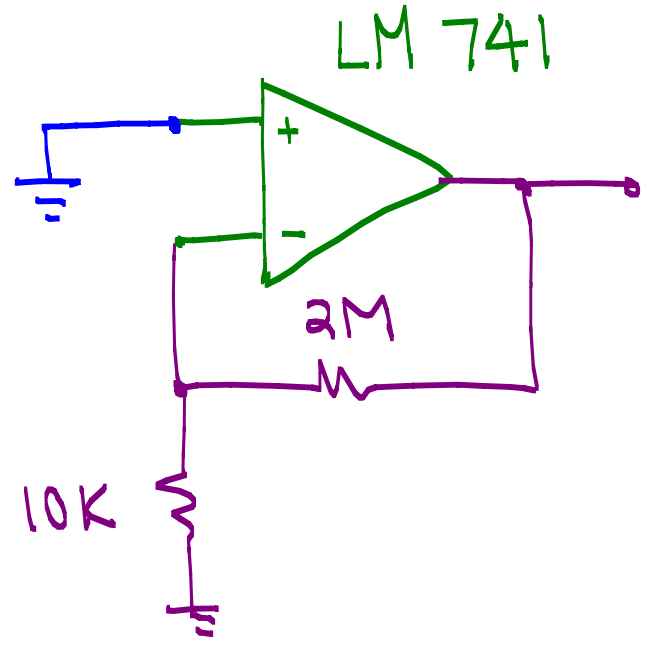Example LM741: $I_{IN(OS)} = 20 \text{ nA (TYP)}$ ($V_{IN} = 0$)

$$\Delta V_{IN} = (20 \times 10^{-9}) \times \left[\frac{9.95 \times 10^3 + 0}{2} \right] = \underline{\underline{0.1 \text{ mV}}}$$

★ Once again, JFET-input op amps
have $I_{IN(BIAS)}$ and $I_{IN(OS)} \sim \underline{\underline{50 \text{ pA}}}$!



3. Input offset voltage

Example LM741: $V_{IN(Offset)} = 1\text{mV (TYP)}$ ($V_{IN} = 0$)

• Putting it all together:



$I_{IN(BIAS)} : \Delta V_{OUT} = 201 \times 0.8\text{mV} = 160.8\text{mV}$

$I_{IN(Offset)} : \Delta V_{OUT} = 201 \times 0.1\text{mV} = 20.1\text{mV}$

$V_{IN(Offset)} : \Delta V_{OUT} = 201 \times 1\text{mV} = 201\text{mV} \leftarrow$ Largest error


• Sometimes, the ΔV_{OUT} cancel each other 😊
 other times, they add together ☹️

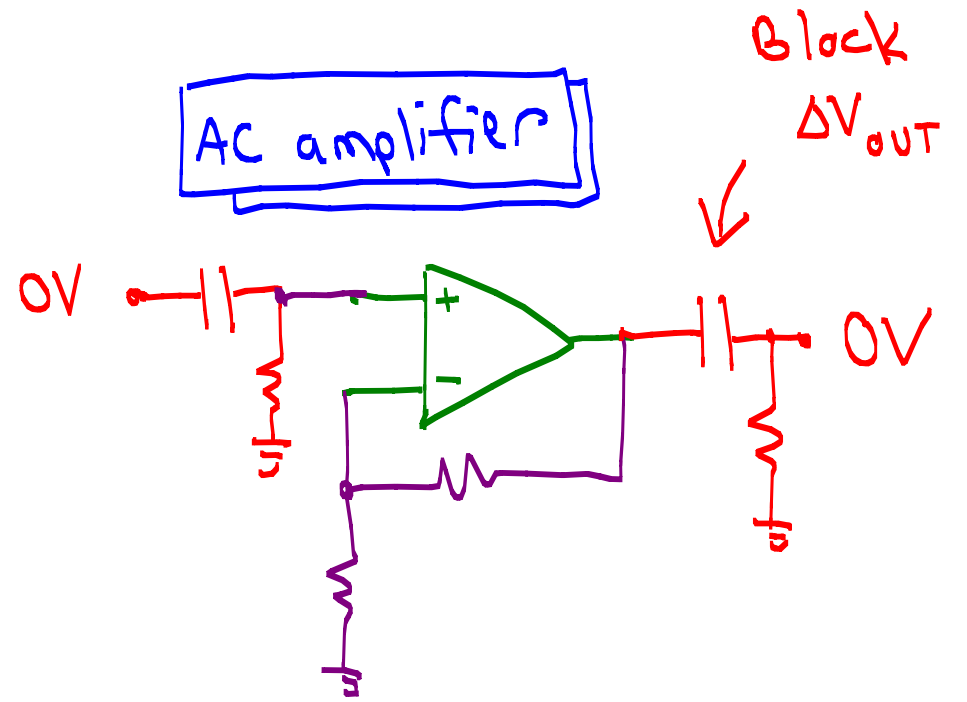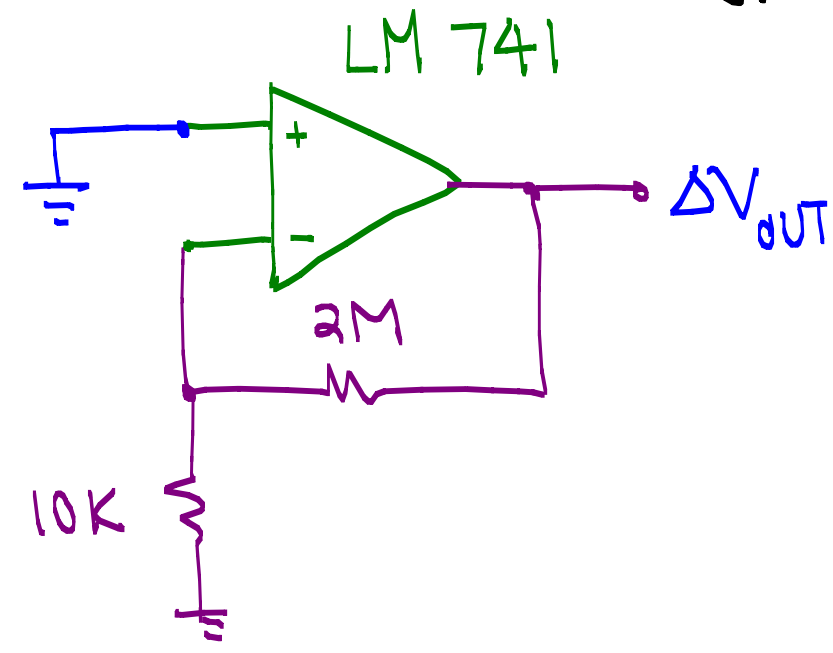★ NOTE: ΔV_{OUT} error is only a problem for DC amplifiers!




• Techniques to reduce ΔV_{OUT} error.

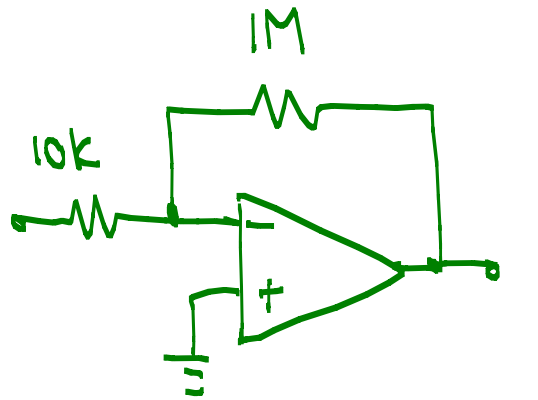① Make $R_{TH(+)} = R_{TH(-)}$ ← Reduce error from $I_{IN}(bias)$



[Ideal op Amp]

VS.

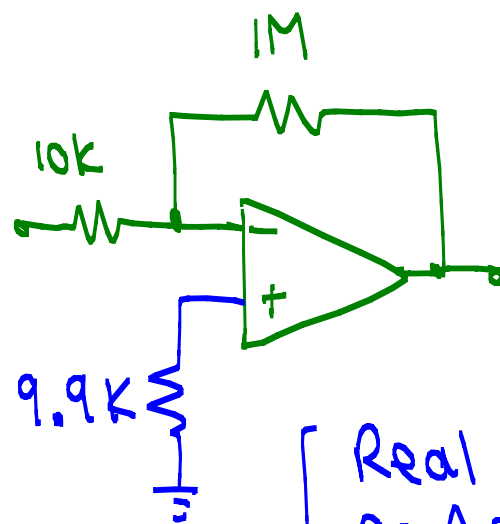



[Real op Amp]

② Use JFET-input op amp ← Reduce error from $I_{IN}(bias) + I_{IN}(os)$

LF356 (30 pA) vs. LM741 (80 nA)

☺ ↗

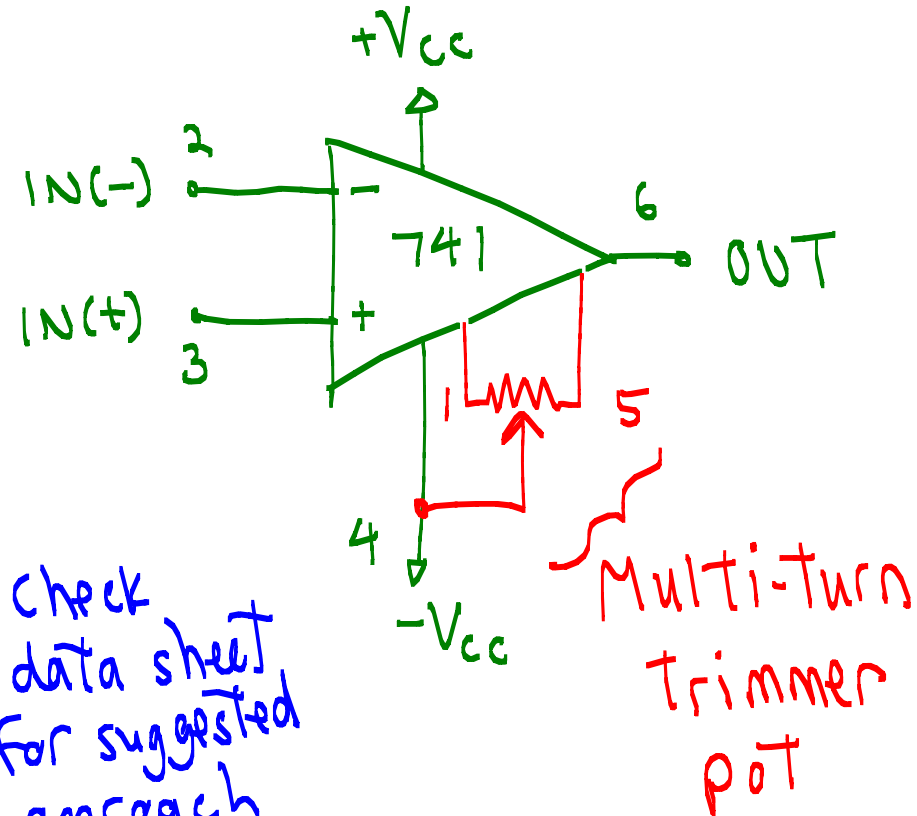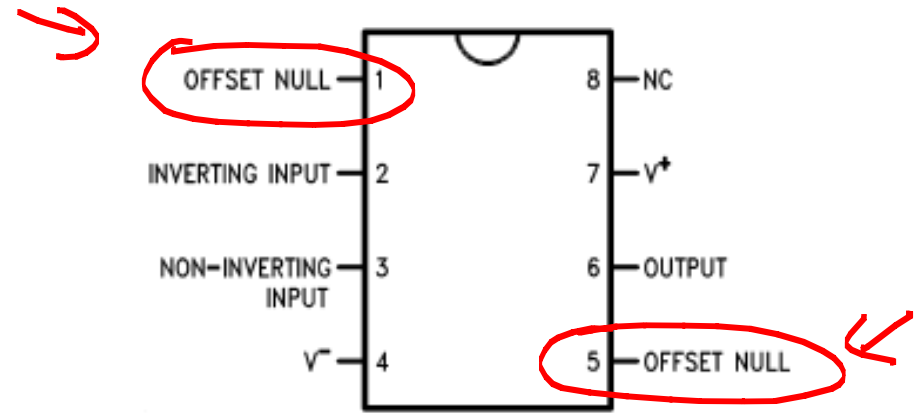③ Due to $V_{IN}(os)$: Trim the op amp! (6.8)



check data sheet for suggested approach

Multi-turn trimmer pot