

Lecture 07: Op Amp Speed

0. Review

1. Op Amp Speed

2. Gain Bandwidth

3. Slew Rate

Textbook reading:

14-1 Amplifier Freq Response

14-9 Rise Time - BW relationship

16-2 The 741 Op Amp
(Slew rate sub-section)

• PreLab 3: Multisim schematic + AC sweep

• HW3 due next Fri (Oct 11)
in box outside my office.

→ No class Oct 8 + 10

Finish Lab 3 on your own

• Quiz 3 (Oct 15) (see handout)

• Exam #1 (Oct 17)

→ HW1, 2, 3


→ QZ1, 2, 3

→ Sample exam on
course website

0. Review

Output Voltage Error




Real op Amp

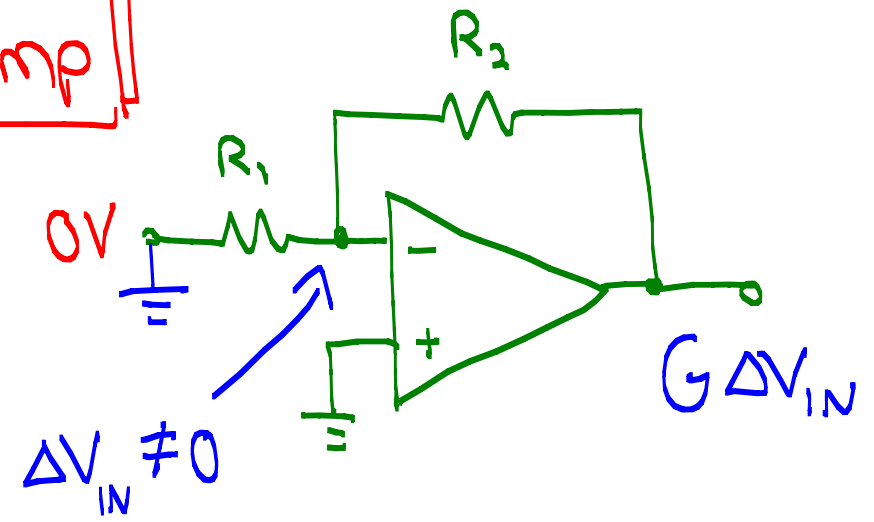

① Input bias current : $I_{IN(BIAS)} * [R_{TH(-)} - R_{TH(+)}]$


② Input offset current : $I_{IN(OS)} * \frac{R_{TH(-)} + R_{TH(+)}}{2}$

③ Input offset voltage : $V_{IN(OS)}$

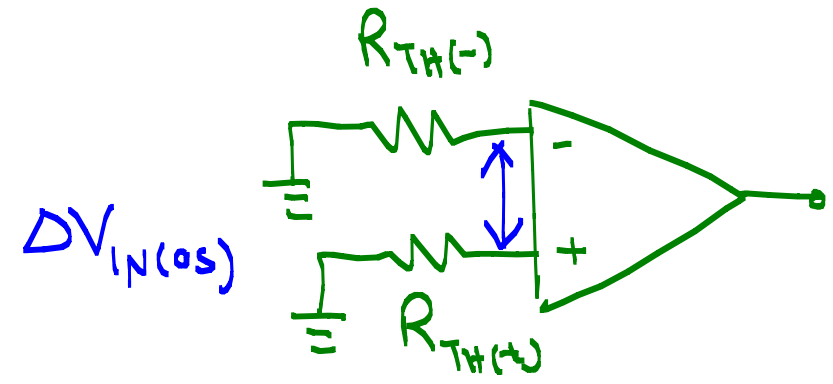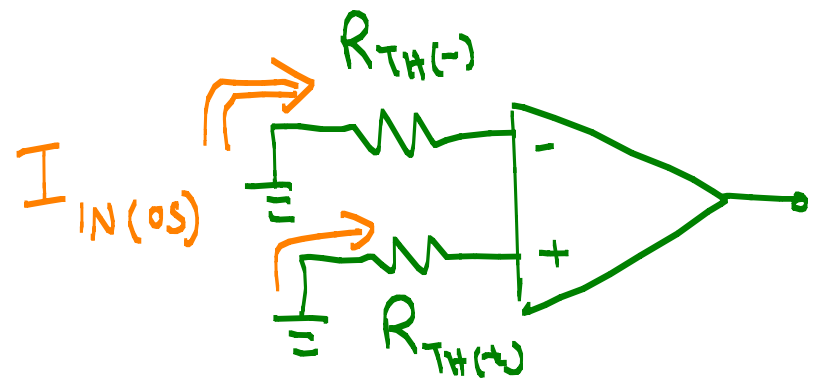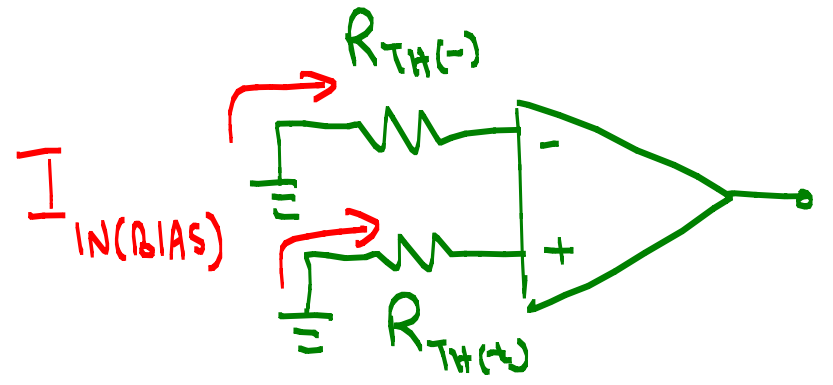

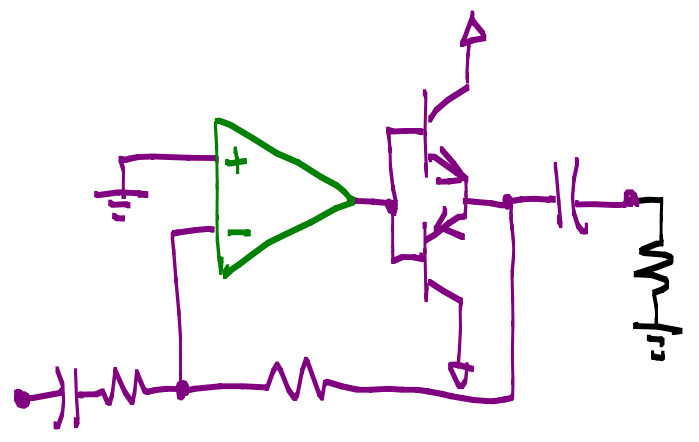1. Op Amp Speed

- In Lab 2, crossover distortion would be much worse at MHz freq



Q: What limits the op amp speed?


A: Depends on ...

2. Gain-Bandwidth Product

• Consider our non-inverting amplifier.

Q: What is its bandwidth?

A:

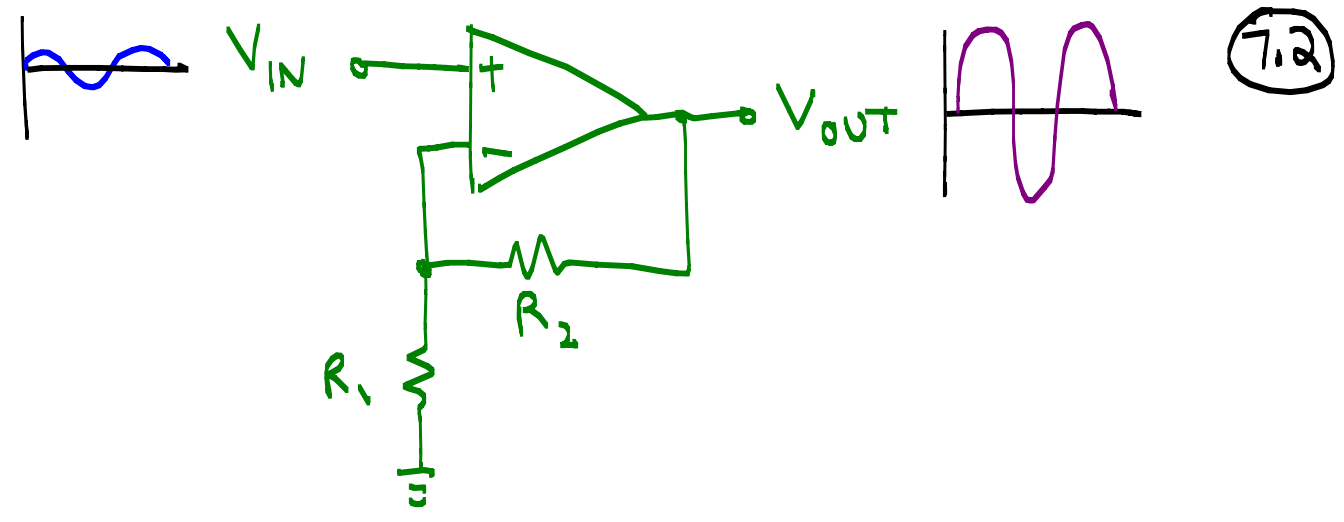


7.2

• GBW product depends on the op amp!

Example

741

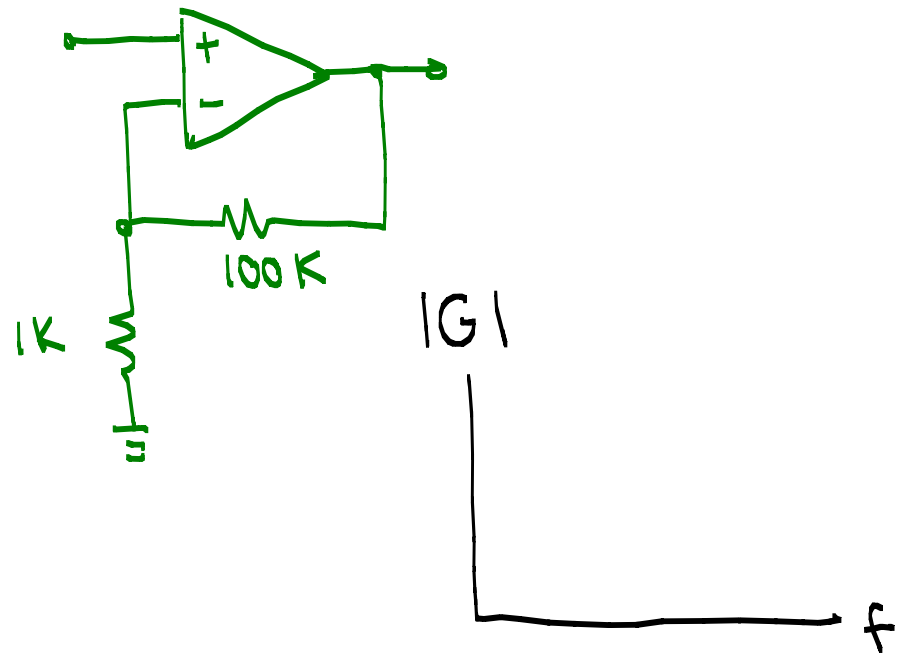


BW =

LF356

G =

BW =

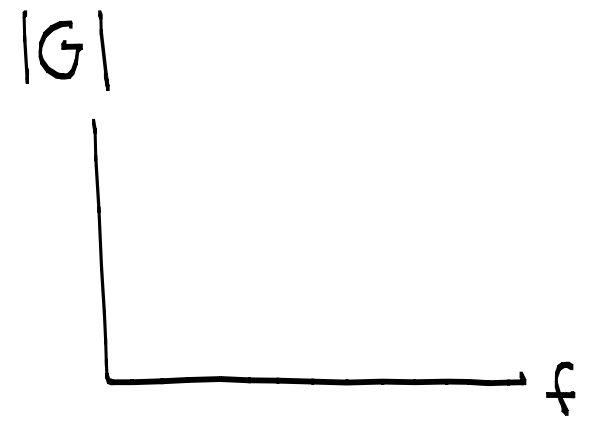

Op Amp

GBW

LM741

LF411




LF356

LT1128


- For many non-sinusoidal signals (e.g. square wave), time-domain response is more meaningful.

V_{IN}

V_{OUT}

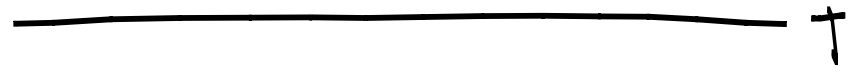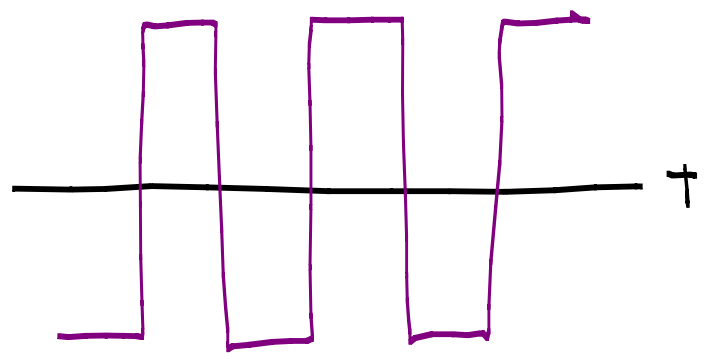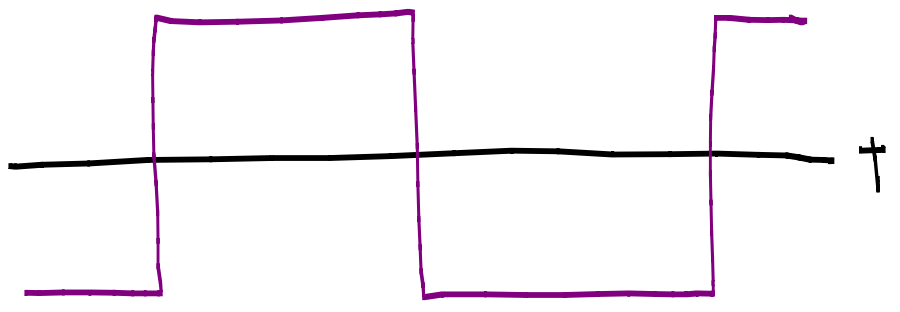


• Rise Time $T_R =$

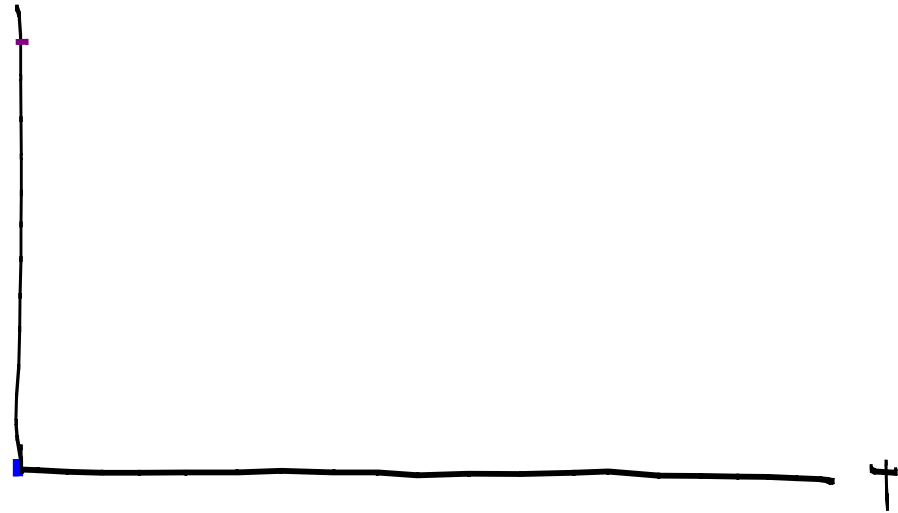

→ Rise Time : $T_R =$

Example

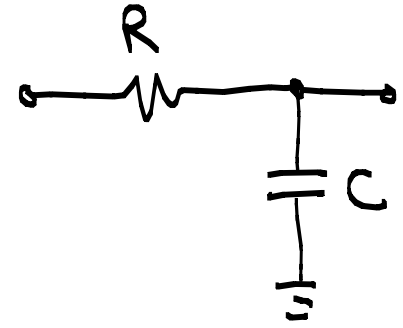

3. Slew Rate (SR)

Slew Rate =

If op amp is SR limited,



Example: Op amp: $GBW = 2 \text{ MHz}$
 $S_R = 1 \text{ V}/\mu\text{s}$

Input: $V_{in} = 0.5 \cdot u(t) \leftarrow \text{step fn}$ 7.7
 $G = 10$

Ideal

Actual V_{out} is limited by BW or SR

①





②




- Bandwidth vs. Slew Rate

Example

7.8

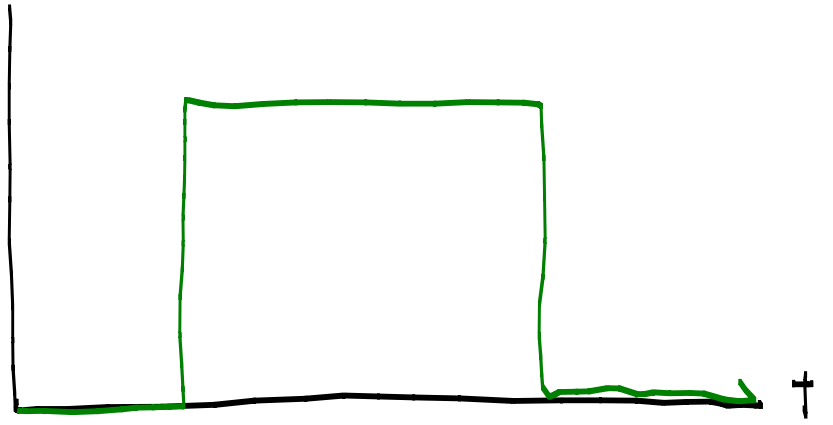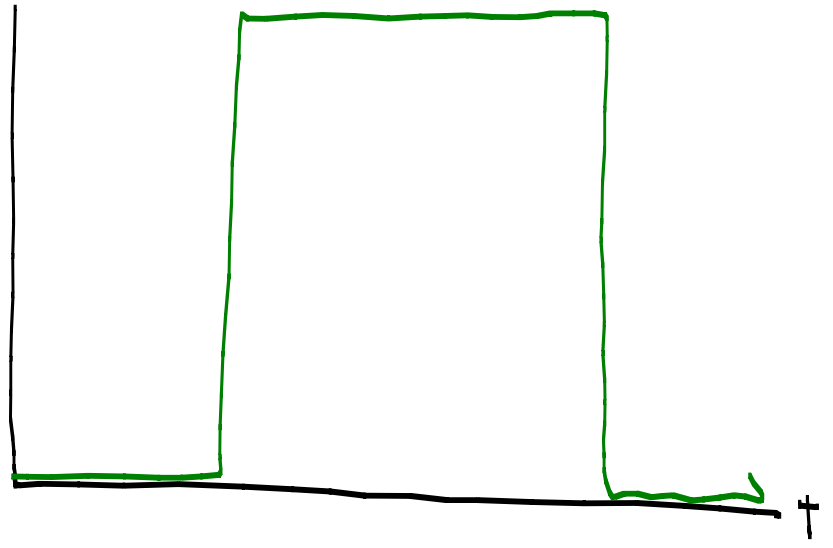

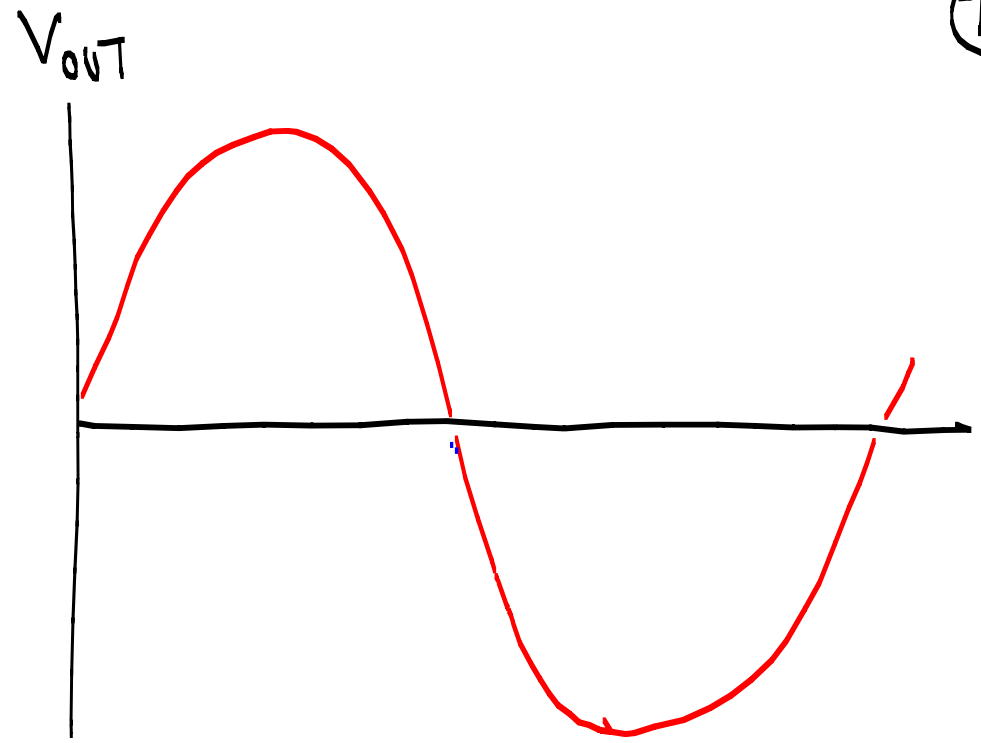③ For sine waves, SR limitation causes distortion.



• Power Bandwidth:

Example

Op amp: $GBW = 2 \text{ MHz}$

$SR = 1 \text{ V}/\mu\text{s}$

Signal: $V_{in} = \sin 2\pi f_0 t$

$f_0 = 100 \text{ kHz}$

$G = 10$

7.10

① Check f_0 vs. BW:

② Check f_0 vs. power bandwidth: