

Lecture 8 : BJT Switches

(Quiz)

1. Intro

2. BJT Analysis

3. BJT Design

- Exam #1 this Thu (Oct 17)
 - Closed notes, closed book
 - HW1, 2, 3 material
 - See course website for sample exam + solns

- This week's lab : wrap up Lab 3 testing/demo


Textbook reading:

6-13 : Recognizing saturation

6-14 : Transistor switch

0. Review

① Bandwidth (small signal)

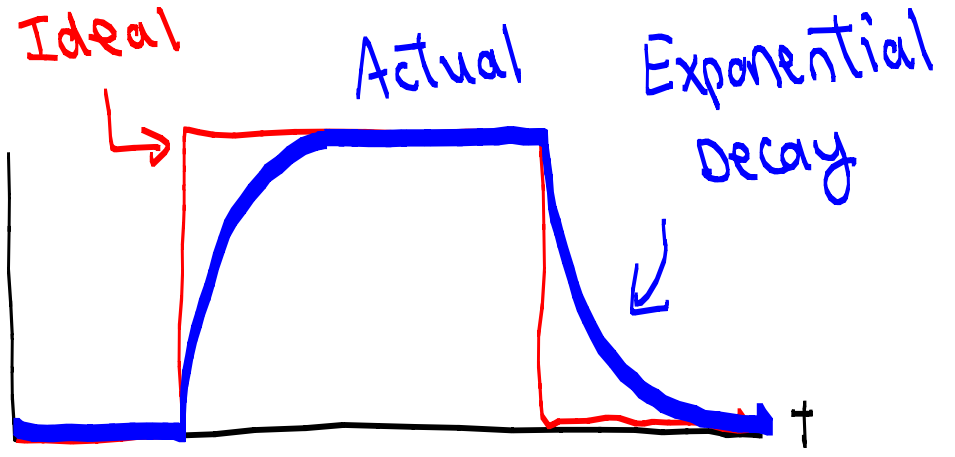


Rise time: $T_R = 0.35/BW$

Bandwidth = $\frac{GBW}{Gain}$

Gain-Bandwidth Product

② Slew Rate (Large signal)

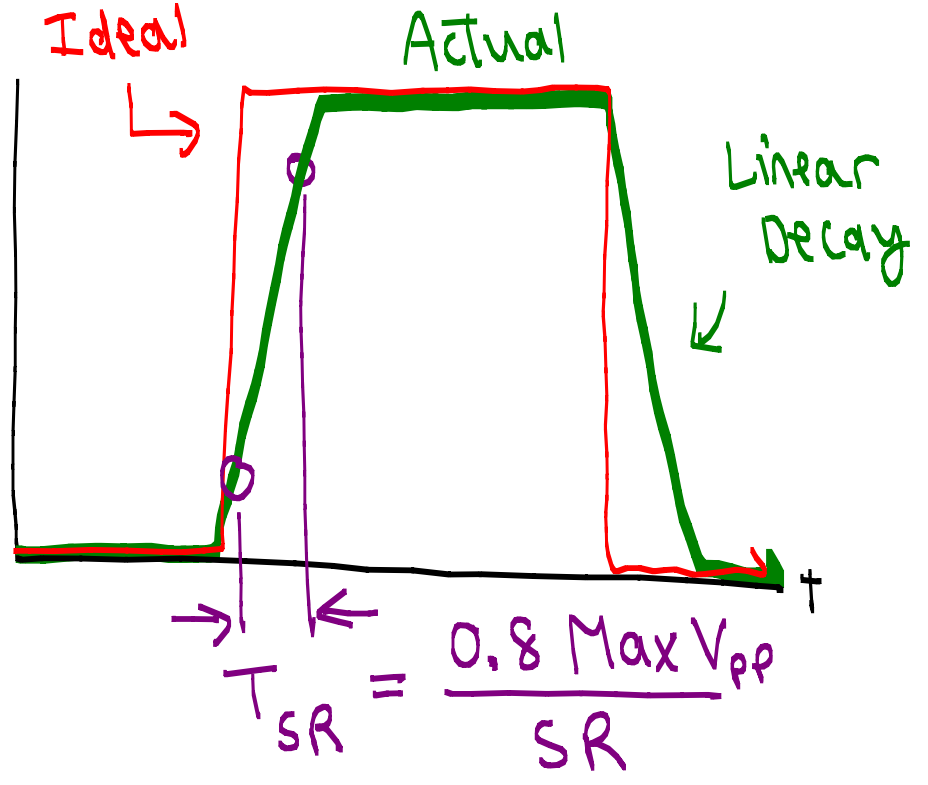


Large signal bandwidth (sine wave only)

$f_{max} = \frac{SR}{2\pi V_p}$


Only for sine wave!

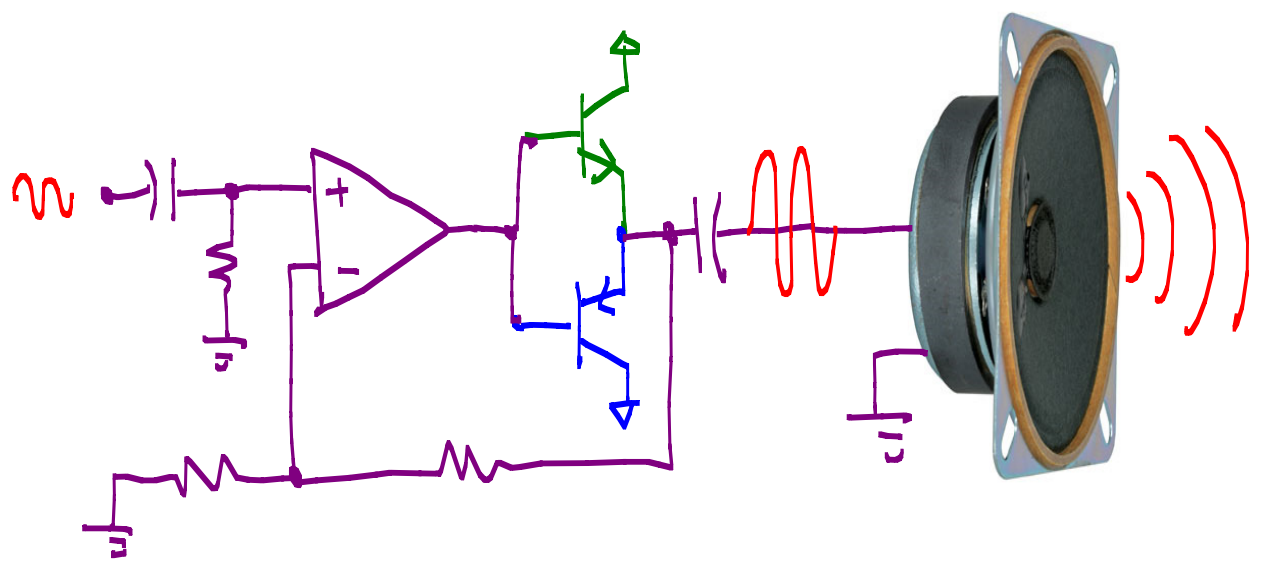1. Intro

- So far, we have used the BJT as an amplifier.
used in active mode!
Variable V_{OUT}



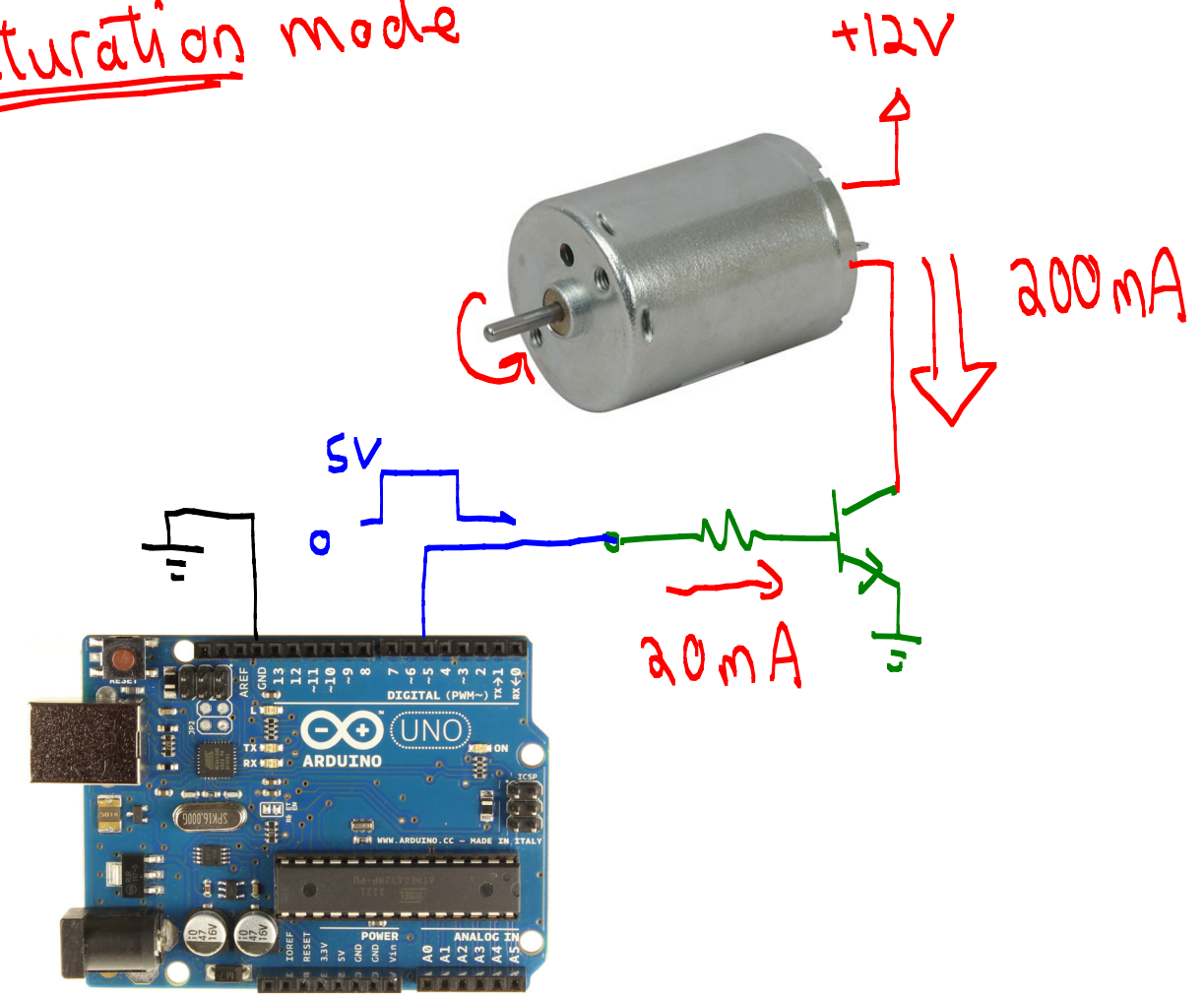- Many devices (e.g. motors) require the BJT as a switch ← open or closed
used in saturation mode







Transistor is like a valve for a large water pipe.

★ Base is like a control knob

Fully Closed

Partially open

Fully Open

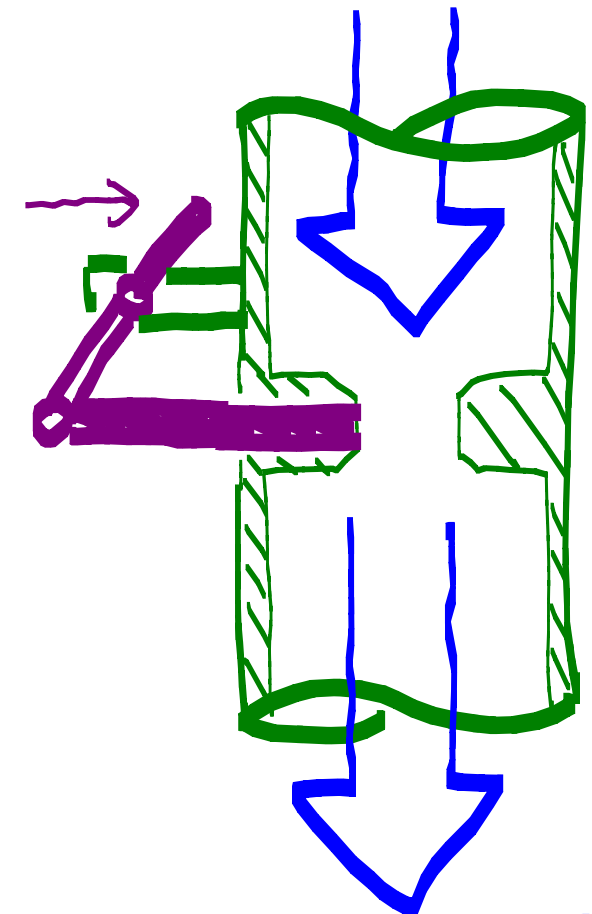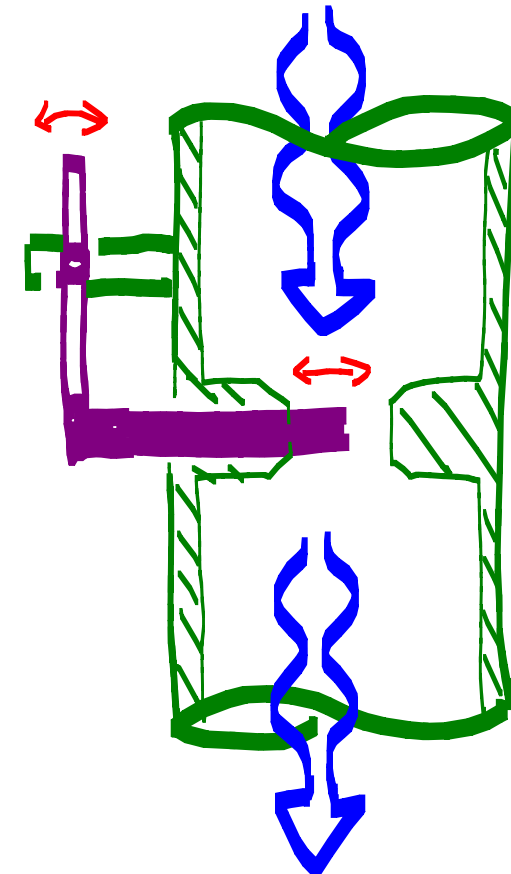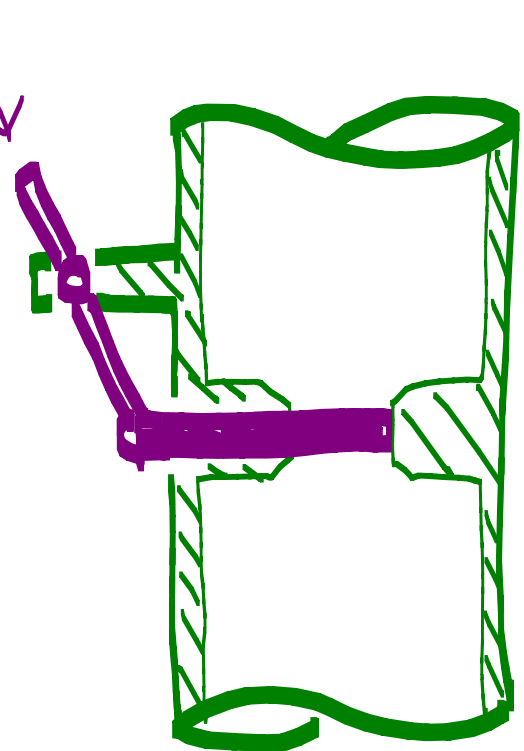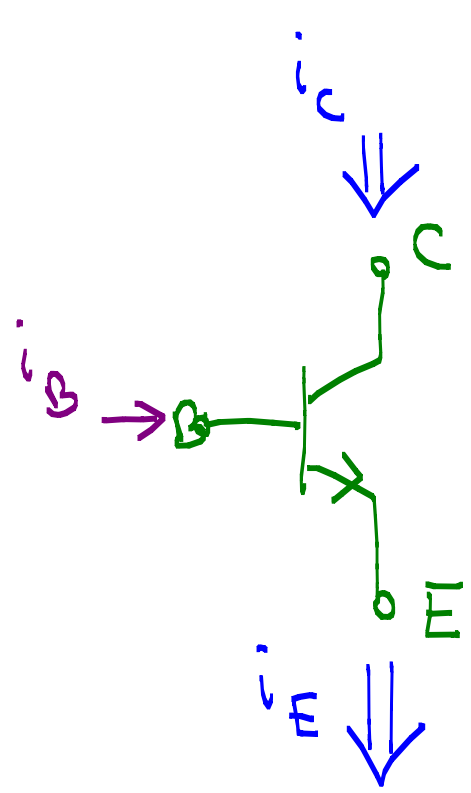

CUT-OFF
(No flow)

ACTIVE
(Variable Flow)

SATURATED
(Max Flow)

2. BJT Switch Analysis

• Review (npn switch)

• BJT switch is either:

① OFF (cut-off)


$\rightarrow I_B = 0$ and $I_C = 0$

② ON (saturation mode)


$\rightarrow V_{BE} = V_{BE,sat}$

$\rightarrow V_{CE} = V_{CE,sat}$ and $I_C \ll \beta I_B$

Switch is OFF

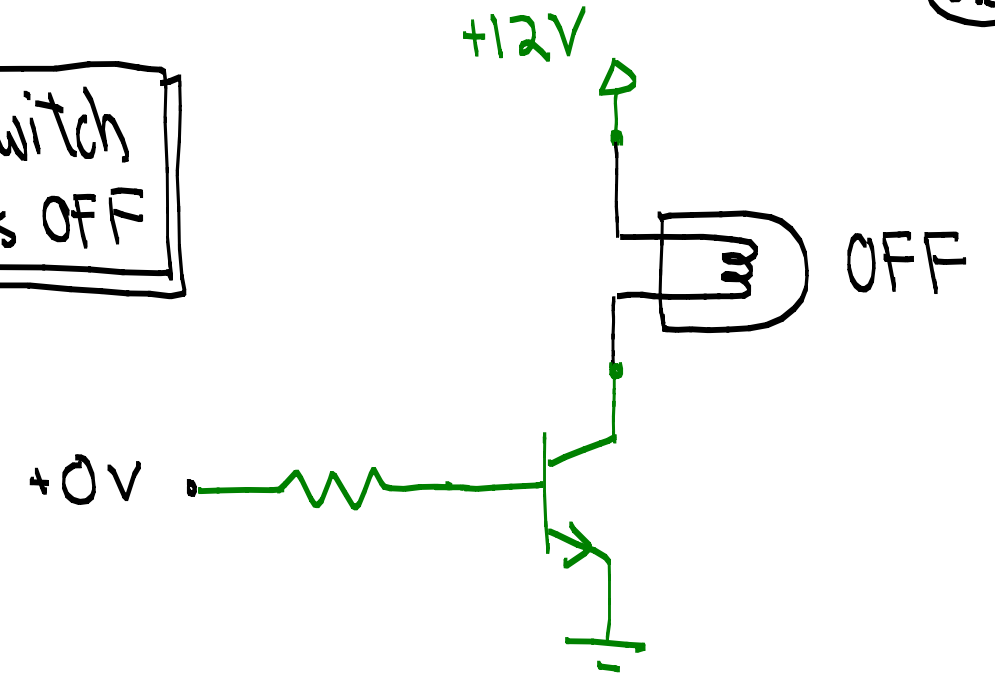


Switch is ON

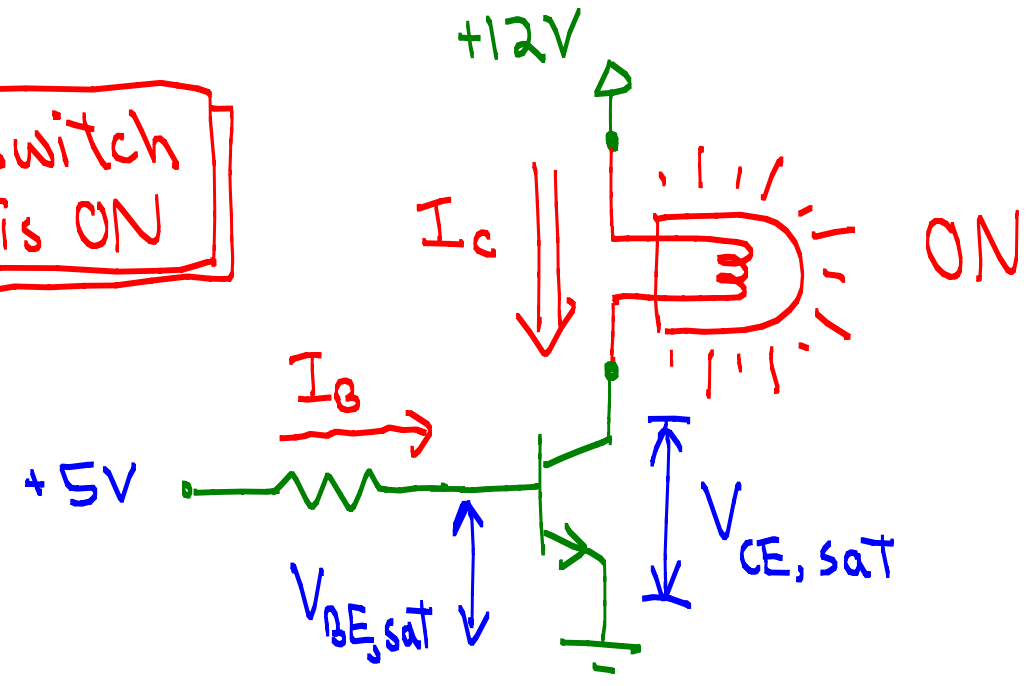

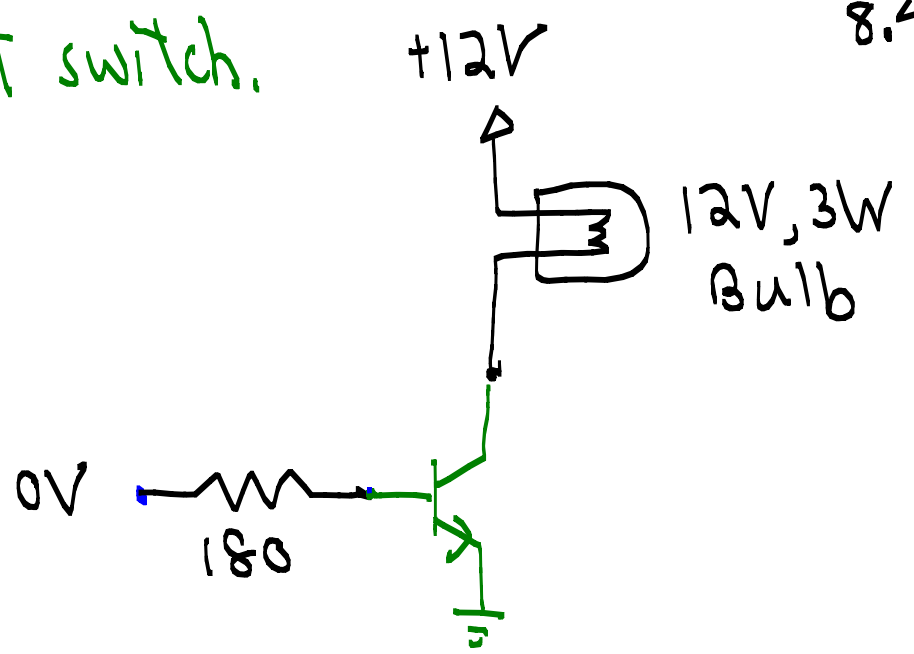Example Incandescent Light bulb driven by BJT switch.

- When $V_{in} = 0V$:
 $I_B = 0 \Rightarrow$ BJT is OFF




- When $V_{in} = 5V$: For "quick" analysis

$$I_B = \frac{5 - V_{BE,sat}}{180\Omega} = \frac{5 - 0.7V}{180\Omega} = \underline{\underline{23.9mA}}$$

$$I_C = \frac{12 - V_{CE,sat}}{48\Omega} = \frac{12 - 0}{48\Omega} = \underline{\underline{250mA}}$$

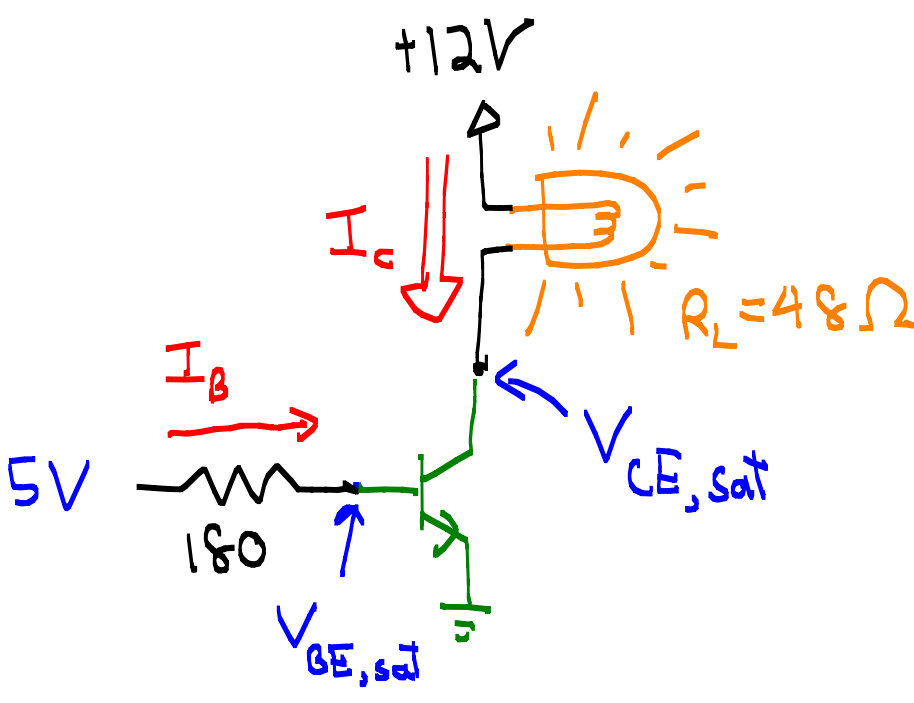[Bulb is basically a resistor,
 so $P = \frac{V^2}{R} \rightarrow R = \frac{144}{3} = 48\Omega$]



• Typical analysis:

→ use transistor data sheet to find $V_{BE,sat}$, $V_{CE,sat}$!


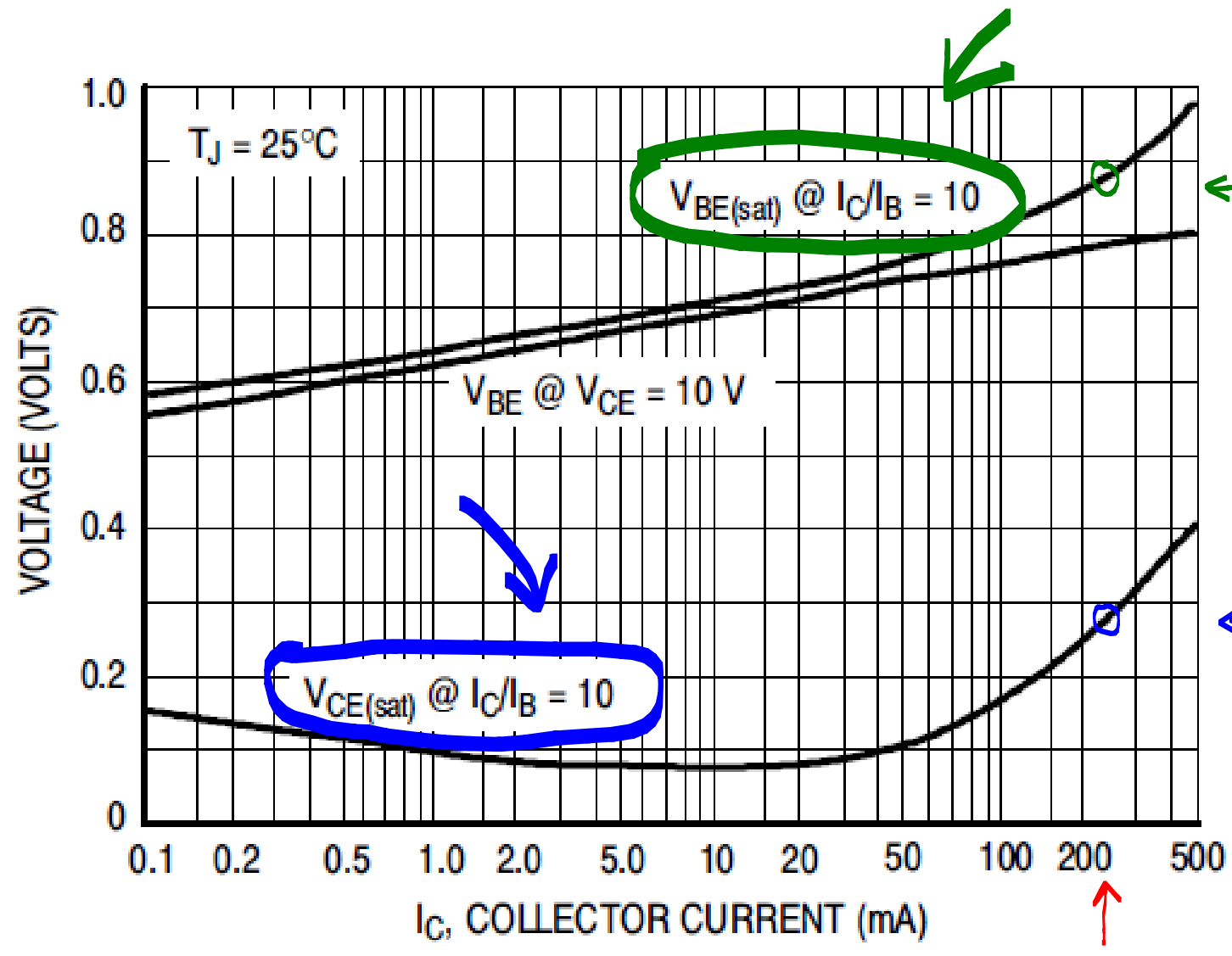


Figure 17. "On" Voltages

250 mA

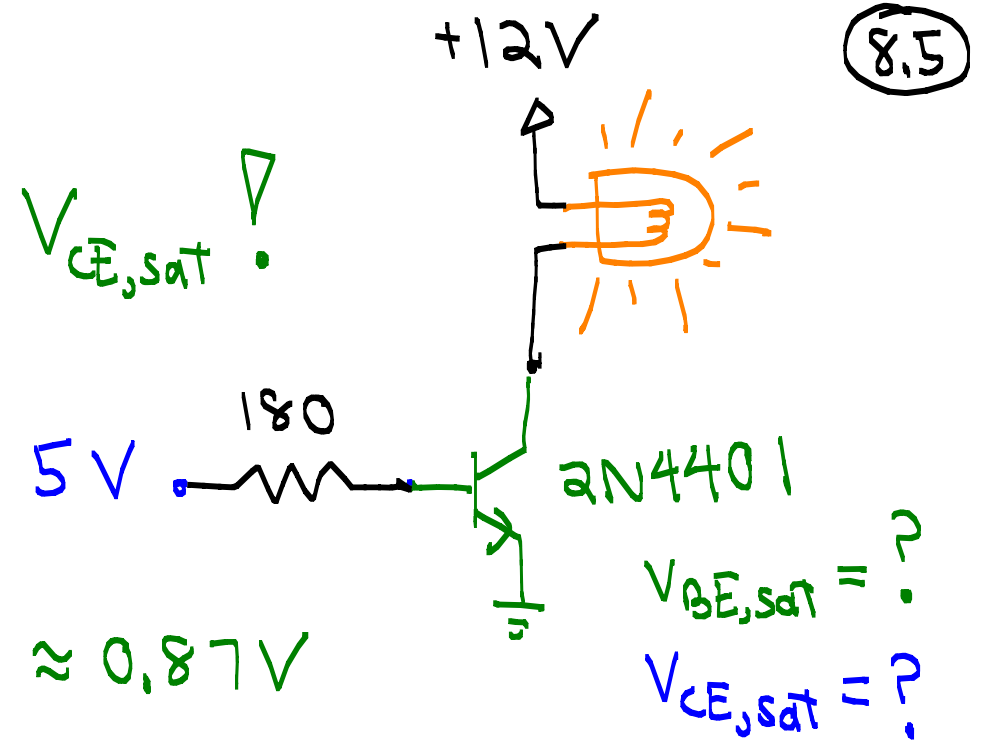

$V_{BE,sat} \approx 0.87V$

$V_{CE,sat} \approx 0.27V$

• Light bulb rating: 12V, 3W

→ $I = \frac{3W}{12V} = 0.25A$
 $= 250mA$

use "quick" analysis OR load rating to determine $V_{BE,sat}$ and $V_{CE,sat}$

From 2N4401 data sheet: $V_{BE,sat} \approx 0.87V$ } Typical values
 $V_{CE,sat} \approx 0.27V$ }

$$I_B = \frac{5 - 0.87V}{180} = 0.0229 A = \underline{\underline{22.9 mA}}$$


$$I_C = \frac{12 - 0.27V}{48\Omega} = 0.244 A = \underline{\underline{244 mA}}$$

★ For reliable operation, a BJT switch should be driven into hard saturation

$$\Rightarrow \boxed{\frac{I_C}{I_B} \sim 10}$$

★ For Darlington BJT:
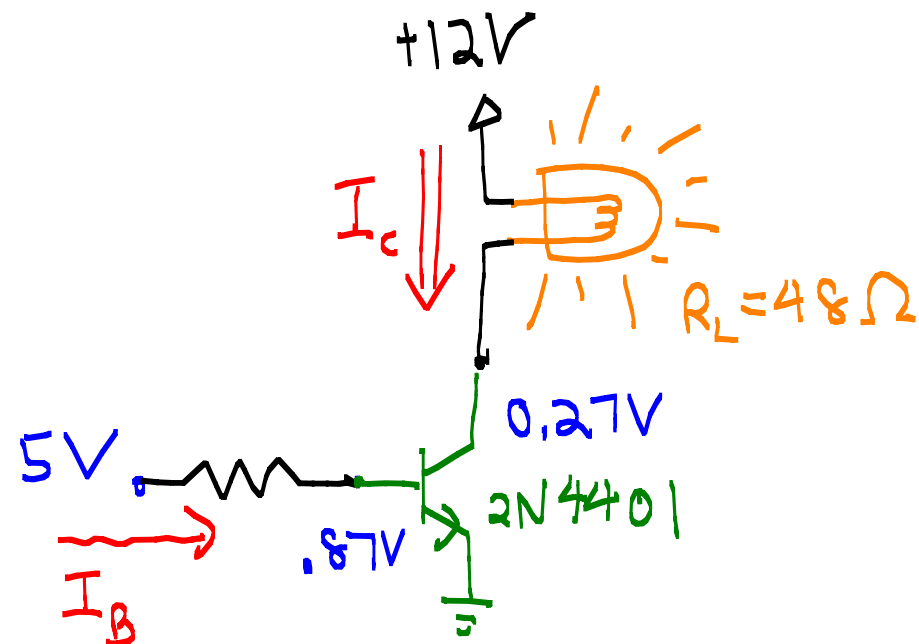
$$\Rightarrow \boxed{\frac{I_C}{I_B} \sim 250}$$



Proper Saturation?

$$\frac{I_C}{I_B} = \frac{244}{22.9} = 10.7 \checkmark$$

3. BJT switch design


Step 1

Know your load: current, voltage, etc

Step 2

Wisely choose the transistor

↳ check max I_c , max V_{CE} , P

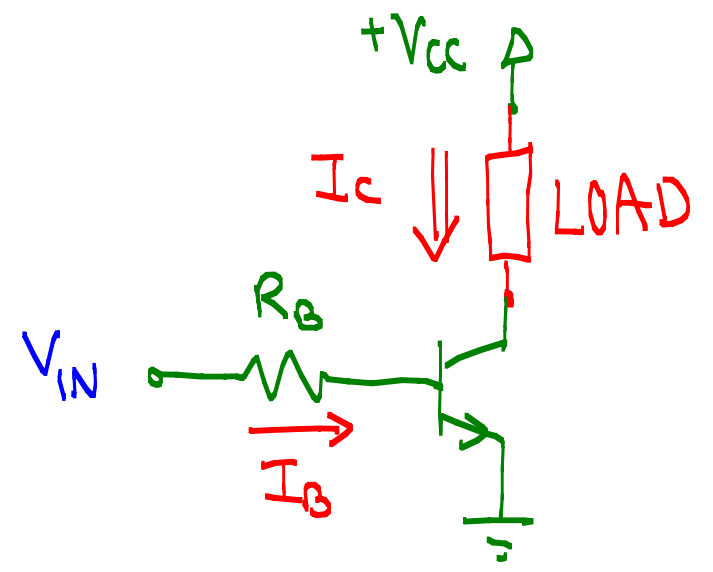

Step 3

Properly saturate the transistor

(A) $V_{CE} = V_{CE,sat}$


(B) $I_B \approx \frac{I_c}{10}$

single BJT



or $I_B \approx \frac{I_c}{250}$

Darlington

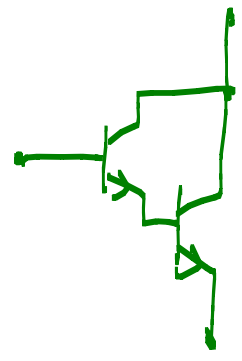


• Design example: Driver for 12V solenoid

STEP 1 Load properties

• Solenoid is essentially a wire coil with resistance $R_L = \frac{12V}{0.8A} = 15\Omega$

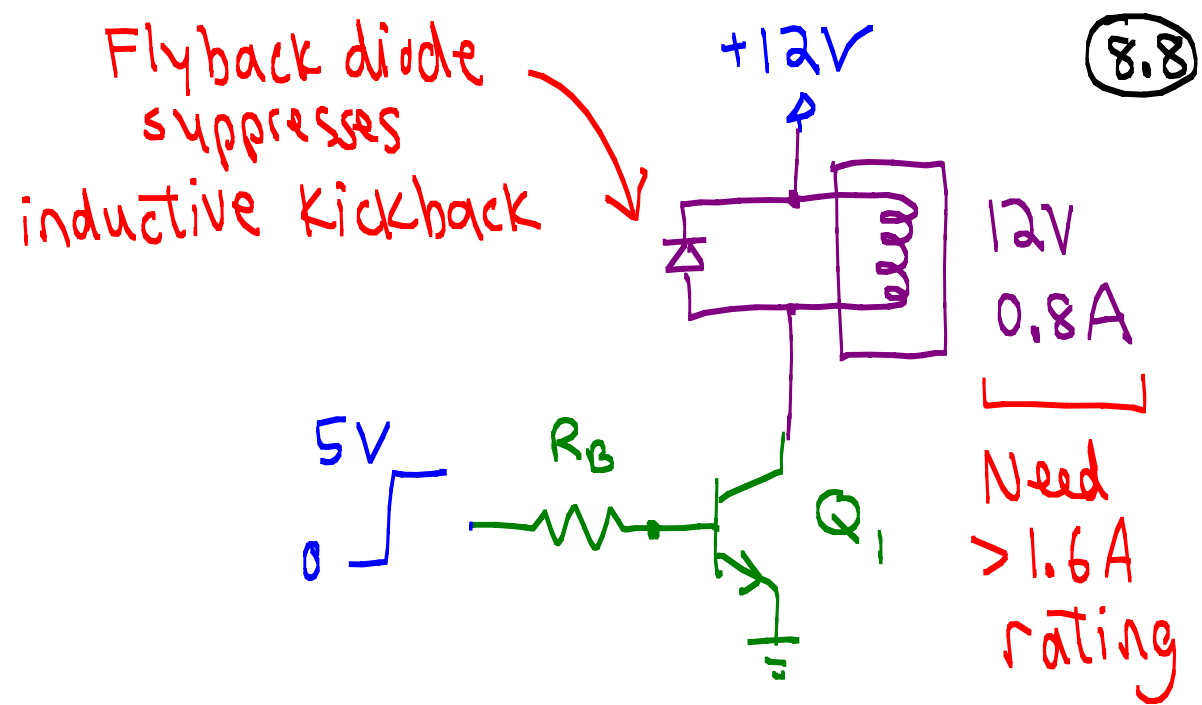• Usually OK for current to be ~75% of rated value



STEP 2 Choose the transistor:

	<u>Max I_c</u>	<u>Max V_{ce}</u>	<u>Max P</u> (no HS)	<u>Max P</u> (w/HS)
<u>2N4401</u>	600 mA X	40V	0.625W ✓	1.5W
<u>TIP31A</u>	3A ✓	40V ✓	2W ✓	40W

$$P = \frac{0.8A}{10} (0.85V) + (0.8A)(0.17V) = 0.204W$$

From data sheet plots $\rightarrow .41W$ rating $\times 2$

★ Choose TIP31A (no HS)


STEP 3. Properly saturate the BJT

① Make sure load is happy

For solenoid: $I_c = \frac{12 - V_{CE,sat}}{15\Omega}$

Typical

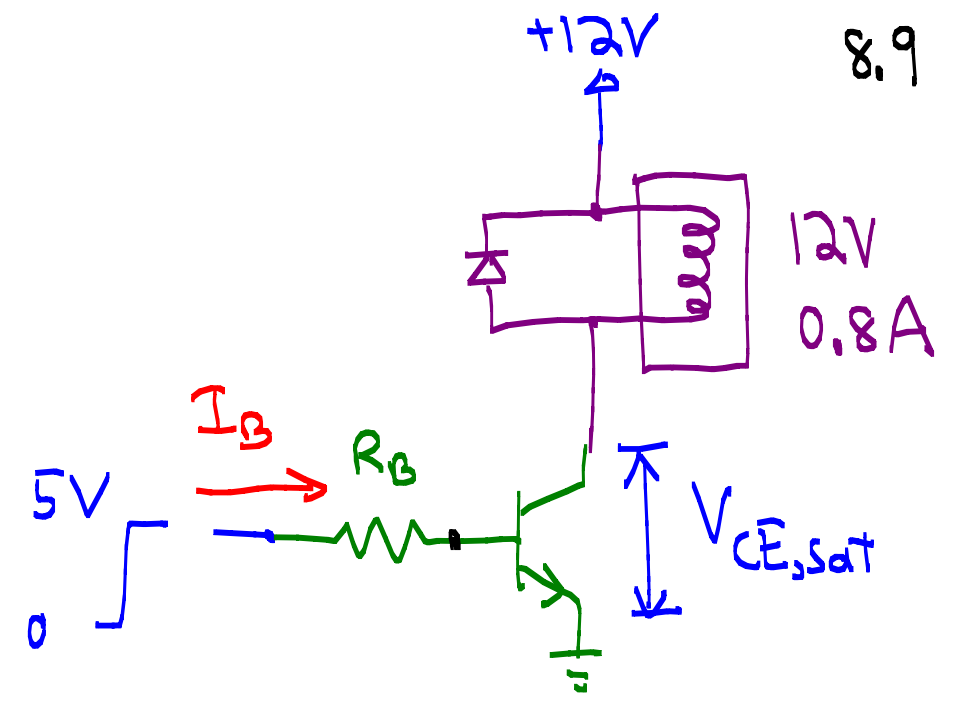$I_c = \frac{12 - 0.17V}{15\Omega} = 0.79A \checkmark$



② Base current drive

$I_B \sim \frac{I_c}{10}$

★ I_B must be large enough to drive the BJT switch into hard saturation

$\rightarrow I_B = \frac{5 - 0.85}{R_B} \approx \frac{0.8A}{10}$


$\Rightarrow R_B \approx 51.9 \Omega$

Choose $R_B = 56 \Omega$

The $I_B \sim \frac{1}{10} I_c$ criterion is pretty flexible (e.g. 62Ω is fine)

• The degree of transistor saturation depends on transistor condition! (8.10)

Typical

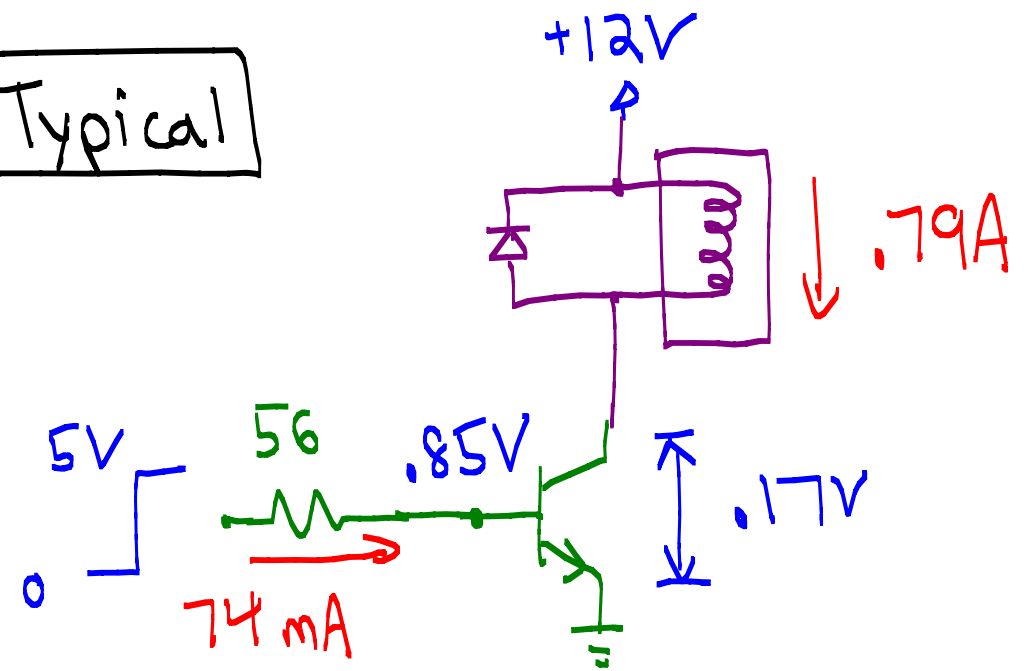


$$I_c = \frac{12 - 0.17}{15\Omega} = 0.79A$$

$$I_b = \frac{5 - 0.85}{56\Omega} = 0.074A$$

$$\Rightarrow \frac{I_c}{I_b} = 10.7$$

Worst Case

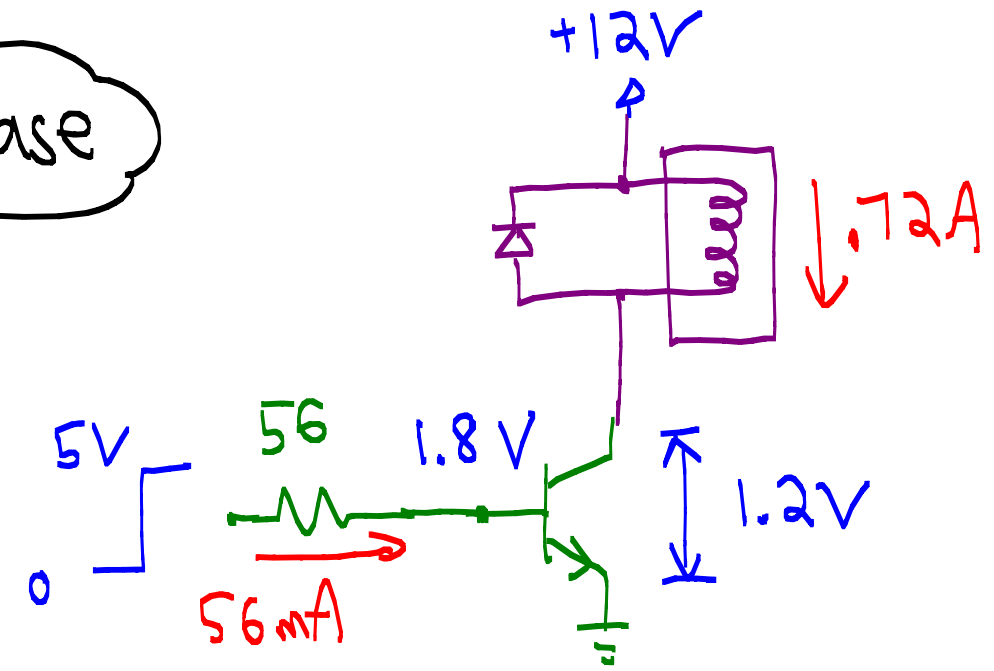

$$I_c = \frac{12 - 1.2}{15\Omega} = 0.72A$$

$$I_b = \frac{5 - 1.8}{56\Omega} = 0.057A$$

$$\Rightarrow \frac{I_c}{I_b} = 12.6$$

← Smaller I_b !

For single BJT

$\frac{I_c}{I_b}$ between 10 to 20 is fine!



• what about the flyback diode?

→ Must be able to withstand the load current (0.8A) for ~1ms

NOTE: The diode current is a short pulse (not continuous).

→ Choose a diode with large enough (> 2x) current rating

Want >1.6A pulsed rating

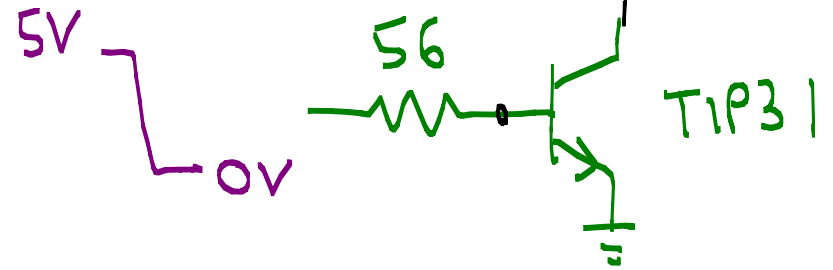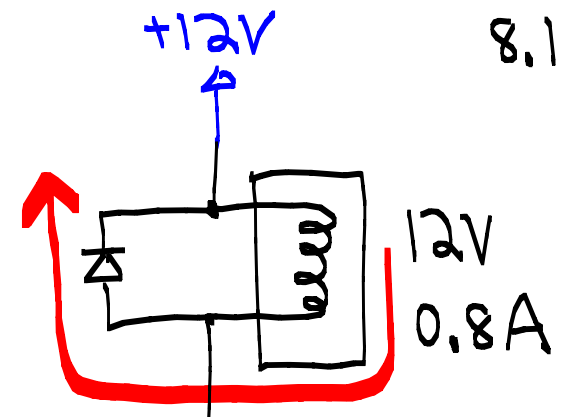

IN4148

IN4002

① "Repetitive Reverse voltage breakdown" V_{RRM}

✓ 75V

100V ✓
30A (8.3ms) ✓

② "Non-repetitive peak forward surge current" I_{FSM}

X 1A (1s)

✓ 2A (1μs)

very short ↗

Safer choice!