

Lecture 10: Schmitt Trigger

0. Review

1. Intro

2. Relaxation Oscillator

3. Schmitt Trigger

- PreLab 4 due today

- HW4 due Fri (Oct 25)

- Exam #1 re-do } next Tue (Oct 29)
Quiz

- Lab 3 report due Nov 04 (Mon)

Textbook Reading:

Ch 20-1 Comparators with zero reference


20-3 Comparators with hysteresis

20-7 Waveform Generation




0. Review

MOSFET switches

NMOS

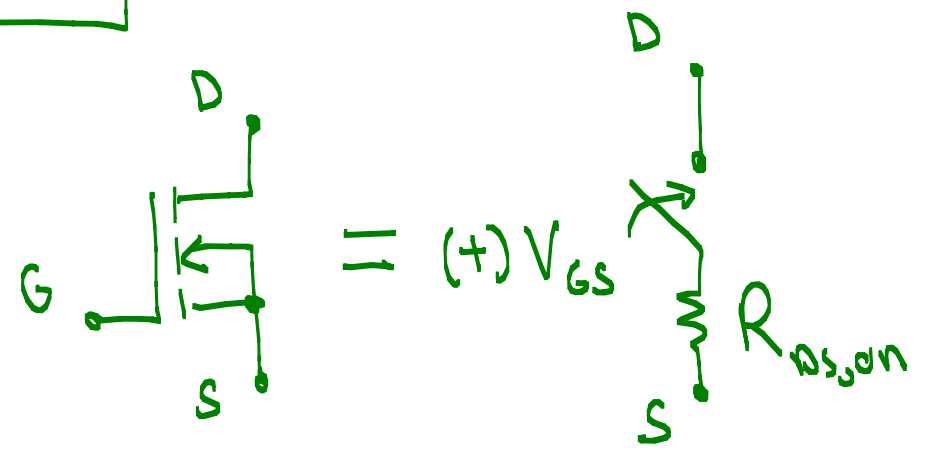

PMOS

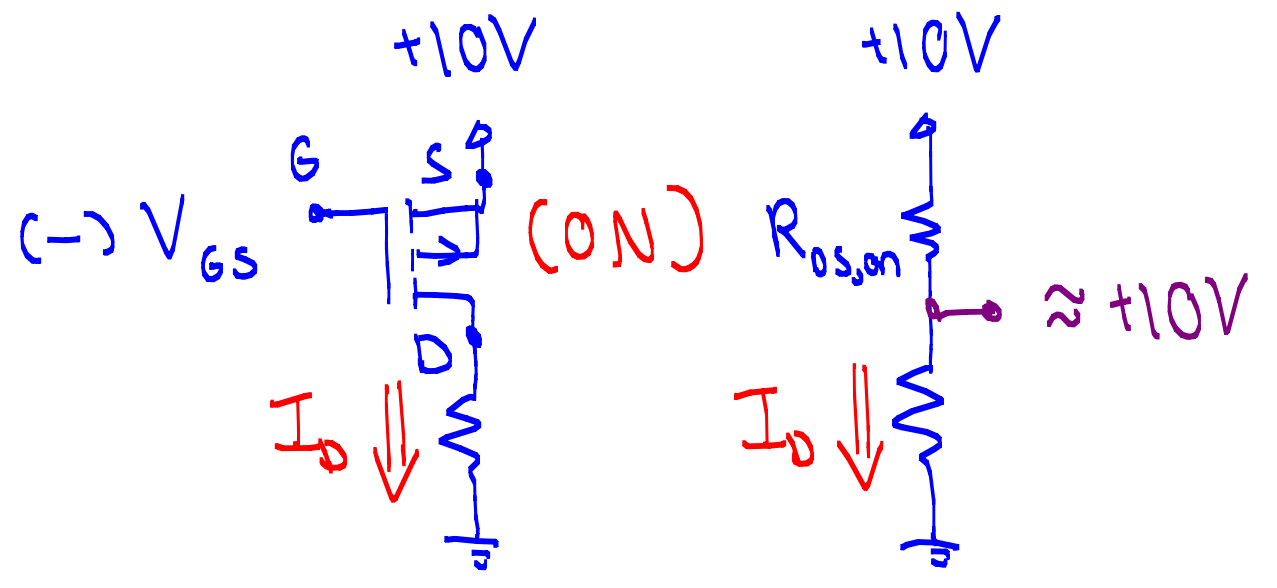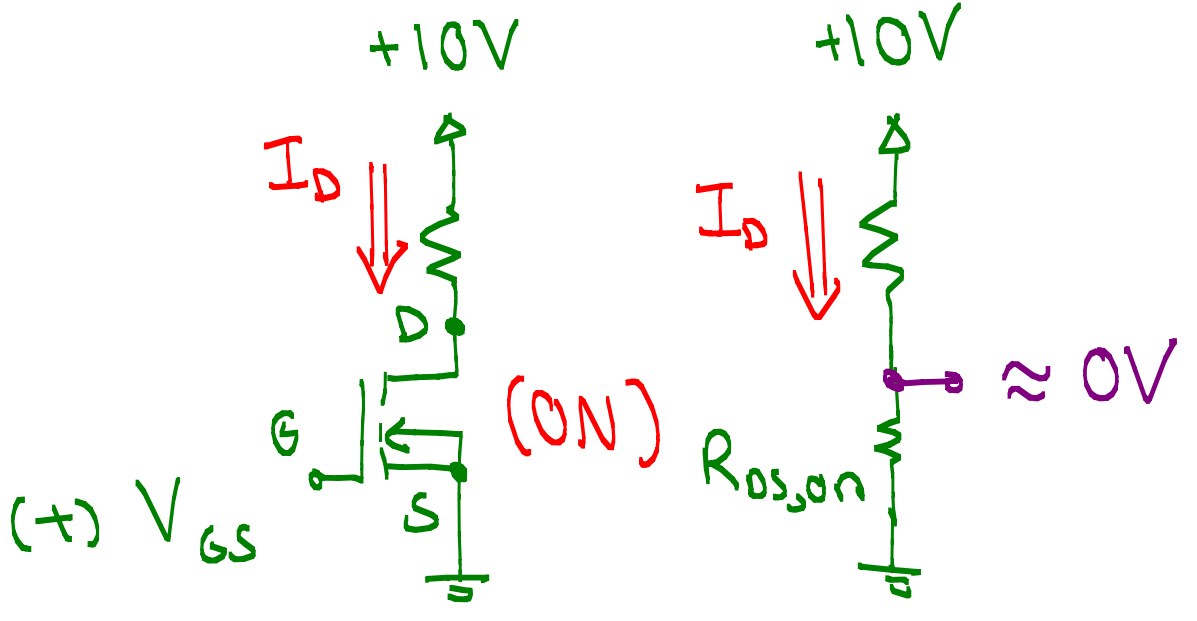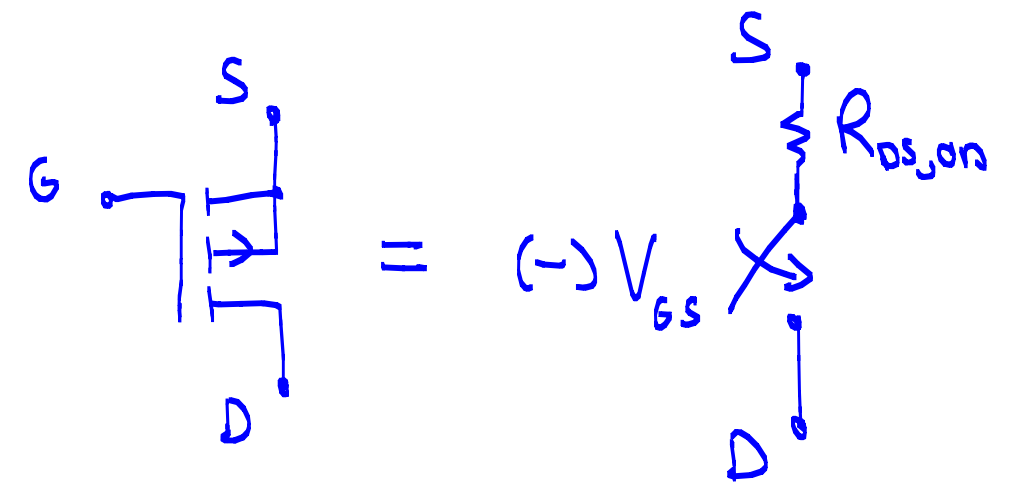


1. Intro

- Unlike amplifiers, waveform generators use positive feedback!

Negative Feedback


Ex:

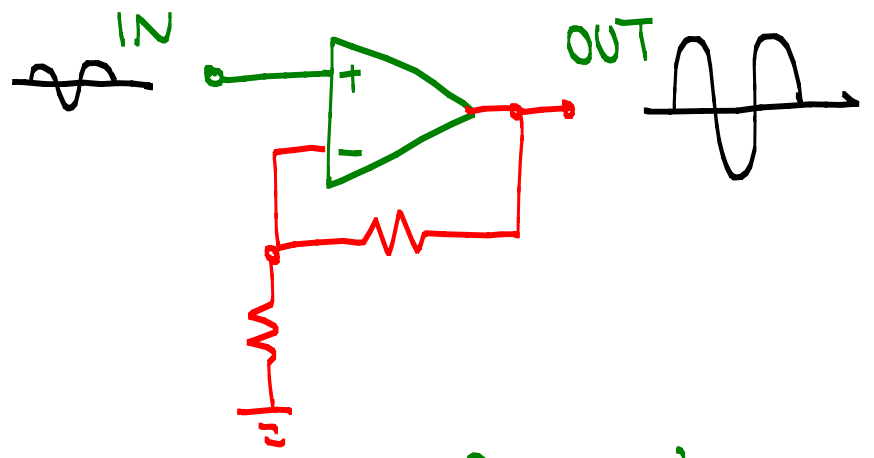

- Most common configuration for op amps
- ⇒ Amplifiers, current sources, filters, voltage references, etc.
- ★ Golden Rules!

Positive Feedback

Ex:

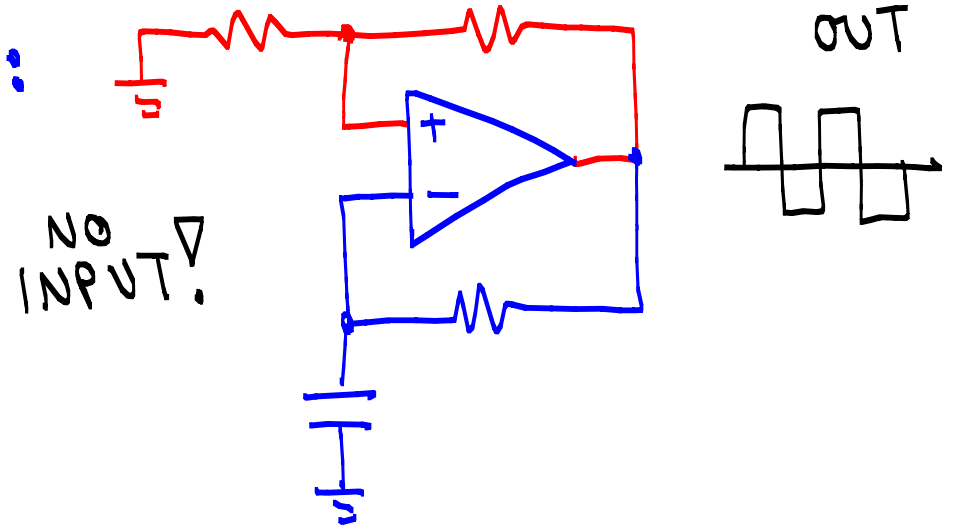

NO INPUT!


- useful to make oscillators, comparators, etc.
- ★ NO Golden Rules! ∴

Example Pulse Width Modulation (PWM)

Const Freq, Variable
duty cycle
PWM

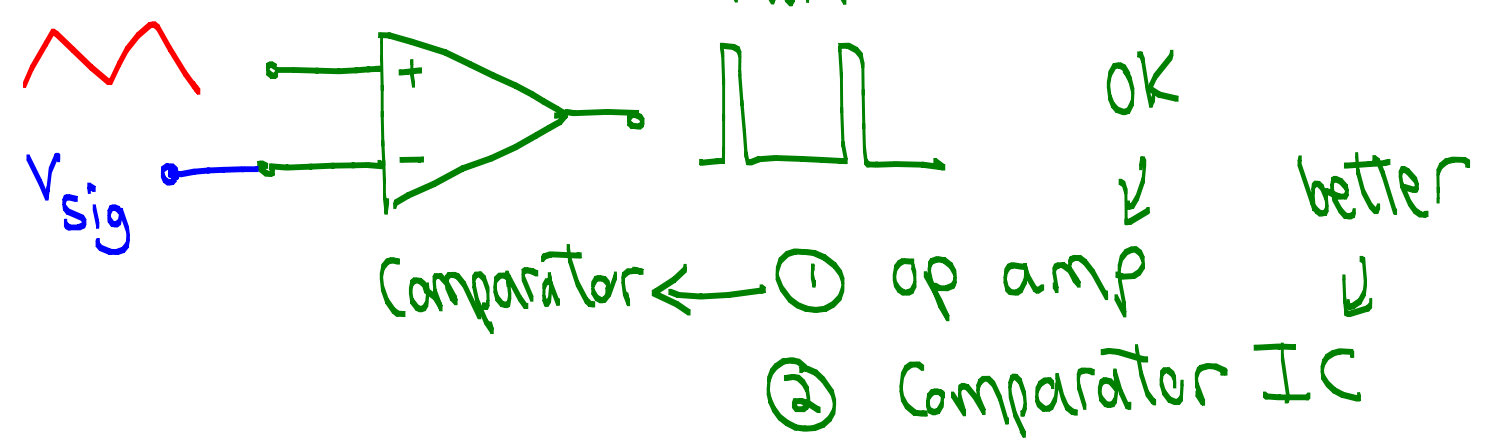10.1b






- Many applications!
- Motors
- Lighting
- Communication etc.
- Servos
- Class D amps



Q: How to implement PWM?


A: Use a voltage comparator

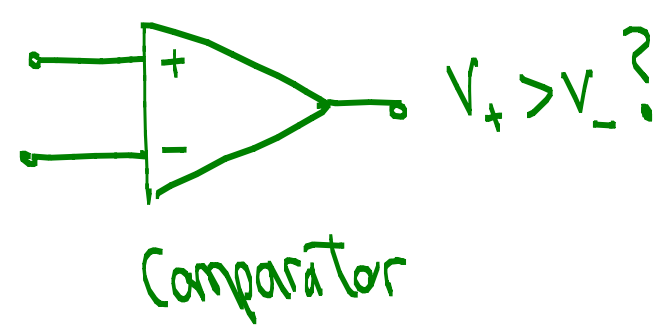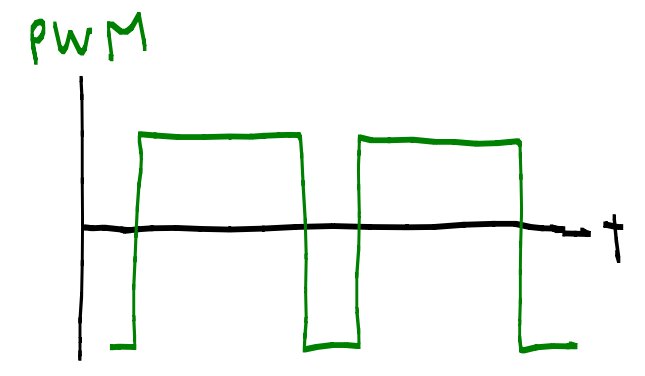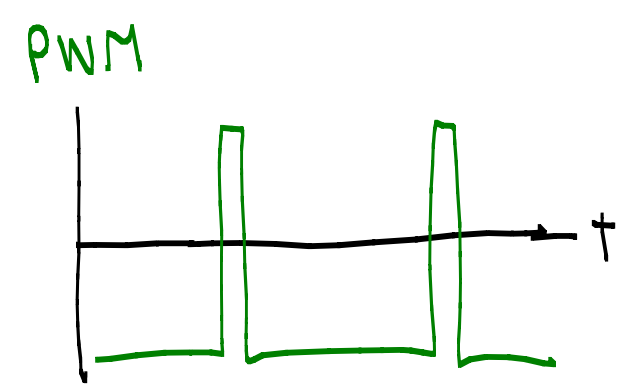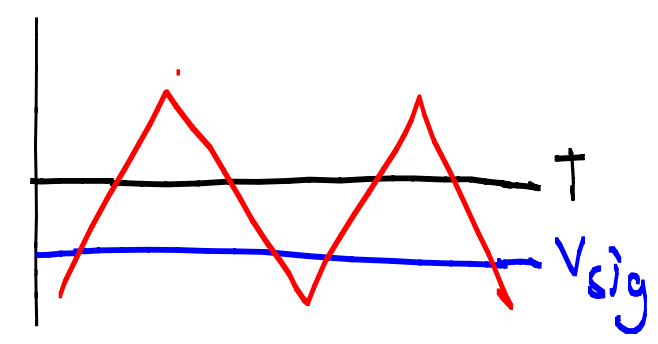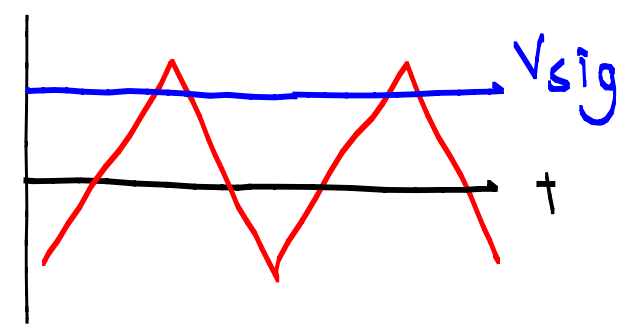to compare a triangle wave (or sawtooth) with a signal input




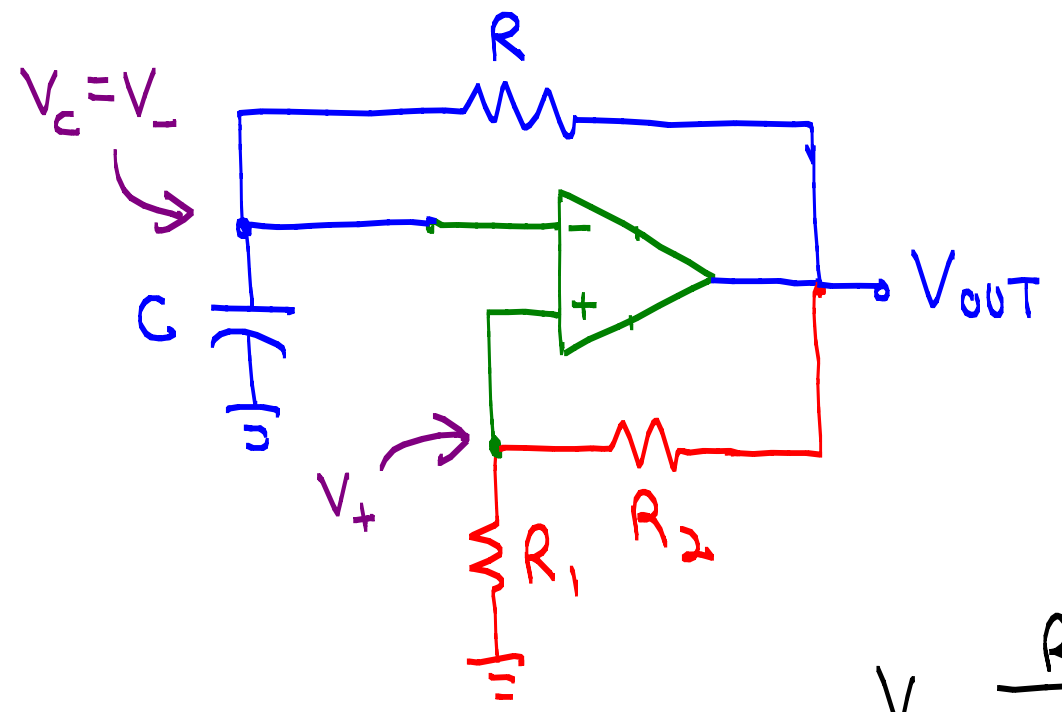2. Relaxation Oscillator

- Simple example of (+) feedback.
- Produces a square wave.




$$V_{sat} \frac{R_1}{R_1 + R_2}$$

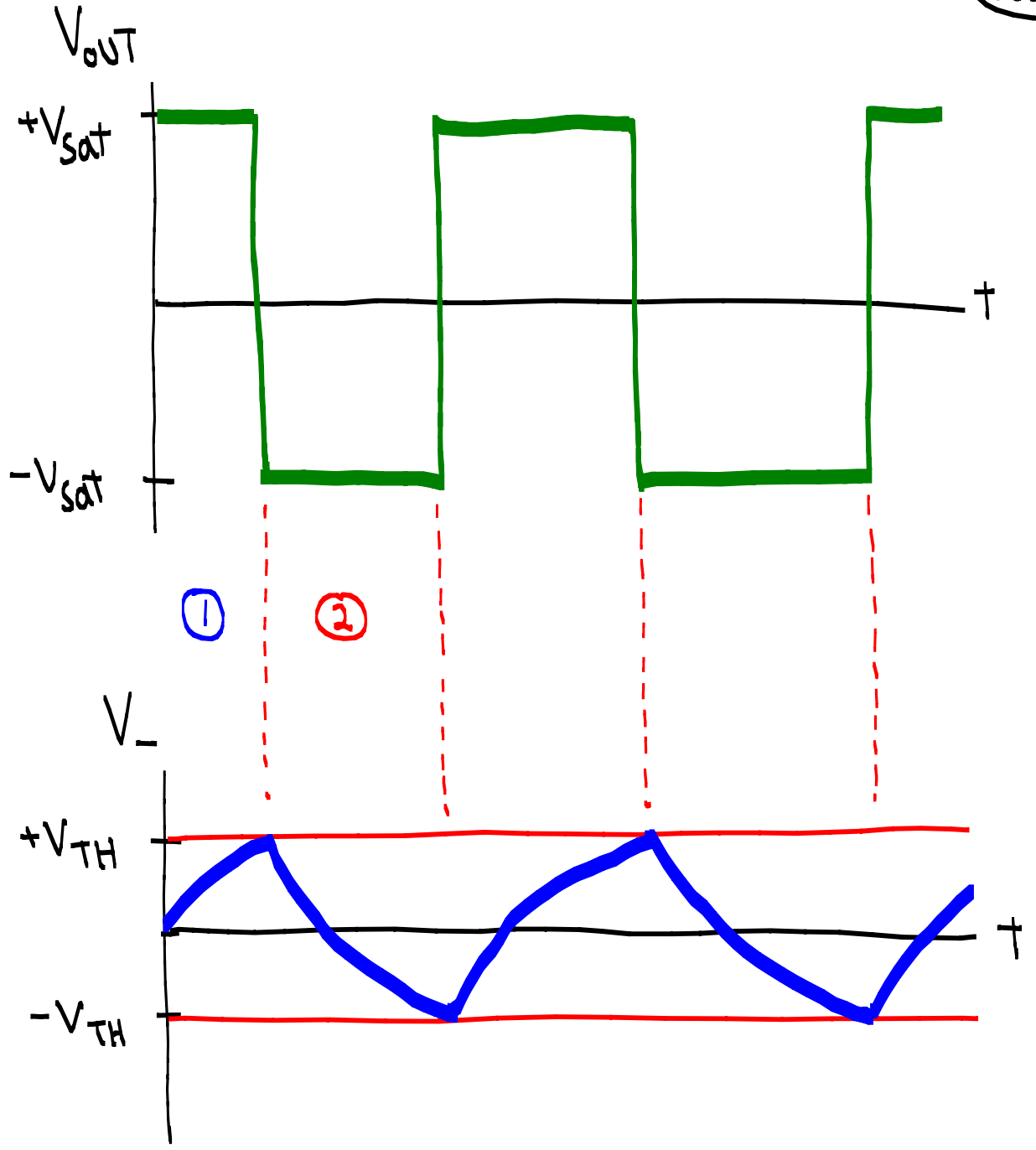

Q: How does this work?

→ Op amp is an ultra-high gain differential amplifier.

Ex:

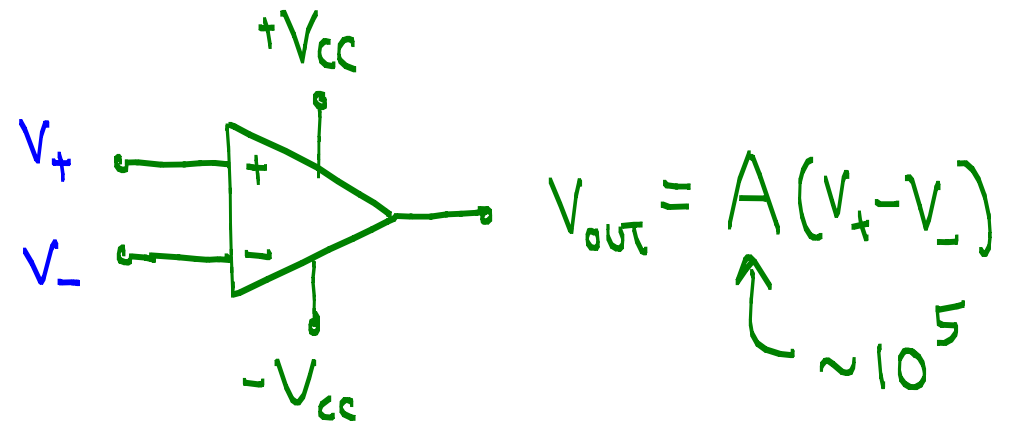


(A) If $V_+ > V_-$, then $V_{out} = +V_{sat}$

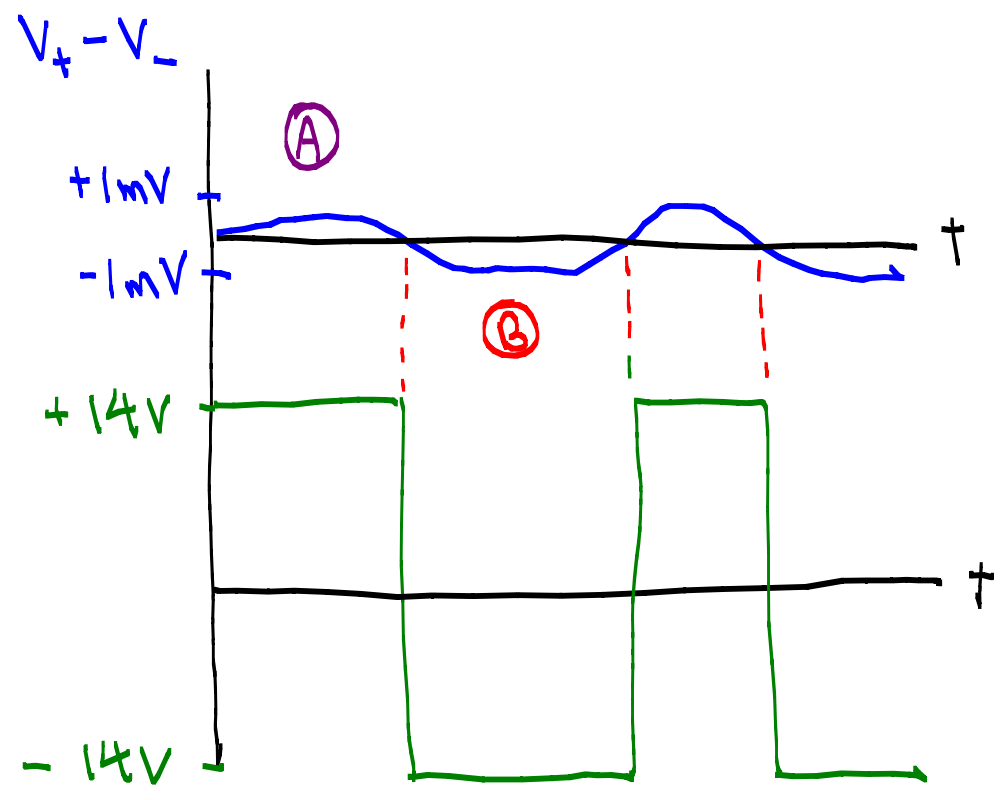(B) If $V_+ < V_-$, then $V_{out} = -V_{sat}$

Typically, $V_{sat} \approx V_{cc} - 1$

Ex: $V_{cc} = 15V \rightarrow V_{sat} = 14V$



Output only has 2 possible values.

• Start with Region ①:

Initially, $V_{out} = +V_{sat}$ and $V_c = 0$

$$\left. \begin{aligned}
 V_- = V_c = 0 \\
 V_+ = V_{sat} \frac{R_1}{R_1 + R_2} = +V_{TH}
 \end{aligned} \right\} V_+ - V_- > 0 \Rightarrow V_{out} = +V_{sat}$$


HOWEVER, the capacitor is charging up!

→ capacitor voltage starts to rise


→ As soon as V_c rises above $+V_{TH}$

⇒ $V_+ - V_- < 0$

⇒ V_{out} jumps to $-V_{sat}$!

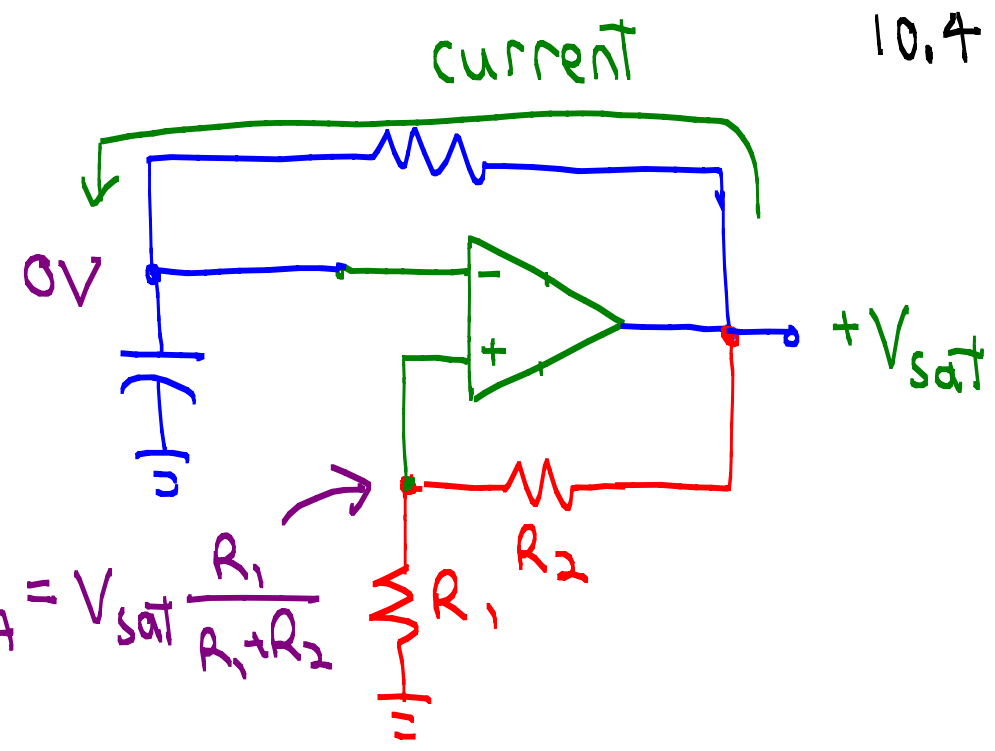
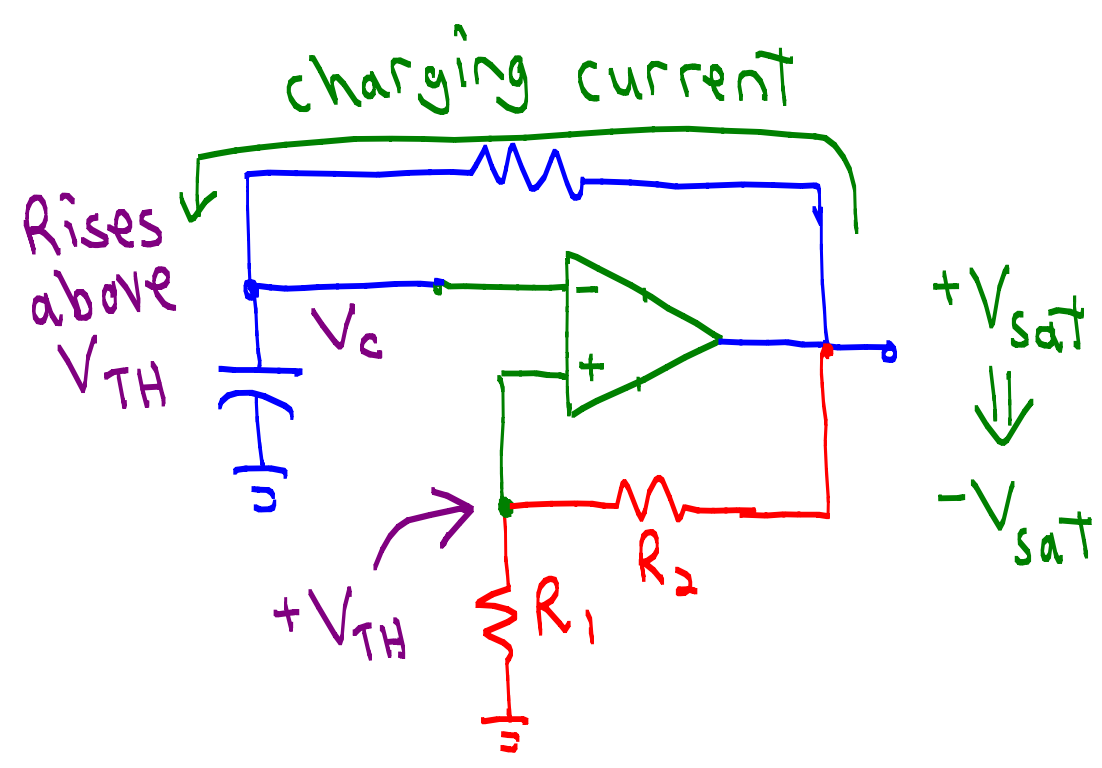
$$+V_{TH} = V_{sat} \frac{R_1}{R_1 + R_2}$$



• Now consider region ②:

Now have $V_{out} = -V_{sat}$ and $V_c = +V_{sat} \frac{R_1}{R_1 + R_2}$

$$\left. \begin{aligned} V_- &= V_c = +V_{TH} \\ V_+ &= -V_{sat} \frac{R_1}{R_1 + R_2} = -V_{TH} \end{aligned} \right\} \begin{aligned} V_+ - V_- &< 0 \\ \Rightarrow V_{out} &= -V_{sat} \end{aligned}$$



HOWEVER, the capacitor is discharging!

→ capacitor voltage starts to fall

⇒ As soon as V_c dips below $-V_{TH}$

⇒ $V_+ - V_- > 0$



⇒ V_{out} jumps to $+V_{sat}$

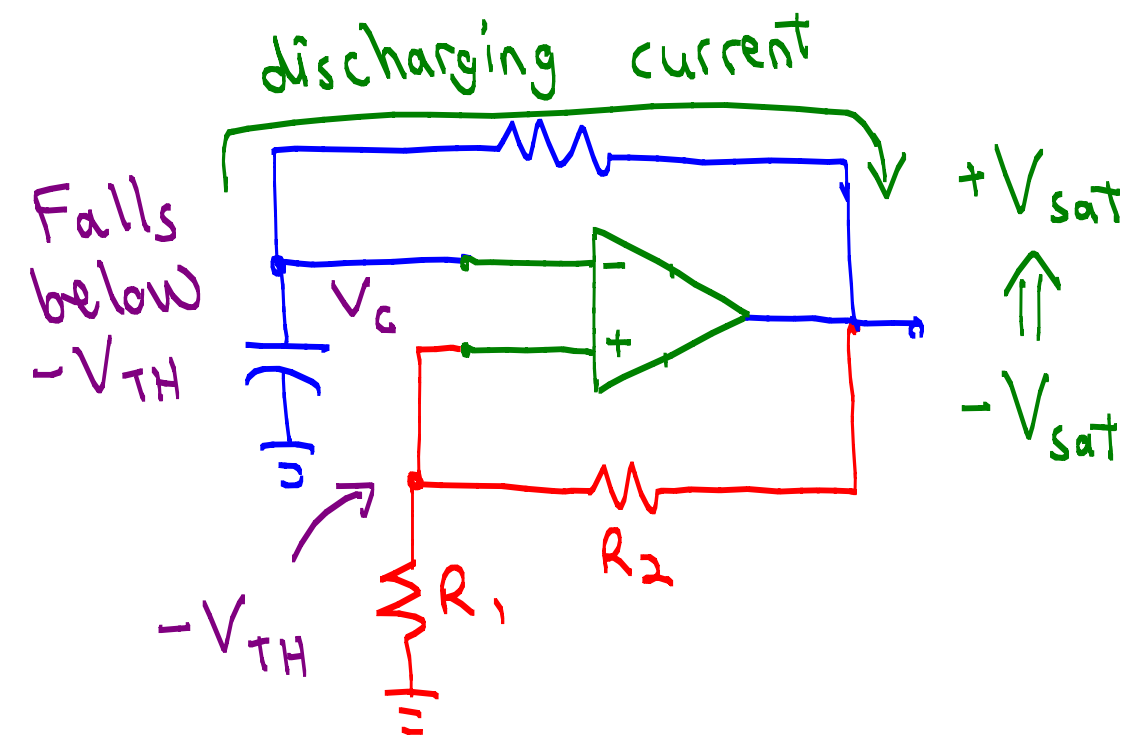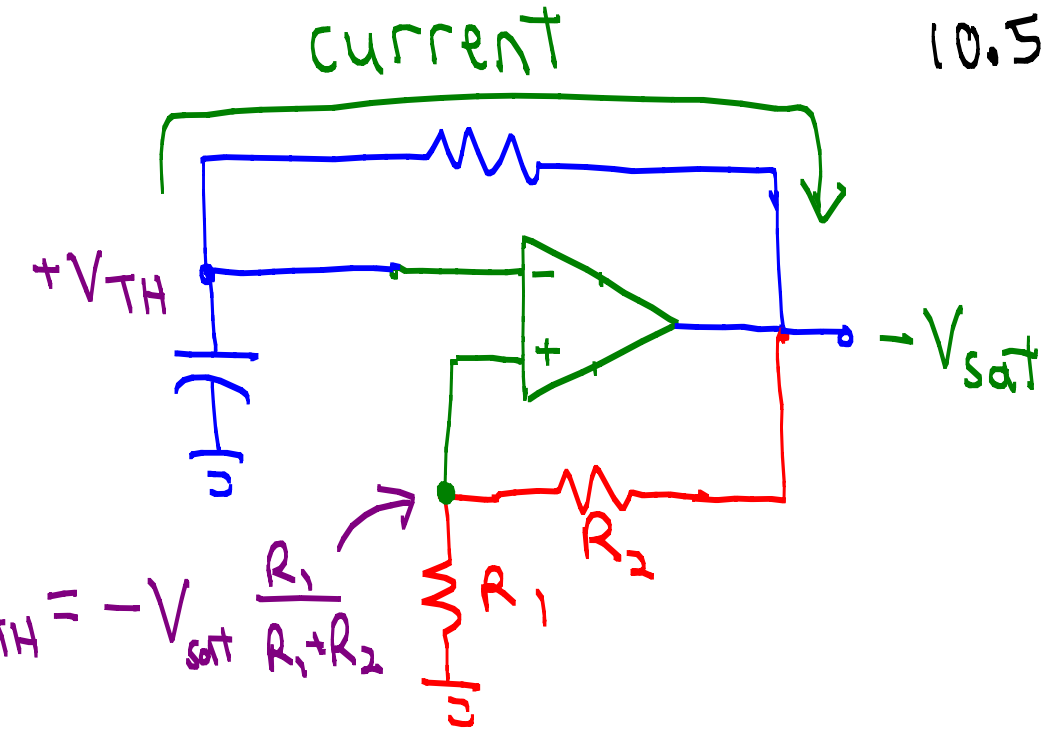

• Period?

$$T = 2RC \ln \left(\frac{1+B}{1-B} \right)$$

$$B = \frac{R_1}{R_1 + R_2}$$

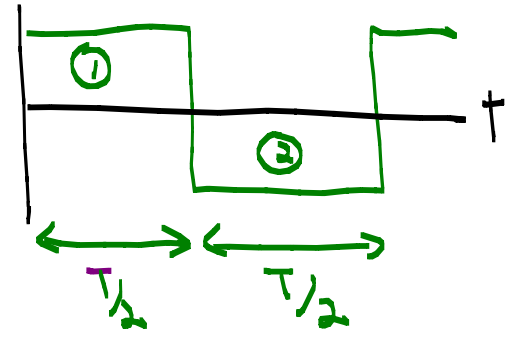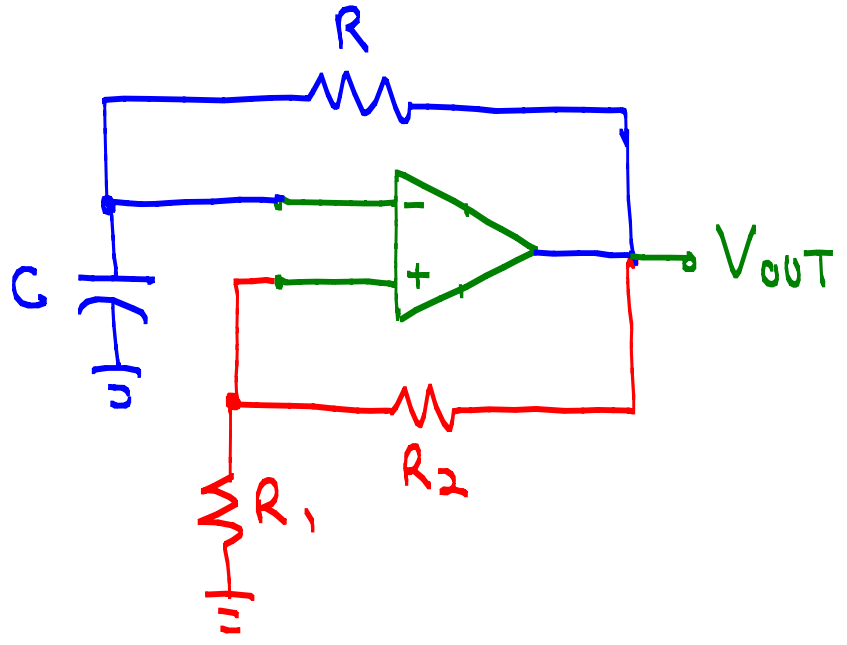


Ex: $R_1 = 18K$
 $R_2 = 2K$
 $C = 0.1 \mu F$
 $R = 1K$

$$B = \frac{18K}{18K + 2K} = 0.9$$


$$T = 2(10^3 \Omega)(10^{-7} F) \ln \left(\frac{1+0.9}{1-0.9} \right)$$
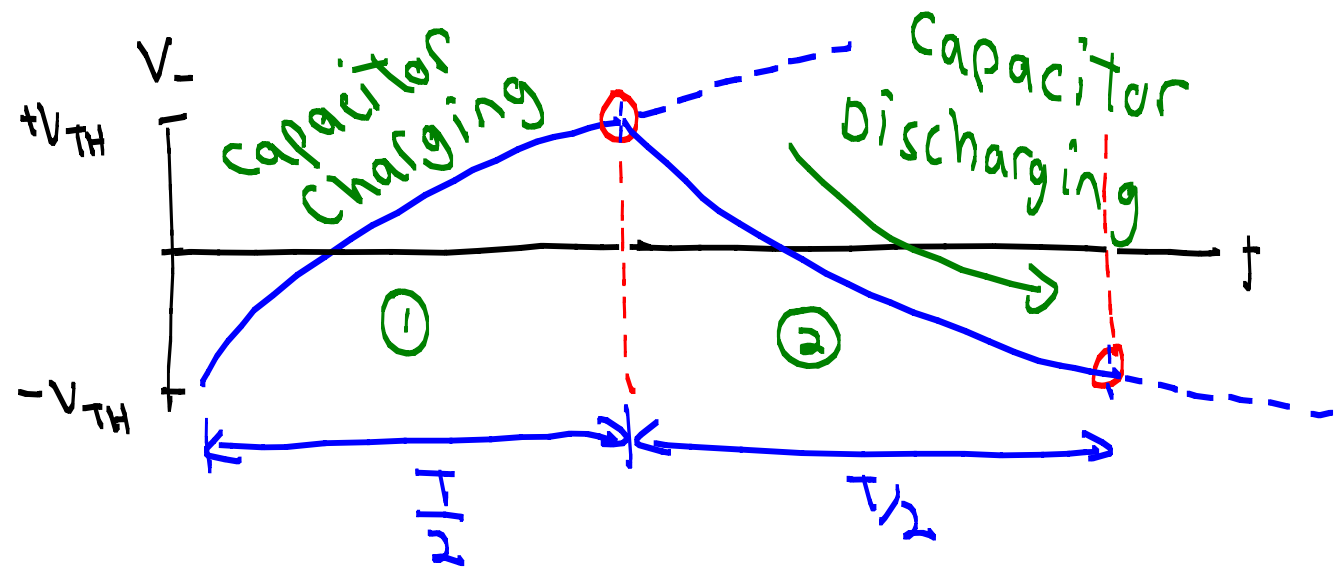
$$= 589 \mu s \quad (f = 1.7 \text{ kHz})$$



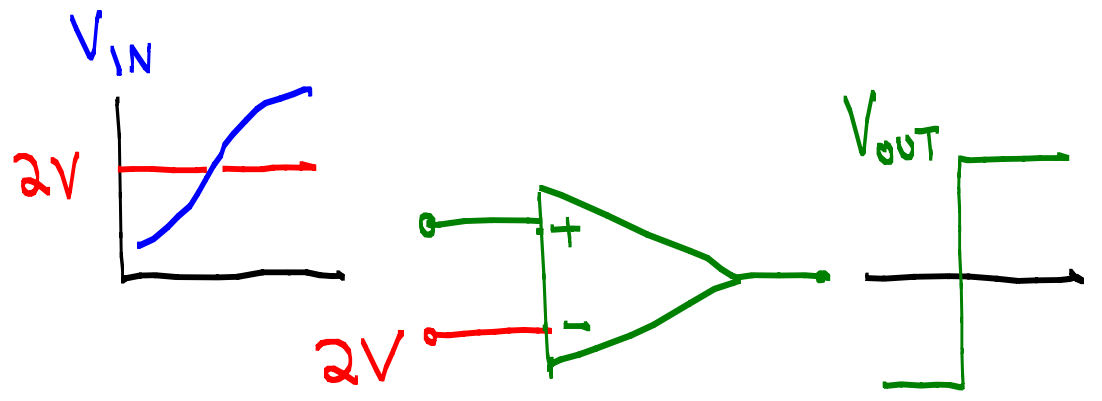3. Schmitt Trigger

- An open loop op amp can be used as a threshold detector.




e.g. ($V_{TH} = +2V$)

$$V_{IN} > 2V \rightarrow V_{OUT} = +V_{SAT}$$

$$V_{IN} < 2V \rightarrow V_{OUT} = -V_{SAT}$$

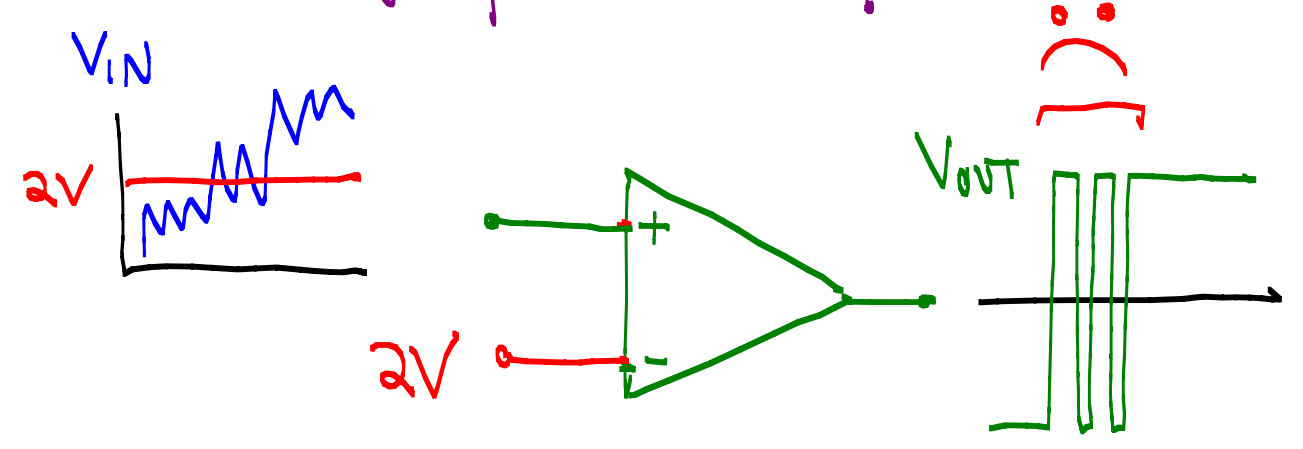- Problem with this circuit...
 → noise can make V_{OUT} very erratic!




Q: How to make V_{OUT} less susceptible to noise?


⇒ Need to include some hysteresis!

• Threshold detector with hysteresis

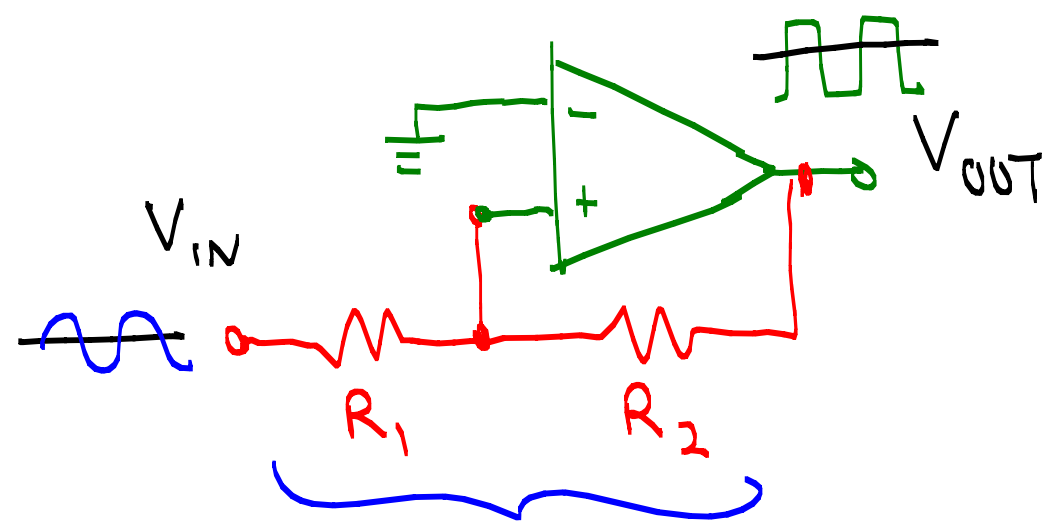→ Value of V_{OUT} depends on whether V_{IN} crosses V_{TH} from below or above.



"Non-inverting Schmitt Trigger"

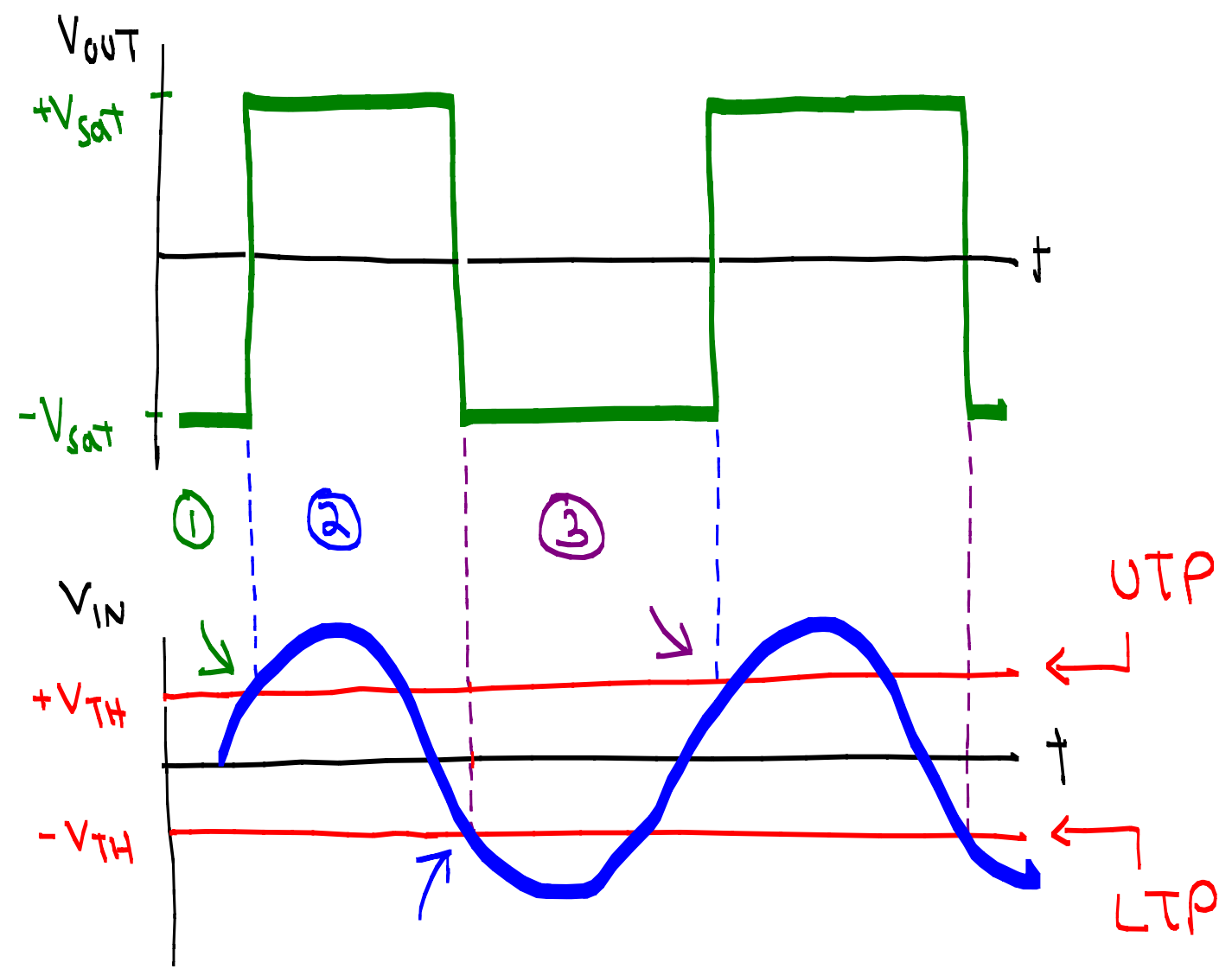

UTP \equiv Upper Trip Point
LTP \equiv Lower Trip Point

How does this work? Assume V_+ draws no current...

Region ①: $V_{out} = -V_{sat}$

(V_{in} approaches UTP from below)

• While $V_{in} < UTP$,

then $V_+ < 0V \Rightarrow V_{out} = -V_{sat}$


• When V_{in} rises above UTP,

then $V_+ > 0V \Rightarrow V_{out}$ jumps to $+V_{sat}$!


What is the UTP?

$$i = \frac{UTP - 0}{R_1} = \frac{0 - (-V_{sat})}{R_2} \Rightarrow \boxed{UTP = \frac{R_1}{R_2} V_{sat}}$$


$V_{in} < UTP$

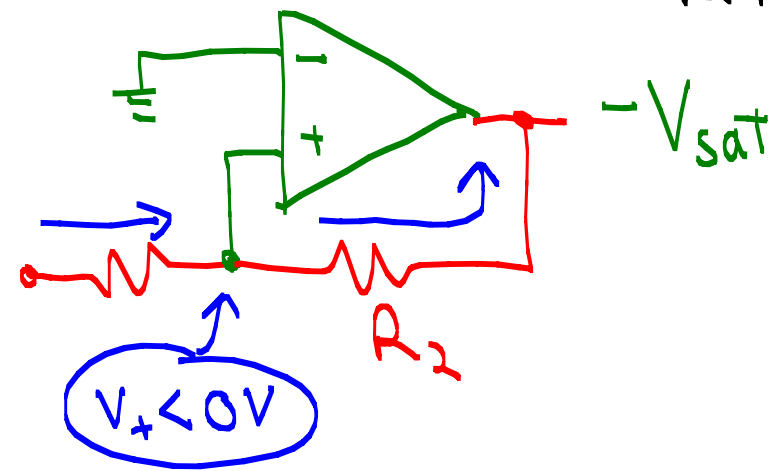

$V_{in} = UTP$

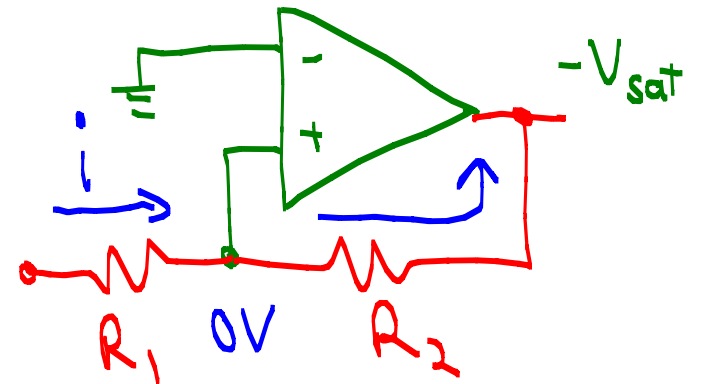

$V_{in} > UTP$

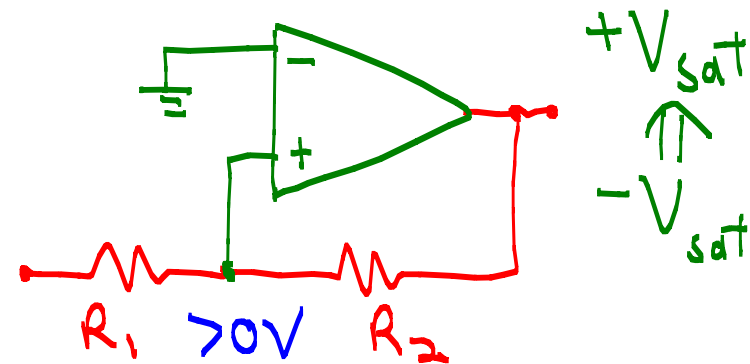

Region ②: $V_{out} = +V_{sat}$

- V_{out} does NOT change, even if V_{in} dips below UTP because V_+ is still > 0 !


- When V_{in} sinks below LTP, then $V_+ < 0 \Rightarrow V_{out}$ jumps to $-V_{sat}$!

$$LTP? : i = \frac{0 - LTP}{R_1} = \frac{V_{sat} - 0}{R_2} \Rightarrow \boxed{LTP = -\frac{R_1}{R_2} V_{sat}}$$


Region ③: $V_{out} = -V_{sat}$

- V_{out} remains same, even if V_{in} rises above LTP.
- V_{out} flips when $V_{in} > UTP \dots$


$V_{in} < UTP$

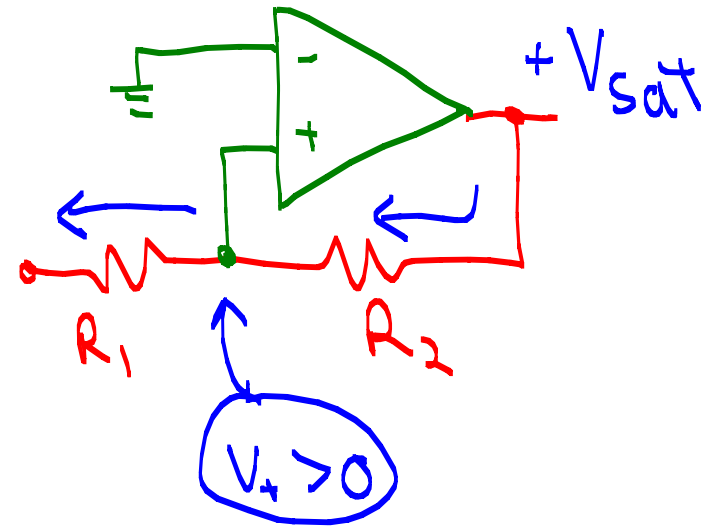

$V_{in} = LTP$

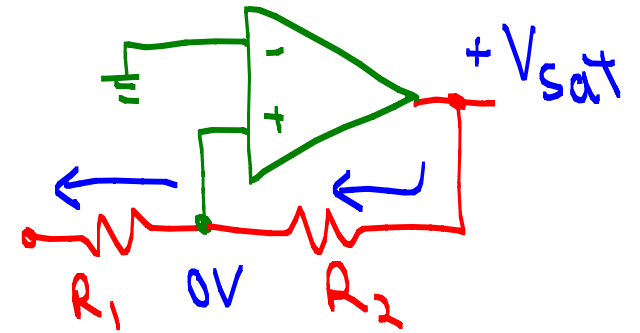

$V_{in} < LTP$

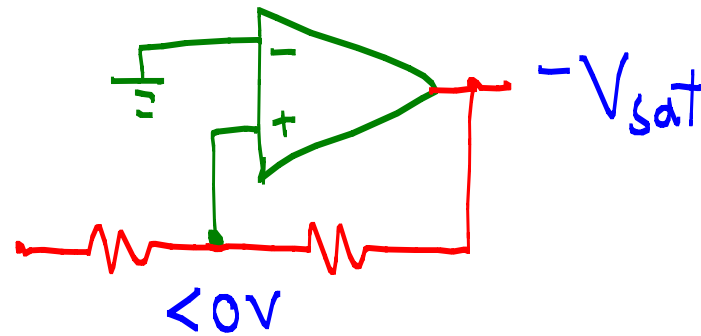

• Noise immunity with Schmitt trigger

