

Lecture 10: Schmitt Trigger

0. Review

1. Intro

2. Relaxation Oscillator

3. Schmitt Trigger

- PreLab 4 due today
- HW4 due Fri (Oct 25)
- Exam #1 re-do } next Tue (Oct 29)
Quiz
- Lab 3 report due Nov 04 (Mon)


Textbook Reading:

- Ch 20-1 Comparators with zero reference
- 20-3 Comparators with hysteresis
- 20-7 Waveform Generation




0. Review

MOSFET switches

NMOS

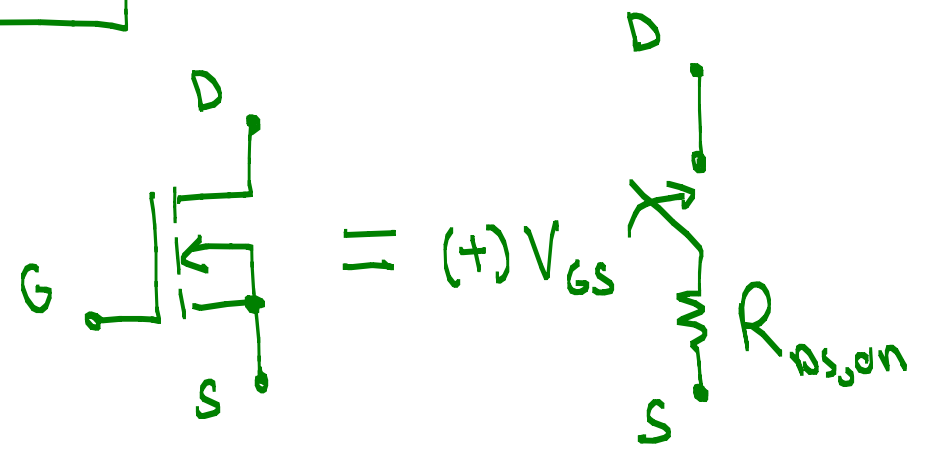

PMOS

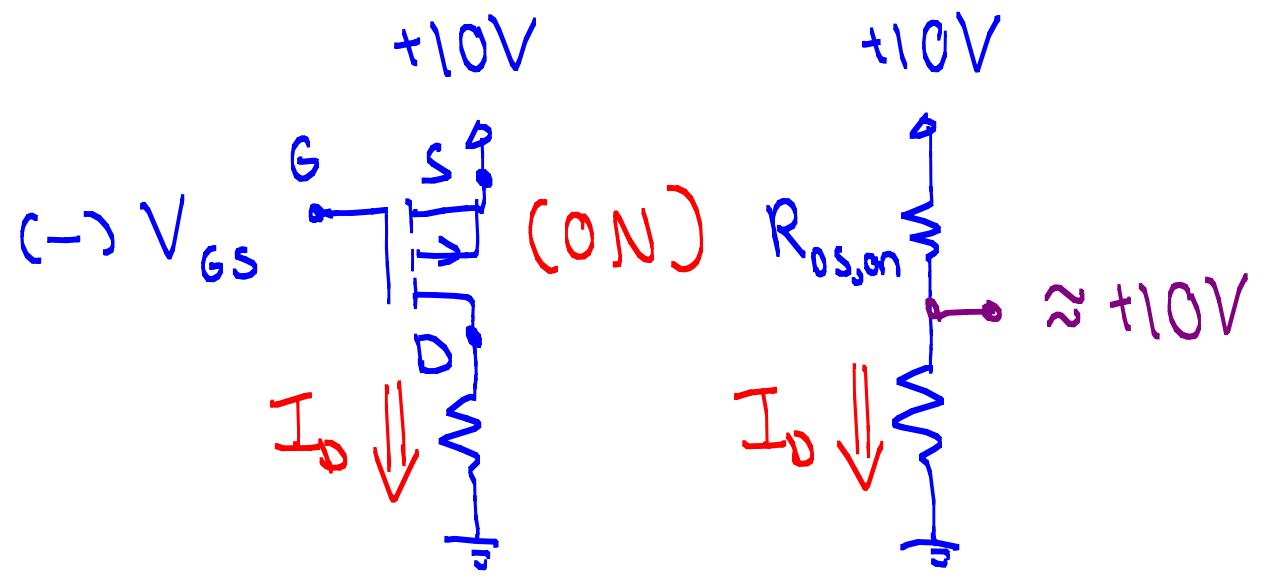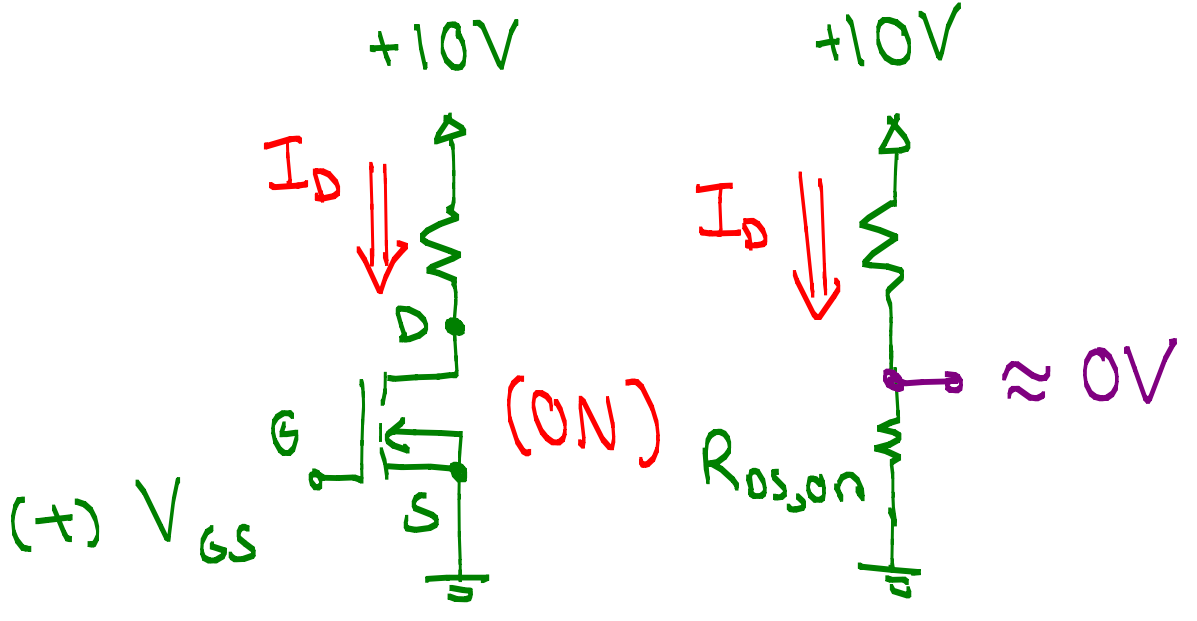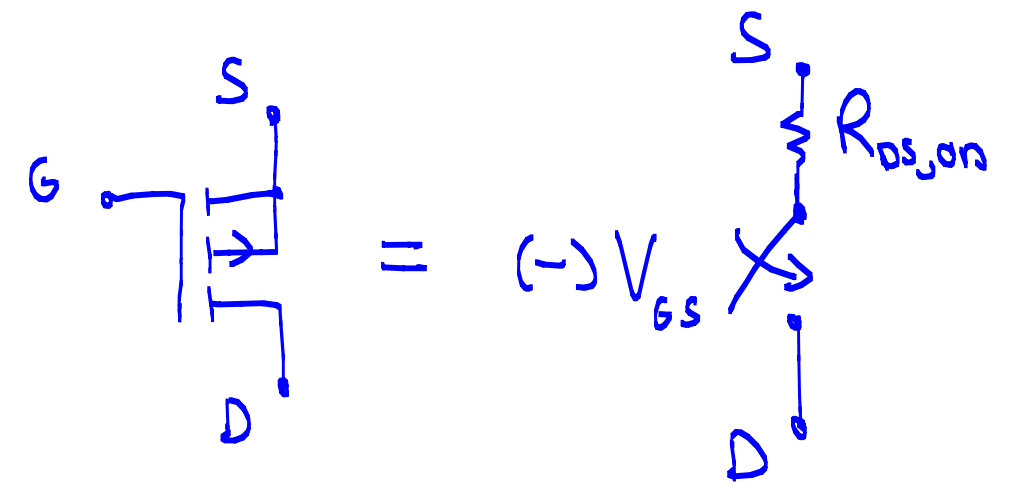


1. Intro

- Unlike amplifiers, waveform generators use positive feedback!


Negative Feedback

Ex:

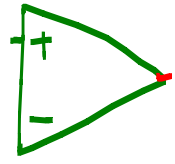


Positive Feedback

Ex:



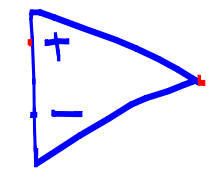


Example Pulse Width Modulation (PWM)

• Many applications!


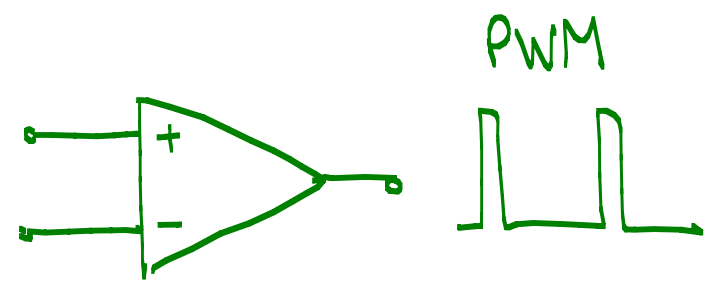


Q: How to implement PWM?

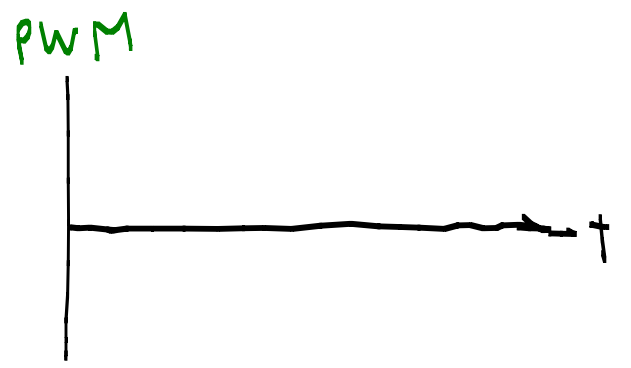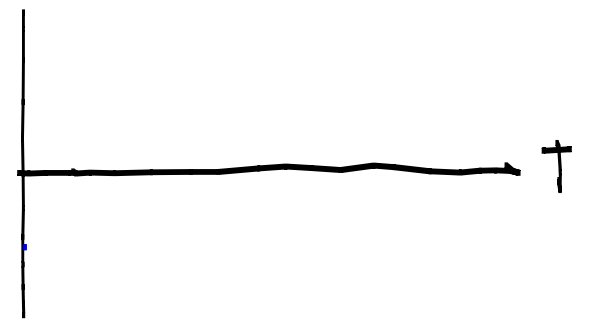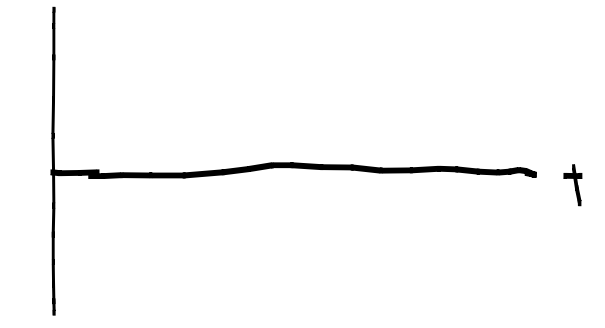

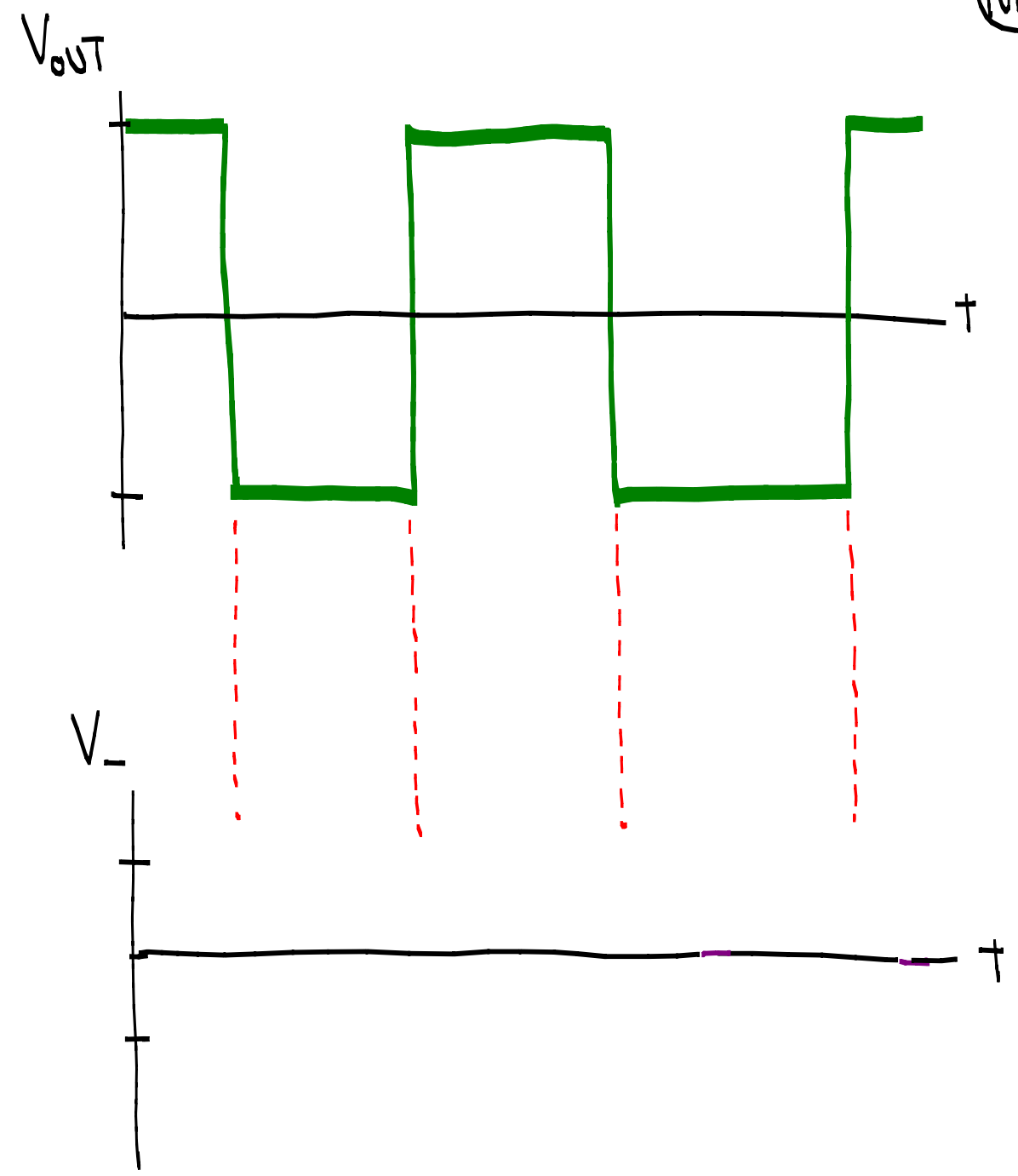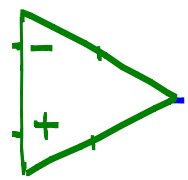2. Relaxation Oscillator

- Simple example of (+) feedback.
- Produces a square wave.




Q: How does this work?

→ Op amp is an ultra-high gain differential amplifier.


Ⓐ If $V_+ > V_-$

Ⓑ If $V_+ < V_-$

Ex:

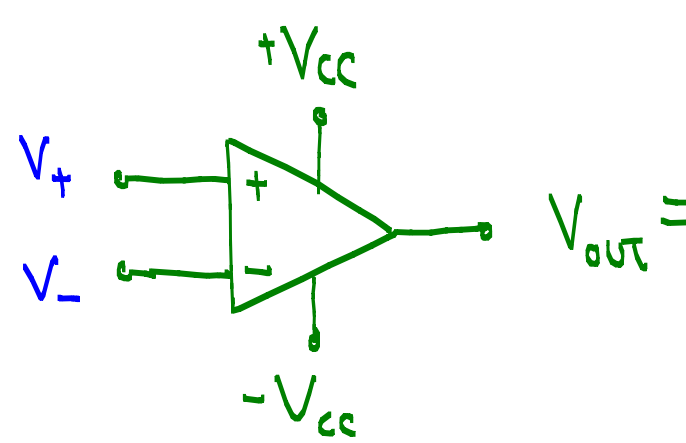

10.3


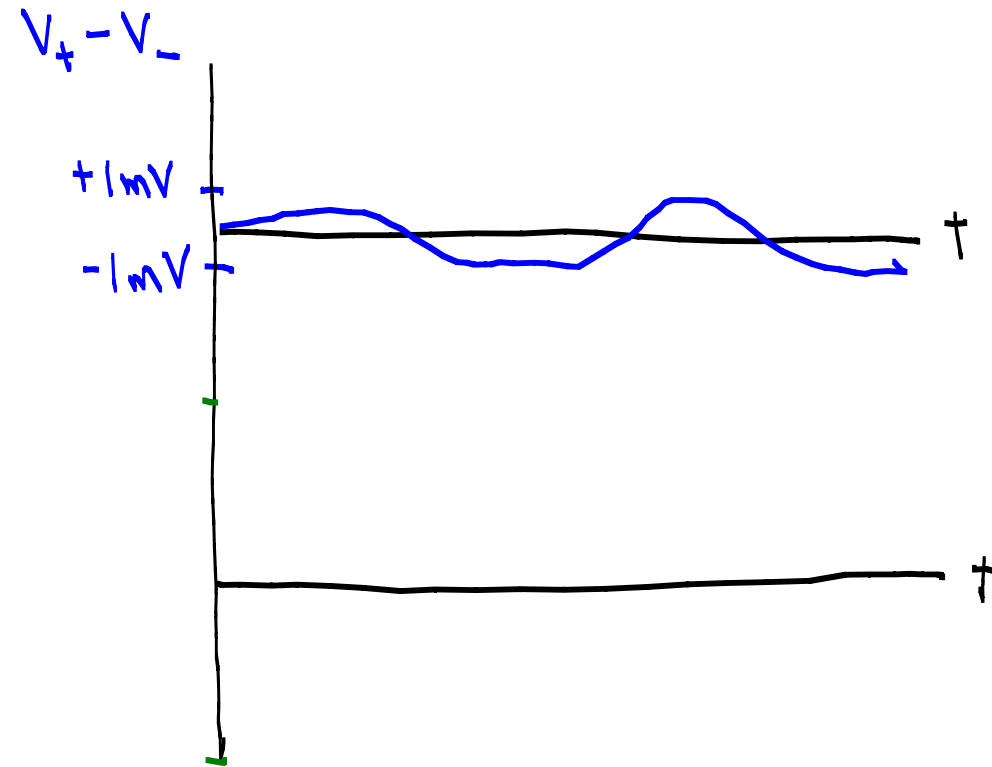


• Start with Region ①:

Initially, $V_{out} = +V_{sat}$ and $V_c = 0$

$$V_- =$$

$$V_+ =$$

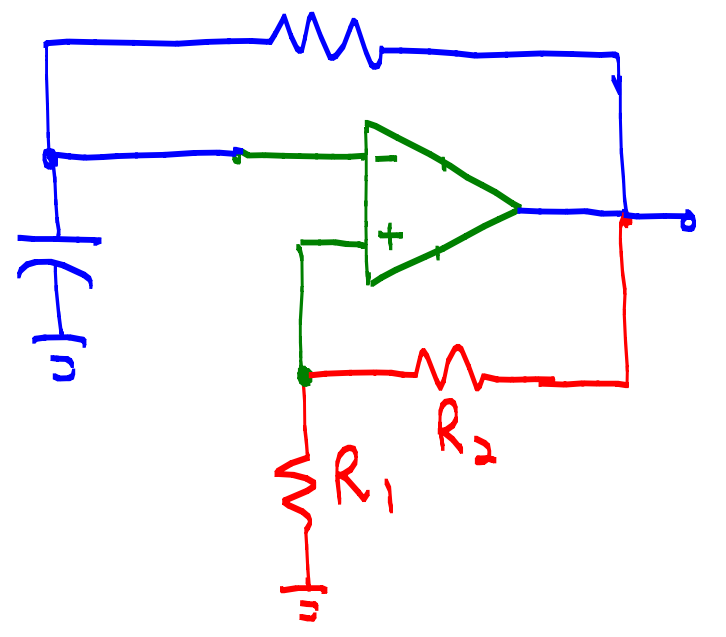
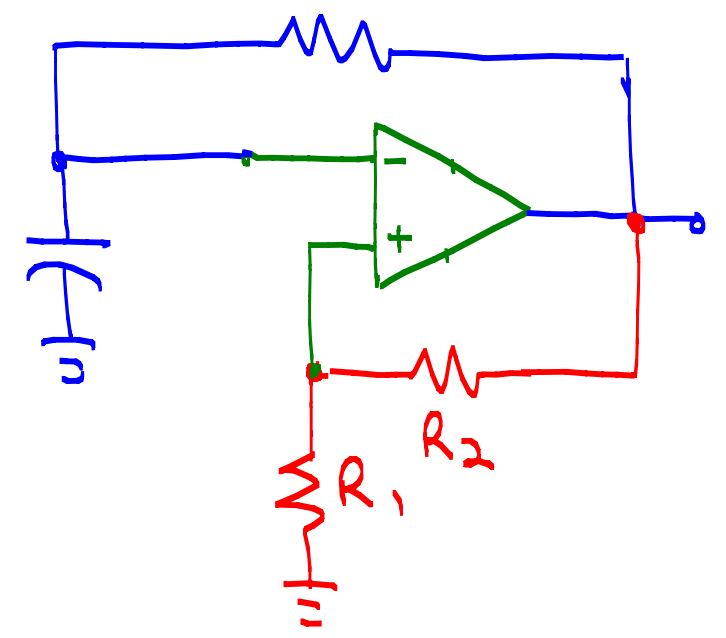


• Now consider region ②:

Now have $V_{out} = -V_{sat}$ and $V_c = +V_{sat} \frac{R_1}{R_1 + R_2}$

$$V_- =$$


$$V_+ =$$

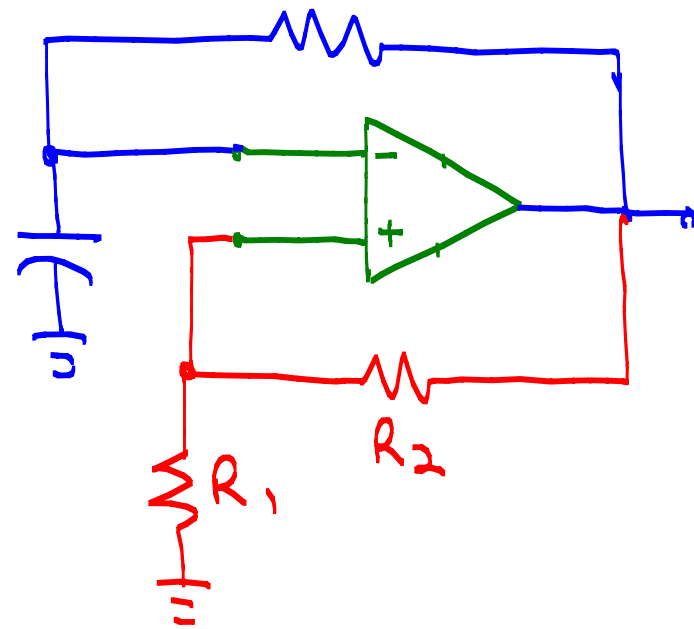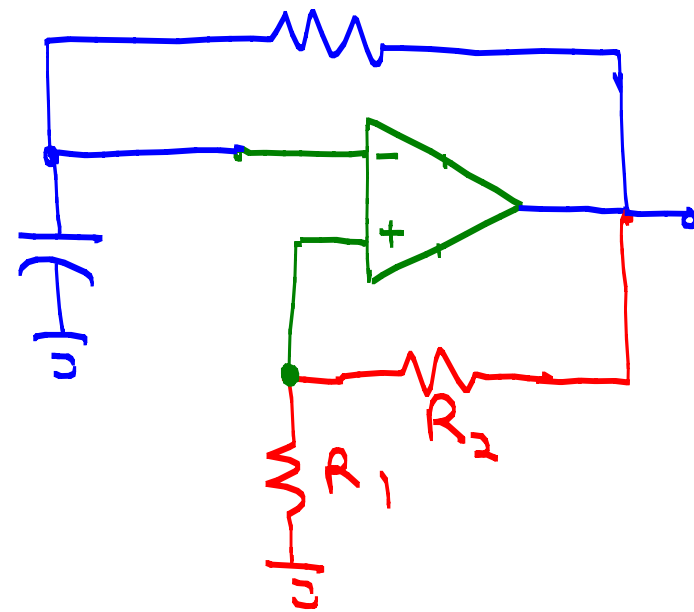


• Period?

$T =$

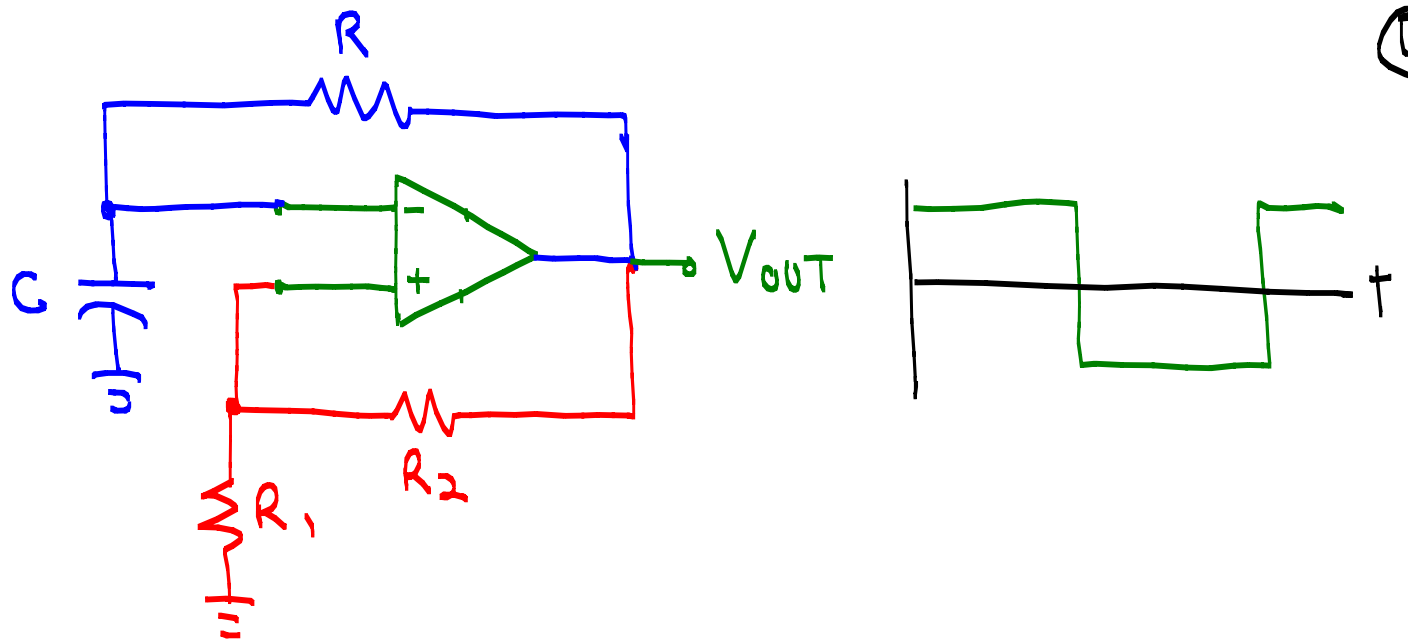Ex: $R_1 = 18K$
 $R_2 = 2K$
 $C = 0.1\mu F$
 $R = 1K$




10.6

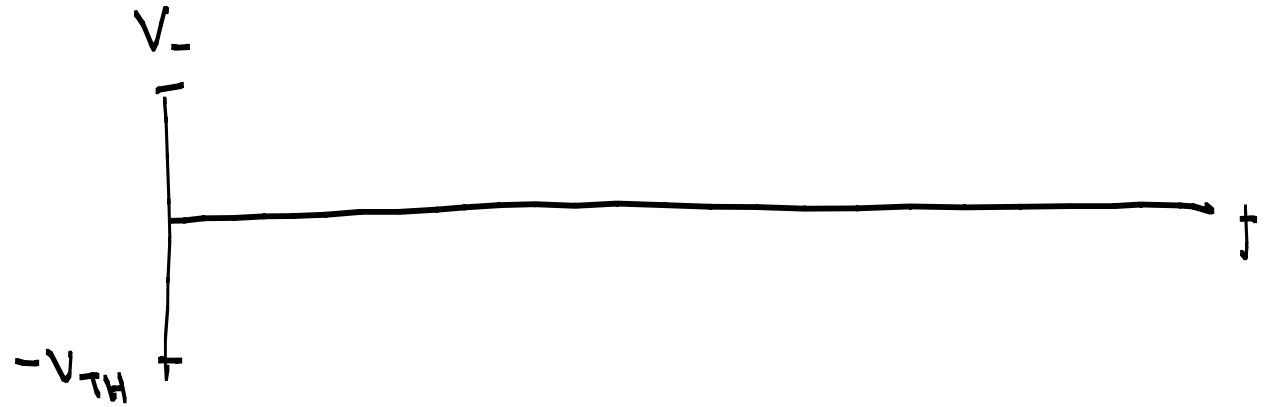

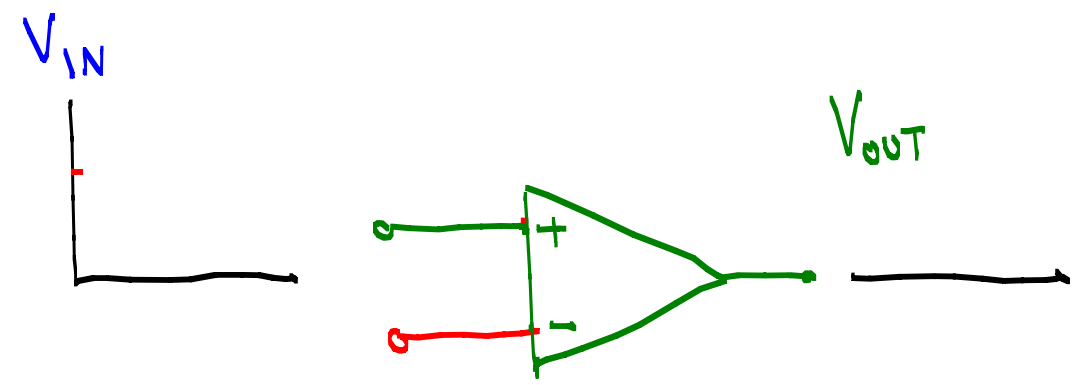
3. Schmitt Trigger

- An open loop op amp can be used as a _____.



e.g.



- Problem with this circuit... 10.7

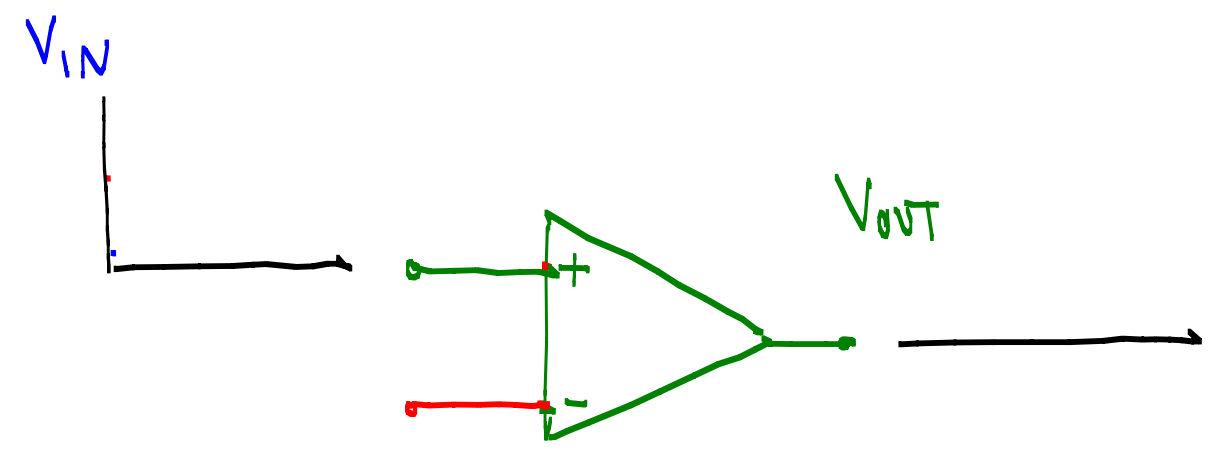

Q:

• Threshold detector with hysteresis

→ Value of V_{OUT} depends on

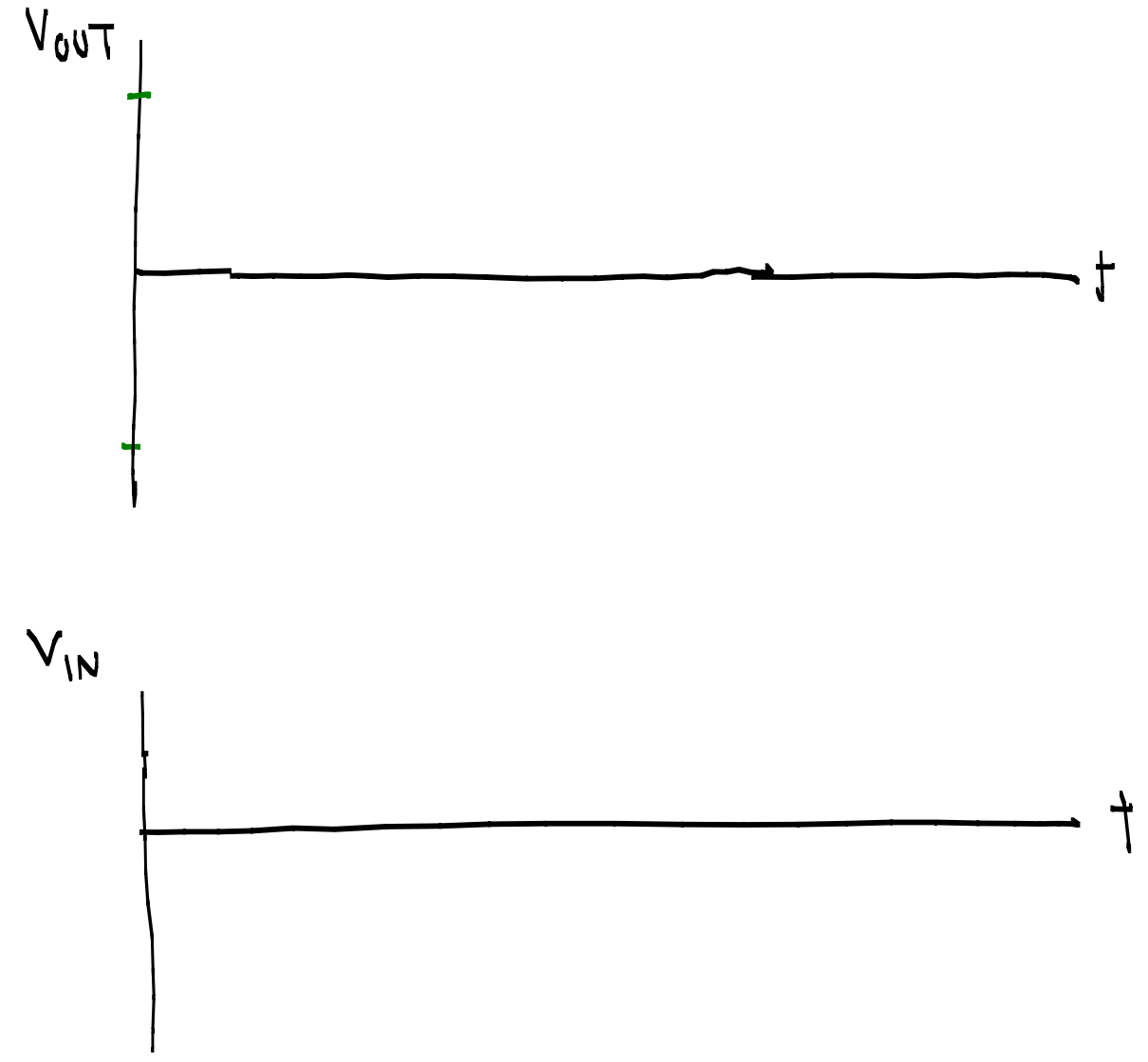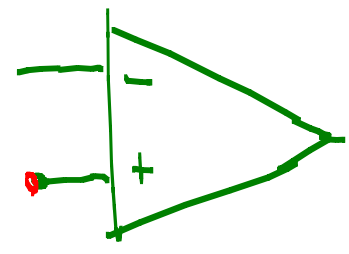

How does this work? Assume V_+ draws no current...




Region ①: $V_{out} = -V_{sat}$

(V_{in})

• While V_{in}
then V_+

• When V_{in}
then V_+




what is the UTP?

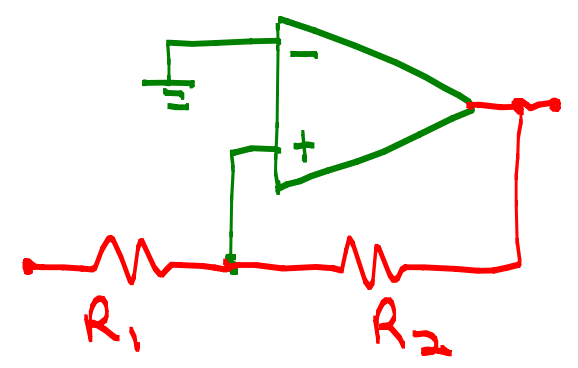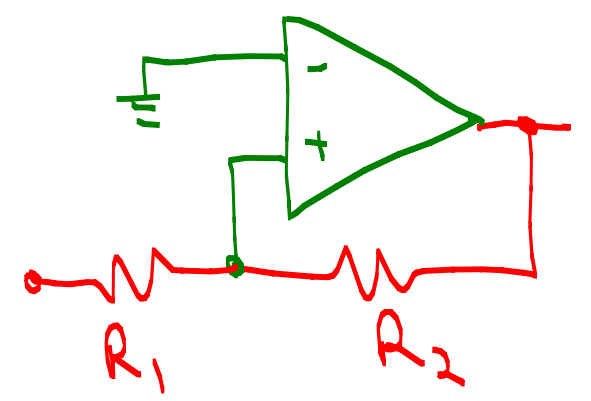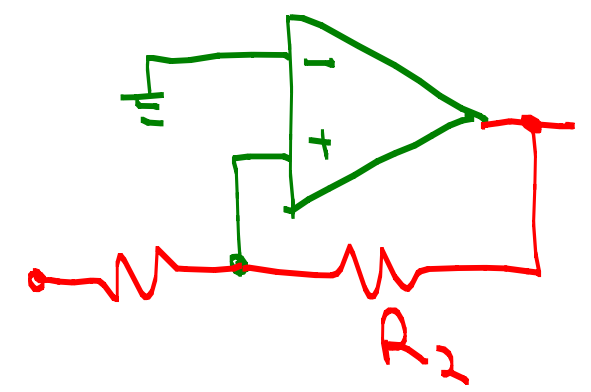

Region ②: $V_{out} = +V_{sat}$

- V_{out}

- When V_{in}
then V_+

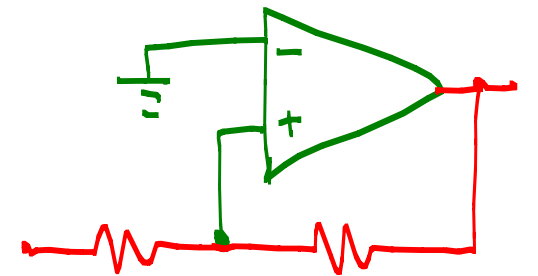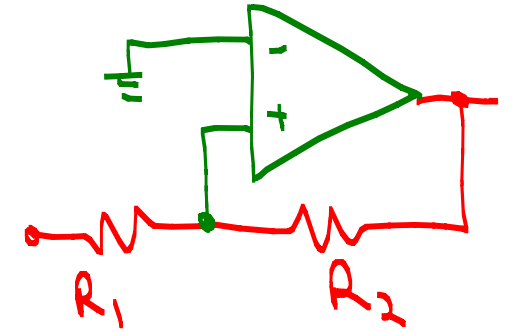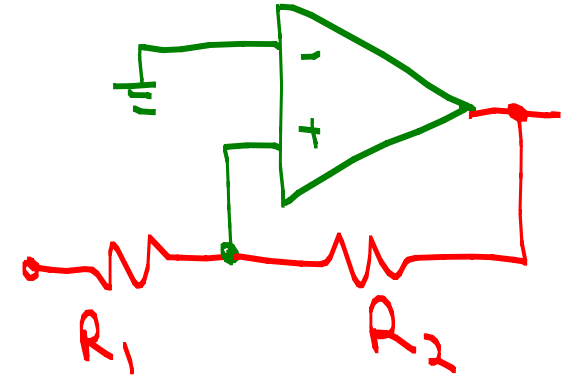


LTP?

Region ③: $V_{out} = -V_{sat}$


- V_{out}

- V_{out}

• Noise immunity with Schmitt trigger

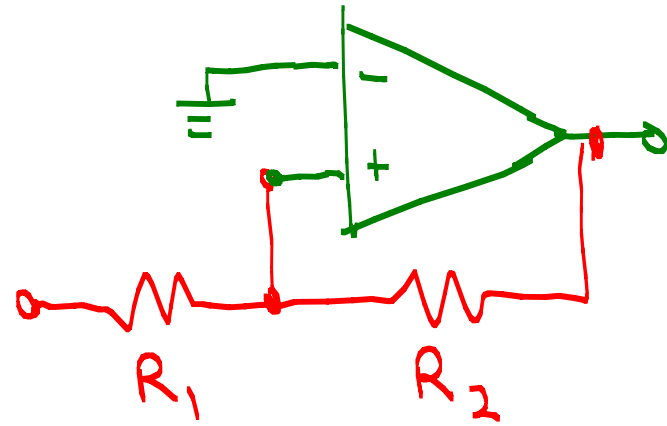

V_{IN}

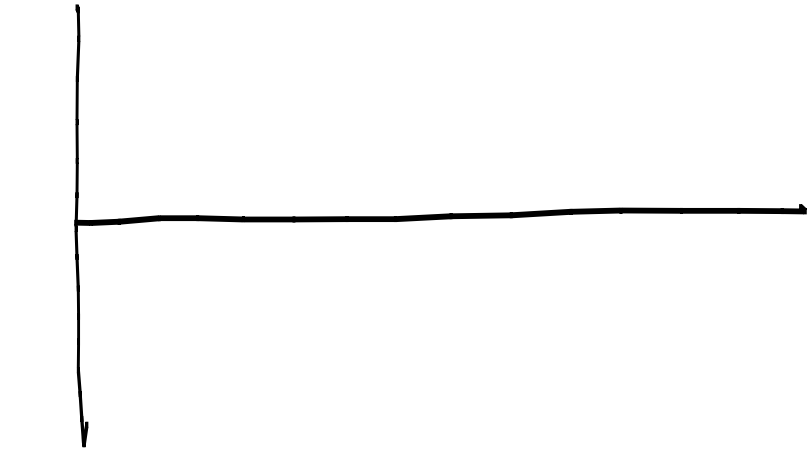

V_{OUT}

