

Lecture 12: Differential Amplifier (Part 1)

0. Review

1. Intro

2. Long-tail Pair

3. Input Impedance

4. Output Impedance

Textbook reading:

15-1 The differential amplifier

15-2 DC analysis

15-3 AC analysis

- HW 5 due Fri (Nov 01)

- PreLab 5 due today

- Team Project (2-3 people)

- Choose from 3 topics

- Determine responsibilities
(who does what circuit)

- Formulate design requirements
(e.g. servo pulse freq)

- "Rough" circuit schematics
(no component values)


- Lab 3 report due Nov 4 (Mon)

- Exam # 2 (Nov 12) !


0. Review

- Triangle Wave Generator using op amps


Split Supply

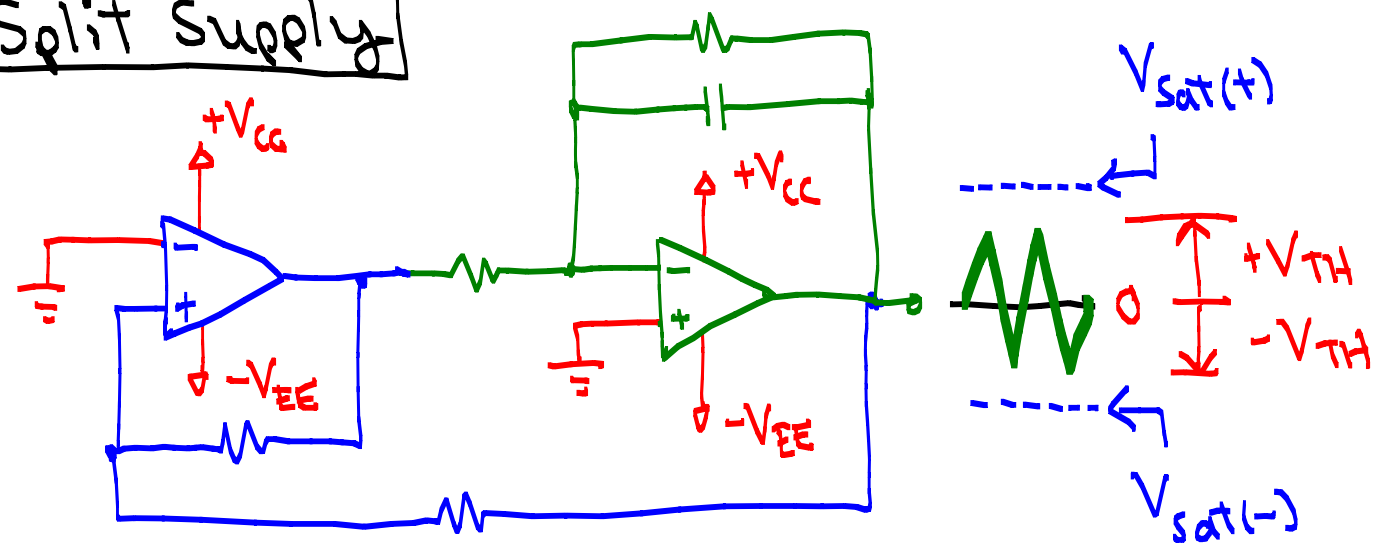

Single Supply

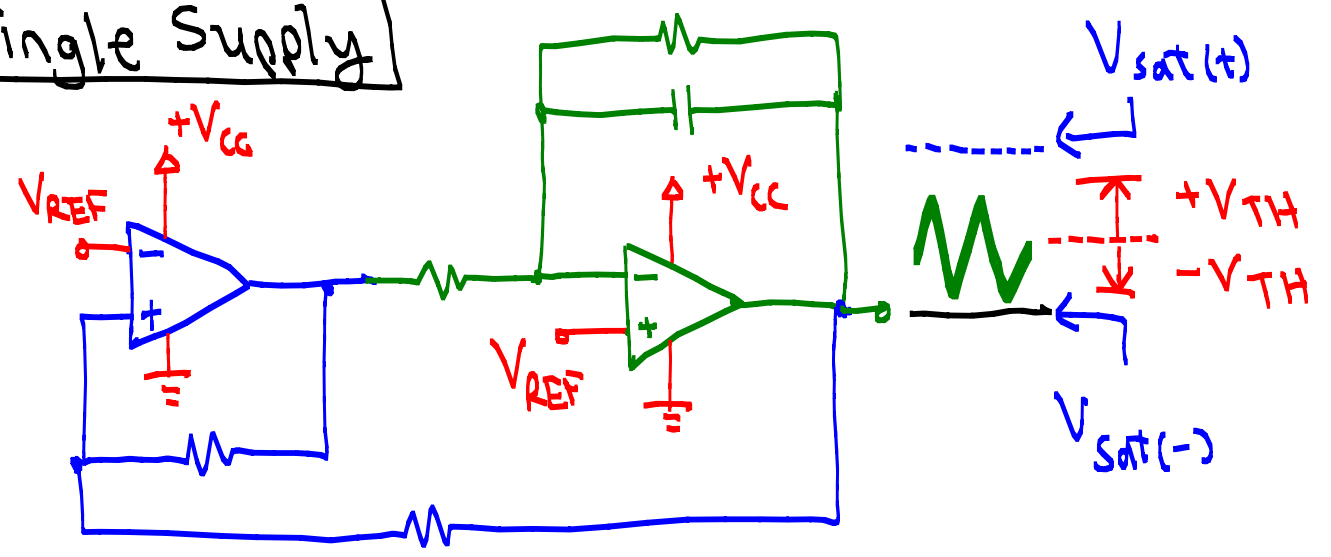

- Sawtooth Generator using 555 timer:

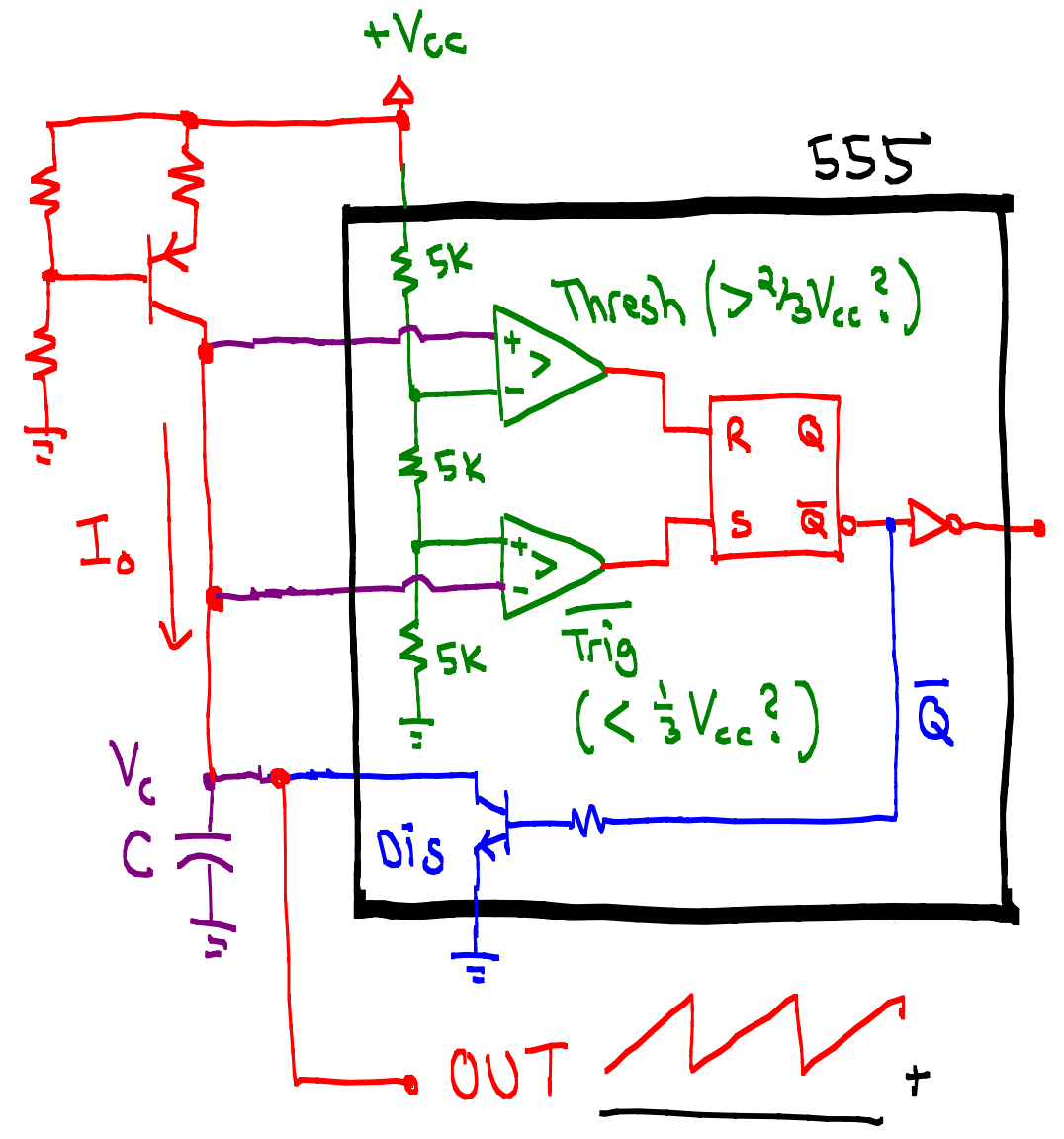

Design example


Triangle Wave w/ single-supply op amps

12.0a

$f = 1 \text{ KHz}, 6 \text{ V}_{pp}$

$V_{CC} = 9\text{V}$ $+V_{sat} = V_{CC} - 1$
 $-V_{EE} = 0\text{V}$ $-V_{sat} = 0$

single supply op amp (e.g. LM358)

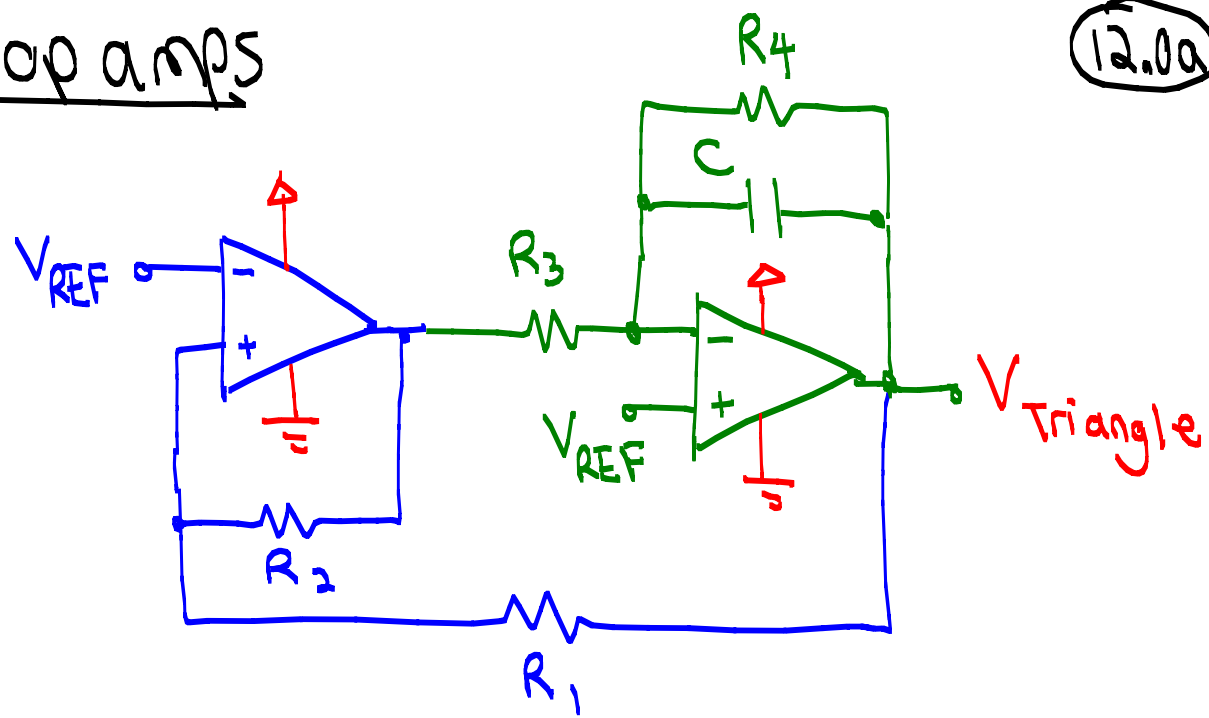


$$\textcircled{1} V_{TH} = \frac{R_1}{R_2} \times 0.5 V_{sat} = 3\text{V}$$

$$\frac{9-1}{2} = 4\text{V} \quad V_{REF} = 0.5 V_{sat}$$

$\rightarrow \frac{R_1}{R_2} = 0.75$

Typically, $R_2 \sim 100 \text{ k}$ range

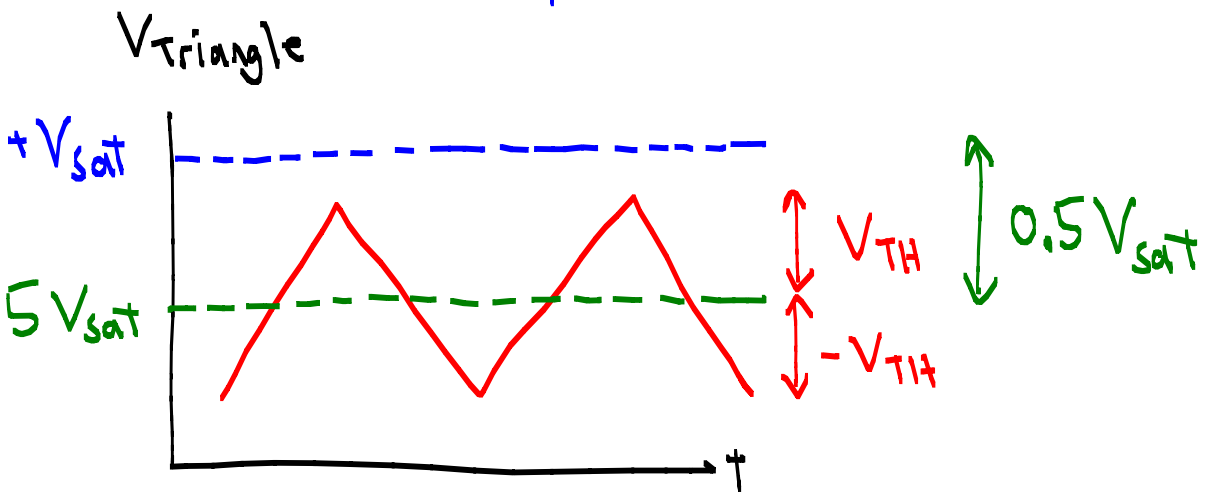Choose $R_1 = 75 \text{ K}$
 $R_2 = 100 \text{ K}$



② $f = \frac{R_2}{4R_1 R_3 C} = \frac{100K}{4 \times 75K \times R_3 C} = 1000 \text{ Hz} \rightarrow R_3 C = 3.333 \times 10^{-4} \text{ s}$

12.0b

Typically $C < 0.1 \mu\text{F}$ and $R_3 \sim 100 \text{ K}$:

R_3	C	$C_{5\%}$	ΔC
100K	3333 pF	3300 pF	33 pF
110K	3030	3000	30 ←
120K	2778	2700	78
130K	2564	2400	164

$$\frac{100K}{4 \times 75K \times (110K)(3000 \text{ pF})} = 1010.1 \text{ Hz}$$

(within 1%)

③ Choose $R_4 > 10 R_3$ (or higher)

→ $R_4 = 1.5 \text{ M}$ (limit to few $\text{M}\Omega$ or less)

$$\textcircled{4} \quad V_{REF} = 0.5 (V_{sat(+)} - V_{sat(-)})$$

$$= 0.5 (8 - 0) = \underline{\underline{4V}}$$


$$\rightarrow 9 \cdot \frac{R_6}{R_5 + R_6} = 4V$$

$$\frac{4}{9} R_6 = R_5 + R_6$$

$$\frac{4}{9} R_6 = 1.25 R_6 = R_5$$



Typically, $R_6 \sim 100K$:

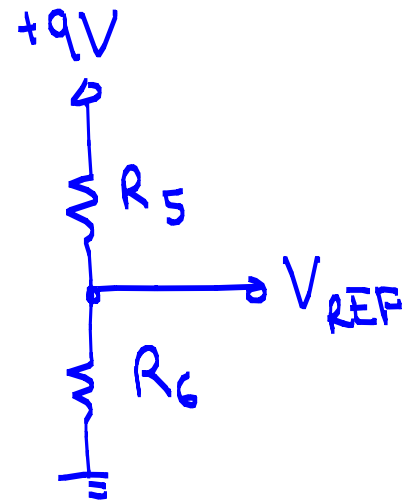


R_6	R_5
100K	125K
110K	137.5K
120K	150K




1. Intro

• Many amplifiers have a single input V_{IN}

Emitter Follower

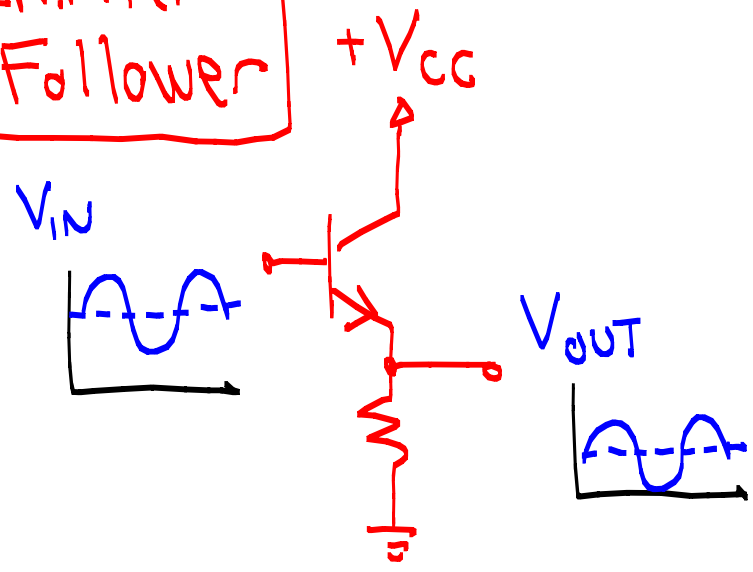


Common Emitter

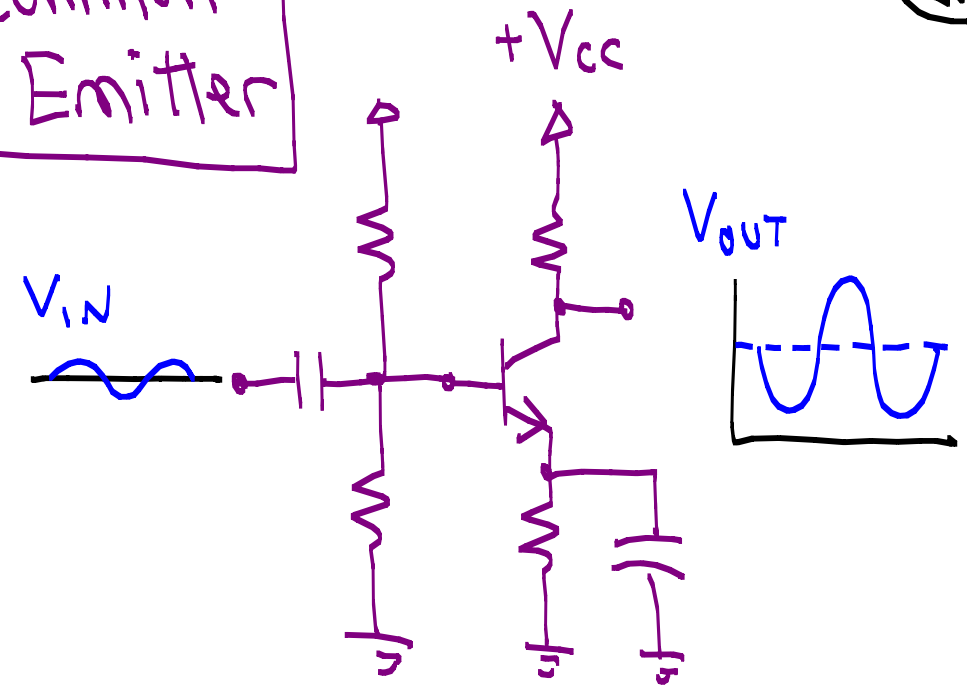

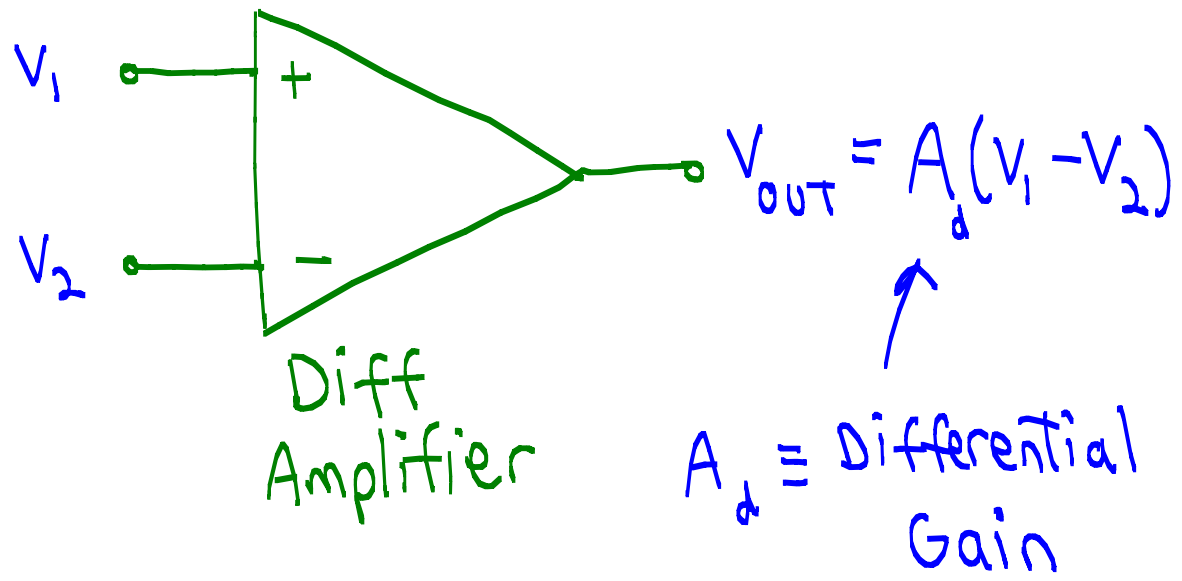12.1


• A differential amplifier has 2 inputs

→ Want to amplify the DIFFERENCE between V_1 and V_2




Application #1

★ Signal transmission over long cables

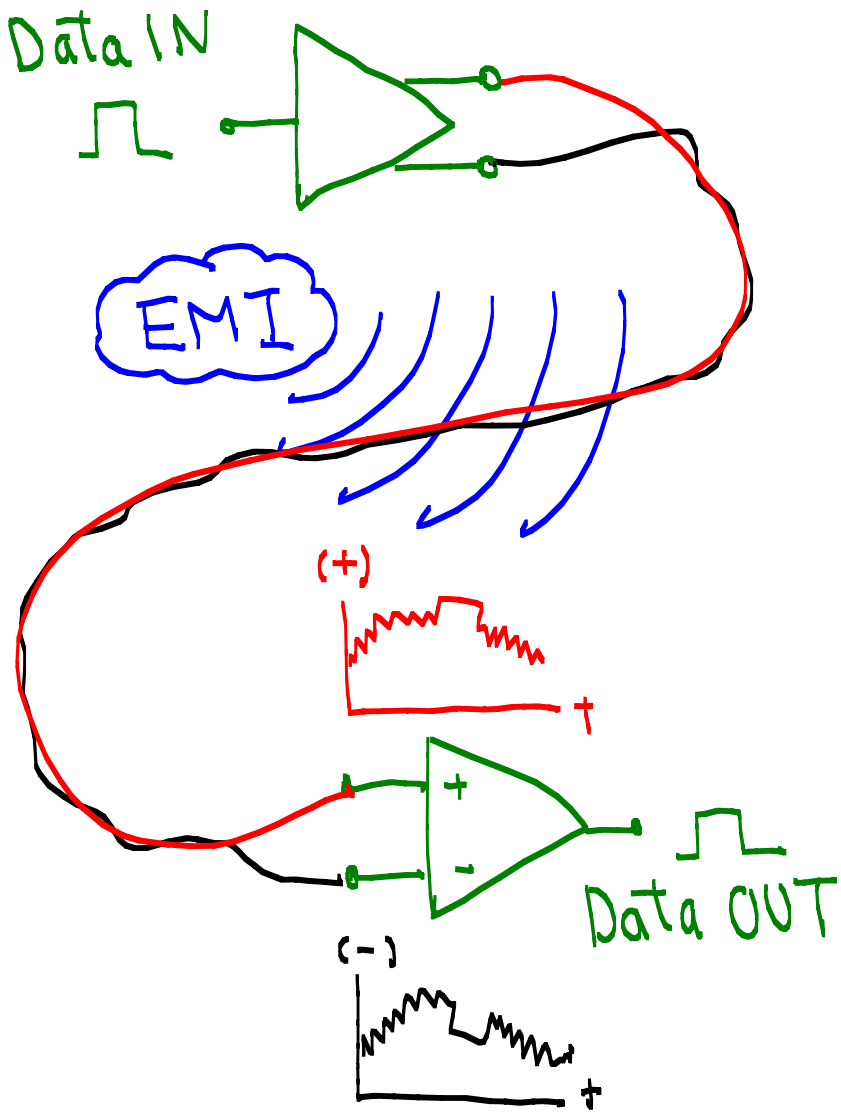

Application #2


Electrocardiogram (ECG) signals

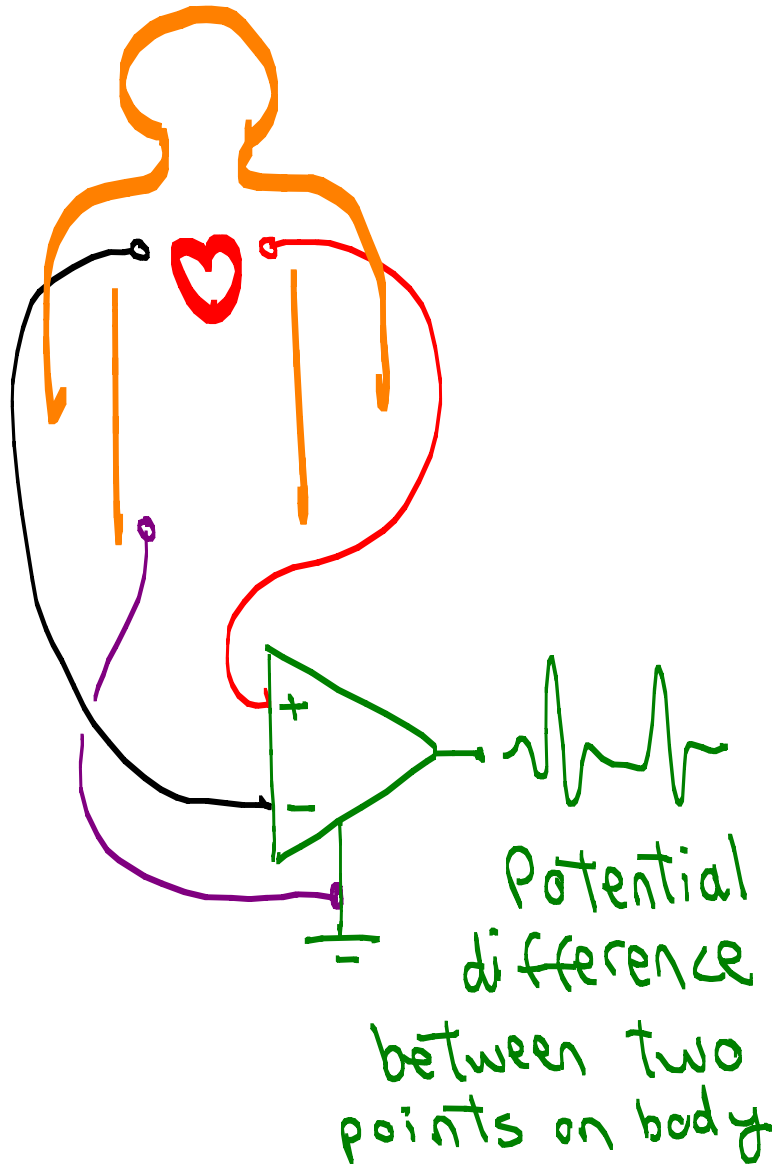

Application #3

(12.2)

Input Stage for an op amp

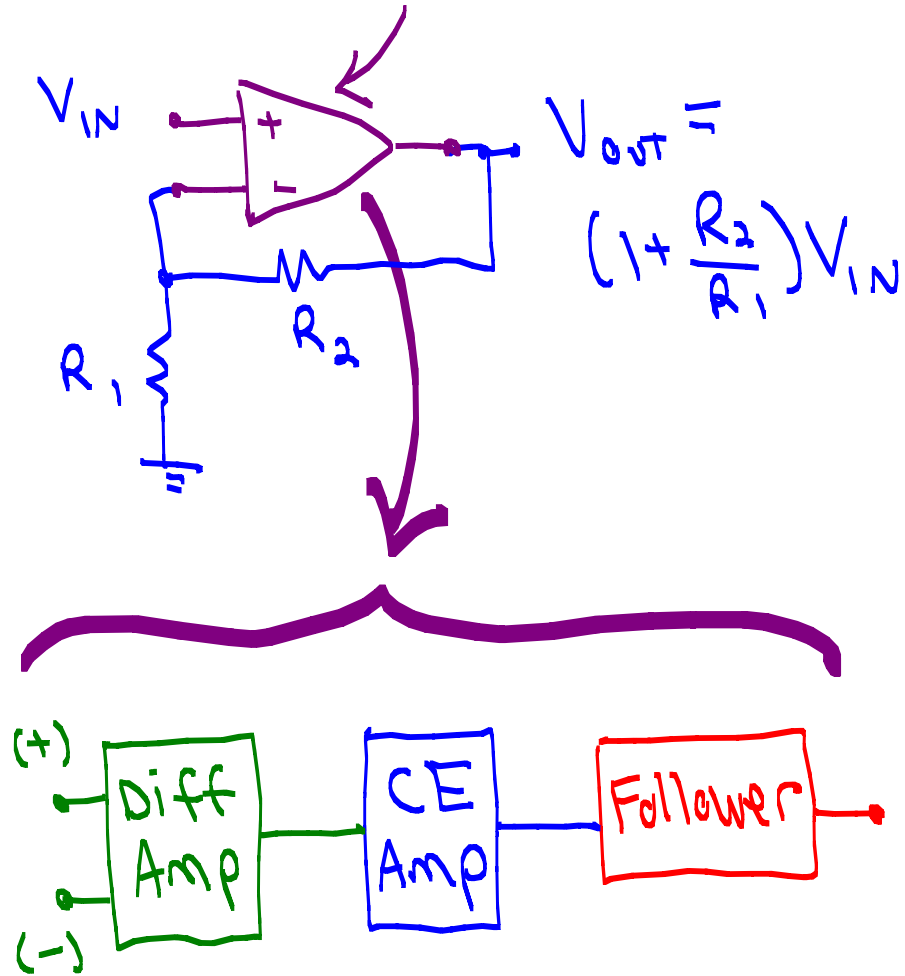

2. BJT Long Tail Pair

● classic configuration for differential amplifier

① Two inputs V_{IN1} and V_{IN2}

② Note the symmetry

→ Ideally, Q_1 and Q_2 are identical ← "matched pair"


③ Output is single-ended ←

most common

differential output is possible


④ R_E is the "tail"

↑ usually a pretty large resistor

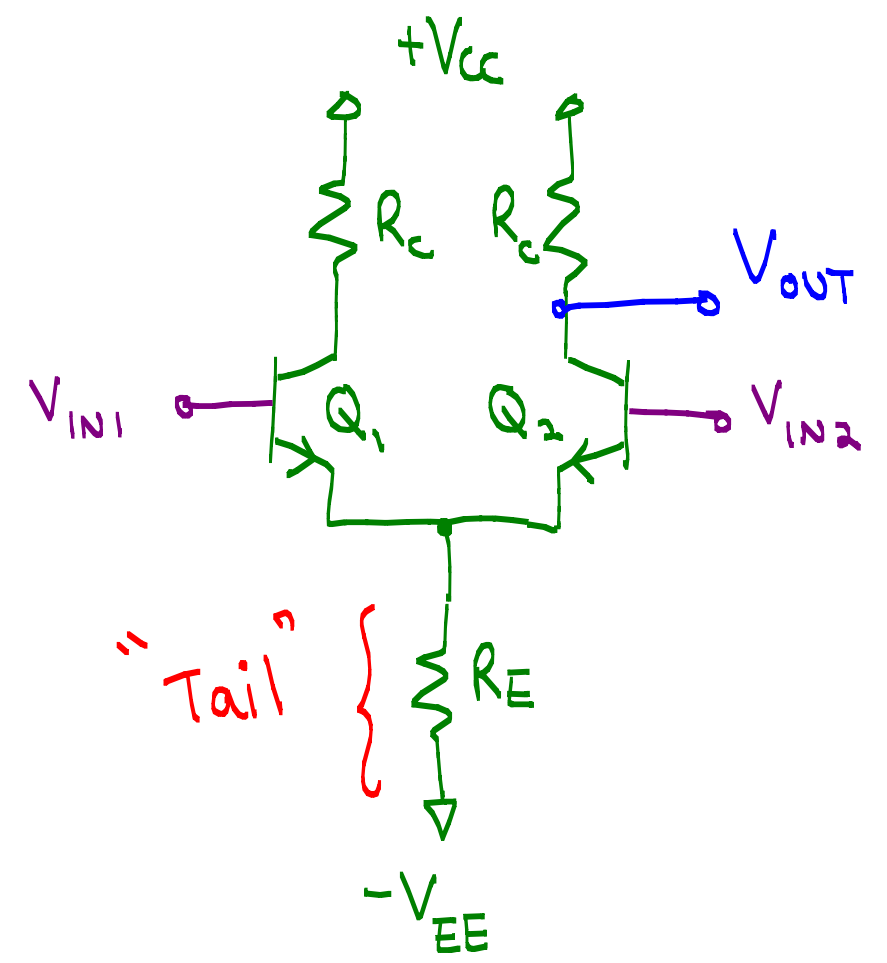


• How does this work?

Quiescent

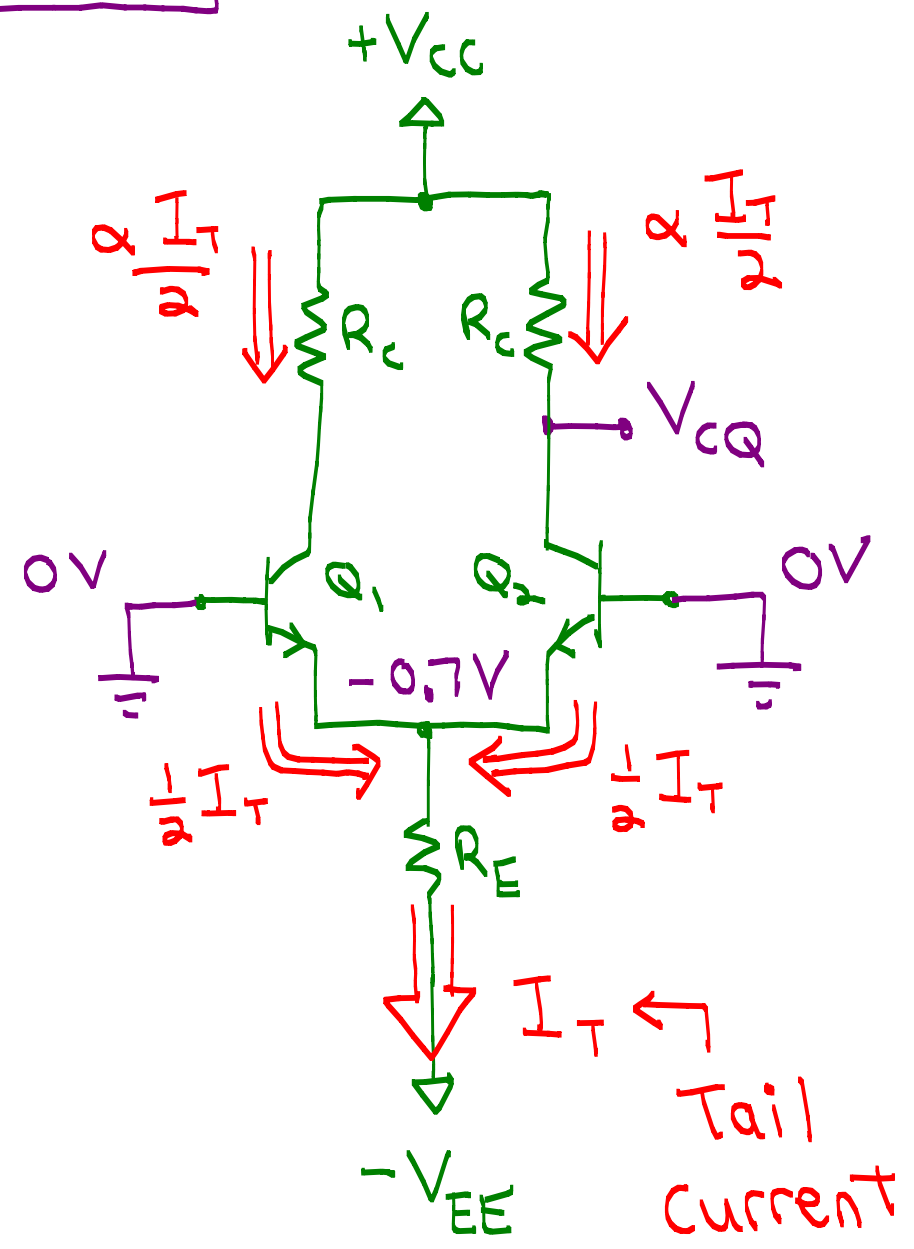

Differential Input

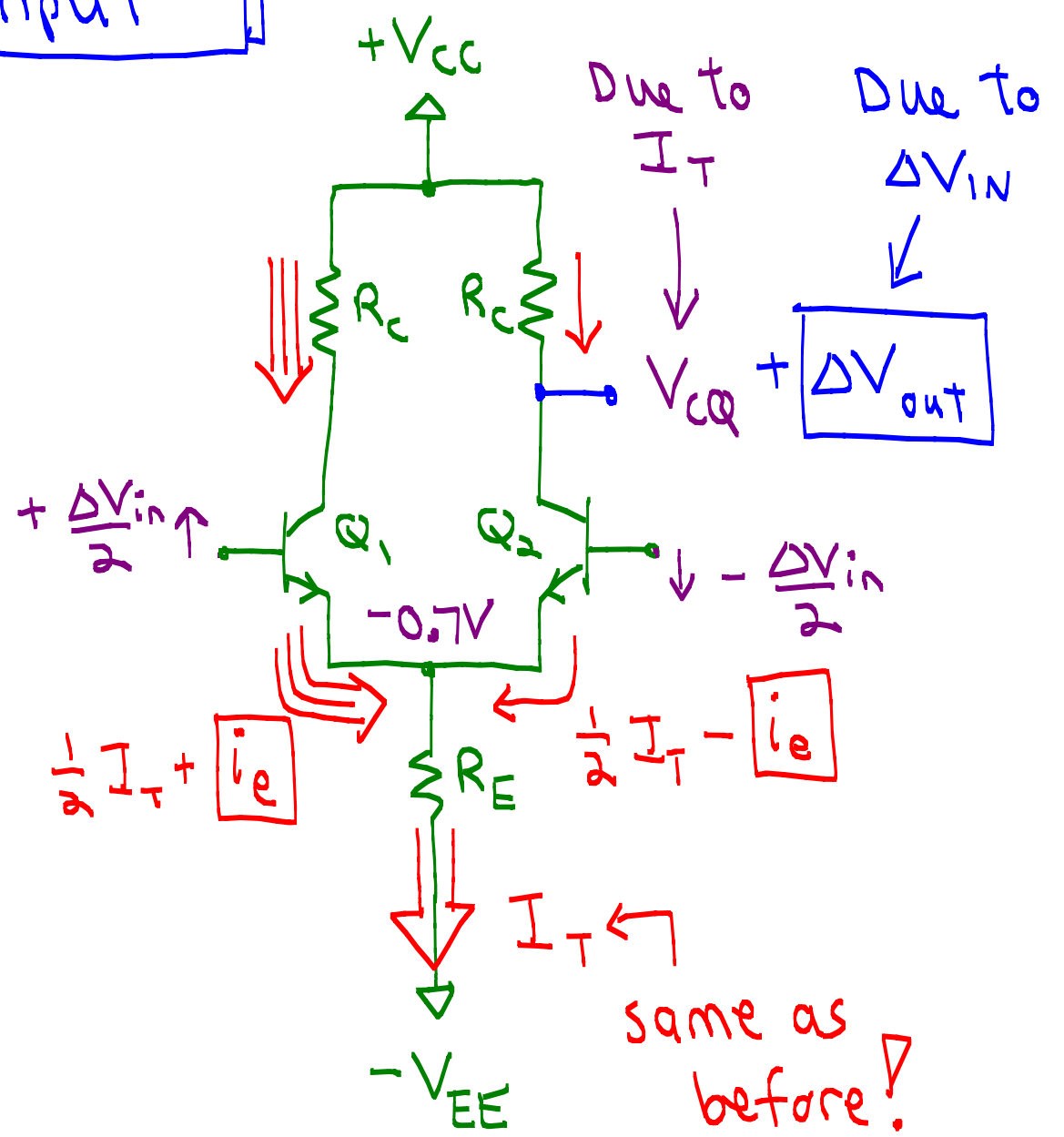

Quiescent ($V_{IN1} = V_{IN2} = 0$)

- Assuming $Q_1 + Q_2$ are ON

- Tail current is therefore

- Due to symmetry,
both Q_1 and Q_2 have

- Quiescent output voltage is $V_{OUT} = V_{CQ} = V_{CC} - I_{CQ} R_C$

DC value
without ΔV_{IN} !

$$\rightarrow \boxed{V_{CQ} = V_{CC} - \alpha \frac{1}{2} I_T R_C}$$

$$V_E = V_B - 0.7 = 0 - 0.7 = -0.7V$$

$$I_T = \frac{(-0.7) - (-V_{EE})}{R_E} = \boxed{\frac{V_{EE} - 0.7}{R_E}}$$

$$I_{EQ} = \frac{1}{2} I_T$$

$$I_{CQ} = \alpha I_{EQ} = \alpha \frac{1}{2} I_T$$

Differential Input

$$(V_{IN1} = +\frac{\Delta V_{in}}{2}, V_{IN2} = -\frac{\Delta V_{in}}{2})$$

- Q_1 and Q_2 act like a "see saw"

Quiescent small signal

$$V_{BE1} = 0.7 + \boxed{\frac{\Delta V_{in}}{2}}$$

small signal

$$V_{BE2} = 0.7 \boxed{-\frac{\Delta V_{in}}{2}}$$

$$i_{E1} = \frac{1}{2} I_T + \boxed{i_e}$$

$$i_{E2} = \frac{1}{2} I_T \boxed{-i_e}$$

$$i_{C1} = \alpha \frac{1}{2} I_T + \boxed{\alpha i_e}$$

$$i_{C2} = \alpha \frac{1}{2} I_T \boxed{-\alpha i_e}$$

- Output voltage is therefore:

$$V_{out} = V_{CC} - i_{C2} R_C = \underbrace{V_{CC} - \alpha \frac{1}{2} I_T R_C}_{\text{Quiescent}} + \boxed{\alpha i_e R_C} \Delta V_{out}$$

• What is i_e ?


Recall the T-Model for BJT small signal behavior

V_{be} = small change in V_{BE}

i_e = small change in i_E

$r_{e'}$ = AC emitter resistance

$$= \frac{0.026V}{I_{EQ}}$$

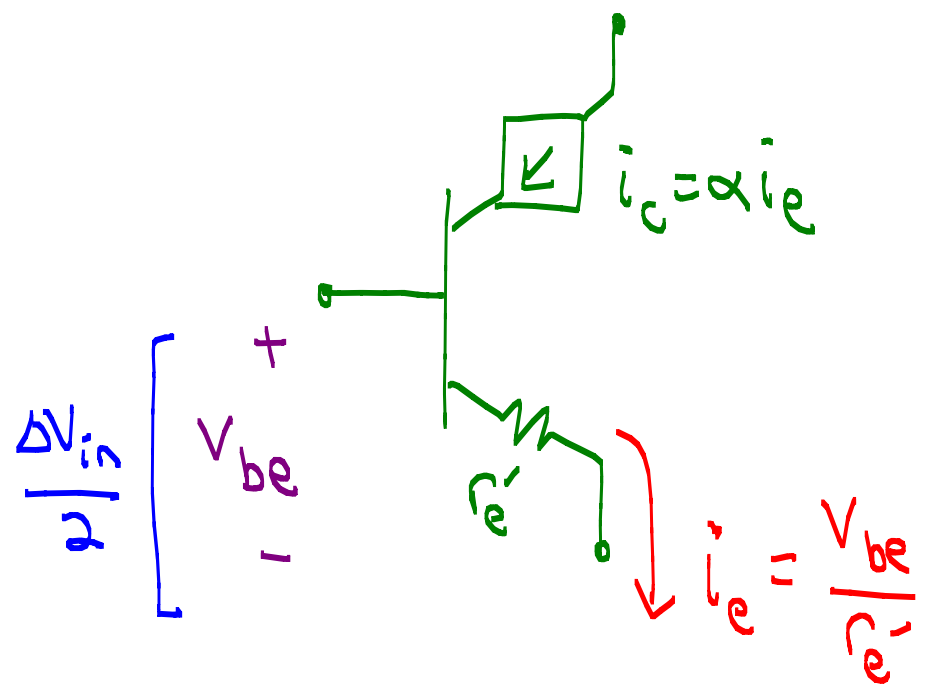


SO,

$$i_e = \frac{\Delta V_{in}/2}{r_{e'}}$$

• Therefore,
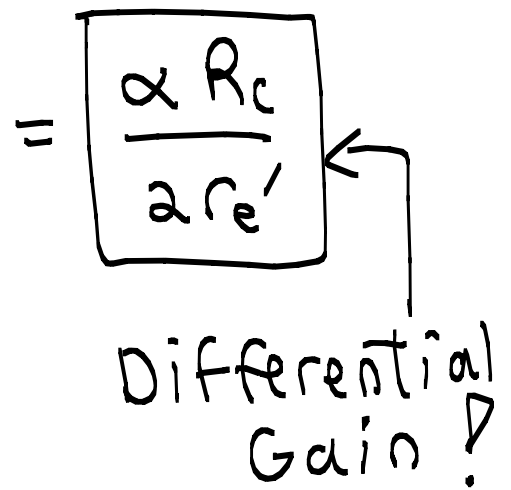
$$A_d = \frac{\Delta V_{out}}{\Delta V_{in}} = \frac{\alpha i_e R_c}{\Delta V_{in}} = \frac{\alpha \frac{\Delta V_{in}/2}{r_{e'}} R_c}{\Delta V_{in}}$$



D. Analysis Example: what is V_{out} ?

$$V_{out} = V_{CQ} + \Delta V_{out}$$

$$V_{CC} - \alpha \frac{1}{2} I_T R_C$$


$$A_d \Delta V_{in}$$

$$V_{IN1} - V_{IN2}$$

$$\alpha R_C$$

$$r_{e'}$$

$$\frac{.026V}{\frac{1}{2} I_T}$$

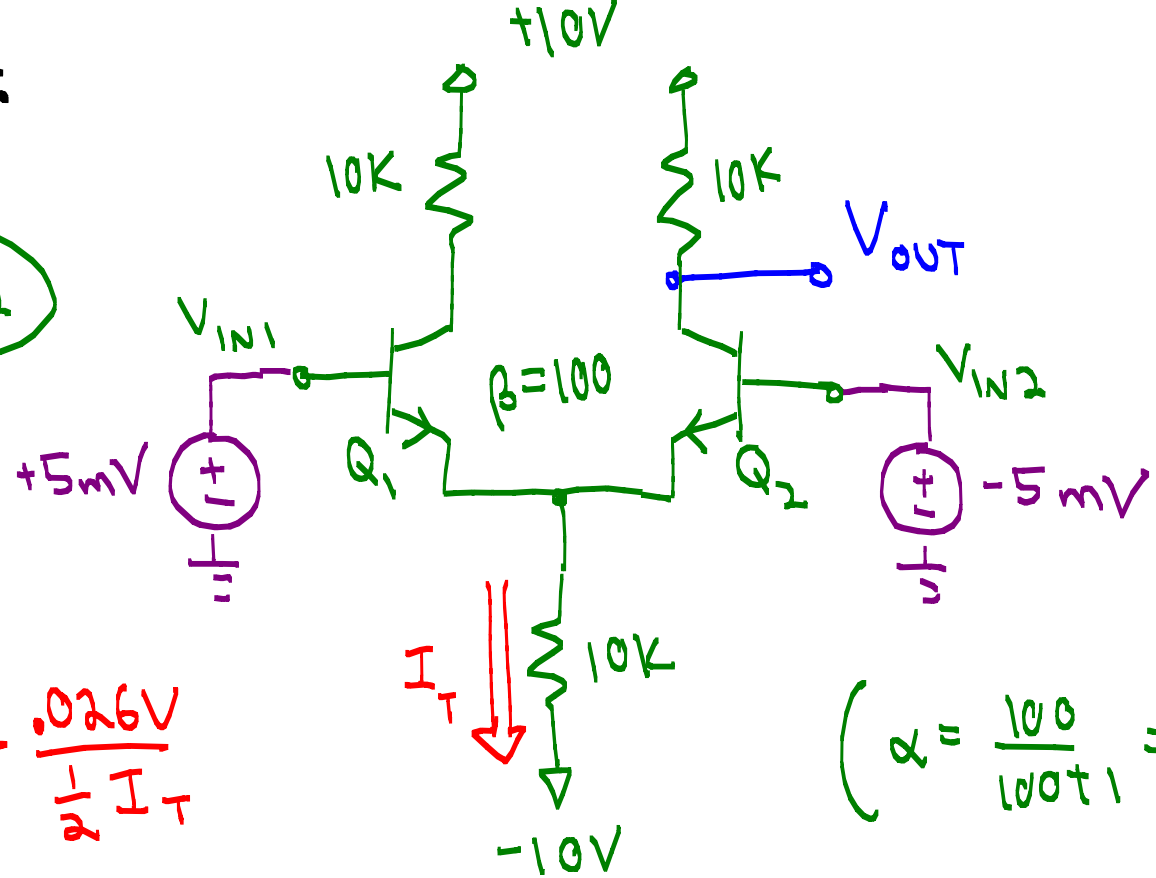

$$\left(\alpha = \frac{100}{100+1} = 0.99 \right)$$

Quiescent

★ We need I_T !

$$I_T = \frac{(-0.7) - (-10V)}{10K}$$

$$= \frac{9.3V}{10K} = 0.93mA$$

$$\Rightarrow V_{CQ} = 10 - 0.99 \frac{1}{2} (0.93mA)(10K) = \underline{\underline{5.4V}}$$

$$r_{e'} = \frac{.026}{0.5 \times 0.93mA} = \underline{\underline{.056K}}, \quad A_d = 88.4$$

$$A_d \Delta V_{in} = 88.4 \times 10mV = \underline{\underline{884mV}}$$

$$V_{IN1} - V_{IN2}$$

$$\Rightarrow \boxed{V_{out} = 6.284V}$$



3. Input Impedance

Derivation 1


$$R_{in} = \frac{\Delta V_{IN}}{\Delta I_{IN}} = \frac{+\frac{\Delta V}{2} - (-\frac{\Delta V}{2})}{\Delta i} = \frac{\Delta V}{\Delta i}$$

Since Δi is a base current, $\Delta i = \frac{i_e}{\beta + 1} = \frac{\Delta V / 2r_e'}{\beta + 1}$

$$\frac{\Delta V}{\Delta i} = R_{in} = 2(\beta + 1)r_e'$$

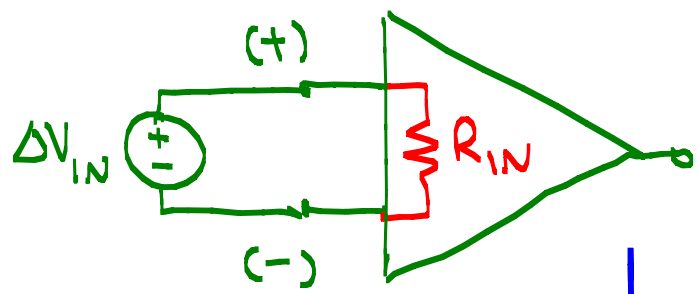
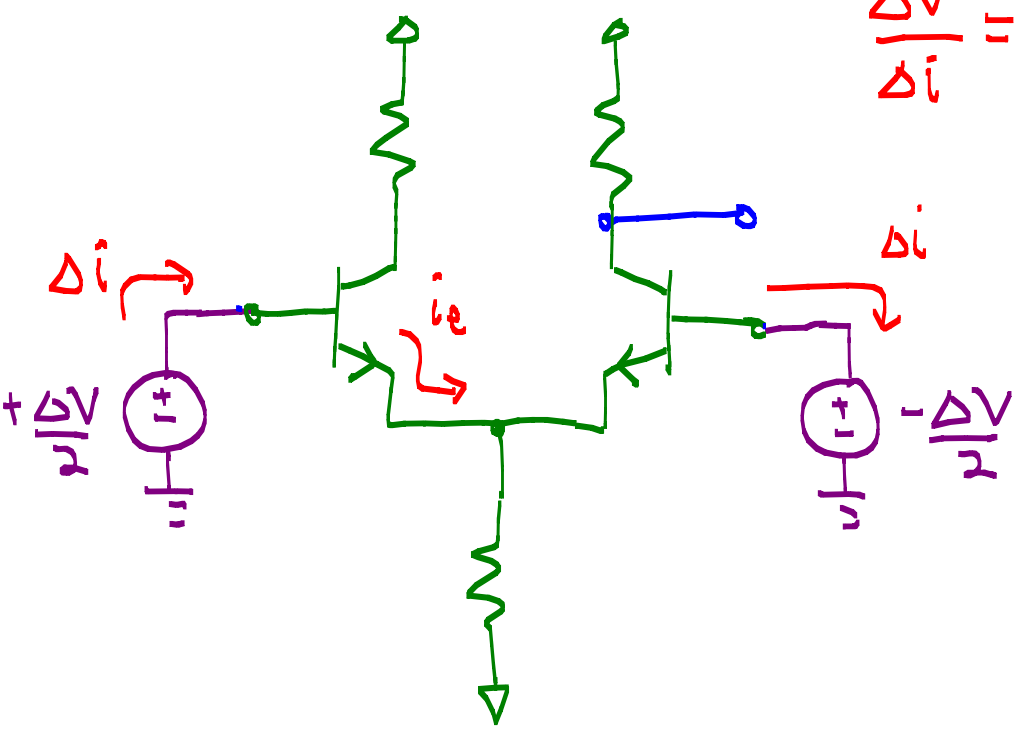


Derivation 2

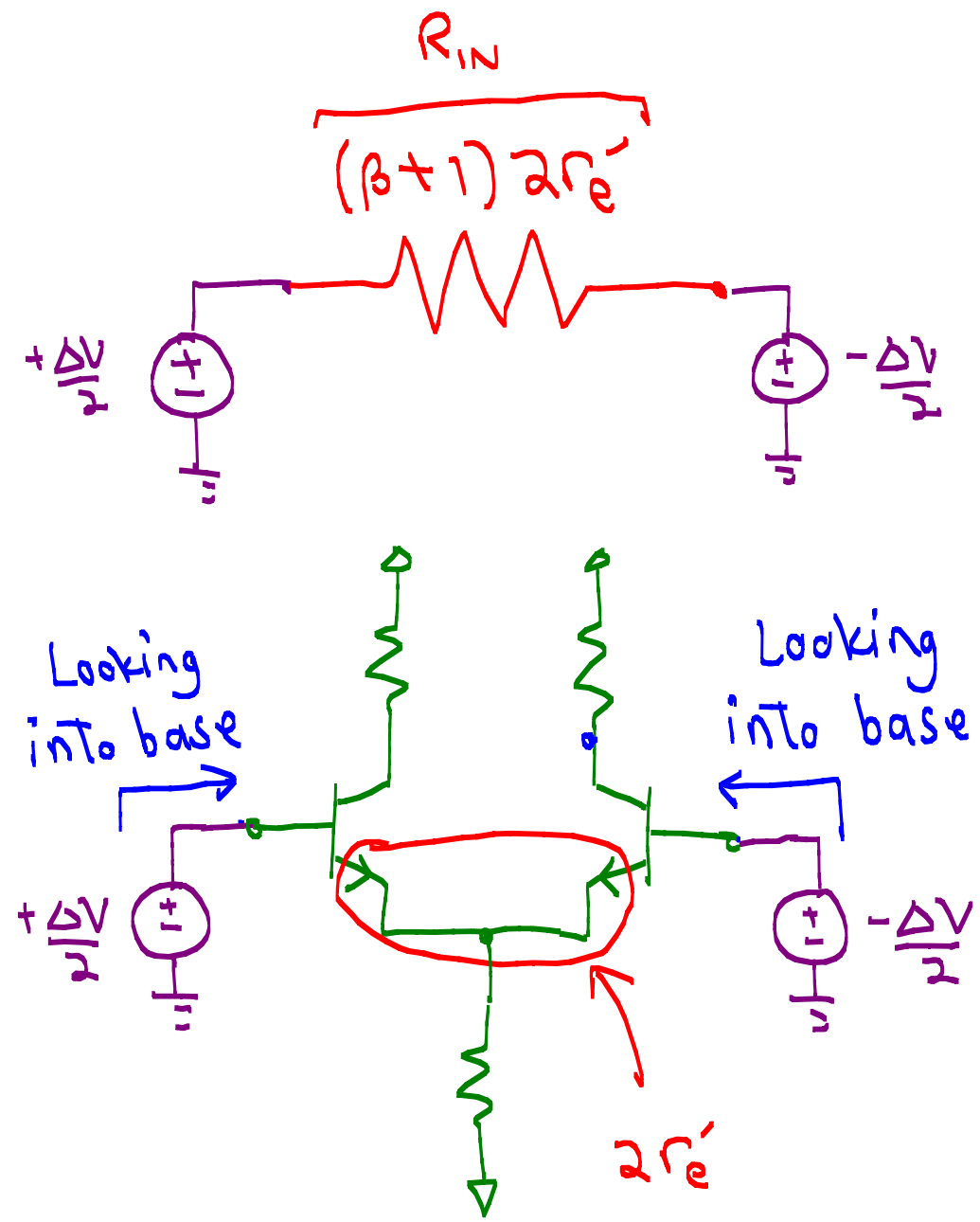

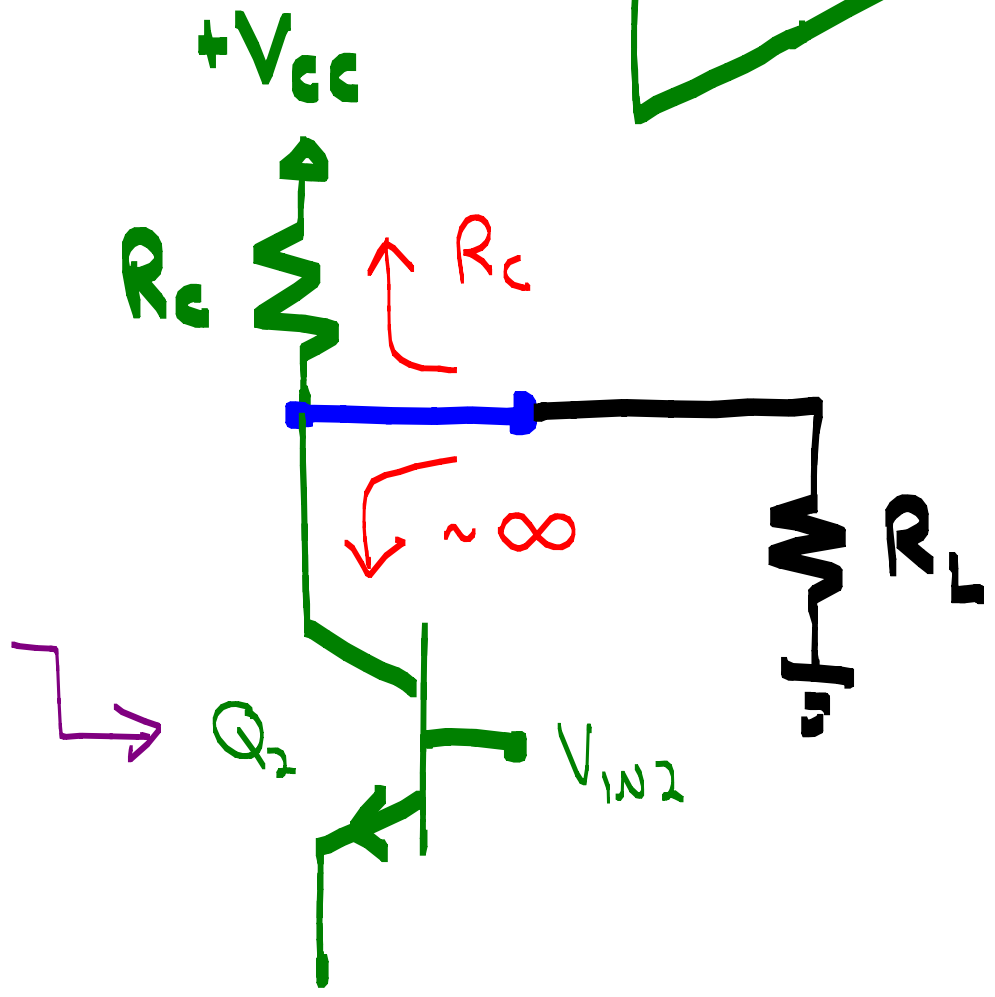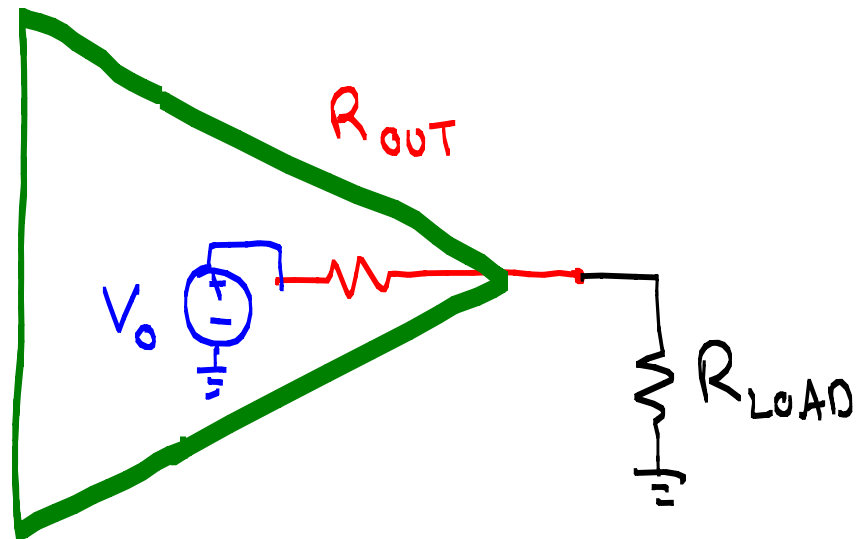4. Output Impedance

- A voltage amplifier ideally has $R_{out} \approx 0\Omega$



BJT collector looks like a current source

~ Infinite source impedance

$R_{out} = R_c$

Typically > 10k

Not good
∴

3. Design Example ← use "default" parameters


Gain ≥ 50 , $R_{in} \geq 10 \text{ k}\Omega$, $V_{CC} = V_{EE} = 15 \text{ V}$

Where to start?

Formulas: $A_d = \frac{\alpha R_c}{2r_{e'}}$

$R_{in} = 2(\beta + 1)r_{e'}$

can solve for this!

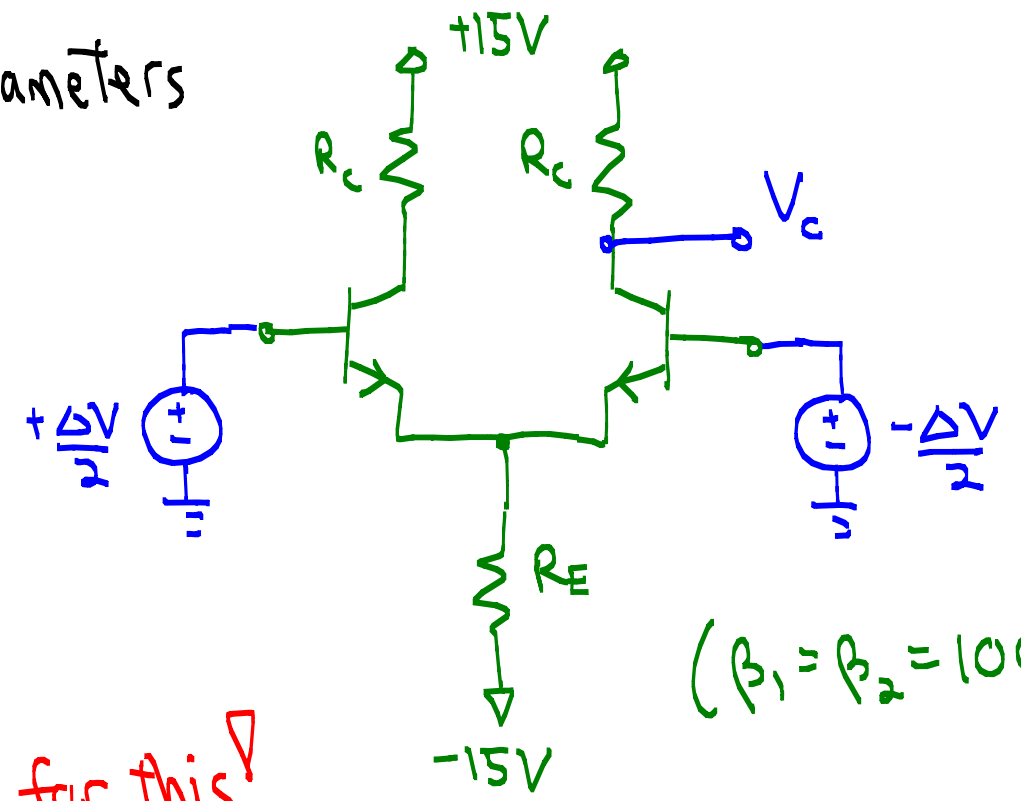

($\beta_1 = \beta_2 = 100$)

① $R_{in} = 2(100 + 1)r_{e'} \geq 10000 \Omega$

$r_{e'} \geq 49.5 \Omega$

Since $r_{e'} = \frac{.026 \text{ V}}{I_E} \geq 49.5 \Omega \Rightarrow \underline{\underline{I_E \leq .53 \text{ mA}}} \Rightarrow \underline{\underline{I_T \leq 1.06 \text{ mA}}}$

② using $I_T = \frac{15 - 0.7}{R_E} < 1.06 \text{ mA}$

$$R_E > 13.49 \text{ k}$$

Choose $R_E = 15 \text{ k}$

③ Actual $I_T = \frac{15 - 0.7}{15 \text{ k}} = 0.95 \text{ mA} \Rightarrow r_{e'} = \frac{0.026 \text{ V}}{\frac{1}{2}(0.95 \text{ mA})} = \underline{\underline{0.0547 \text{ k}}}$

$$R_w = 2(100 + 1)(0.0547 \text{ k}) = \underline{\underline{11.05 \text{ k}}} \checkmark$$

④ $A_d = \frac{\alpha R_c}{2r_{e'}} = \frac{0.99 R_c}{2 \times 0.0547 \text{ k}} \geq 50$

$R_c \geq 5.53 \text{ k} \Rightarrow \underline{\underline{\text{Choose } 5.6 \text{ k}}}$

Actual gain is $A_d = \frac{0.99 \times 5.6 \text{ k}}{2 \times 0.0547 \text{ k}} = \underline{\underline{50.7}} \checkmark$