

Lecture 13: Differential Amplifiers (Part 2)

(Quiz)

0. Review

1. Common mode rejection ratio

2. Current Source Biasing

3. BJT current source

Textbook reading: 15-5 Common Mode Gain

• PreLab 5b (Multisim)
due at lab session

• HW 6 due this Fri (Nov 08)

• Exam #2 next Tue (Nov 12)

→ HW 4, 5, 6



→ Q 24, 5, 6 ← sample on website

→ Sample exam on course website


0. Review

Differential Amplifier

Quiescent

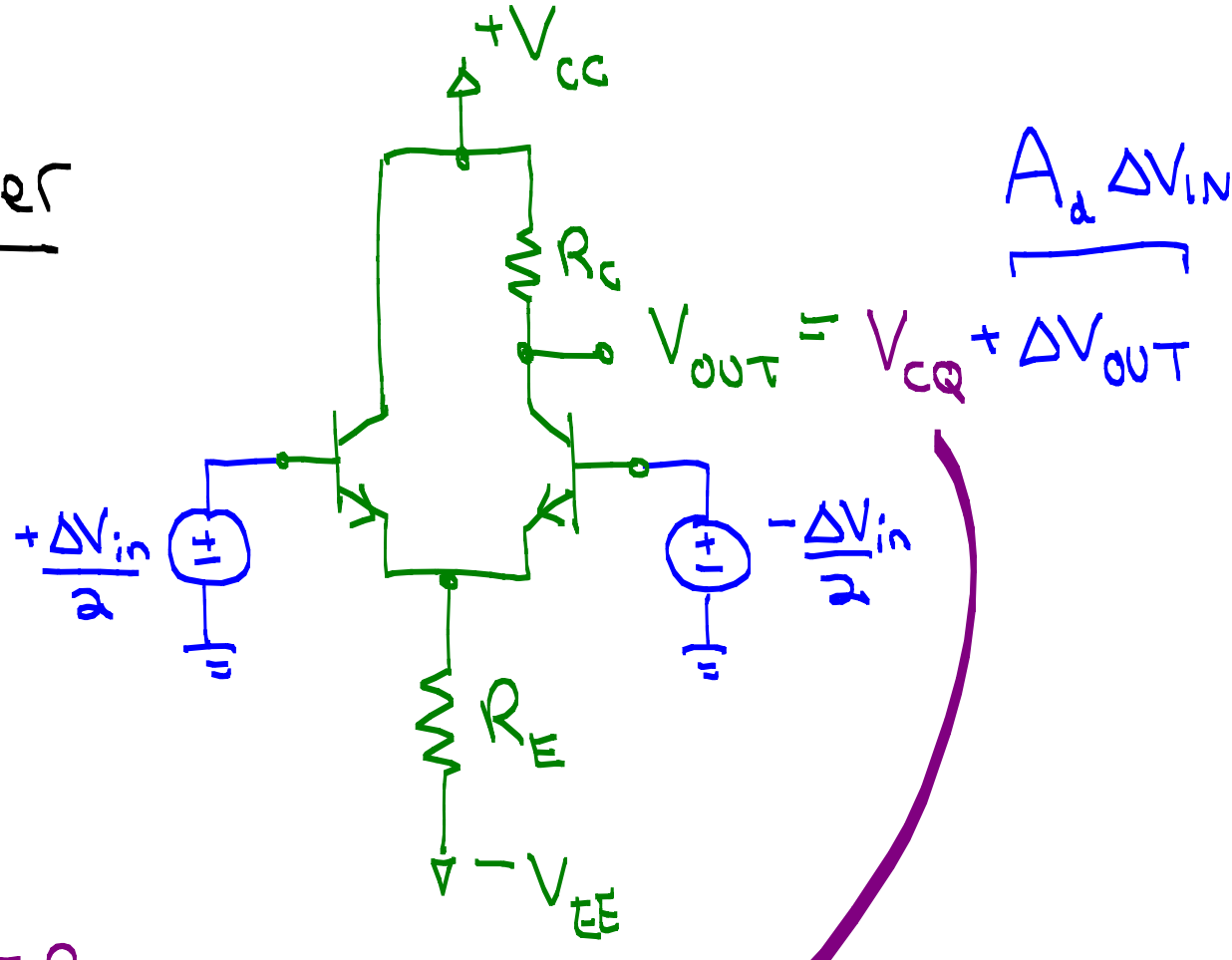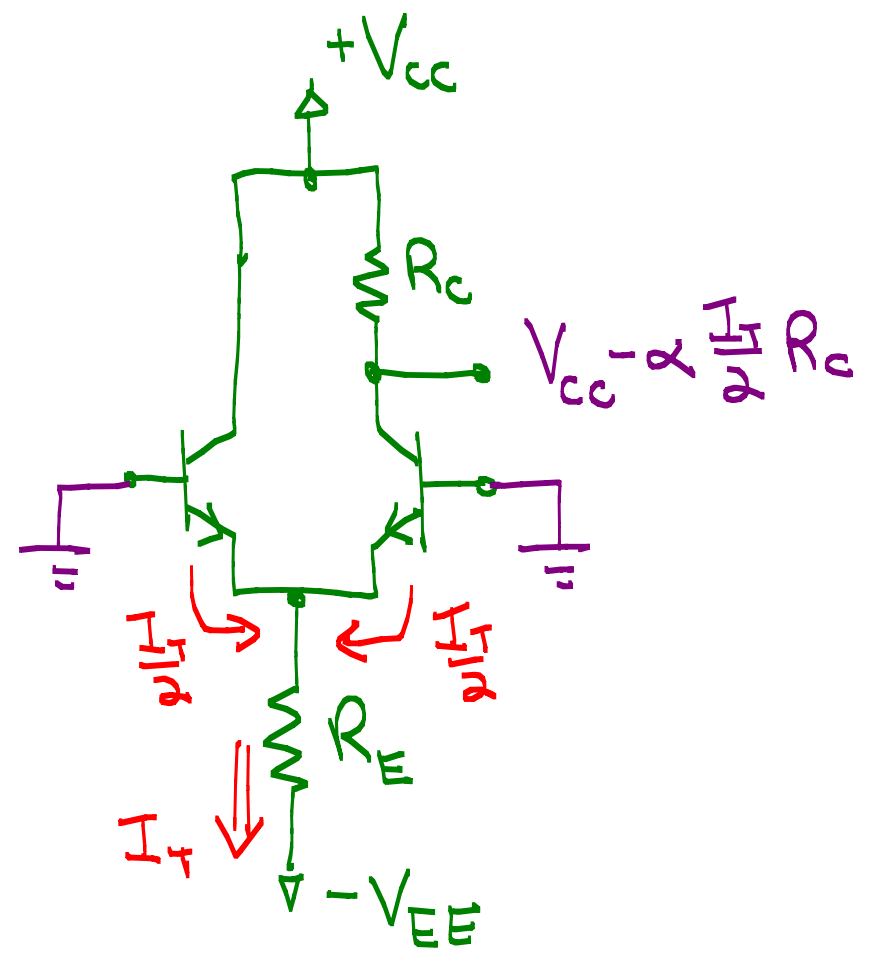

Signal

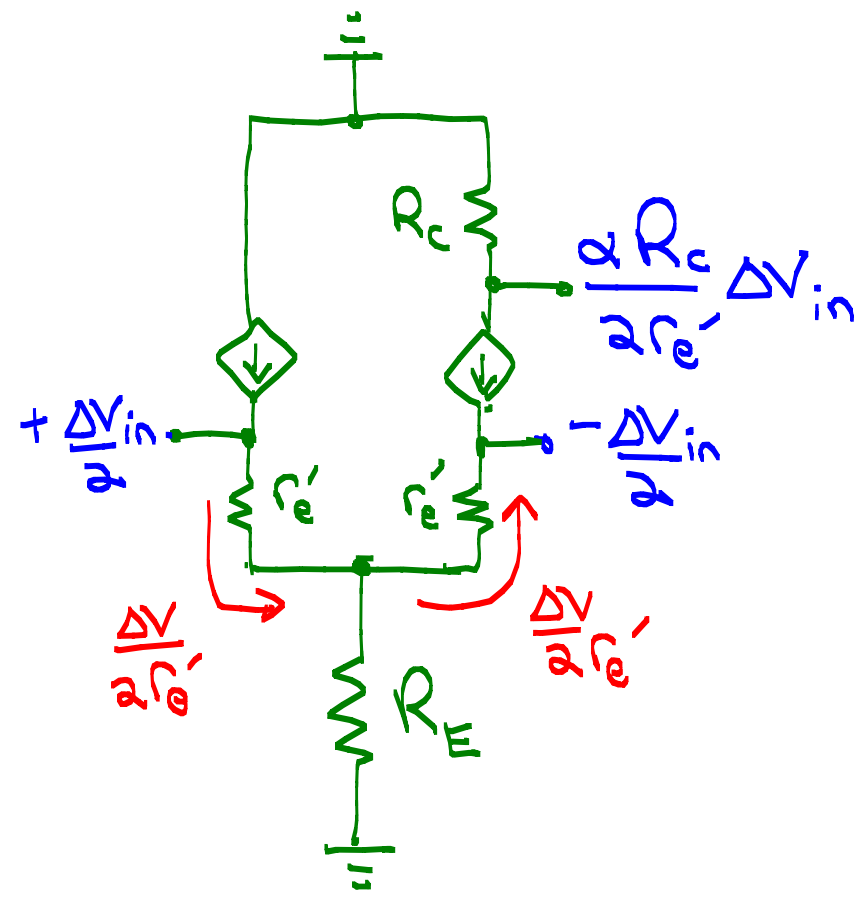

Also...

$$Z_{IN} = 2(\beta + 1)r_{e'}$$

$$Z_{OUT} = R_C$$


1. Common Mode Rejection Ratio (CMRR)

- In many situations, V_{IN1} and V_{IN2} have a large offset V_{CM} .

$$V_{IN1} = V_{CM} + \frac{\Delta V}{2}$$

$$V_{IN2} = V_{CM} - \frac{\Delta V}{2}$$

Common Mode Input

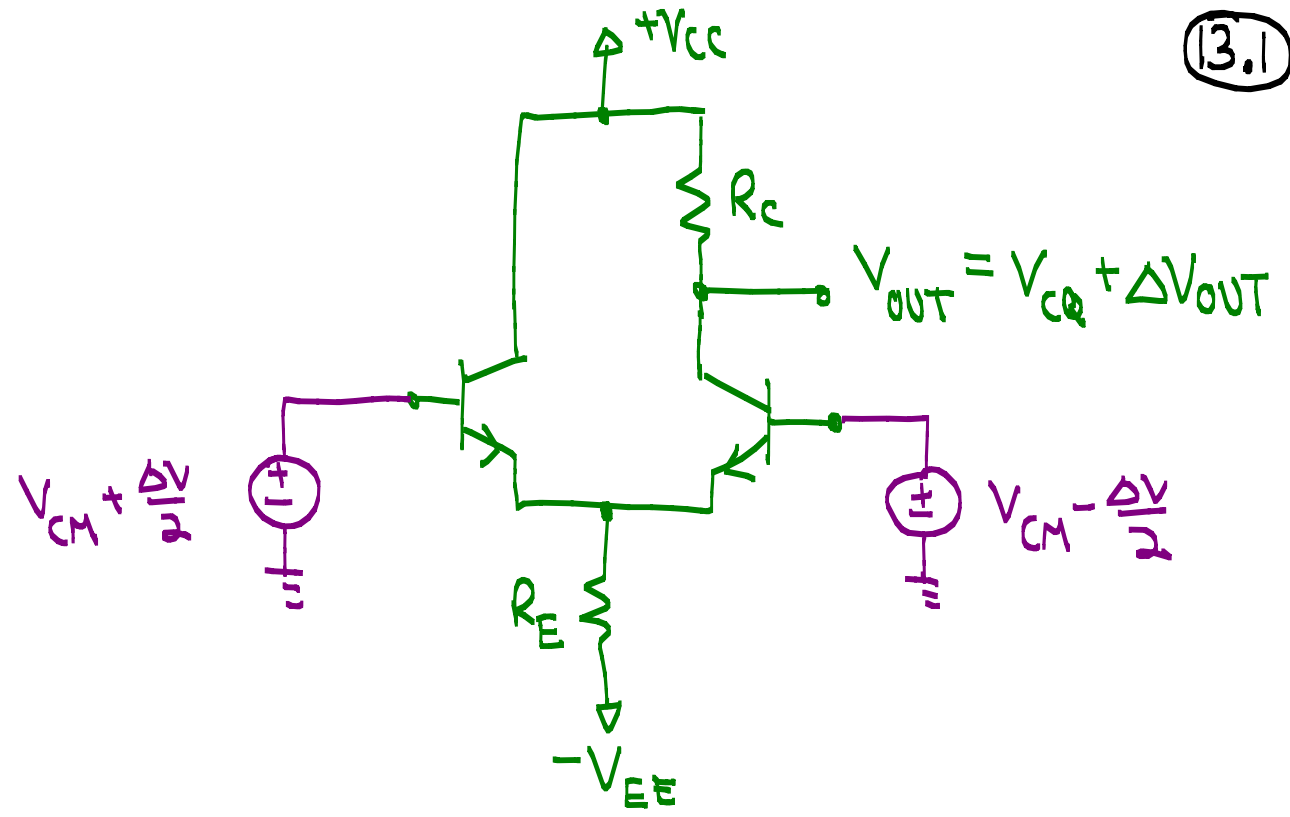

- Ideally, ΔV_{OUT} only depends on $\Delta V_{IN} = V_{IN1} - V_{IN2} = \Delta V$

- In reality, ΔV_{OUT} is affected by V_{CM} .

Differential Gain

Common Mode Gain (Ideally zero)

$$\Delta V_{OUT} = A_d \Delta V_{IN} + A_{CM} V_{CM}$$

$\Delta V_{IN} = \frac{V_{IN1} - V_{IN2}}$
 $V_{CM} = \frac{V_{IN1} + V_{IN2}}{2}$

Example

$$V_{IN1} = 3.01V, V_{IN2} = 2.99V$$

$$A_d = 100, A_{CM} = .01$$

What is ΔV_{OUT} ?

$$\rightarrow \Delta V_{OUT} = A_d \Delta V_{IN} + A_{CM} V_{CM}$$

$$\frac{V_{IN1} + V_{IN2}}{2} = \underline{\underline{3V}}$$

$$\Rightarrow \Delta V_{OUT} = \underbrace{100 \times .02}_{\text{Ideal result}} + \underbrace{.01 \times 3}_{\text{Error term}} = \boxed{2.03V}$$

Ideal result
= 2V

Error term

- A good differential amplifier has very small A_{cm} (e.g. 0.001)
→ Called common mode rejection

- Extremely important metric of a differential amplifier is the common mode rejection ratio (CMRR)

$$\Rightarrow \boxed{CMRR = 20 \log_{10} \left| \frac{A_d}{A_{cm}} \right|}$$

Example $A_d = 120$, $A_{cm} = .005$

13.3

$$\begin{aligned} CMRR &= 20 \log_{10} \left(\frac{120}{.005} \right) \\ &= 20 \log_{10} (24000) \\ &= \boxed{87.6 \text{ dB}} \end{aligned}$$

★ Good differential amplifier has $CMRR > 80 \text{ dB}$

$$\underbrace{20 \log_{10} (10,000)}$$

• Common mode gain for long-tail pair

★ V_{CM} causes a change in tail current! ☹️

$$I_T' = \frac{(V_{CM} - 0.7) - (-V_{EE})}{R_E}$$

$$= \frac{V_{EE} - 0.7}{R_E} + \frac{V_{CM}}{R_E} = I_T + \Delta I_T$$

So, $I_{EQ}' = \frac{I_T}{2} + \frac{\Delta I_T}{2}$


causes change in V_{OUT} ! ☹️

$$\rightarrow V_o' = \underbrace{V_C - \alpha \frac{I_T}{2} R_C}_{\text{Quiescent}} + \alpha \frac{\Delta I_T}{2} R_C$$

$$\Delta V_{OUT} = - \frac{\alpha V_{CM}}{2 R_E} R_C$$

(-) sign!
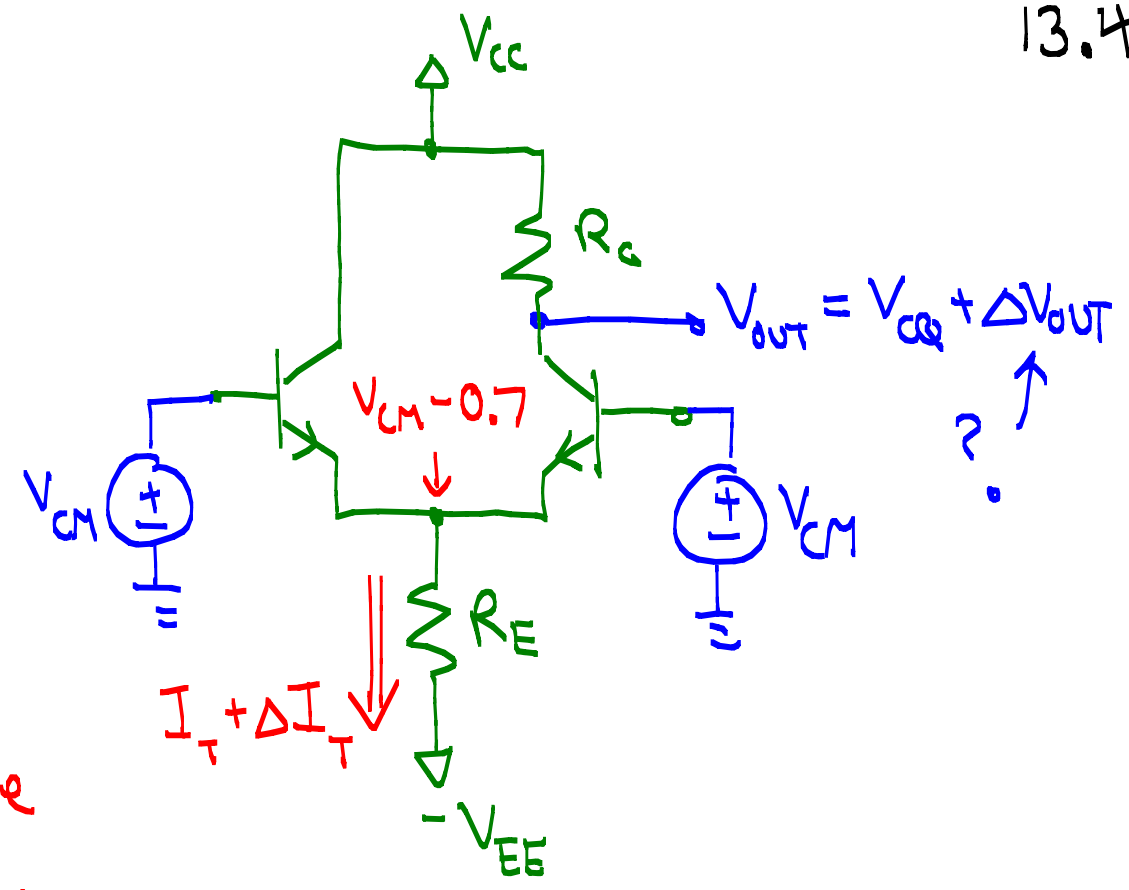
$$\frac{\Delta V_{OUT}}{V_{CM}} = A_{CM} = - \frac{\alpha R_C}{2 R_E}$$



• CMRR for long-tail pair

$$CMRR = 20 \log_{10} \left| \frac{A_d}{A_{cm}} \right|$$

$$= 20 \log_{10} \left| \frac{\alpha R_c / 2r_{e'}}{-\alpha R_c / 2R_E} \right|$$


$$= \boxed{20 \log_{10} \left(\frac{R_E}{r_{e'}} \right)}$$

↑
only depends
on R_E and r_{e}'

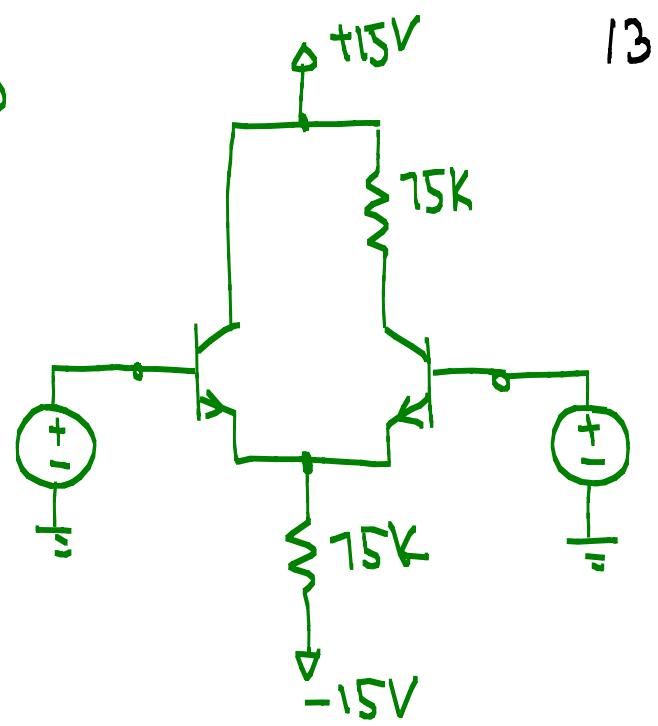Example Compute A_d , A_{cm} ,
and CMRR

$$\bullet I_T = \frac{15 - 0.7}{75K} = 0.19 \text{ mA}$$

$$r_{e}' = \frac{0.026V}{0.095 \text{ mA}} = 0.274K$$



$$\bullet A_d = \frac{75K}{2 \times 0.274K} = 137, \quad A_{cm} = \frac{-75K}{2(75K)} = \underline{\underline{-0.5!}}$$

$$\Rightarrow CMRR = 20 \log_{10} \left(\frac{75K}{0.274K} \right) \text{ or } 20 \log_{10} \left| \frac{137}{-0.5} \right|$$
$$= 20 \log_{10}(174) = \boxed{48.8 \text{ dB}}$$

(not very good)
☹



2. Current Source Biasing

$$20 \log_{10} (R_E / r_e')$$

Q: How to improve CMRR?



Increase R_E ? Tiny $I_T \rightarrow Q_1, Q_2$ OFF :-)

★ Recall that:

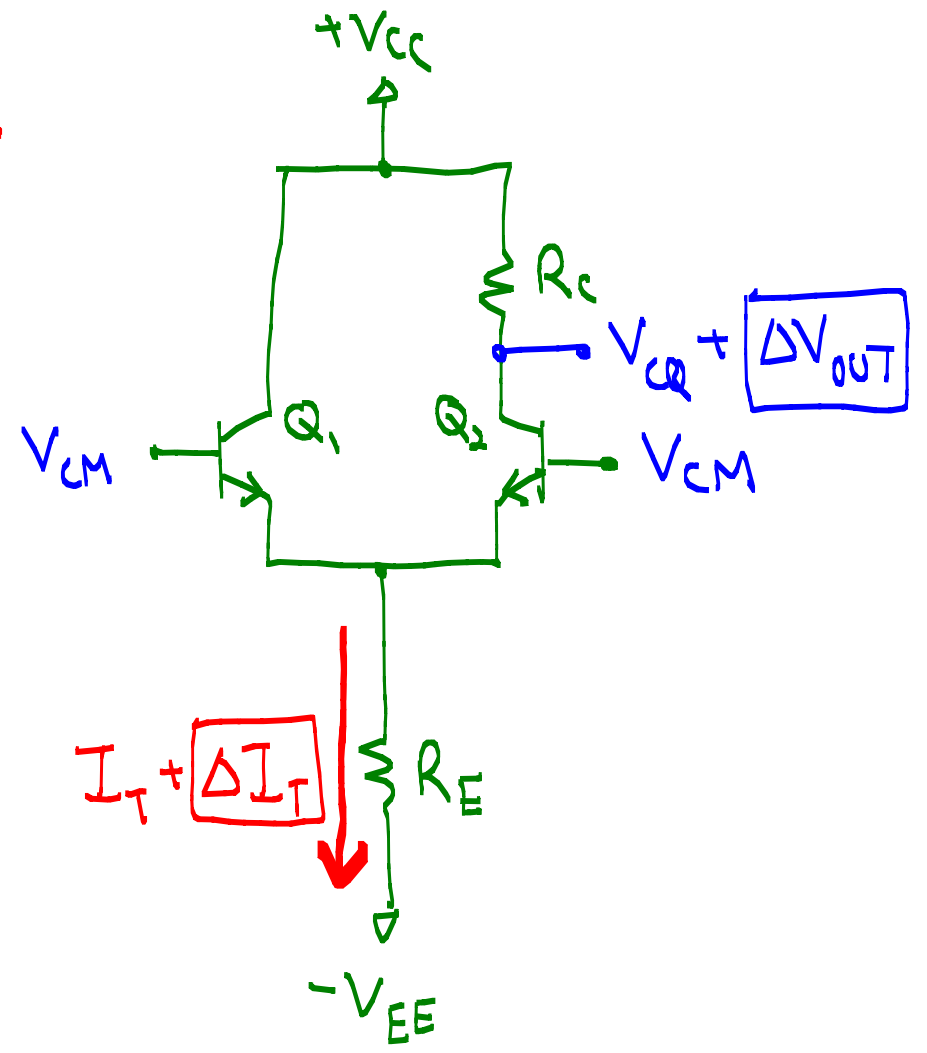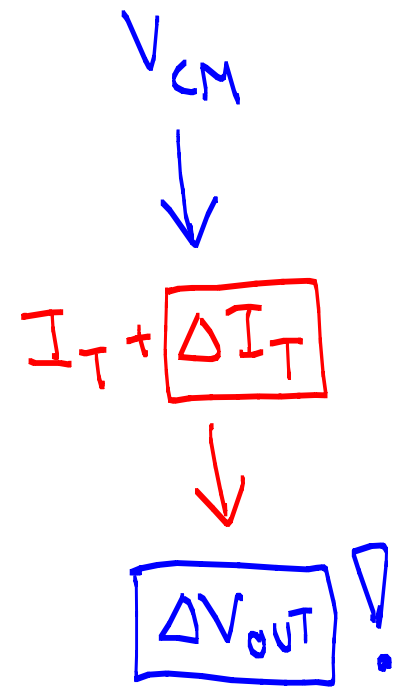

★ Key is to make I_T insensitive to V_{CM} . (13.6)

⇒ Use constant current source for I_T !

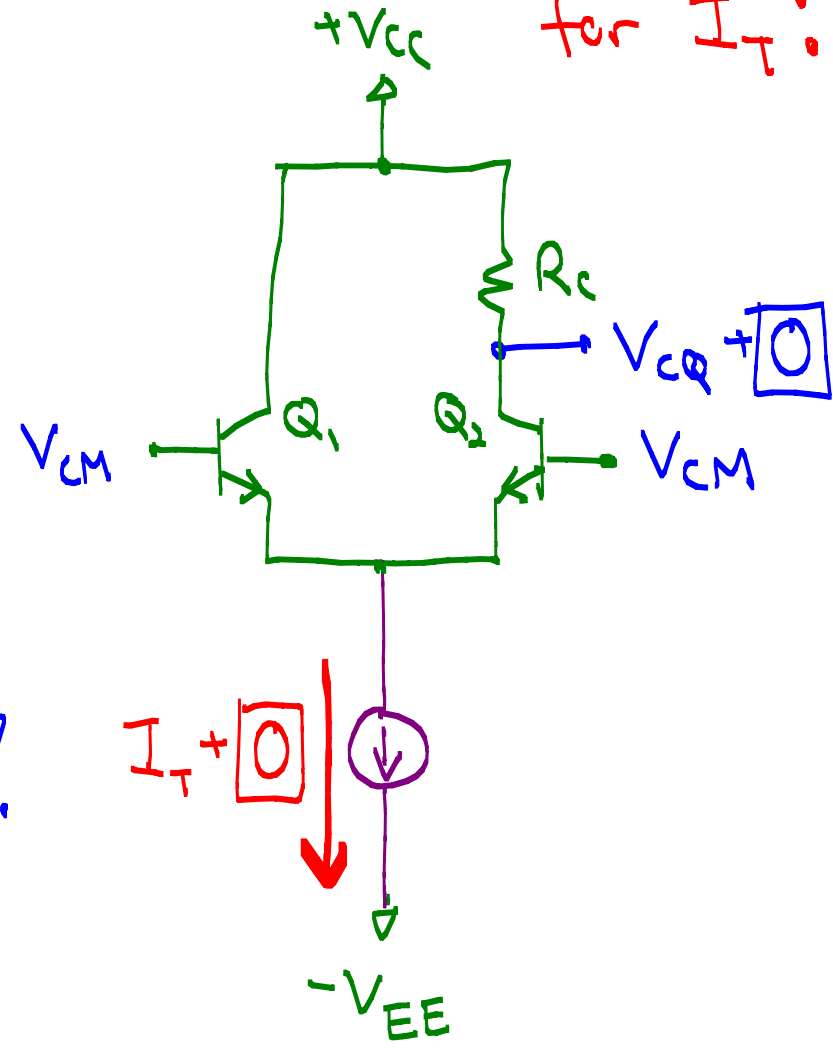
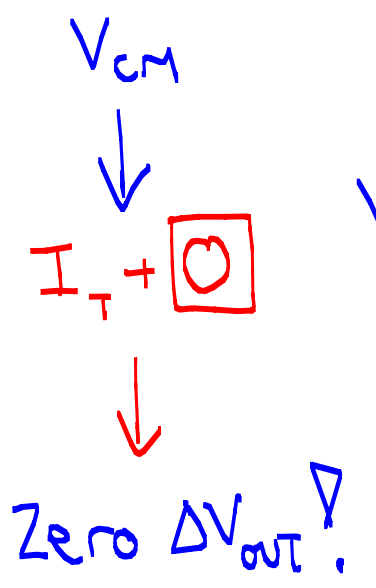


3. BJT Current Source

Fortunately, a good current source can be made from a BJT

Example

Does not depend on V_{CC} !

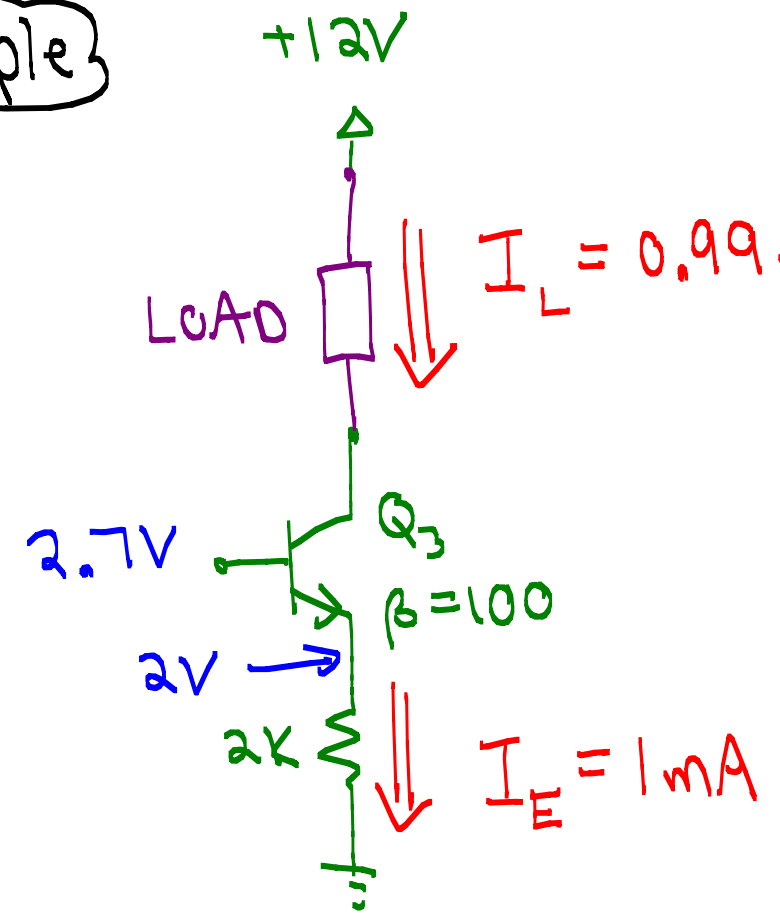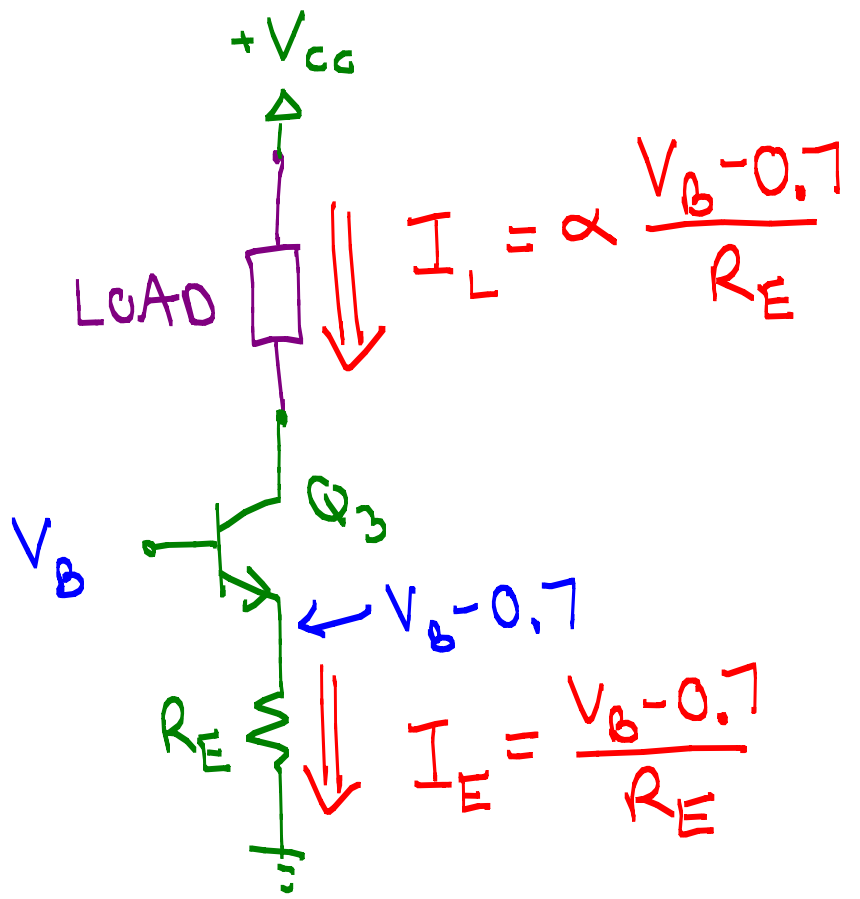

★ I_L depends on V_B and R_E !

Q: How to set the Q₃ base voltage?

A common method is to use some diodes as a voltage reference.



* Q₃ is biased with some diodes

→ Make sure I_D ~ 1 mA!

$$i_D = \frac{12 - 1.4}{10K} - \frac{1mA}{100 + 1}$$

$$= 1.06 mA - 0.01 mA$$

$$= 1.05 mA \checkmark$$

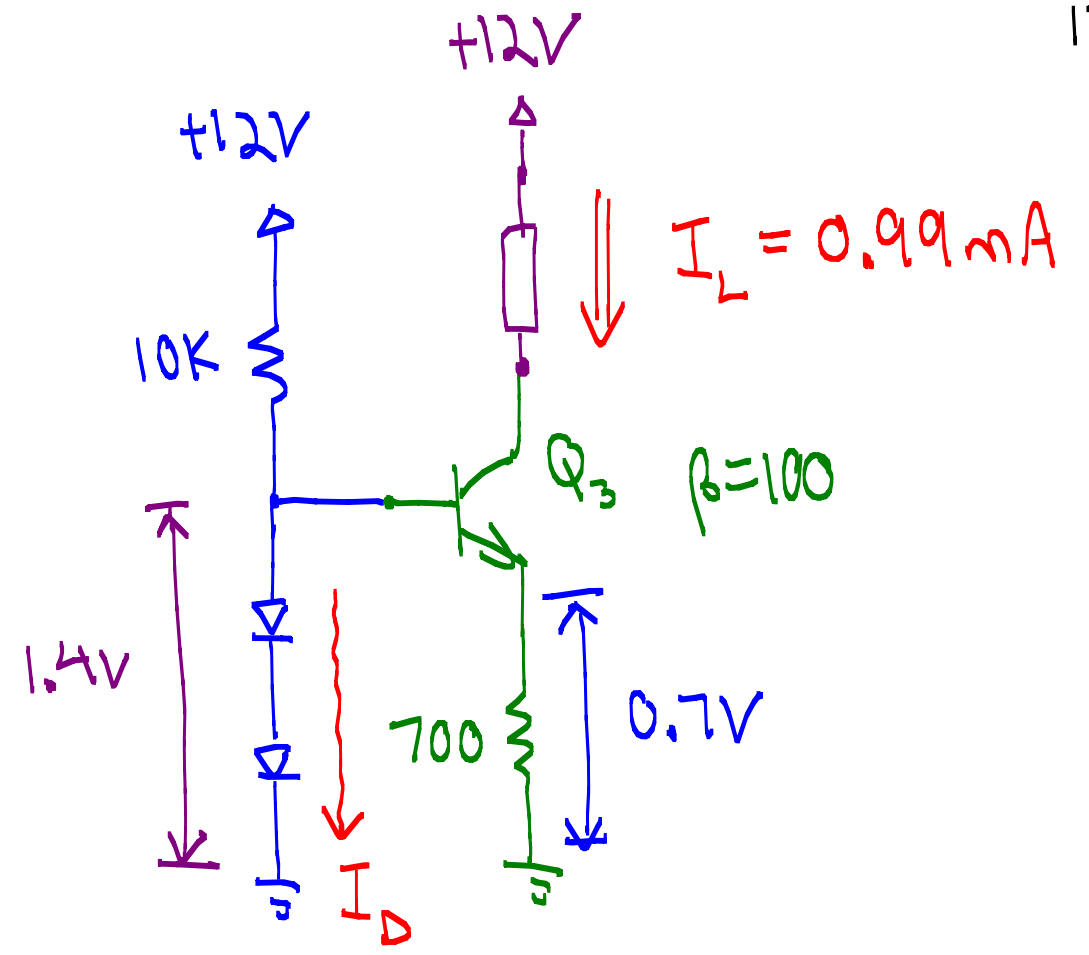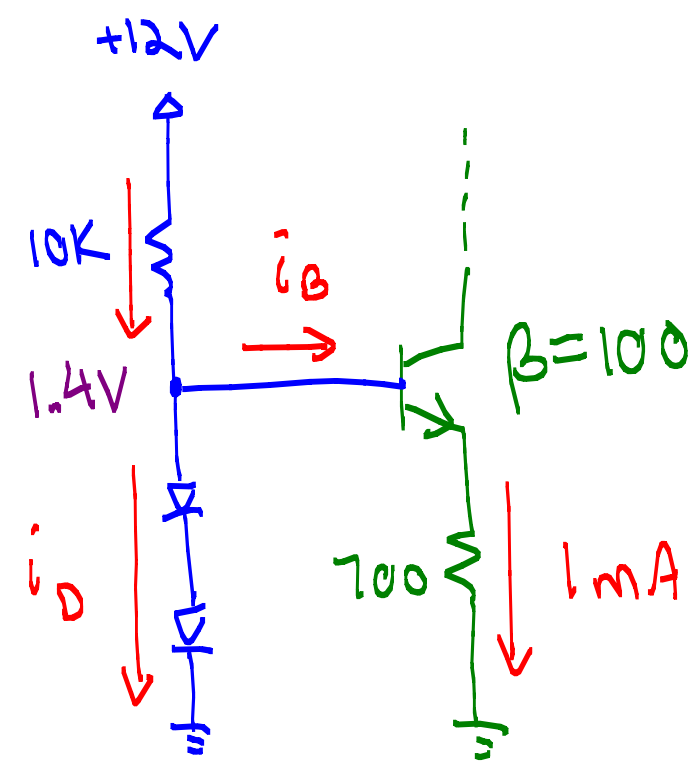

- For BJT diff pair, the current source often operates from negative voltage.

- Assuming diodes have enough current,


$$I_E = \frac{1.4 - 0.7}{3.3 \text{ K}} = 0.21 \text{ mA}$$

$$I_T = 0.99 \times 0.21 = 0.207 \text{ mA}$$

Check diodes:


$$i_D = \frac{0 - (-12 + 1.4)}{10 \text{ K}} - \frac{0.21 \text{ mA}}{100 + 1}$$
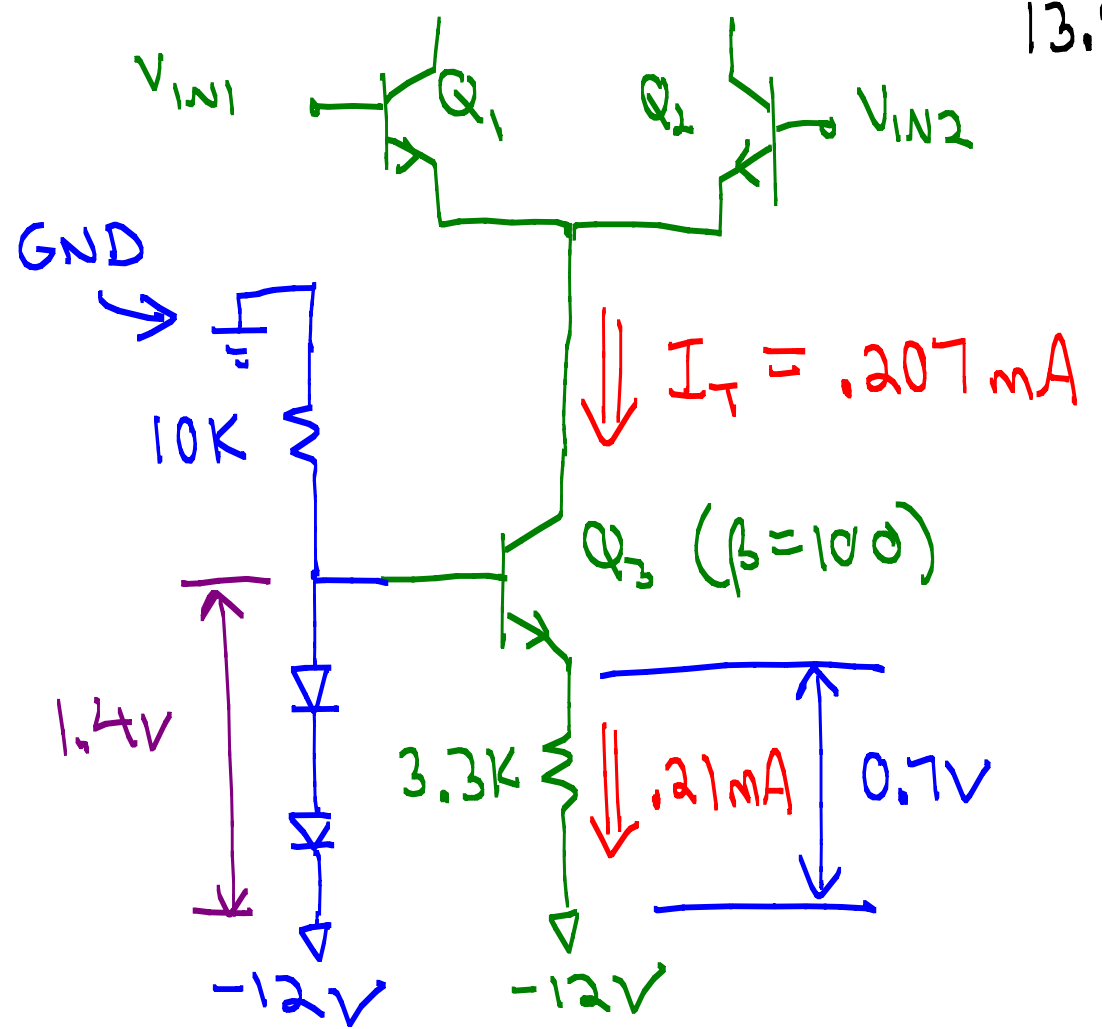
$$= 1.06 \text{ mA} - 0.002 \text{ mA} = 1.058 \text{ mA}$$




• But what is the CMRR?

Ideal Current Source

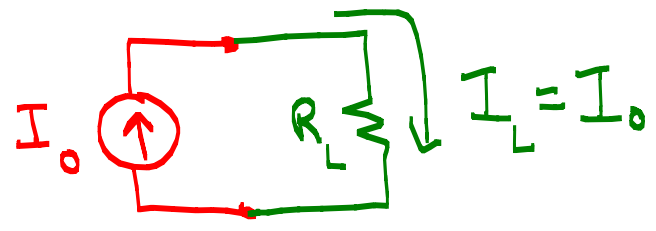

Real Current source



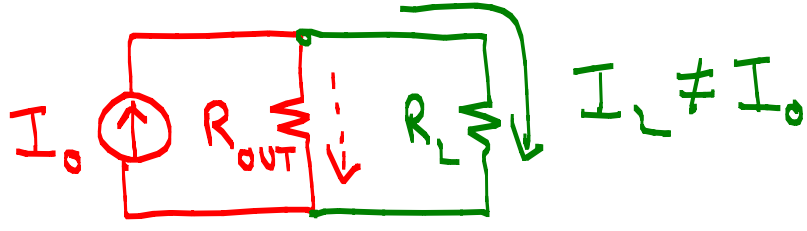


→ Output impedance R_OUT < ∞

So, $CMRR = 20 \log_{10} \left(\frac{R_{OUT}}{r_{e'}} \right)$

• For our simple current source,

R_OUT is typically several MΩ.

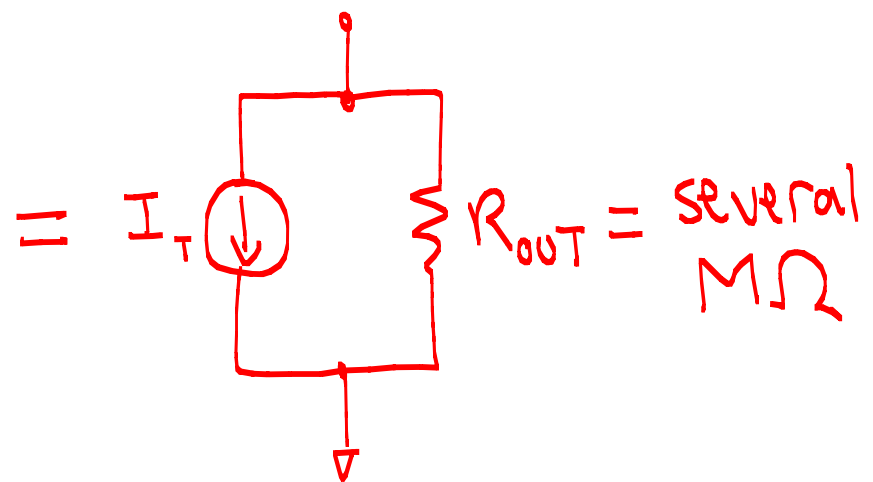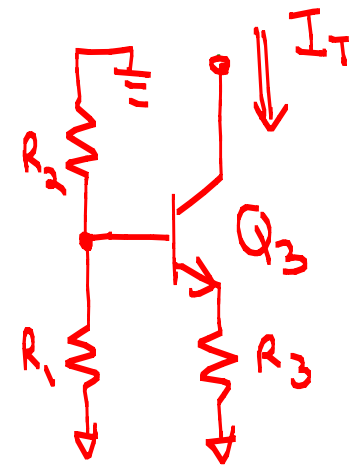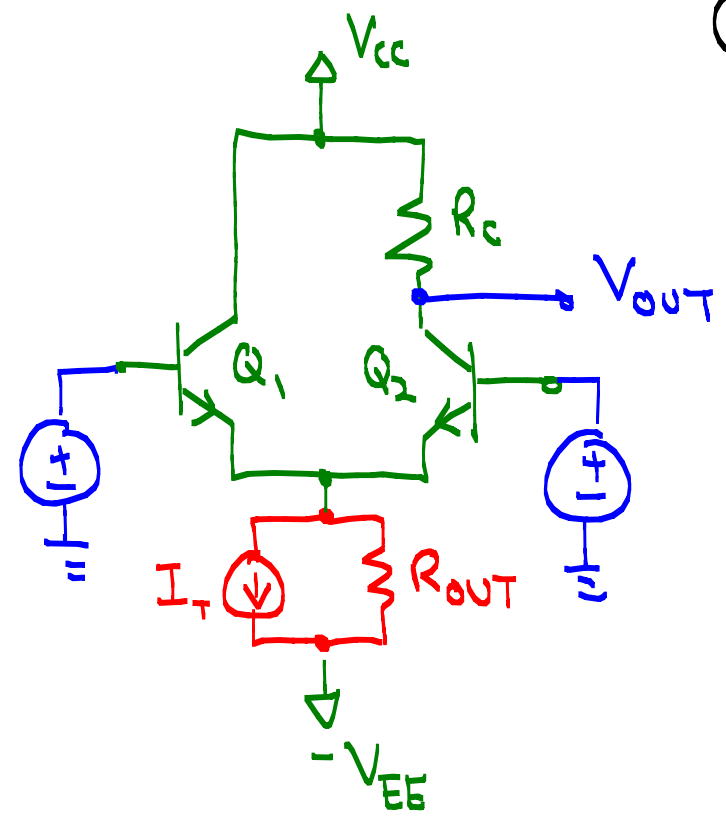

• Design Example ← from Lecture 12

Gain ≥ 50 , $R_{in} \geq 10 \text{ k}\Omega$, $V_{CC} = V_{EE} = 15 \text{ V}$

$R_{in} = 2(\beta + 1)r_{e'} \geq 10 \text{ k}\Omega$

$\frac{0.026 \text{ V}}{q I_T} \rightarrow r_{e'} \geq 49.5 \Omega$


$I_T \leq 1.06 \text{ mA}$

Current Source:

$I_T = \alpha \frac{1.4 - V_{BE}}{R_2} \leq 1.06 \text{ mA}$

$R_2 \geq 0.65 \text{ k} \Rightarrow \text{Choose } R_2 = 680 \Omega$

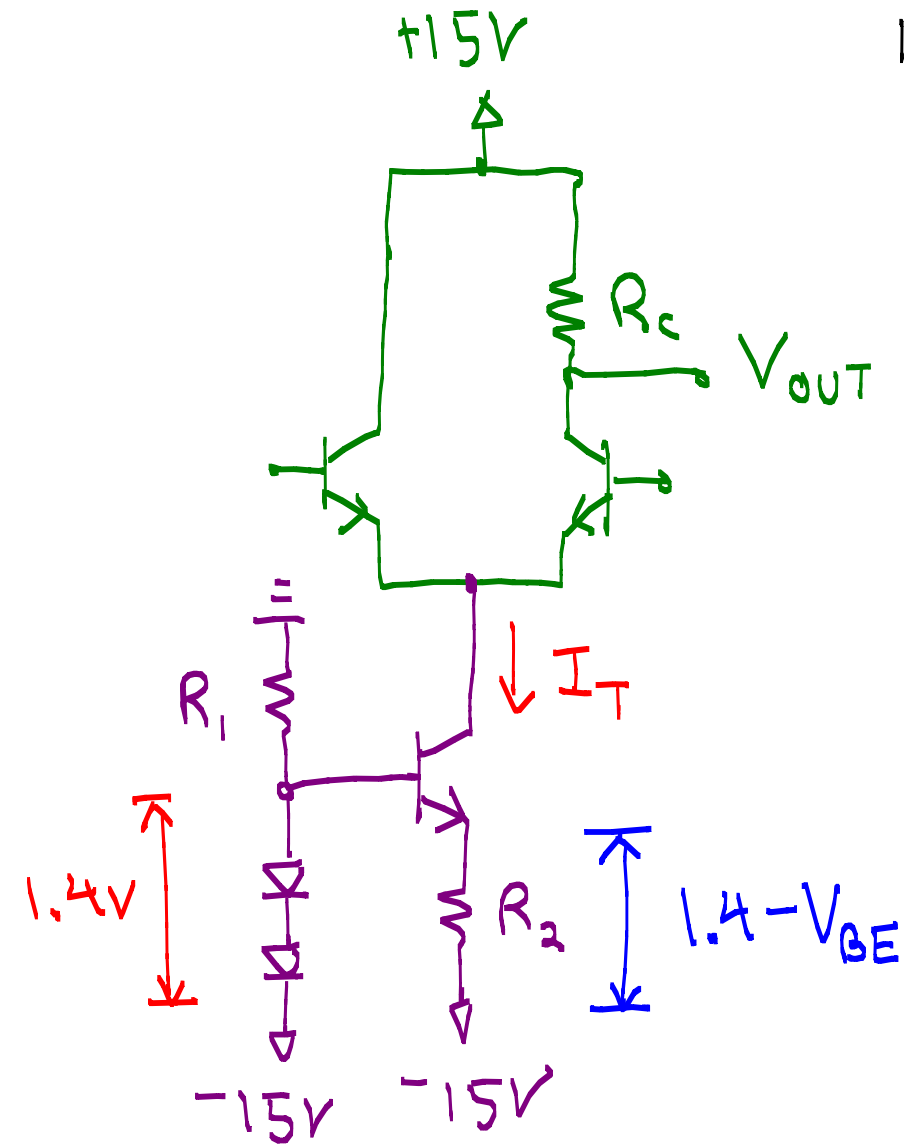$\Rightarrow I_T = .99 \frac{0.7 \text{ V}}{680 \Omega} = 1.02 \text{ mA} \checkmark$, $r_{e'} = 51.0 \Omega \checkmark$




- R_1 ? Want $i_D \approx 1 \text{ mA}$ (not critical)

$$i_D = i_1 - i_B = \frac{0 - (-13.6\text{V})}{R_1} - \frac{1}{101} \frac{0.7\text{V}}{680\Omega} \approx 1 \text{ mA}$$

$$\Rightarrow R_1 = 13.5 \text{ K}$$

$$\Rightarrow \text{Choose } \boxed{R_1 = 13 \text{ K}}$$

(15K would also be fine)

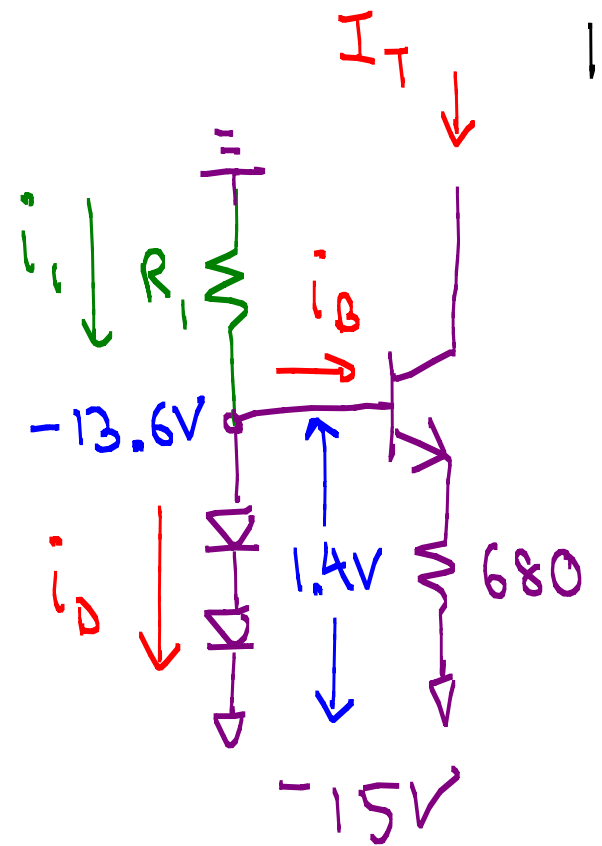

- CMRR? Assuming $R_{out} \sim 2 \text{ M}\Omega$

$$\text{CMRR} = 20 \log_{10} \left(\frac{3000 \text{ K}}{.051 \text{ K}} \right) = 91.9 \text{ dB} \quad \left. \begin{array}{l} \text{MUCH higher} \\ \text{than using} \\ \text{tail resistor } (\sim 41 \text{ dB}) \end{array} \right\}$$

- R_c ? $A_d = \frac{2R_c}{2r_e} \approx 50 \Rightarrow R_c \approx 5.15 \text{ K}$

$$\text{Choose } \boxed{R_c = 5.6 \text{ K}}$$