

Lecture 14: Filters

0. Review

1. Passive Filters

2. Active Filters

- PreLab 5b (Multisim) due at lab session
- HW 6 due this Fri (Nov 08)
- Exam #2 next Tue (Nov 12)

Textbook Reading:

- 19-1 Ideal Responses
- 19-2 Approximate Responses
- 19-3 Passive Filters
- 19-4 First order stages
- 19-5 VCVS unity-gain 2nd order LPF
- 19-6 Higher order filters

- HW 4, 5, 6
- Q 24, 5, 6 ← sample on website
- Sample exam on course website

0. Review

$$V_{OUT} = V_{CQ} + \underbrace{A_d \Delta V_{IN} + A_{CM} V_{CM}}_{\Delta V_{OUT}}$$

$$\Delta V_{IN} = V_{IN1} - V_{IN2}$$

$$V_{CM} = \frac{1}{2} (V_{IN1} + V_{IN2})$$

$$A_d = \frac{2 R_c}{2 r_{e1}}$$

$$A_{CM} = -\frac{2 R_c}{2 R_{EF}}$$

$$CMRR = 20 \log_{10} \left| \frac{A_d}{A_{CM}} \right|$$



$$= 20 \log_{10} \left(\frac{R_c}{r_{e1}} \right)$$

$$A_d = \frac{2 R_c}{2 r_{e1}}$$

$$A_{CM} = -\frac{2 R_c}{2 R_{OUT}}$$

$$CMRR = 20 \log_{10} \left| \frac{A_d}{A_{CM}} \right|$$
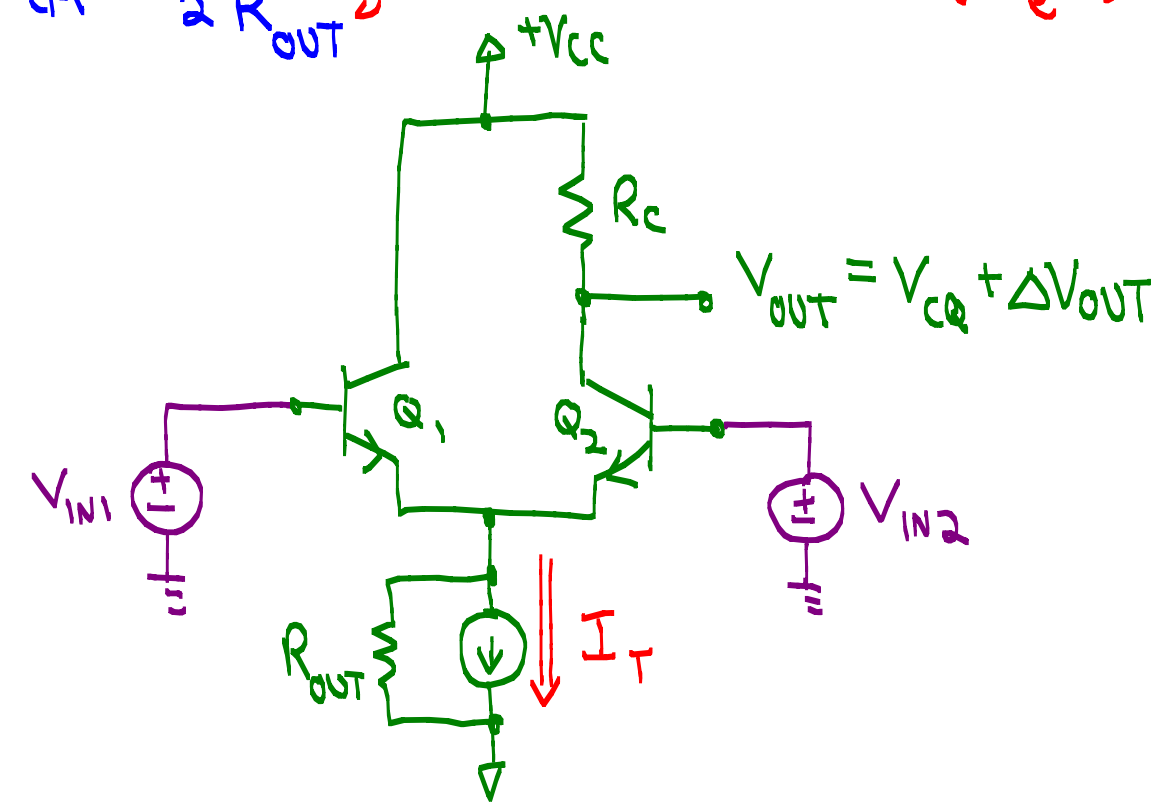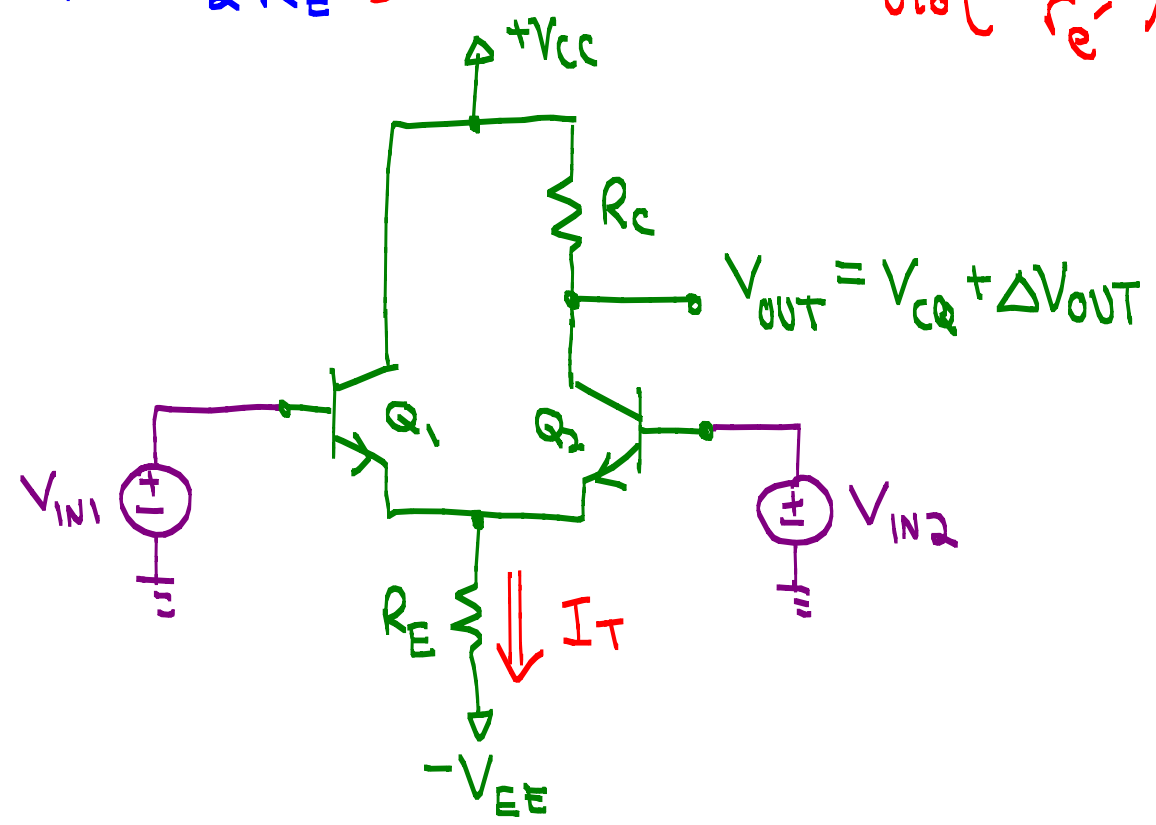
$$= 20 \log_{10} \left(\frac{R_{OUT}}{r_{e1}} \right)$$



1. Passive Filters

A. Intro


- In many applications, the desired signal competes with noise.

Need a filter to clean up the signal!

Ex: ECG




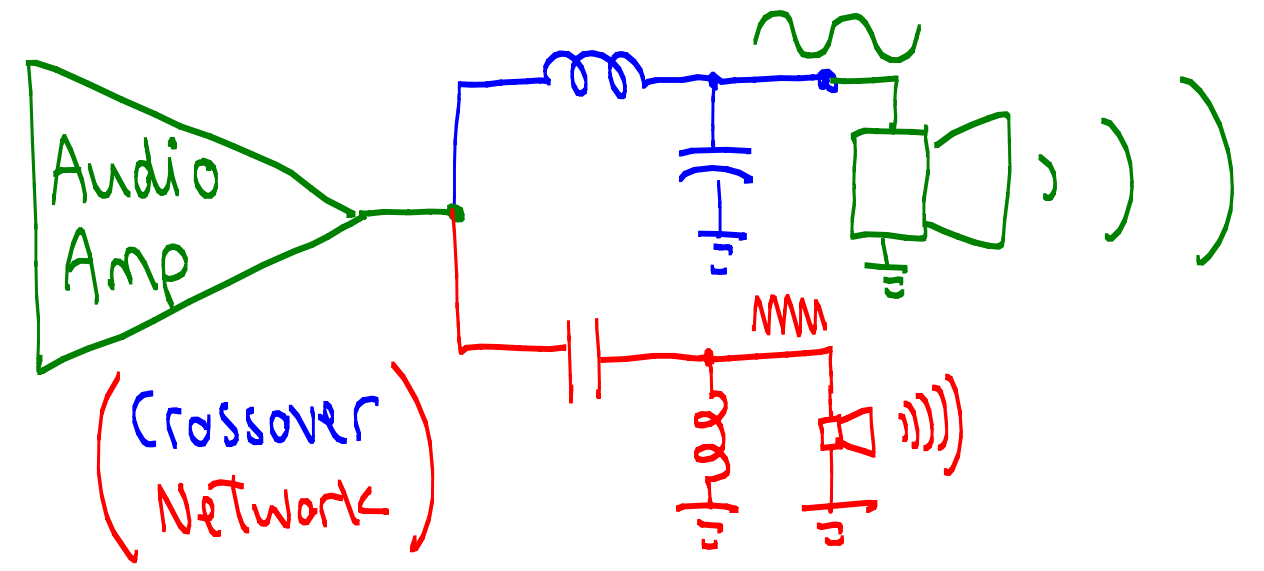- Other applications use filters to separate signals.



- We will only discuss low-pass filters, but most concepts apply to high-pass and band-pass filters.

B. Filter Parameters

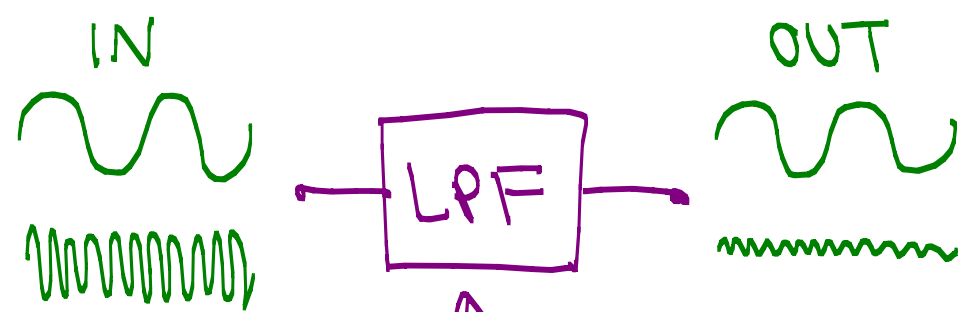

$$\text{Filter gain} = \left| \frac{V_{OUT}}{V_{IN}} \right|$$


- The gain of a low-pass filter has three "frequency zones":

Pass band

$f_c \equiv$ cut-off frequency (or passband edge)

$A_p \equiv$ passband ripple

Decibels

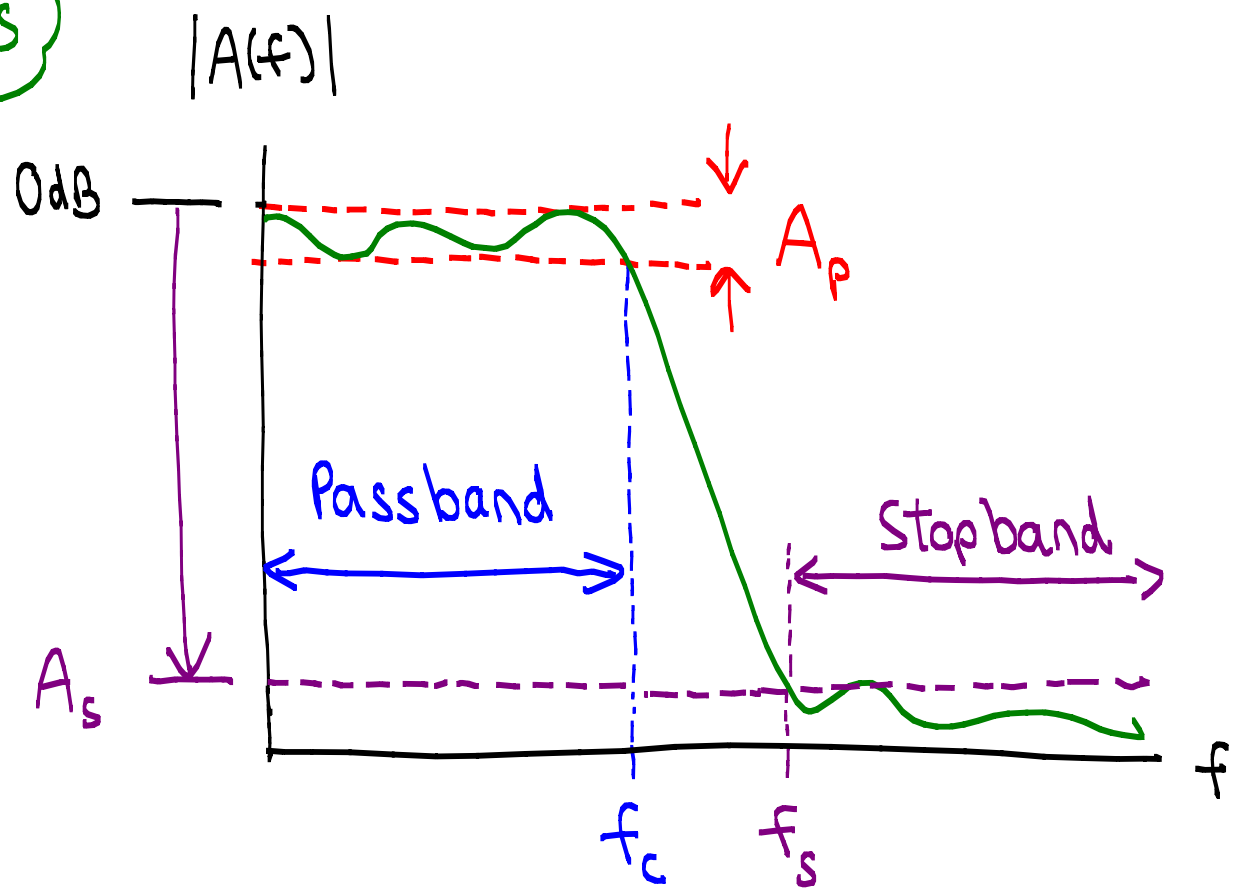

Transition

Steepness (roll off) depends on filter order

Stopband



$f_s \equiv$ Stopband edge

$A_s \equiv$ Stopband gain

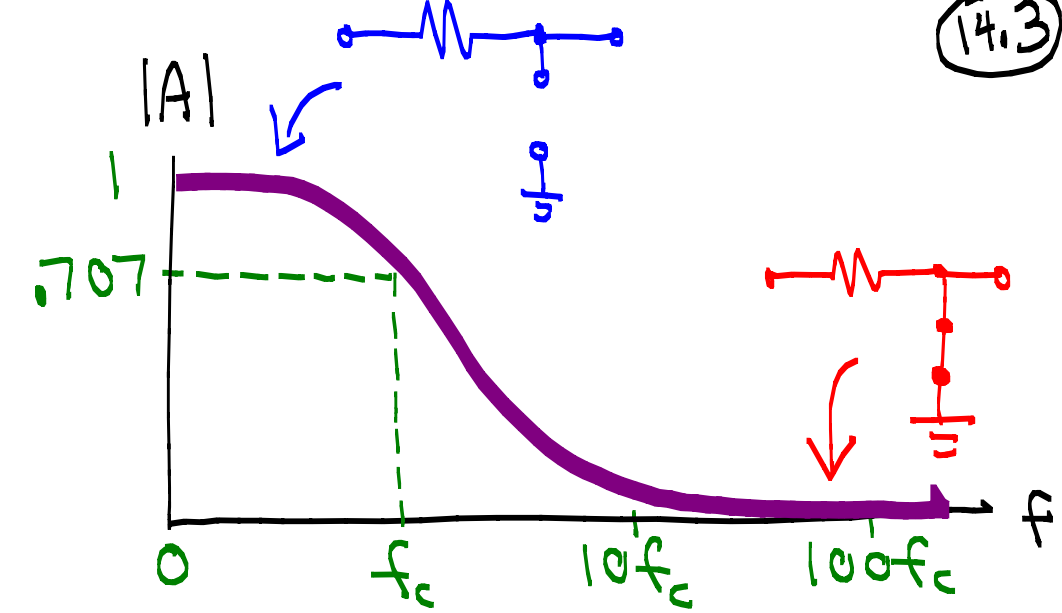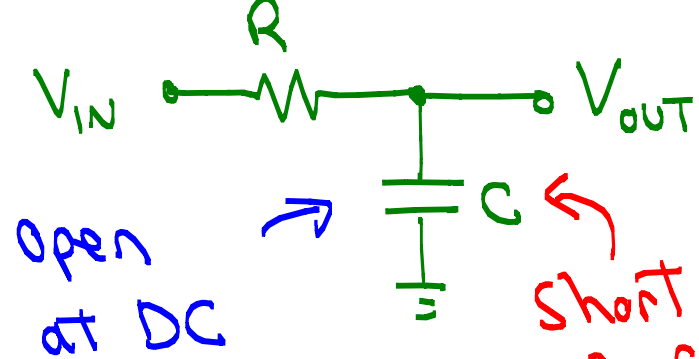C. Passive RC Filter (1st order filter)

$$V_{OUT} = V_{IN} \frac{Z_c}{Z_c + R}$$


$$= V_{IN} \frac{1/j\omega C}{1/j\omega C + R} = V_{IN} \frac{1}{1 + j\omega RC}$$



Filter Gain $\equiv A(f) = \frac{V_{out}(f)}{V_{in}(f)} = \frac{1}{1 + j f/f_c}$

"Cut-off" frequency $f_c = \frac{1}{2\pi RC}$

$$|A(f)| = \frac{1}{\sqrt{1 + (f/f_c)^2}} \approx \begin{cases} 1, & f \ll f_c \\ \frac{1}{(f/f_c)}, & f \gg f_c \end{cases}$$

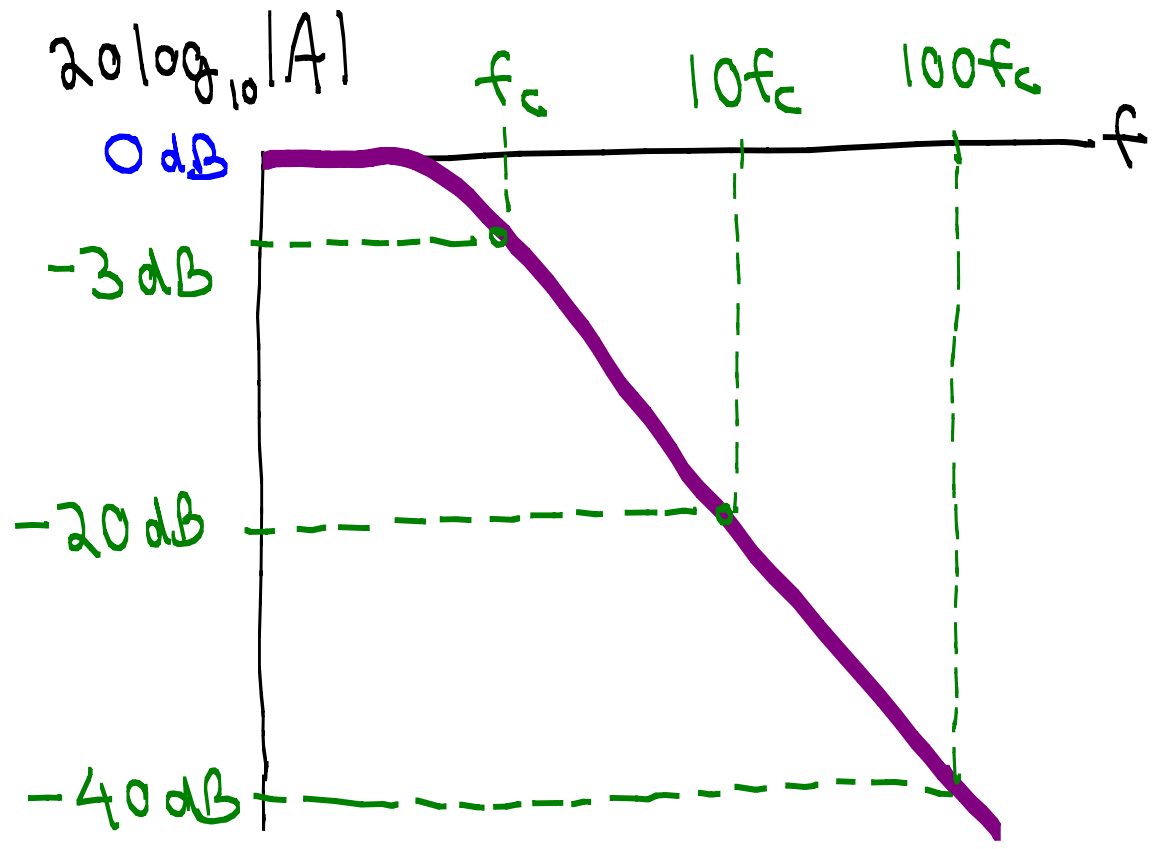

D. Passive LC filter

An LC circuit can produce faster freq roll off.




$$\Rightarrow \frac{V_{OUT}}{V_{IN}} = \frac{\frac{1}{j\omega C} // R}{\frac{1}{j\omega C} // R + j\omega L} = \frac{\frac{R}{1 + j\omega RC}}{\frac{R}{1 + j\omega RC} + j\omega L}$$

$$= \frac{1}{1 + j\omega \frac{L}{R} (1 + j\omega RC)} = \frac{1}{1 + j\omega \frac{L}{R} - \omega^2 LC}$$

$$= \frac{1}{1 + j \frac{\omega}{\omega_0 Q} - \omega^2 / \omega_0^2}$$


$$\left\{ \begin{aligned} \omega_0 &= \frac{1}{\sqrt{LC}} \\ Q &= \frac{1}{\omega_0} R/L \end{aligned} \right.$$

$$\left| \frac{V_{OUT}}{V_{IN}} \right| = \frac{1}{\sqrt{1 - (2 - \frac{1}{Q^2}) \frac{\omega^2}{\omega_0^2} + \frac{\omega^4}{\omega_0^4}}} \leftarrow \text{2nd order response} \rightarrow$$

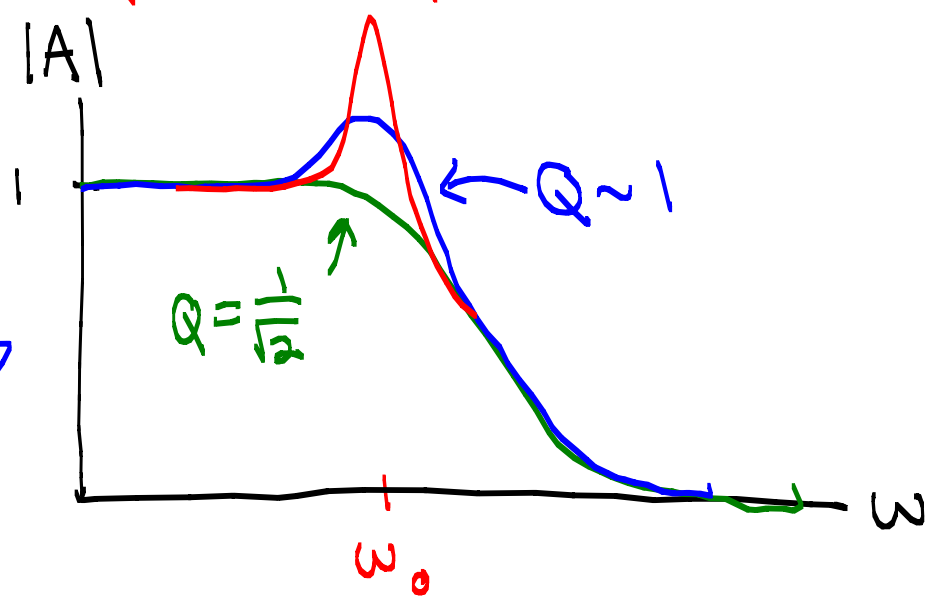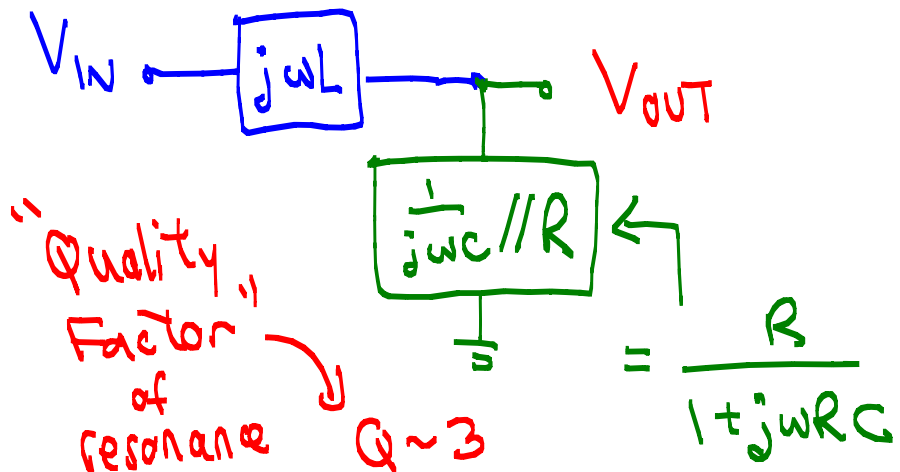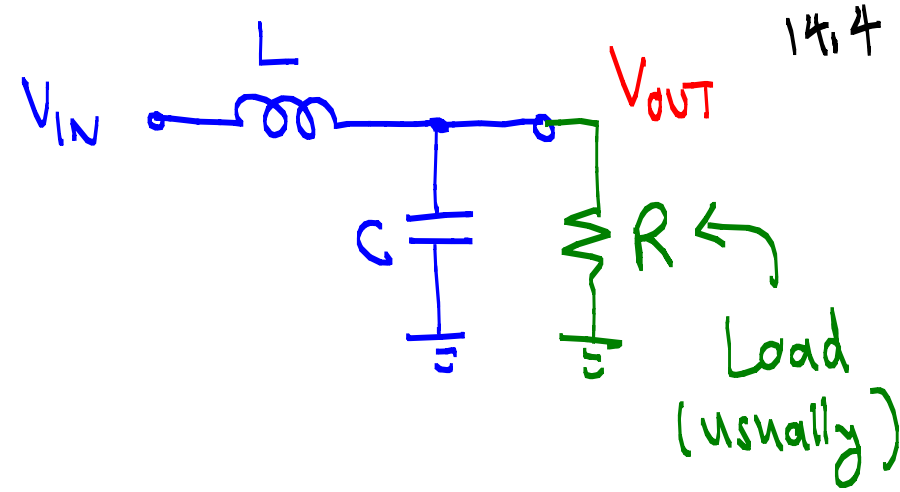


- Simple RC filter (1st order filter) is OK if a gradual rolloff is acceptable.

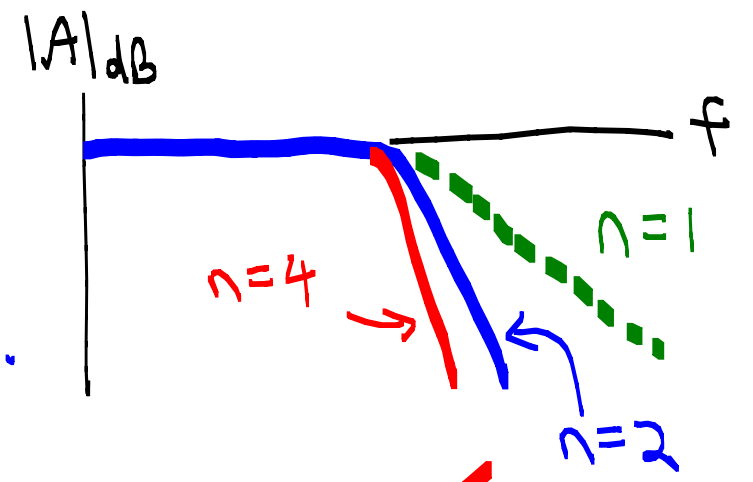→ Higher order filters have sharper cut-off.




Q: Higher order = Multiple passive filters?

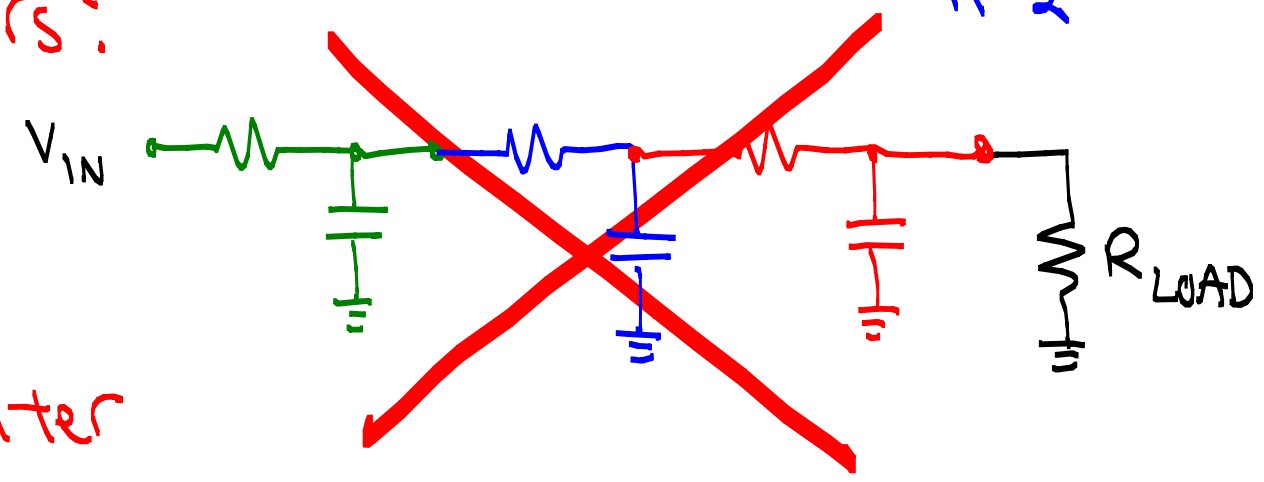A: NO! Each section's input impedance loads the previous section ☹️



→ Difficult to design a high order filter

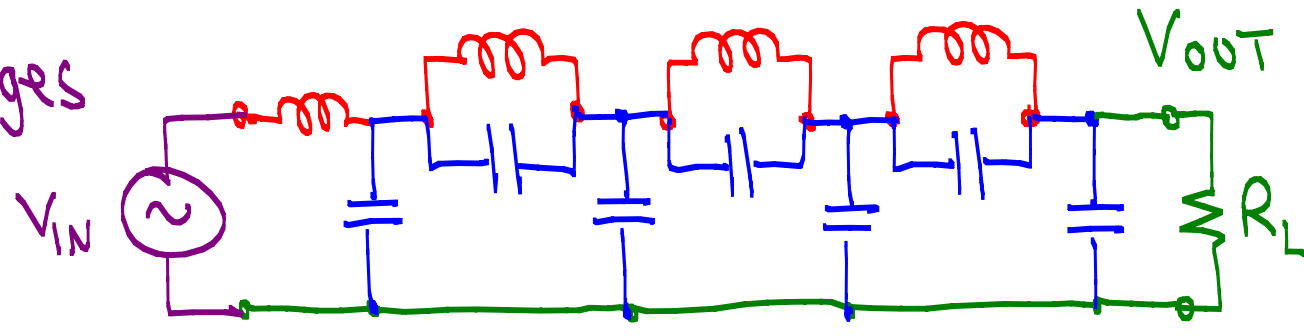- Passive RLC filters with multiple stages can achieve very sharp cut-off.



Disadvantage: Inductors are not easy to use.

Q: Can we make inductorless filters with same properties as RLC circuits?

2. Active Filters

→ Active filters can produce very steep roll-off without inductors!



• Butterworth Filter

$$|A(f)| = \frac{1}{\sqrt{1 + (f/f_c)^{2n}}}$$

→ Produces the flattest passband ($A_p = 0$ dB)

→ BUT, transition steepness is less than some other filter types.

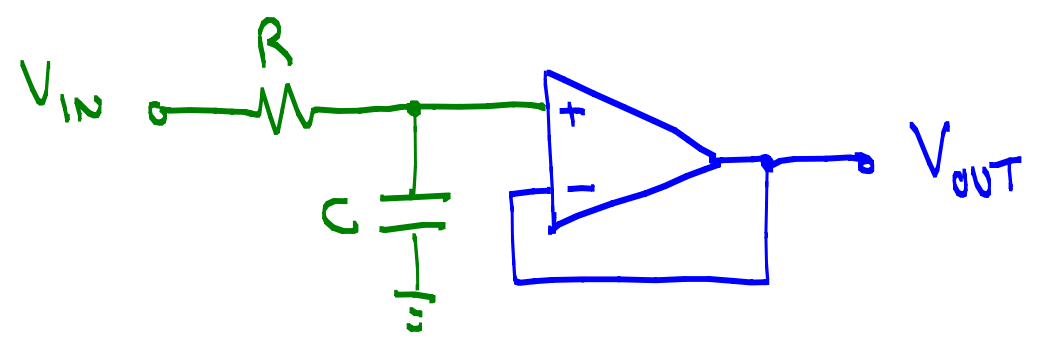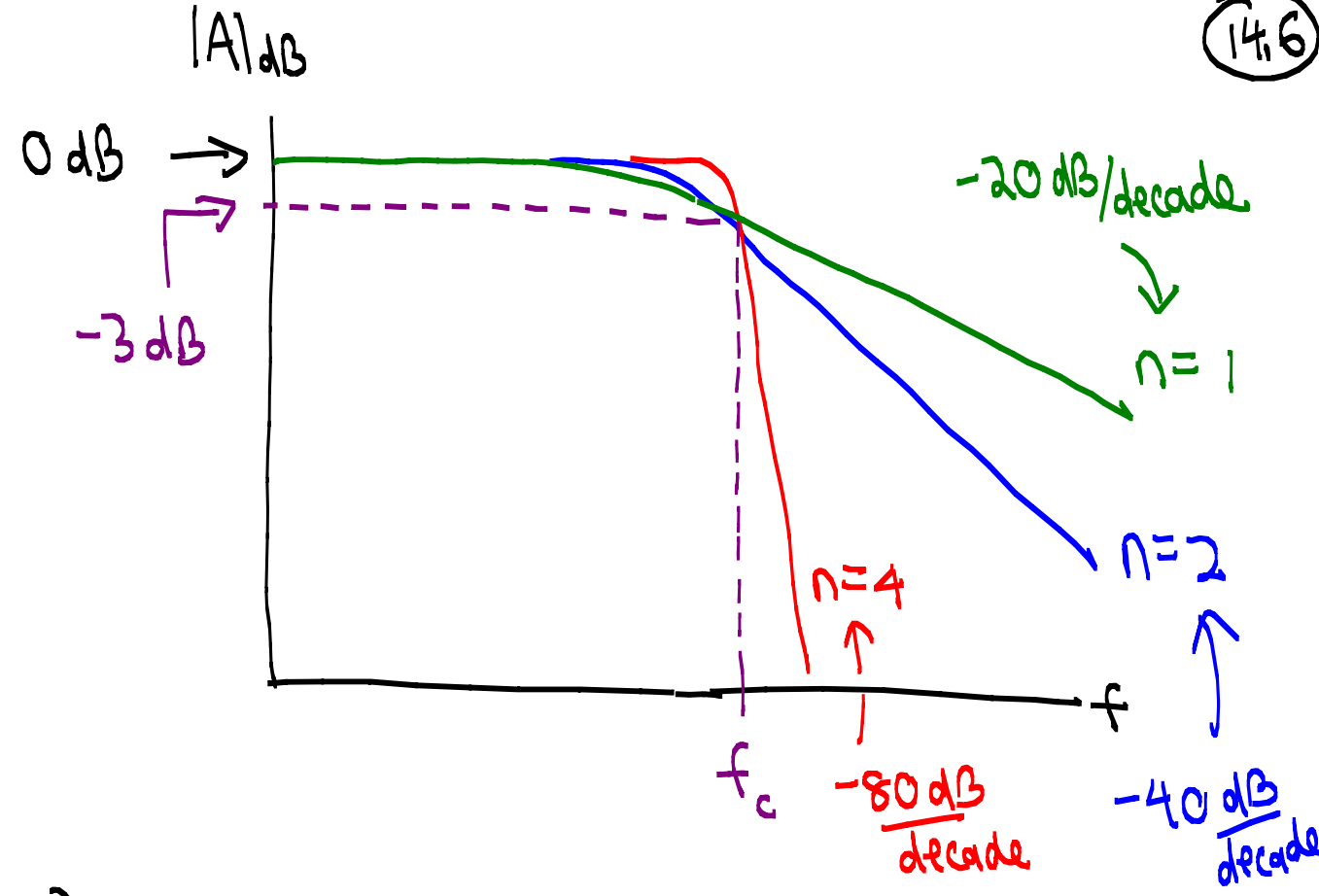1st order Butterworth ($n=1$)
Just add a buffer!




$$\Rightarrow |A| = \frac{1}{\sqrt{1 + (f/f_c)^2}}, \quad f_c = \frac{1}{2\pi RC}$$

2nd order Butterworth

$$|A| = \frac{1}{\sqrt{1 + (f/f_c)^4}}$$

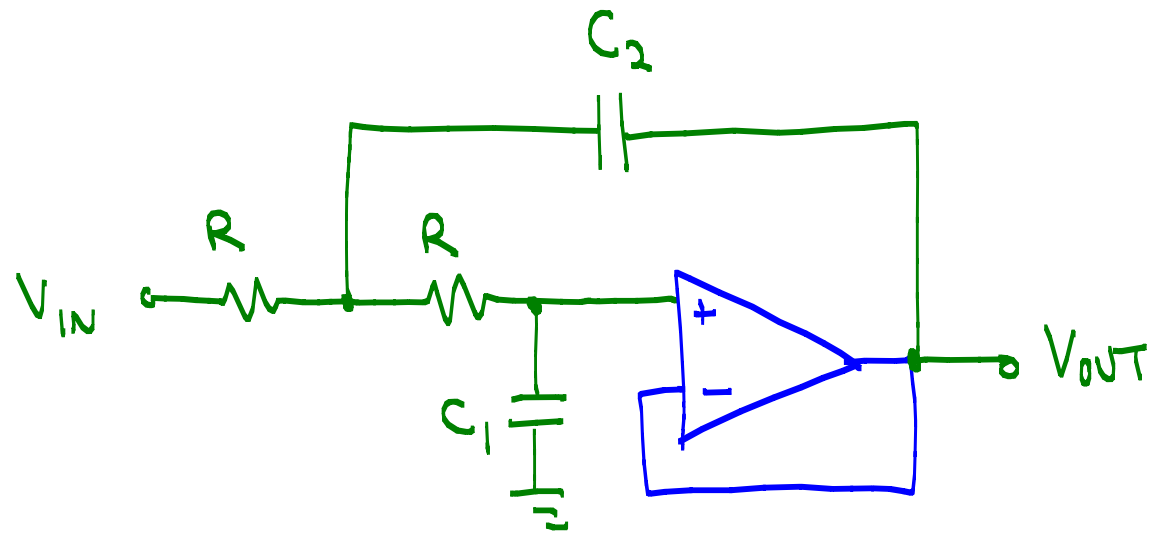- A simple implementation is to use a "Sallen-and-Key" design.



Example

$R = 30\text{ k}$, $C_1 = 820\text{ pF}$
 $C_2 = 1.64\text{ nF}$

① $Q = \frac{1}{2} \sqrt{\frac{C_2}{C_1}} = 0.707$

↑

"Quality Factor"

$\Rightarrow C_2 = 2C_1$



- Is Q correct? $\frac{C_2}{C_1} = 2 \Rightarrow Q = \frac{1}{2} \sqrt{2} = \underline{\underline{0.707}}$ ✓

② $f_c = \frac{1}{2\pi R \sqrt{C_1 C_2}}$

• $f_c?$ $f_c = \underline{\underline{4.58\text{ kHz}}}$

Design Example

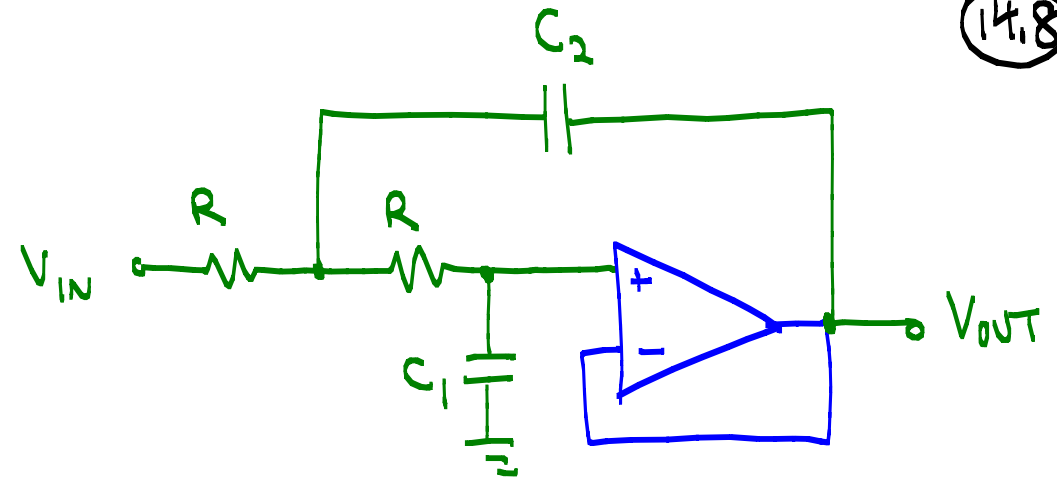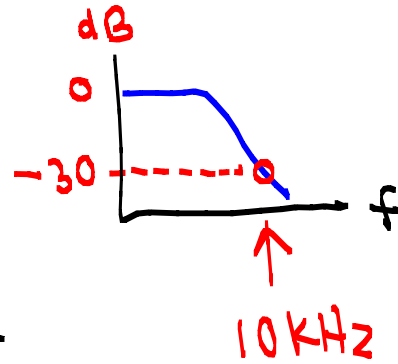2nd order Butterworth LPF
with -30 dB gain at 10 kHz



① $A_{dB} = -30 \text{ dB} = 20 \log_{10} |A|$

$\Rightarrow |A| = 10^{-30/20} = 0.0316 \text{ at } f = 10 \text{ kHz}$

$C_2 = 2C_1$

② $|A| = \frac{1}{\sqrt{1 + \left(\frac{10^4 \text{ Hz}}{f_c}\right)^4}} = 0.0316$

$\Rightarrow 1000 = 1 + \left(\frac{10^4 \text{ Hz}}{f_c}\right)^4$

$f_c = \frac{10^4}{999^{1/4}} = \underline{\underline{1778.7 \text{ Hz}}}$

③ $f_c = \frac{1}{2\pi R \sqrt{C_1 C_2}} = \frac{1}{2\sqrt{2} \pi R C_1}$

let $C_1 = 1 \text{ nF} \rightarrow R = \frac{1}{2\sqrt{2} \pi (10^{-9}) (1778.7)}$
 $C_2 = 2 \text{ nF}$
 $= 63270.7 \Omega$

5% value \Rightarrow Choose R = 62 K

Higher Order Butterworth


How to make a 4th order Butterworth?

We cannot simply cascade two identical 2nd order Butterworth filters. ☹️


$$|A| = \frac{1}{\sqrt{1 + (f/f_c)^4}} \times \frac{1}{\sqrt{1 + (f/f_c)^4}}$$

$$= \frac{1}{1 + (f/f_c)^4} \neq \frac{1}{\sqrt{1 + (f/f_c)^8}}$$

$$|A| = \frac{1}{\sqrt{1 + (f/f_c)^8}}$$

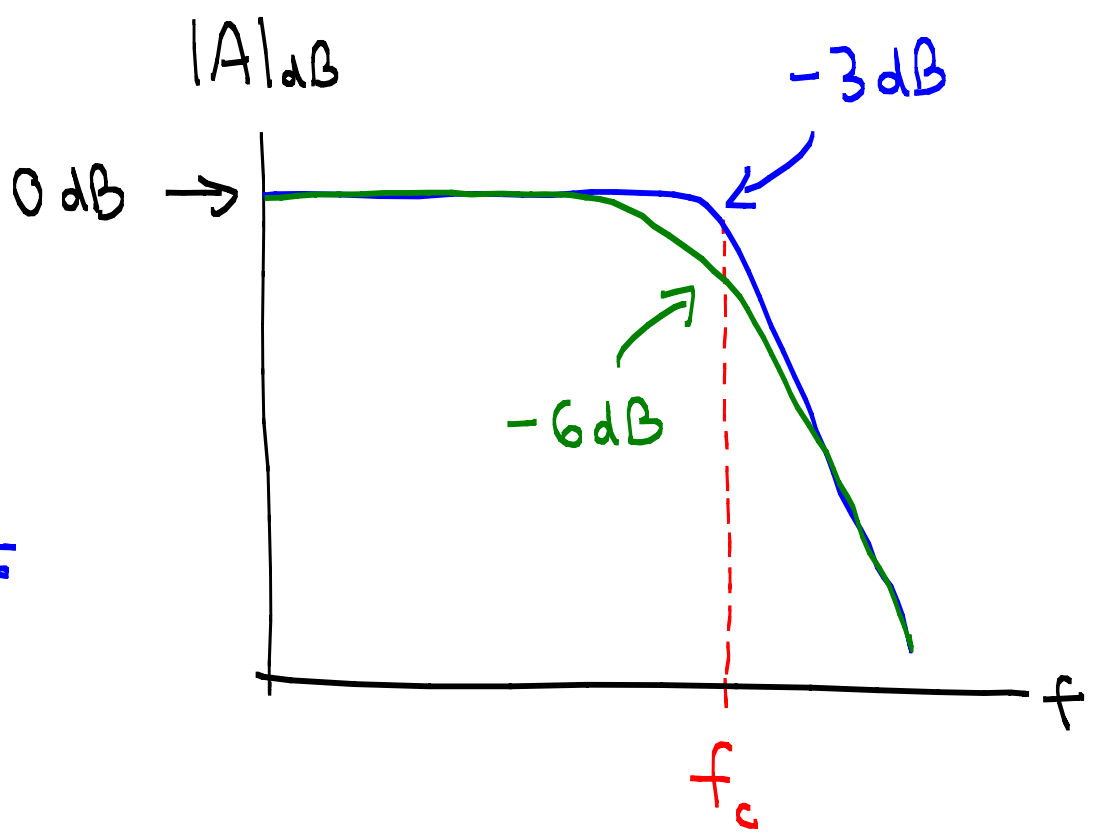

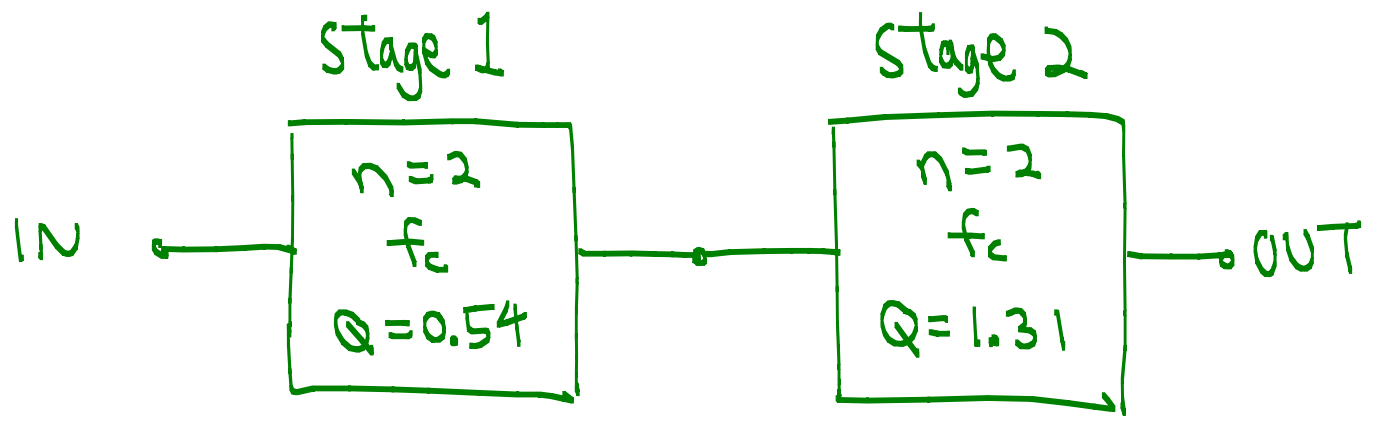- Fortunately, we can cascade two $n=2$ Sallen-Key filters with the same f_c but different Q !



- This "staggered Q " technique can be used for higher orders:

(Table 19-3 in textbook)

	<u>Stage 1</u>	<u>Stage 2</u>	<u>Stage 3</u>	<u>Stage 4</u>	<u>Stage 5</u>
$n=2$.707				
$n=4$.54	1.31			
$n=6$.52	1.93	.707		
$n=8$.51	2.56	0.6	0.9	
$n=10$.51	3.2	.56	1.1	.707

• Chebyshev Filter

→ Produce a steeper transition than Butterworth
BUT, passband has slight ripple!

→ Same op amp circuit, but the filter parameters are slightly more complicated...


$$Q = 0.5 \sqrt{\frac{C_2}{C_1}} > 0.707$$

"Pole Freq" → $f_p = \frac{1}{2\pi R \sqrt{C_1 C_2}}$

"Cut-off freq" → $f_c = K_c f_p$

A_p : Passband ripple ←

Should be < 1 dB

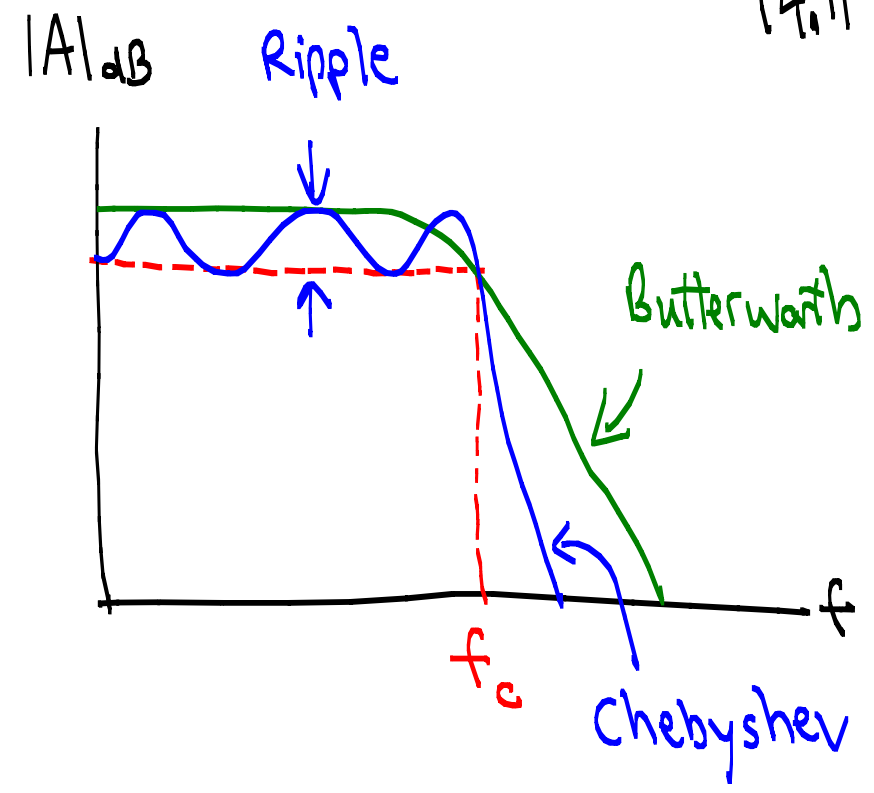

Ex: $n=2$ Chebyshev

→ $A_p = 0.69 \text{ dB}$

$Q = 0.9$

$f_c = 0.874 f_p$