

Lecture 14: Filters

0. Review

1. Passive Filters

2. Active Filters

- PreLab 5b (Multisim) due at lab session
- HW 6 due this Fri (Nov 08)
- Exam #2 next Tue (Nov 12)

Textbook Reading:

- 19-1 Ideal Responses
- 19-2 Approximate Responses
- 19-3 Passive Filters
- 19-4 First order stages
- 19-5 VCVS unity-gain 2nd order LPF
- 19-6 Higher order filters

- HW 4, 5, 6
- Q 24, 5, 6 ← sample on website
- Sample exam on course website

0. Review

$$V_{OUT} = V_{CQ} + \underbrace{A_d \Delta V_{IN} + A_{CM} V_{CM}}_{\Delta V_{OUT}}$$

$$\Delta V_{IN} = V_{IN1} - V_{IN2}$$

$$V_{CM} = \frac{1}{2} (V_{IN1} + V_{IN2})$$

$$A_d = \frac{2 R_c}{2 r_{e1}}$$

$$A_{CM} = -\frac{2 R_c}{2 R_{EF}}$$

$$CMRR = 20 \log_{10} \left| \frac{A_d}{A_{CM}} \right|$$



$$= 20 \log_{10} \left(\frac{R_c}{r_{e1}} \right)$$

$$A_d = \frac{2 R_c}{2 r_{e1}}$$

$$A_{CM} = -\frac{2 R_c}{2 R_{OUT}}$$

$$CMRR = 20 \log_{10} \left| \frac{A_d}{A_{CM}} \right|$$
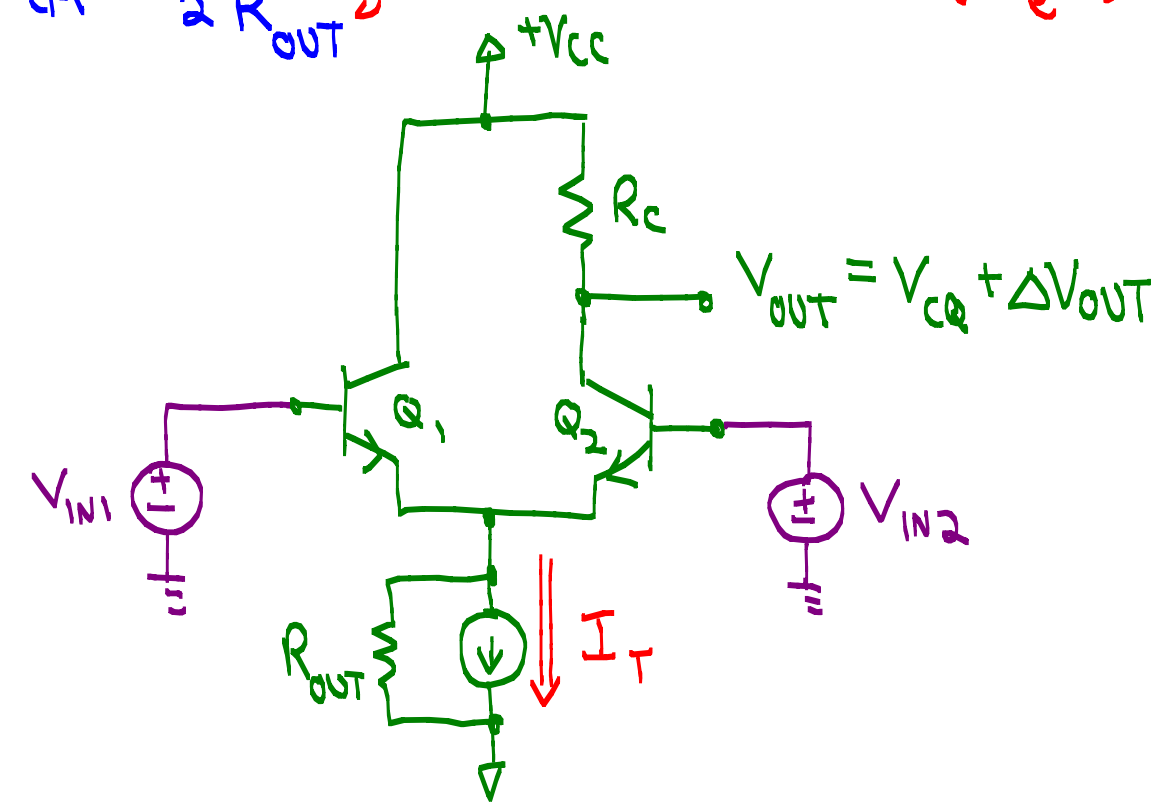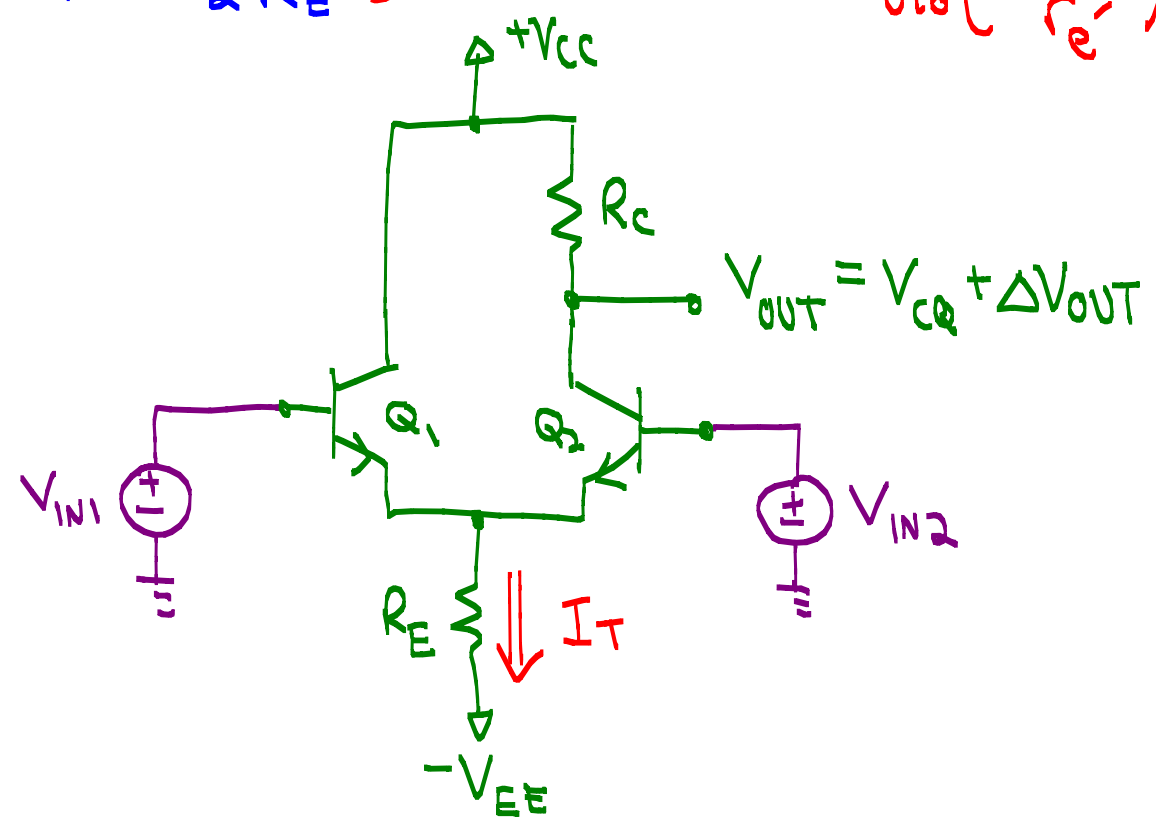
$$= 20 \log_{10} \left(\frac{R_{OUT}}{r_{e1}} \right)$$




1. Passive Filters



A. Intro

- In many applications, the desired signal competes with noise.

Ex: ECG

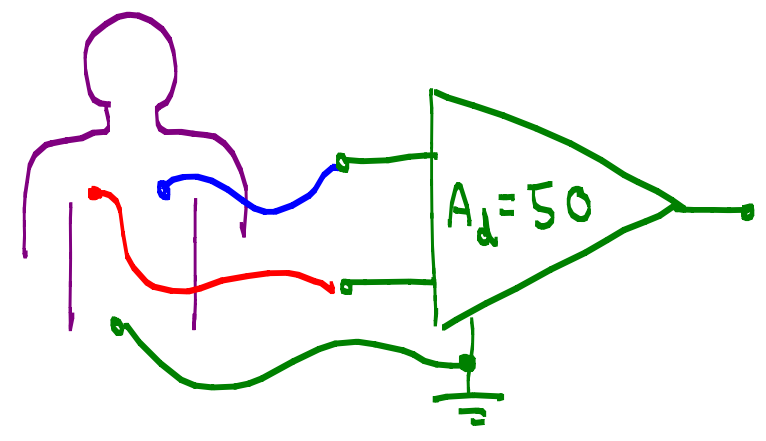


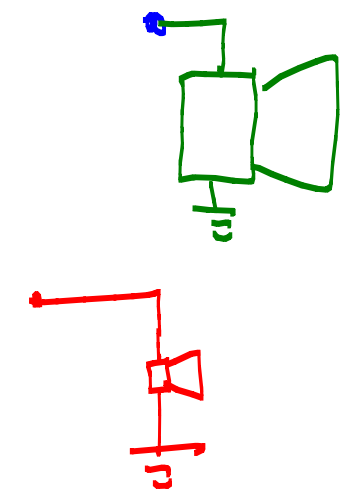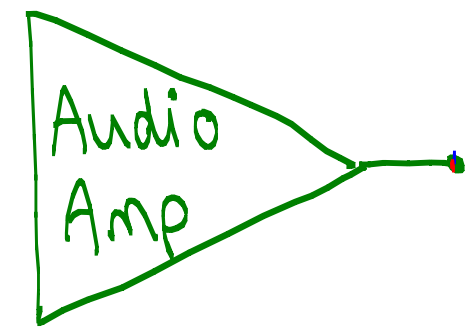- Other applications use filters to separate signals.




- We will only discuss low-pass filters, but most concepts apply to high-pass and band-pass filters.

B. Filter Parameters

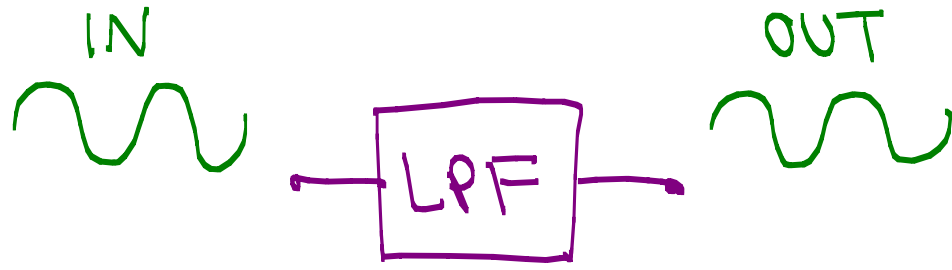


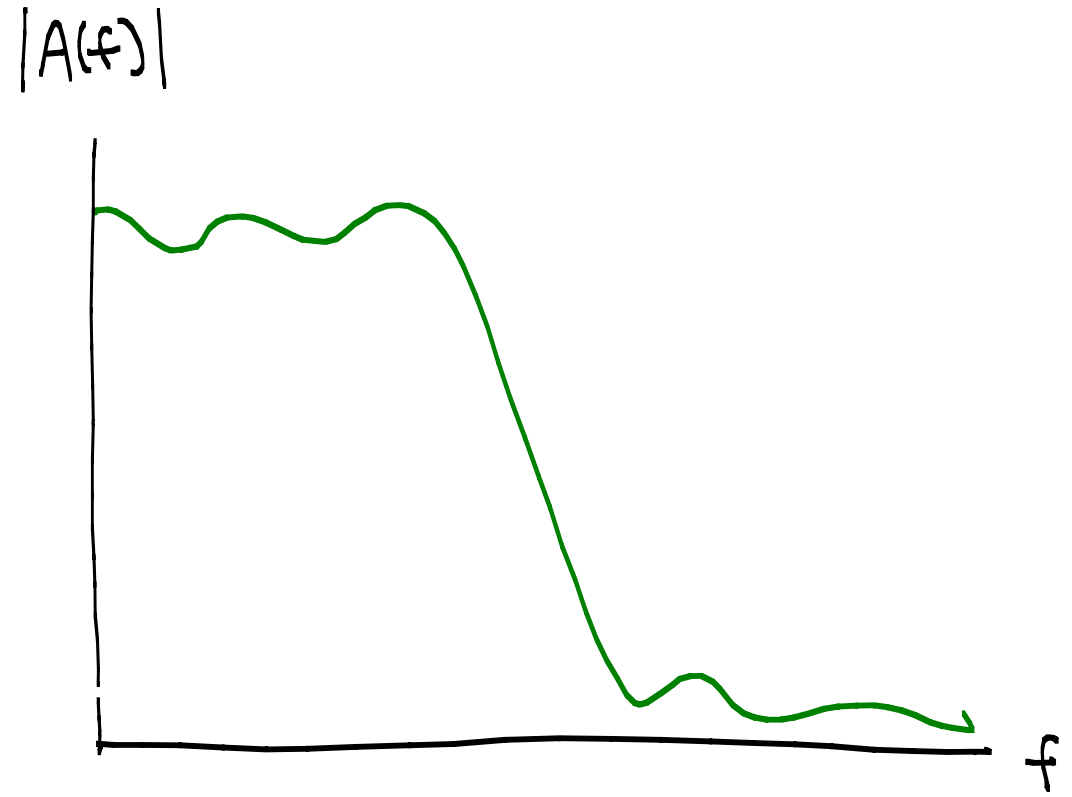- The gain of a low-pass filter has three "frequency zones":





C. Passive RC Filter (1st order filter)

$V_{OUT} =$

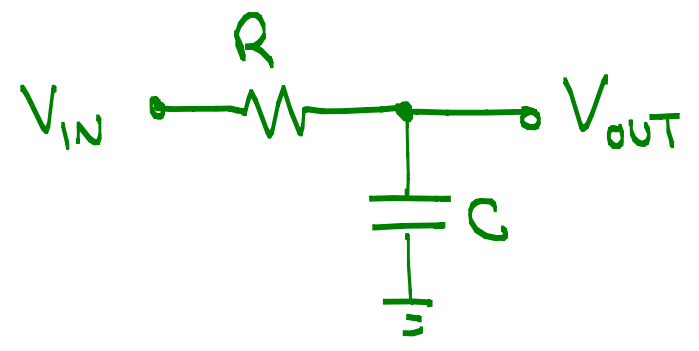

Filter
Gain


$|A(f)|$

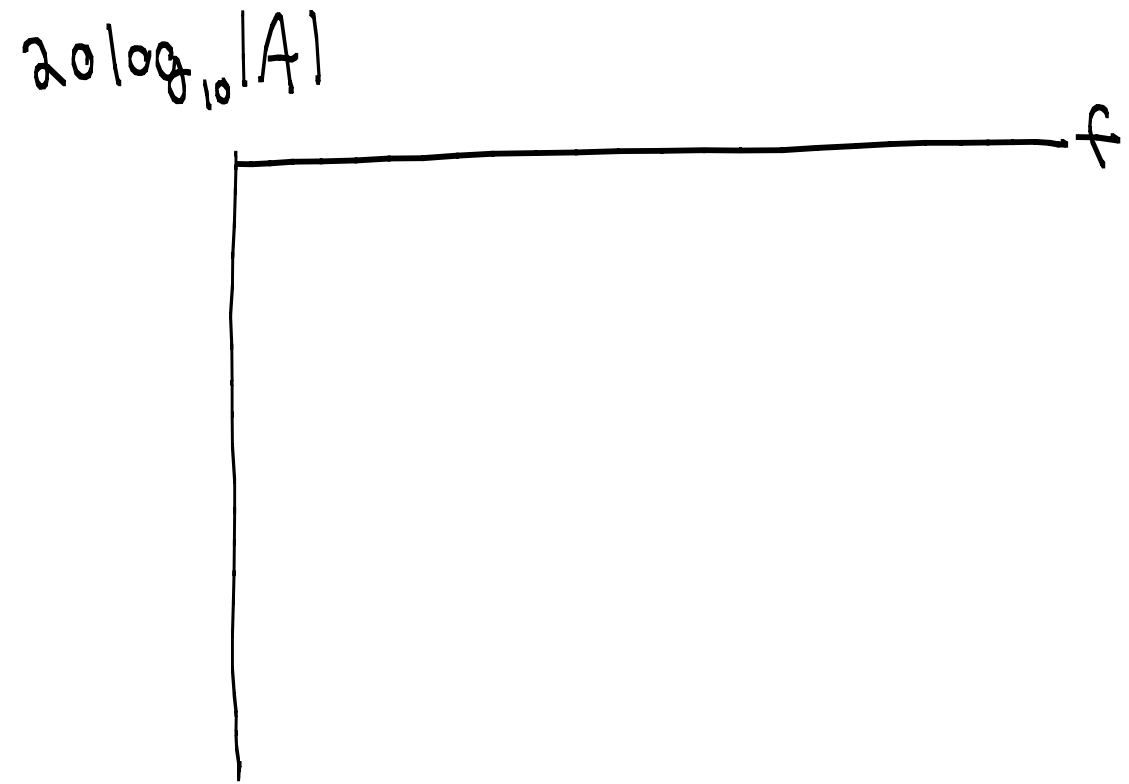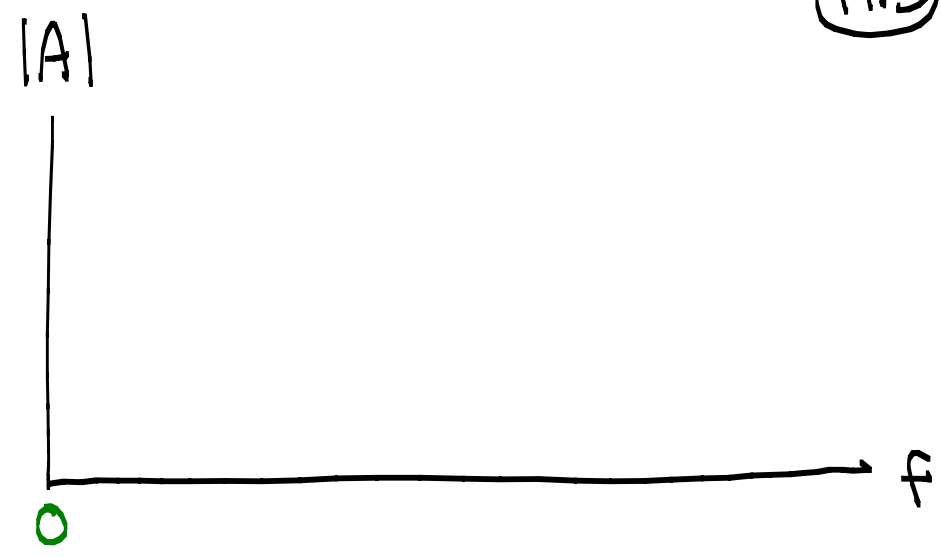

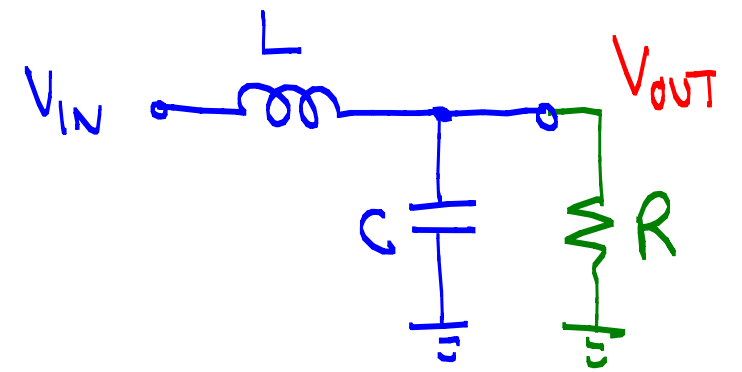
D. Passive LC filter

An LC circuit can produce faster freq roll off.


$$\Rightarrow \frac{V_{OUT}}{V_{IN}} = 1$$



14.4

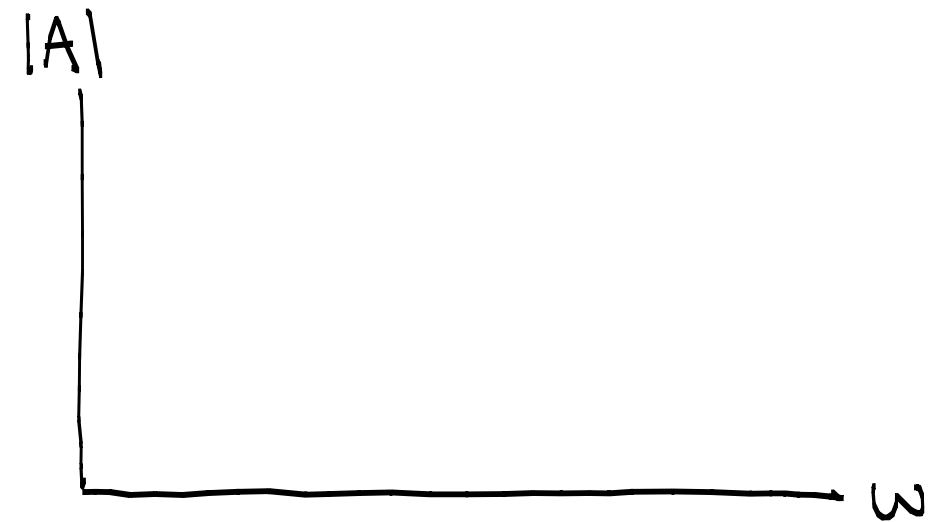

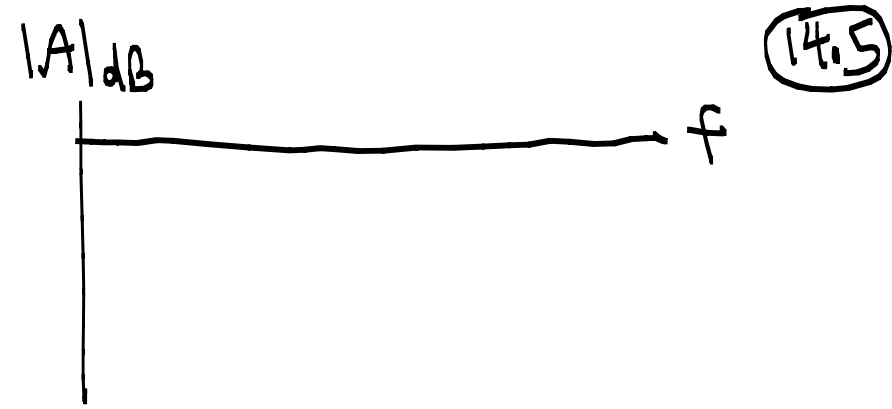
- Simple RC filter (1st order filter)
is OK if a gradual rolloff is acceptable.



Q: Higher order = Multiple passive filters?

A: NO!

V_{IN} ↑

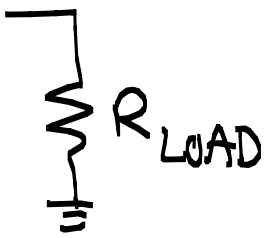

Disadvantage:

Q: Can we make _____ filters with same properties as RLC circuits?

2. Active Filters

→ Active filters can produce very steep roll-off without inductors!

- Butterworth Filter

$$|A(f)| =$$



1st order Butterworth ($n=1$)

2nd order Butterworth

$$|A| = \frac{1}{\sqrt{1 + \omega^4}}$$

- A simple implementation is to use a "Sallen-and-Key" design.

① $Q =$

② $f_c =$

Example

$$R = 30 \text{ k}, \quad C_1 = 820 \text{ pF}$$

$$C_2 = 1.64 \text{ nF}$$

- Is Q correct?

- f_c ?


Design Example

2nd order Butterworth LPF
with -30 dB gain at 10 kHz

①

②

③

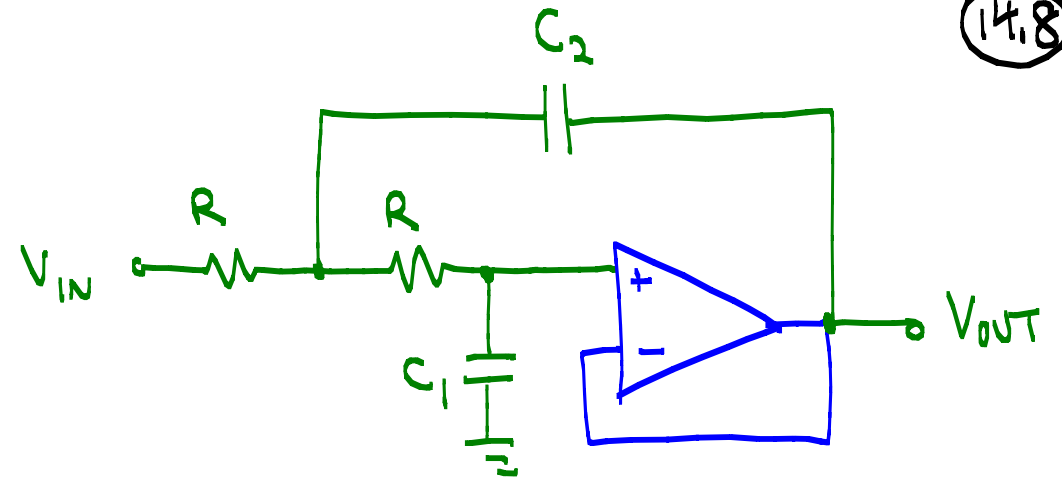

- Higher Order Butterworth

How to make a 4th order Butterworth?


We cannot simply cascade two identical 2nd order Butterworth filters.

$$|A| = \frac{1}{\sqrt{\quad}}$$

$|A|_{dB}$



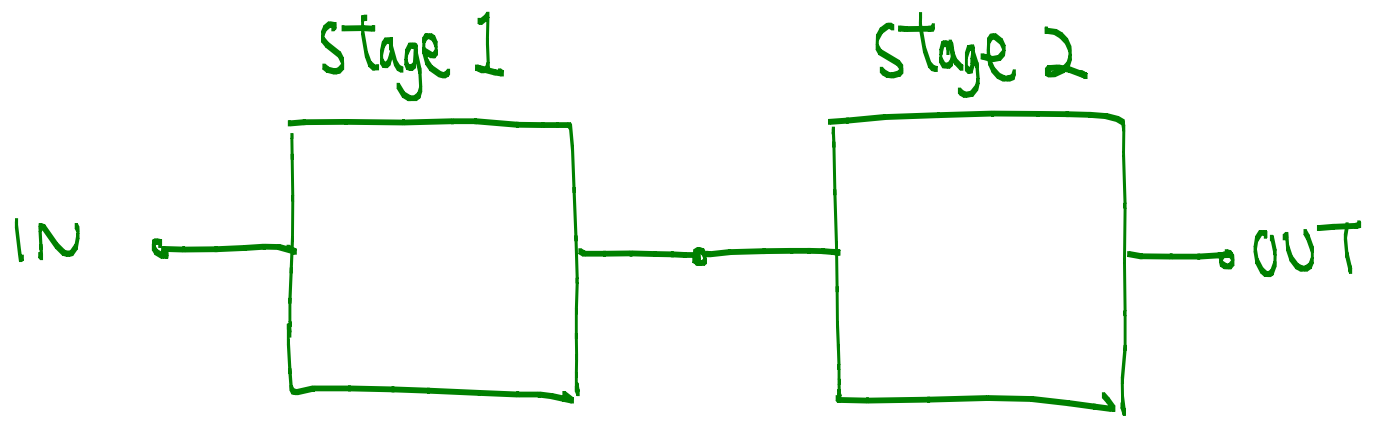- Fortunately, we can cascade two $n=2$ Sallen-Key filters



- This technique can be used for higher orders:

(Table 19-3 in textbook)

$n=2$

$n=4$

$n=6$

$n=8$

$n=10$




• Chebyshev Filter

→ Produce a steeper transition than Butterworth

BUT,

→ Same op amp circuit, but the filter parameters are slightly more complicated...

$|A|_{dB}$

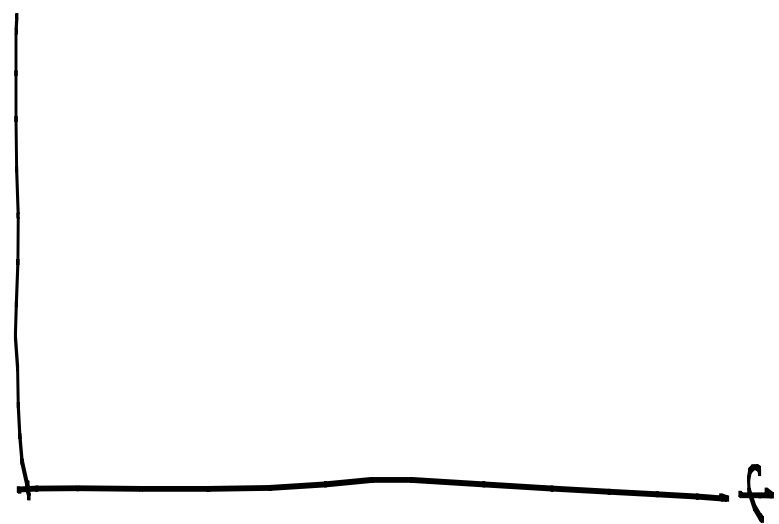

$$Q =$$

$$f_p =$$

$$f_c =$$

$$A_p :$$

Ex: $n=2$ Chebyshev

$$\rightarrow A_p = 0.69 \text{ dB}$$

$$Q = 0.9$$

$$f_c = 0.874 f_p$$