

# Lecture 16: Amplifier Stability

0. Review

1. Frequency Response

2. Feedback Stability

Textbook reading:

Ch 14.6 Bode plots

14.7 More Bode plots

• Exam #2 re-do due today

• HW7 due Thu (Nov 21)

(box outside my office)

• Lab 5 report due Nov 26 (Tue)  
(1 per team)

• Final Exam Nov 26 (Tue)


↳ Location TBD

(N100 not available)

↳ see course website for  
sample exam, solutions

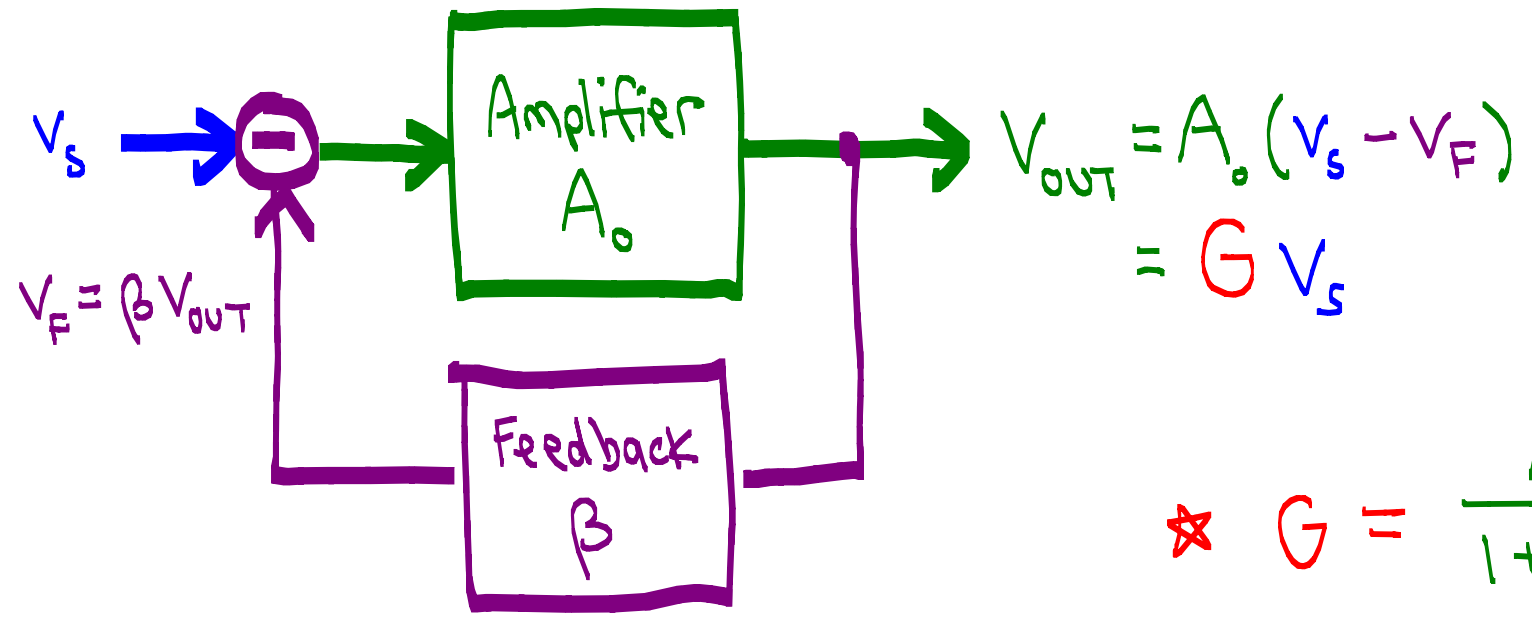0. Review

① Negative feedback for voltage amplifier




$$V_{OUT} = A_o (V_s - V_F)$$

$$= G V_s$$

$$\star G = \frac{A_o}{1 + A_o \beta}$$

② "Series-shunt" Feedback

Subtract voltage with series connection

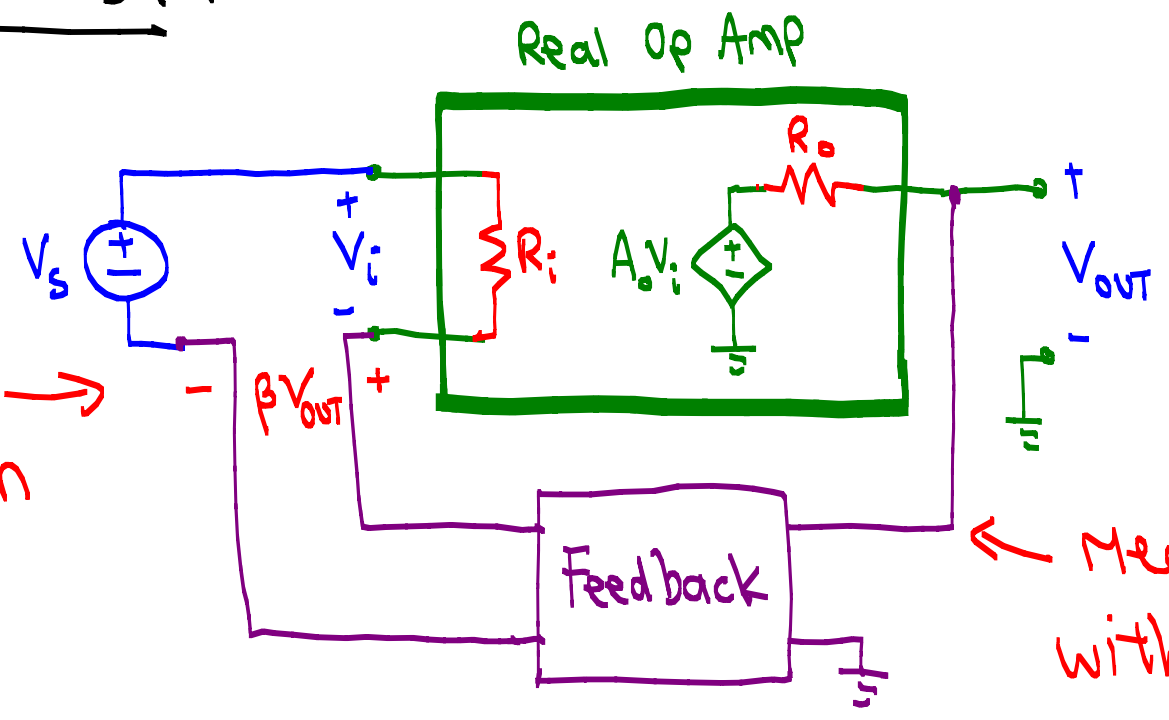


$$\star Z_{IN} = (1 + A_o \beta) R_i$$

$$\star Z_{OUT} = \frac{1}{(1 + A_o \beta)} R_o$$


Measure voltage with shunt connection
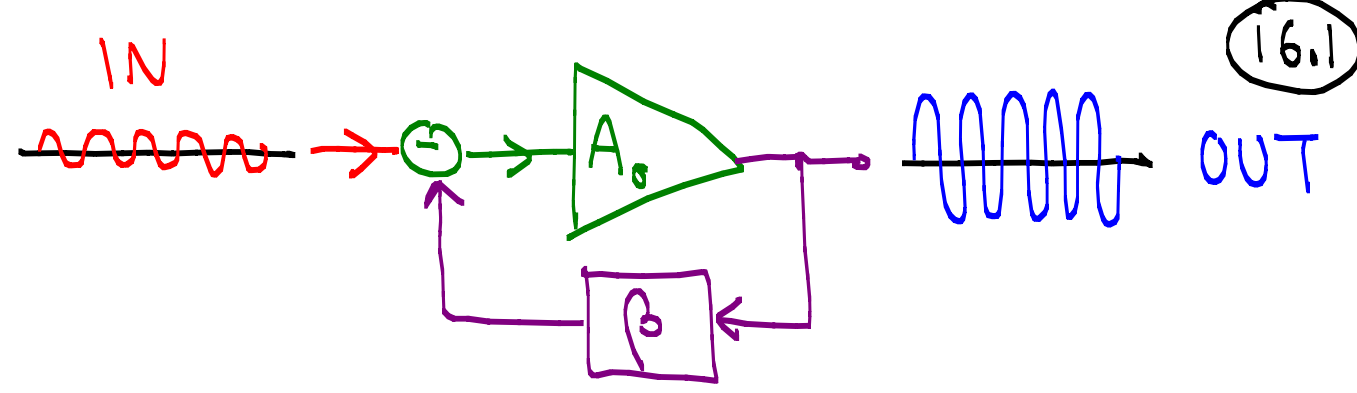
# 1. Frequency Response

- Negative feedback usually improves circuit properties
- HOWEVER, both  $A$  and  $\beta$  can depend on freq!



16.1

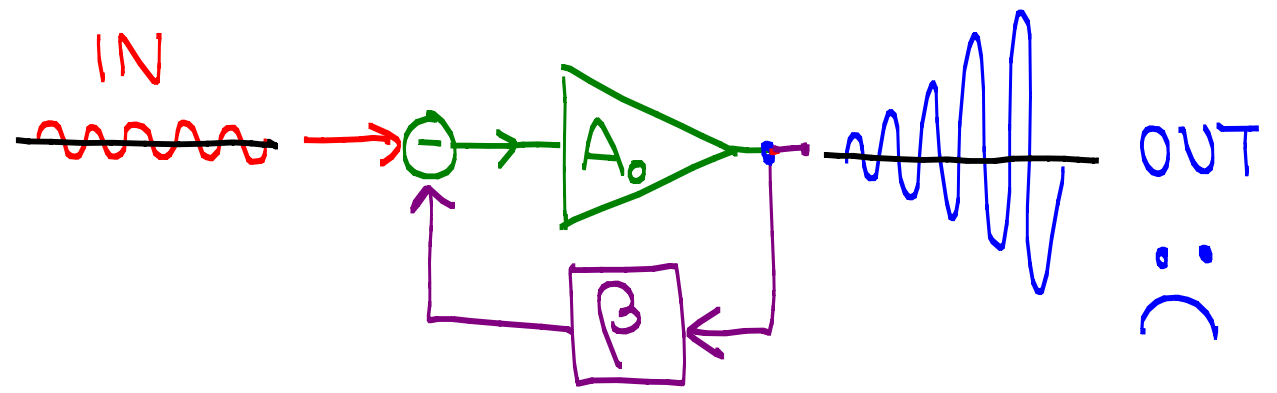

$$G(f) = \frac{A(f)}{1 + \boxed{A(f)\beta(f)}}$$

"Loop Gain"

Instability occurs if  $A\beta = -1$ !

① Magnitude:  $|A| = 1/\beta$

② Phase:  $\angle(A\beta) = -180^\circ$

$$\frac{A(f)}{1+(-1)} = \infty!$$

★ we must take a closer look at the frequency response of  $A$ !

BOTH conditions must be met!

# A. Dominant Pole

LF411

Open Loop Frequency Response


16.2

- For most op amps,  $A$  is really high (e.g.  $10^5$ ) only at very low freq!

- $A(f)$  typically resembles 1<sup>st</sup> order low-pass filter

$$A(f) = \frac{A_0}{1 + j f/f_p}$$

$A_0$  ← DC gain

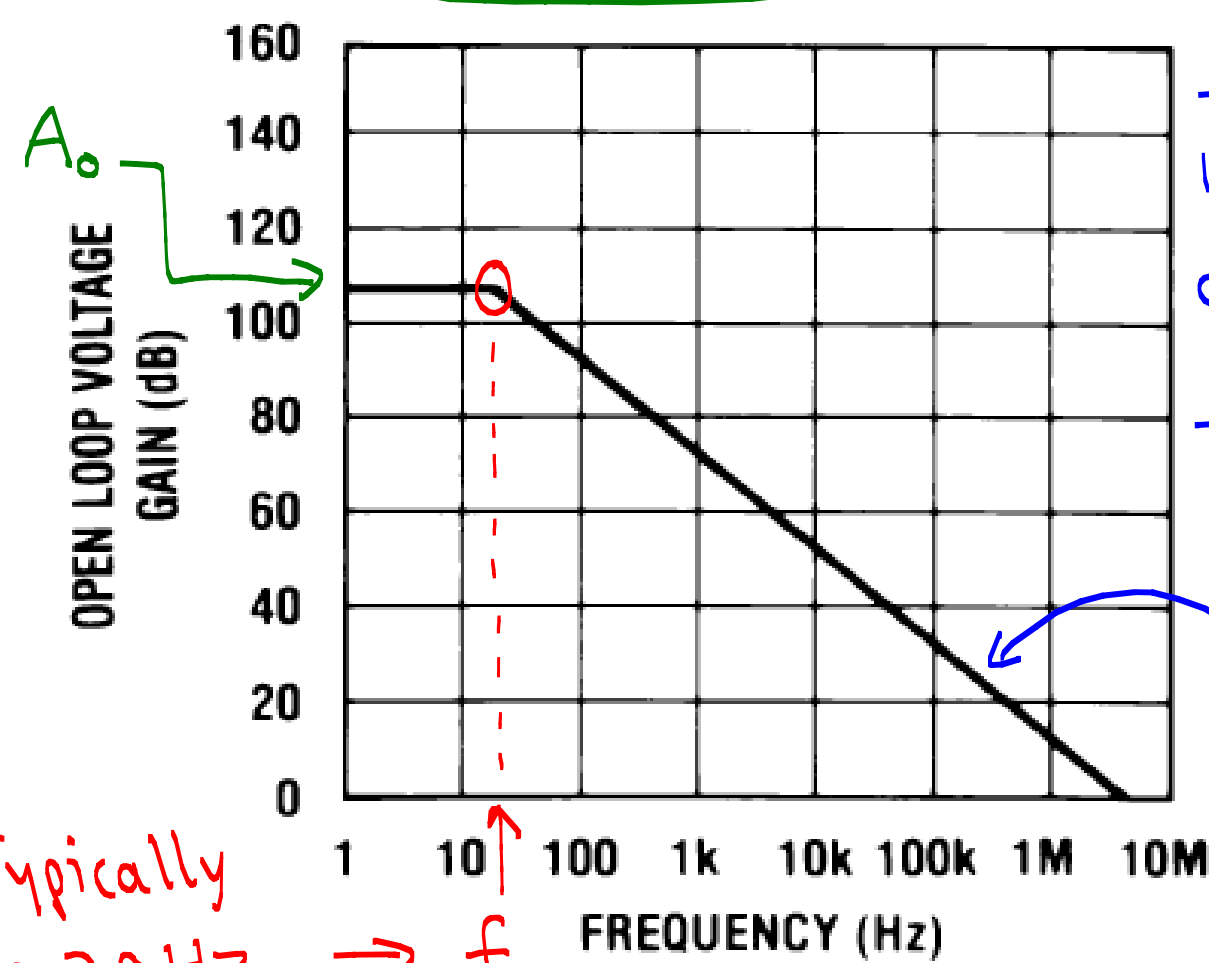

$ A $	$f$
110 dB	10 Hz
90 dB	$10^2$ Hz
70 dB	$10^3$ Hz

Typically  $\sim 20$  Hz  $\rightarrow f_p$

-20 dB per decade


$$|A(f)| = \frac{A_0}{\sqrt{1 + (f/f_p)^2}}$$

"Dominant" Pole

When  $|A(f)|$  is 3 dB lower than  $A_0$

# B. Bode plots ← Textbook Ch 14.6 is useful

- Linear scale is NOT very useful
  - Cannot show large freq range
  - cannot show both tiny and large |A|

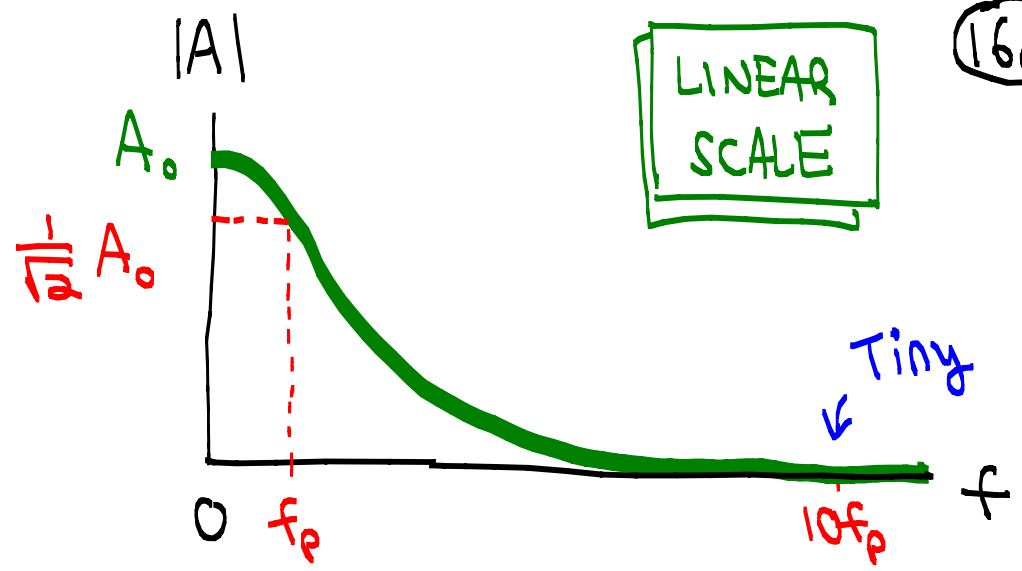

- Log-Log scale is most common.


Ex:  $|A(f)| = \frac{A_0}{\sqrt{1+(f/f_p)^2}}$

$\sim 1 \quad (f \ll f_p)$   
 $\sim f/f_p \quad (f \gg f_p)$

$20 \log_{10} |A| = 20 \log_{10} A_0 - 20 \log_{10} \sqrt{1+(f/f_p)^2}$

$f \ll f_p : 20 \log_{10} |A| \approx 20 \log_{10} A_0$

$f \gg f_p : 20 \log_{10} |A| \approx 20 \log_{10} A_0 - \boxed{20 \log_{10} (f/f_p)}$

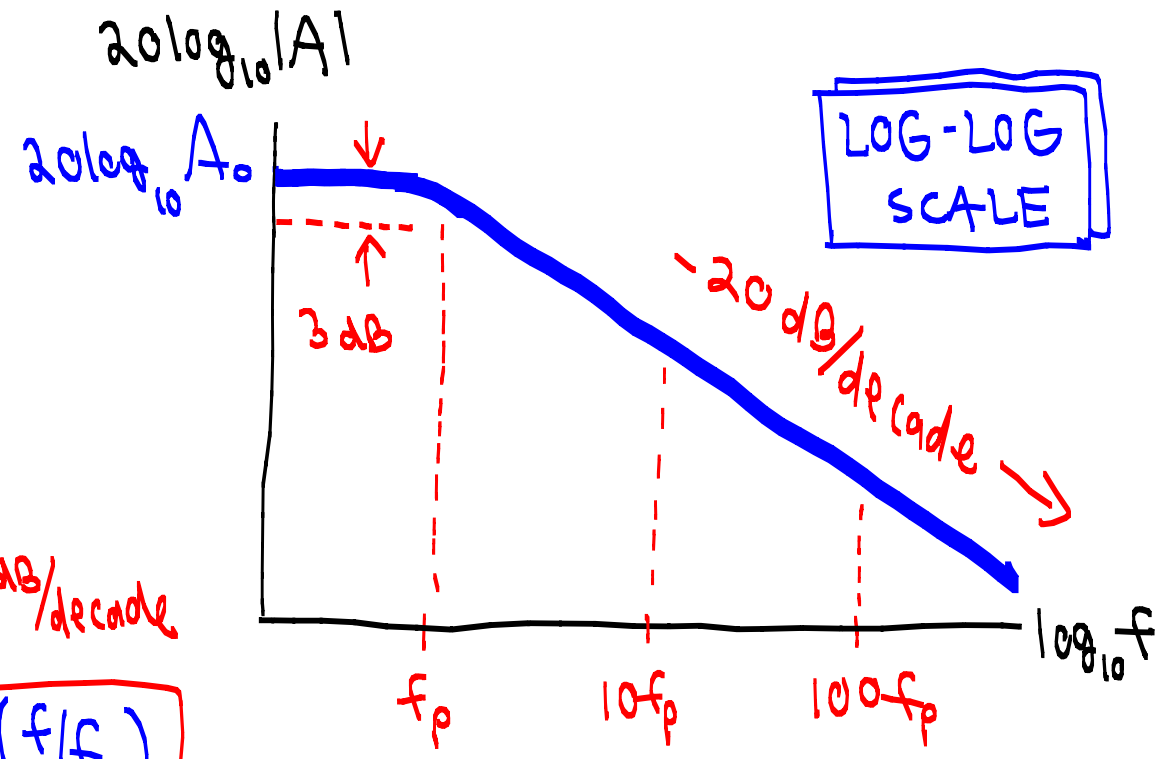

• what about phase?

★ Bode plot is an approximation using straight line segments 16.4



$$A = \frac{A_0}{1 + jf/f_p} = \frac{A_0}{\sqrt{1 + (f/f_p)^2}} e^{j \tan^{-1}(f/f_p)}$$

$$= \underbrace{\frac{A_0}{\sqrt{1 + (f/f_p)^2}}}_{\text{Magnitude}} e^{j \underbrace{[-\tan^{-1}(f/f_p)]}_{\phi < 0} \text{ Phase}}$$

$\phi \approx 0^\circ$ ,  $f \leq \frac{1}{10} f_p$

$\phi = -45^\circ$ ,  $f = f_p$

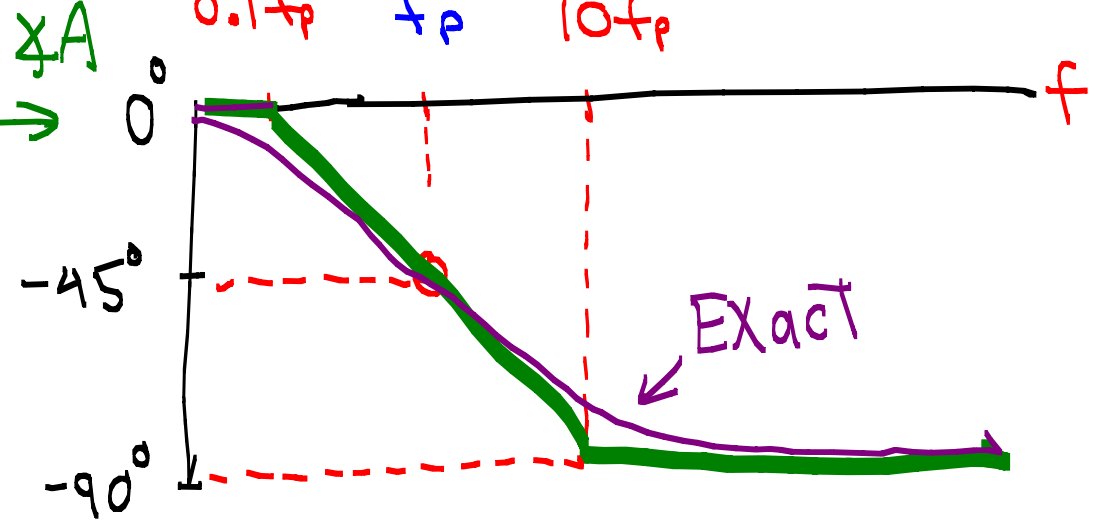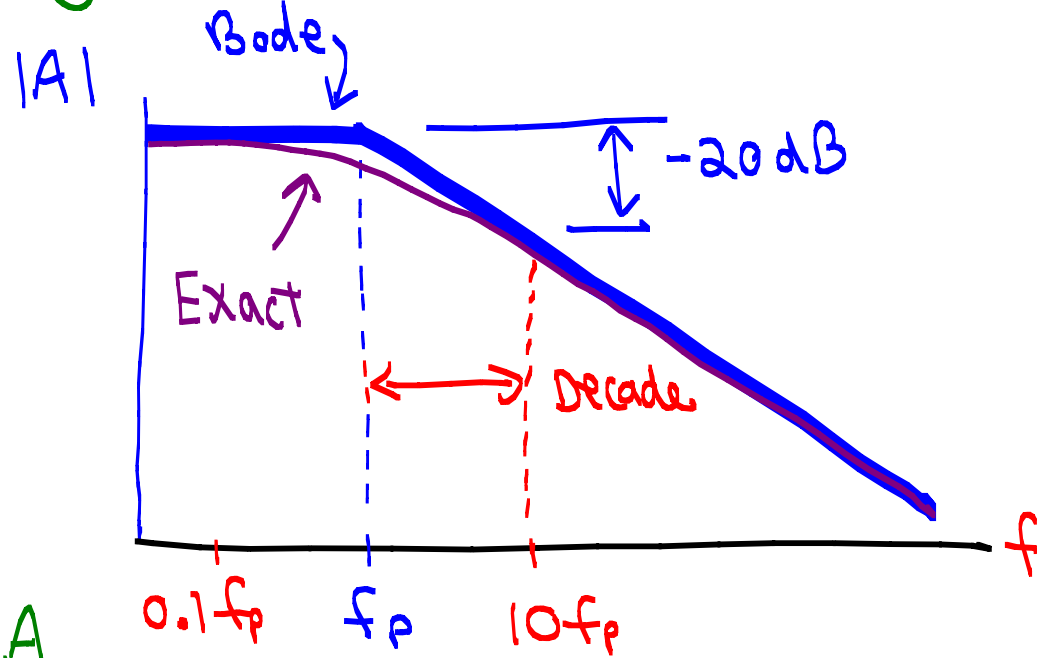$\phi \approx -90^\circ$ ,  $f \geq 10 f_p$



## 2. Amplifier Stability

**Example** 1-pole amplifier


Consider an amplifier with  $G = 100$

$$\text{and } A(f) = 10^6 \frac{1}{1 + j(f/100)}$$

Is the amplifier stable?

**STEP 1** Draw Bode plot for  $|A(f)|$

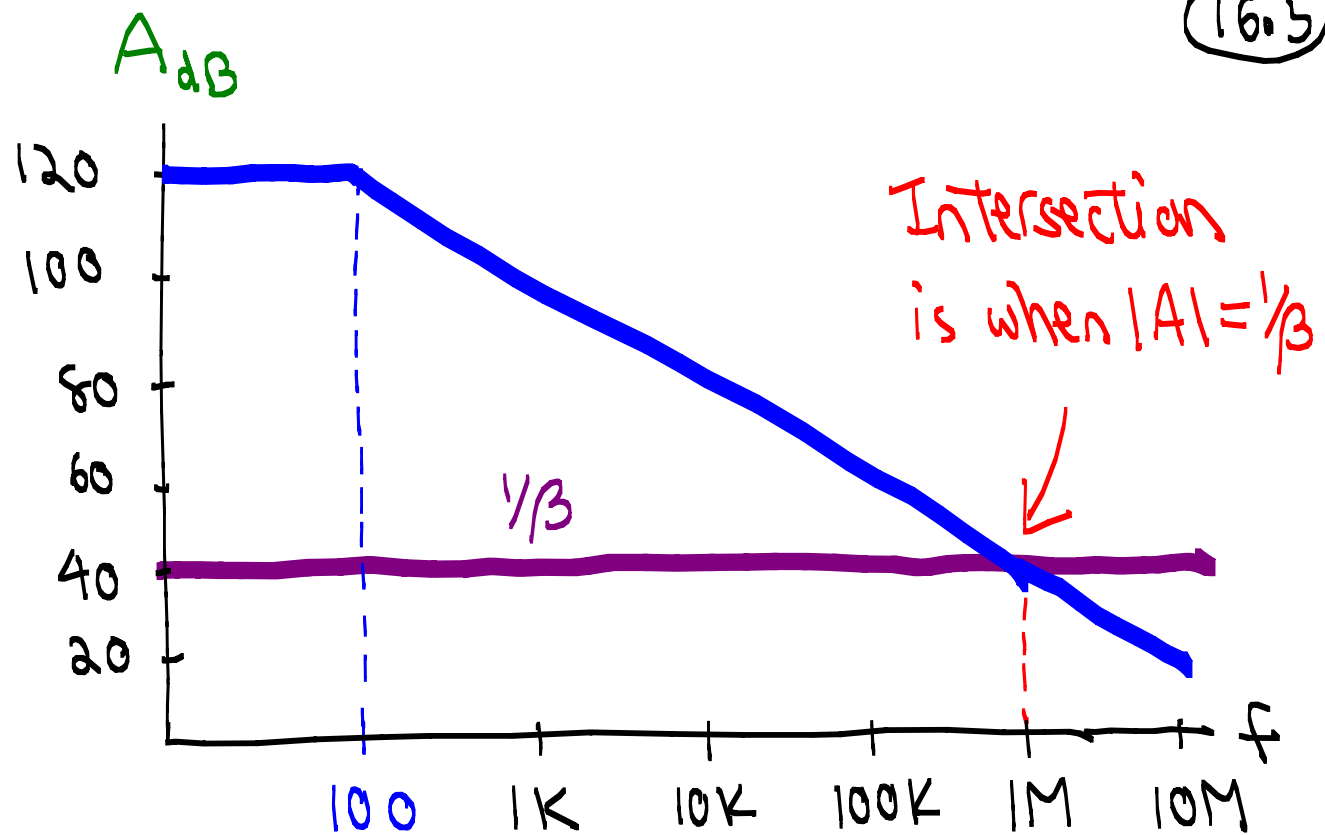- $20 \log_{10} A_0 = 120 \text{ dB}$   
 $\uparrow$   
 $f=0$
- One pole freq  $\rightarrow f_{p1} = 100 \text{ Hz}$
- $-20 \text{ dB/decade}$  after 1st pole




**STEP 2** Find  $\Omega \leftarrow$  when  $|A| = 1/\beta$

$$G = 100 = \frac{10^6}{1 + 10^6 \beta} \rightarrow \frac{1}{\beta} = 100.01$$

$$20 \log_{10}(1/\beta) = \underline{\underline{40 \text{ dB}}} \Rightarrow \boxed{\Omega = 1 \text{ MHz}}$$

**STEP 3** Draw Bode plot for  $\angle A$

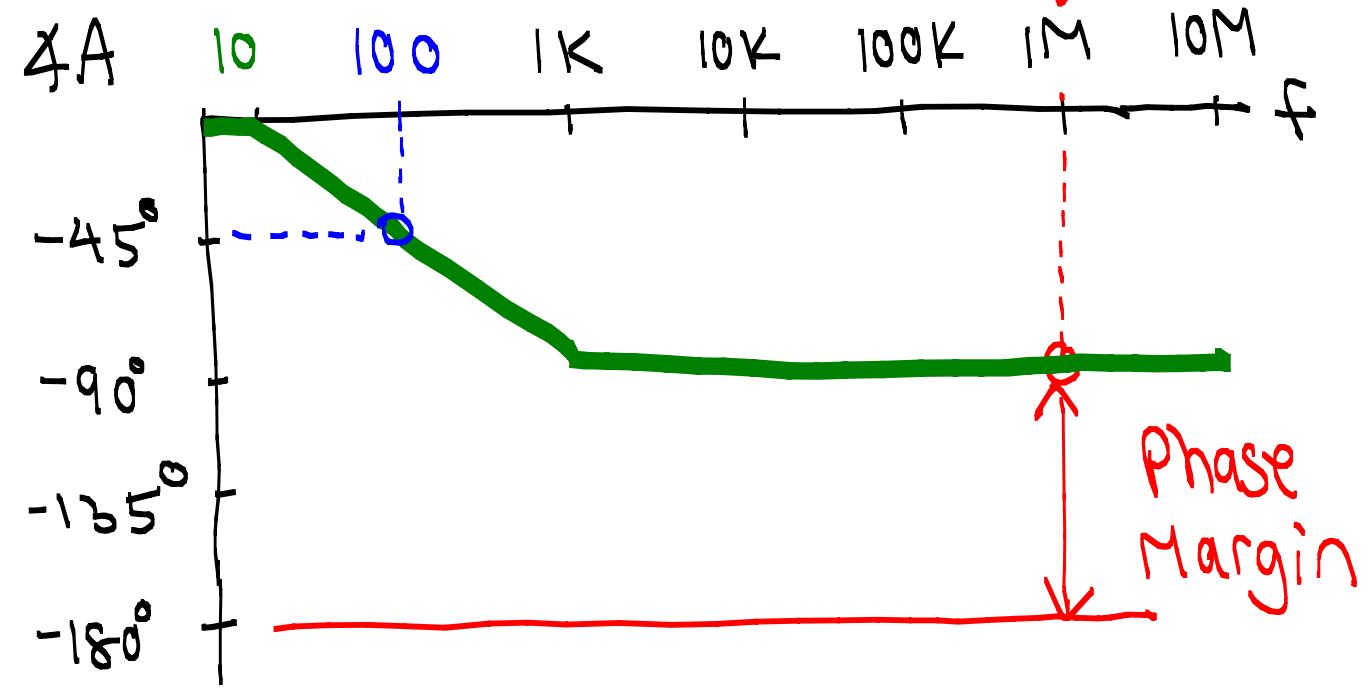$\angle A = -\tan^{-1}(f/100)$   
 $\rightarrow \angle A = 0^\circ @ f < \frac{1}{10} f_{p1}$   
 $\angle A = -45^\circ @ f_{p1}$   
 $\angle A = -90^\circ @ f \geq 10 f_{p1}$



**STEP 4** Phase Margin

- Bode plot shows quick estimate
- Compute exact phase margin: like "head room"

At  $f = \Omega$ :  $\angle A = -\tan^{-1}\left(\frac{10^6}{10^2}\right) = -89.99^\circ$   
 Phase margin =  $\angle A - (-180^\circ) = \underline{\underline{90.01^\circ}}$

★ Phase Margin  $\geq 45^\circ$  is stable

→ This amplifier is stable

★ Any single-pole amplifier is stable!




**Example** 2-pole amplifier  
with  $G = 100$

$$A = 10^6 \frac{1}{1+j(f/100)} \frac{1}{1+j(f/10K)}$$

**STEP 1** Draw Bode plot for  $|A|$

- $20 \log_{10} |A_0| = 120 \text{ dB}$   
     $\uparrow$   
     $f=0$
- Two pole freq:  $f_{p1} = 100 \text{ Hz}$   
     $f_{p2} = 10 \text{ KHz}$

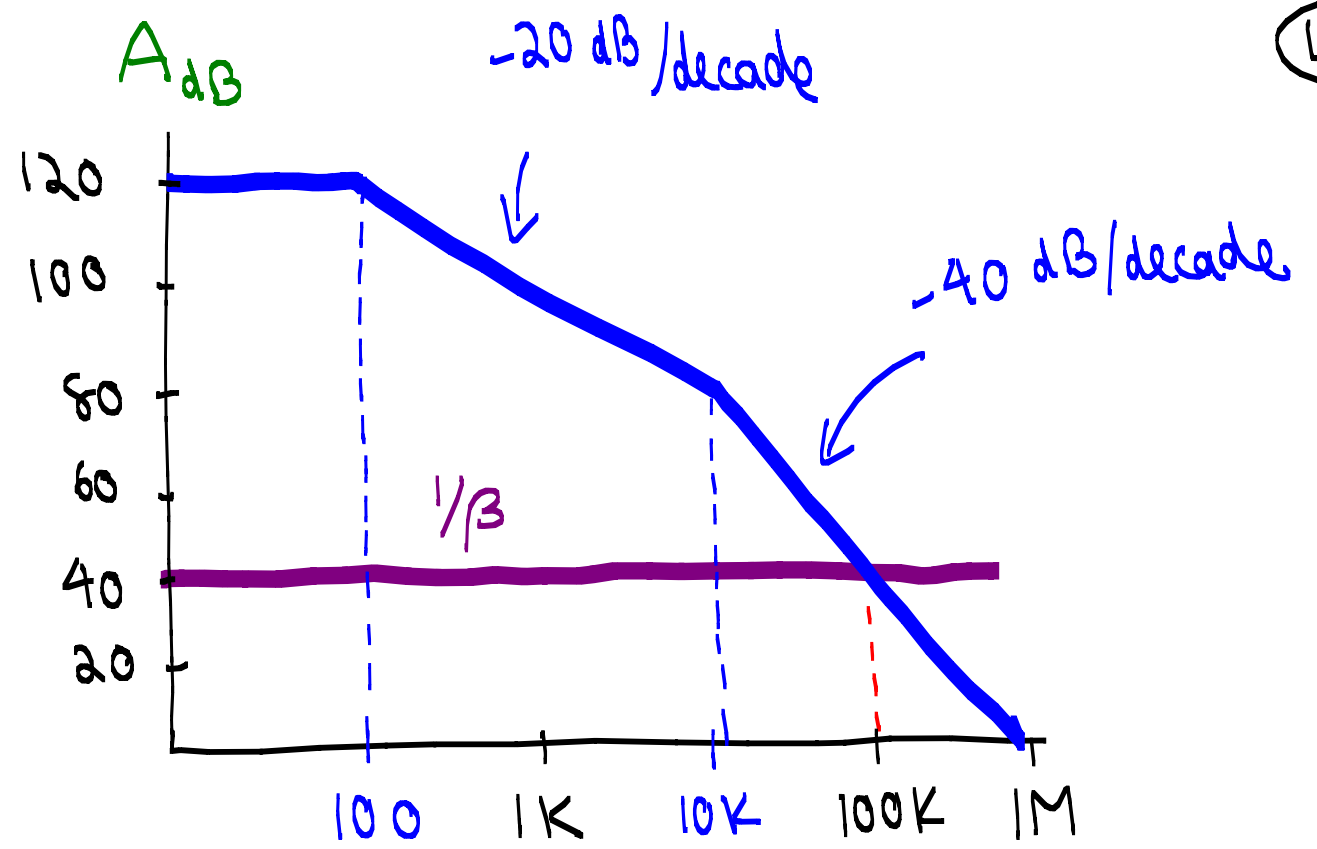
\* Extra  $-20 \text{ dB/decade}$  after each pole!




**STEP 2** Find  $\Omega$

$$G = 100 = \frac{A_0}{1 + A_0 \beta} \rightarrow \frac{1}{\beta} = 100.01 = 40 \text{ dB}$$

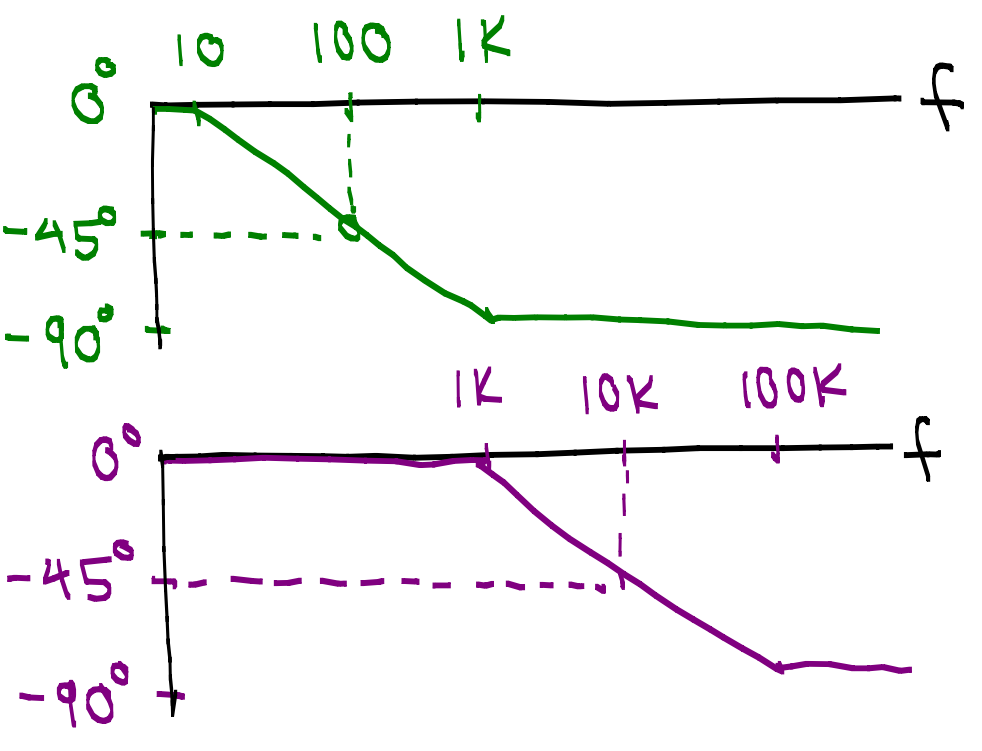**STEP 3** Draw Bode plot for  $\angle A = \underbrace{-\tan^{-1}(f/100)}_{\text{green}} - \underbrace{\tan^{-1}(f/10K)}_{\text{purple}}$



Add plots together →

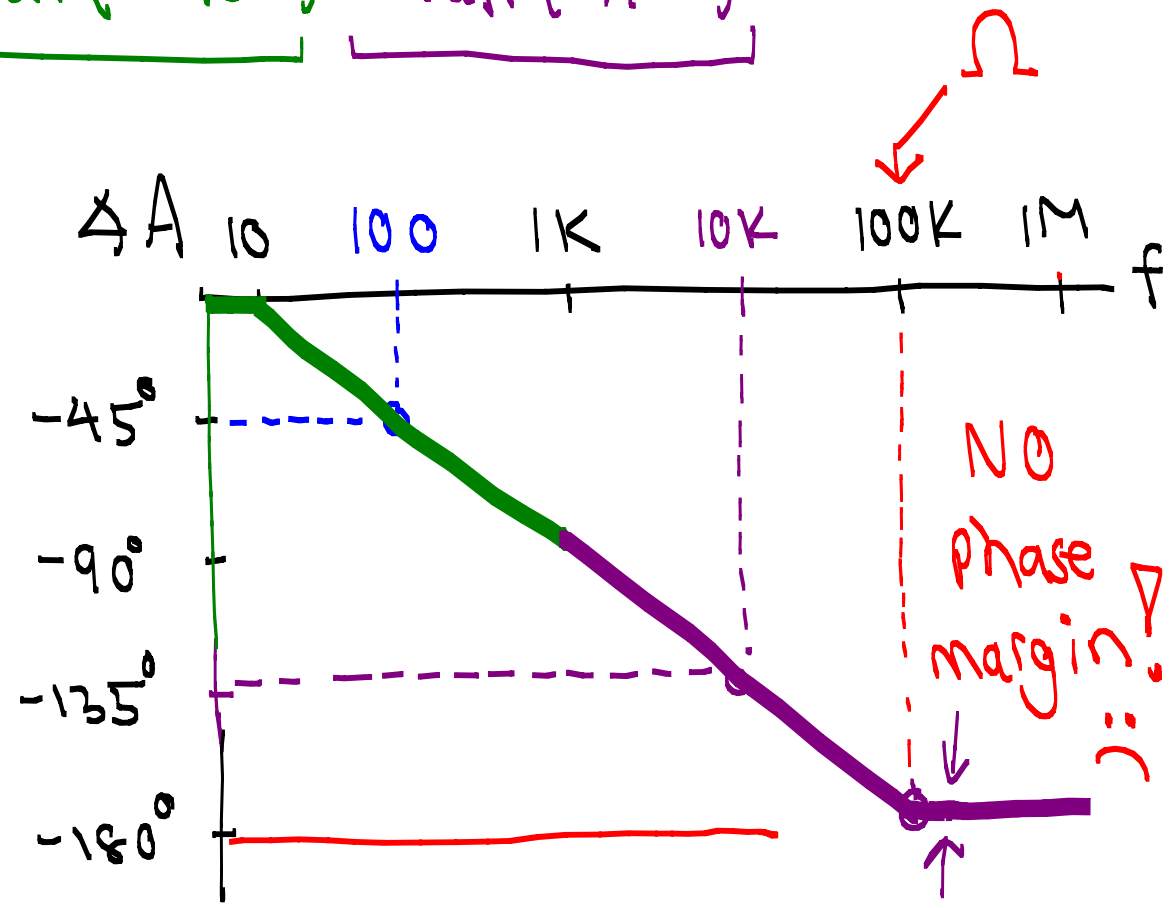

**STEP 4** Exact phase margin

At  $f = \Omega$ :  $\angle A = -\tan^{-1}\left(\frac{10^4}{10^2}\right) - \tan^{-1}\left(\frac{10^4}{10^3}\right) = -89.4^\circ - 84.3^\circ = -173.7^\circ$



Phase margin =  $\angle A - (-180^\circ) = \boxed{6.3^\circ} < 45^\circ$  **NOT STABLE!**

• 2-pole amplifier may or may not be stable!

$$A(f) = A_0 \frac{1}{1 + j f/f_{p1}} \frac{1}{1 + j f/f_{p2}}$$



Depends on  $\Omega$  vs.  $f_{p2}$

$\Omega < f_{p2}$

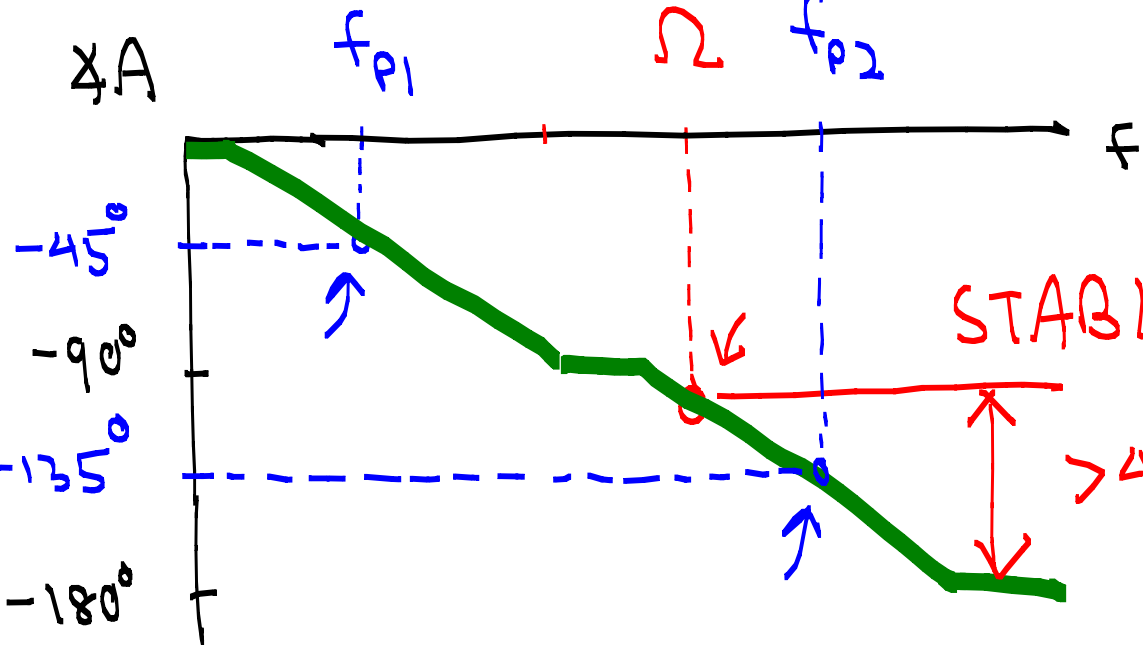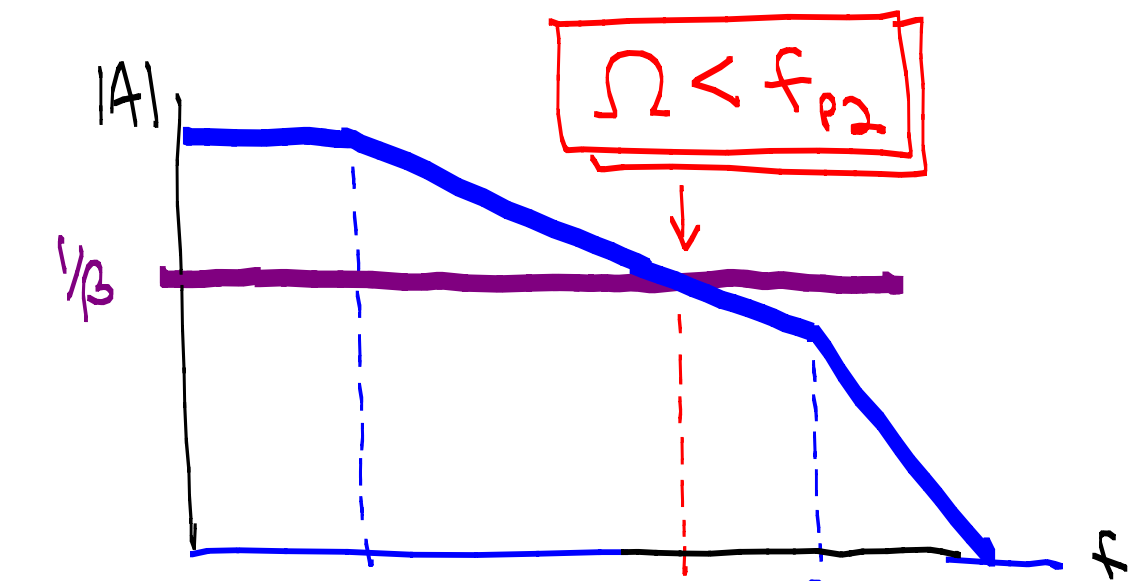

STABLE ✓  
> 45° ☺

$\Omega > f_{p2}$

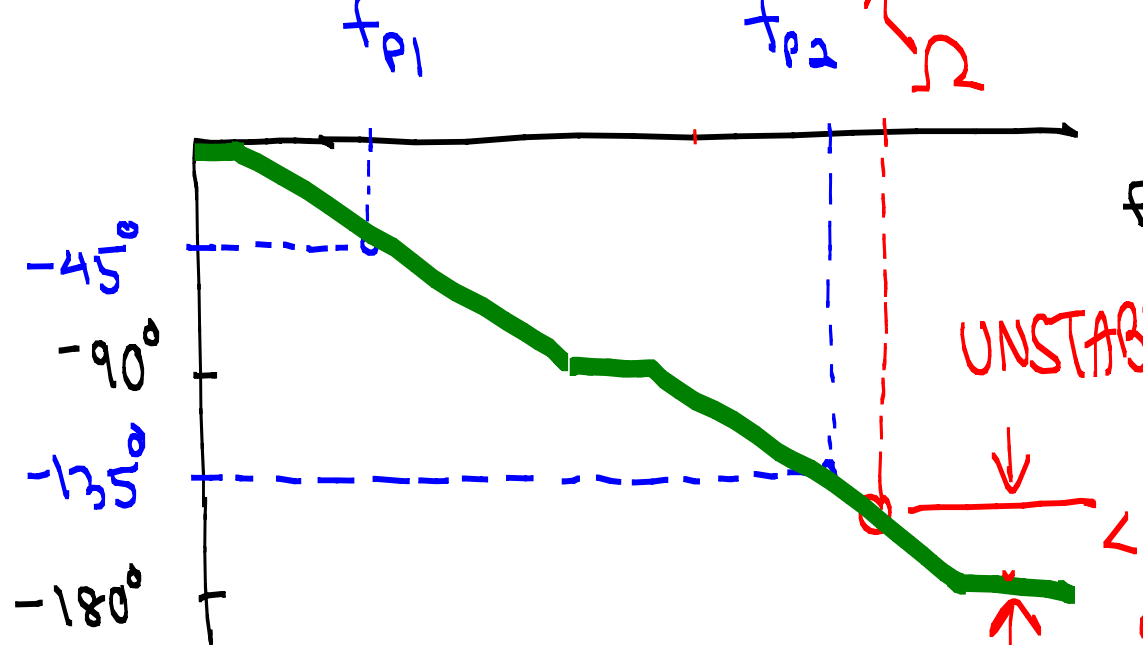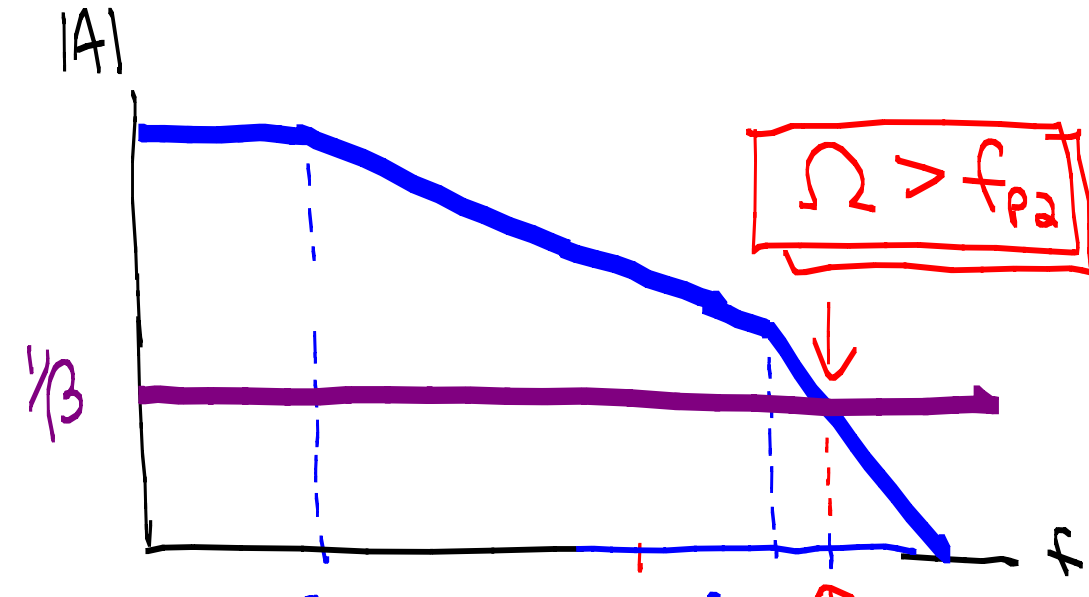

UNSTABLE! ☹  
< 45° ☹

• Same with 3-pole amplifier

$$A_o(f) = A_o \frac{1}{1 + j f/f_{p1}} \frac{1}{1 + j f/f_{p2}} \frac{1}{1 + j f/f_{p3}}$$

$\angle A$	$f$
$-45^\circ$	$f_{p1}$
$-135^\circ$	$f_{p2}$
$-225^\circ$	$f_{p3}$

$45^\circ$  Phase margin

★ Amplifier is unstable if  $\Omega > f_{p2}$ !

