

Lecture 16: Amplifier Stability

0. Review

1. Frequency Response

2. Feedback Stability

Textbook reading:


Ch 14.6 Bode plots

14.7 More Bode plots

- Exam #2 re-do due today
- HW7 due Thu (Nov 21)
(box outside my office)
- Lab 5 report due Nov 26 (Tue)
(1 per team)
- Final Exam Nov 26 (Tue)
 - ↳ Location TBD
(N100 not available)
 - ↳ see course website for sample exam, solutions

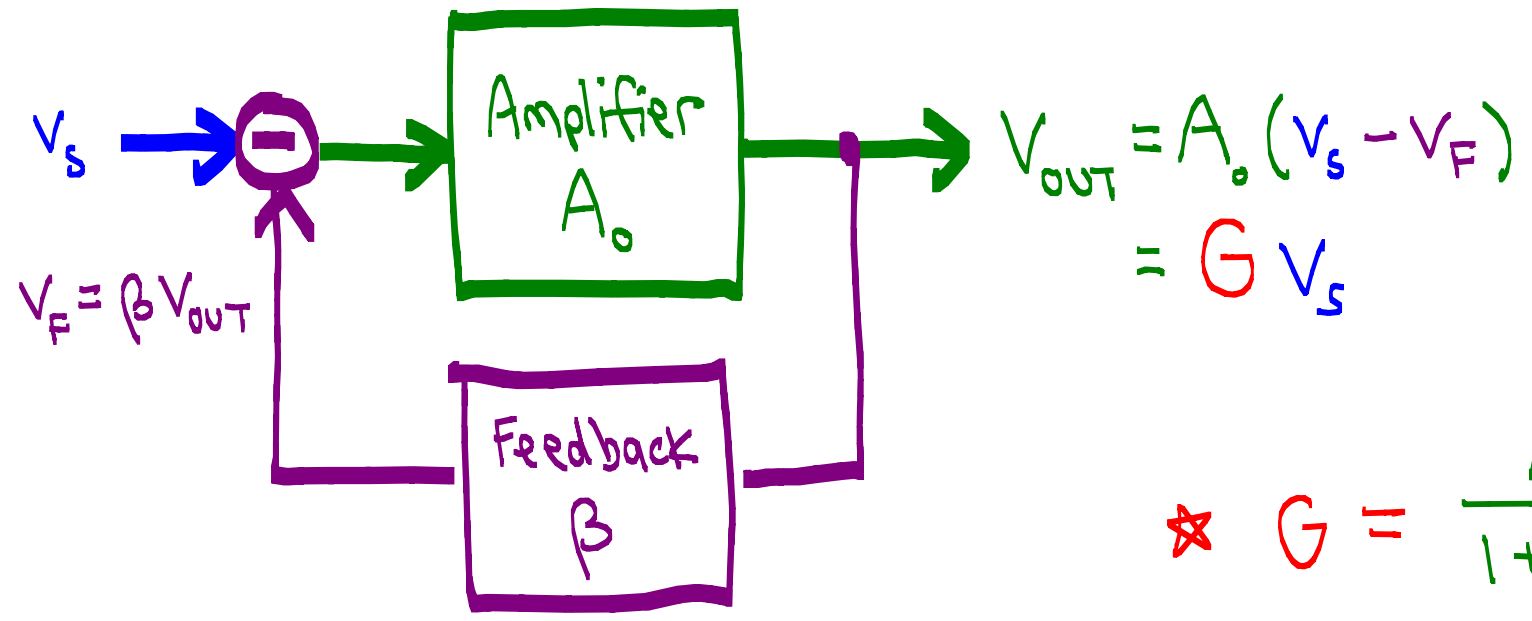0. Review

① Negative feedback for voltage amplifier




$$V_{OUT} = A_o (V_s - V_F)$$

$$= G V_s$$

② "Series-shunt" Feedback

Subtract voltage with series connection

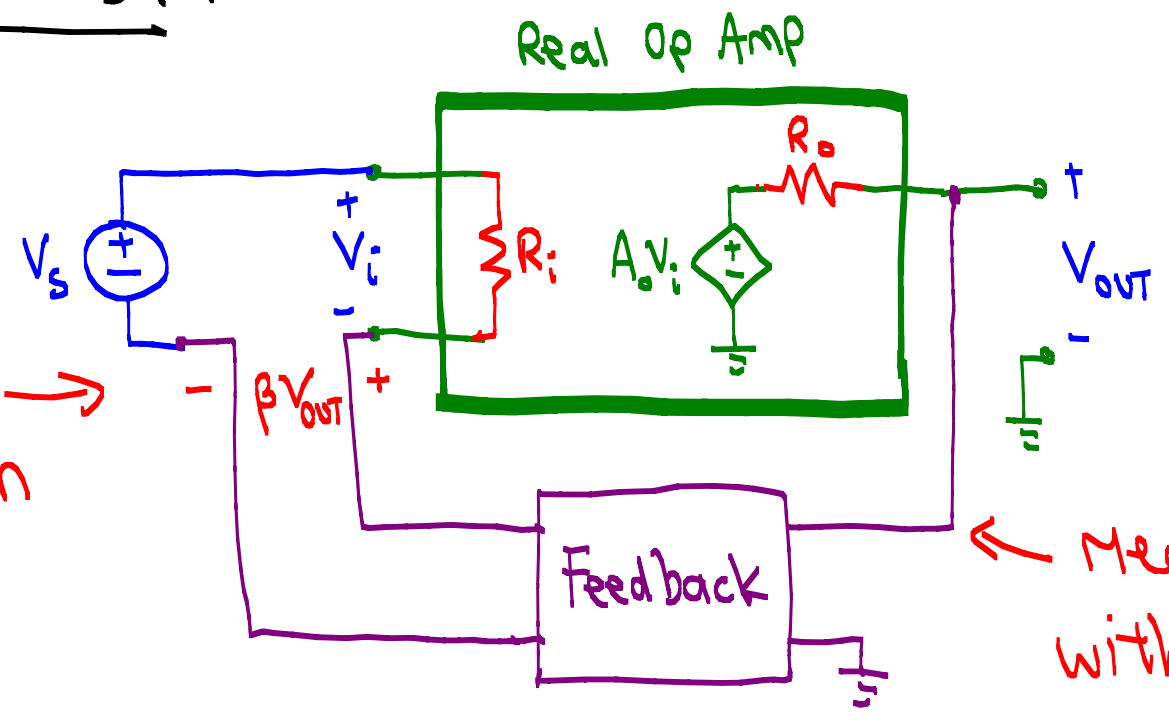



$$* Z_{IN} = (1 + A_o \beta) R_i$$

$$* Z_{OUT} = \frac{1}{(1 + A_o \beta)} R_o$$

Measure voltage with shunt connection

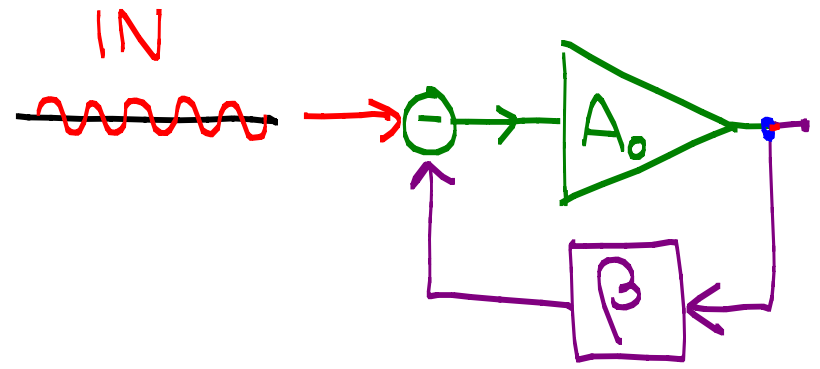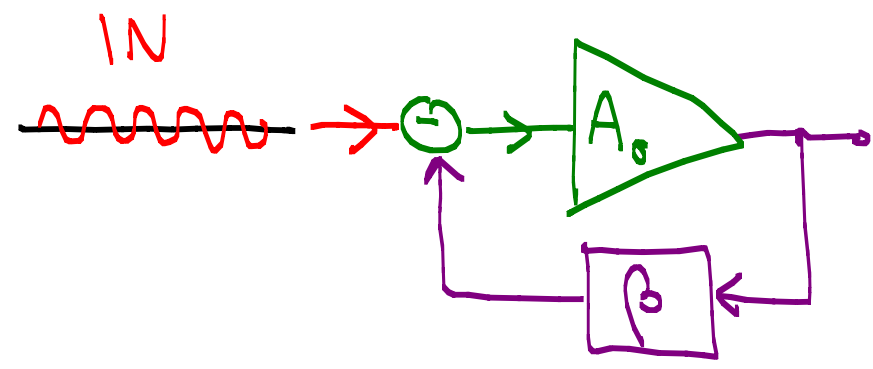1. Frequency Response

- Negative feedback usually improves circuit properties
- HOWEVER, both A and β can depend on freq!




A. Dominant Pole

LF411

- For most op amps, A is really high (e.g. 10^5) only at very low freq!
- $A(f)$ typically resembles 1st order low-pass filter

Open Loop Frequency Response


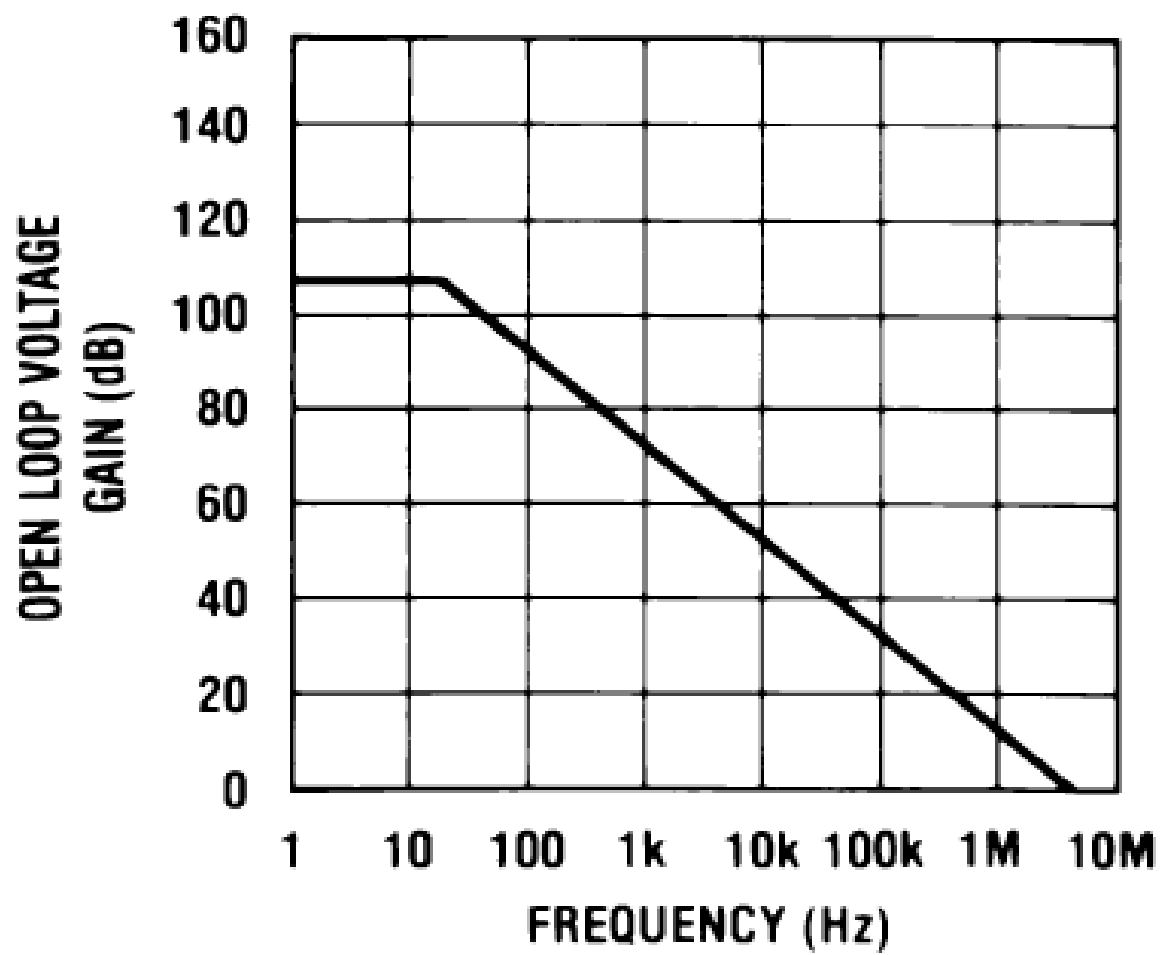


B. Bode plots ← Textbook Ch 14.6 is useful

- Linear scale is NOT very useful

- Log-Log scale is most common.


$$\text{Ex: } |A(f)| = \frac{A_0}{\sqrt{1 + (f/f_p)^2}}$$

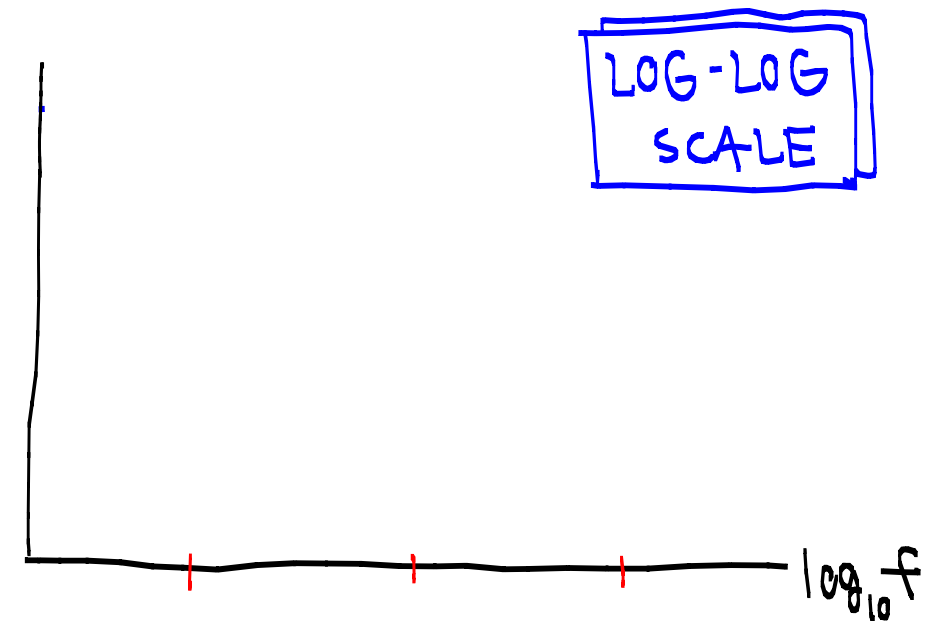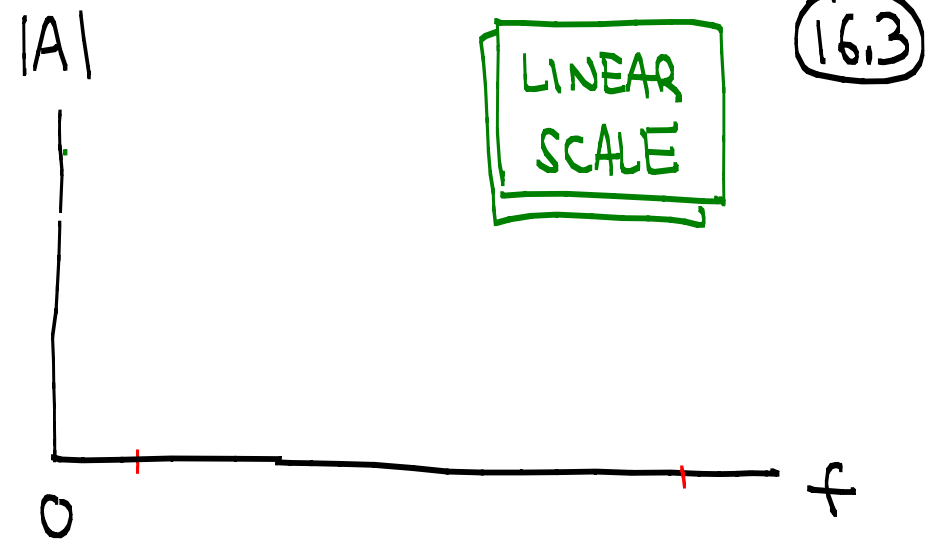

• what about phase?

$$A = \frac{A_0}{1 + jf/f_p}$$

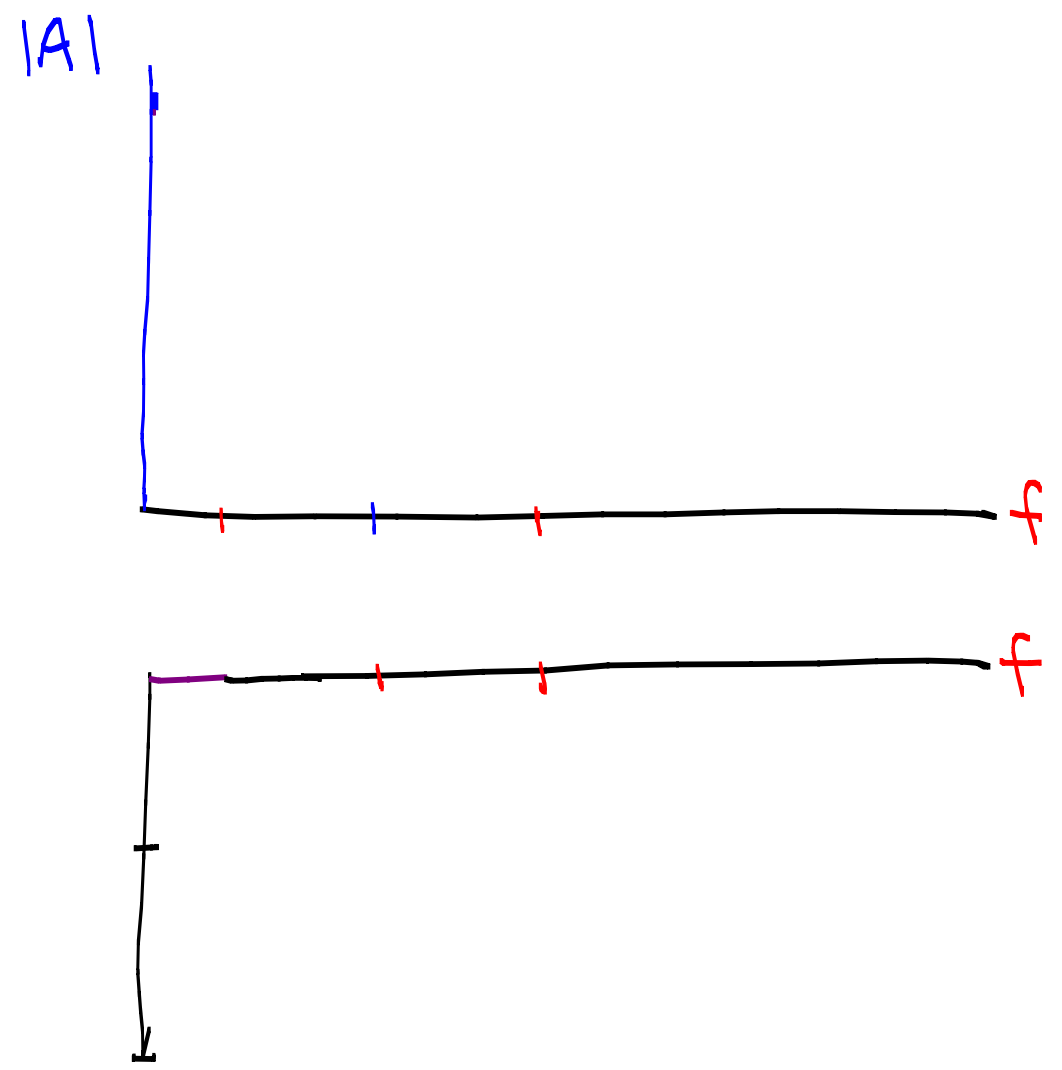★ Bode plot is an approximation using straight line segments 16.4



2. Amplifier Stability


Example 1-pole amplifier

Consider an amplifier with $G = 100$

$$\text{and } A(f) = 10^6 \frac{1}{1 + j(f/100)}$$


Is the amplifier stable?

STEP 1 Draw

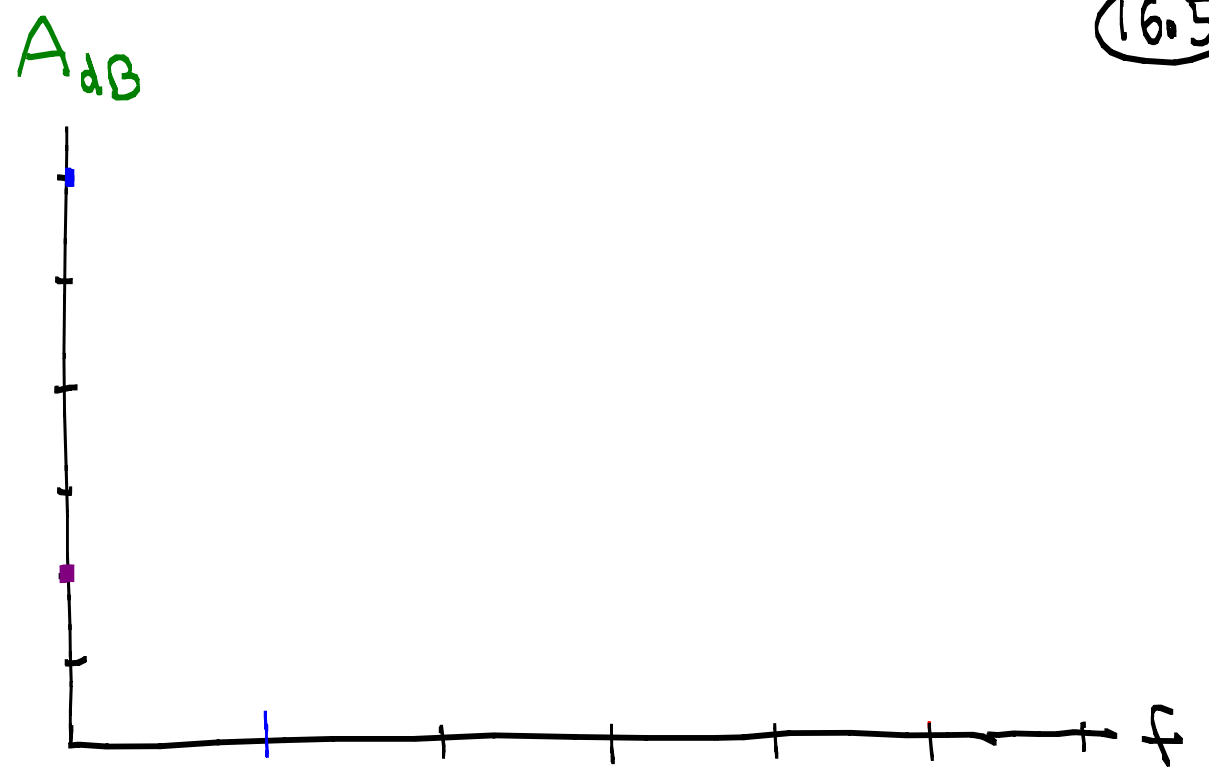

STEP 2 Find

STEP 3 Draw

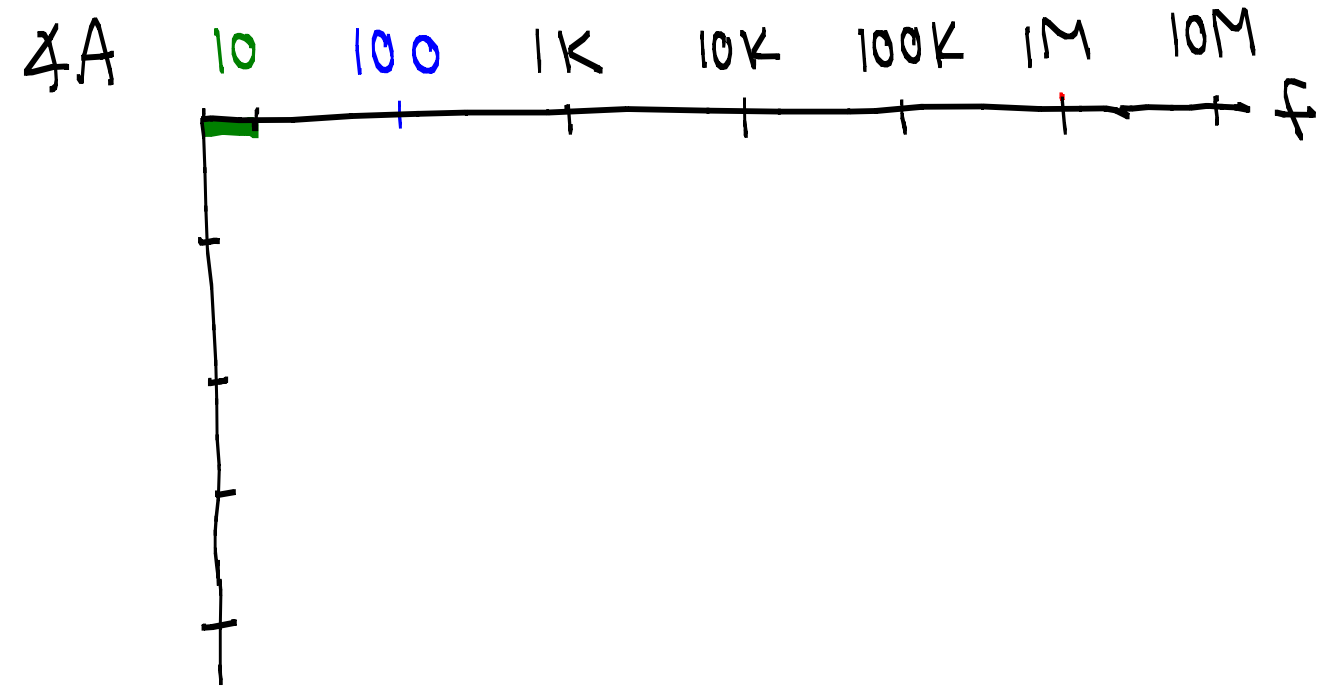


STEP 4 Phase Margin

Example 2-pole amplifier
with $G = 100$



$$A = 10^6 \frac{1}{1+j(f/100)} \frac{1}{1+j(f/10k)}$$

STEP 1 Draw Bode plot for $|A|$

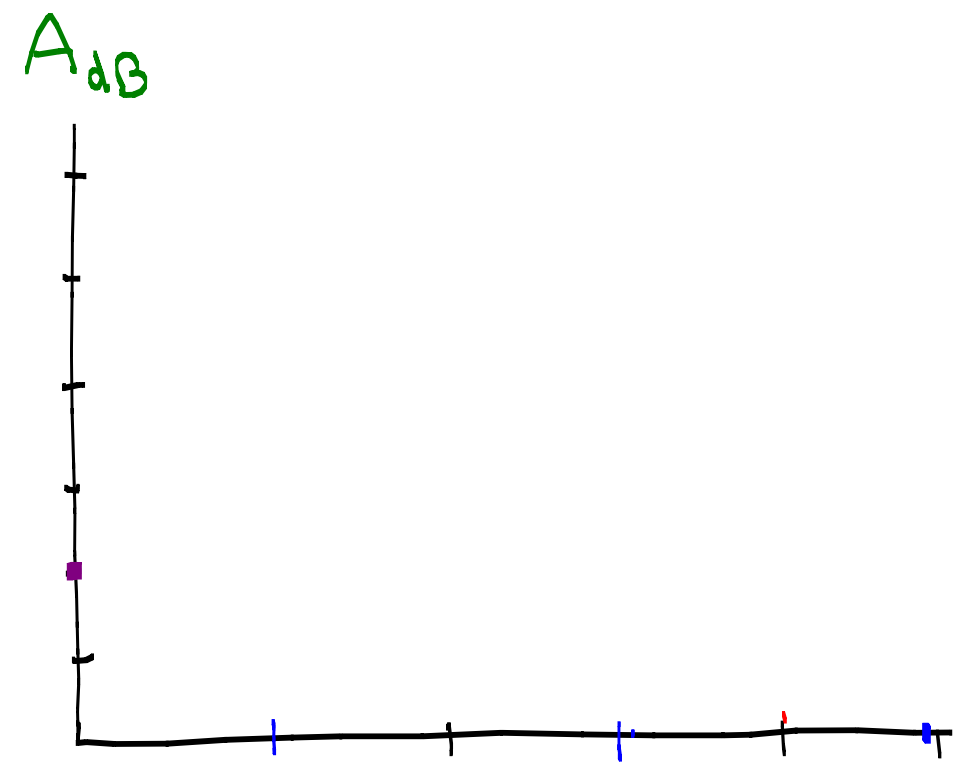

STEP 2 Find Ω

STEP 3 Draw Bode plot for $\Delta A =$

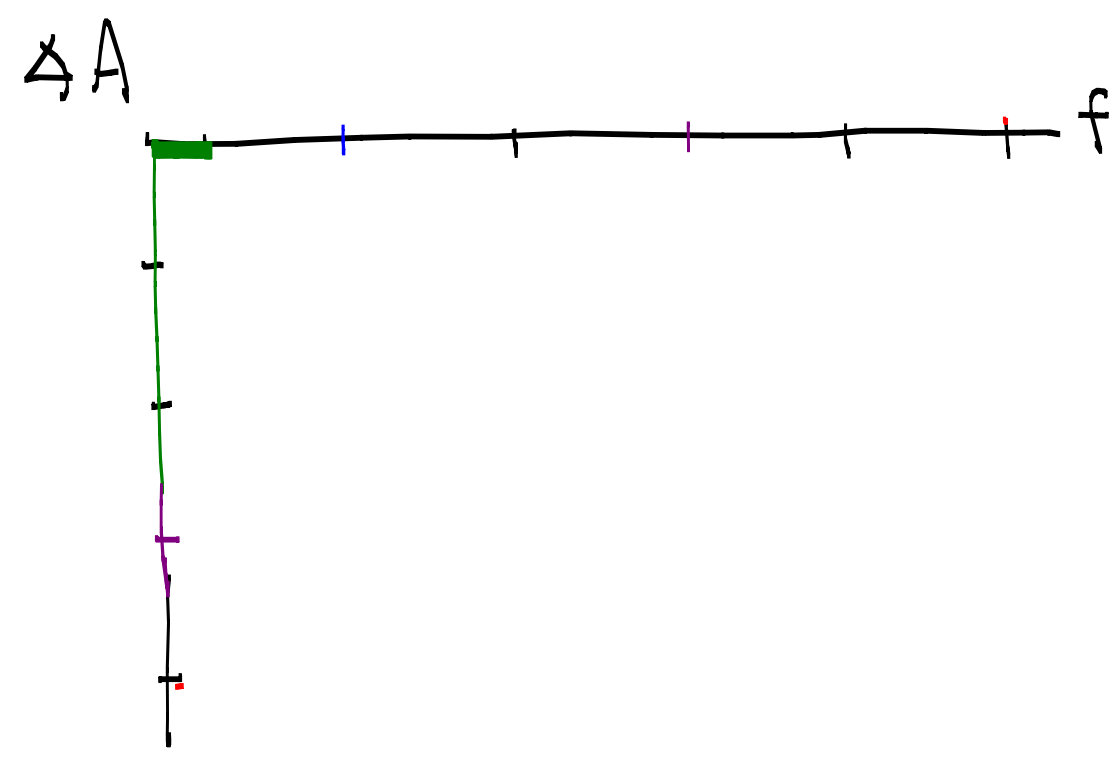
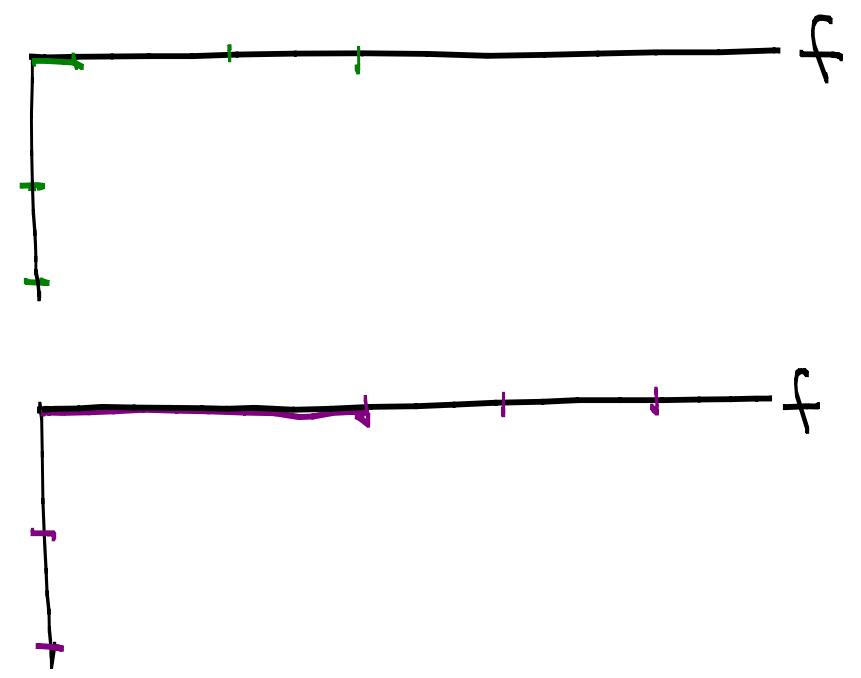


STEP 4 Exact phase margin

- 2-pole amplifier may or may not be stable!

$$A(f) = A_0 \frac{1}{1 + j f/f_{p1}} \frac{1}{1 + j f/f_{p2}}$$

16.9

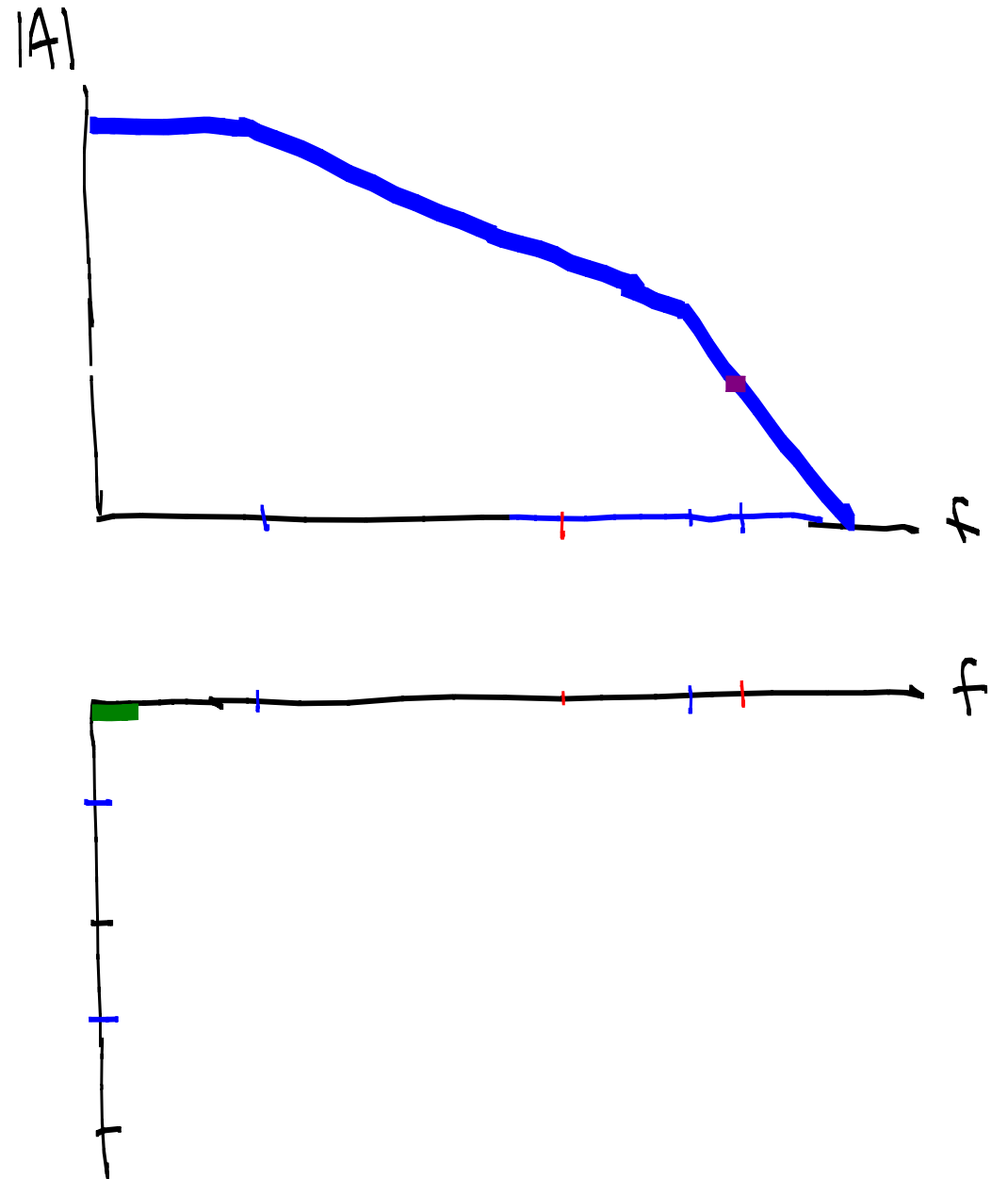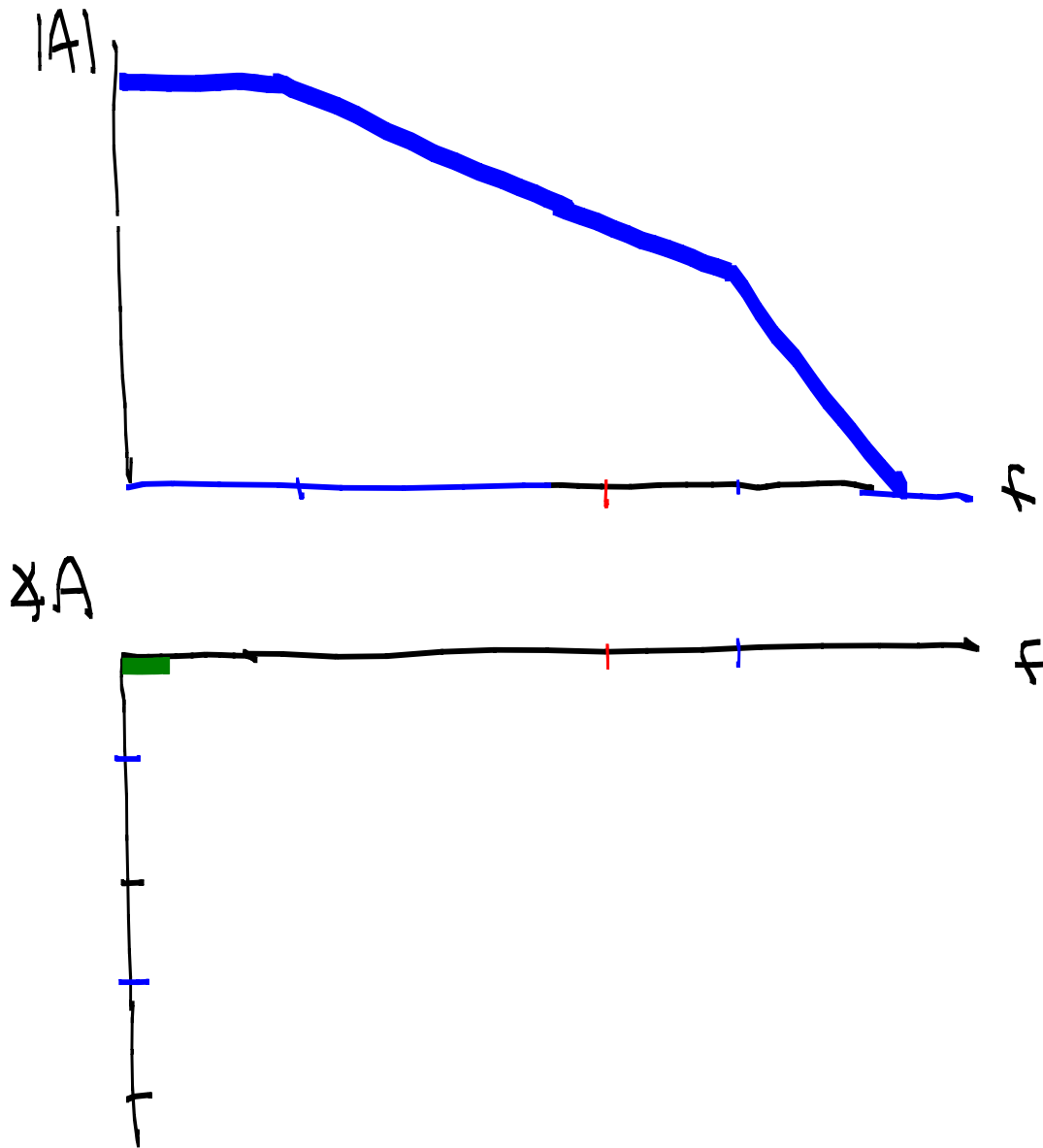

- Same with 3-pole amplifier

$$A_o(f) = A_o \frac{1}{1 + j f/f_{p1}} \frac{1}{1 + j f/f_{p2}} \frac{1}{1 + j f/f_{p3}}$$

↑
↑
↑

