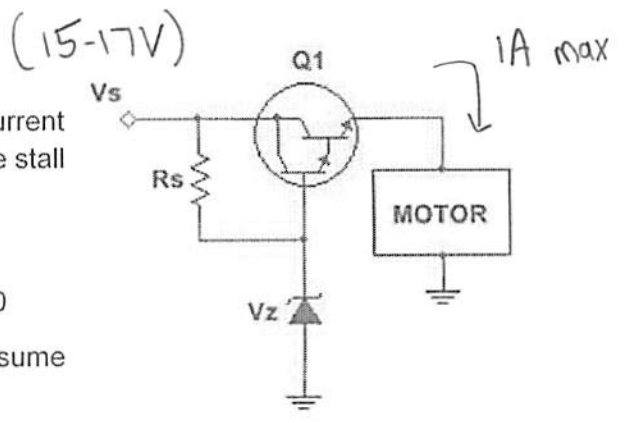


1 problem for 20 pts

Emitter Follower Design

1) You are asked to design a power supply for a 12V DC motor. The input voltage V_s comes from a supply that can vary from ~~10~~¹⁵ V to 17V. Here are the design constraints:

- Output voltage: must be within +/- 5% of 12V.
- The motor has a "no-load" current of 100 mA and a "stall" current of 2A. Design the power supply to provide up to 50% of the stall current.
- The zener must either be 11, 13, or 15V
- The Darlington transistor can either be a KSP13 or TIP120
- Available heat sinks are $\theta_{SA} = 6, 12, 18, \text{ and } 24 \text{ } ^\circ\text{C/W}$ (assume $T_A = 25 \text{ } ^\circ\text{C}$ and $\theta_{CS} = 0.5 \text{ } ^\circ\text{C/W}$).
- Use standard 5% resistor values.



- (a) Using "quick" analysis assumptions, determine the appropriate zener diode voltage. Show all work!
- (b) Perform a "quick" analysis to determine the appropriate transistor. If you need a heat sink, you must choose one of the available θ_{SA} . You MUST explain why you chose one transistor and not the other one.
- (c) Using "typical" parameters for your choice of transistor from part (b), determine the appropriate resistor R_s (choose standard 5% value).
- (d) Determine the proper power ratings for the zener and resistor. Choose from 1/4, 1/2, 1, or 2 W rating.

(a) $V_{LOAD} = V_z - 1.4 \rightarrow V_z = 12 + 1.4 = 13.4V \rightarrow$ choose 13V zener

+3

check: $V_{Load} = 11.6V$ (-3.33% error) ✓

	Max I_c	P_{rating} (no HS)	P_{rating} (with HS)	
KSP13	0.5A X	0.625W		* KSP13 cannot handle current.
TIP120	5A ✓	2W X	65W ✓	

Power dissipation?
 $Max P = \frac{1A}{2501} (1.4V) + \frac{2500}{2501} (1A)(17-11.6)$

+7

$= 0.0056 + 5.39784$
 $\approx 5.4W$

Need heat sink!

(extra sheet for work)

$$1.92 \text{ } ^\circ\text{C/W} \quad .5 \text{ } ^\circ\text{C/W}$$


$$\text{Want } T_J = T_A + P(\theta_{JC} + \theta_{CS} + \theta_{SA}) < 85^\circ\text{C}$$

$$\theta_{SA} < \frac{85^\circ\text{C} - 25^\circ\text{C}}{5.4\text{W}} - 1.92 \text{ } ^\circ\text{C/W} - .5 \text{ } ^\circ\text{C/W}$$

$$< \underline{\underline{8.69 \text{ } ^\circ\text{C/W}}} \quad \text{Choose } \boxed{\theta_{SA} = 6 \text{ } ^\circ\text{C/W}}$$

c
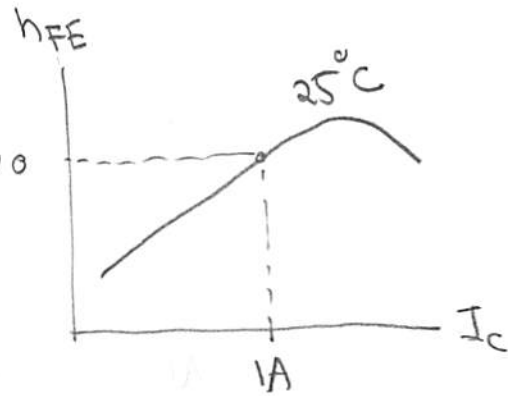
$$\text{Min } I_2 = \frac{15-13}{R_s} - \frac{1\text{A}}{3501} > .01\text{A} \quad \sim 3500$$



$$R_s < 194\Omega \leftarrow \text{Not critical to multiply by } 0.95 \text{ for } 5\% \text{ resistor tolerance.}$$

$$\text{Choose } \boxed{R_s = 180\Omega}$$

$I_2 > 10\text{mA}$ is not super strict guideline.

$$\text{Resistor: Max } P = \frac{(17-13)^2}{180\Omega} = .089\text{W} \xrightarrow{\times 2} .178\text{W}$$

$$\Rightarrow \boxed{\frac{1}{4}\text{W}}$$

$$\text{Zener: Max } P = (\text{Max } I_2) \cdot 13\text{V}$$

$$= \left(\frac{17-13}{180\Omega} - \frac{1\text{A}}{3501} \right) (13\text{V}) = .285\text{W} \xrightarrow{\times 2} .57\text{W}$$

$$\text{Choose } \boxed{1\text{W}}$$

However, $\frac{1}{2}\text{W}$ would probably be OK.