Name

Physics 111 Quiz #2, October 2, 2015

*Please show all work, thoughts and/or reasoning in order to receive partial credit. The quiz is worth 10 points total.* 

I affirm that I have carried out my academic endeavors with full academic honesty.

You are given the circuit below in which a battery V = 12V is connected to some resistors, where each resistor has a value  $R = 200\Omega$ . There is also a switch S wired in the circuit.



1. By what factor does the current increase or decreases when the switch S is open compared to when it's closed? That is, calculate the ratio of  $I_{closed}/I_{open}$  and state whether the current increases or decreases when the switch is closed.

Switch Open:

$$R_{3} \text{ and } R_{4} \text{ are in parallel: } \frac{1}{R_{34}} = \frac{1}{R_{3}} + \frac{1}{R_{4}} = \frac{1}{200\Omega} + \frac{1}{200\Omega} = \frac{2}{200\Omega} \rightarrow R_{34} = 100\Omega$$

$$R_{1} \text{ and } R_{34} \text{ are in series: } R_{eq} = R_{1} + R_{34} = 200\Omega + 100\Omega = 300\Omega$$
The current produced:  $I_{open} = \frac{V}{R_{eq}} = \frac{12V}{300\Omega} = 0.04A = 40 \text{ mA}$ 

Switch Closed:

The current produced: 
$$I_{closed} = \frac{V}{R_{eq}} = \frac{12V}{266.7\Omega} = 0.045A = 45mA$$

The ratio  $\frac{I_{closed}}{I_{open}} = \frac{45mA}{40mA} = 1.1$  and the current increases.

- 2. When the switch S is closed (compared to when the switch S is open) what happens to the potential difference across  $R_4$ ?
  - a. The potential difference across  $R_4$  increases.
  - b.) The potential difference across  $R_4$  decreases.
  - c. The potential difference across  $R_4$  stays the same.
  - d. The potential difference across  $R_4$  is unable to be determined.
- 3. Suppose that each resistor is rated at  $\frac{1}{2}W$ . What is the maximum size battery you could use to power the circuit when the switch S is closed?

The needed power produced by the battery is the sum of all the powers of all the resistors.

$$P = \sum_{i} P_i = 4\left(\frac{1}{2}W\right) = 2W$$

Since we know the equivalent resistance we can determine the current that the battery needs to produce. We have:

$$P = I_{total}^2 R_{eq} \rightarrow I_{total} = \sqrt{\frac{P}{R_{eq}}} = \sqrt{\frac{2W}{266.7\Omega}} = 0.087A.$$

The maximum potential is given from  $P = I_{total}V \rightarrow V = \frac{P}{I_{total}} = \frac{2W}{0.087A} = 23.1V$ .

**Physics 111 Equation Sheet** 

**Electric Forces, Fields and Potentials** 

$$\vec{F} = k \frac{Q_1 Q_2}{r^2} \hat{r}$$
$$\vec{E} = \frac{\vec{F}}{q}$$
$$\vec{E}_Q = k \frac{Q}{r^2} \hat{r}$$
$$PE = k \frac{Q_1 Q_2}{r}$$
$$V(r) = k \frac{Q}{r}$$
$$E_x = -\frac{\Delta V}{\Delta x}$$
$$W = -q \Delta V_{f,i}$$

## **Magnetic Forces and Fields**

 $F = qvB\sin\theta$   $F = IlB\sin\theta$   $\tau = NIAB\sin\theta = \mu B\sin\theta$   $PE = -\mu B\cos\theta$  $B = \frac{\mu_0 I}{2\pi r}$ 

 $\mathcal{E}_{induced} = -N \frac{\Delta \phi_B}{\Delta t} = -N \frac{\Delta (BA \cos \theta)}{\Delta t}$ Constants  $g = 9.8 \frac{m}{s^2}$   $le = 1.6 \times 10^{-19} C$   $k = \frac{1}{4\pi \varepsilon_o} = 9 \times 10^9 \frac{C^2}{Nm^2}$   $\varepsilon_o = 8.85 \times 10^{-12} \frac{Nm^2}{C^2}$   $leV = 1.6 \times 10^{-19} J$   $\mu_o = 4\pi \times 10^{-7} \frac{Tm}{A}$   $c = 3 \times 10^8 \frac{m}{s}$   $h = 6.63 \times 10^{-34} Js$   $m_e = 9.11 \times 10^{-31} kg = \frac{0.511 MeV}{c^2}$   $m_p = 1.67 \times 10^{-27} kg = \frac{937.1MeV}{c^2}$   $m_n = 1.69 \times 10^{-27} kg = \frac{948.3MeV}{c^2}$   $lamu = 1.66 \times 10^{-27} kg = \frac{931.5MeV}{c^2}$   $N_A = 6.02 \times 10^{23}$   $Ax^2 + Bx + C = 0 \rightarrow x = \frac{-B \pm \sqrt{B^2 - 4AC}}{2A}$  **Electric Circuits** 

$$I = \frac{\Delta Q}{\Delta t}$$

$$V = IR = I \left(\frac{\rho L}{A}\right)$$

$$R_{series} = \sum_{i=1}^{N} R_{i}$$

$$\frac{1}{R_{parallel}} = \sum_{i=1}^{N} \frac{1}{R_{i}}$$

$$P = IV = I^{2}R = \frac{V^{2}}{R}$$

$$Q = CV = \left(\frac{\kappa \varepsilon_{0} A}{d}\right)V = (\kappa C_{0})V$$

$$PE = \frac{1}{2}QV = \frac{1}{2}CV^{2} = \frac{Q^{2}}{2C}$$

$$Q_{charge}(t) = Q_{max}\left(1 - e^{-\frac{t}{RC}}\right)$$

$$Q_{discharge}(t) = Q_{max}e^{-\frac{t}{RC}}$$

$$C_{parallel} = \sum_{i=1}^{N} C_{i}$$

$$\frac{1}{C_{series}} = \sum_{i=1}^{N} \frac{1}{C_{i}}$$

Light as a Particle & Relativity  $E = hf = \frac{hc}{\lambda} = pc$   $KE_{max} = hf - \phi = eV_{stop}$   $\Delta \lambda = \frac{h}{m_e c} (1 - \cos \phi)$   $\gamma = \frac{1}{\sqrt{1 - \frac{v^2}{c^2}}}$   $p = \gamma mv$   $E_{total} = KE + E_{rest} = \gamma mc^2$   $E_{total}^2 = p^2 c^2 + m^2 c^4$   $E_{rest} = mc^2$   $KE = (\gamma - 1)mc^2$ 

## Geometry

Circles:  $C = 2\pi r = \pi D$   $A = \pi r^2$ Triangles:  $A = \frac{1}{2}bh$ Spheres:  $A = 4\pi r^2$   $V = \frac{4}{3}\pi r^3$  Light as a Wave

1

$$c = f\lambda = \frac{1}{\sqrt{\varepsilon_o \mu_o}}$$

$$S(t) = \frac{energy}{time \times area} = c\varepsilon_o E^2(t) = c \frac{B^2(t)}{\mu_0}$$

$$I = S_{avg} = \frac{1}{2} c\varepsilon_o E_{max}^2 = c \frac{B_{max}^2}{2\mu_0}$$

$$P = \frac{S}{c} = \frac{Force}{Area}$$

$$S = S_o \cos^2 \theta$$

$$v = \frac{1}{\sqrt{\varepsilon\mu}} = \frac{c}{n}$$

$$\theta_{inc} = \theta_{refl}$$

$$n_1 \sin \theta_1 = n_2 \sin \theta_2$$

$$\frac{1}{f} = \frac{1}{d_o} + \frac{1}{d_i}$$

$$M = \frac{h_i}{h_o} = -\frac{d_i}{d_o}$$

$$M_{total} = \prod_{i=1}^N M_i$$

$$S_{out} = S_{in} e^{-\sum_i \mu_i x_i}$$

$$HU = \frac{\mu_w - \mu_m}{\mu_w}$$

Nuclear Physics  $E_{binding} = (Zm_p + Nm_n - m_{rest})c^2$   $\frac{\Delta N}{\Delta t} = -\lambda N_o \rightarrow N(t) = N_o e^{-\lambda t}$   $A(t) = A_o e^{-\lambda t}$   $m(t) = m_o e^{-\lambda t}$   $t_{\frac{1}{2}} = \frac{\ln 2}{\lambda}$ 

**Misc. Physics 110 Formulae** 

$$\vec{F} = \frac{\Delta \vec{p}}{\Delta t} = \frac{\Delta (mv)}{\Delta t} = m\vec{a}$$
  

$$\vec{F} = -k\vec{y}$$
  

$$\vec{F}_c = m\frac{v^2}{R}\hat{r}$$
  

$$W = \Delta KE = \frac{1}{2}m(v_f^2 - v_i^2) = -\Delta PE$$
  

$$PE_{gravity} = mgy$$
  

$$PE_{spring} = \frac{1}{2}ky^2$$
  

$$|\vec{A}| = \sqrt{A_x^2 + A_y^2}$$
  

$$\phi = \tan^{-1}\left(\frac{A_y}{A_x}\right)$$
  

$$\vec{v}_f = \vec{v}_i + \vec{a}t$$
  

$$v_f^2 = v_i^2 + 2a\Delta x$$
  

$$\vec{x}_f = \vec{x}_i + \vec{v}_i t + \frac{1}{2}\vec{a}t^2$$