Name_____

Physics 111 Quiz #3, January 29, 2021

Please show all work, thoughts and/or reasoning in order to receive partial credit. The quiz is worth 10 points total.

I affirm that I have carried out my academic endeavors with full academic honesty.

1. A capacitor of unknown capacitance is needed in a circuit containing a $100M\Omega$ resistor and a 30V battery. This circuit will be used as a timer in part of a larger device. The design of the other device requires the capacitor to charge to 72% of its maximum value in a time of 1.7s. What value of the capacitance would be needed to achieve this?

$$Q(t) = Q_{max} \left(1 - e^{-\frac{t}{RC}} \right) \rightarrow -\frac{t}{RC} = \ln \left(\frac{Q(t)}{Q_{max}} \right) \rightarrow C = -\frac{t}{R \ln \left(\frac{Q(t)}{Q_{max}} \right)} = -\frac{1.7s}{100 \times 10^6 \Omega \ln \left(\frac{0.72Q_{max}}{Q_{max}} \right)}$$
$$C = 1.3 \times 10^{-8} F$$

2. When fully charged, what maximum charge could the capacitor store?

 $Q_{max} = CV_{max} = 1.3 \times 10^{-8} F \times 30V = 4 \times 10^{-7} C$

3. How much energy is stored in the capacitor when it is 72% charged?

$$U = \frac{1}{2}CV^2 = \frac{1}{2} \times 1.3 \times 10^{-8}F(0.72 \times 30V)^2 = 3 \times 10^{-6}J$$

4. Suppose that the plates of this capacitor were separated by a distance d = 1cm. If the plates were circular in shape, what would be the radius the capacitor plates? Assume the capacitor is air-filled so that $\kappa = 1$.

$$C = \frac{\kappa \varepsilon_0 A}{d} = \frac{\kappa \varepsilon_0 \pi r^2}{d} \to r = \sqrt{\frac{Cd}{\pi \kappa \varepsilon_0}} = \sqrt{\frac{1.3 \times 10^{-8} F \times 0.01 m}{\pi \times 8.85 \times 10^{-12} \frac{C^2}{Nm^2}}} = 2.16m$$

- 5. Suppose that you wired a different air-filled capacitor with capacitance C to a battery with potential difference V. After you wired this capacitor to the battery you realized that the value of the capacitance was too small for what you needed it to do. To change the value of the capacitance you could unwire the entire circuit and start over or realizing that you could increase the capacitance to the value you need by inserting a dielectric between the plates of the capacitor. Which of the following quantities will also increase due to you inserting the dielectric between the plates of the capacitor?
 - a. The electric field between the plates would also increase.
 - b. The potential difference across the plates would increase.
 - c. The area of the plates would increase.
 - d.) The charge on the plates would increase.
 - e. None of the above quantities would increase.

Physics 111 Equation Sheet

Electric Forces, Fields and Potentials

$$\vec{F} = k \frac{Q_1 Q_2}{r^2} \hat{r}$$
$$\vec{E} = \frac{\vec{F}}{q}$$
$$\vec{E}_Q = k \frac{Q}{r^2} \hat{r}$$
$$PE = k \frac{Q_1 Q_2}{r}$$
$$V(r) = k \frac{Q}{r}$$
$$E_x = -\frac{\Delta V}{\Delta x}$$
$$W = -q \Delta V_{f,i}$$

Magnetic Forces and Fields

 $F = qvB\sin\theta$ $F = IlB\sin\theta$ $\tau = NIAB\sin\theta = \mu B\sin\theta$ $PE = -\mu B\cos\theta$ $B = \frac{\mu_0 I}{2\pi r}$

$$\varepsilon_{induced} = -N \frac{\Delta (\psi_B)}{\Delta t} = -N \frac{\Delta (D) A \cos (S)}{\Delta t}$$
Constants
 $g = 9.8 \frac{m}{s^2}$
 $le = 1.6 \times 10^{-19} C$
 $k = \frac{1}{4\pi\varepsilon_o} = 9 \times 10^9 \frac{Nm^2}{C^2}$
 $\varepsilon_o = 8.85 \times 10^{-12} \frac{C^2}{Nm^2}$
 $leV = 1.6 \times 10^{-19} J$
 $\mu_o = 4\pi \times 10^{-7} \frac{Tm}{A}$
 $c = 3 \times 10^8 \frac{m}{s}$
 $h = 6.63 \times 10^{-34} Js$
 $m_e = 9.11 \times 10^{-31} kg = \frac{0.511 MeV}{c^2}$
 $m_p = 1.67 \times 10^{-27} kg = \frac{937.1MeV}{c^2}$
 $m_n = 1.69 \times 10^{-27} kg = \frac{948.3MeV}{c^2}$
 $lamu = 1.66 \times 10^{-27} kg = \frac{931.5MeV}{c^2}$
 $N_A = 6.02 \times 10^{23}$
 $Ax^2 + Bx + C = 0 \rightarrow x = \frac{-B \pm \sqrt{B^2 - 4AC}}{2A}$

Electric Circuits

$$I = \frac{\Delta Q}{\Delta t}$$

$$V = IR = I\left(\frac{\rho L}{A}\right)$$

$$R_{series} = \sum_{i=1}^{N} R_{i}$$

$$\frac{1}{R_{parallel}} = \sum_{i=1}^{N} \frac{1}{R_{i}}$$

$$P = IV = I^{2}R = \frac{V^{2}}{R}$$

$$Q = CV = \left(\frac{\kappa \varepsilon_{0}A}{d}\right)V = (\kappa C_{0})V$$

$$PE = \frac{1}{2}QV = \frac{1}{2}CV^{2} = \frac{Q^{2}}{2C}$$

$$Q_{charge}(t) = Q_{max}\left(1 - e^{-\frac{t}{RC}}\right)$$

$$Q_{discharge}(t) = Q_{max}e^{-\frac{t}{RC}}$$

$$C_{parallel} = \sum_{i=1}^{N} C_{i}$$

$$\frac{1}{C_{series}} = \sum_{i=1}^{N} \frac{1}{C_{i}}$$

 $\Delta \phi_B = \sqrt{\Delta(BA\cos\theta)}$ Light as a Particle & Relativity Nuclear Physics

$$E = hf = \frac{hc}{\lambda} = pc$$

$$KE_{max} = hf - \phi = eV_{stop}$$

$$\Delta \lambda = \frac{h}{m_e c} (1 - \cos \phi)$$

$$\gamma = \frac{1}{\sqrt{1 - \frac{v^2}{c^2}}}$$

$$p = \gamma mv$$

$$E_{total} = KE + E_{rest} = \gamma mc^2$$

$$E_{total}^2 = p^2 c^2 + m^2 c^4$$

$$E_{rest} = mc^2$$

$$KE = (\gamma - 1)mc^2$$

Geometry

 $Ci \ r \ c \ l \ e \ s \ C = 2\pi r = \pi D$ $A = \pi r^2$ $Tri angles A = \frac{1}{2}bh$ *Spheres* $A = 4\pi r^{2}$ $V = \frac{4}{3}\pi r^{3}$

Light as a Wave

$$c = f I = \frac{1}{\sqrt{e_o m_o}}$$

$$S(t) = \frac{energy}{time \ area} = ce_o E^2(t) = c \frac{B^2(t)}{m_0}$$

$$I = S_{avg} = \frac{1}{2} ce_o E_{max}^2 = c \frac{B_{max}^2}{2m_0}$$

$$P = \frac{S}{c} = \frac{Force}{Area}$$

$$S = S_o \cos^2 q$$

$$v = \frac{1}{\sqrt{em}} = \frac{c}{n}$$

$$q_{inc} = q_{refl}$$

$$n_1 \sin q_1 = n_2 \sin q_2$$

$$\frac{1}{f} = \frac{1}{d_o} + \frac{1}{d_i}$$

$$M = \frac{h_i}{h_o} = -\frac{d_i}{d_o}$$

$$M_{total} = \bigotimes_{i=1}^{N} M_i$$

$$S_{out} = S_{in} e^{-\frac{a_i}{t}}$$

$$HU = \frac{m_w - m_m}{m_w}$$

$$\begin{split} E_{binding} &= \left(Zm_p + Nm_n - m_{rest} \right) c^2 \\ \frac{\Delta N}{\Delta t} &= -\lambda N_o \rightarrow N(t) = N_o e^{-\lambda t} \\ A(t) &= A_o e^{-\lambda t} \\ m(t) &= m_o e^{-\lambda t} \\ t_{\frac{1}{2}} &= \frac{\ln 2}{\lambda} \end{split}$$

Misc. Physics 110 Formulae

$$\vec{F} = \frac{\Delta \vec{p}}{\Delta t} = \frac{\Delta (mv)}{\Delta t} = m\vec{a}$$

$$\vec{F} = -k\vec{y}$$

$$\vec{F}_c = m\frac{v^2}{R}\hat{r}$$

$$W = \Delta KE = \frac{1}{2}m(v_f^2 - v_i^2) = -\Delta PE$$

$$PE_{gravity} = mgy$$

$$PE_{spring} = \frac{1}{2}ky^2$$

$$|\vec{A}| = \sqrt{A_x^2 + A_y^2}$$

$$\phi = \tan^{-1}\left(\frac{A_y}{A_x}\right)$$

$$\vec{v}_f = \vec{v}_i + \vec{a}t$$

$$v_f^2 = v_i^2 + 2a\Delta x$$

$$\vec{x}_f = \vec{x}_i + \vec{v}_i t + \frac{1}{2}\vec{a}t^2$$