Name

Physics 111 Quiz #4, January 30, 2019

Please show all work, thoughts and/or reasoning in order to receive partial credit. The quiz is worth 10 points total.

I affirm that I have carried out my academic endeavors with full academic honesty.

A circuit is constructed using five resistors each with resistance 100Ω connected to a 15V battery. The switch S is used to put in or take out resistors R_4 and R_5 from the circuit. Unless otherwise specified, assume that the switch S is closed.



1. What is the total current produced by the battery?

 R_{4} and R_{5} are in series: $R_{45} = R_{4} + R_{5} = 100\Omega + 100\Omega = 200\Omega$

 R_{3} and R_{45} are in parallel: $\frac{1}{R_{345}} = \frac{1}{R_{3}} + \frac{1}{R_{45}} = \frac{1}{100\Omega} + \frac{1}{200\Omega} = \frac{3}{200\Omega} \rightarrow R_{345} = \frac{200}{3}\Omega = 66.7\Omega$

 R_1 , R_2 , and R_{345} are in series: $R_{eq} = R_{12345} = R_1 + R_2 + R_{345} = 100\Omega + 100\Omega + 66.7\Omega = 266.7\Omega$

The total current is: $I_{total} = \frac{V}{R_{eq}} = \frac{15V}{266.7\Omega} = 0.0563A = 56.3mA$

2. What is the potential difference across resistor R_4 ?

$$\begin{split} &V - V_{R_1} - V_{R_{345}} - V_{R_2} = 0 \\ &\to V_{R_{345}} = V - V_{R_1} - V_{R_2} = V - I_{total} \left(R_1 + R_2 \right) = 15V - 0.0563A \times 200 = 3.74V \\ &\to V_{R_{345}} = V_{R_3} = V_{R_{45}} \\ &\to V_{R_{45}} = V_{R_4} + V_{R_5} = 2V_{R_4} \Longrightarrow V_{R_4} = \frac{V_{R_{45}}}{2} = \frac{3.74V}{2} = 1.87V \end{split}$$

3. What is the current through resistor R_3 ?

$$V_{R_{345}} = V_{R_3} = I_3 R_3 \rightarrow I_3 = \frac{V_{R_{345}}}{R_3} = \frac{3.74V}{100\Omega} = 0.0374A = 37.4mA$$

4. What is the total power produced by the battery?

$$P = I_{total} V = I_{total}^2 R_{eq} = \frac{V^2}{R_{eq}} = (0.0563A)^2 266.7\Omega = 0.845W = 845mW$$

- 5. What happens to the current through resistor R_3 when the switch S is opened?
 - a. The current through resistor R_3 increases because the equivalent circuit resistance increases.
 - b. The current through resistor R_3 increases because the equivalent circuit resistance decreases.

c.) The current through resistor R_3 decreases because the equivalent circuit resistance increases.

- d. The current through resistor R_3 decreases because the equivalent circuit resistance decreases.
- e. The current through resistor R_3 remains the same because the battery has a constant voltage.

Physics 111 Equation Sheet

Electric Forces, Fields and Potentials

$$\vec{F} = k \frac{Q_1 Q_2}{r^2} \hat{r}$$
$$\vec{E} = \frac{\vec{F}}{q}$$
$$\vec{E}_Q = k \frac{Q}{r^2} \hat{r}$$
$$PE = k \frac{Q_1 Q_2}{r}$$
$$V(r) = k \frac{Q}{r}$$
$$E_x = -\frac{\Delta V}{\Delta x}$$
$$W = -q \Delta V_{f,i}$$

Magnetic Forces and Fields

 $F = qvB\sin\theta$ $F = IlB\sin\theta$ $\tau = NIAB\sin\theta = \mu B\sin\theta$ $PE = -\mu B\cos\theta$ $B = \frac{\mu_0 I}{2\pi r}$ $\Lambda \neq \Lambda(R\Lambda \cos \theta)$

$$\varepsilon_{induced} = -N \frac{\Delta \phi_B}{\Delta t} = -N \frac{\Delta (BA \cos \theta)}{\Delta t}$$

Constants

$$\begin{split} g &= 9.8 \frac{m}{s^2} \\ le &= 1.6 \times 10^{-19} C \\ k &= \frac{1}{4\pi\varepsilon_o} = 9 \times 10^9 \frac{Nm^2}{C^2} \\ \varepsilon_o &= 8.85 \times 10^{-12} \frac{C^2}{Nm^2} \\ leV &= 1.6 \times 10^{-19} J \\ \mu_o &= 4\pi \times 10^{-7} \frac{Tm}{A} \\ c &= 3 \times 10^8 \frac{m}{s} \\ h &= 6.63 \times 10^{-34} Js \\ m_e &= 9.11 \times 10^{-31} kg = \frac{0.511 MeV}{c^2} \\ m_p &= 1.67 \times 10^{-27} kg = \frac{937.1 MeV}{c^2} \\ m_n &= 1.69 \times 10^{-27} kg = \frac{948.3 MeV}{c^2} \\ lamu &= 1.66 \times 10^{-27} kg = \frac{931.5 MeV}{c^2} \\ N_A &= 6.02 \times 10^{23} \\ Ax^2 + Bx + C &= 0 \rightarrow x = \frac{-B \pm \sqrt{B^2 - 4AC}}{2A} \end{split}$$

Electric Circuits 10

$$I = \frac{\Delta Q}{\Delta t}$$

$$V = IR = I \left(\frac{\rho L}{A}\right)$$

$$R_{series} = \sum_{i=1}^{N} R_i$$

$$\frac{1}{R_{parallel}} = \sum_{i=1}^{N} \frac{1}{R_i}$$

$$P = IV = I^2 R = \frac{V^2}{R}$$

$$Q = CV = \left(\frac{\kappa \varepsilon_0 A}{d}\right) V = (\kappa C_0) V$$

$$PE = \frac{1}{2} QV = \frac{1}{2} CV^2 = \frac{Q^2}{2C}$$

$$Q_{charge}(t) = Q_{max} \left(1 - e^{-\frac{t}{RC}}\right)$$

$$Q_{discharge}(t) = Q_{max} e^{-\frac{t}{RC}}$$

$$C_{parallel} = \sum_{i=1}^{N} C_i$$

$$\frac{1}{C_{series}} = \sum_{i=1}^{N} \frac{1}{C_i}$$

Light as a Particle & Relativity Nuclear Physics

$$E = hf = \frac{hc}{\lambda} = pc$$

$$KE_{max} = hf - \phi = eV_{stop}$$

$$\Delta \lambda = \frac{h}{m_e c} (1 - \cos \phi)$$

$$\gamma = \frac{1}{\sqrt{1 - \frac{v^2}{c^2}}}$$

$$p = \gamma mv$$

$$E_{total} = KE + E_{rest} = \gamma mc^2$$

$$E_{total}^2 = p^2 c^2 + m^2 c^4$$

$$E_{rest} = mc^2$$

$$KE = (\gamma - 1)mc^2$$

Geometry

Circles: $C = 2\pi r = \pi D$ $A = \pi r^2$ Triangles: $A = \frac{1}{2}bh$ *Spheres*: $A = 4\pi r^{2}$ $V = \frac{4}{3}\pi r^{3}$

Light as a Wave

$$c = f\lambda = \frac{1}{\sqrt{\varepsilon_o \mu_o}}$$

$$S(t) = \frac{energy}{time \times area} = c\varepsilon_o E^2(t) = c\frac{B^2(t)}{\mu_0}$$

$$I = S_{arg} = \frac{1}{2}c\varepsilon_o E_{max}^2 = c\frac{B_{max}^2}{2\mu_0}$$

$$P = \frac{S}{c} = \frac{Force}{Area}$$

$$S = S_o \cos^2 \theta$$

$$v = \frac{1}{\sqrt{\varepsilon\mu}} = \frac{c}{n}$$

$$\theta_{inc} = \theta_{refl}$$

$$n_1 \sin \theta_1 = n_2 \sin \theta_2$$

$$\frac{1}{f} = \frac{1}{d_o} + \frac{1}{d_i}$$

$$M = \frac{h_i}{h_o} = -\frac{d_i}{d_o}$$

$$M_{total} = \prod_{i=1}^{N} M_i$$

$$S_{out} = S_{in} e^{\sum_i \mu_i x_i}$$

$$HU = \frac{\mu_w - \mu_m}{\mu_w}$$

$$E_{binding} = (Zm_p + Nm_n - m_{rest})c^2$$
$$\frac{\Delta N}{\Delta t} = -\lambda N_o \rightarrow N(t) = N_o e^{-\lambda t}$$
$$A(t) = A_o e^{-\lambda t}$$
$$m(t) = m_o e^{-\lambda t}$$
$$t_{\frac{1}{2}} = \frac{\ln 2}{\lambda}$$

Misc. Physics 110 Formulae

$$\vec{F} = \frac{\Delta \vec{p}}{\Delta t} = \frac{\Delta (mv)}{\Delta t} = m\vec{a}$$

$$\vec{F} = -k\vec{y}$$

$$\vec{F}_{c} = m\frac{v^{2}}{R}\hat{r}$$

$$W = \Delta KE = \frac{1}{2}m(v_{f}^{2} - v_{i}^{2}) = -\Delta PE$$

$$PE_{gravity} = mgy$$

$$PE_{spring} = \frac{1}{2}ky^{2}$$

$$|\vec{A}| = \sqrt{A_{x}^{2} + A_{y}^{2}}$$

$$\phi = \tan^{-1}\left(\frac{A_{y}}{A_{x}}\right)$$

$$\vec{v}_{f} = \vec{v}_{i} + \vec{a}t$$

$$v_{f}^{2} = v_{i}^{2} + 2a\Delta x$$

$$\vec{x}_{f} = \vec{x}_{i} + \vec{v}_{i}t + \frac{1}{2}\vec{a}t^{2}$$