

Name _____

Physics 121 Quiz #3, February 2, 2018

Please show all work, thoughts and/or reasoning in order to receive partial credit. The quiz is worth 10 points total.

I affirm that I have carried out my academic endeavors with full academic honesty.

A parallel plate capacitor is constructed out of two square metal plates of length $L = 25\text{cm}$ separated by 6mm of paper ($\kappa = 2.3$).

1. What is the capacitance of the system?

$$C = \frac{\kappa \epsilon_0 A}{s} = \frac{2.3 \times 8.85 \times 10^{-12} \frac{\text{C}^2}{\text{Nm}^2} \times (0.25\text{m})^2}{6 \times 10^{-6} \text{m}} = 2.12 \times 10^{-10} \text{F}$$

2. Suppose that two of these capacitors were wired in series and the combination was wired to a $50\text{M}\Omega$ resistor. What is the time constant of the circuit?

$$\frac{1}{C_{eq}} = \frac{1}{C_2} + \frac{1}{C_1} = \frac{2}{C} \rightarrow C_{eq} = \frac{C}{2} = \frac{2.12 \times 10^{-10} \text{F}}{2} = 1.06 \times 10^{-10} \text{F}$$

$$\tau = RC = 50 \times 10^6 \Omega \times 1.06 \times 10^{-10} \text{F} = 5.3 \times 10^{-3} \text{s}$$

3. The two capacitors and resistor are wired to a battery with constant potential difference V . In multiples or fractions of the time constant, how long will it take to charge this two capacitor system to 83.7% of the rated battery potential?

$$V(t) = 0.837V = V \left(1 - e^{-\frac{t}{RC}} \right) \rightarrow t = -RC \ln \left(1 - \frac{V(t)}{V} \right) = -RC \ln \left(1 - \frac{0.837V}{V} \right) = 1.8RC$$

4. How much energy is stored in each of the capacitors when fully charged? Assume that the two capacitors and resistor are connected to a $10V$ battery.

$$U_1 = U_2 = \frac{1}{2} C V_1^2 = \frac{1}{2} \times 2.12 \times 10^{-10} F \times (5V)^2 = 2.7 \times 10^{-9} J$$

$$U_T = \frac{1}{2} C_{eq} V^2 = \frac{1}{2} \times 1.06 \times 10^{-10} F \times (10V)^2 = 5.3 \times 10^{-9} J = U_1 + U_2 = 2U_1 \rightarrow U_1 = \frac{U_T}{2} = 2.7 \times 10^{-9} J$$

5. Suppose instead that you have a single resistor R connected to a capacitor C . This resistor-capacitor combination is connected to a switch S and a battery with constant potential V . The capacitor is initially uncharged and the switch is open. At time $t = 0$ the switch is closed and the capacitor begins to charge. As time increases, which of the following is true?
- $V_C \uparrow$ and $V_R \uparrow$.
 - $V_C \uparrow$ and $V_R \downarrow$.
 - $V_C \downarrow$ and $V_R \uparrow$.
 - $V_C \downarrow$ and $V_R \downarrow$.
 - Both V_C and V_R remain at a constant potential because the battery has a constant potential.

Physics 121 Equation Sheet

Electric Forces, Fields and Potentials

$$\vec{F} = k \frac{Q_1 Q_2}{r^2} \hat{r}; \quad \hat{r} = \frac{\vec{r}_o - \vec{r}_s}{|\vec{r}_o - \vec{r}_s|}$$

$$\vec{E} = \frac{\vec{F}}{q} = \int d\vec{E} = \int dE \hat{r} = \int \frac{k dq}{r^2} \hat{r}$$

$$\vec{E}_o = k \frac{Q}{r^2} \hat{r}$$

$$|\vec{E}_{||}| = \frac{2kqs}{r^3}; \text{ dipole } r \gg s$$

$$|\vec{E}_{\perp}| = \frac{kqs}{r^3}; \text{ dipole } r \gg s$$

$$|\vec{E}_{rod\perp}| = \frac{1}{4\pi\epsilon_0} \left[\frac{Q}{r\sqrt{r^2 + (L/2)^2}} \right]$$

$$|\vec{E}_{rod||}| = \frac{1}{4\pi\epsilon_0} \left[\frac{Q}{r(L+r)} \right]; |\vec{E}_{rod||}| \sim \frac{1}{4\pi\epsilon_0} \left(\frac{Q}{rL} \right) \quad L \gg r$$

$$|\vec{E}_{ring}| = \frac{1}{4\pi\epsilon_0} \left[\frac{Qz}{(R^2 + z^2)^{3/2}} \right]$$

$$|\vec{E}_{disk}| = \frac{Q}{2\pi\epsilon_0 R^2} \left[1 - \frac{z}{\sqrt{R^2 + z^2}} \right]; |\vec{E}_{disk}| \sim \frac{Q}{2\epsilon_0 A} \left[1 - \frac{z}{R} \right] \quad z \ll R; \quad |\vec{E}_{disk}| \sim \frac{Q}{2\epsilon_0 A} \quad z \ll R$$

$$|\vec{E}_{capacitor}| \sim \frac{Q}{\epsilon_0 A}; \quad |\vec{E}_{fringe}| \sim \frac{Q}{2\epsilon_0 A} \left(\frac{s}{R} \right)$$

$$W = -q\Delta V = -\Delta U = \Delta K; \quad U = \sum_{i \neq j} \frac{kQ_i Q_j}{r_{ij}}$$

$$V_o = \frac{kQ}{r}; \quad V_{Q's} = \sum_i \frac{kQ_i}{r_i}$$

$$\Delta V = -\int \vec{E} \cdot d\vec{r}$$

$$E_x = -\frac{\Delta V}{\Delta x}; \quad E_y = -\frac{\Delta V}{\Delta y}; \quad E_z = -\frac{\Delta V}{\Delta z}; \quad \vec{E} = -\left\langle \frac{dV}{dx}, \frac{dV}{dy}, \frac{dV}{dz} \right\rangle$$

$$Q = \left(\frac{\kappa\epsilon_0 A}{s} \right) \Delta V$$

$$U = \frac{1}{2} QV = \frac{1}{2} CV^2 = \frac{Q^2}{2C}$$

$$Q = Q_{\max} \left(1 - e^{-\frac{t}{RC}} \right); \quad Q = Q_{\max} e^{-\frac{t}{RC}}$$

$$I = \frac{\Delta Q}{\Delta t} = i|e| = n|e|Av_d; \quad \vec{v}_d = \mu\vec{E}$$

$$\vec{B} = \frac{\mu_o}{4\pi} \left(\frac{q\vec{v} \times \hat{r}}{r^2} \right)$$

$$d\vec{B} = \frac{\mu_o I}{4\pi} \left(\frac{d\vec{l} \times \hat{r}}{r^2} \right)$$

$$|\vec{B}_{wire}| = \frac{\mu_o I l}{4\pi r \sqrt{(\frac{l}{2})^2 + r^2}}; \quad |\vec{B}_{wire}| \approx \frac{\mu_o I}{2\pi r} \quad L \gg r$$

$$|\vec{B}_{ring}| = \frac{\mu_o IR^2}{2(z^2 + R^2)^{3/2}}; \quad |\vec{B}_{ring}| \approx \frac{\mu_o IR^2}{2z^3} \quad z \ll R$$

Constants

$$g = 9.8 \frac{m}{s^2}$$

$$1e = 1.6 \times 10^{-19} C$$

$$k = \frac{1}{4\pi\epsilon_o} = 9 \times 10^9 \frac{Nm^2}{C^2}$$

$$\epsilon_o = 8.85 \times 10^{-12} \frac{C^2}{Nm^2}$$

$$1eV = 1.6 \times 10^{-19} J$$

$$\mu_o = 4\pi \times 10^{-7} \frac{Tm}{A}$$

$$c = 3 \times 10^8 \frac{m}{s}$$

$$h = 6.63 \times 10^{-34} Js$$

$$m_e = 9.11 \times 10^{-31} kg = \frac{0.511 MeV}{c^2}$$

$$m_p = 1.67 \times 10^{-27} kg = \frac{937.1 MeV}{c^2}$$

$$m_n = 1.69 \times 10^{-27} kg = \frac{948.3 MeV}{c^2}$$

$$1amu = 1.66 \times 10^{-27} kg = \frac{931.5 MeV}{c^2}$$

$$N_A = 6.02 \times 10^{23}$$

$$Ax^2 + Bx + C = 0 \rightarrow x = \frac{-B \pm \sqrt{B^2 - 4AC}}{2A}$$