


**4 problems for 100 pts****Problem #1: Short Answers (25 pts)**

- (a) Strain Gauge (2 pts): Constantan is an alloy of which two metallic elements?
- (b) True or False (2 pts): An instrumentation amplifier should have high input impedance and high common-mode gain. **If you choose false, explain why.**
- (c) Thermistor (2 pts): What is a common material and sign of tempco (positive or negative) of a thermistor?
- (d) Thermocouple (2 pts): Briefly explain the purpose of cold junction compensation in a thermocouple probe.
- (e) True or False (2 pts): The output of a thermopile detector depends on  $(T_{\text{OBJ}} - T_{\text{AMB}})^4$ , where  $T_{\text{OBJ}}$  is the object temperature and  $T_{\text{AMB}}$  is the ambient temperature. **If you choose false, explain why.**

- (f) ECG electrodes (3 pts): What is the most common type of ECG electrode, and what chemical reactions occur to allow current to flow out of the body?
- (g) Action Potential (3 pts): The action potential of a nerve involves a travelling repolarization (inward rush of Krypton atoms) followed by a travelling depolarization (outward rush of calcium ions). **Make corrections, wherever necessary, to the previous statement about the action potential in a nerve cell.**
- (h) ECG (3 pts): Explain the positions of the lead vectors in 12-lead ECG.
- (i) ECG (3 pts): Choose true or false for each of the following statements. **If you choose false, then provide the correct statement.**
- (i) The natural pacemaker of the heart is the Kirchhoff Current (KC) node.
  - (ii) In the cardiac cycle, the right atrium and left ventricle contract together, followed by the left atrium and right ventricle contracting together.
  - (iii) The T-wave corresponds to atrial repolarization.
- (j) EMG (3 pts): Explain the smallest neuromuscular unit that can be activated and also how these units are involved in high muscle activity.
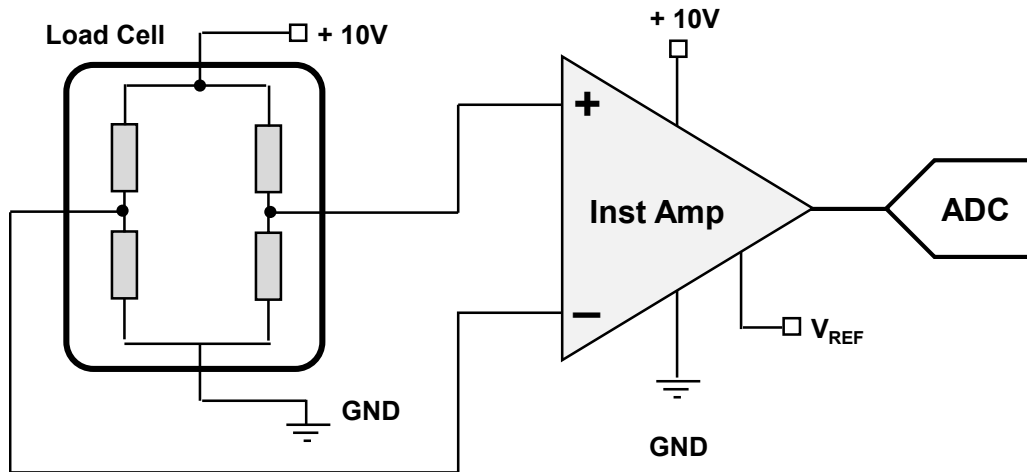
## Problem #2: Load Cell (25 pts)

You are asked to help design a materials testing system that can both compress and stretch a sample. The customer wants to measure a maximum load of +3 kN (compress) and -3 kN (stretch) with a sensitivity of 10 N. The load cell has  $RO = 1.2 \text{ mV/V @ 6 kN}$  with an excitation voltage  $V_S = +10\text{V}$ . The amplifier has a differential gain  $A_d = 200$  and an output noise voltage  $V_N = 2 \text{ mV}_{\text{RMS}}$ . The amplifier is powered by +10V and GND, so you can assume the amplifier output is limited to 1V (min) and 9V (max). The ADC has 10 bits (0 to 5V).




- a) The reference voltage can be either  $V_{\text{REF}} = 2\text{V}$  or  $3.5\text{V}$ . Which values (i.e. none, one of them, or both) satisfy all the design specs? **You must clearly explain why a  $V_{\text{REF}}$  works or does not work.** Show all work!
- b) Suppose you find an ADC that operates from 0 to 10V with 14 bits. Explain whether this new ADC produces a system that satisfies all the design specs. Show all work! NOTE: You can use any relevant results from part (a) (i.e. you do not need to re-do all calculations).

(extra sheet for work)
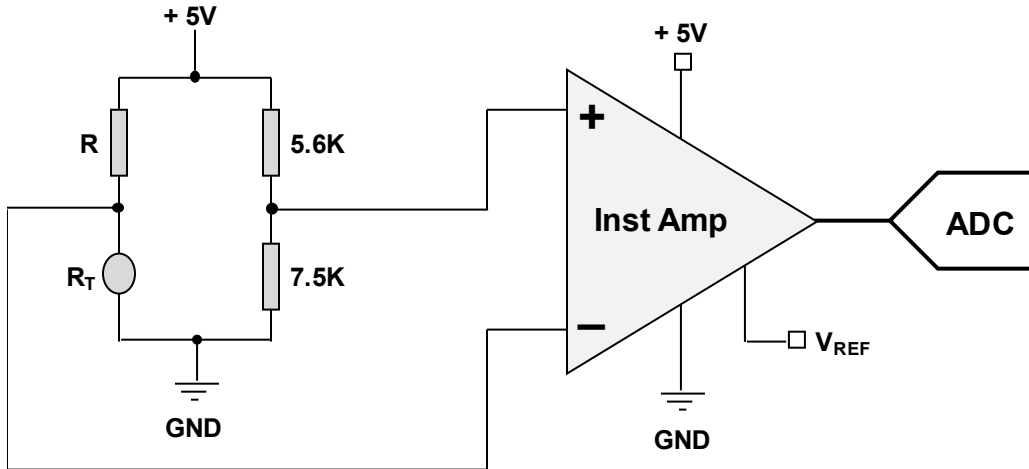
### Problem #3: Temperature (25 pts)

You are asked to design a temperature measurement system that operates from 20 °C to 45 °C (e.g. for an egg incubator) with a sensitivity of 0.1 °C. You decide to use a thermistor  $R_T$  in a quarter bridge powered by +5V, as shown in the figure below. The instrumentation amplifier ( $A_d = 2$ ) is powered by +5V and GND, so you can assume the amplifier output is limited to within 1V of each power supply. The reference voltage is  $V_{REF} = 3V$ . The ADC operates from 0 to 5V with 10 bits. The thermistor properties are the following:

- $T = 20\text{ °C}$ :  $R_T = 12.49\text{ kohm}$   $\alpha = -4.51\text{ \%/°C}$
- $T = 45\text{ °C}$ :  $R_T = 4.37\text{ kohm}$   $\alpha = -3.91\text{ \%/°C}$



- You must choose between a bridge resistor  $R = 3.3\text{ kohm}$  or  $4.7\text{ kohm}$ . Is an operating temperature range of 20 °C to 45 °C feasible with one, neither, or either resistor value? **If you rule out a resistor, you must clearly explain why.**
- Suppose the amplifier has an output noise voltage of  $V_N = 1\text{ mV}_{RMS}$ . We can ignore self-heating if the temperature rise is less than the sensitivity at  $T = 20\text{ °C}$ . Can we ignore self-heating? Assume a dissipation factor  $\delta = 7\text{ mW/°C}$ . Show all work!


(extra sheet for work)

## Problem #4: ECG Amplifier (25 pts)

Consider an ECG system where the input PQRST waveform has a 1.5 mV amplitude R-wave. The patient's heart rate is 90 beats per minute. The patient's breathing motion also produces an input differential voltage described by a 20 mV peak-to-peak, 0.25 Hz sine wave. Power line interference produces a 3V peak-to-peak, 60 Hz common mode voltage. The instrumentation amplifier has a differential gain  $A_d = 20$ , CMRR = 85 dB, and  $V_{REF} = 1V$ .

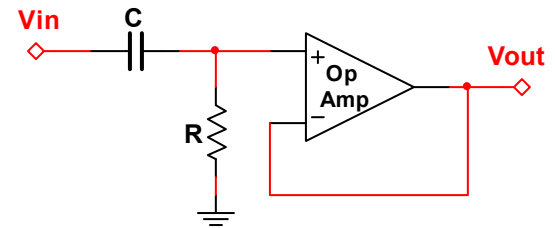- a) Compute and sketch the instrumentation amplifier output over a 4 second interval. Label important features!
- b) After the instrumentation amplifier, we want a circuit that blocks DC. Use the Golden Rules to show that the op amp output is:

$$\frac{V_{out}}{V_{in}} = \frac{jf/f_c}{1+jf/f_c}$$



**NOTE: Make sure to clearly define  $f_c$ !**

- c) Let us assume that the circuit from Part (b) passes a signal frequency when  $|V_{OUT}/V_{IN}| > 0.9$ . Let your ECG signal have frequency content that spans from 2 to 100 Hz. Suppose  $C = 0.33 \mu F$ . The available resistor values are  $R = 100 \text{ kohm}$ ,  $220 \text{ kohm}$ ,  $560 \text{ kohm}$ ,  $820 \text{ kohm}$ , and  $1 \text{ Mohm}$ . Which is the minimum acceptable value? Show all work!

(extra sheet for work)



(extra sheet for work)