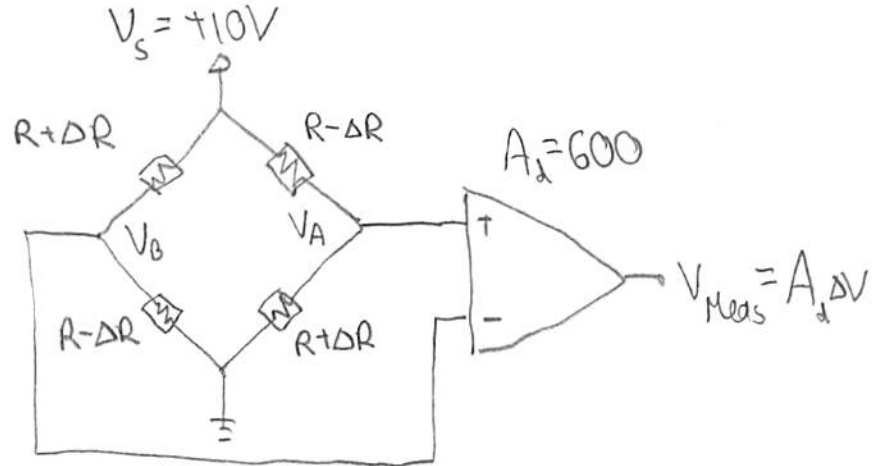


① +5

$$V_A = \frac{V_s}{(R-\Delta R) + (R+\Delta R)} (R+\Delta R)$$

$$= V_s \frac{R+\Delta R}{2R} = \frac{V_s}{2} + \frac{V_s}{2} \left[\frac{\Delta R}{R} \right]$$

↑
GE



$$V_A = \frac{V_s}{2} + \frac{V_s}{2} GE = \frac{10}{2} + \frac{10}{2} (2.1)(350 \times 10^{-6}) = \boxed{5.003675V}$$

$$V_B = \frac{V_s}{(R-\Delta R) + (R+\Delta R)} (R-\Delta R) = \frac{V_s}{2} - \frac{V_s}{2} GE$$

$$= \frac{10}{2} - \frac{10}{2} (2.1)(350 \times 10^{-6}) = \boxed{4.996325V}$$

②

$$\Delta V = V_A - V_B = 5.003675 - 4.996325 = \boxed{.00735V}$$

+5

$$V_{Meas} = A_d \Delta V = 600 \times .00735V = \boxed{4.41V}$$

③

+5

$$V_{Meas} = A_d V_s GE \rightarrow \epsilon = \frac{V_{Meas}}{A_d V_s G} = \frac{-2V}{600(10V)(2.1)}$$


$$= -1.587 \times 10^{-4}$$

$$= -158.7 \times 10^{-6}$$

$$= \boxed{-158.7 \mu\text{strain}}$$


④ Half-bridge

+3

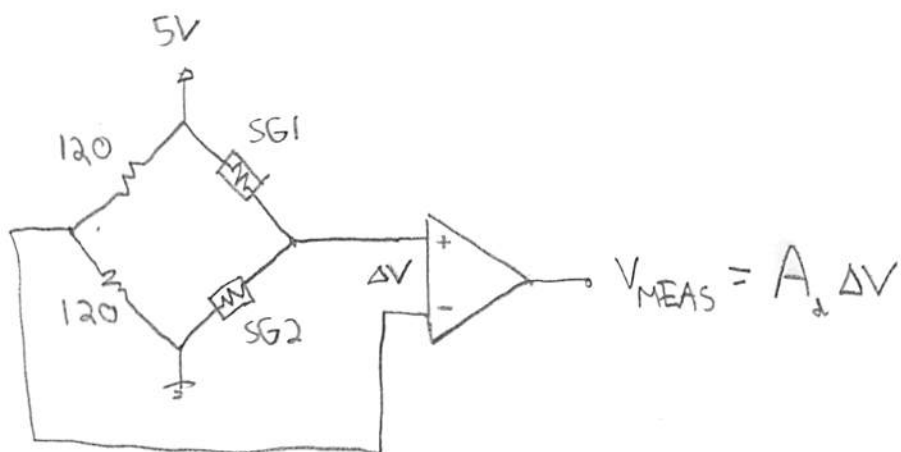

⑤

+10

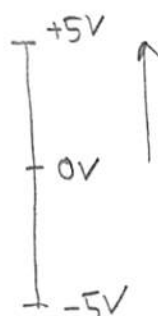

Max (+) signal $\leftarrow$ want $V_{MEAS} = A_d \Delta V_{MAX} < 5V$

For $\frac{1}{2}$ bridge!

$$\begin{aligned} \Delta V_{MAX} &= \frac{V_s}{2} \left(\frac{\Delta R}{R} \right)_{max} = \frac{V_s}{2} G \epsilon_{MAX} \\ &= \frac{5V}{2} (2.1) (600 \times 10^{-6}) \\ &= 3.15 \times 10^{-3} V \end{aligned}$$

$$\text{So, } A_d < \frac{5V}{3.15 \times 10^{-3} V} = 1587.3$$

$\rightarrow$ choose $A_d = 1000$

⑥ Want $\Delta V_{ADC} < \frac{1}{2} V_{n,rms} \Rightarrow \frac{10V}{2^n - 1} < \frac{1}{2} (1.002V) \Rightarrow 2^n > 10001$

+10

Method 1: $2^{10} = 1024 \times$
 $2^{12} = 4096 \times$
 $2^{14} = 16384 \checkmark$

Method 2: $\log(2^n) > \log(10001)$

$$n > \frac{\log(10001)}{\log(2)} = 13.3$$

Choose

$n = 14$

Choose $n = 14$

(7)

$$\Delta \varepsilon_{\min} = \frac{\Delta V_{\min}}{\frac{\partial V_{\text{MEAS}}}{\partial \varepsilon}}$$

Since $\Delta V_{\text{ADC}} < V_{\text{N, rms}}$,

we know that $\Delta V_{\min} = 2 \text{ mV}$

$$V_{\text{MEAS}} = A_s \frac{V_s}{2} G \varepsilon \quad \left[\text{For } \frac{1}{2} \text{ bridge?} \right]$$

$$\frac{\partial V_{\text{MEAS}}}{\partial \varepsilon} = A_s \frac{V_s}{2} G$$

$$\Rightarrow \Delta \varepsilon_{\min} = \frac{0.002 \text{ V}}{1000 \times \frac{5 \text{ V}}{2} \times 2.1} = 3.81 \times 10^{-7} = 0.381 \times 10^{-6} = 0.38 \text{ microstrain}$$

(8)

Full Bridge:

+12

$$V_A = i \times (R + \Delta R)$$


$$= \frac{V_s}{R - \Delta R + R + \Delta R} (R + \Delta R)$$

$$= \frac{V_s}{2R} (R + \Delta R) = \frac{V_s}{2} + V_s \frac{\Delta R}{2R}$$

$$V_B = i' \times (R - \Delta R)$$

$$= \frac{V_s}{R + \Delta R + R - \Delta R} (R - \Delta R)$$
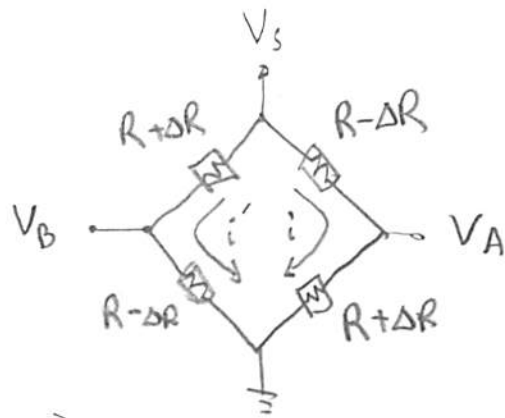
$$= \frac{V_s}{2R} (R - \Delta R) = \frac{V_s}{2} - V_s \frac{\Delta R}{2R}$$



$$\Delta V = V_A - V_B$$

$$= \frac{V_s}{2} + V_s \frac{\Delta R}{2R} - \left(\frac{V_s}{2} - V_s \frac{\Delta R}{2R} \right)$$

$$\Delta V = V_s \frac{\Delta R}{R}$$

Half-Bridge

$$V_A = i(R + \Delta R)$$


$$= \frac{V_s}{R - \Delta R + R + \Delta R} (R + \Delta R)$$

$$= \frac{V_s}{2} + V_s \frac{\Delta R}{2R}$$

$$V_B = i' R = \frac{V_s}{2R} R = \frac{V_s}{2}$$

$$\Delta V = V_A - V_B$$
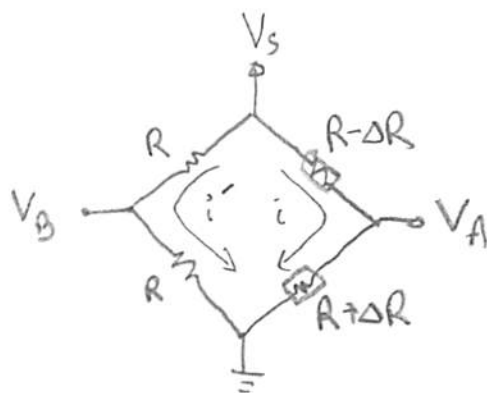
$$= \left(\frac{V_s}{2} + \frac{V_s \Delta R}{2R} \right) - \frac{V_s}{2} = \boxed{V_s \frac{\Delta R}{2R}}$$



Quarter Bridge

$$V_A = i R$$


$$= \frac{V_s}{R - \Delta R + R} \cdot R$$

$$= \frac{V_s}{2R(1 - \frac{\Delta R}{2R})} \cdot R = \frac{V_s}{2} \frac{1}{1 - \frac{\Delta R}{2R}}$$

$$\approx \frac{V_s}{2} \left(1 + \frac{\Delta R}{2R} \right) = \frac{V_s}{2} + V_s \frac{\Delta R}{4R}$$


$$V_B = i' R = \frac{V_s}{2R} R = \frac{V_s}{2} \Rightarrow \Delta V = V_A - V_B = \left(\frac{V_s}{2} + V_s \frac{\Delta R}{4R} \right) - \frac{V_s}{2}$$

$$= \boxed{V_s \frac{\Delta R}{4R}}$$

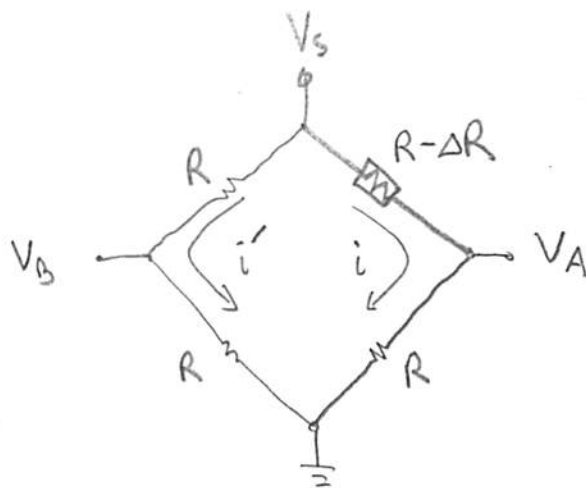

★ NOTE: The approximation $\frac{1}{1+x} \sim 1-x$ (for $x \ll 1$) is very useful! It is simply a 1st order Taylor Series expansion of $\frac{1}{1+x}$ about $x=0$.

ADC:

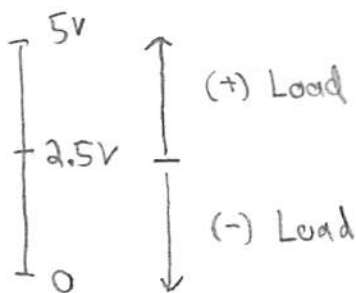

want

$$V_{MEAS} = 2.5 + A_d \Delta V < 5V$$

$$\Delta V_{MAX} = \frac{1.5 \text{ mV}}{V} \times 5V \times \frac{3 \text{ kN}}{5 \text{ kN}} = 4.5 \text{ mV}$$

$$\text{SO, } 2.5 + A_d \times 0.0045V < 5V$$

$$A_d < \frac{5 - 2.5V}{0.0045V} = 555.6 \rightarrow \boxed{\text{Choose } A_d = 500}$$

$$\Delta L_{MIN} = \frac{\frac{\Delta V_{MIN}}{\partial V_{MEAS}}}{\frac{\partial L}{\partial V_{MEAS}}}$$

• ΔV_{MIN} is larger of ΔV_{AOC} and $V_{n,rms}$


$$\frac{5V}{2^{12} - 1} = 1.22 \text{ mV}$$

This is ΔV_{MIN}

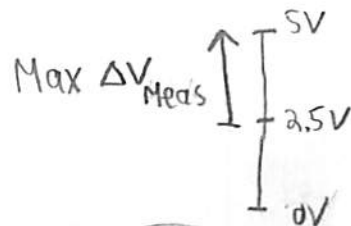0.5 mV

$$\begin{aligned} \frac{\partial V_{MEAS}}{\partial L} &= A_d R O V_s \frac{1}{L_{rated}} \\ &= 500 \left(1.5 \frac{\text{mV}}{V} \right) (5V) \frac{1}{5000N} \\ &= 0.75 \frac{\text{mV}}{N} \end{aligned}$$

$$\Rightarrow \Delta L_{MIN} = \frac{1.22 \text{ mV}}{0.75 \text{ mV/N}} = \boxed{1.63 N}$$



$$\textcircled{11} \text{ DR} = 20 \log_{10} \frac{\text{Max } \Delta V_{Meas}}{\Delta V_{MIN}} = 20 \log_{10} \frac{2.5V}{0.00122V} = \boxed{66.2 \text{ dB}} \textcircled{+5}$$

...
 (12) Design requirements are Max Load = 1 kg
 (15) Sensitivity = 1 g] Must make sure BOTH are satisfied!

• Many ways to solve this problem. One reasonable way is to compute the max V_{MEAS} (corresponding to $L = 1\text{ kg}$) and ΔL_{MIN} for all 4 combinations.

Want $\overset{\text{Max}}{V_{MEAS}} = 5 + A_s R_O V_s \frac{1\text{ kg}}{L_{rated}} < 10\text{ V}$ ↙ Limited by ADC for this problem

Want $\Delta L_{MIN} = \frac{\Delta V_{MIN}}{\frac{\partial V_{MEAS}}{\partial L}} = \frac{\Delta V_{MIN}}{A_s R_O V_s} L_{rated} < 1\text{ g}$ ↑

$$\Delta V_{ADC} = \frac{10\text{ V}}{2^{14} - 1} = .6\text{ mV}$$

OK if ΔL_{MIN} is smaller than desired

• LC #1
Amp #1

$$\overset{\text{Max}}{V_{MEAS}} = 5 + 200 (.008) 10 \frac{1\text{ kg}}{10\text{ kg}} = 6.6\text{ V} \checkmark$$

$$\left. \begin{array}{l} V_n = 2\text{ mV} \leftarrow \Delta V_{MIN} \\ \Delta V_{ADC} = .6\text{ mV} \end{array} \right\} \Delta L_{MIN} = \frac{2\text{ mV}}{200 \left(\frac{.6\text{ mV}}{\text{V}} \right) 10\text{ V}} \times 10^4 \text{ g} = 1.25\text{ g X (too big)}$$

• LC #1
Amp #2

$$\overset{\text{Max}}{V_{MEAS}} = 5 + 500 (.008 \frac{\text{V}}{\text{V}}) 10\text{ V} \frac{1\text{ kg}}{10\text{ kg}} = 9\text{ V} \checkmark$$

$$\left. \begin{array}{l} V_n = 5\text{ mV} \leftarrow \Delta V_{MIN} \\ \Delta V_{ADC} = .6\text{ mV} \end{array} \right\} \Delta L_{MIN} = \frac{5\text{ mV}}{500 \left(\frac{.6\text{ mV}}{\text{V}} \right) 10\text{ V}} \times 10^4 \text{ g} = 1.25\text{ g X}$$

• LC #2
Amp #1

$$\text{Max } V_{\text{MEAS}} = 5 + 200 \left(.0025 \frac{\text{V}}{\text{V}} \right) 10\text{V} \frac{1\text{kg}}{2\text{kg}} = 7.5\text{V} \checkmark$$

$$\Delta L_{\text{MIN}} = \frac{2\text{mV}}{200 \left(2.5 \frac{\text{mV}}{\text{V}} \right) 10\text{V}} \times 2000\text{g} = 0.8\text{g} \checkmark$$

• LC #2
Amp #2

$$\text{Max } V_{\text{MEAS}} = 5 + 500 \left(.0025 \frac{\text{V}}{\text{V}} \right) 10\text{V} \frac{1\text{kg}}{2\text{kg}} = 11.25\text{V} \times \left(\begin{smallmatrix} \text{too} \\ \text{big} \end{smallmatrix} \right)$$

$$\Delta L_{\text{MIN}} = \frac{5\text{mV}}{500 \left(2.5 \frac{\text{mV}}{\text{V}} \right) 10\text{V}} 2000\text{g} = 0.8\text{g} \checkmark$$

WINNER is LC #2, Amp #1 

NOTE: Another approach to this problem is to compute L_{max} and ΔL_{MIN} for each combo.

$$\text{Max } V_{\text{MEAS}} = 10\text{V} = 5 + A_d R_O V_s \frac{L_{\text{MAX}}}{L_{\text{rated}}}$$

$$\Rightarrow \text{we want } L_{\text{MAX}} = \frac{5\text{V}}{A_d R_O V_s} L_{\text{rated}} \geq 1\text{kg} \nabla$$

$$\text{we also want } \Delta L_{\text{MIN}} = \frac{\Delta V_{\text{MIN}}}{A_d R_O V_s} L_{\text{rated}} \leq 1\text{g} \nabla$$

• LC1
Amp1

$$\frac{L_{\max}}{200(.008)(10)} = 3.13 \text{ kg} \checkmark$$

$$\frac{\Delta L_{\min}}{200(.008)10} \times 10^4 = 1.25 \text{ g} \times$$

• LC1
Amp2

$$\frac{5}{500(.008)10} 10 \text{ kg} = 1.25 \text{ kg} \checkmark$$

$$\frac{.005}{500(.008)10} \times 10^4 = 1.25 \text{ g} \times$$

• LC2
Amp1

$$\frac{5}{200(.0025)10} 2 \text{ kg} = 2.0 \text{ kg} \checkmark$$

$$\frac{.002}{200(.0025)10} \times 2000 \text{ g} = 0.8 \text{ g} \checkmark$$

• LC2
Amp2

$$\frac{5}{500(.0025)10} 2 \text{ kg} = 0.8 \text{ kg} \times$$

$$\frac{.002}{500(.0025)10} \times 2000 \text{ g} = 0.8 \text{ g} \checkmark$$

WINNER is LC2, Amp1

