


1) $V_A = 5 \frac{10K}{10K + R_T}$

(+8)

$V_B = 5 \frac{10K}{10K + 5.6K}$


$\Delta V = 5 \left(\frac{10K}{10K + R_T} - \frac{10K}{15.6K} \right)$

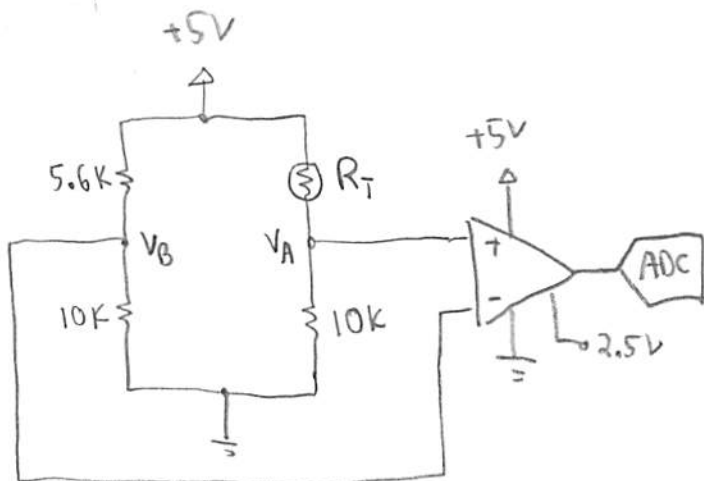$= 5 \left(\frac{10K}{10K + R_T} - 0.641 \right) \rightarrow V_{MEAS} = 2.5 + A_d \cdot 5 \left(\frac{10K}{10K + R_T} - 0.641 \right)$



2) What limits V_{MEAS} ?

(+10)

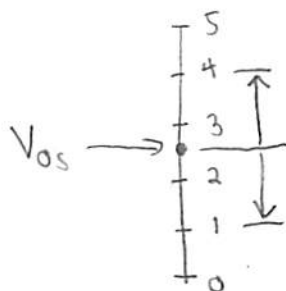

	Amplifier	ADC
Max	4V	5V
Min	1V	0V

Choose $A_d = 3$

• Want Max $V_{MEAS} < 4V$

$\Rightarrow 2.5 + A_d \cdot 5 \left(\frac{10K}{10K + 3.6K} - 0.641 \right) < 4V$
0.469

$\Rightarrow A_d < 3.2$

Limiting factor
(smaller value)

• Want Min $V_{MEAS} > 1V$

$\Rightarrow 2.5 + A_d \cdot 5 \left(\frac{10K}{10K + 8.6K} - 0.641 \right) > 1V$
-0.436

$\Rightarrow A_d < 3.44$

$T_{MAX} = 50^\circ C$

$T_{MIN} = 30^\circ C$

$$3) \Delta T_{MIN} = \frac{\Delta V_{MIN}}{\frac{\partial V_{MEAS}}{\partial T}} \quad V_N = 4 \text{ mV}$$

This is ΔV_{MIN} ²

(+10)

$$\Delta V_{ADC} = \frac{5V}{2^8 - 1} = 0.0196V = 19.6 \text{ mV}$$

$$V_{MEAS} = 2.5 + A \cdot 5 \left(\frac{10K}{10K + R_T} - 0.641 \right)$$

$$\frac{\partial V_{MEAS}}{\partial R_T} = -A \cdot 5 \frac{10K}{(10K + R_T)^2}$$

$$\text{So, } \frac{\partial V_{MEAS}}{\partial T} = \frac{\partial V_{MEAS}}{\partial R_T} \alpha R_T = -3.5V \frac{10K}{(10K + 3.61K)^2} \left(-0.038 \frac{1}{^\circ C} \right) (3.61K)$$

$$= +0.111 \text{ V}/^\circ C$$

$$\rightarrow \Delta T_{MIN} = \frac{0.0196V}{0.111 \text{ V}/^\circ C} = \boxed{0.18^\circ C}$$


$$4) \Delta V_{ADC} = \frac{5V}{2^{12} - 1} = 1.22 \text{ mV} < V_N = 4 \text{ mV} \quad \Delta V_{MIN}$$

(+6)

$$\text{So, } \Delta T_{MIN} = \frac{0.004V}{0.111 \text{ V}/^\circ C} = \boxed{0.036^\circ C}$$

$$5) \text{ At } T = 30^\circ C, R_T = 8.06 \text{ k}\Omega$$
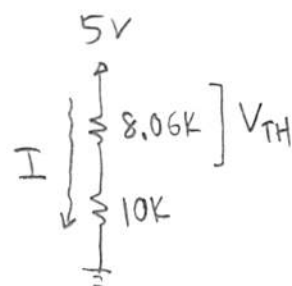
$$(18) P = I V_{TH} = I^2 (8.06K) = \left(\frac{5V}{18.06K} \right)^2 (8.06K)$$



$$\delta T = \frac{0.618 \text{ mW}}{7 \text{ mW}/^\circ C} = \boxed{0.088^\circ C} = \underline{\underline{0.618 \text{ mW}}}$$

$$30^\circ C \Rightarrow \frac{\partial V_{MEAS}}{\partial T} = -3.5V \cdot \frac{10K}{(10K + 8.06K)^2} (-0.0425 \text{ V}/^\circ C) (8.06K) = 0.158 \text{ V}/^\circ C$$

$$8\text{-bit ADC} \rightarrow \Delta T_{MIN} = \frac{0.0196V}{0.158 \text{ V}/^\circ C} = \boxed{0.124^\circ C}$$


$\delta T_{self} < \Delta T_{MIN} \checkmark$
YES, we can ignore self heating.

6) (+10)

$$\Delta V = V_A - V_B$$

$$= 5 \frac{R}{R+R_T} - 5 \frac{R}{R+10K}$$
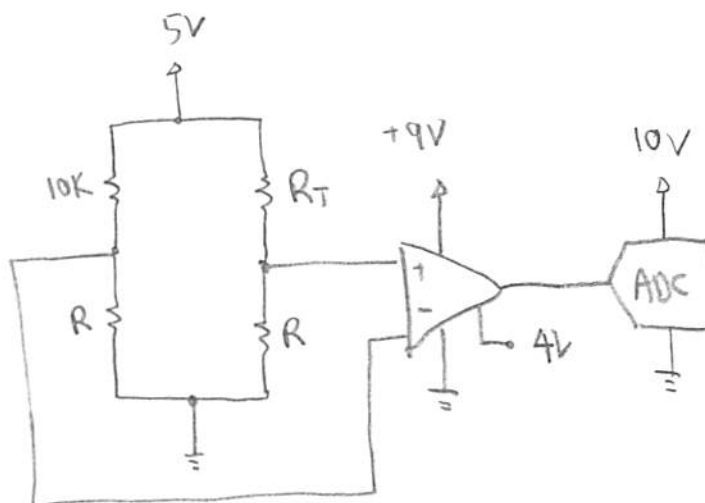
$$= 5 \left(\frac{R}{R+R_T} - \frac{R}{R+10K} \right)$$



$$V_{MEAS} = 4 + A_d \Delta V = 4 + 2.5 \times \left(\frac{R}{R+R_T} - \frac{R}{R+10K} \right)$$

• When \$T \uparrow\$, then \$R_T \downarrow\$, so \$V_{MEAS} \uparrow\$

At \$T=100^\circ\text{C}\$, \$V_{MEAS} < 8V\$ (limited by amplifier)

$$\text{Max } V_{MEAS} = 4 + 10 \left(\frac{R}{R+0.677K} - \frac{R}{R+10K} \right) < 8V$$

\$R=10K\$:

$$\text{Max } V_{MEAS} = 4 + 10 \left(\frac{10K}{10.677K} - \frac{10K}{20K} \right) = 8.37V \times (T_{\text{high}})$$

\$R=20K\$:

$$\text{Max } V_{MEAS} = 4 + 10 \left(\frac{20K}{20.677K} - \frac{20K}{30K} \right) = 7V \quad \checkmark$$

• When \$T \downarrow\$, then \$R_T \uparrow\$, so \$V_{MEAS} \downarrow\$

At \$T=0^\circ\text{C}\$, \$V_{MEAS} > 1V\$ (limited by amplifier)

$$\text{Min } V_{MEAS} = 4 + 10 \left(\frac{R}{R+32.554K} - \frac{R}{R+10K} \right)$$

$$R=10k: 4 + 10 \left(\frac{10k}{42.554k} - \frac{10k}{20k} \right) = 1.35V \checkmark$$

$$R=20k: 4 + 10 \left(\frac{20k}{52.554k} - \frac{20k}{30k} \right) = 1.14V \checkmark$$

$$\Rightarrow \text{choose } \boxed{R=20k}$$

$$\Delta V_{MIN} \rightarrow V_N = 10mV$$

$$\Delta V_{ADC} = \frac{10V}{2^{12}-1} = 2.44mV$$

$$7) \quad \Delta T_{MIN} = \frac{\Delta V_{MIN}}{\frac{\partial V_{MEAS}}{\partial T}} = \frac{V_{N,rms}}{\frac{\partial V_{MEAS}}{\partial R_T} \propto R_T}$$

(+10)

$$V_{MEAS} = 4 + 10 \left(\frac{20k}{20k + R_T} - \frac{2}{3} \right)$$

$$\frac{\partial V_{MEAS}}{\partial R_T} = -10 \frac{20k}{(20k + R_T)^2}$$

$$\begin{aligned} 0^\circ C \quad \Rightarrow \quad \frac{\partial V_{MEAS}}{\partial T} &= -10V \frac{20k}{(20k + 32.554k)^2} (-0.0509/^\circ C)(32.554k) \\ &= 0.12 V/^\circ C \end{aligned}$$

$$\Rightarrow \Delta T_{MIN} = \frac{0.010V}{0.12 V/^\circ C} = \boxed{0.083^\circ C}$$


$$\begin{aligned} 100^\circ C \quad \Rightarrow \quad \frac{\partial V_{MEAS}}{\partial T} &= -10V \frac{20k}{(20k + 0.677k)^2} (-0.0294/^\circ C)(0.677k) \\ &= 0.0093 V/^\circ C \end{aligned}$$

$$\Rightarrow \Delta T_{MIN} = \frac{0.010V}{0.0093 V/^\circ C} = \boxed{1.08^\circ C}$$

8) $P = I^2 R_T$

+8)
$$= \left(\frac{5V}{32.554k + 20k} \right)^2 (32.554k)$$

$$= 0.295 \text{ mW}$$

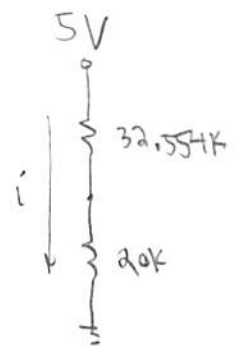

$$\delta T = \frac{.295 \text{ mW}}{5 \text{ mW/}^\circ\text{C}} = \underline{0.059^\circ\text{C}} < .083^\circ\text{C} \quad \checkmark$$

YES, we can ignore self-heating!

9)
$$\underbrace{\text{Compensating voltage}}_{V_{CTC}} = \Delta S \times T_o = (51 \mu\text{V/}^\circ\text{C})(30^\circ\text{C}) = 1530 \mu\text{V}$$

$$= \boxed{1.53 \text{ mV}}$$

10)
$$V_{MEAS} = G \times \left(\underbrace{V_{CTC}}_{\substack{\uparrow \\ \Delta S \times (T_{obj} - T_o)}} + \Delta S \times T_o \right) = G \times \underbrace{\Delta S \times T_{obj}}_{10 \text{ mV/}^\circ\text{C}}$$

+8)
$$\text{Want } G = \frac{10 \text{ mV/}^\circ\text{C}}{.051 \text{ mV/}^\circ\text{C}} = \boxed{196.1}$$

11)
$$G = 1 + \frac{R}{1k} = 196.1 \quad (\text{closest } 1\% \text{ value})$$

+8)
$$R = 195.1k \Rightarrow \text{Choose } \boxed{R = 196k}$$

Actual gain = $1 + \frac{196k}{1k} = \boxed{197}$

NOTE: OK to choose $R = 191k$
 $\Rightarrow G = 192$

NOTE: This is not max gain. The problem only asked for a gain that produces 10 mV/°C

(12)

$$V_{MEAS} = G \Delta S T_{obj}$$

+8

If max $V_{MEAS} = 5V$, what is corresponding T_{obj} ?

$$\text{Max } T_{obj} = \frac{5V}{197 \times (51 \times 10^{-6} V/^{\circ}C)} = \boxed{497.7^{\circ}C}$$

NOTE: If $G = 192$, then $T_{MAX} = 510.6^{\circ}C$

$$\begin{aligned} \Delta T_{MIN} &= \frac{\Delta V_{MIN}}{\frac{\partial V_{MEAS}}{\partial T}} = \frac{\Delta V_{AOC}}{A \Delta S} \leftarrow \begin{array}{l} V_N = 3 \text{ mV} \\ \Delta V_{AOC} = \frac{10V}{2^{10}-1} = \underline{\underline{9.8 \text{ mV}}} \\ \text{(bigger)} \end{array} \\ &= \frac{0.0098V}{197 \times 51 \times 10^{-6} V/^{\circ}C} = \boxed{0.98^{\circ}C} \end{aligned}$$

NOTE: If $G = 192$, then $\Delta T_{MIN} = 1.00^{\circ}C$