

## PreLab 2 – Thermistor Measurement System (9 problems for 30 pts)

### INTRODUCTION

In this lab, you will develop a temperature measurement system. A system block diagram is shown in Fig. 1. Here's how it works:

- 1) The thermistor (in a quarter bridge) converts temperature to a voltage signal.
- 2) The instrumentation amplifier increases the signal amplitude.
- 3) The amplifier output is recorded by the Arduino and sent to a computer.
- 4) The computer processes the data (using MATLAB) to produce a plot of temperature versus time.

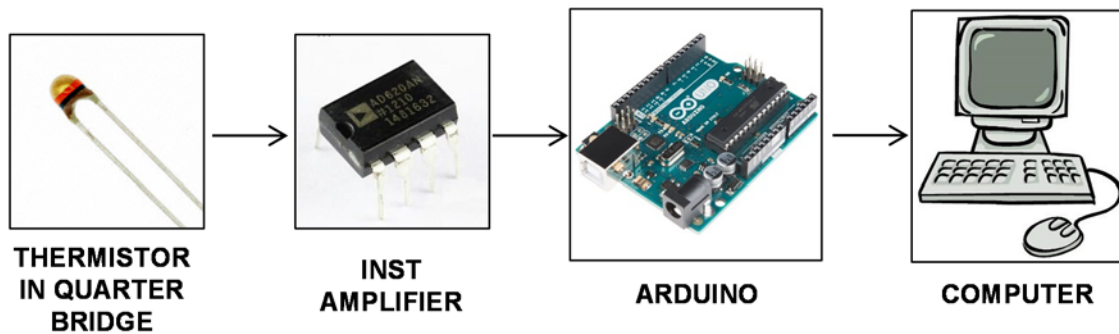


Fig. 1: Overall temperature measurement system.

### PART 1: SYSTEM DESIGN

In Lab2, we want to build a temperature measurement system that operates between  $T = 10\text{ }^{\circ}\text{C}$  and  $+35\text{ }^{\circ}\text{C}$ . Consider the signal conditioning electronics shown in Fig. 2. The bridge consists of a 10 kohm thermistor and three 10.0 kohm resistors (1% tolerance). The quarter bridge and amplifier are powered by +5 V and GND. The AD620 has a reference  $V_{\text{REF}} \approx 2.5\text{V}$  provided by the voltage divider at pin 5.

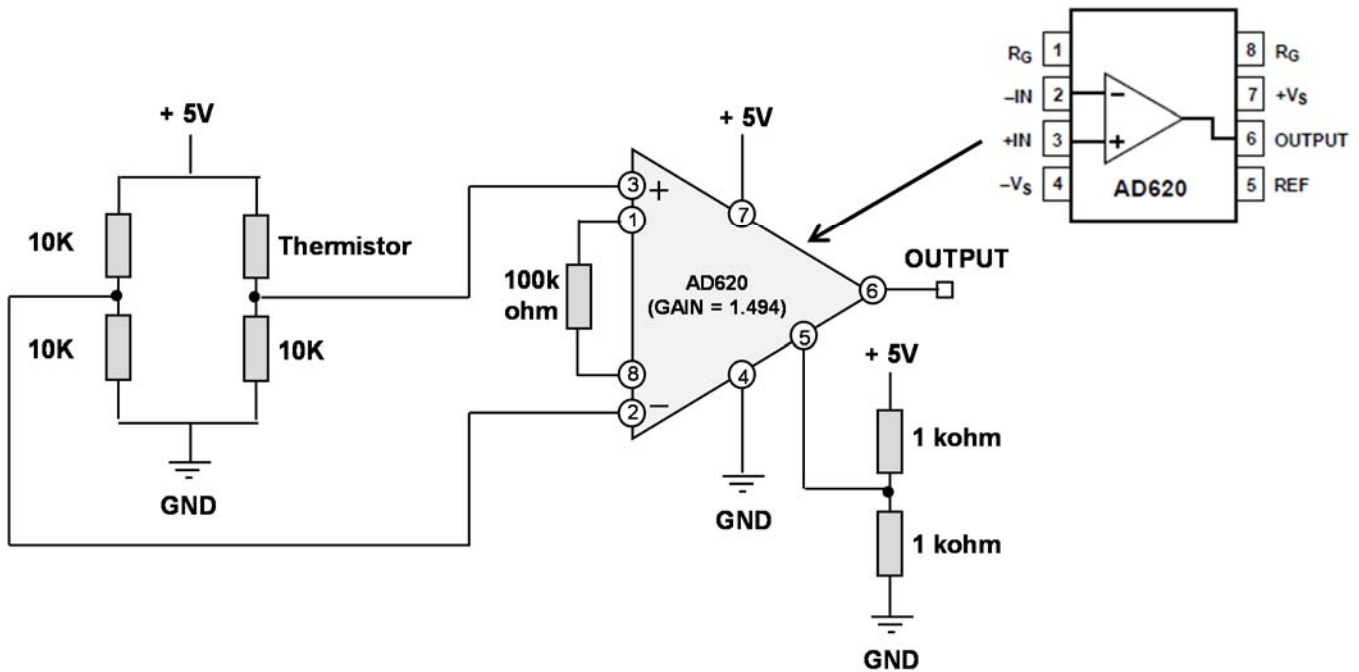


Fig. 2: Signal conditioning electronics for the thermistor.  $V_{ref} = 2.5V$  is applied to pin 5 of the AD620 chip.

- **PROBLEM 1:** Show that the resistor bridge voltage is given by:

$$\Delta V = \left( \frac{10k\Omega}{10k\Omega + R_T} - 0.5 \right) \times V_S \quad \text{Eq.(1)}$$

where  $R_T$  is the thermistor resistance and  $V_S$  is the power supply.

- **PROBLEM 2:** The thermistor datasheet has a table of thermistor resistance values versus temperature. The table has values for a variety of thermistors. We are using a 10 kohm thermistor, which means the resistance is 10 kohm at  $T = 25^\circ\text{C}$ . What is the thermistor resistance  $R_{T,HOT}$  at  $T_{HOT} = 35^\circ\text{C}$ ? What is the thermistor resistance  $R_{T,COLD}$  and  $T_{COLD} = 10^\circ\text{C}$ ? Express your answer in kohms.
- **PROBLEM 3:** Based on your answers to Problem 1 and 2, show that  $\Delta V_{HOT} = 0.524V$  and  $\Delta V_{COLD} = -0.826V$ .

How to choose the amplifier gain  $A_d$ ?

- We always want our measured voltage  $V_{MEAS}$  to be within the allowable measurement range. In other words, we must make sure that  $V_{MEAS,MIN} < V_{MEAS} < V_{MEAS,MAX}$ .

- Depending on the system,  $V_{MEAS,MIN}$  and  $V_{MEAS,MAX}$  are determined by either the amplifier or the ADC. We already know the Arduino can measure from 0 to 5V. What limitations are imposed by the amplifier?
- Most instrumentation amplifiers have a limited output voltage range. If an amplifier is powered by  $+V_S$  and GND, the highest output is typically  $V_S - 1$  while the lowest output is typically  $+1V$ . For example, an amplifier powered by  $+9V$  and GND has a maximum output of 8V and a minimum output of 1V. **For this lab, the amplifier is powered by  $+5V$  and GND.**
- **PROBLEM 4:** Keeping in mind that  $V_{MEAS} = V_{REF} + A_d \Delta V$ , determine the maximum allowable amplifier gain such that  $V_{MEAS} < V_{MEAS,MAX}$  at  $T_{MAX} = 35^\circ C$ . Do a similar calculation for  $T_{MIN} = 10^\circ C$ , except you now want  $V_{MEAS} > V_{MEAS,MIN}$ . The SMALLER gain value is the correct choice for the maximum usable amplifier gain for the entire temperature range.
- **PROBLEM 5:** You must choose between  $A_d = 1, 1.5, 2.5$ , and 3. Choose one, compute the closest 5% resistor value, and then compute the actual gain based on your choice of resistor.

Hint #1: Remember that the AD620 gain is determined by:  $A_d = 1 + \frac{49400}{R_G}$

Hint #2: You should get 100 kohm.

OK, now we need to convert the measured voltage to a temperature value! This is actually a two step process. First, we convert the measured voltage  $V_{MEAS}$  to the thermistor resistance  $R_T$ . Second, use the Steinhart-Hart equation to convert  $R_T$  into a temperature.

- **PROBLEM 6:** Derive the following expression that converts  $V_{MEAS}$  into  $R_T$ :

$$R_T = (10 \text{ kohm})(0.5 - \beta)/(0.5 + \beta) \quad \text{where} \quad \beta = (V_{MEAS} - V_{REF})/(A_d V_S) \quad \text{Eq. (2)}$$

- **PROBLEM 7:** Suppose the instrumentation amplifier has a gain of  $A_d = 1.5$ , and that your measured voltage is  $V_{MEAS} = 1.5V$ . Use the Extended Steinhart-Hart Equation to determine the thermistor temperature in  $^\circ C$ . The extended Steinhart-Hart equation is given below (T is in Kelvin):

$$T = \frac{1}{A + B \ln\left(\frac{R_T}{R_{25}}\right) + C \left(\ln\left(\frac{R_T}{R_{25}}\right)\right)^2 + D \left(\ln\left(\frac{R_T}{R_{25}}\right)\right)^3} \quad \text{Eq. (3)}$$

where  $A = 3.354016 \text{ E-3}$ ,  $B = 2.569850 \text{ E-4}$ ,  $C = 2.620131 \text{ E-6}$ , and  $D = 6.383091 \text{ E-8}$ . You will need to convert your answer from the above equation (in Kelvin) to  $^\circ C$ . You will use Eq. (2) and Eq. (3) in your MATLAB program.

Hint: Your final answer should be close to 13°C.

## PART 2: OTHER SYSTEM SPECIFICATIONS

- **PROBLEM 8:** Suppose your measurement system has a noise voltage of 2 mV<sub>RMS</sub>. The Arduino ADC has 10 bits from 0 to 5V. What is the temperature sensitivity at  $T = 10^{\circ}\text{C}$ ? Consult the thermistor data sheet to find the tempco value, which is listed as “TCR” in the table. Hint:  $\Delta T_{\text{MIN}}$  should be around 0.06 °C.
- **PROBLEM 9:** Assuming the thermistor is left in the open air at  $T = 25^{\circ}\text{C}$ , the thermistor temperature should also be  $T = 25^{\circ}\text{C}$ . Let the 10k thermistor have a dissipation factor of 7 mW/°C. Let us adopt the criterion that self-heating can be ignored if it produces a temperature rise less than the sensitivity  $\Delta T_{\text{MIN}}$  of your measurement system at  $T = 25^{\circ}\text{C}$ . Can we ignore self-heating? Show all work! Hint:  $\Delta T_{\text{SELF}}$  should be around 0.09 °C.

NOTE: You will find that  $\Delta T_{\text{SELF}}$  is only slightly higher than  $\Delta T_{\text{MIN}}$ . Technically, this means we cannot ignore self-heating. Realistically, it is OK to ignore self-heating if the desired temperature sensitivity is much bigger (e.g. desired  $\Delta T_{\text{MIN}} = 0.5^{\circ}\text{C}$ ) than the actual  $\Delta T_{\text{MIN}}$  of your system.

(End of PreLab2)