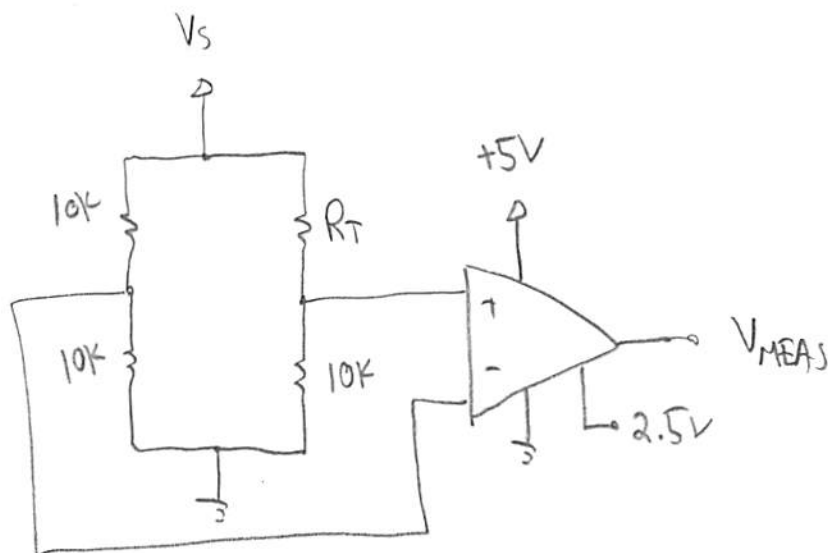


$$1) \Delta V = V_s \frac{10k}{10k + R_T} - V_s \frac{10k}{10k + 10k}$$

$$\Delta V = V_s \left(\frac{10k}{10k + R_T} - 0.5 \right)$$



2) According to data sheet:

$$R_T = 19.872k @ 10^\circ C$$

$$6.535k @ 35^\circ C$$

$$3) \Delta V = 5 \left(\frac{10k}{10k + 19.872k} - 0.5 \right) = \boxed{-0.826V} @ T = 10^\circ C$$

$$\Delta V = 5 \left(\frac{10k}{10k + 6.535k} - 0.5 \right) = \boxed{0.524V} @ T = 35^\circ C$$

$$4) V_{MEAS} = 2.5 + A_d \Delta V$$

$$\text{At } T = 35^\circ C: V_{MEAS} < 4V$$

$$2.5 + A_d (0.524V) < 4V$$

$$A_d < \underline{\underline{2.86}}$$

↙ Limited by amplifier!

At $T=10^{\circ}\text{C}$: $V_{\text{MEAS}} > 1\text{V}$ ← limited by amplifier?

$$2.5 + A_d (-0.826) > 1\text{V}$$

$$1.5\text{V} > A_d (0.826)$$

$$A_d < \underline{1.82}$$

$$\Rightarrow \text{Max allowable } A_d = 1.82$$

Satisfies both

$$A_d < 2.86$$

AND

$$A_d < 1.82$$

5) Closest available gain = 1.5

$$1.5 = 1 + \frac{49400}{R_g} \Rightarrow R_g = 98.8\text{K}$$

$$\Rightarrow \text{Closest } 5\% \text{ value} = \boxed{100\text{K}}$$

$$\text{Actual gain} = 1 + \frac{49400}{100000} = \boxed{1.494}$$

6) $V_{\text{MEAS}} = V_{\text{REF}} + A_d \Delta V = V_{\text{REF}} + A_d \times V_s \left(\frac{10\text{K}}{10\text{K} + R_T} - 0.5 \right)$

$$\frac{V_{\text{MEAS}} - V_{\text{REF}}}{A_d V_s} = \beta = \frac{10\text{K}}{10\text{K} + R_T} - 0.5$$

$$10\text{K} + R_T = \frac{10\text{K}}{\beta + 0.5}$$

$$R_T = 10\text{K} \left(\frac{1}{\beta + 0.5} - 1 \right) = 10\text{K} \left(\frac{1}{\beta + 0.5} - \frac{\beta + 0.5}{\beta + 0.5} \right)$$

$$\boxed{R_T = 10\text{K} \left(\frac{0.5 - \beta}{0.5 + \beta} \right)} \leftarrow \beta = \frac{V_{\text{MEAS}} - V_{\text{REF}}}{A_d V_s}$$

$$7) \quad V_{MEAS} = 1.5V$$

$$\rightarrow \beta = \frac{1.5 - 2.5}{(1.494)(5)} = -0.134$$

$$R_T = 10k \left(\frac{0.5 - (-0.134)}{0.5 + (-0.134)} \right) = 17.322k$$

$$T = \frac{1}{A + B \ln\left(\frac{17.322k}{10k}\right) + C \left[\ln\left(\frac{17.322k}{10k}\right) \right]^2 + D \left[\ln\left(\frac{17.322k}{10k}\right) \right]^3} - 273.15$$

$$= \boxed{12.95^\circ C}$$

$$8) \quad \Delta V_{ADC} = \frac{5V}{2^{10} - 1} = 4.9mV > \overbrace{2mV_{RMS}}^{\text{noise}}$$

$$\text{Therefore, } \Delta T_{MIN} = \frac{\Delta V_{ADC}}{\frac{\partial V_{MEAS}}{\partial T}}$$


$$V_{MEAS} = V_{REF} + A_d V_s \left(\frac{10k}{10k + R_T} - 0.5 \right)$$

$$\frac{\partial V_{MEAS}}{\partial T} = -A_d V_s \frac{10k}{(10k + R_T)^2} \propto R_T = -1.494 \times 5 \frac{10k}{(10k + 19.872k)^2}$$

$\nearrow$
 $(-0.0479\%)(19.872k)$

$$= -0.080\% / ^\circ C$$
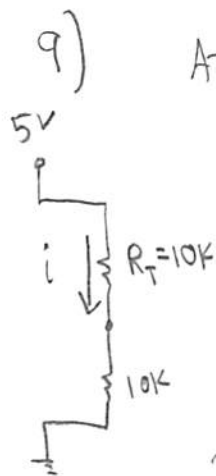
$$\Rightarrow \Delta T_{MIN} = \frac{0.0049V}{0.080V/^\circ C} = \boxed{0.06^\circ C}$$



At $T = 25^\circ\text{C}$:

$$P = \left(\frac{5V}{20K}\right)^2 10K = 0.625\text{mW}$$

or can use $P = IV = \left(\frac{5V}{20K}\right) \times \left(\frac{5V}{20K} \cdot 10K\right) = 0.625\text{mW}$

$$\Delta T_{\text{SELF}} = \frac{0.625\text{mW}}{7\text{mW}/^\circ\text{C}} = 0.09^\circ\text{C}$$

$$\frac{\partial V_{\text{MEAS}}}{\partial T} = -1.494 \times 5 \times \frac{10K}{(10K + 10K)^2} (-0.0438\%/^\circ\text{C})(10K) = 0.082\%/^\circ\text{C}$$

$$\Delta T_{\text{MIN}} = \frac{0.0049V}{0.082\%/^\circ\text{C}} = \underline{\underline{0.06^\circ\text{C}}}$$

← Basically the same as value at 10°C

NO, we cannot



but ok if desired

ΔT_{MIN} is much bigger than actual ΔT_{MIN} .