

BME 386
Prelab 3 Solns


Total = 30 pts

①

$\leq 1\text{mV}$

$$\Delta V = (\text{PQRST}) + 0.2\text{V}$$

↑
Max differential
offset

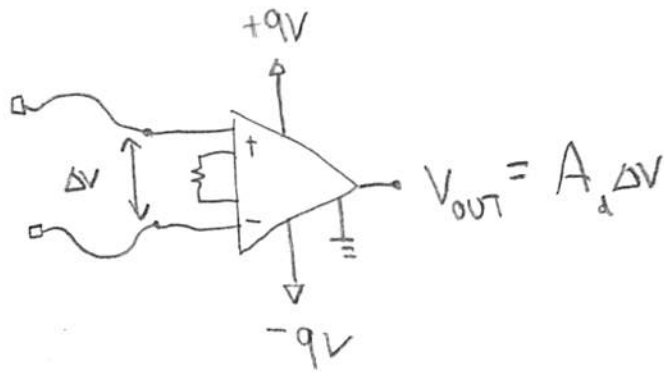

+2

$$\text{Max } \Delta V \sim 0.2\text{V} \rightarrow \text{Max } V_{\text{OUT}} < 8\text{V}$$

$$A_d \times 0.2\text{V} < 8\text{V} \Rightarrow A_d < 40$$



②

+2

$$V_{\text{OUT}} = iR = \frac{V_{\text{IN}}}{Z_c + R} R$$

$$\frac{V_{\text{OUT}}}{V_{\text{IN}}} = \frac{R}{Z_c + R}$$
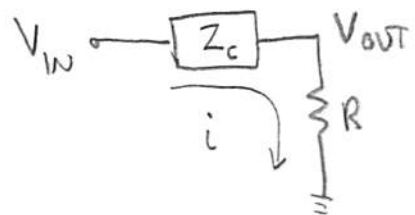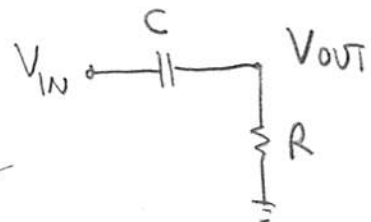
$$= \frac{R}{\frac{1}{j\omega C} + R} = \frac{j\omega RC}{1 + j\omega RC}$$



using $\omega = 2\pi f$

$$\rightarrow \frac{V_{\text{OUT}}}{V_{\text{IN}}} = \frac{j f \cdot 2\pi RC}{1 + j f \cdot 2\pi RC}$$

$$\text{let } f_c = \frac{1}{2\pi RC} \Rightarrow$$

$$\frac{V_{\text{OUT}}}{V_{\text{IN}}} = \frac{j f / f_c}{1 + j f / f_c}$$

$$\text{where } Z_c = \frac{1}{j\omega C}$$

$$\textcircled{3} \quad f_c = \frac{1}{2\pi(10^6\Omega)(0.1\text{nF})} = \boxed{1.6 \text{ Hz}}$$

(+3)

$$\frac{V_{out}}{V_{in}} = \frac{j f/f_c}{1+j f/f_c} \xrightarrow{\text{Let } b = f/f_c} \frac{V_{out}}{V_{in}} = \frac{j b}{1+j b}$$

Many ways to compute $\left| \frac{V_{out}}{V_{in}} \right| \dots$

Method 1 Use $\left| \frac{a+jb}{c+jd} \right| = \frac{\sqrt{a^2+b^2}}{\sqrt{c^2+d^2}} \Rightarrow \left| \frac{V_{out}}{V_{in}} \right| = \frac{b}{\sqrt{1+b^2}} \quad (1)$

When $f=f_c \Rightarrow b=1 \Rightarrow \boxed{\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{2}} = 0.707}$

Method 2 Make denominator real:

$$\frac{V_{out}}{V_{in}} = \frac{j b}{1+j b} \times \frac{1-j b}{1-j b} = \frac{b^2 + j b}{1+b^2} = \frac{b}{1+b^2} (b + j)$$

Then take magnitude:

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{b}{1+b^2} |b+j| = \frac{b}{1+b^2} \sqrt{b^2+1} = \frac{b}{\sqrt{1+b^2}} \leftarrow \text{same as (1)}$$

Method 3 Re-write both numerator and denominator as phasors:

$$\frac{V_{out}}{V_{in}} = \frac{j b}{1+j b} = \frac{b e^{j\pi/2}}{\sqrt{1+b^2} e^{j \tan^{-1}(b)}} = \frac{b}{\sqrt{1+b^2}} e^{j(\pi/2 - \tan^{-1} b)}$$

$$\rightarrow \left| \frac{V_{out}}{V_{in}} \right| = \frac{b}{\sqrt{1+b^2}} \leftarrow \text{same as (1)}$$

④ When $f = f_{\text{stop}}$, $\left| \frac{V_{\text{out}}}{V_{\text{in}}} \right| = 0.1$

+2

Let $b_s = \frac{f_{\text{stop}}}{f_c} \rightarrow \frac{b_s}{\sqrt{1+b_s^2}} = 0.1 = \frac{1}{10}$

$100 b_s^2 = 1 + b_s^2 \rightarrow b_s = \sqrt{\frac{1}{99}} \quad 1.6 \text{ Hz}$

$f_{\text{stop}} = \sqrt{\frac{1}{99}} f_c$
 $= \boxed{0.16 \text{ Hz}}$

⑤ When $f = f_{\text{pass}}$, $\left| \frac{V_{\text{out}}}{V_{\text{in}}} \right| = 0.9$

Let $b_p = \frac{f_{\text{pass}}}{f_c} \rightarrow \frac{b_p}{\sqrt{1+b_p^2}} = 0.9$

+2


$b_p^2 = 0.81 (1 + b_p^2)$

$0.19 b_p^2 = 0.81 \rightarrow b_p = \sqrt{\frac{0.81}{0.19}} = 2.065$

$f_{\text{pass}} = 2.065 f_c = \boxed{3.3 \text{ Hz}}$

⑥

+3


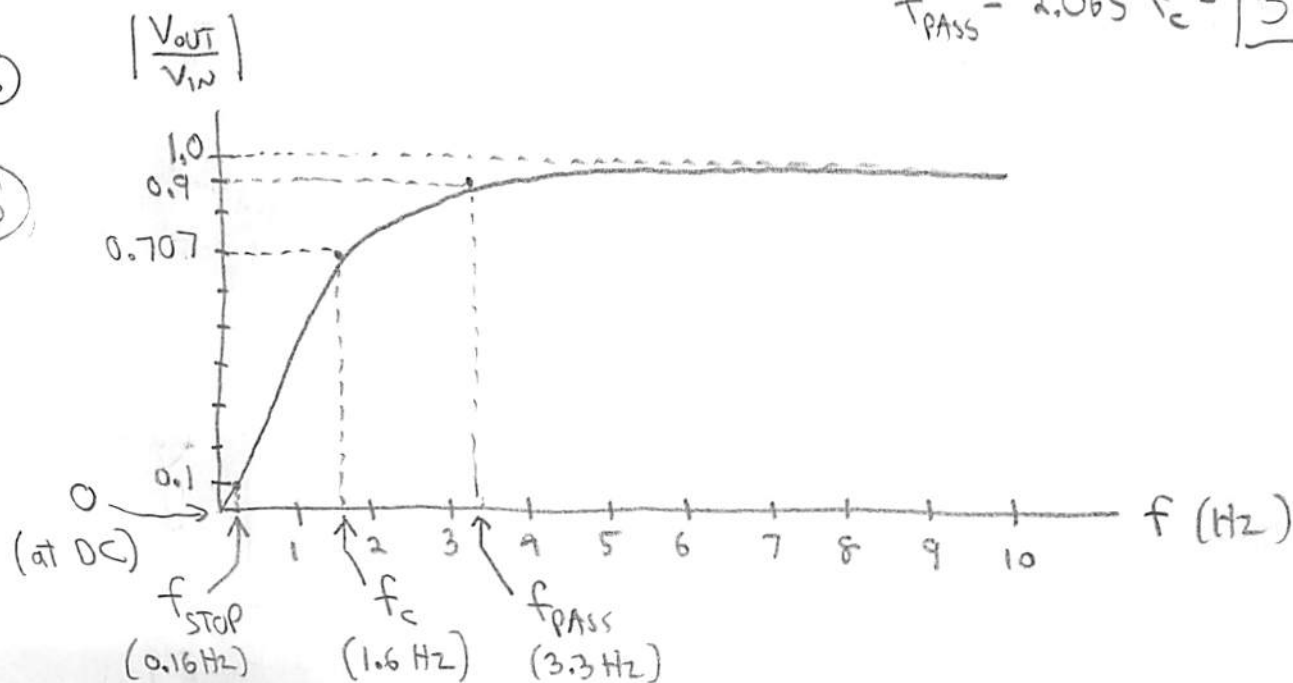


7

+3

● Rule #1: $V_- = V_+ = V_{IN}$

● KCL at node V_- :

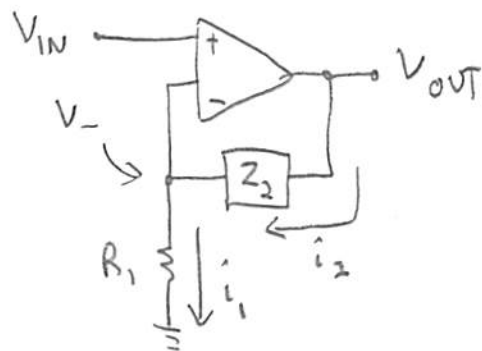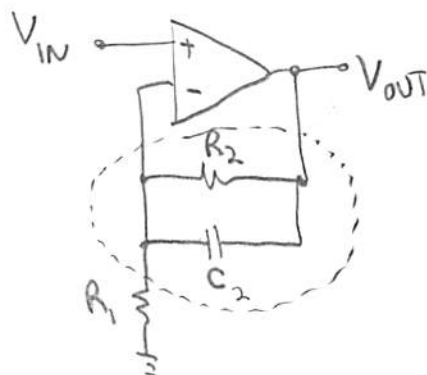

$$i_2 = i_1 + 0 \quad \text{Rule \#2}$$

$$\frac{V_{OUT} - V_-}{Z_2} = \frac{V_- - 0}{R_1}$$

$$V_{OUT} = \left(1 + \frac{Z_2}{R_1}\right) V_- = \left(1 + \frac{Z_2}{R_1}\right) V_{IN}$$

$$\Rightarrow \frac{V_{OUT}}{V_{IN}} = 1 + \frac{Z_2}{R_1} = 1 + \frac{R_2}{R_1} \frac{1}{1 + j\omega R_2 C_2}$$

$$= 1 + \frac{R_2}{R_1} \frac{1}{1 + j f \underbrace{2\pi R_2 C_2}_{1/f_c}}$$

$$\boxed{\frac{V_{OUT}}{V_{IN}} = 1 + \frac{R_2}{R_1} \frac{1}{1 + j f/f_c}}$$

$$\text{where } f_c = \frac{1}{2\pi R_2 C_2}$$

⑧ DC means $f = 0$!

$$\frac{V_{OUT}}{V_{IN}} = 1 + \frac{R_2}{R_1} = G_o \Rightarrow G_o = 1 + \frac{100k}{1k} = \boxed{101}$$

+2

⑨

$$f_c = \frac{1}{2\pi (10^5 \Omega)(0.1 \times 10^{-6} F)} = \boxed{15.9 \text{ Hz}}$$

+3

Need expression for $|G|$

$$G = 1 + 100 \frac{1}{1 + j f/f_c}$$

$$\text{Let } b = f/f_c \Rightarrow G = 1 + 100 \frac{1}{1 + jb} = \frac{1 + jb}{1 + jb} + \frac{100}{1 + jb} = \frac{101 + jb}{1 + jb}$$

$$\text{using } \left| \frac{a + jb}{c + jd} \right| = \frac{\sqrt{a^2 + b^2}}{\sqrt{c^2 + d^2}} \Rightarrow |G| = \frac{\sqrt{101^2 + b^2}}{\sqrt{1 + b^2}}$$

$$\text{When } f = f_c \Rightarrow b = 1 \Rightarrow |G| = \frac{\sqrt{101^2 + 1}}{\sqrt{2}} = \boxed{71.4}$$

$$\textcircled{10} \text{ Let } b_p = \frac{f_{pass}}{f_c} \Rightarrow 0.9 G_0 = \frac{\sqrt{101^2 + b_p^2}}{\sqrt{1 + b_p^2}}$$

+2

$$0.81 G_0^2 (1 + b_p^2) = 101^2 + b_p^2$$

$$0.81 (101)^2 b_p^2 - b_p^2 = 101^2 - 0.81 (101)^2$$

$$8261.81 b_p^2 = 1938.19 \Rightarrow b_p = 0.484 \quad 15.9 \text{ Hz}$$

$$f_{pass} = 0.484 f_c \quad \swarrow \\ = \boxed{7.7 \text{ Hz}}$$

$$\textcircled{11} \text{ Let } b_s = \frac{f_{stop}}{f_c} \Rightarrow 0.1 \times 101 = \frac{\sqrt{101^2 + b_s^2}}{\sqrt{1 + b_s^2}}$$

+3


$$(10.1)^2 (1 + b_s^2) = 101^2 + b_s^2$$

$$102.01 b_s^2 - b_s^2 = 101^2 - 102.01$$


$$101.01 b_s^2 = 10098.99$$

$$b_s = 9.999 \rightarrow f_{\text{stop}} = 9.999 f_c = \boxed{159 \text{ Hz}}$$

$\uparrow$
 15.9 Hz

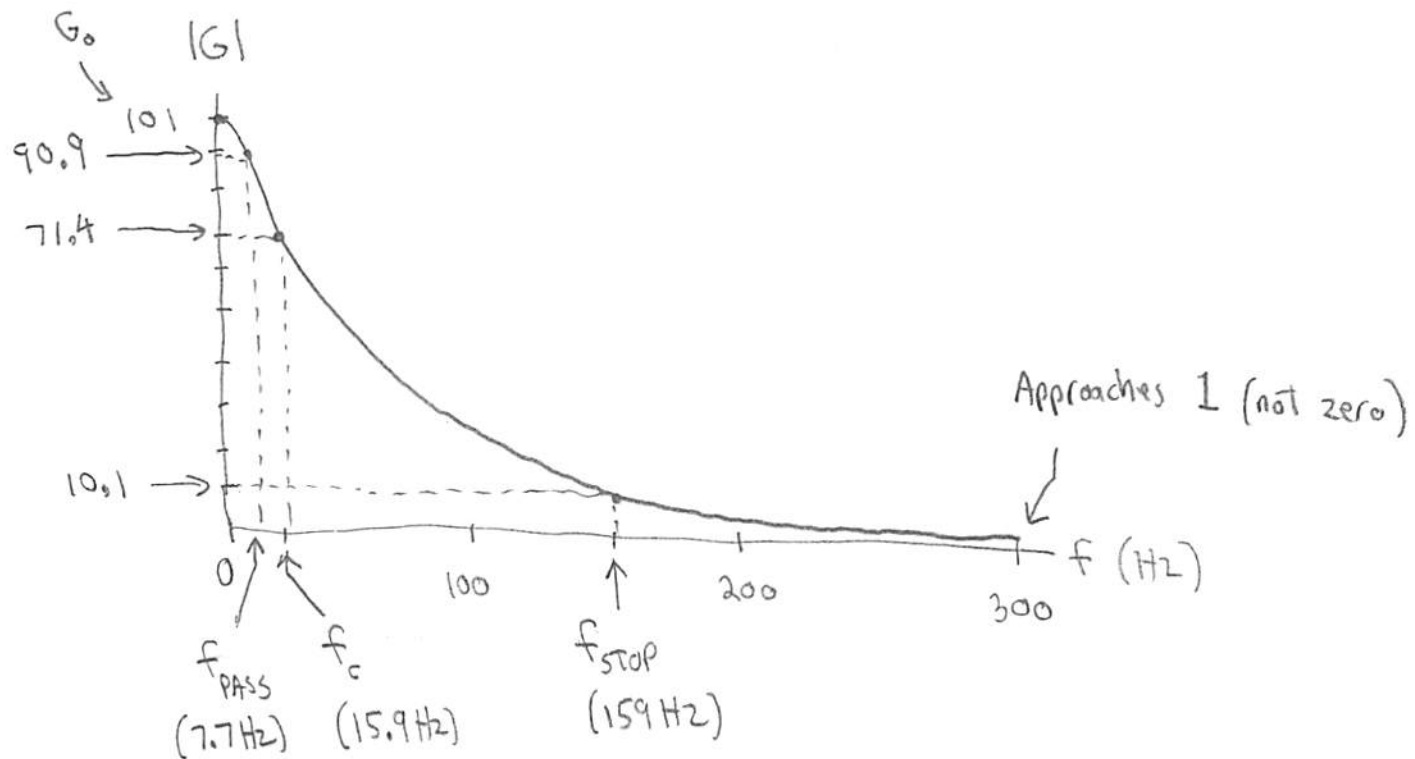

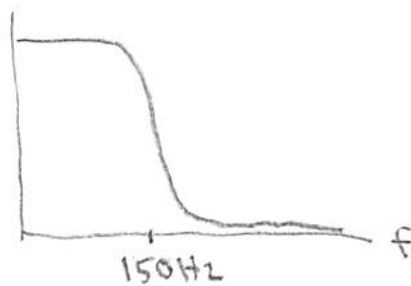NOTE: It would be MUCH better to have something like



But this requires a $>4^{\text{th}}$ order filter
 (more complicated circuit)