

Lecture 3: Thermistor



0. Review

1. Thermistor

2. Signal Conditioning + Processing

3. Temperature Sensitivity


- Hw1 due Thu (Jan 16) ^{Hw1 material}
Quiz next Tue (Jan 21) ←

- PreLab 1 due at
lab session
-


- Reading: Thermistor
tutorial (pdf)
- PreLab 2 due next
lab session

0. Review

① Load cells :

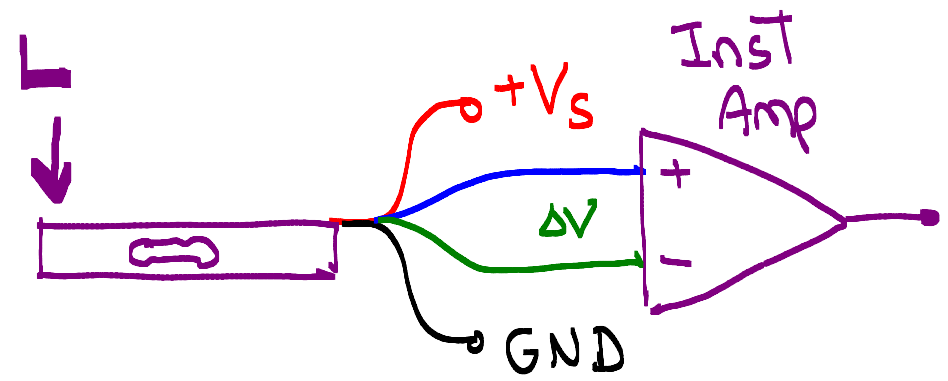

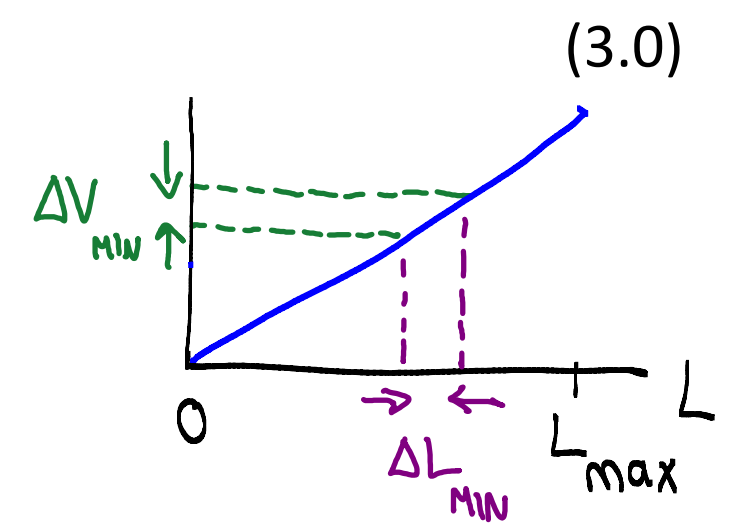
$$V_{MEAS} = A_s \cdot V_s \cdot R_O \cdot \frac{L}{L_{Rated}}$$



② Sensitivity:


$$\Delta L_{MIN} = \frac{\Delta V_{MIN}}{\partial V_{MEAS} / \partial L}$$

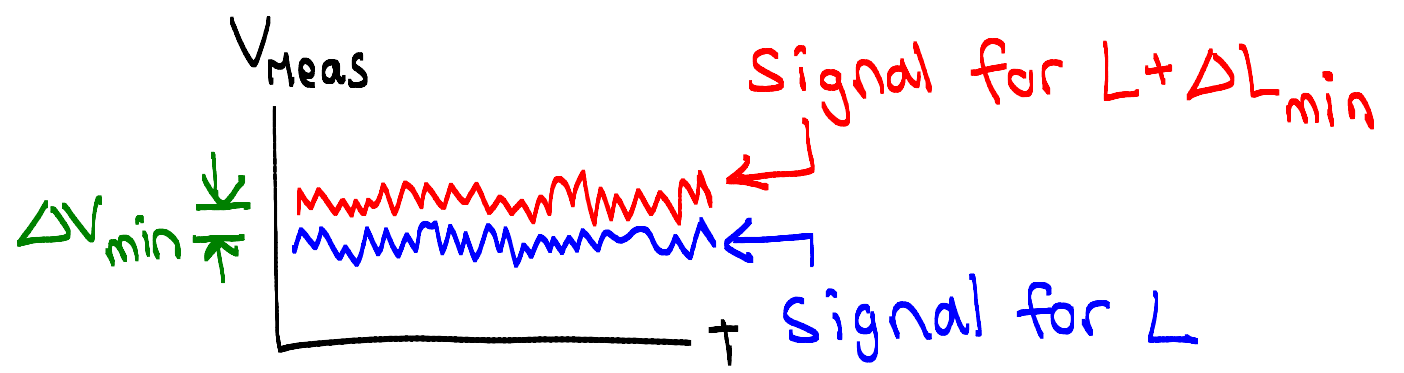← Larger $\left\{ \begin{matrix} V_{n,rms} \\ \Delta V_{ADC} \end{matrix} \right.$




③ Analog-to-Digital Conversion

Vertical Resolution:

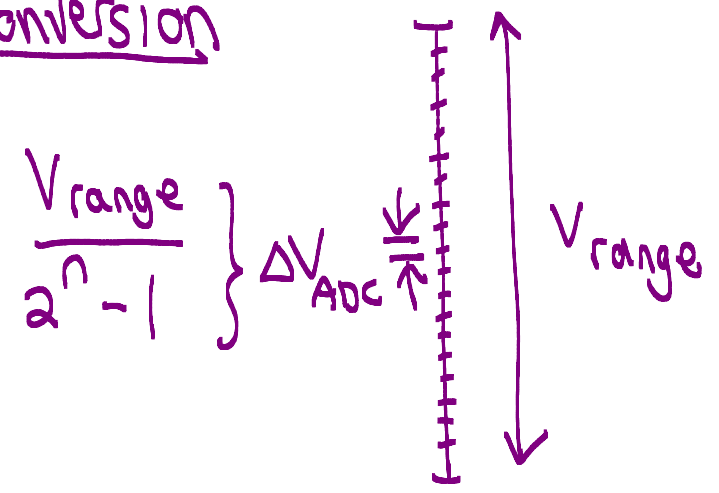

Sampling Interval:

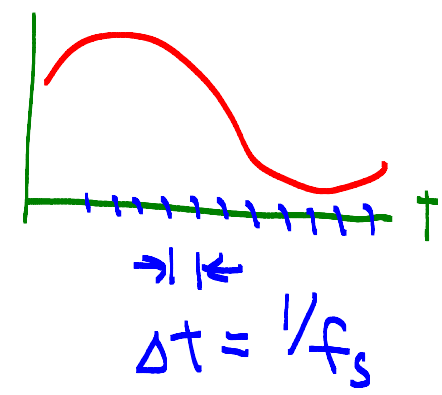

1. Thermistor

A. Temperature Intro

Q: Why measure temperature?

① In medicine, external body temperature is an important indicator of health

→ Low temp (shock)

→ High temp (fever)

② Many biomedical experiments require temperature control


→ Egg incubator

→ chemical reactions

→ simulate human body conditions



ourlocalpharmacy.com

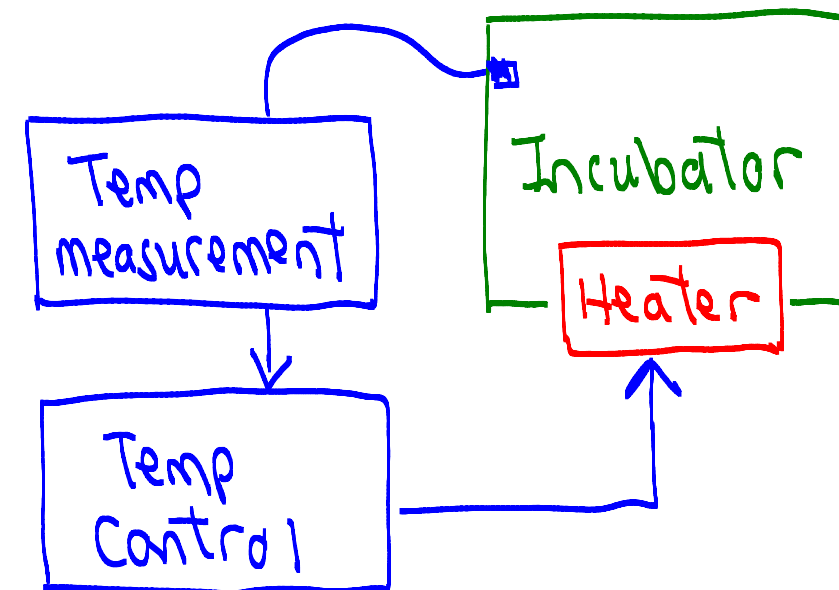

B. Thermistor Basics (THERMally sensitive resISTOR)

- Similar concept to strain gauge, except:

① R_T strongly depends on temperature

② R_T has negative temp dependence


③ R_T has nonlinear temp dependence

④ Material is a ceramic semiconductor (e.g. manganese oxide)

- Lots of resistance values ($R_{25} = 10, 15, \dots, 1k, 2.2k, \dots, 100k$)

- Temperature range is typically ~ -50 to 200°C

- Common shapes: Bead, Disc, Chip

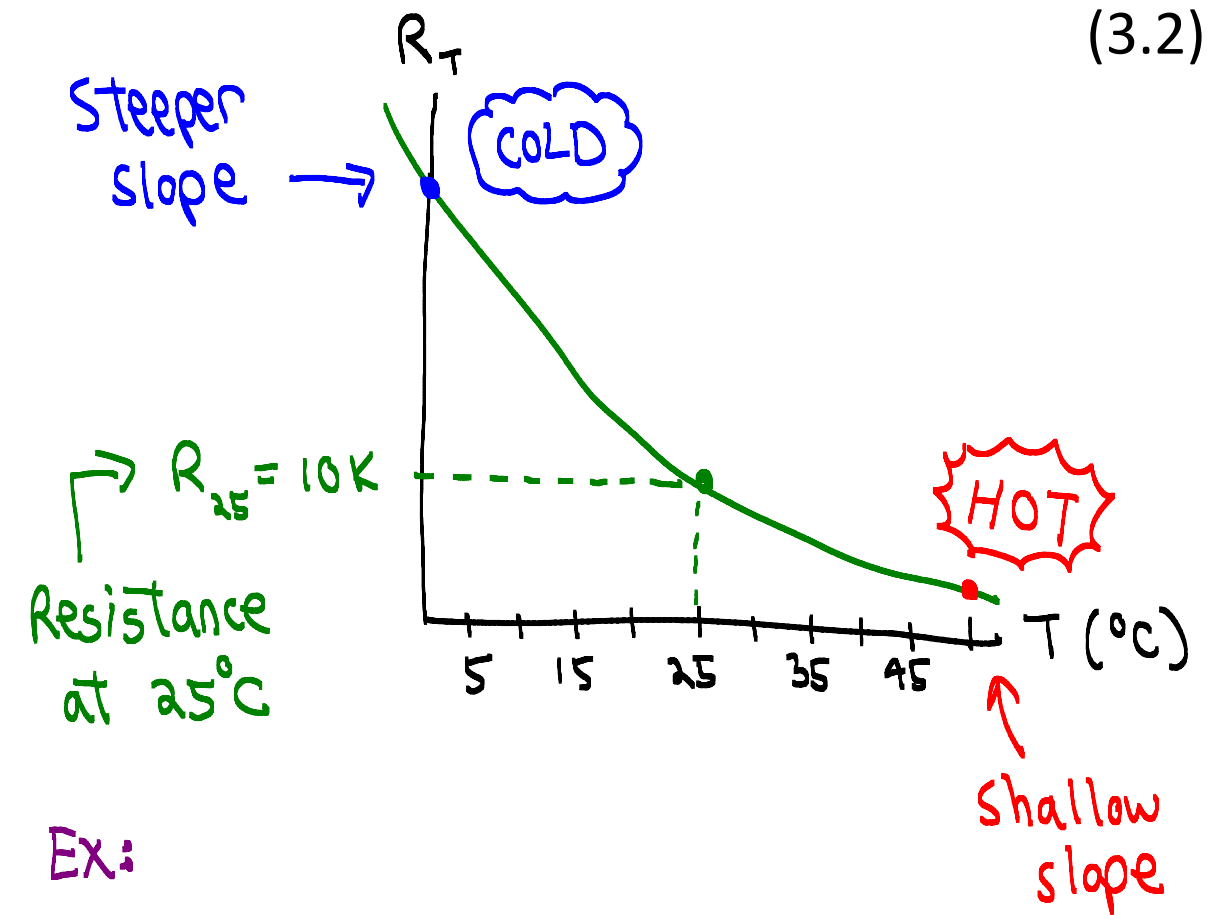

EX:



www.vishay.com


C. Negative Temp Coefficient (NTC)

$$\text{Slope} = \frac{\partial R_T}{\partial T} = \boxed{\alpha} R_T$$

↑
Tempco

* α depends on temperature!

Ex: 10K thermistor

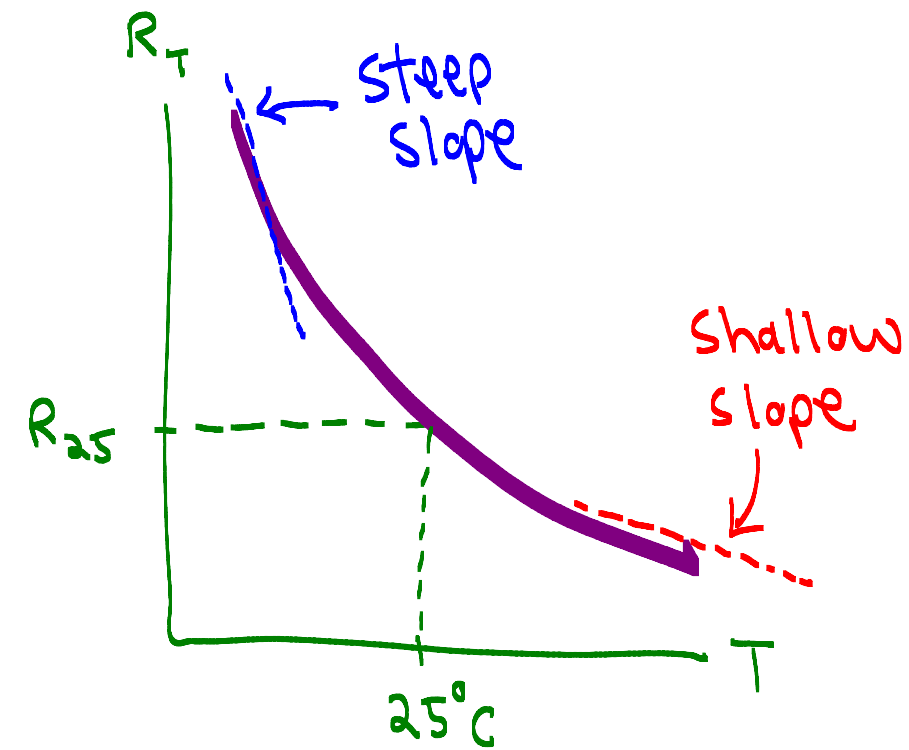

T	R_T	α	$\text{Slope} = \alpha R_T$
10°C	$19.87\text{ k}\Omega$	$-4.79\text{ \%/}^\circ\text{C}$	$(-0.0479\text{ }^\circ\text{C}^{-1})(19.87\text{ k}\Omega) = -0.95\text{ k}\Omega/^\circ\text{C}$
40°C	$5.33\text{ k}\Omega$	$-4.02\text{ \%/}^\circ\text{C}$	$(-0.0402\text{ }^\circ\text{C}^{-1})(5.33\text{ k}\Omega) = -0.21\text{ k}\Omega/^\circ\text{C}$

2. Signal conditioning + processing

A. Signal Conditioning


use a quarter bridge + inst amp.

$$V_{MEAS} = V_{REF} + A_d \Delta V$$

↑
Reference voltage
↑
From bridge

Acts like a "default" value (when $\Delta V = 0$, then $V_{MEAS} = V_{REF}$)

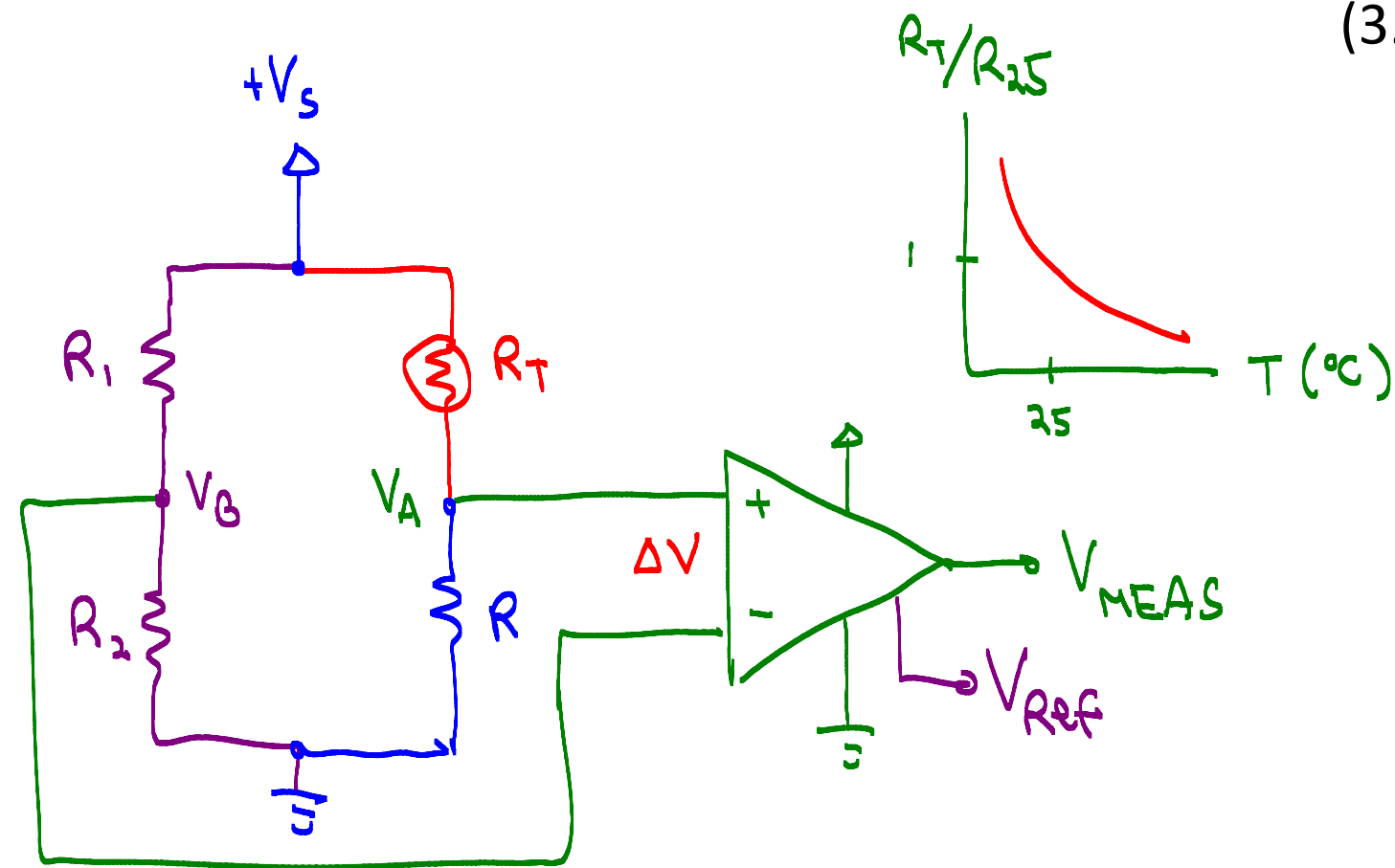- As temp $\uparrow$, then $R_T \downarrow$, so $V_A \uparrow \Rightarrow \Delta V > 0 \Rightarrow V_{MEAS}$ increases
- As temp $\downarrow$, then $R_T \uparrow$, so $V_A \downarrow \Rightarrow \Delta V < 0 \Rightarrow V_{MEAS}$ decreases



What is the measured signal?

Ex: Left side of bridge has R
Right side has R_{25}


$$V_{MEAS} = V_{REF} + A_d \left[V_A - V_B \right]$$

PreLab 2
Problem: $\Delta V = V_s \left(\frac{R_{25}}{R_T + R_{25}} - \frac{1}{2} \right)$

$$V_{MEAS} = V_{REF} + A_d V_s \left(\frac{R_{25}}{R_T + R_{25}} - \frac{1}{2} \right)$$

↑ varies with temp

only valid
for this example!

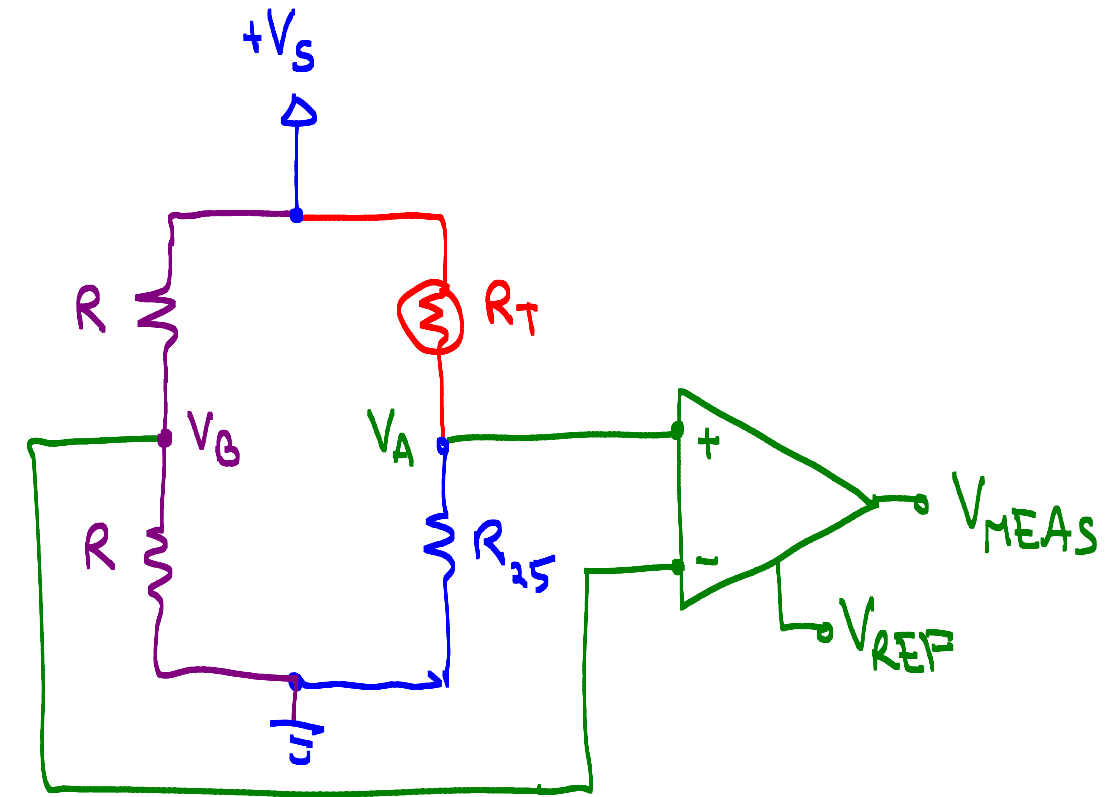

Ex: $R_{25} = 10K$ $R_T = 18K$ $V_s = 5V$

$A_d = 3$ $V_{REF} = 2.5V$

$$V_{MEAS} = 2.5 + 3 \times 5 \left(\frac{10K}{18K + 10K} - \frac{1}{2} \right)$$

$$= \underline{\underline{0.36V}}$$

B. Signal Processing

Q: How to convert V_{MEAS} to a temperature value?

Step 1: Convert V_{MEAS} to R_T

$$\text{use } \Delta V = \frac{V_{MEAS} - V_{REF}}{A_d} = V_s \left[\frac{R_{25}}{R_T + R_{25}} - \frac{1}{2} \right]$$

Only for previous example


Solve for R_T

Step 2: Convert R_T to Temperature

Use the "Extended Steinhart-Hart Equation"

$$\frac{1}{T} = A + B \ln \frac{R_T}{R_{25}} + C \left[\ln \frac{R_T}{R_{25}} \right]^2 + D \left[\ln \frac{R_T}{R_{25}} \right]^3$$

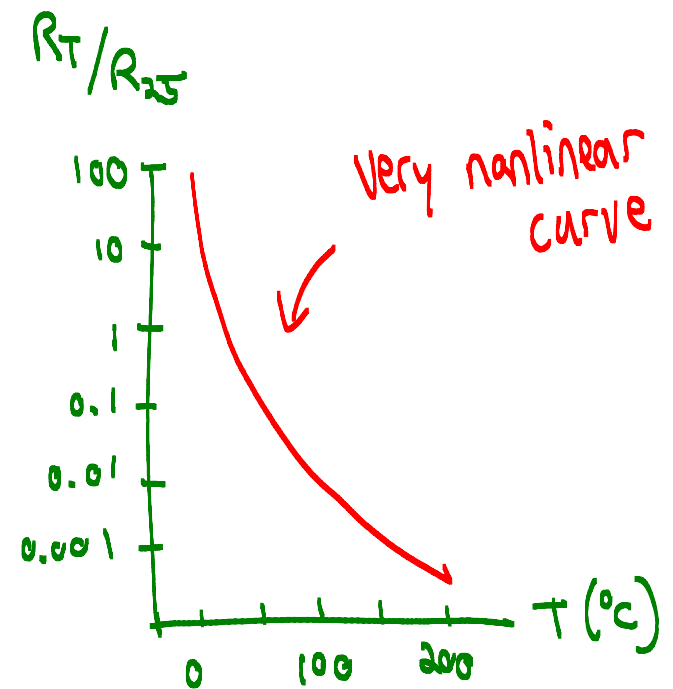Very accurate over a $\sim 100^\circ\text{C}$ temp range



Best done with a microprocessor or computer.

EX: $A = 3.354016 \times 10^{-3}$
 $B = 2.569850 \times 10^{-4}$
 $C = 2.620131 \times 10^{-5}$
 $D = 6.383091 \times 10^{-6}$

(3.6)

C. Self-Heating

At $T = 25^\circ\text{C}$, $R_T = R_{25}$ (eg. 10K).

However, R_T dissipates power.

$\rightarrow P = I^2 R$ } Heat causes thermistor to get slightly warm


$\Rightarrow$ Resistance is lower

Q: How to compute self-heating?

$$\Delta T = \frac{\left[\text{Power dissipation in thermistor} \right]}{\left[\text{Dissipation Factor} \right]}$$

$\nearrow$ $\text{mW}/^\circ\text{C}$

3.7

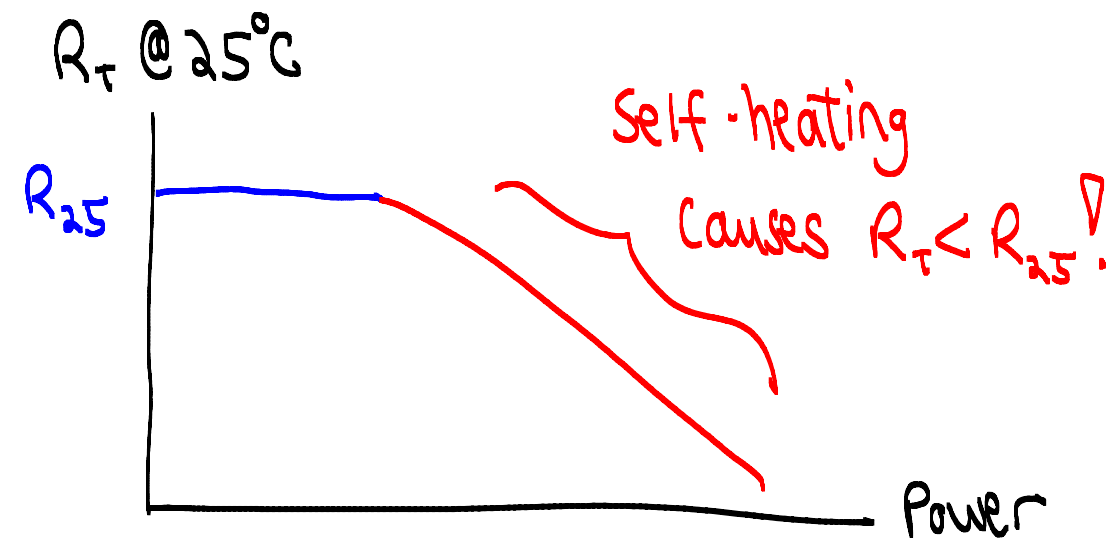


Ex: $\delta = 5\text{ mW}/^\circ\text{C}$

$R_T = R = 5\text{K}$

$V_s = 10\text{V}$
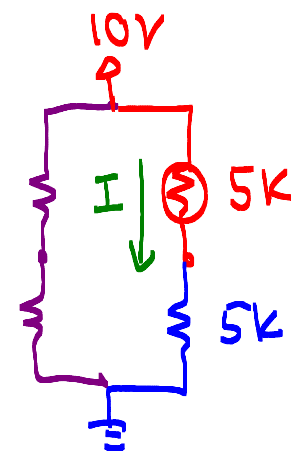
$$\rightarrow P = IV = \frac{10\text{V}}{5\text{K} + 5\text{K}} \times 5\text{V} = 5\text{ mW}$$



$$\rightarrow \Delta T = \frac{P}{\delta} = 5\text{ mW} / (5\text{ mW}/^\circ\text{C}) = 1^\circ\text{C}$$

NOT good (want $< 0.1^\circ\text{C}$)

D. Overall System


- Signal conditioning is similar to strain gauge.

→ Resistor bridge (Quarter bridge)

→ Instrumentation Amplifier


- Processing must convert recorded voltage to R_T , then compute temperature.

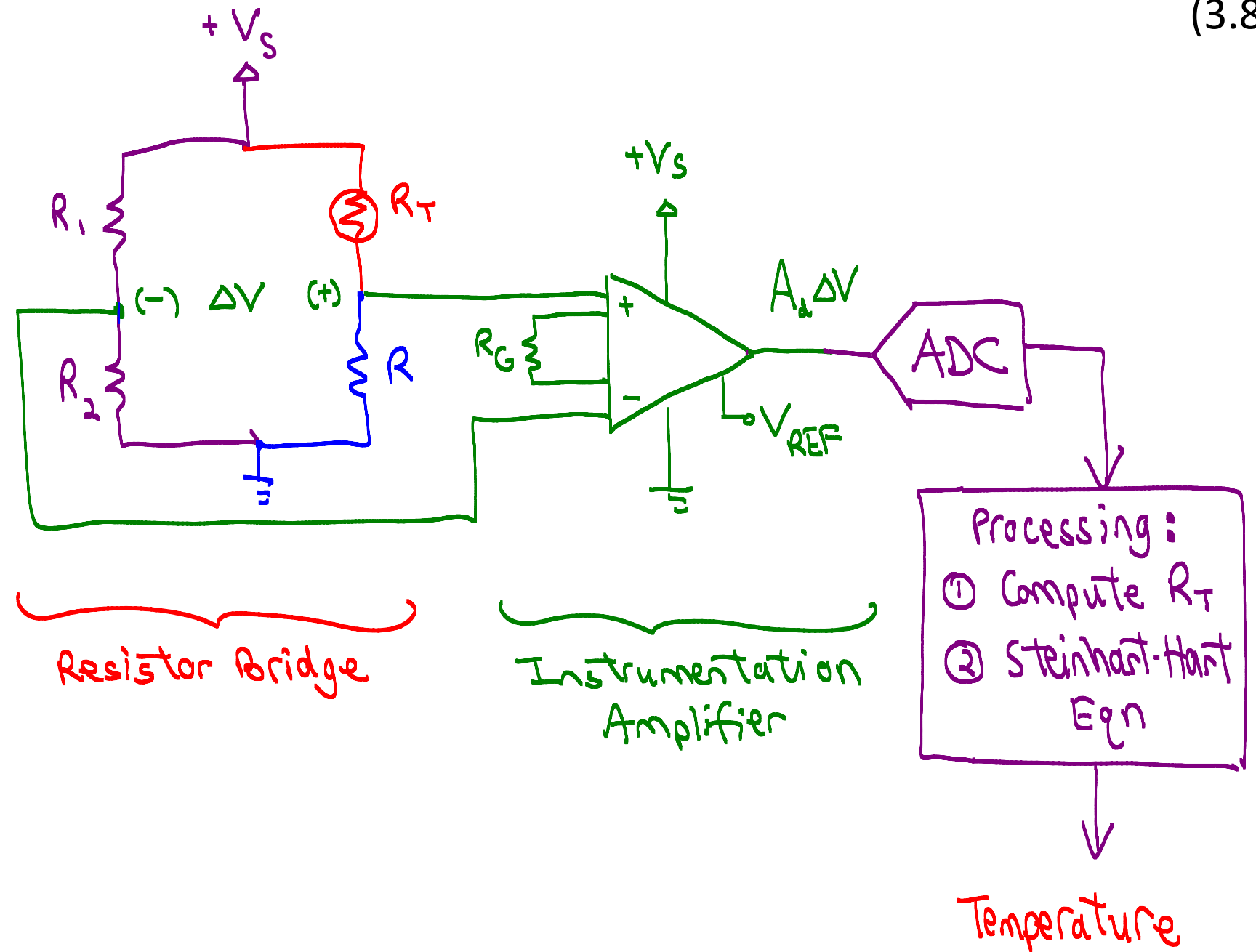- Sensitivity can be $\Delta T_{\min} \sim 0.01^\circ\text{C}$!



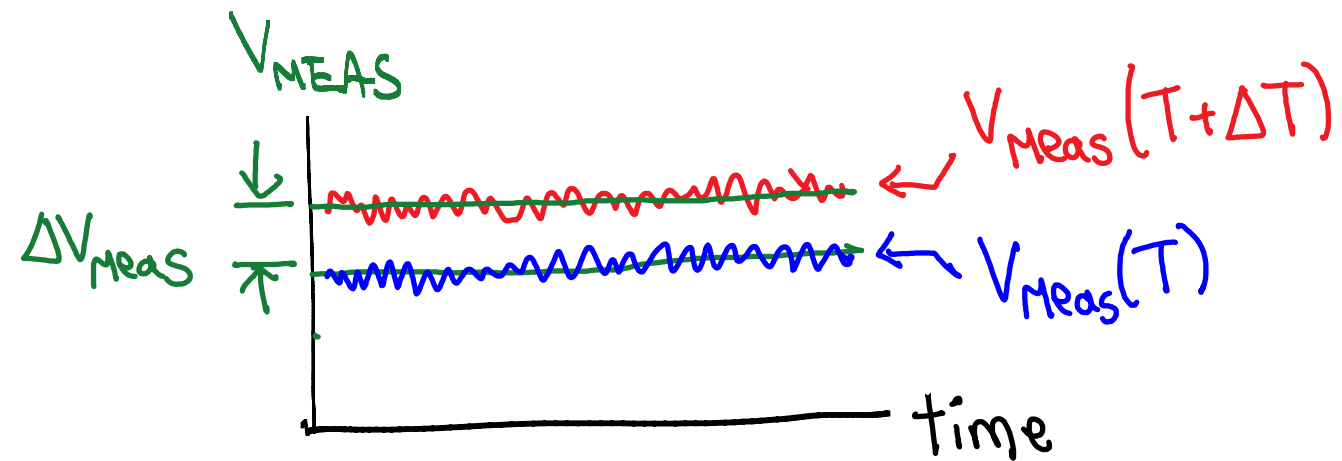3. Temperature Sensitivity

ΔT_{MIN} = smallest detectable change in temp




$$\Delta V_{\text{MEAS}} = V_{\text{MEAS}}(T + \Delta T) - V_{\text{MEAS}}(T)$$

$$\approx \frac{\partial V_{\text{MEAS}}}{\partial T} \Delta T$$

★ ΔT_{MIN} produces smallest detectable ΔV_{MEAS} !
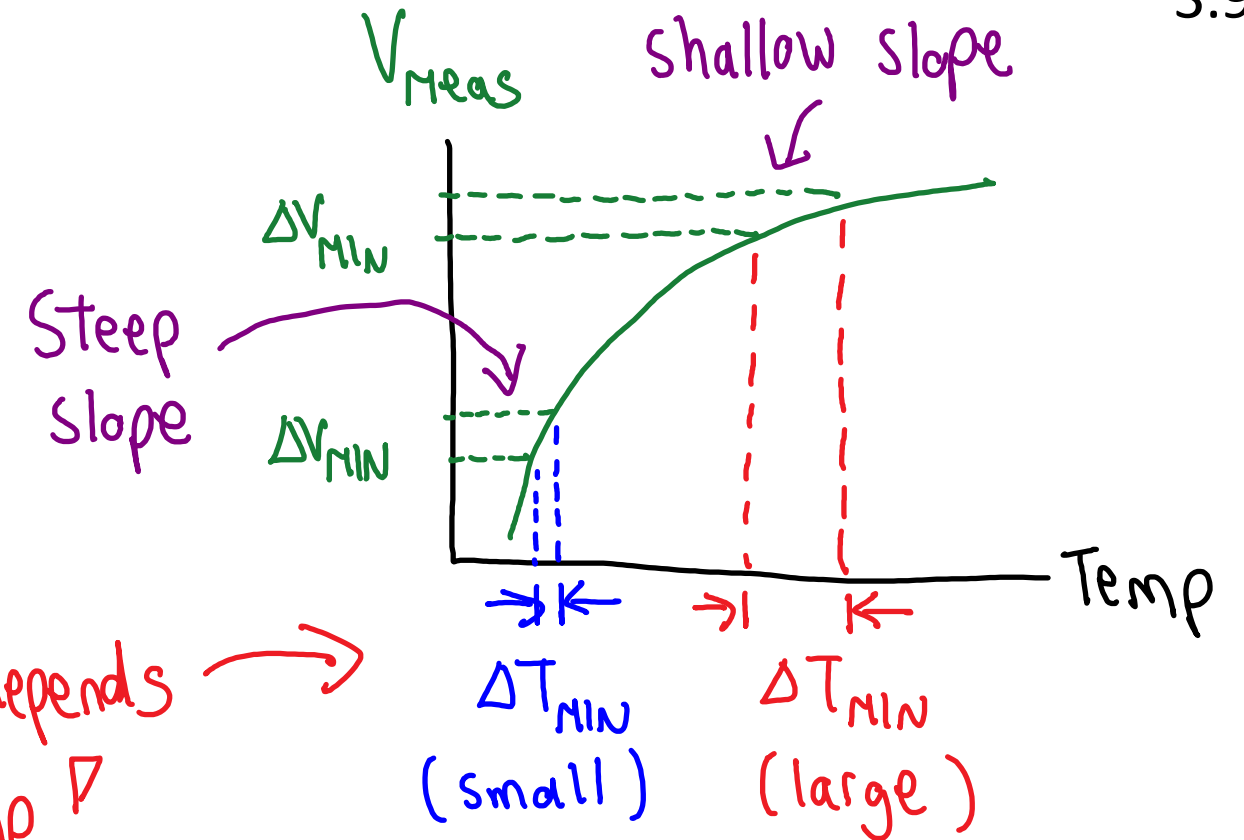
$$\Delta V_{\text{MIN}} = \frac{\partial V_{\text{MEAS}}}{\partial T} \Delta T_{\text{MIN}}$$



ΔT_{MIN} depends on temp!

$$\Delta T_{\text{MIN}} = \frac{\Delta V_{\text{MIN}}}{\frac{\partial V_{\text{MEAS}}}{\partial T}}$$

Larger of $V_{\text{N,rms}}$ vs. ΔV_{ADC}

slope

• Example: If $\Delta V_{MIN} = 10 \text{ mV}$, what is ΔT_{MIN} ?

$$\star \Delta T_{MIN} = \frac{\Delta V_{MIN}}{\frac{\partial V_{MEAS}}{\partial T}} \leftarrow !$$

① Need expression for V_{MEAS}


$$V_{MEAS} = V_{REF} + A_d \cdot V_s \cdot \left[\frac{10K}{R_T + 10K} - \frac{1}{2} \right]$$

↑
constant

Where $\rightarrow \Delta V$
is T ? ☹

② use chain rule:
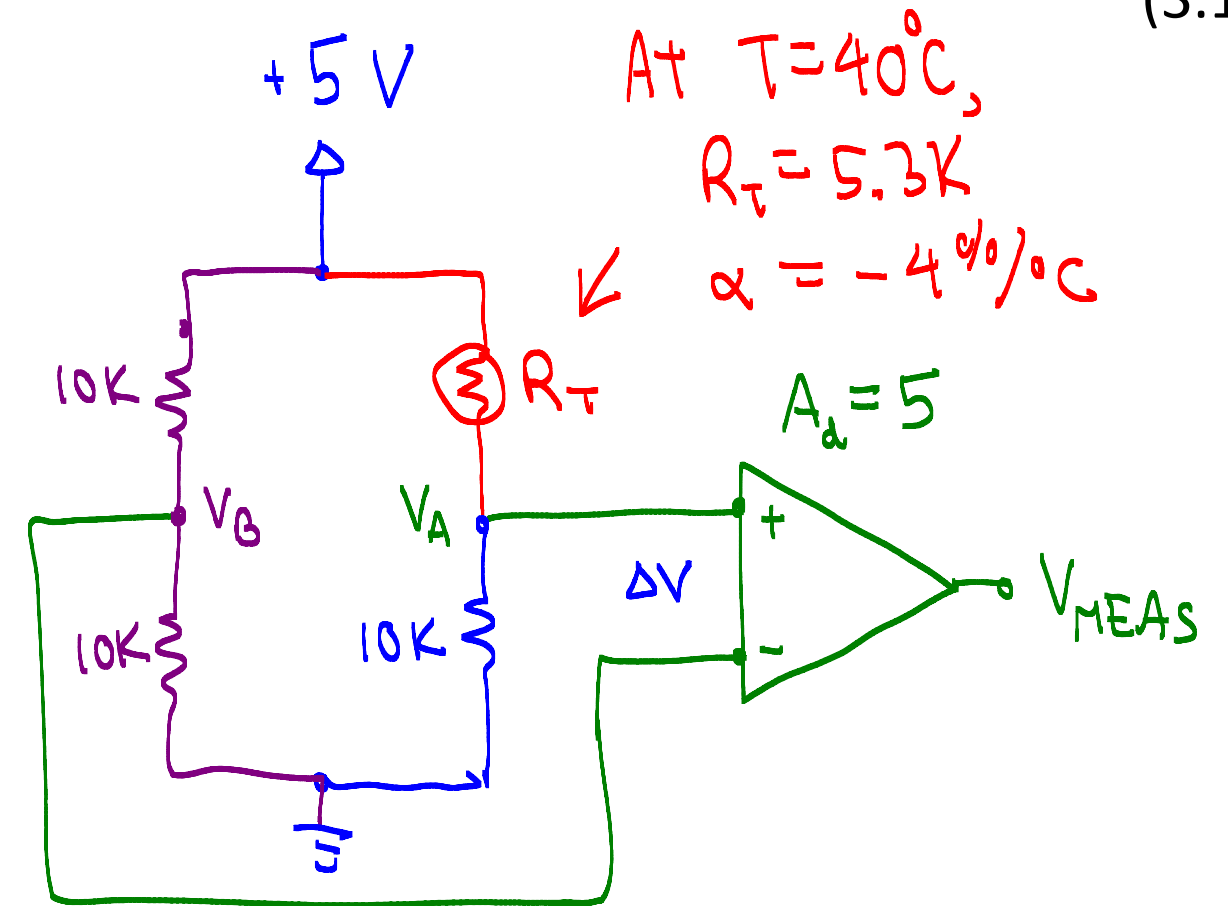
$$\frac{\partial V_{MEAS}}{\partial T} = \frac{\partial V_{MEAS}}{\partial R_T} \frac{\partial R_T}{\partial T} = \left[-A_d V_s \frac{10K}{(R_T + 10K)^2} \right] [\alpha R_T]$$



using $\frac{\partial R_T}{\partial T} = \alpha R_T$

$$\text{So, } \frac{\partial V_{\text{NEAS}}}{\partial T} = \left[-5 \times 5V \frac{10K}{(5.3K + 10K)^2} \right] \left[-\underline{0.04} \%_C \cdot \underset{\uparrow}{5.3K} \right] = 0.226 \%_C$$

use ≥ 3 decimal places!

$$\textcircled{3} \text{ Finally, } \Delta T_{\text{MIN}} = \frac{\Delta V_{\text{MIN}}}{\frac{\partial V_{\text{NEAS}}}{\partial T}} = \frac{.010V}{.226 \%_C} = \boxed{.044^\circ C}$$

only at $40^\circ C$!

ΔT_{MIN} is NOT identical at other temp!

NOTE: Suppose at $T = 25^\circ C \rightarrow R_T = 10K$ and $\alpha = -4.3\%$

$$\Rightarrow \frac{\partial V_{\text{NEAS}}}{\partial T} = \left[-5 \times 5V \cdot \frac{10K}{(\underset{\uparrow}{10K} + 10K)^2} \right] \left[-\underline{.043} \%_C \cdot \underset{\uparrow}{10K} \right] = 0.269 \%_C$$

$$\Rightarrow \Delta T_{\text{MIN}} = \frac{.010V}{.269 \%_C} = \boxed{0.037^\circ C} \leftarrow \text{slightly better sensitivity than @ } 40^\circ C$$