

## Lecture 6 : ECG (Part 2)

### 0. Review

### 1. 12-Lead ECG

### 2. ECG system

### 3. Mini Lab

- Today : HW2 due

- Fri (Jan 24) : Lab 1 report due

- Next week : Quiz (Jan 28) ← HW2 material

PreLab 3 (due at lab session)

HW 3 (due Jan 30)

Lab 2 report (due Jan 31)

↑ see course website for template


- Exam #1 (Feb 6) !

→ course website will have  
sample exam + solutions

## 0. Review


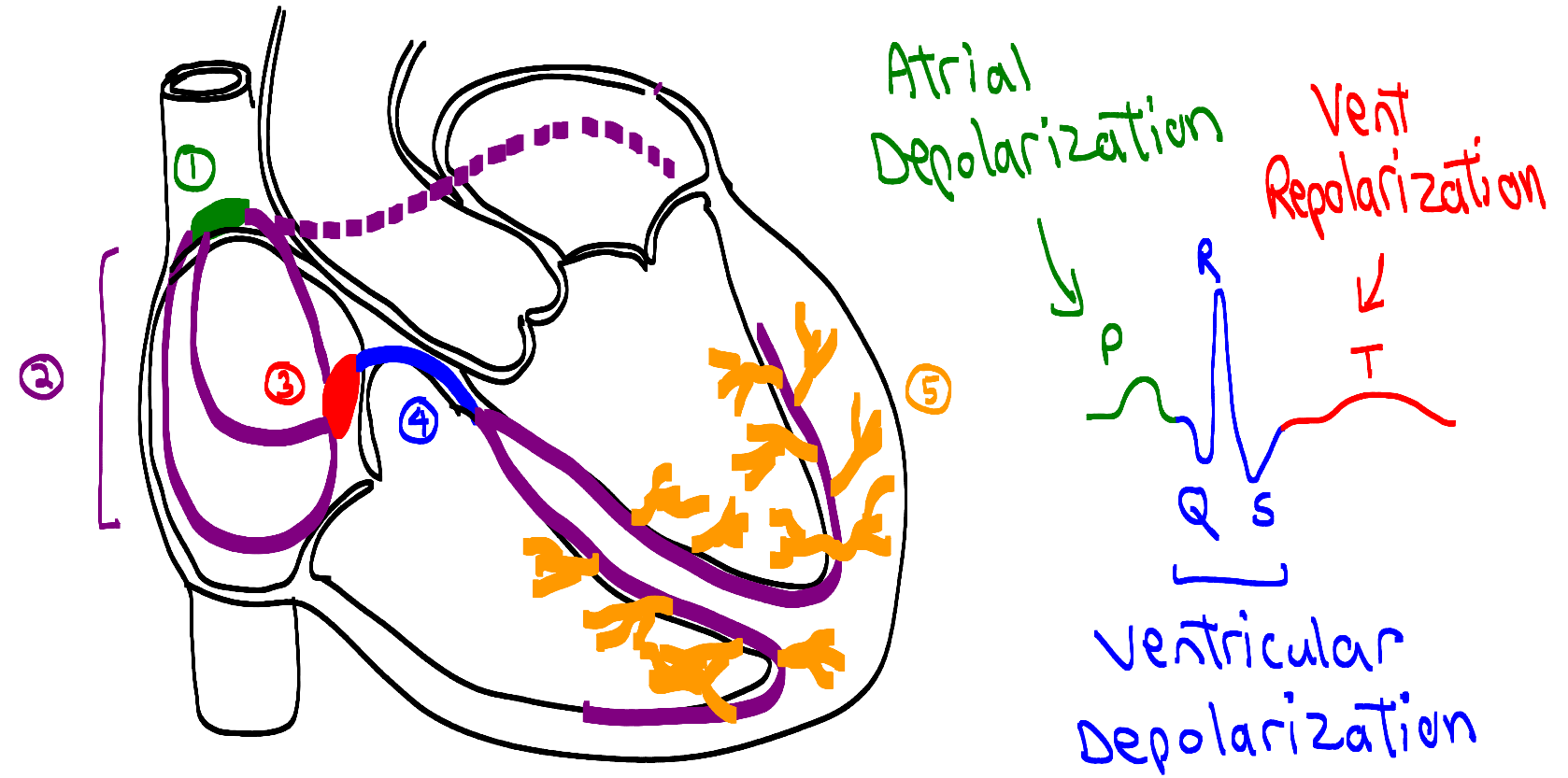
### A. Electrical network of the heart

- ① SA node
- ② Internodal Tracts + Bachmann's Bundle
- ③ AV node
- ④ His, left + right bundles
- ⑤ Purkinje fibers



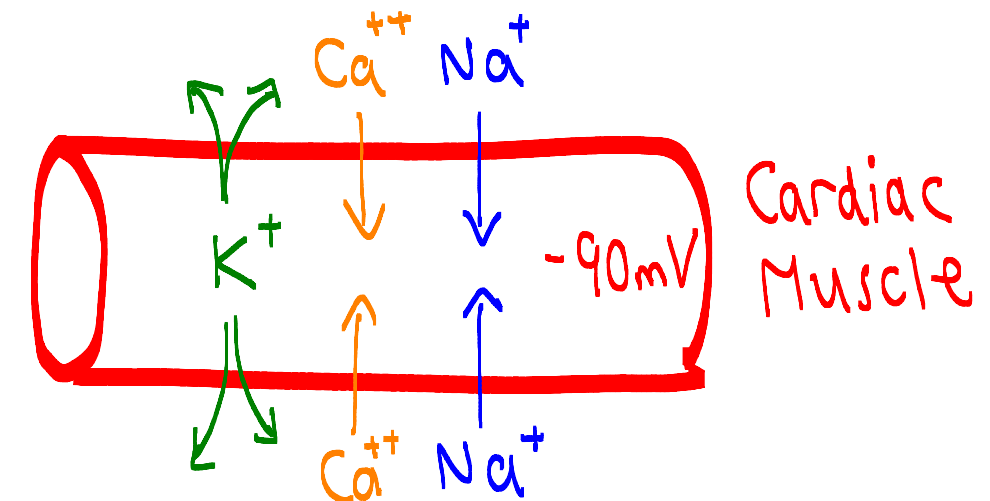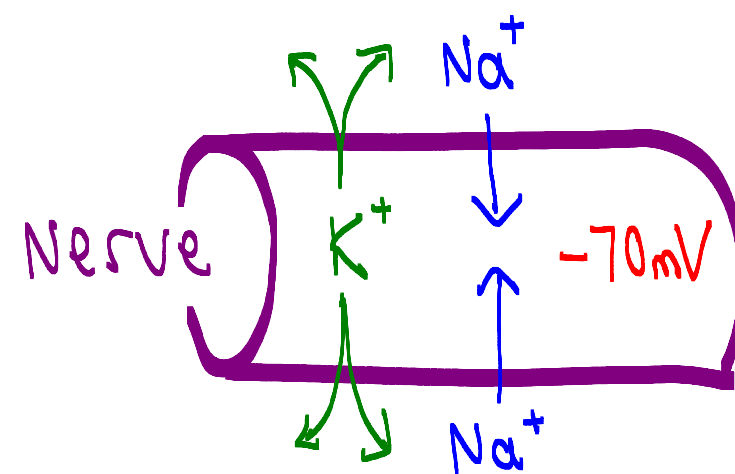
### B. Action Potentials

Rest potential  
Depolarization  
Repolarization




1. 12-Lead ECG ← standard method

3 Einthoven's Triangle

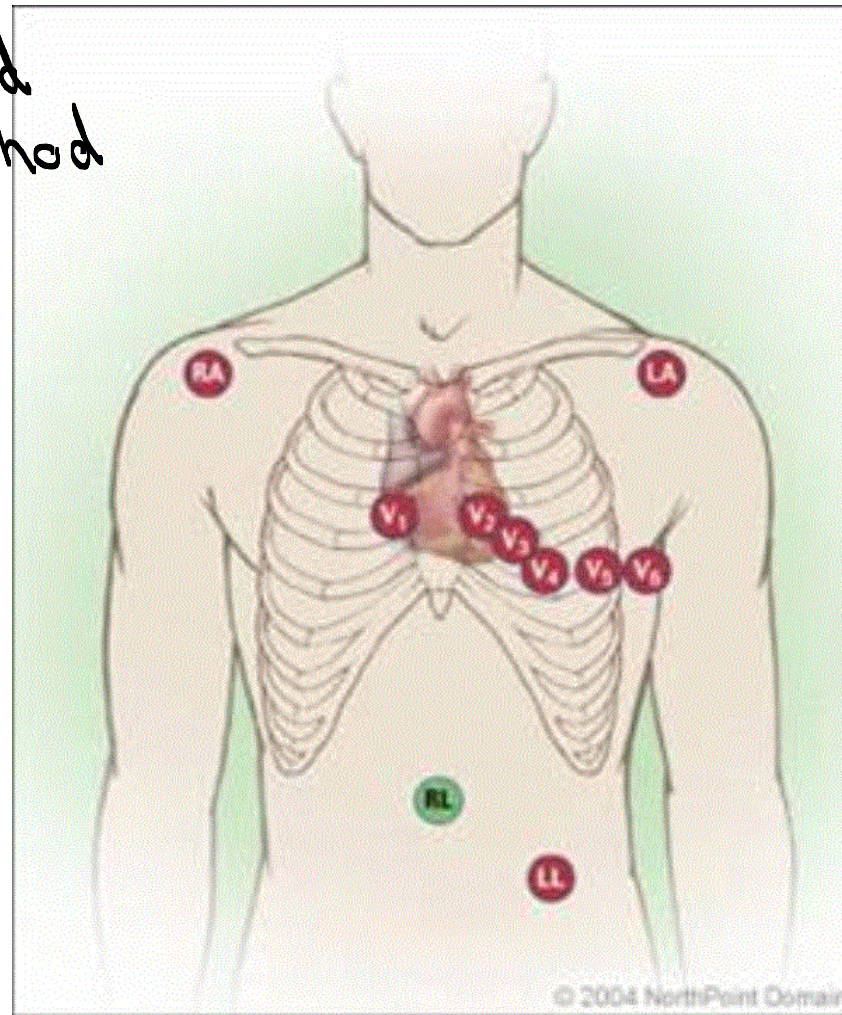

homepages.cae.wisc.edu

(6.1)

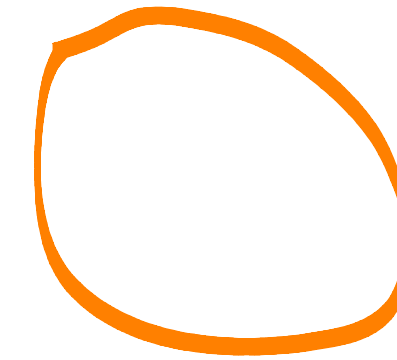


VS

RA

LA

VS

LL

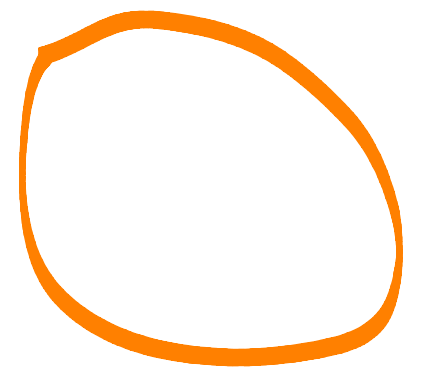

RA

LA

LL


Q: Why so many leads?



- Augmented Leads

The RA, LA, and LL electrodes also define

(6.2)

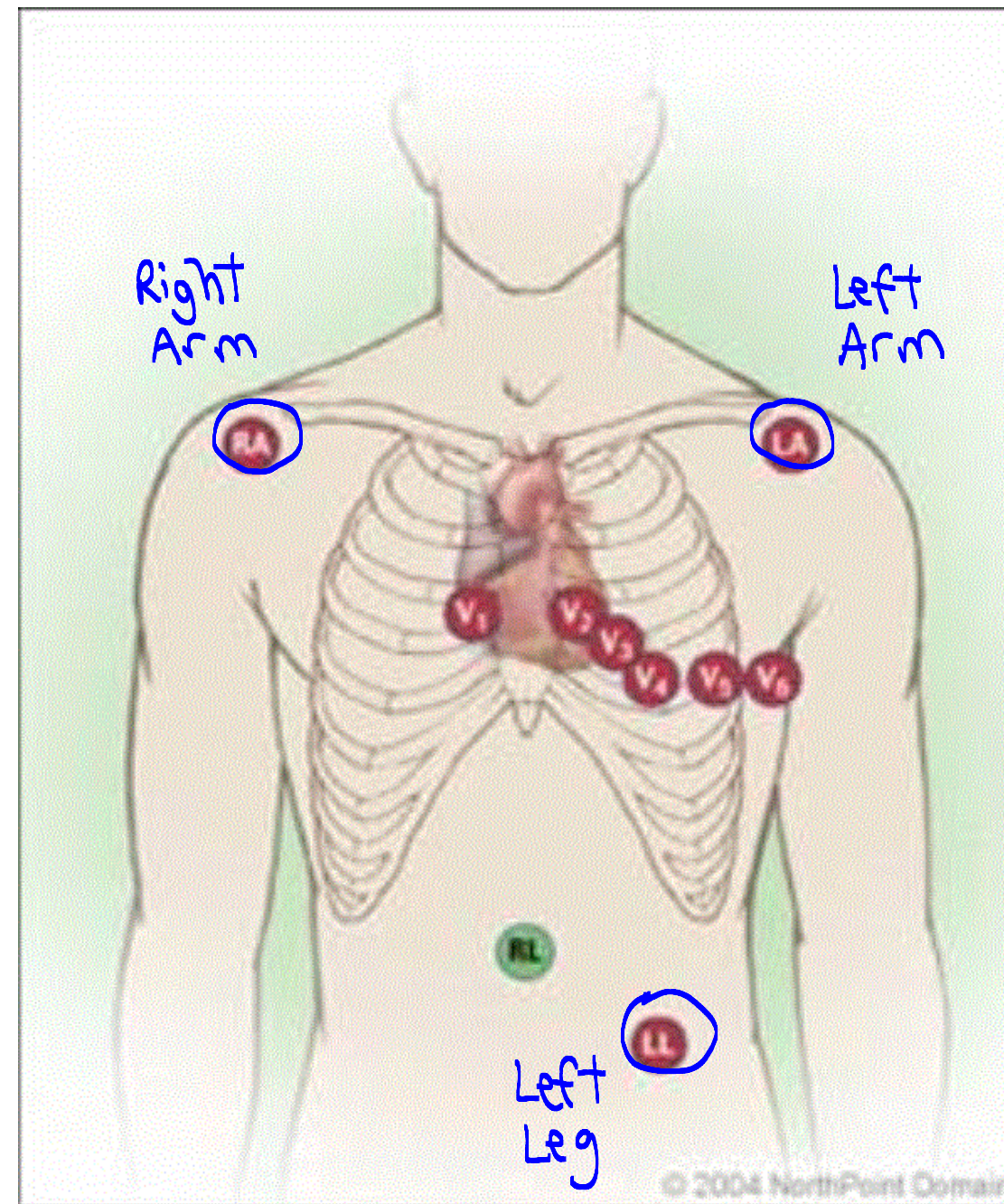

RA

LA

LL


homepages.cae.wisc.edu




- Precordial Leads

→            more electrodes placed on  
BACK

           ,

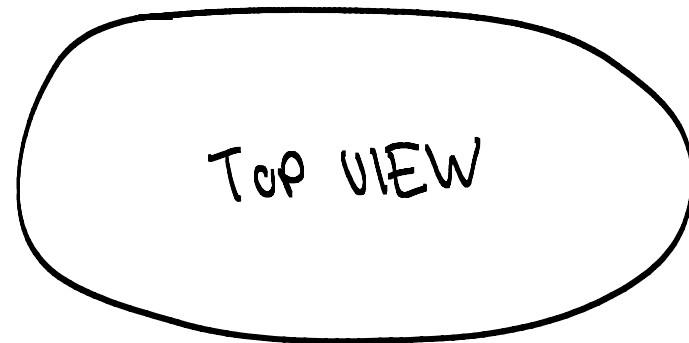

CHEST

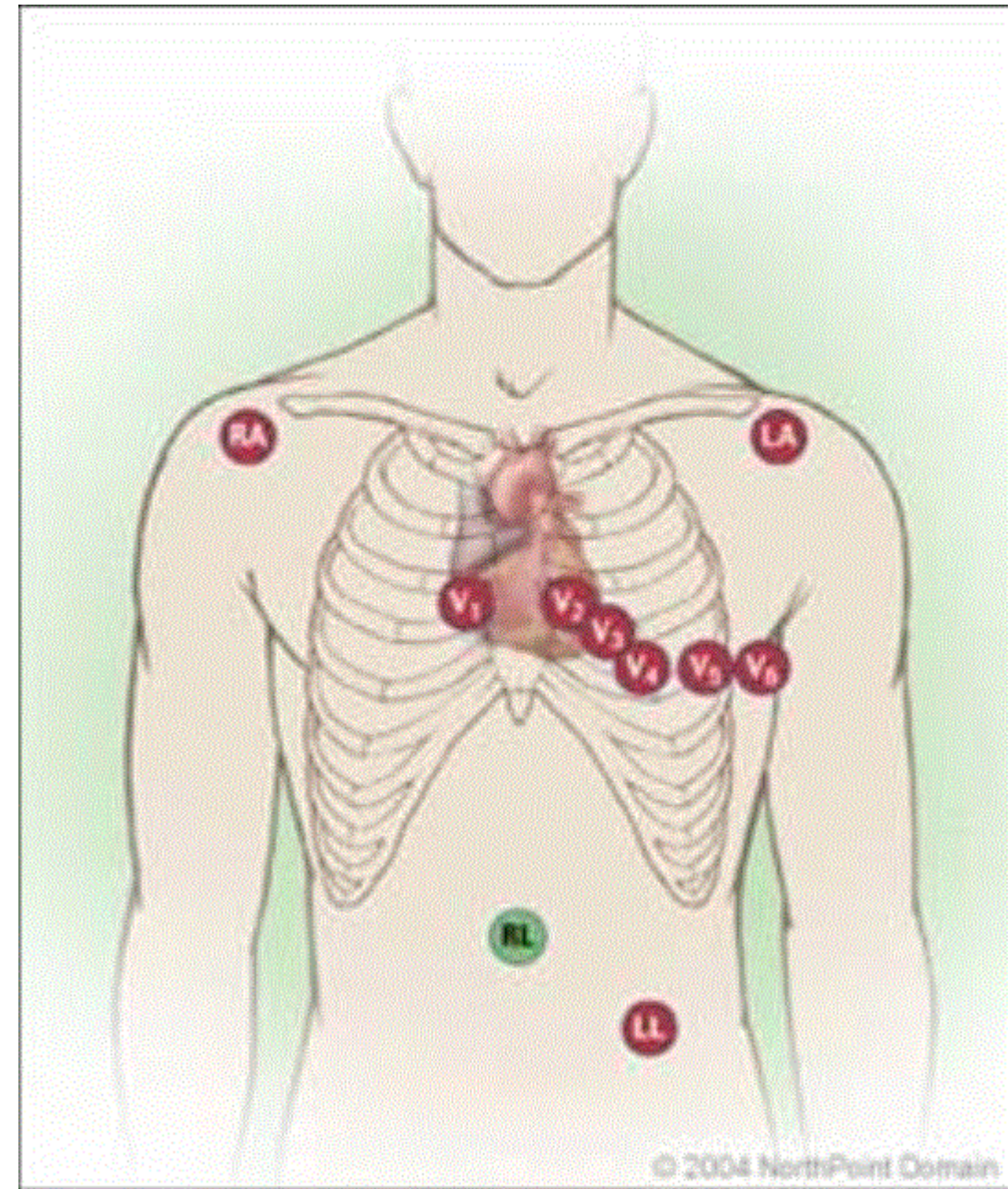


homepages.cae.wisc.edu

(6.3)

## 2. ECG System

(6.4)

ECG  
Lab3 is the simplest case:

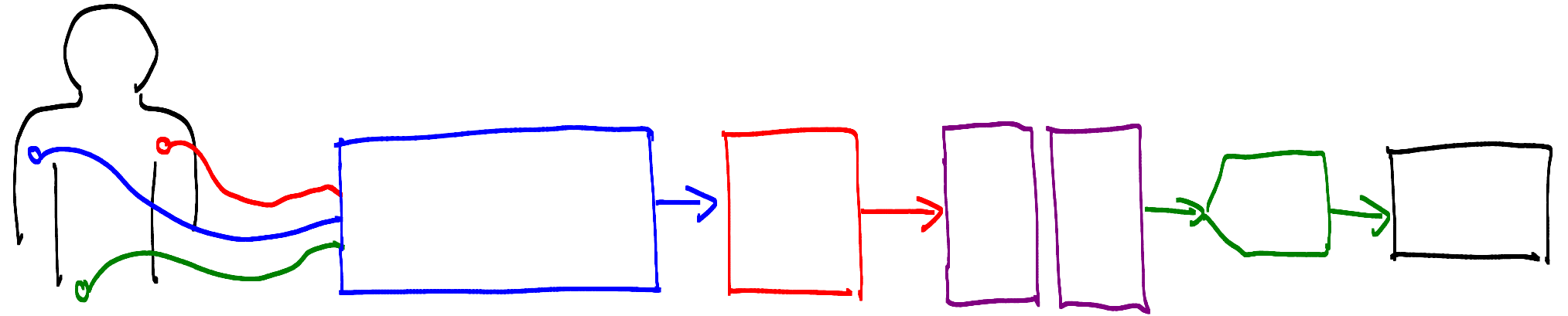


### A. Preamplifier

- Instrumentation amplifier amplifies  $\Delta V =$



vs.

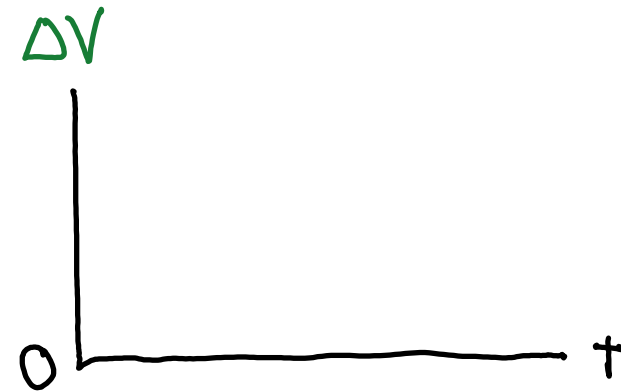




# • Input protection

ECG amplifier inputs usually have



• **Electrode 1**  
 $V_1$

**Electrode 2**  
 $V_2$

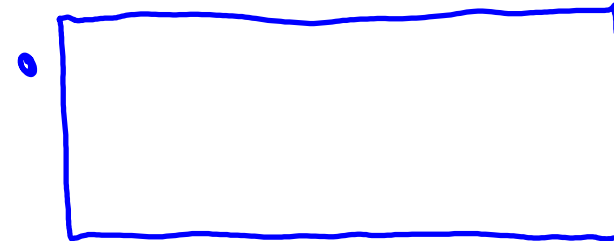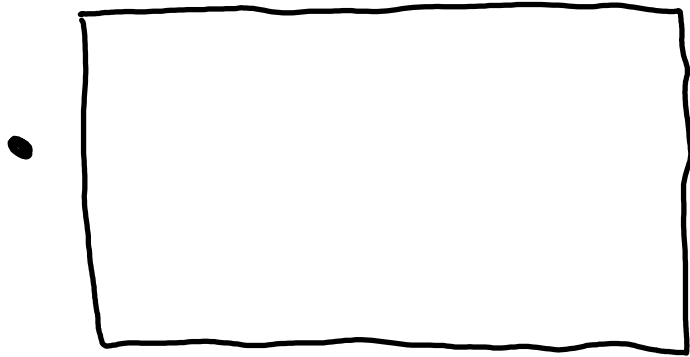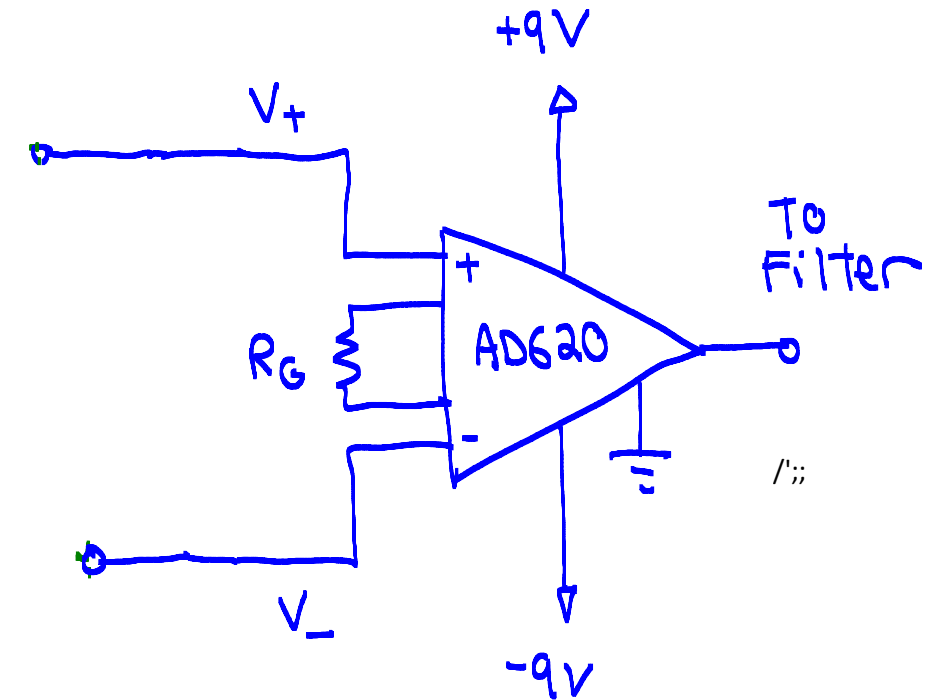


Ex:



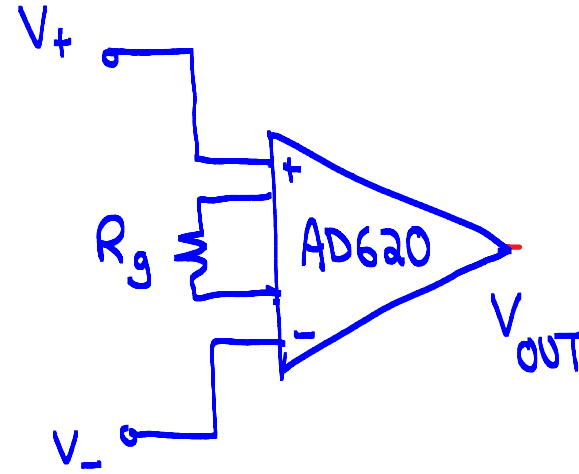
## B. Filter

- Mismatch in skin-electrode contact potential creates an input DC offset voltage



- At DC

Ex:

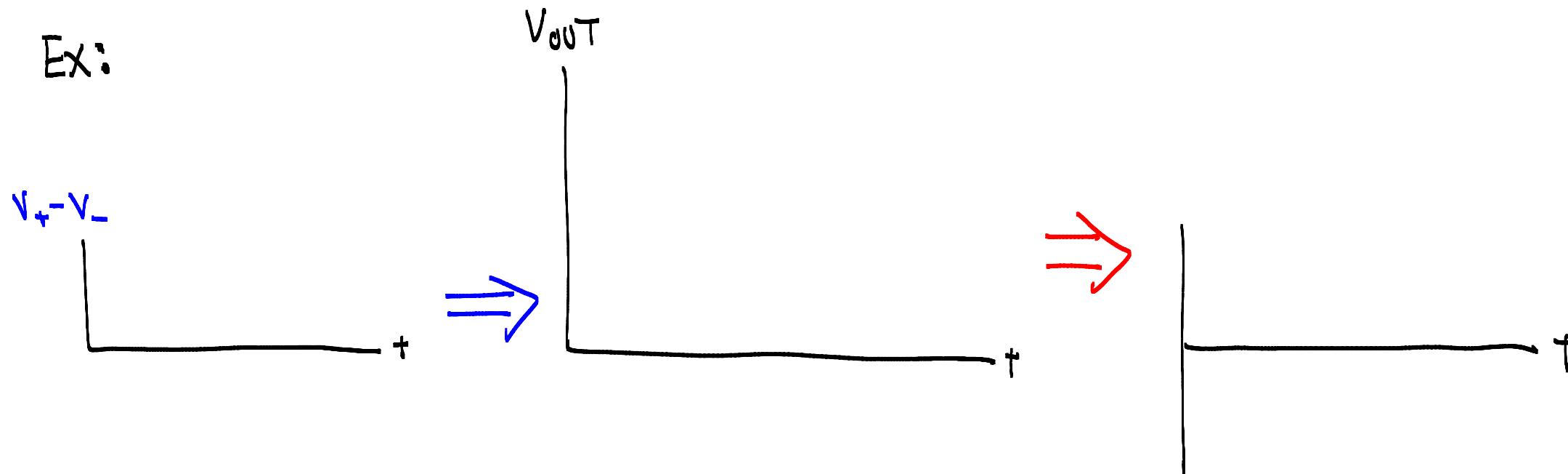


- At high freq,




- HPF Frequency Response  
Straightforward to show that:

$$\frac{V_{OUT}}{V_{IN}} =$$

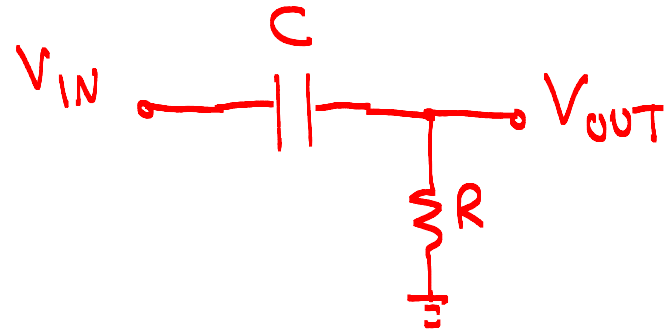


NOTE:

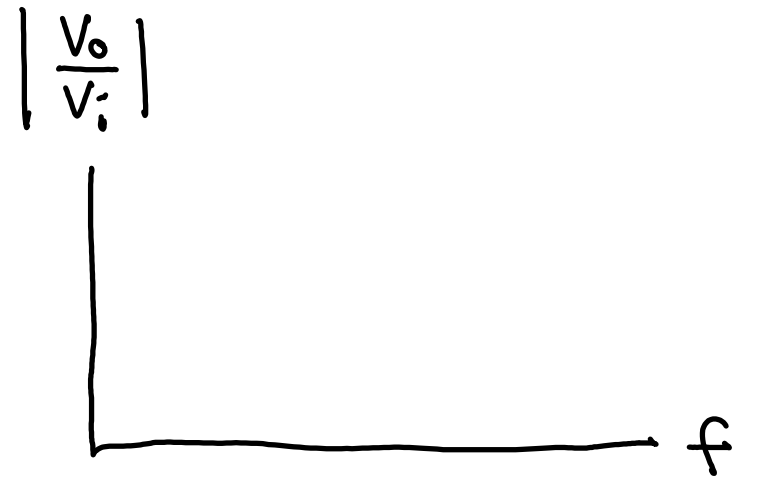

Can easily show that



$$\left| \frac{V_{OUT}}{V_{IN}} \right| =$$

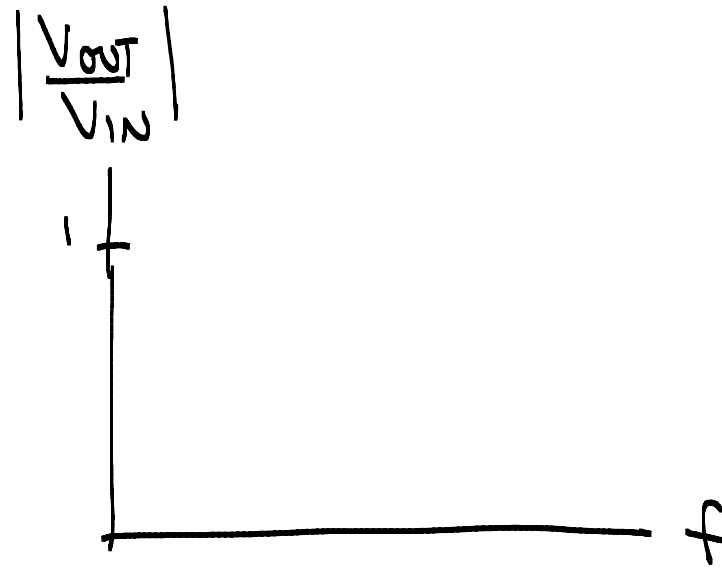

- After the HPF, the ECG signal is pretty small

①

②

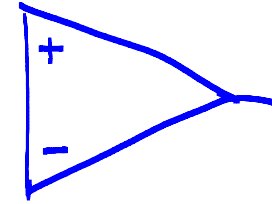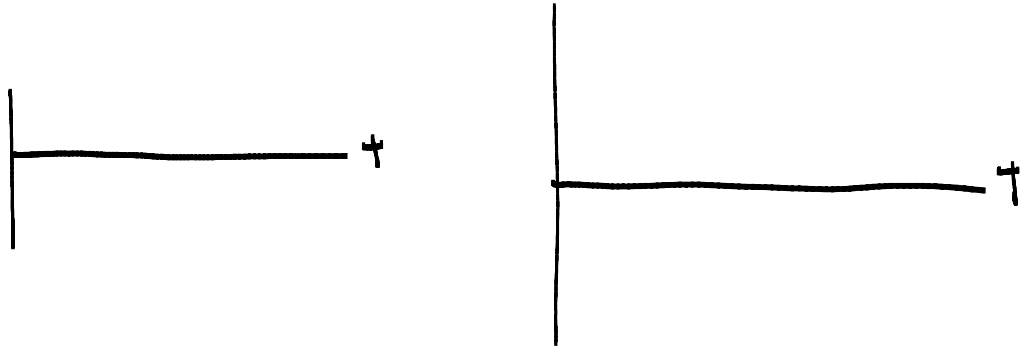

How to derive  $V_{out}/V_{in}$ ?


Recall the op Amp Golden Rules:

①

②



NOTE: These golden rules  
an ideal op amp used  
with negative feedback!

Ex:

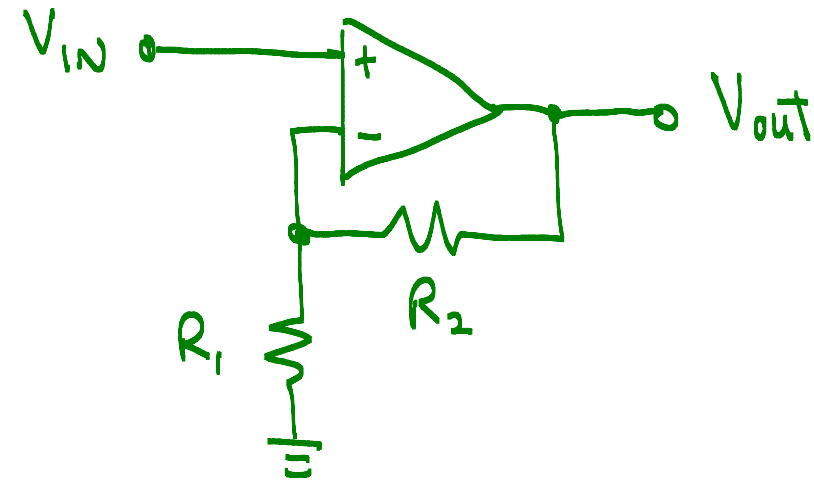

Adding a capacitor

(6.10)

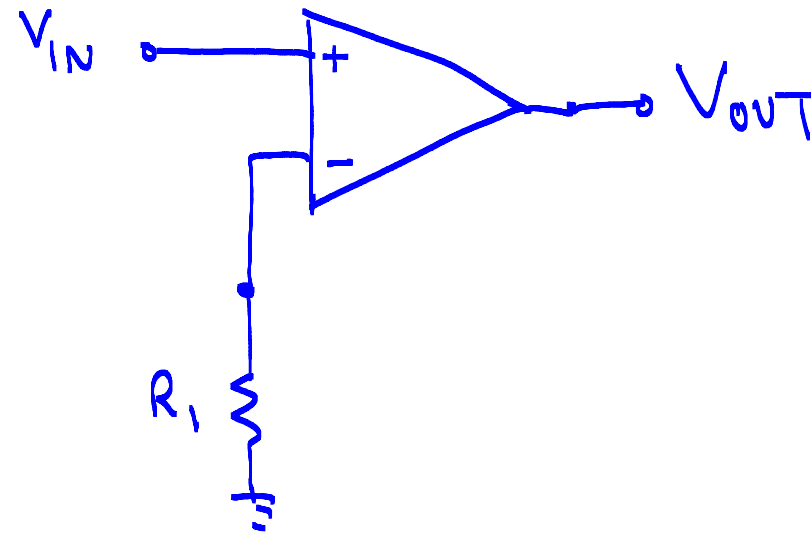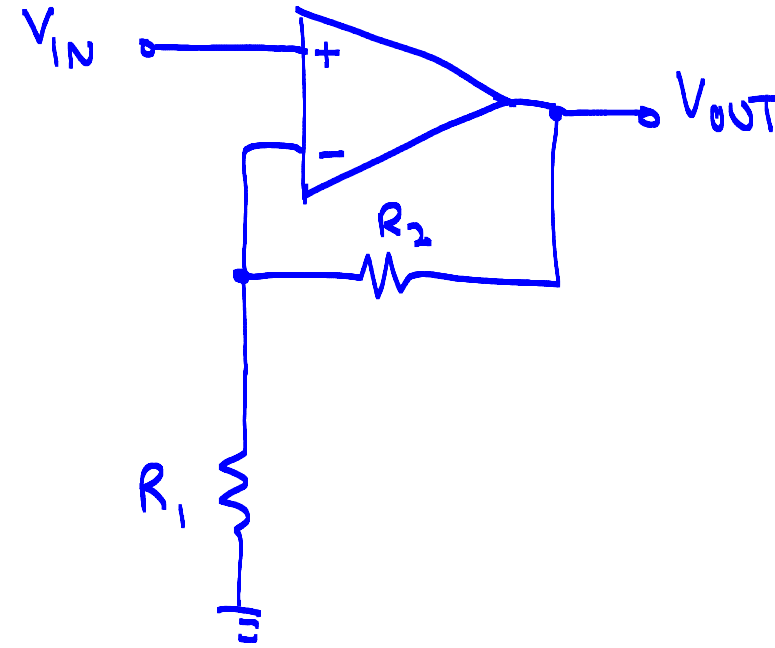




### 3. MiniLab

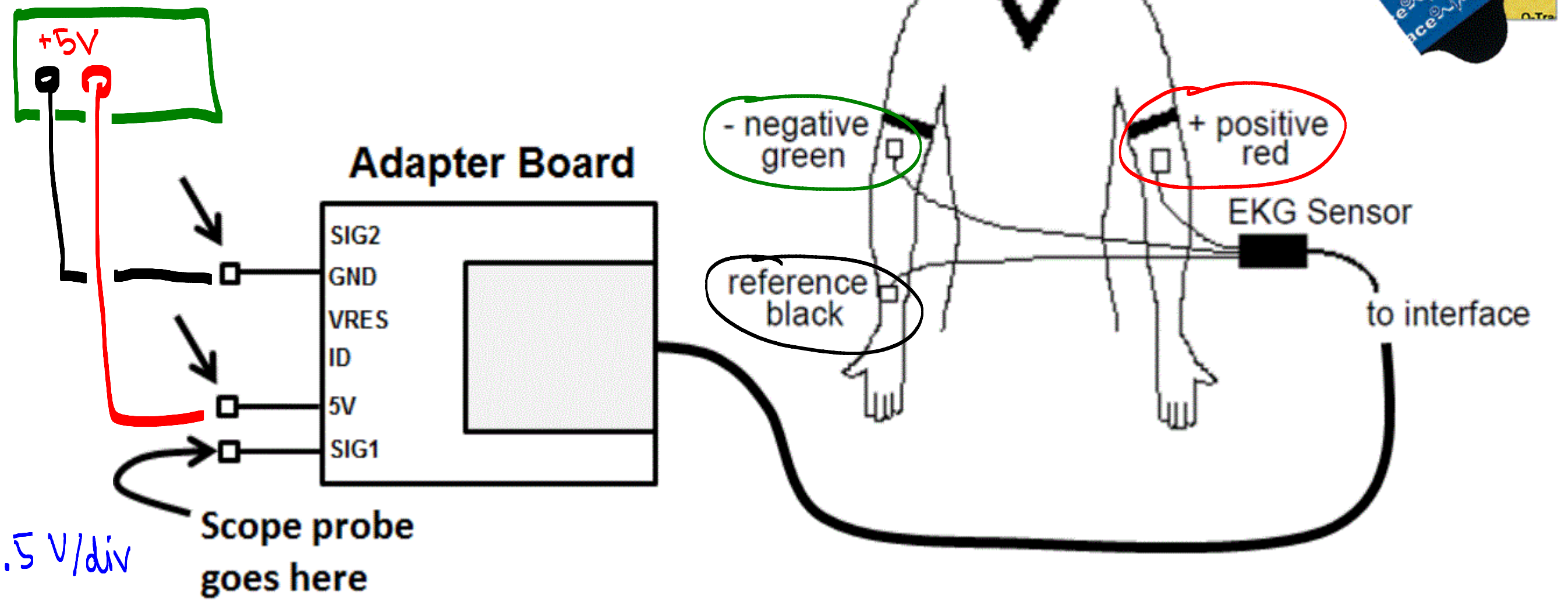(6.11)

GOAL: Use a commercial ECG sensor to detect P&RST waveform!



Scope:  
Vertical = 0.5 V/div  
Horizontal = 200 ms/div